



1. An enhancement-load inverter having  $(W/L)_1 = 3$  and  $(W/L)_2 = 1/3$  is fabricated with a technology for which the minimum practical transistor dimension (length or width) is  $5 \mu\text{m}$ . Find the area occupied by this inverter and the value of its  $K_R$ . if  $K_R$  is to be quadrupled, find the ration  $(W/L)$  for each device so that the silicon area required by the inverter is the minimum possible.
  
2. Consider an enhancement-load inverter having  $V_{t0} = 1 \text{ V}$ ,  $(W/L)_1 = 3$ ,  $(W/L)_2 = 1/3$ ,  $\mu_n C_{OX} = 20 \mu\text{A}/\text{V}^2$ ,  $2\Phi_f = 0.6 \text{ V}$ ,  $\gamma = 0.5 \text{ V}^{1/2}$  and  $V_{DD} = 5 \text{ V}$ .
  - a) Neglecting the body effect, find the critical points of the voltage transfer characteristic, and hence find the noise margins.
  - b) Taking the body effect into account, find the modified values of  $V_{OH}$  and  $NM_H$ .
  - c) Find the inverter current in both states, and hence find the average static power dissipation.
  
3. For the enhancement-load inverter of Fig. 1, find  $K_R$  that result in  $V_{OL} = 0.1 \text{ V}$   
Let  $V_{t1} = V_{t2} = 1 \text{ V}$  and  $V_{DD} = 5 \text{ V}$ , and neglect the body effect.

 


Fig.1

4. Use the approximate expressions (1) and (2) to determine  $t_p$  and DP for the inverter of problem (2). Let  $C = 0.1\mu\text{F}$

EMOS

Expression (1) :  $t_p = 1/2 t_{PLH} = 0.4C/\{K_2(V_{DD}-V_t)\}$

Expression (2) :  $DP = 0.2CV_{DD}(V_{DD}-V_t)$