
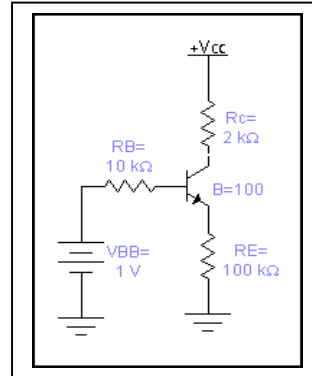


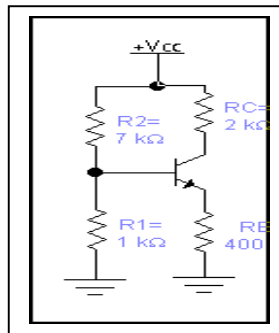


1-Find the location of the Q-point of the amplifier shown in figure,when an npn transistor is used.Assume that  $V_{CC}=10V$ ,  $V_{BB}=1V$ ,  $R_B=10k\Omega$ ,  $R_C=2k\Omega$ ,  $R_E=100\Omega$ ,  $\beta=100$ ,  $V_{BE}=0.7V$ .What is the new location if  $R_B=1k\Omega$ .



2-Find the maximum peak-to-peak swing of  $i_c$  in the circuit shown in figure. Assume that  $R_1=1k\Omega$ ,  $R_2=7k\Omega$ ,  $V_{CC}=24V$ ,  $R_C=2k\Omega$ ,  $R_E=400\Omega$ , and  $\beta=100$ .Draw the dc load line.



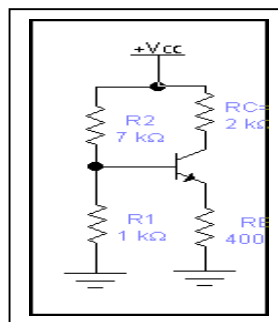3-With the circuit shown in figure,find the values of  $R_1, R_2$  that yield the maximum possible peak-to-peak swing of  $i_c$ . Draw the dc load line.



4-For the amplifier of the shown figure,calculate the following:

- a-Power supplied by the battery.
- b-Power dissipated by  $R_1, R_2, R_E$  and  $R_C$ .
- c-Power dissipated by the collector junction.

