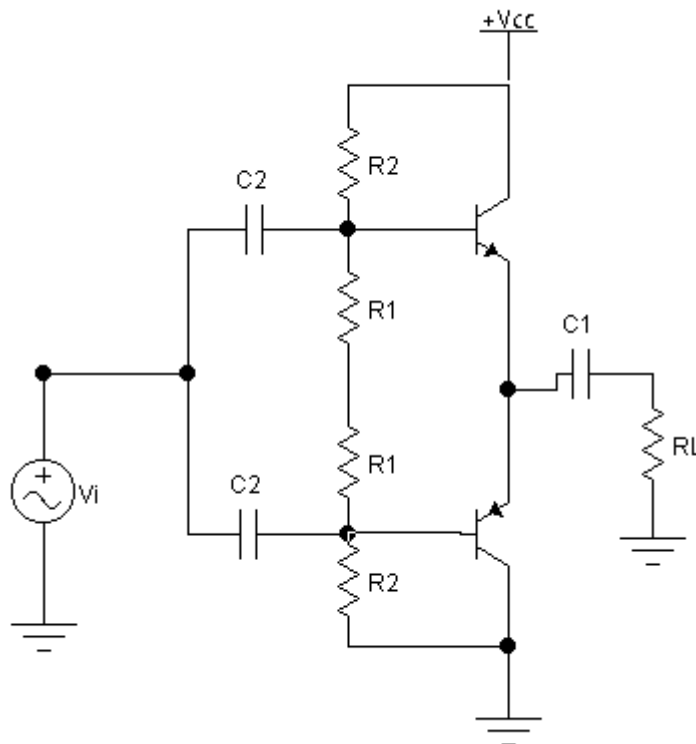




- 1- Design a complementary symmetry class **B** power amplifier to drive a $12\ \Omega$ load. Refer to the circuit below. Use $V_{CC} = 18\text{ V}$, $V_{BE} = 0.7\text{ V}$ and $\beta = 60$. Calculate the total power dissipated in the load, the input resistance, and the power rating of the transistor. Select values of R_1 and R_2 and C_1 for a 20 Hz to 20 kHz frequency response and for a current gain of $A_i = 20$.



- 2- Design a complementary symmetry class **B** power amplifier to drive an $8\ \Omega$ load. Using $V_{CC} = 12\text{ V}$, $V_{BE} = \pm 0.7\text{ V}$, $\beta = 60$ and a frequency range of 100 Hz to 15 kHz. Use the circuit of the previous problem with a required current gain of $A_i = 20$. frequency response and for a current gain of $A_i = 20$.
- Find the quiescent voltages and currents.
 - Find the maximum power delivered to the load.
 - Select values for R_1, R_2 , and C_1 .
 - Determine R_{in} .

Use the above circuit diagram.