

CMOS Digital Integrated Circuits




Lec 13

Semiconductor Memories



Semiconductor Memory Types

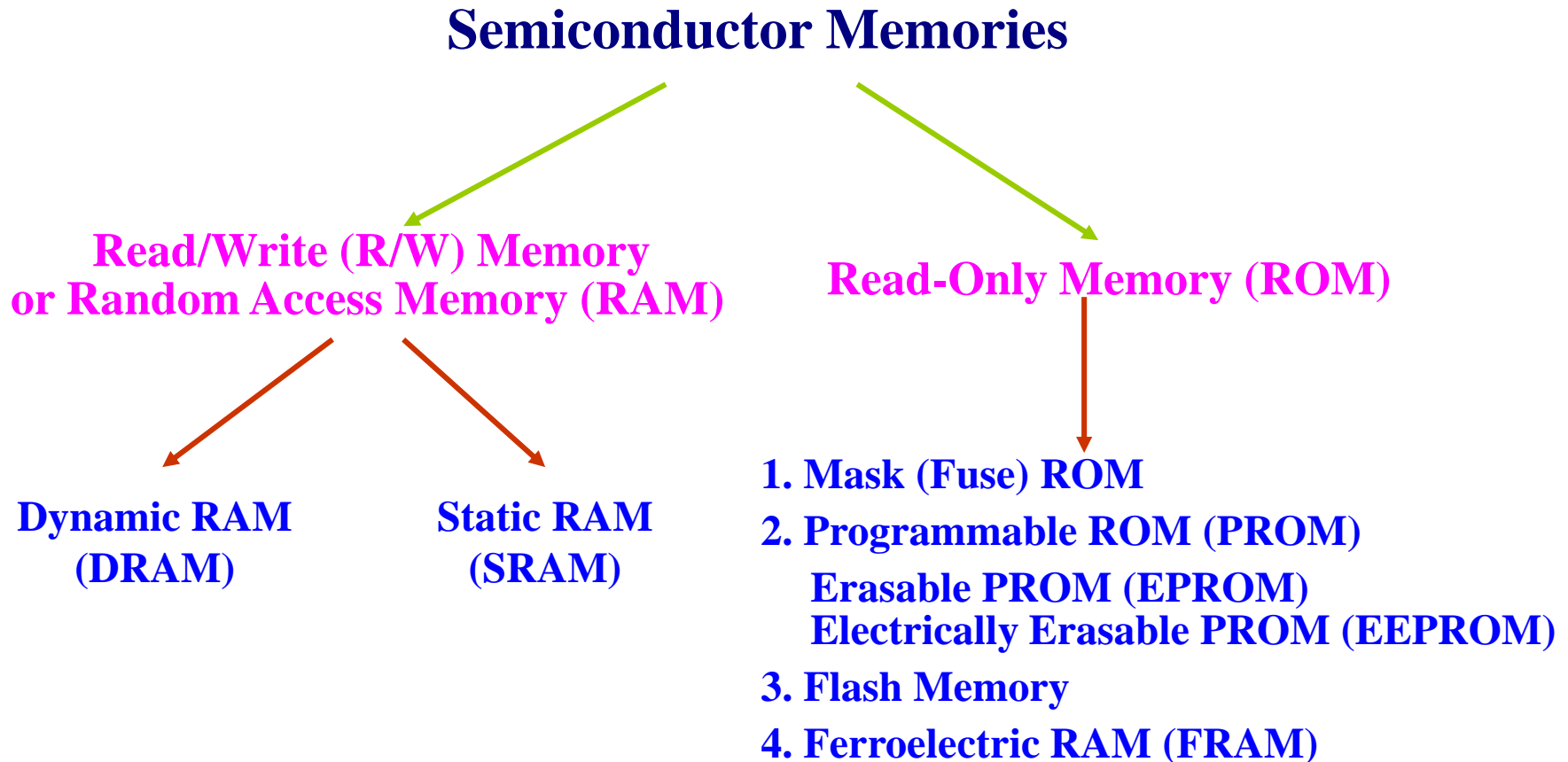

Semiconductor Memory Types (Cont.)

■ Design Issues

- **Area Efficiency of Memory Array:** # of stored data bits per unit area
- **Memory Access Time:** the time required to store and/or retrieve a particular data bit.
- **Static and Dynamic Power Consumption**

■ RAM: the stored data is volatile

• *DRAM*

- » A capacitor to store data, and a transistor to access the capacitor
- » **Need refresh operation**
- » **Low cost**, and **high density** \Rightarrow it is used for main memory

• *SRAM*

- » Consists of a latch
- » **Don't need the refresh operation**
- » **High speed** and **low power consumption** \Rightarrow it is mainly used for cache memory and memory in hand-held devices



Semiconductor Memory Types (Cont.)

■ ROM: 1, nonvolatile memories


2, only can access data, cannot to modify data

3, lower cost: used for permanent memory in printers, fax, and game machines, and ID cards

- **Mask ROM:** data are written **during** chip fabrication by a **photo mask**
- **PROM:** data are written electrically **after** the chip is fabricated.
 - » **Fuse ROM:** data **cannot** be erased and modified.
 - » **EPROM and EEPROM:** data **can be rewritten**, but the number of subsequent re-write operations is limited to 10^4 - 10^5 .
 - **EPROM uses ultraviolet rays** which can penetrate through the crystal glass on package to erase whole data simultaneously.
 - **EEPROM uses high electrical voltage** to erase data in 8 bit units.
- **Flash Memory:** similar to EEPROM
- **FRAM:** utilizes the **hysteresis** characteristics of a capacitor to overcome the slow written operation of EEPROMs.




Random-Access Memory Array Organization

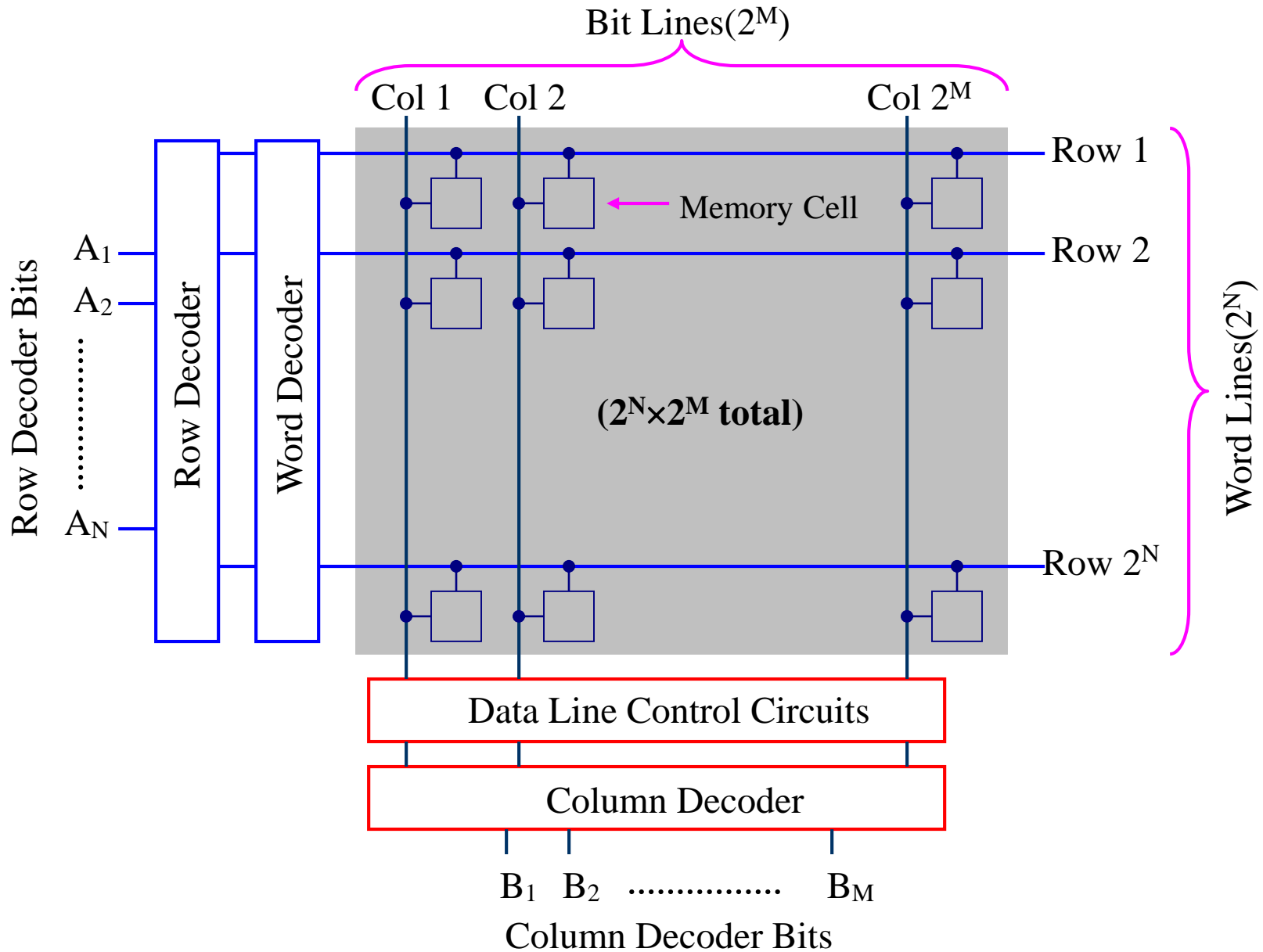

Nonvolatile Memory

4Bit × 4Bit NOR-based ROM Array

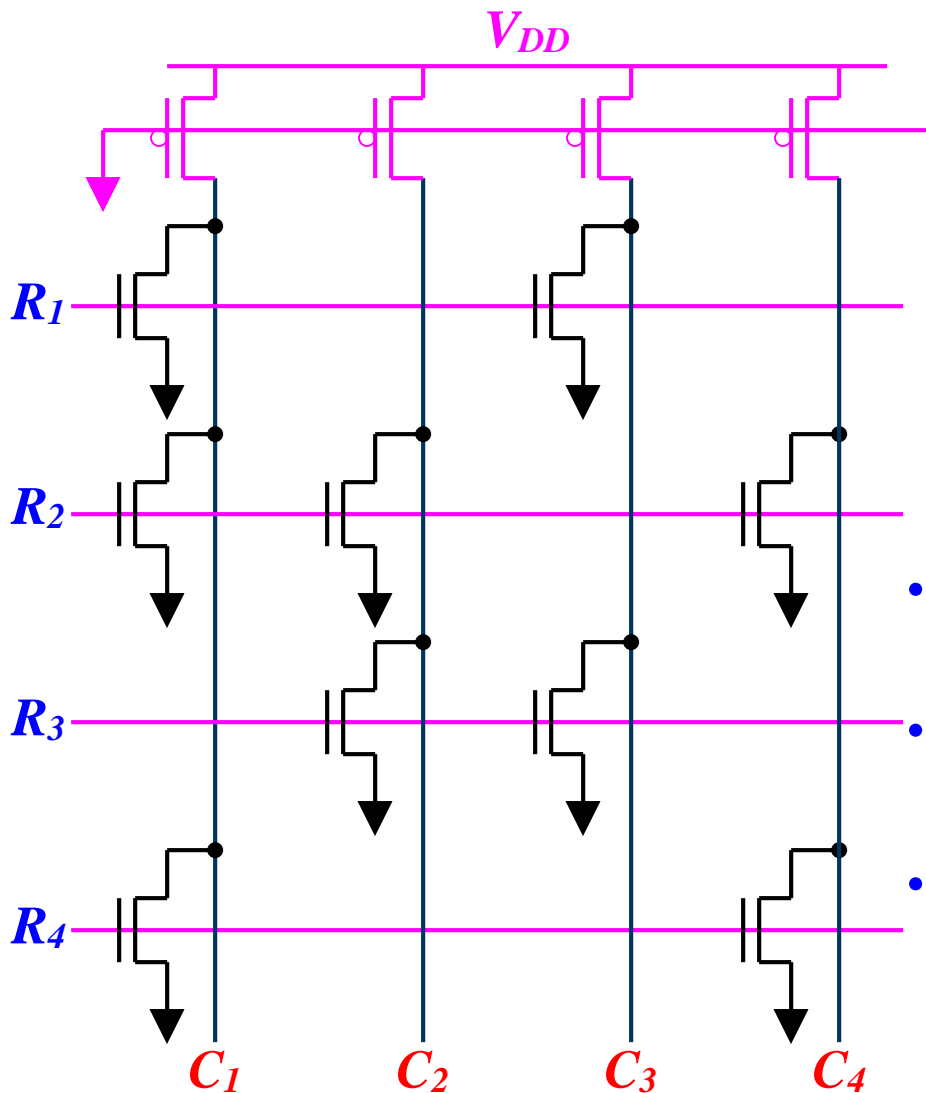


R_1	R_2	R_3	R_4	C_1	C_2	C_3	C_4
1	0	0	0	0	1	0	1
0	1	0	0	0	0	1	1
0	0	1	0	1	0	0	1
0	0	0	1	0	1	1	0

- One word line " R_i " is activated by raising its voltage to V_{DD}
- Logic "1" is stored: Absent transistor
Logic "0" is stored: Present transistor
- To reduce static power consumption, the pMOS can be driven by a periodic pre-charge signal.



 Layout of Contact-Mask Programmable NOR ROM




- **“0” bit:** drain is connected to metal line via a metal-to-diffusion contact
- **“1” bit:** omission the connect between drain and metal line.
- **To save silicon area:** the transistors on every two adjacent rows share a common ground line, also are routed in n-type diffusion



Layout of Contact-Mask Programmable

4Bit × 4Bit NOR ROM

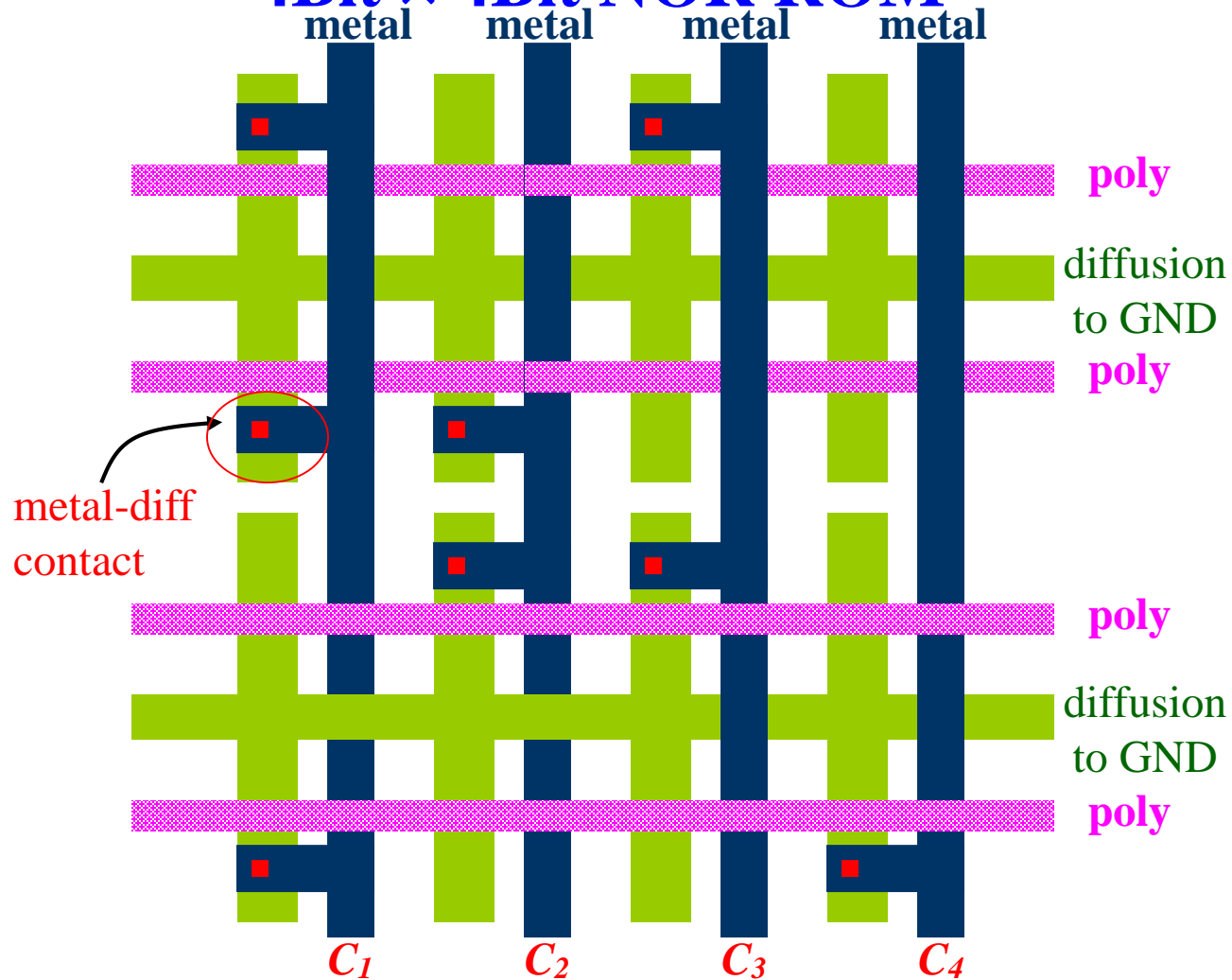


- In reality, the metal lines are **laid out directly on top** of diffusion columns to reduce the horizontal dimension.



Implant-Mask Programmable NOR ROM Array

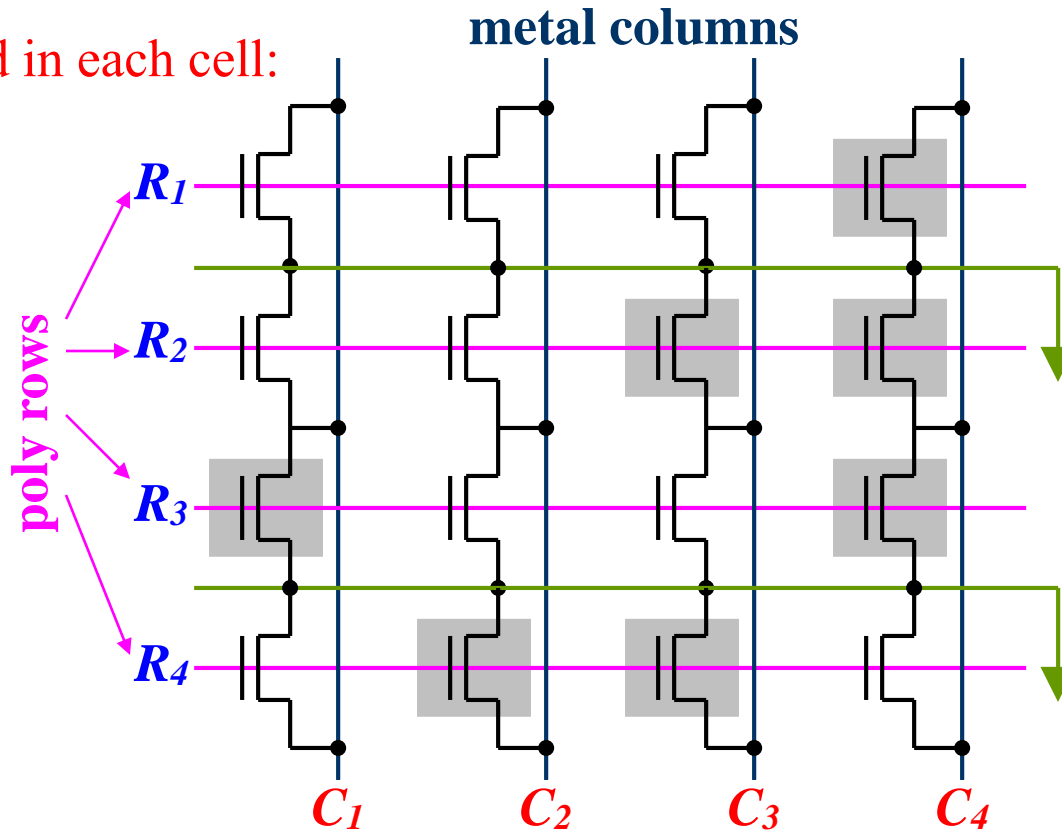Logic “0” is stored in each cell:
Present transistor




- V_{T0} is implanted to activate 1 bit:
Let $V_{T0} > V_{DD} \Rightarrow$ permanently **turn off** transistor
 \Rightarrow disconnect the contact



Layout of Implant-Mask Programmable


4Bit × 4Bit NOR ROM

 

- Each diffusion-to-metal contact is **shared by two adjacent transistors**
⇒ need smaller area than contact-mask ROM layout



4Bit × 4Bit NAND-based ROM Array

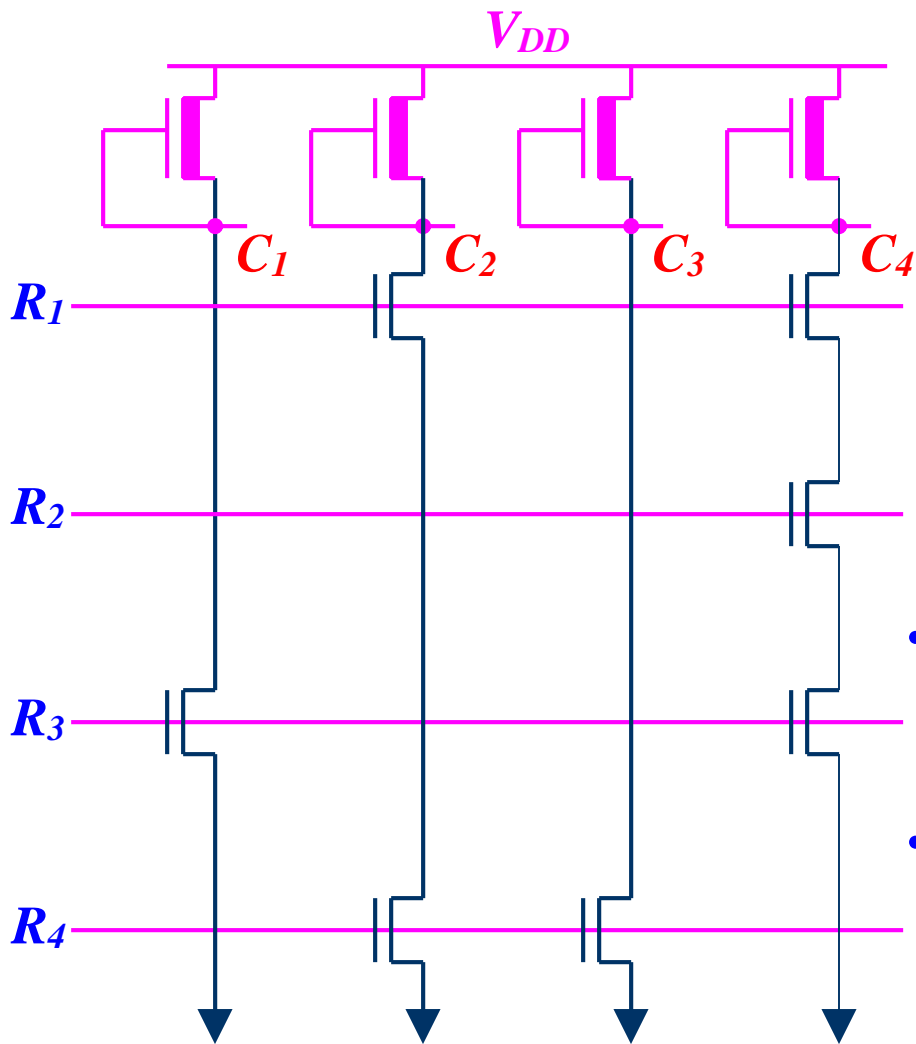


R_1	R_2	R_3	R_4	C_1	C_2	C_3	C_4
0	1	1	1	0	1	0	1
1	0	1	1	0	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	0

- All word lines are kept at logic “1” level, except the selected line pulled down by “0” level.
- Logic “0” is stored: Absent transistor
Logic “1” is stored: Present transistor



 Layout of Implant-Mask Programmable 4Bit × 4Bit NAND ROM




- No contact in the array \Rightarrow **More compact than NOR ROM array**
- Series-connected nMOS transistors exist in each column
 \Rightarrow **The access time is slower than NOR ROM**



Design of Row and Column Decoders

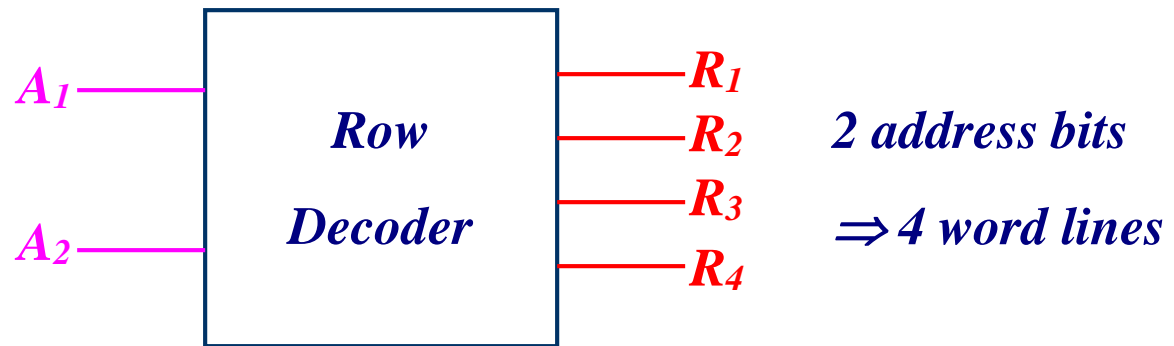- Row and Column Decoders: To select **a particular memory location** in the array.




A_1	A_2	R_1	R_2	R_3	R_4
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



NOR-based Row Decoder Circuit

2 Address Bits and 4 Word Lines

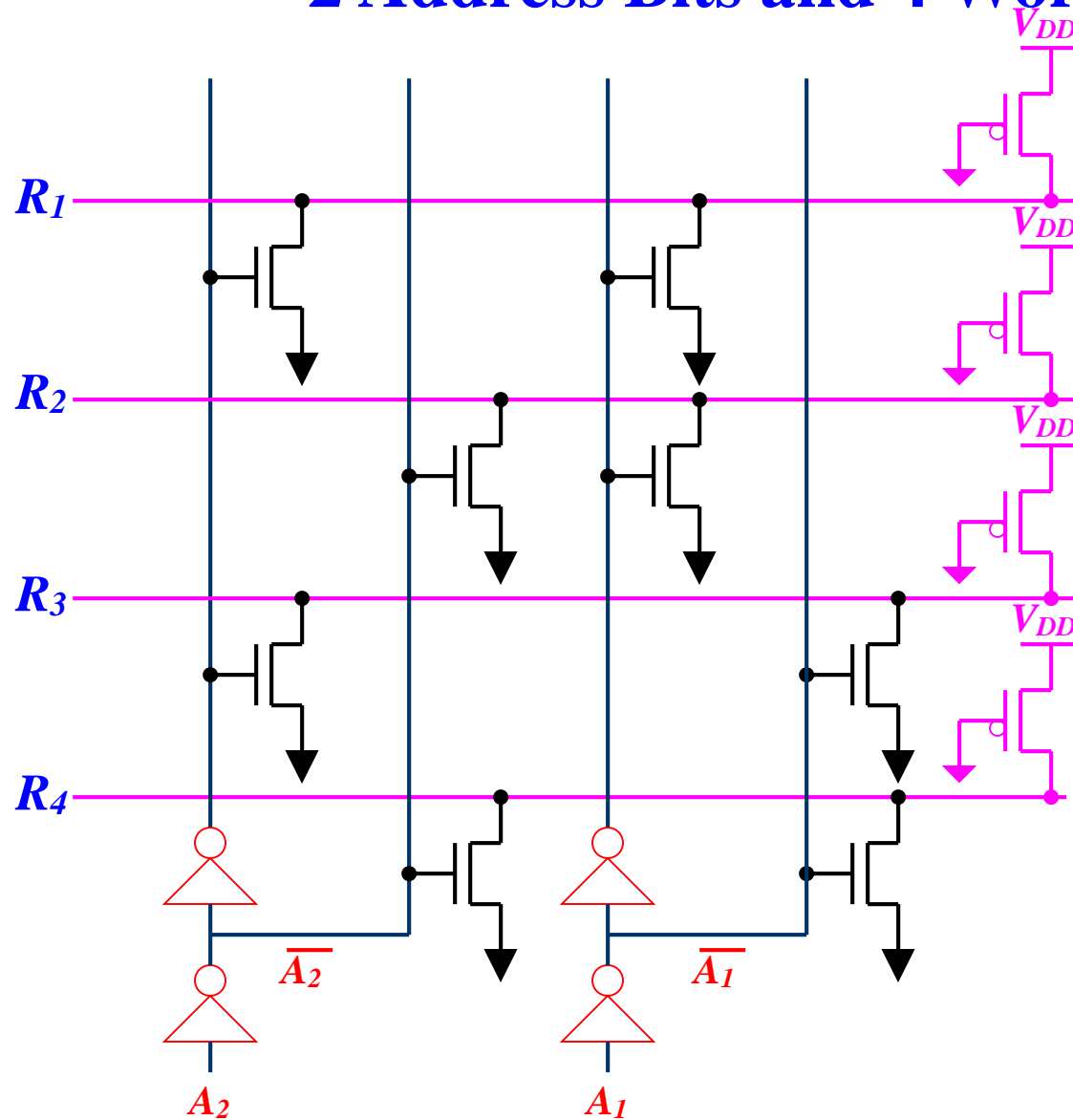


A_1	A_2	R_1	R_2	R_3	R_4
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1




Implementation of Row Decoder and ROM

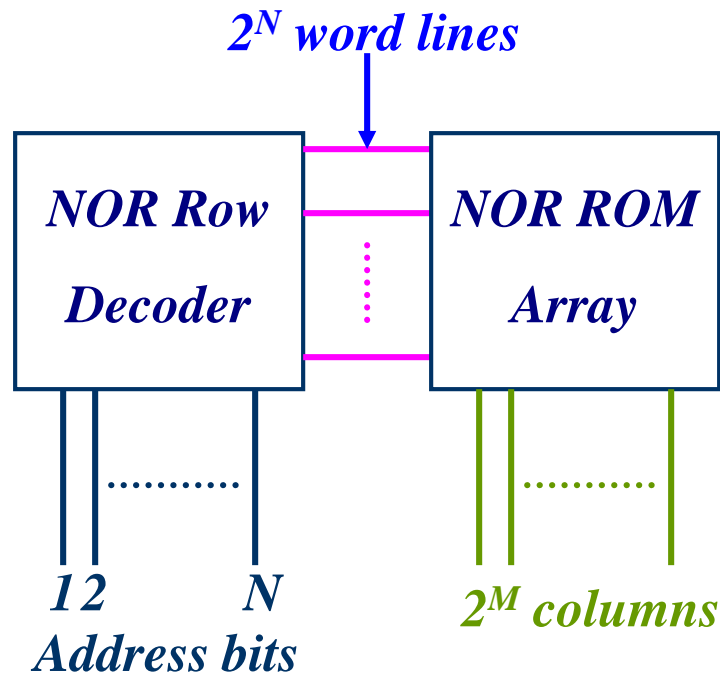- Can be implemented as *two adjacent* NOR planes



Implementation of Row Decoder and ROM (Cont.)

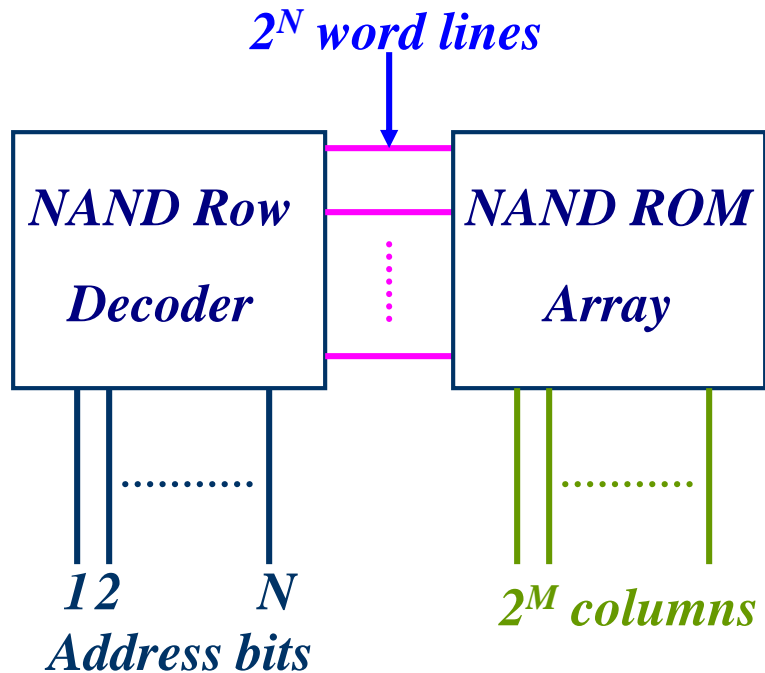- Can also be implemented as *two adjacent* NAND planes



A_1	A_2	R_1	R_2	R_3	R_4
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0


4×4 NAND ROM Array



Column Decoder (1)

NOR Address Decoder and Pass Transistors

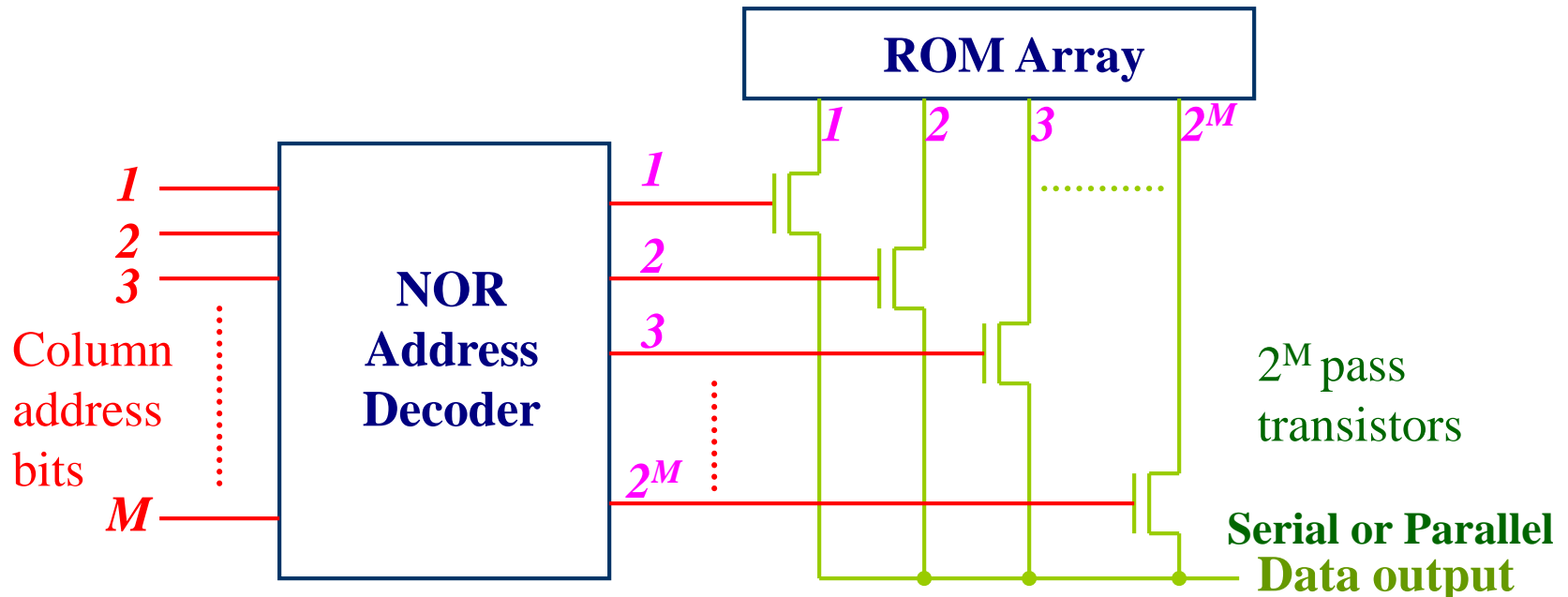
- **Column Decoder:** To select one out of 2^M bits lines of the ROM array, and to route the data of the selected bit line to the data output
- **NOR-based column address decoder and pass transistors:**
 - » Only one nMOS pass transistor is turned on at a time
 - » # of transistors required: $2^M(M+1)$ (2^M pass transistors, $M2^M$ decoder)



Column Decoder (2)


Binary Tree Decoder

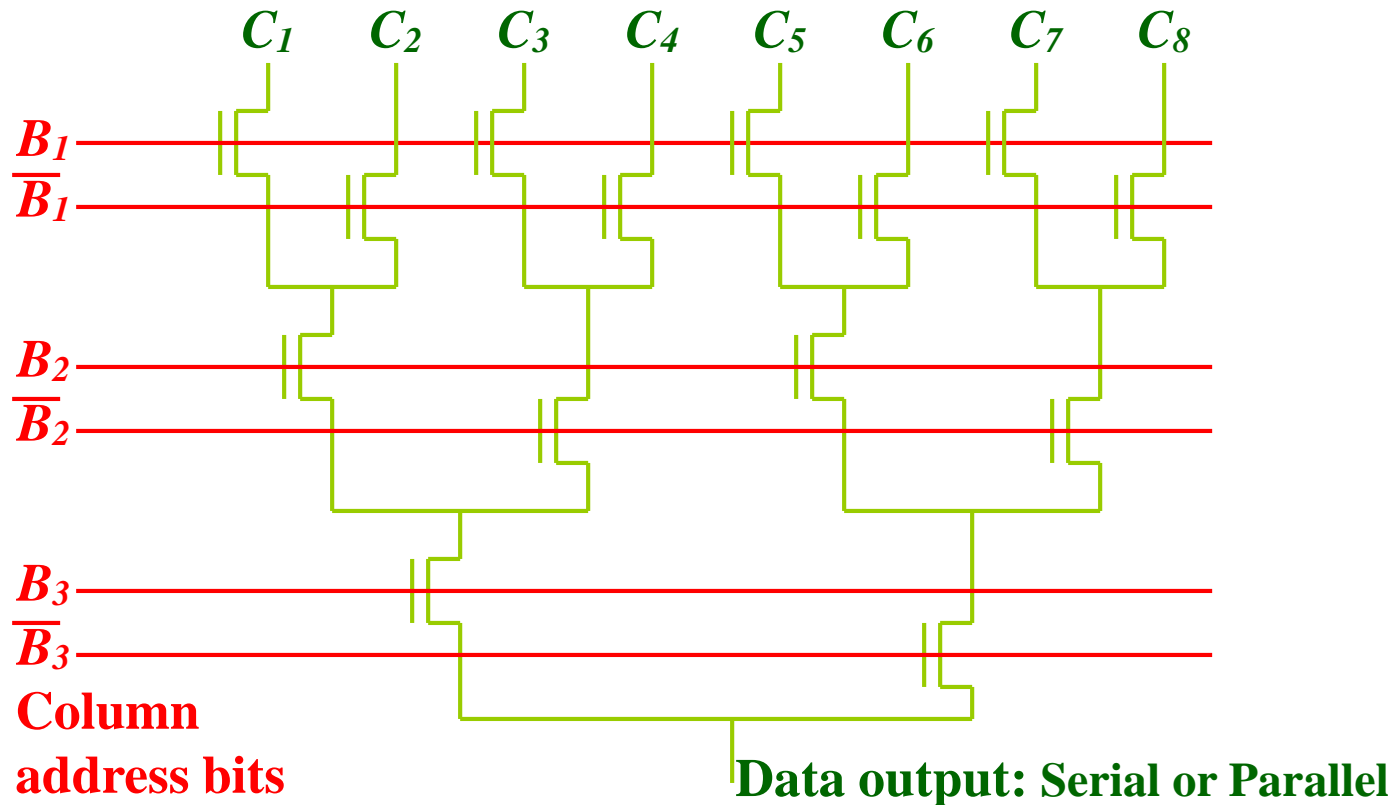- **Binary Tree Decoder:** A binary selection tree with consecutive stages
 - » The pass transistor network is used to select one out of every two bit lines at each stages. The NOR address decoder is not needed.
 - » **Advantage:** Reduce the transistor count ($2^{M+1}-2+2M$)
 - » **Disadvantage:** Large number of series connected nMOS pass transistors \Rightarrow long data access time



An Example of NOR ROM Array

- Consider the design of a 32-kbit **NOR ROM** array and the design issues related to *access time analysis*
 - » # of total bits: 15 ($2^{15}=32,768$)
 - » 7 row address bits ($2^7 = 128$ rows)
 - » 8 column address bits ($2^8 = 256$ columns)
 - » Layout: implant-mask
 - » $W = 2 \mu\text{m}$, $L = 1.5 \mu\text{m}$
 - » $\mu_n C_{ox} = 20 \mu\text{A}/\text{V}^2$
 - » $C_{ox} = 3.47 \mu\text{F}/\text{cm}^2$
 - » $R_{sheet-poly} = 20 \Omega/\text{square}$

 


- R_{row} , and C_{row} / unit memory cell
 - » $C_{row} = C_{ox} \cdot W \cdot L = 10.4 \text{ fF/bit}$
 - » $R_{row} = (\# \text{ of squares}) \times R_{sheet-poly} = 3 \times 20 = 60 \Omega$



An Example of NOR ROM Array (Cont.)

 - The poly word line can be modeled as a RC transmission line with up to 256 transistors




- The row access time t_{row} : delay associated with selecting and activating 1 of 128 word lines in ROM array. It can be approximated as

$$t_{row} \approx 0.38 \cdot R_T \cdot C_T = 15.53 \text{ ns}$$

$$R_T = \sum_{\text{all cols}} R_i = 15.36 \text{ k}\Omega$$
 
$$C_T = \sum_{\text{all cols}} C_i = 2.66 \text{ pF}$$




An Example of NOR ROM Array (Cont.)

- A **more accurate** RC delay value: *Elmore time constant* for RC ladder circuits


$$t_{row} = \sum_{k=1}^{256} R_{jk} C_k = 20.52 \text{ ns}$$

 - The **column access time** t_{column} : worst case delay τ_{PHL} associated with discharging the precharged bit line when a row is activated.



An Example of NOR ROM Array (Cont.)

 - $C_{column} = 128 \times (C_{gd,driver} + C_{db,driver}) \approx 1.5\text{pF}$
where $C_{gd,driver} + C_{db,driver} = 0.0118\text{ pF/word line}$
- Since only one word line is activated at a time, the above circuit can be reduced to **an inverter circuit**



Remark: τ_{PLH} is not considered because the bit line is precharged high before each row access operation


$$t_{column} = \tau_{PHL} = \frac{C_{load}}{k_n (V_{OH} - V_{T0,n})} \left[\frac{2V_{T0,n}}{V_{OH} - V_{T0,n}} + \ln \left(\frac{4(V_{OH} - V_{T0,n})}{V_{OH} + V_{OL}} - 1 \right) \right] = 18\text{ns}$$

$$t_{access} = t_{row} + t_{column} = 20.52 + 18 = 38.52\text{ ns}$$




Static Random Access Memory (SRAM)

 - **SRAM:** The stored data can be retained indefinitely, without any need for a periodic refresh operation.




1-bit SRAM cell

 



- **Complementary Column** arrangement is to achieve a more reliable SRAM operation




Resistive-Load SRAM Cell

 

Full CMOS and Depletion-Load SRAM Cell

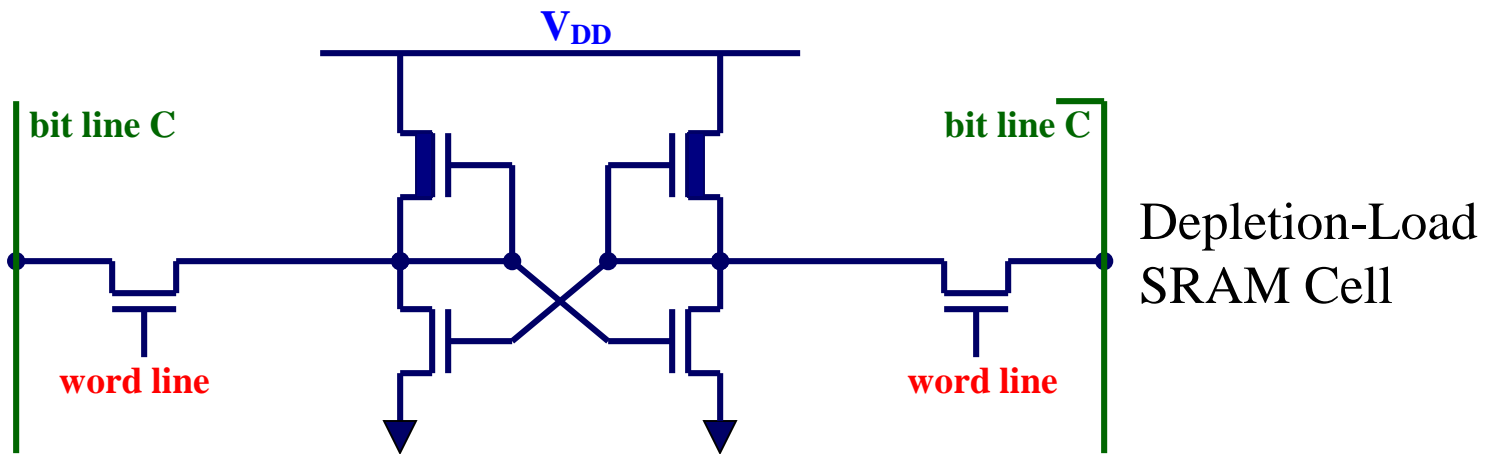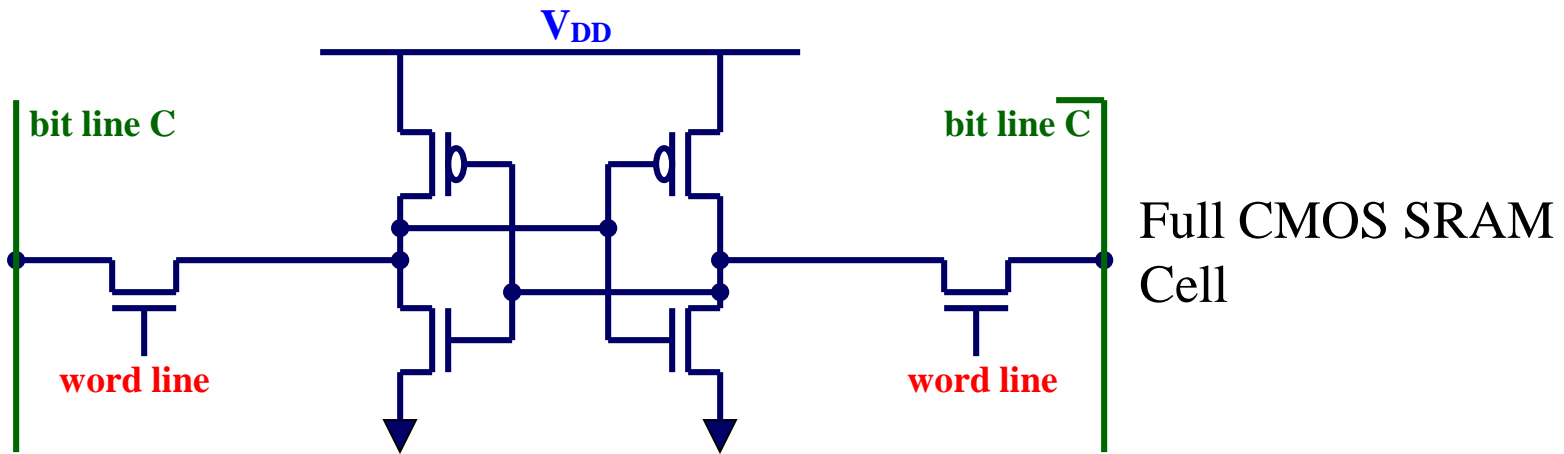

SRAM Operation Principles

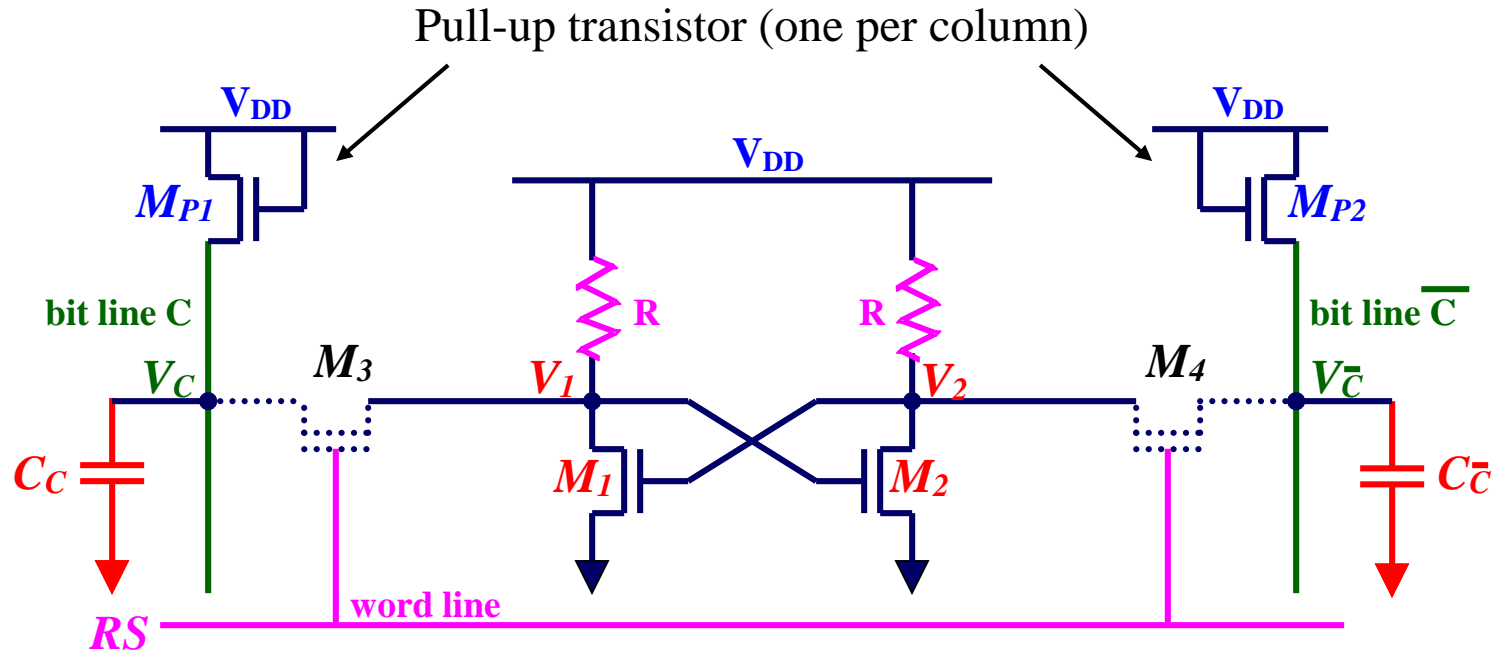


- **$RS=0$** : The word line is not selected. M_3 and M_4 are OFF
- One data-bit is held: The latch preserves one of its two stable states.
- **If $RS=0$ for all rows**: C_C and $C_{\bar{C}}$ are charged up to near V_{DD} by pulling up of M_{P1} and M_{P2} (both in saturation)

$$V_{\bar{C}} = V_C = V_{DD} - \left(V_{T0} + \gamma \sqrt{|2\phi_F| + V_C} - \sqrt{|2\phi_F|} \right)$$

- Ex: $V_C = V_{\bar{C}} = 3.5\text{V}$ for $V_{DD} = 5\text{V}$, $V_{T0} = 1\text{V}$, $|2\phi_F| = 0.6\text{V}$, $= 0.4\text{V}^{1/2}$



SRAM Operation Principles (Cont.)

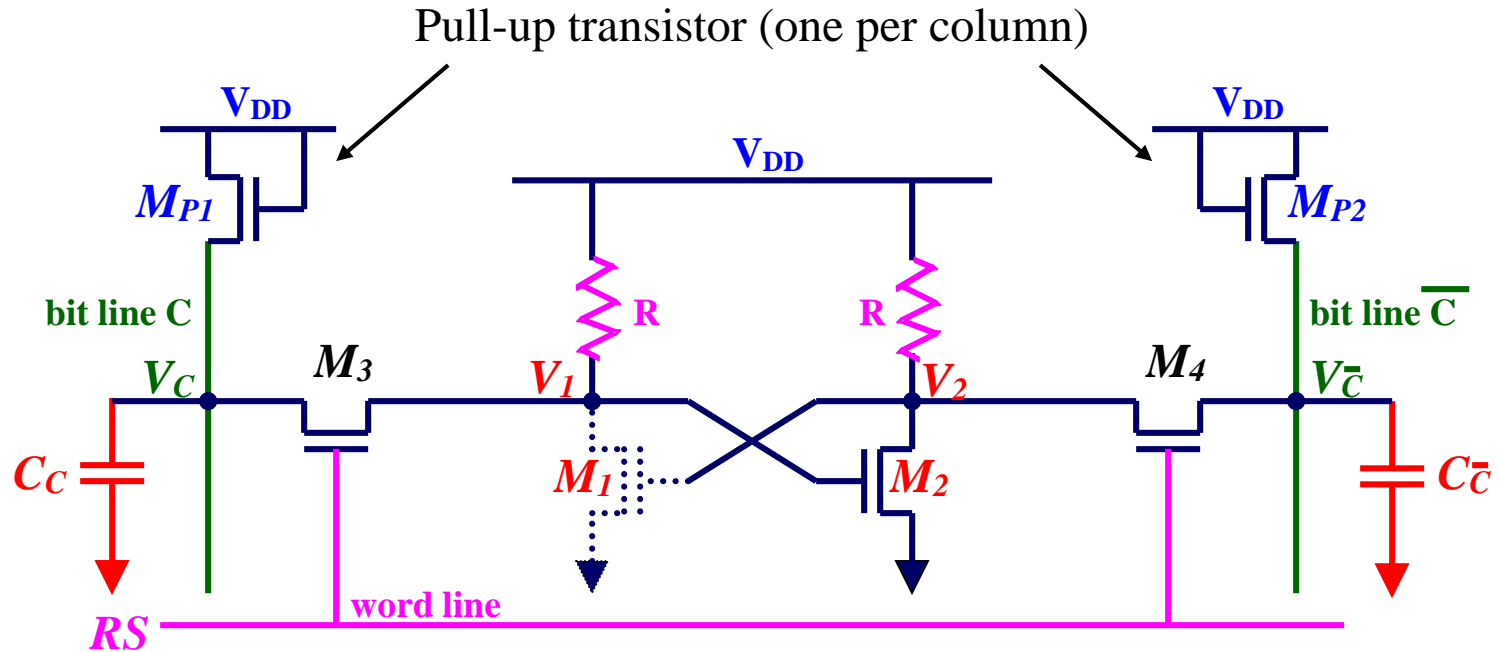


- $RS=1$: The word line is now selected. M_3 and M_4 are ON

Four Operations

1. **Write "1" Operation** ($V_1=V_{OL}$, $V_2=V_{OH}$ at $t=0^-$):

$V_{\bar{C}} \Rightarrow V_{OL}$ by the *data-write circuitry*. Therefore, $V_2 \Rightarrow V_{OL}$, then M_1 turns *off* $V_1 \Rightarrow V_{OH}$ and M_2 turns on pulling down $V_2 \Rightarrow V_{OL}$.


SRAM Operation Principles (Cont.)

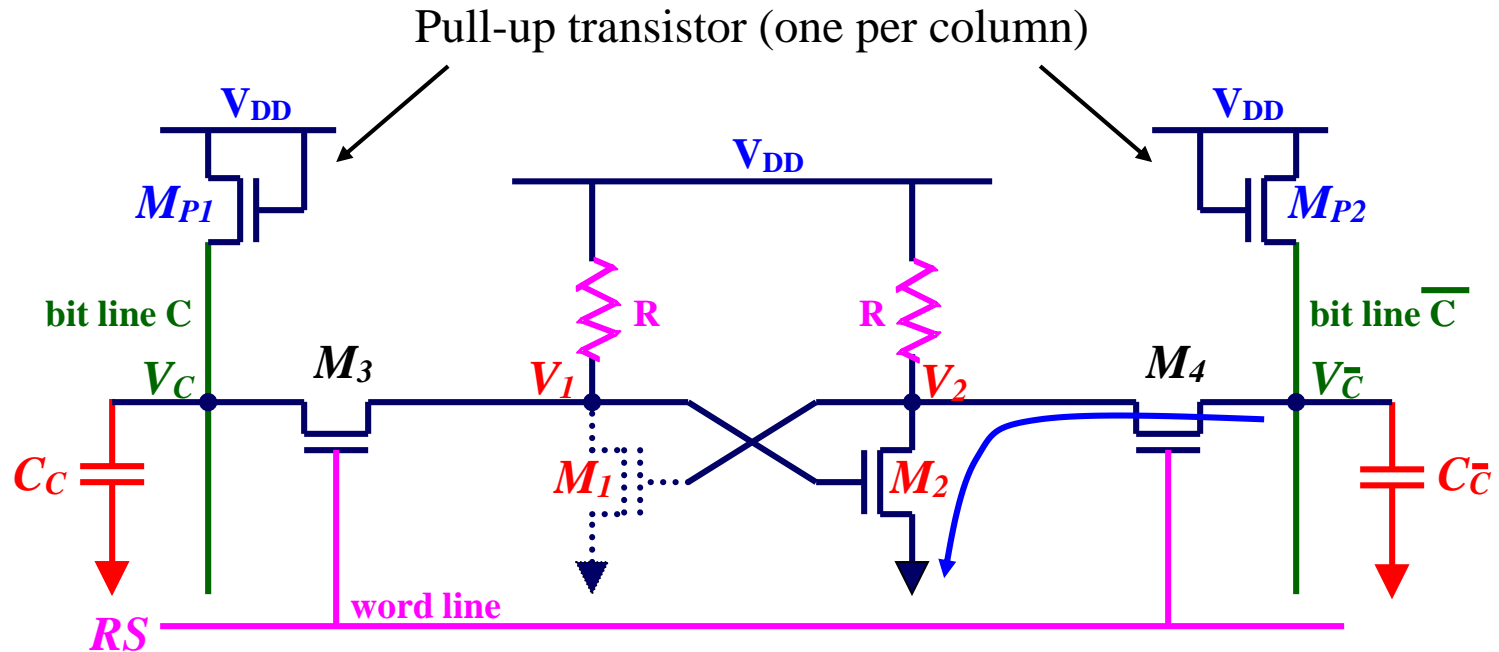

2. Read "1" Operation ($V_1 = V_{OH}$, $V_2 = V_{OL}$ at $t = 0^-$):

V_c retains pre-charge level, while $V_{\bar{c}} \Rightarrow V_{OL}$ by M_2 ON. *Data-read circuitry* detects small voltage difference $V_c - V_{\bar{c}} > 0$, and amplifies it as a "1" data output.

SRAM Operation Principles (Cont.)

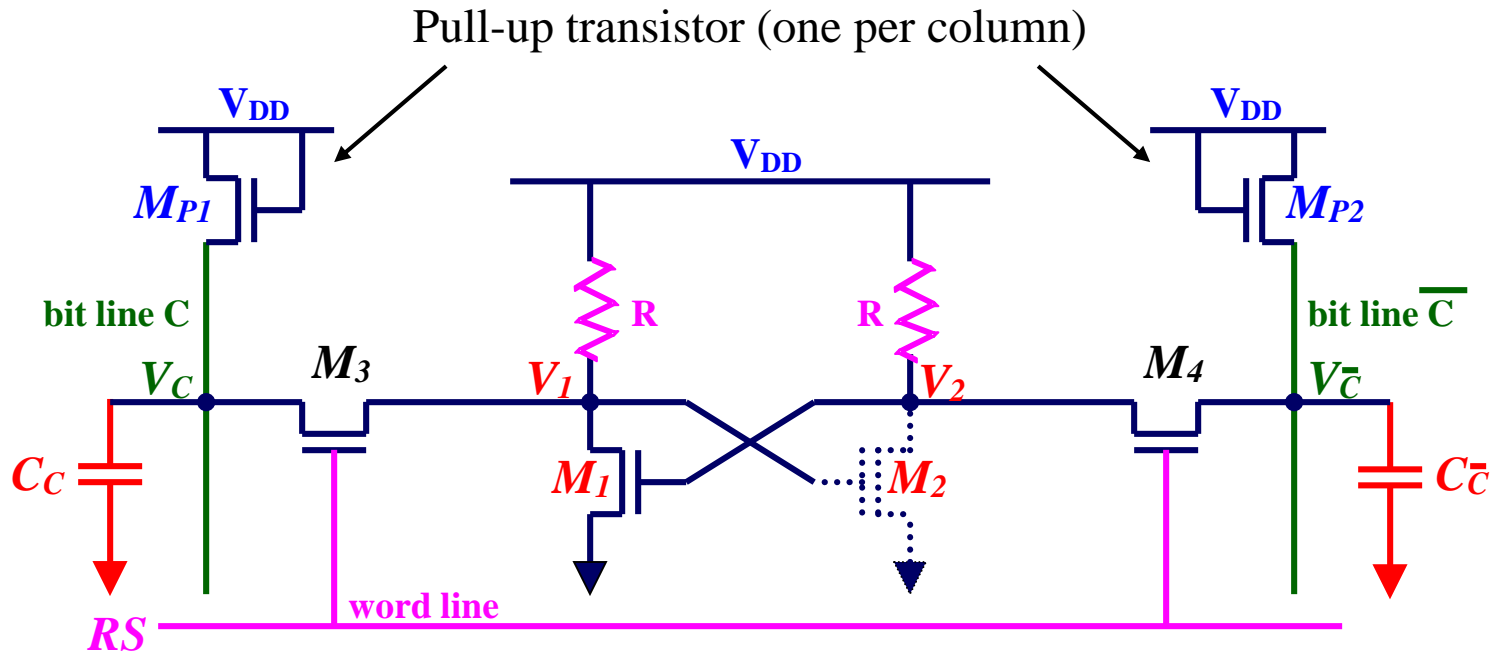


3. Write “0” Operation ($V_1 = V_{OH}$, $V_2 = V_{OL}$ at $t = 0^-$):

$V_C \Rightarrow V_{OL}$ by the *data-write circuitry*.

Since $V_1 \Rightarrow V_{OL}$, M_2 turns off, therefore $V_2 \Rightarrow V_{OH}$.

SRAM Operation Principles (Cont.)

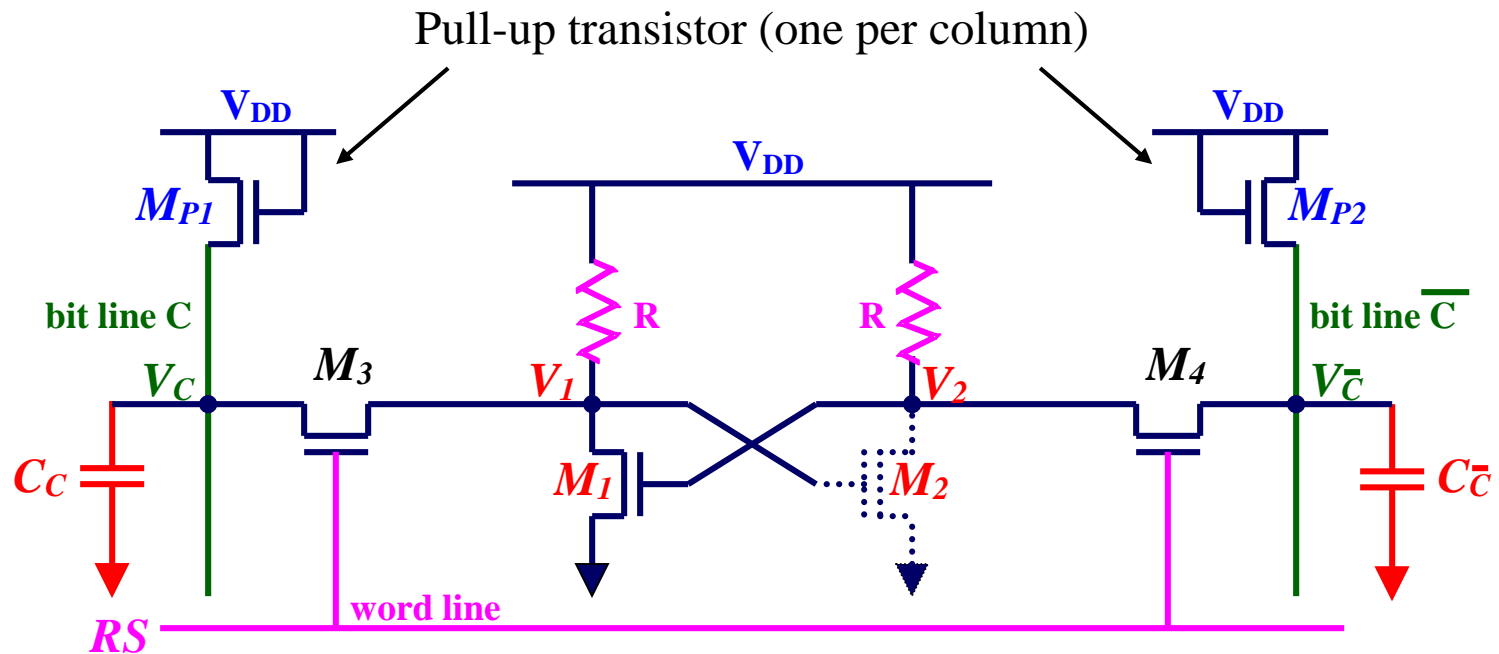

4. Read "0" Operation ($V_1=V_{OL}$, $V_2=V_{OH}$ at $t=0^-$):



$V_{\bar{C}}$ retains pre-charge level, while $V_C \Rightarrow V_{OL}$ by M_1 ON.

Data-read circuitry detects small voltage difference $V_C - V_{\bar{C}} < 0$, and amplifies it as a "0" data output.




SRAM Operation Principles (Cont.)

Pull-up transistor (one per column)

  

Static or “Standby” Power Consumption

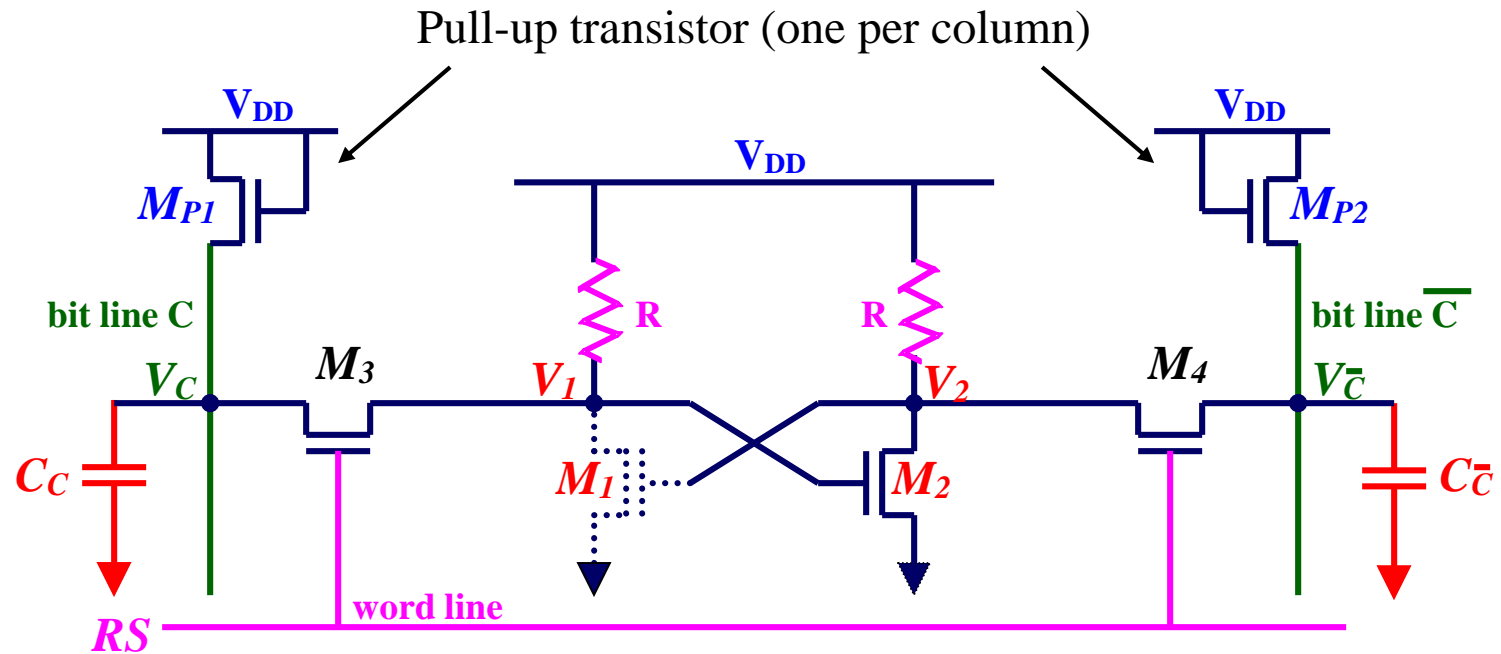


- *Assume:* 1 bit is stored in the cell $\Rightarrow M_1$ OFF, M_2 ON $\Rightarrow V_1 = V_{OH}$, $V_2 = V_{OL}$. I.E. One load resistor is always conducting non-zero current.

$$P_{\text{standby}} = (V_{DD} - V_{OL})^2 / R$$

with $R = 100\text{M}\Omega$ (undoped poly), $P_{\text{standby}} \approx 0.25 \mu\text{W}$ per cell for $V_{DD} = 5\text{V}$

Circuit of CMOS SRAM Cell

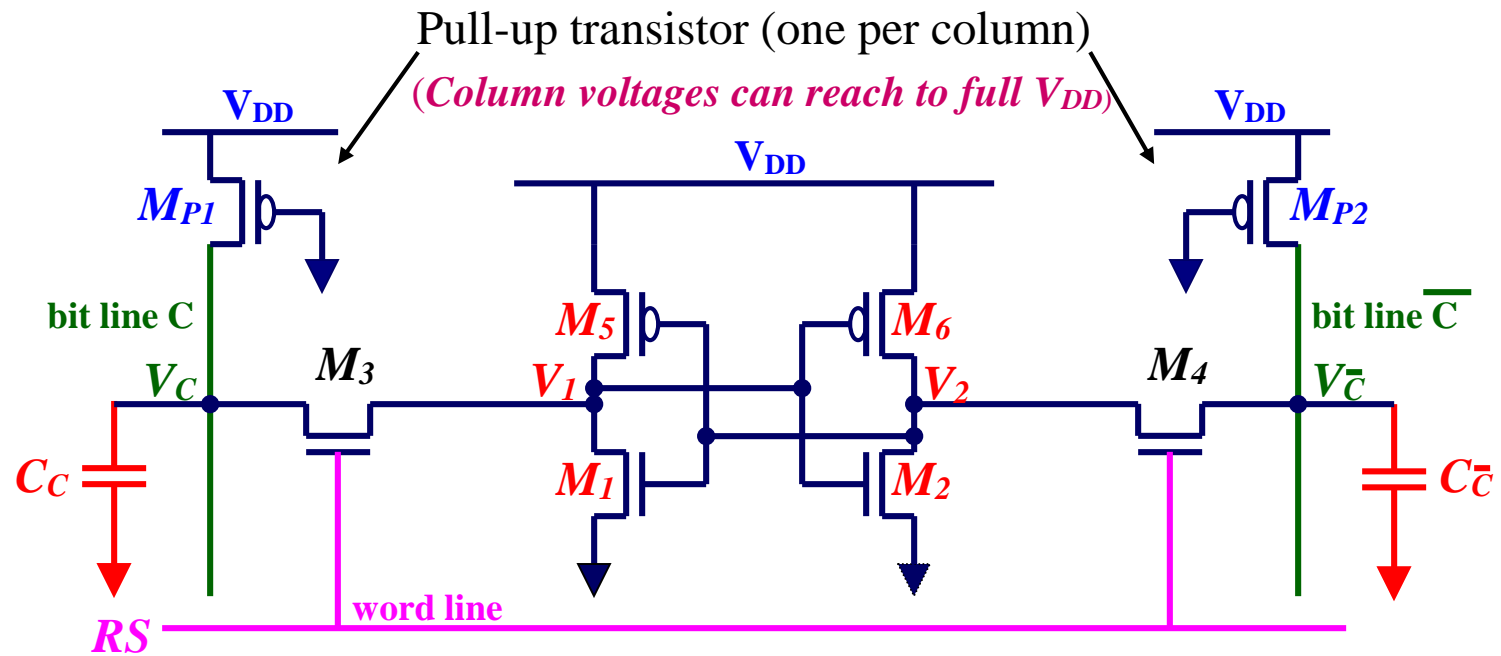

■ Advantages


- Very **low standby power** consumption
- **Large noise margins** than **R-load SRAMS**
- **Operate at lower supply voltages** than **R-load SRAMS**

■ Disadvantages

- **Larger die area**: To accommodate the n-well for pMOS transistors and polysilicon contacts. The area has been reduced by using multi-layer polysilicon and multi-layer metal processes
- **CMOS more complex process**



6T-SRAM — Layout

 


Source: Digital Integrated Circuits 2nd



CMOS SRAM Cell Design strategy

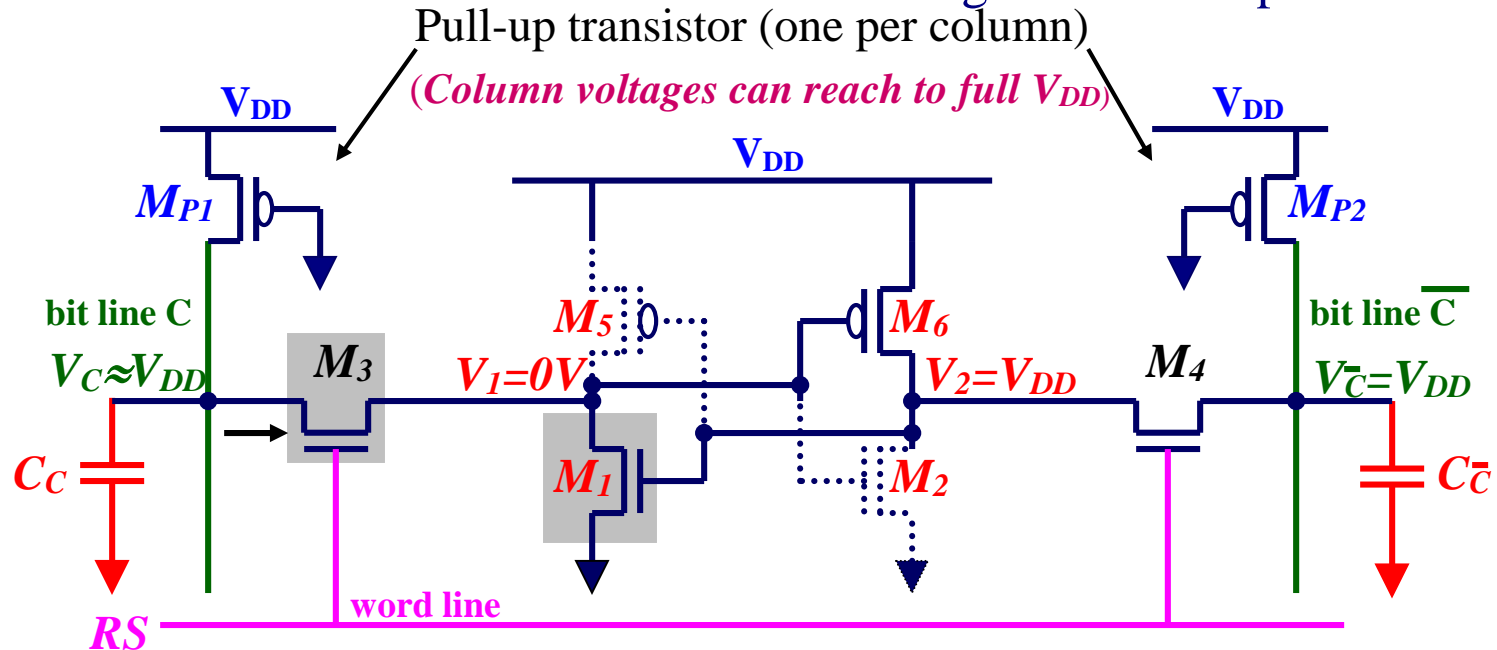- Two basic requirements which dictate W/L ratios
 - Data-read operation should **not destroy data** in the cell
 - Allow modification** of stored data during data-write operation




- Read "0" operation

- at $t=0^-$: $V_1=0V$, $V_2=V_{DD}$; M_3, M_4 OFF; M_2, M_5 OFF; M_1, M_6 Linear
- at $t=0$: $RS = V_{DD}$, M_3 Saturation, M_4 Linear; M_2, M_5 OFF; M_1, M_6 Linear

- Slow discharge of large C_c : Require $V_1 < V_{T,2} \Rightarrow$ Limits M_3 W/L wrt M_1 W/L



CMOS SRAM Cell Design Strategy (Cont.)

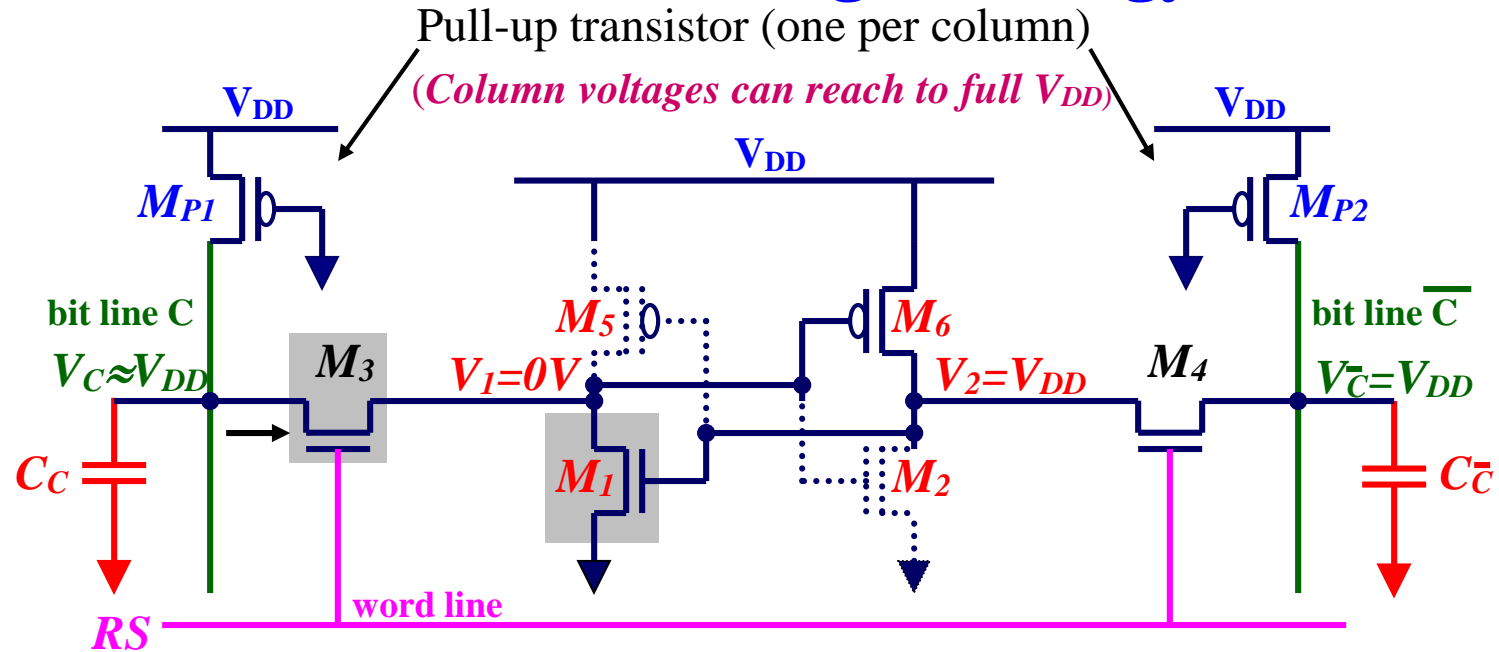

- **Design Constraint:** $V_{1,max} < V_{T,2} = V_{T,n}$ to keep M_2 OFF

» M_3 saturation, M_1 linear \Rightarrow

$$k_{n,3}(V_{DD}-V_1-V_{T,n})^2/2 = k_{n,1}(2(V_{DD}-V_{T,n})V_1-V_1^2)/2$$

» Therefore,


$$\frac{k_{n,3}}{k_{n,1}} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} < \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} - 2V_{T,n})^2}$$

Symmetry:

Same for $k_{n,4}/k_{n,2}$
(M_1 OFF for Read “1”)

CMOS SRAM Cell Design Strategy (Cont.)

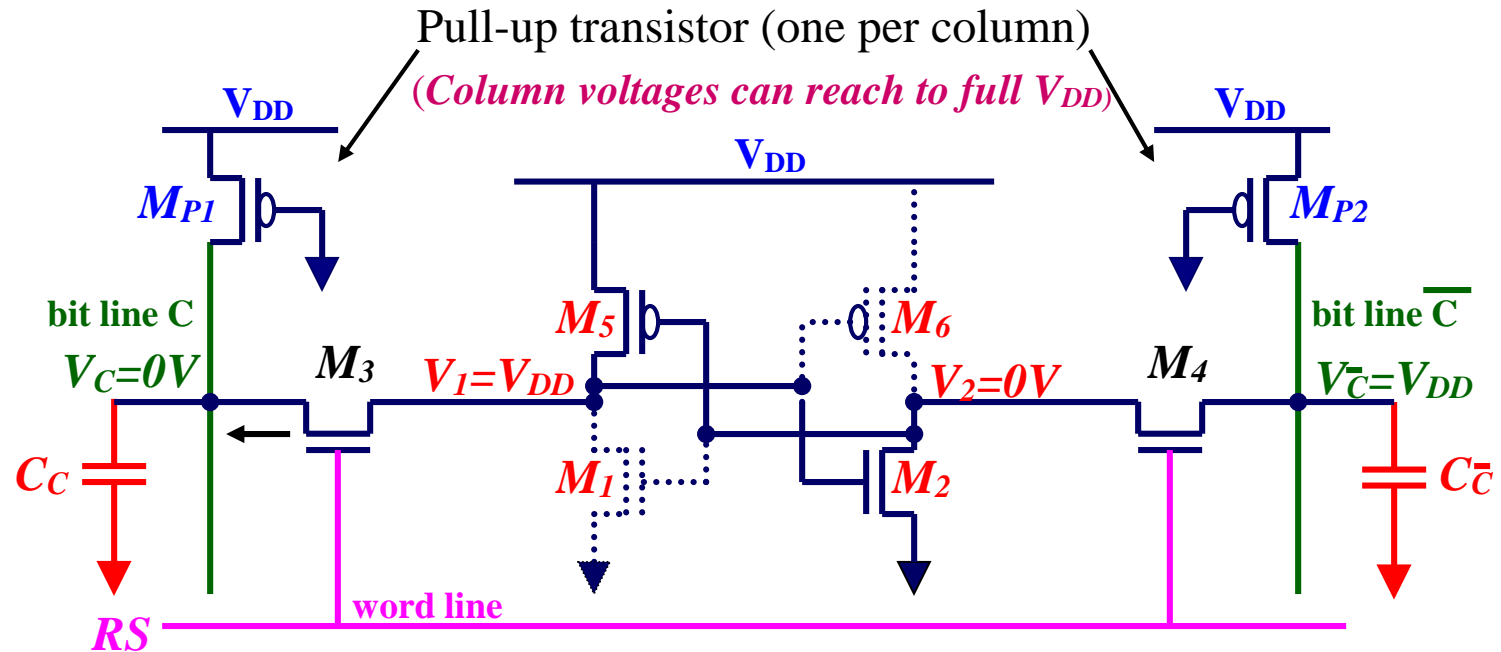- Write “0” operation with “1” stored in cell:



- V_C is set “0” by data-write circuit (“1” stored)
 - at $t=0^-$: $V_1=V_{DD}$, $V_2=0V$; M_3, M_4 OFF; M_2, M_5 Linear; M_1, M_6 OFF
 - at $t=0$: $V_C=0V$, $V_{\bar{C}}=V_{DD}$; M_3, M_4 saturation; M_2, M_5 Linear; M_1, M_6 OFF
 - » Write “0” $\Rightarrow V_1: V_{DD} \rightarrow 0 (< V_{2T,n})$ and $V_2: 0 \rightarrow V_{DD} (M_2 \rightarrow OFF)$



CMOS SRAM Cell Design Strategy (Cont.)

- **Design constraint: $V_{1,max} < V_{T,2} = V_{T,n}$ to keep M_2 OFF**

» When $V_1 = V_{T,n}$: M_3 Linear and M_5 saturation \Rightarrow

$$k_{p,5}(0 - V_{DD} - V_{T,p})^2/2 = k_{n,3}(2(V_{DD} - V_{T,n})V_{T,n} - V_{T,n}^2)/2$$


» $V_1 < V_{T,n}$, i.e. $M_2(M_1)$ **forced OFF**

$$\frac{k_{p,5}}{k_{n,3}} = \frac{k_{p,6}}{k_{n,4}} < \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} + V_{T,p})^2} \Rightarrow$$


By symmetry

$$\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 < \frac{\mu_n}{\mu_p} \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} + V_{T,p})^2} \Rightarrow$$
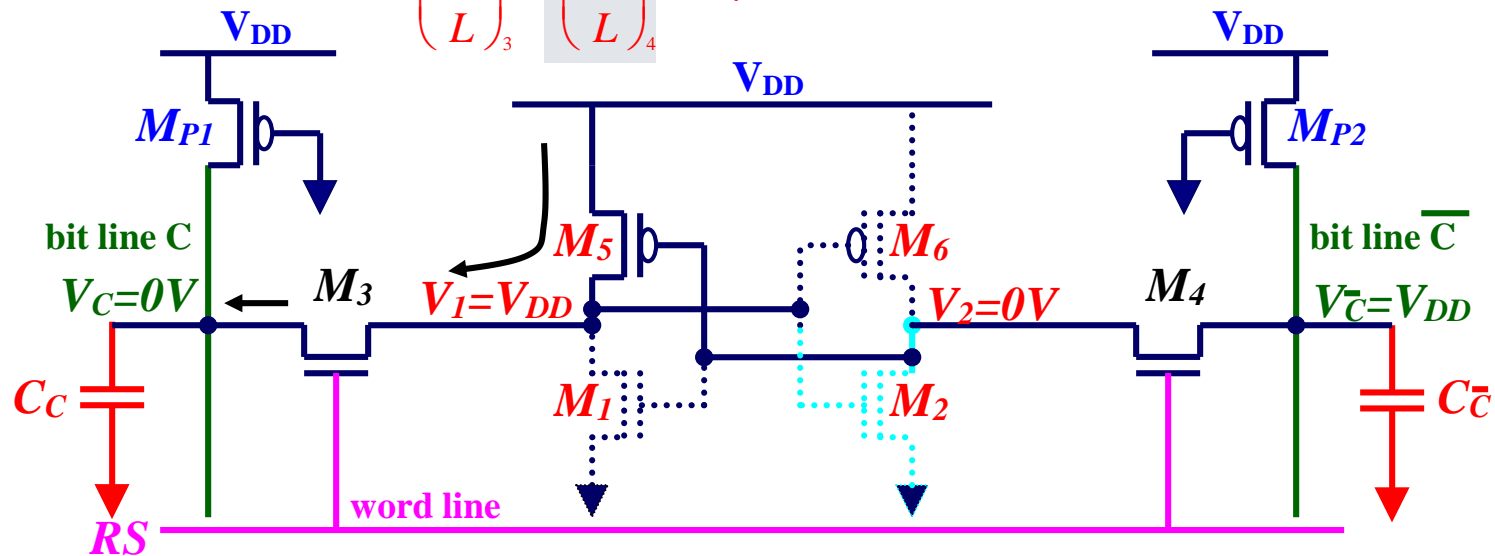
$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$$



SRAM Write Circuit

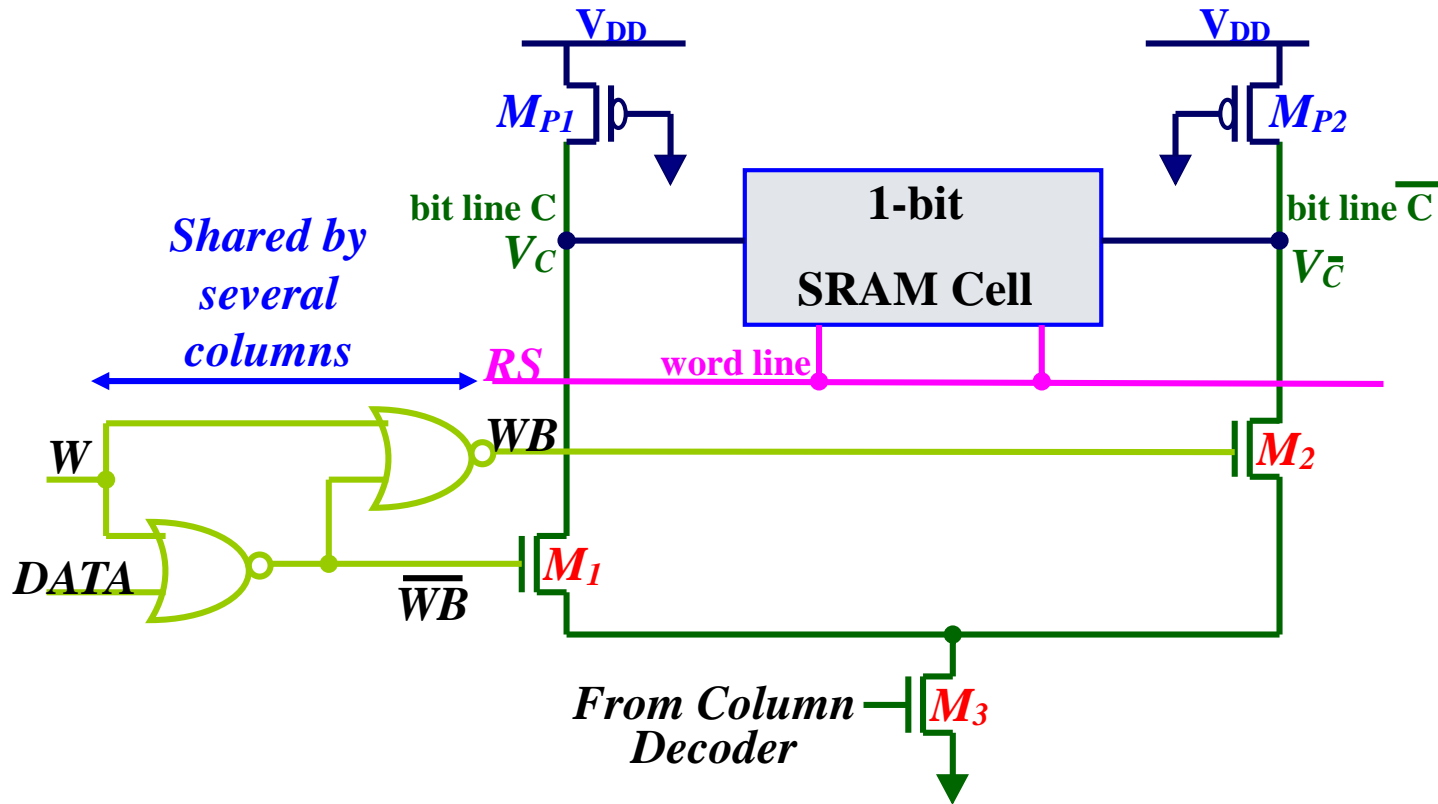


W	$DATA$	\bar{W}	WB	Operation (M_3 on)
0	1	0	1	M_1 off, M_2 on $\Rightarrow V_{\bar{C}} \rightarrow$ low
0	0	1	0	M_1 on, M_2 off $\Rightarrow V_C \rightarrow$ low
1	X	0	0	M_1 off, M_2 off $\Rightarrow V_C, V_{\bar{C}}$ no change



SRAM Read Circuit

Source coupled differential amplifier

 

$$I_{D1} = \frac{k_n}{2} (V_c - V_x - V_{T1,n})^2$$

$$I_{D2} = \frac{k_n}{2} (V_{\bar{c}} - V_x - V_{T2,n})^2$$

$$A_{sense} = \frac{\partial(V_{o1} - V_{o2})}{\partial(V_c - V_{\bar{c}})} = -g_m R$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \sqrt{2k_n I_D}$$


Increase R →

Use active load

Use cascade



Sense Amp Operation

 


Source: Digital Integrated Circuits 2nd

CMOS Digital Integrated Circuits



Fast Sense Amplifier

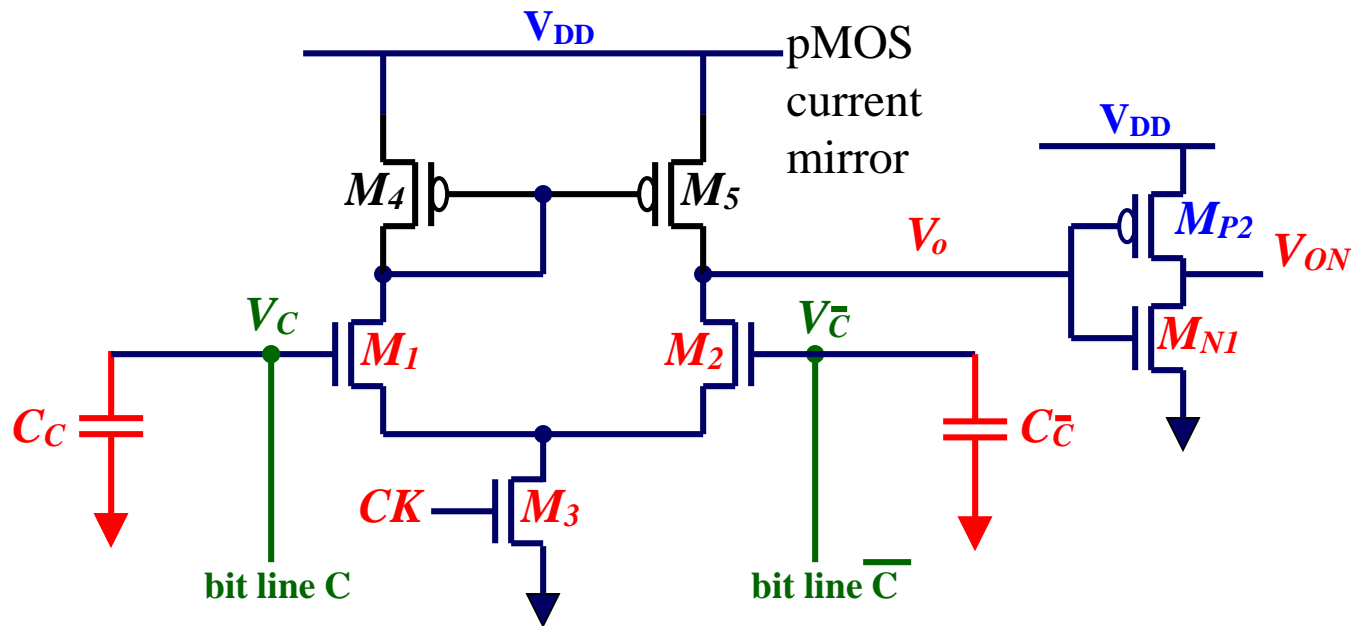


- $V_C < V_{\bar{C}}$: $M_1 \Rightarrow OFF$, V_o decreases, $V_{ON} \Rightarrow High$
- $V_C > V_{\bar{C}}$: $M_2 \Rightarrow OFF$, V_o remains high, $V_{ON} = Low$


$$A_{sense} = -g_{m2}(r_{o2} || r_{o5})$$



 
Two-Stage differential Current-Mirror Amplifier Sense Circuit



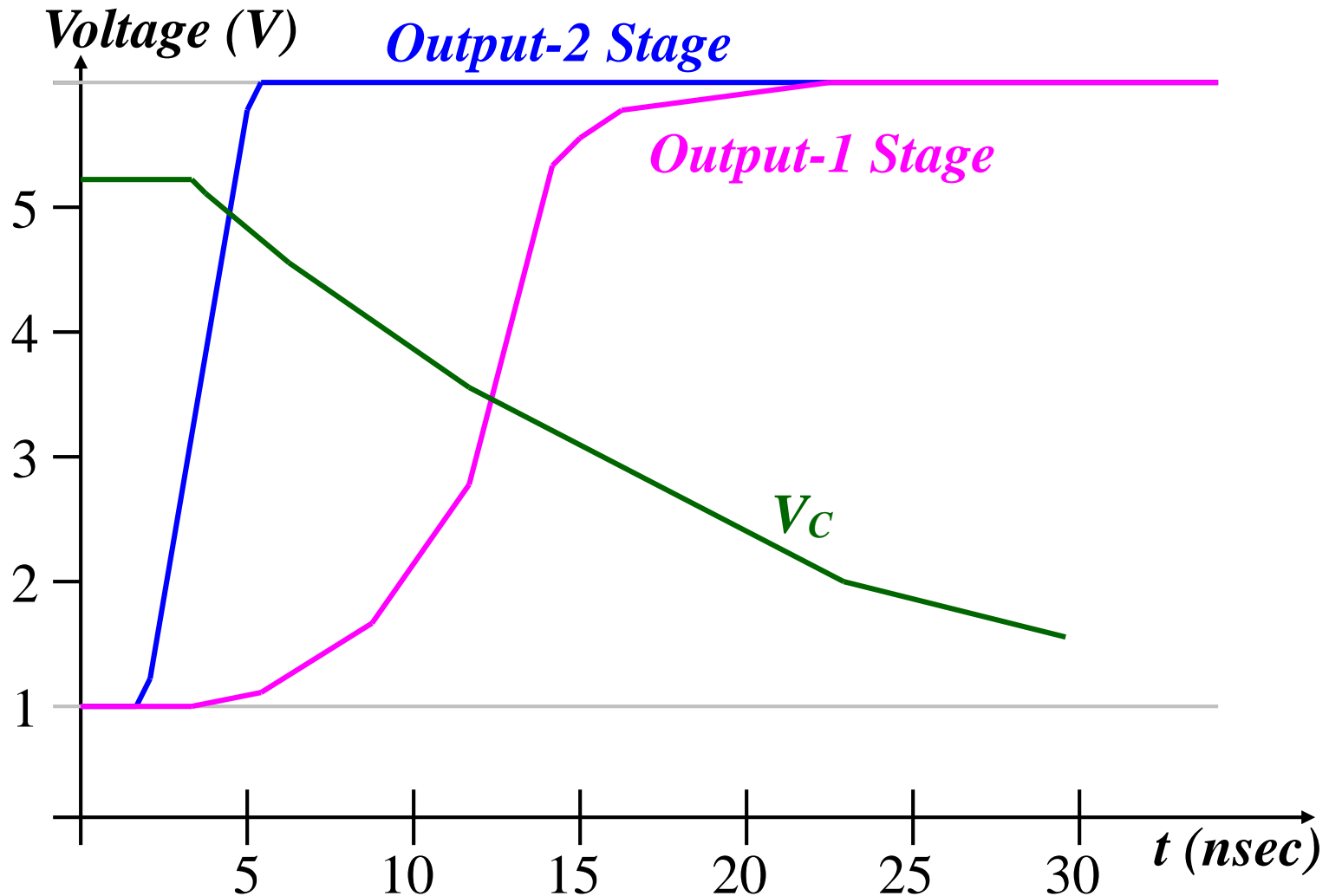Typical Dynamic Response for One and Two Stage Sense Amplifier Circuits



Cross-Coupled nMOS Sense Amplifier

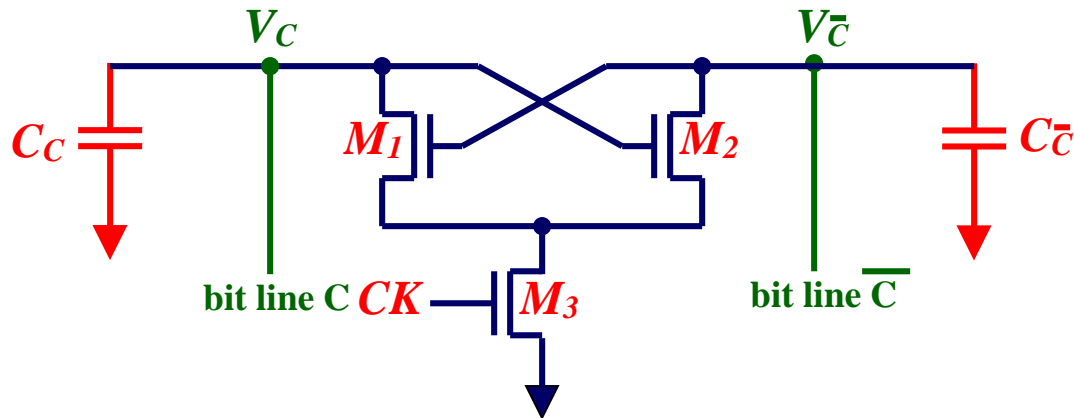

- **Assume:** M_3 OFF, V_C and $V_{\bar{C}}$ are initially precharged to V_{DD}
- **Access:** V_C drops slightly less than $V_{\bar{C}}$
- $M_3 \Rightarrow$ ON and $V_C < V_{\bar{C}}$: M_1 ON first, pulling V_C lower
 M_2 turns OFF, C_C discharge via M_1 and M_3

Enhances differential voltage $V_C - V_{\bar{C}}$

Does not generate output logic level




Dynamic Read-Write Memory (DRAM) Circuits

- **SRAM:** 4~6 transistors per bit
4~5 lines connecting as charge on capacitor
- **DRAM:** Data bit is stored as charge on capacitor

Reduced die area


Require periodic refresh

 

Four-Transistor DRAM Cell



DRAM Circuits (Cont.)

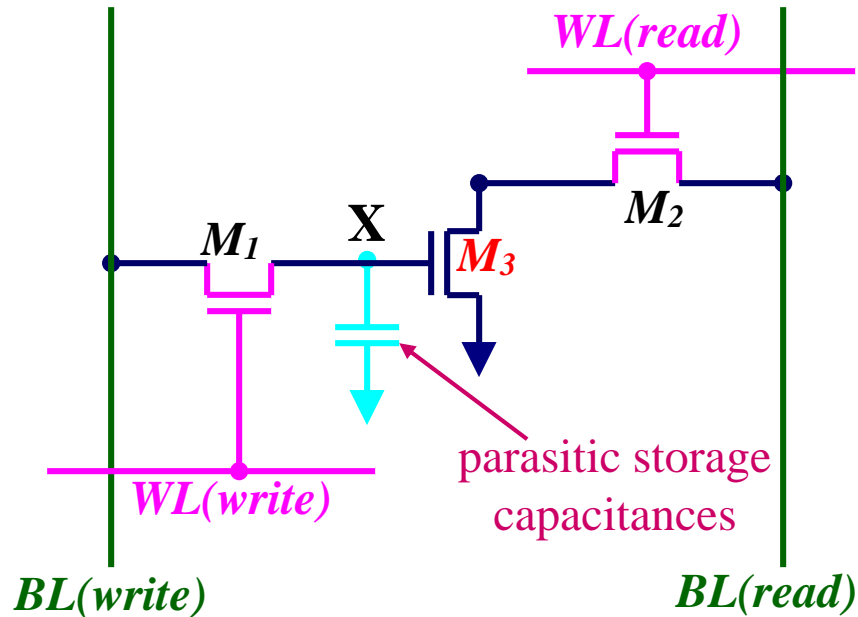

Three-Transistor DRAM Cell


No constraints on device ratios

Reads are non-destructive

Value stored at node X when writing a “1” = $V_{WWL} - V_{Tn}$




3T-DRAM — Layout

 

Source: Digital Integrated Circuits 2nd



One-Transistor DRAM Cell

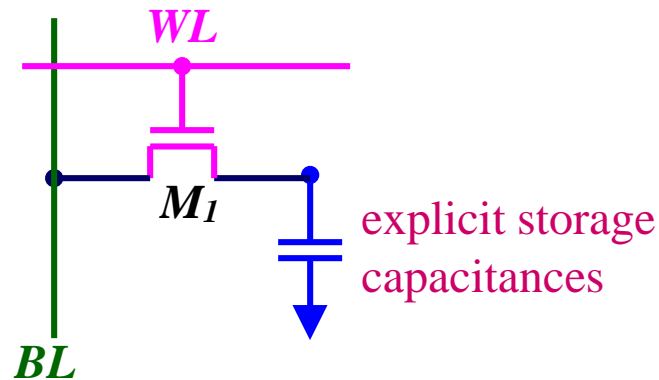


One-Transistor DRAM Cell

- **Industry standard** for high density dram arrays
- **Smallest** component count and silicon area per bit
- Separate or “**explicit**” capacitor (dual poly) per cell




Operation of Three-Transistor DRAM Cell

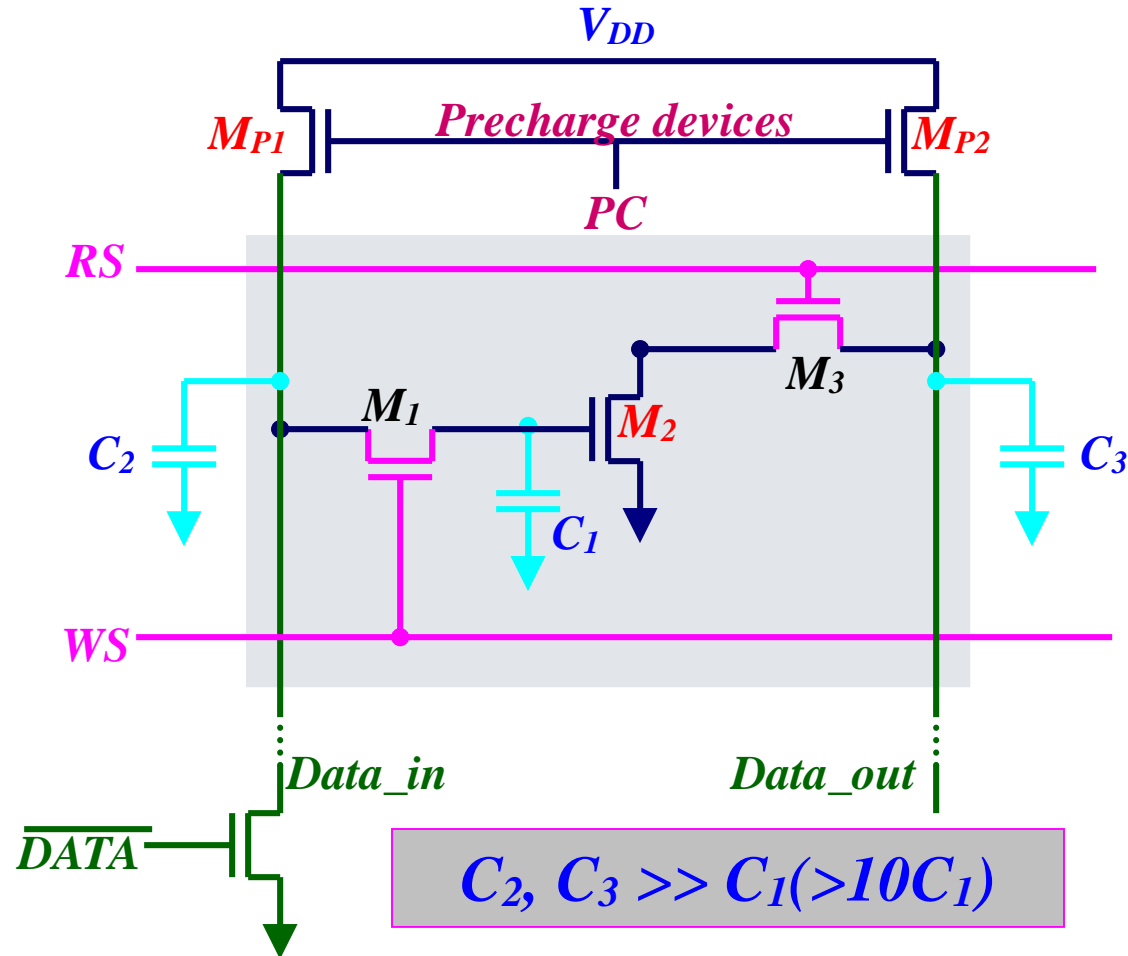

- The binary information is stored as the charge in C_1
- **Storage transistor M_2** is on or off depending on the charge in C_1
- **Pass transistors M_1 and M_3** : access switches
- Two separate bit lines for “data read” and “data write”




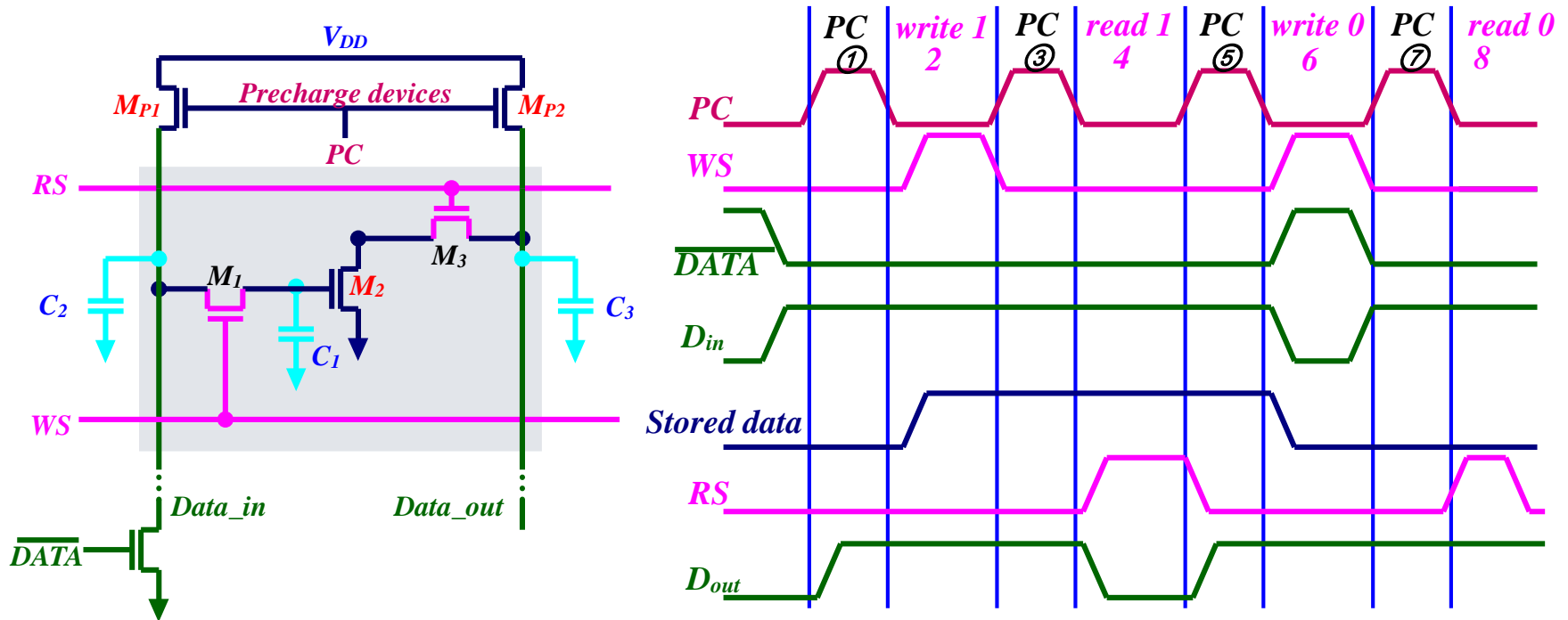Operation of Three-Transistor DRAM Cell (Cont.)



- The operation is based on a **two-phase non-overlapping clock scheme**
 - » The precharge events are driven by ϕ_1 , and the “read” and “write” operations are driven by ϕ_2 .
 - » Every “read” and “write” operation is preceded by a precharge cycle, which is initiated with **PC going high**.

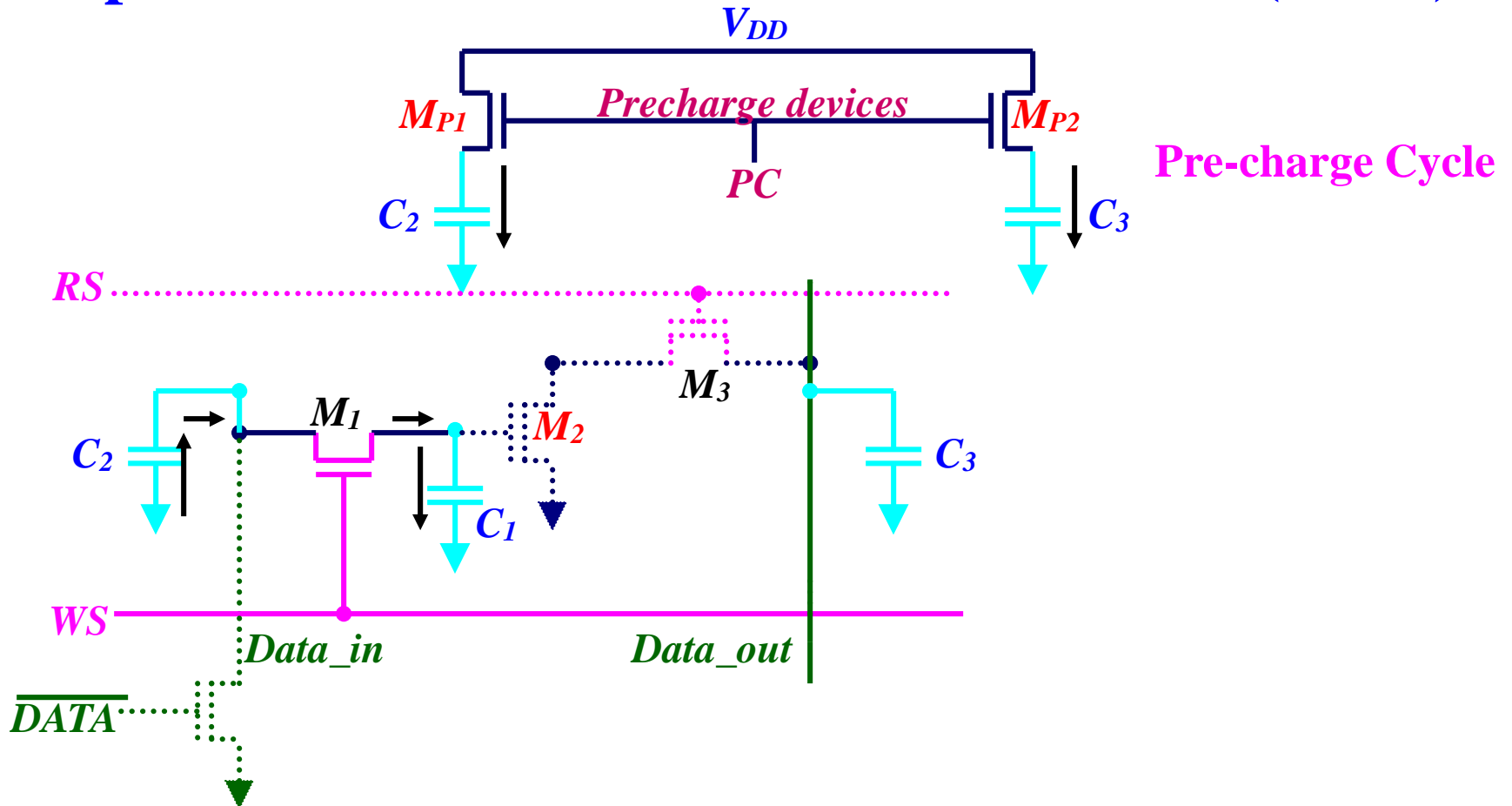
Operation of Three-Transistor DRAM Cell (Cont.)



- **Write "1" OP:** $\overline{DATA} = 0$, $WS = 1$; $RS = 0$

- » C_2 , C_1 Share charge due to M_1 ON
- » Since $C_2 \gg C_1$, the storage node C_1 attains approximately the same logic level.

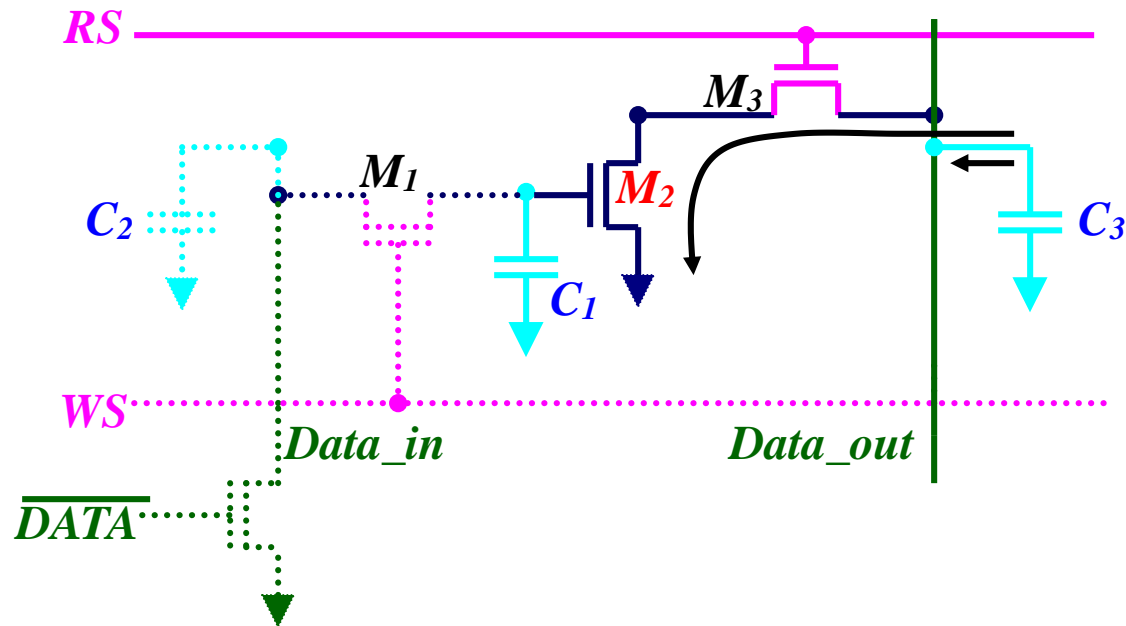
Operation of Three-Transistor DRAM Cell (Cont.)



- **Read “1” OP:** $\overline{DATA} = 0$, $WS = 0$; $RS = 1$
 - » M_2, M_3 ON $\Rightarrow C_3, C_1$ discharges through M_2 and M_3 , and the falling column voltage is interpreted by the “data read” circuitry as a stored logic “1”.




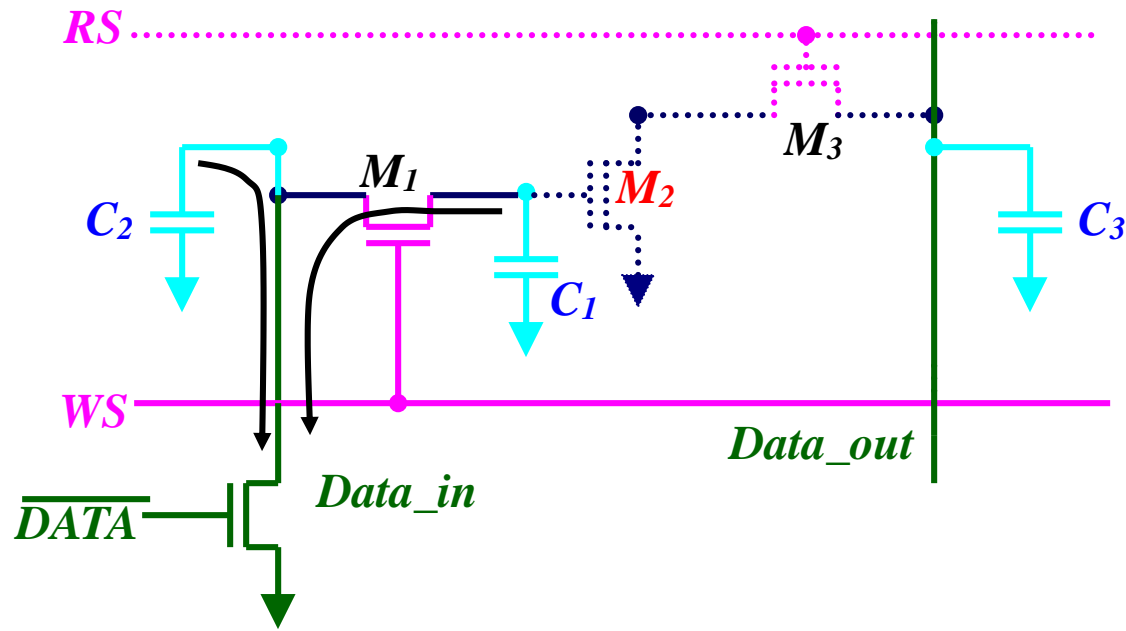Operation of Three-Transistor DRAM Cell (Cont.)



- **Write “0” OP:** $\overline{DATA} = 1$, $WS = 1$; $RS = 0$
 - » M_2, M_3 **ON** $\Rightarrow C_2$ and C_1 discharge to 0 through M_1 and $data_in$ **nMOS**.

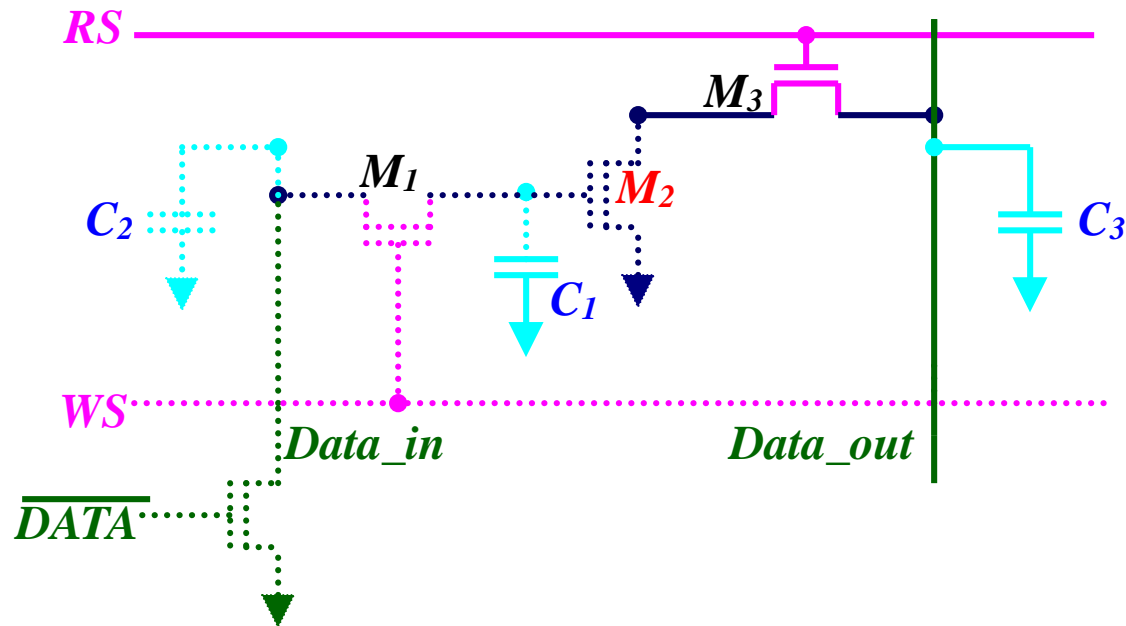
Operation of Three-Transistor DRAM Cell (Cont.)



- **Read “0” OP:** $\overline{DATA} = 1$, $WS = 0$; $RS = 1$
 - » C_3 does not discharge due to M_2 OFF, and the logic-high level on the *Data_out* column is interpreted by the data read circuitry as a stored “0” bit.



Operation of One-Transistor DRAM Cell

 

- **Write “1” OP:** $BL = 1$, $WL = 1$ (M_1 ON) $\Rightarrow C_1$ charges to “1”
- **Write “0” OP:** $BL = 0$, $WL = 1$ (M_1 ON) $\Rightarrow C_1$ discharges to “0”
- **Read OP:** destroys stored charge on $C_1 \Rightarrow$ destructive refresh is needed after every data read operation



Appendix

■ Derivation of $\frac{k_{n,3}}{k_{n,1}} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} < \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} - 2V_{T,n})^2}$

$$k_{n,3}(V_{DD} - V_1 - V_{T,n})^2/2 = k_{n,1}(2(V_{DD} - V_{T,n})V_1 - V_1^2)/2$$

■ Therefore,

$$\frac{k_{n,3}}{k_{n,1}} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} = -1 + \frac{(V_{DD} - V_{T,n})^2}{(V_{DD} - V_1 - V_{T,n})^2} < -1 + \frac{(V_{DD} - V_{T,n})^2}{(V_{DD} - 2V_{T,n})^2} = \frac{2(V_{DD} - 1.5V_{T,n})}{(V_{DD} - 2V_{T,n})^2}$$

