 


Digital IC Design and Architecture




Combinational Logic and Circuits

Static CMOS Circuit

At every point in time (except during the switching transients) each **gate output is connected to either V_{DD} or V_{SS}** via a low-resistive path.


The outputs of the gates **assume at all times the value of the Boolean function**, implemented by the circuit (ignoring, once again, the transient effects during switching periods).

 This is in contrast to the **dynamic** circuit class, which relies on temporary storage of signal values on the capacitance of high impedance circuit nodes.



V_{out} is Boolean function of inputs,
 $V_1, V_2, V_3, \dots, V_N$.

 
"1" $\Rightarrow V_{DD}$
 "0" $\Rightarrow 0$



NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal


 
NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1





PMOS Transistors in Series/Parallel Connection

  PMOS switch closes when switch control input is low



PMOS Transistors pass a “strong” 1 but a “weak” 0

Threshold Drops

    

Complementary CMOS Logic Style

- PUP is the DUAL of PDN
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

- The complementary gate is inverting




$$\text{AND} = \text{NAND} + \text{INV}$$

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN: $G = A \cdot B \Rightarrow$ Conduction to GND


PUN: $F = \overline{\overline{A} + \overline{B}} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$\overline{G(\overline{In}_1, \overline{In}_2, \overline{In}_3, \dots)} \equiv F(\overline{In}_1, \overline{In}_2, \overline{In}_3, \dots)$$


Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 


Complex CMOS Gate

 

Digital IC Design and Architecture

 

Combinational Logic:
CMOS
Implementation

 


Symmetrical EQUIV INV

$$k_{pEQV} = k_{nEQV} \text{ and } V_{Tn} = |V_{Tp}| \Rightarrow V_{th}(\text{INV}) = V_{DD}/2$$

$$V_{th}(\text{ND2}) = V_{DD}/2 \Rightarrow k_n = 4k_p$$

 PARASITIC CAPS FOR CMOS ND2 (CONSERVATIVE) 25



$$\begin{aligned}
 C_{gdn1} &= C_{gdn2} = C_{gdn} \\
 C_{dbn1} &= C_{dbn2} = C_{dbn} \\
 C_{gdp1} &= C_{gdp2} = C_{gdp} \\
 C_{dbp1} &= C_{dbp2} = C_{dbp} \\
 C_{gsp1} &= C_{gsp2} = C_{gsp} \\
 C_{sbp1} &= C_{sbp2} = C_{sbp}
 \end{aligned}$$

WORST CASE for PULL-UP => $V_1 = V_{DD}$, $V_2 = V_{DD} \rightarrow 0$ & $V_x = \text{low} \rightarrow \text{high}$

$$C_{\text{load-ND2}} \approx 2C_{dbn} + C_{sbn} + 2C_{dbp} + C_{int} + C_{gb} = 3C_{dbn} + 2C_{dbp} + C_{int} + C_{gb}$$

WORST CASE for PULL-DOWN => $V_1 = V_{DD}$, $V_2 = 0 \rightarrow V_{DD}$ & $V_x = \text{high} \rightarrow \text{low}$

$$C_{\text{load-ND2}} \approx 2C_{dbn} + C_{sbn} + 2C_{dbp} + C_{int} + C_{gb} = 3C_{dbn} + 2C_{dbp} + C_{int} + C_{gb}$$

$$\text{NDn: } C_{\text{load-ND2}} \approx (2n-1)C_{dbn} + nC_{dbp} + C_{int} + C_{gb}$$

ND2:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(ND2) = V_{DD}/2 \Rightarrow k_n = 4k_p$$

2. Propogation delay τ_{PHL} or τ_{PLH} :

$$\tau_{PHL-ND2} \approx \frac{C_{load-ND2}}{k_n / 2} \left[\frac{2V_{TO_n}}{V_{DD} - V_{TO_n}} + \ln \left(\frac{4(V_{DD} - V_{TO_n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-ND2} \approx \frac{C_{load-ND2}}{2k_p} \left[\frac{2|V_{TO_p}|}{V_{DD} - |V_{TO_p}|} + \ln \left(\frac{4(V_{DD} - |V_{TO_p}|)}{V_{DD}} - 1 \right) \right]$$

NDn:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(NDn) = V_{DD}/2 \Rightarrow k_n = n^2 k_p$$

2. Propogation delay τ_{PHL} or τ_{PLH} :



$$\tau_{PHL-NDn} \approx \frac{C_{load-NDn}}{k_n / n} \left[\frac{2V_{TO_n}}{V_{DD} - V_{TO_n}} + \ln \left(\frac{4(V_{DD} - V_{TO_n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NDn} \approx \frac{C_{load-NDn}}{nk_p} \left[\frac{2|V_{TO_p}|}{V_{DD} - |V_{TO_p}|} + \ln \left(\frac{4(V_{DD} - |V_{TO_p}|)}{V_{DD}} - 1 \right) \right]$$


CMOS LOGIC GATES

19

2-INPUT NOR (NR2)

  

 nMOS Net ON, pMOS Net OFF
or
nMOS Net OFF, pMOS Net ON




Symmetrical EQUIV INV

$k_{pEQV} = k_{nEQV}$ or $k_{pEQV}/k_{nEQV} = 1$ and $V_{Tn} = |V_{Tp}| \Rightarrow V_{th}(INV) = V_{DD}/2$

$$V_{th}(NR2) = V_{DD}/2 \Rightarrow k_p = 4k_n$$

PARASITIC CAPS FOR CMOS NR2 (CONSERVATIVE)

22

 

WORST CASE for PULL-UP => $V_1 = 0, V_2 = V_{DD} \rightarrow 0 \text{ & } V_x = \text{low} \rightarrow \text{high}$

$$C_{\text{load-NR2}} \approx 2C_{\text{dbn}} + 2C_{\text{dbp}} + C_{\text{sbp}} + C_{\text{int}} + C_{\text{gb}} = 2C_{\text{dbn}} + 3C_{\text{dbp}} + C_{\text{int}} + C_{\text{gb}}$$

WORST CASE for PULL-DOWN => $V_1 = 0, V_2 = 0 \rightarrow V_{DD} \text{ & } V_x = \text{high} \rightarrow \text{low}$

$$C_{\text{load-NR2}} \approx 2C_{\text{dbn}} + 2C_{\text{dbp}} + C_{\text{sbp}} + C_{\text{int}} + C_{\text{gb}} = 2C_{\text{dbn}} + 3C_{\text{dbp}} + C_{\text{int}} + C_{\text{gb}}$$

NRn: $C_{\text{load-NR2}} \approx nC_{\text{dbn}} + (2n-1)C_{\text{dbp}} + C_{\text{int}} + C_{\text{gb}}$

NR2:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(NR2) = V_{DD}/2 \Rightarrow k_p = 4k_n$$

2. Propogation delay τ_{PHL} or τ_{PLH} :

$$\tau_{PHL-NR2} \approx \frac{C_{load-NR2}}{2k_n} \left[\frac{2V_{TOn}}{V_{DD} - V_{TOn}} + \ln \left(\frac{4(V_{DD} - V_{TOn})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NR2} \approx \frac{C_{load-NR2}}{k_p / 2} \left[\frac{2|V_{TOp}|}{V_{DD} - |V_{TOp}|} + \ln \left(\frac{4(V_{DD} - |V_{TOp}|)}{V_{DD}} - 1 \right) \right]$$

NRn:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:


$$V_{th}(NRn) = V_{DD}/2 \Rightarrow k_p = n^2 k_n$$

2. Propogation delay τ_{PHL} or τ_{PLH} :

$$\tau_{PHL-NRn} \approx \frac{C_{load-NRn}}{nk_n} \left[\frac{2V_{TOn}}{V_{DD} - V_{TOn}} + \ln \left(\frac{4(V_{DD} - V_{TOn})}{V_{DD}} - 1 \right) \right]$$


$$\tau_{PLH-NRn} \approx \frac{C_{load-NRn}}{k_p / n} \left[\frac{2|V_{TOp}|}{V_{DD} - |V_{TOp}|} + \ln \left(\frac{4(V_{DD} - |V_{TOp}|)}{V_{DD}} - 1 \right) \right]$$

MACROMODELING

 

$$\tau_{PLH} = \tau_{int,LH} + [(C_{L2} - C_{L1})/C_{L2}] \times \tau_{ext,LH}$$

 
$$\tau_{PHL} = \tau_{int,HL} + [(C_{L2} - C_{L1})/C_{L2}] \times \tau_{ext,HL}$$



$$\tau_{PLH} = 0.26 + C_L \times 2.12 \text{ ns}$$

$$\tau_{PHL} = 0.42 + C_L \times 3.88 \text{ ns}$$

Load Conditions





 


Time	$C_L = 0$	$C_L = 0.5 \text{ pF}$	$C_L = 1.0 \text{ pF}$
$\tau_{PLH} \text{ (ns)}$	0.26	1.32	2.38
$\tau_{PHL} \text{ (ns)}$	0.42	2.36	4.30
$\tau_{ext,LH} \text{ (ns/pF)}$	0	2.12	2.12
$\tau_{ext,HL} \text{ (ns/pF)}$	0	3.88	3.88

TYPICAL CMOS NAND AND NOR DELAYS



Delays for a Family of **NAND & NOR** gates

     1. $W_n = 6.4 \mu\text{m}$, $L_n = 1 \mu\text{m}$, and $W_p = 12.8 \mu\text{m}$, $L_p = 1 \mu\text{m}$.
2. $t_{\text{input-rise/fall}} = 0.1 \text{ ns}$ and $C_{\text{load}} = 0 \rightarrow 1 \text{ pF}$.




COLOR LEGEND

	n-Well
	p-Well
	n ⁺
	Polysilicon
	p ⁺
	Gate Oxide
	Field Oxide
	Metal 1
	Metal 2
	Metal 3
	Contact/via

  

STICK DIAGRAM →

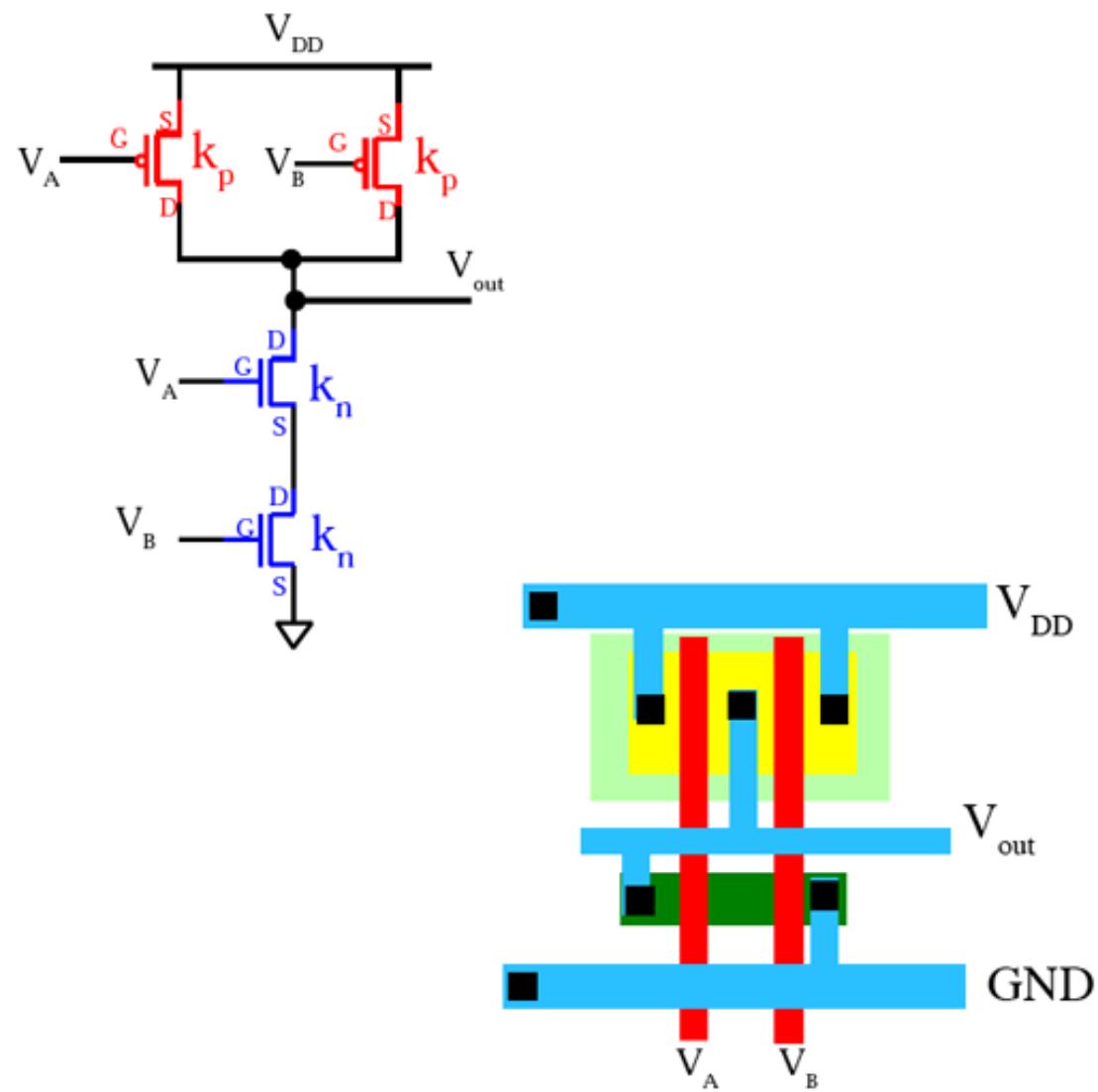


COLOR LEGEND 30


- █ n-Well
- █ p-Well
- █ n⁺
- █ Polysilicon
- █ p⁺
- █ Gate Oxide
- █ Field Oxide
- █ Metal 1
- █ Metal 2
- █ Metal 3
- █ Contact/via

COMPLEX LOGIC GATES

$$Z = \overline{A(D + E)} + BC$$

 “OR” OPS PERFORMED BY PARALLEL CONNECTED DRIVERS.
 “AND” OPS PERFORMED BY SERIES CONNECTED DRIVERS.
 “INVERSION” IS PROVIDED BY NATURE OF MOS CIRCUIT OP.




 

ON Drivers	Out-GND Path
A-D	Class 1
A-E	Class 1
B-C	Class 1
A-D-E	Class 2
A-D-B-C	Class 3
A-E-B-C	Class 3
A-D-E-B-C	Class 4
$G_1 < G_2 < G_3 < G_4$	
$V_{OL1} > V_{OL2} > V_{OL3} > V_{OL4}$	

EQV INVERTER (for case G4 where $A = B = C = D = E = 1$)
 
$$\left(\frac{W}{L}\right)_{EQV} = \frac{1}{\left(\frac{W}{L}\right)_B + \left(\frac{W}{L}\right)_C} + \frac{1}{\left(\frac{W}{L}\right)_A + \left(\frac{W}{L}\right)_D + \left(\frac{W}{L}\right)_E}$$



$$\left(\frac{W}{L}\right)_{EQV-ND2} = \frac{1}{2} \left(\frac{W}{L}\right)$$

DESIGN STRATEGY:


1. Identify all WORST CASE Paths (e.g. Class 1).
2. Determine nMOS transistor sizes such that each Class 1 path has $(W/L)_{EQV}$

$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_D = 2 \left(\frac{W}{L}\right)_{EQV}$$



$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_E = 2 \left(\frac{W}{L}\right)_{EQV}$$

$$\left(\frac{W}{L}\right)_B = \left(\frac{W}{L}\right)_C = 2 \left(\frac{W}{L}\right)_{EQV}$$

 
OPTIMIZED LAYOUT OF COMPLEX FULL CMOS GATES



  
OPTIMIZED LAYOUT OF COMPLEX FULL CMOS GATES



ARBITRARY ORDERING OF GATE COLUMNS



 


MINIMIZE NUMBER OF DIFFUSION BREAKS

 


COMMON
EULER PATH:
E-D-A-B-C


Is A-D-E-C-B a
common Euler
path?

   

Arbitrary Stack

 


Optimized Stack

 

ALGORYTHYM FOR LINE OF GATES LAYOUT STYLE

1. Find all Euler paths that cover the graph.
2. Find common n- and p- Euler paths.
3. If no Euler paths are found in step 2, break the gate in the minimum number of places that to achieve step 2 with separate common Euler paths.

FULL CMOS XOR GATE

 


$$\begin{aligned}
 (\overline{A} \cdot \overline{B}) + (A \cdot B) &= (\overline{A} \cdot \overline{B}) \cdot (\overline{A} \cdot B) + (\overline{A} \cdot \overline{B}) \cdot (A \cdot \overline{B}) + (A \cdot B) \cdot (\overline{A} \cdot B) + (A \cdot B) \cdot (A \cdot \overline{B}) \\
 (A + B) \cdot (\overline{A} + \overline{B}) &= A \cdot \overline{A} + \overline{A} \cdot B + A \cdot \overline{B} + B \cdot \overline{B} = \overline{A} \cdot B + A \cdot \overline{B}
 \end{aligned}$$


AOI & OAI GATES

40


 
AOI -> AND-OR-INVERT (for SUM - of - PRODUCTS Realization)
OAI -> OR-AND-INVERT (for PRODUCT - of - SUMS Realization)




AOI

 

  OAI -> OR-AND-INVERT (for PRODUCT - of - SUMS Realization)




Pseudo-nMOS OAI Realization

 

CMOS Transmission Gates (TGs) & TG Logic

SYMBOLS

 


SWITCH CHARACTERISTICS

<u>Input</u>	<u>Output</u>
0 a —○→○— b	Strong 0
1 a —○→○— b	Strong 1

$$I_C = I_{DSn} + I_{SDp}$$

$$V_{in} = V_{DD}$$

 


$$V_{DSn} = V_{DD} - V_{out}$$

$$V_{GSn} = V_{DD} - V_{out}$$

$$V_{DSP} = V_{out} - V_{DD}$$

$$V_{GSp} = -V_{DD}$$

 

$$R_{eqn} = \frac{V_{DD} - V_{out}}{I_{DSn}}$$

$$R_{eqp} = \frac{V_{DD} - V_{out}}{I_{SDp}}$$

$$R_{eqTOT} = R_{eqn} \parallel R_{eqp}$$

REGION 1:
nMOS: SAT
pMOS: SAT

$$R_{eqn} = \frac{2(V_{DD} - V_{out})}{k_n(V_{DD} - V_{out} - V_{Tn})^2}$$

$$R_{eqp} = \frac{2(V_{DD} - V_{out})}{k_p(V_{DD} - |V_{Tp}|)^2}$$

REGION 2
nMOS: SAT
pMOS: LIN


$$R_{eqn} = \frac{2(V_{DD} - V_{out})}{k_n(V_{DD} - V_{out} - V_{Tn})^2}$$



$$R_{eqp} = \frac{2(V_{DD} - V_{out})}{k_p[2(V_{DD} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2]} \\ = \frac{2}{k_p[2(V_{DD} - |V_{Tp}|) - (V_{DD} - V_{out})]}$$

REGION 3
nMOS: OFF
pMOS: LIN


$$R_{eqn} = \infty$$

$$R_{eqp} = \frac{2}{k_p[2(V_{DD} - |V_{Tp}|) - (V_{DD} - V_{out})]}$$

 


  

TRANSMISSION GATE LAYOUTS

 

 Simple and small,
but no metal lines
can pass
horizontally




poly used to achieve
horizontal metal1
transparency




metal2 used to
achieve
horizontal metal1
transparency

 
Routing Gate Signals to Transmission Gate



horizontal, via
metal1

 


vertical, via poly

 

vertical, via metal1 straps
metal2 used to achieve vertical
metal1 transparency




2-INPUT MULTIPLEXER

 


$$\text{output} = A_S + B \cdot \bar{S}$$

A	B	s	\bar{s}	output
x	0	0	1	0 (B)
x	1	0	1	1 (B)
0	x	1	0	0 (A)
1	x	1	0	1 (A)

 XOR (COMPLEMENTARY PASS-TRANSISTOR LOGIC OR CPL)




 

SOME OF THE FUNCTIONS REALIZED BY THE BOOLEAN FUNCTION UNIT (CPL)

OPERATION (Z)	F_1	F_2	F_3	F_4
NOR(A, B)	0	0	0	1
XOR(A, B)	0	1	1	0
NAND(A, B)	0	1	1	1
AND(A, B)	1	0	0	0
OR(A, B)	1	1	1	0


Digital IC Design and Architecture

 


Combinational Logic with Resistive Load



MOS LOGIC CIRCUITS WITH RESISTOR LOADS

2-INPUT NOR GATE (NR2)

 

 
$$I_L = \begin{cases} 0 & \text{CUTOFF} \\ \sum_{m(\text{ON})} \frac{k'_{n,d}}{2} \left(\frac{W}{L} \right)_m \left[2(V_{GS,m} - V_{T0,n}) V_{out} - (V_{out})^2 \right] & \text{LIN} \\ \sum_{m(\text{ON})} \frac{k'_{n,d}}{2} \left(\frac{W}{L} \right)_m \left[(V_{GS,m} - V_{T0,n})^2 \right] & \text{SAT} \end{cases}$$



  

$$\underline{V_{OH} = V_{DD}}: V_A = V_B = 0 \Rightarrow I_{D1} = I_{D2} = 0 \Rightarrow I_L = 0$$



V_A	V_B	V_{out}
LOW	V_{DD}	LOW
V_{DD}	LOW	LOWER

 

$$G_i = \frac{I_{Di}}{V_{DS}} = \frac{I_D}{V_{DS}} \propto KP_i \left(\frac{W}{L} \right)_i = KP \left(\frac{W}{L} \right)$$

$$k_{nEQV-NR2} R_L = \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL-NR2} + V_{OL-NR2}^2}$$

CASE	V_A	V_B	$G_{EQV-NR2}$	$(W/L)_{EQV-NR2}$
1	V_{DD}	V_{OL}	G	(W/L)
2	V_{OL}	V_{DD}	G	(W/L)
3	V_{DD}	V_{DD}	$2G$	$2(W/L)$

  

TRANSIENT ANALYSIS OF 2-INPUT NOR


For all Input Conditions:



$$C_{\text{load-NR2}} = C_{\text{gd1}} + C_{\text{gd2}} + C_{\text{db1}} + C_{\text{db2}} + C_{\text{int}} + C_{\text{gb}}$$

$$= 2C_{\text{gd}} + 2C_{\text{db}} + C_{\text{int}} + C_{\text{gb}}$$

$$\text{where } C_{\text{gd1}} = C_{\text{gd2}} = C_{\text{gd}} \text{ and } C_{\text{db1}} = C_{\text{db2}} = C_{\text{db}}$$

 Note: $C_{\text{load-NR2}} > C_{\text{load-INV}}$



  

Recall for the INV:

$$\tau_{PHL-INV} = \frac{C_{load-INV}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OH} + V_{OL-INV}} - 1 \right) \right]$$

For the NR2:

$C_{load-INV} \rightarrow C_{load-NR2}$ (input pattern independent)

$k_{EQV} \rightarrow m k_n$ where $m = 1$ or 2 .

$V_{OL-INV} \rightarrow V_{OL-NR2}$ (input pattern dependent)

$\tau_{PHL-INV} \rightarrow \tau_{PHL-NR2}$ (input pattern dependent)

NR2 DESIGN STRATEGY

1. Design V_{OL} for worst case: CASE 1 or CASE 2 - V_A or $V_B = V_{DD}$.

Set $(W/L)_1 = (W/L)_2 = (W/L)_{EQV-NR2}$.

WHERE for EQV INV

$$k_{nEQV-NR2} R_L = \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL-NR2} + V_{OL-NR2}^2}$$

2. Design for delay for worst case: CASE 1 or CASE 2 i.e. one input switching L->H and other input set at V_{OL} .

$$\tau_{PHL-INV} = \frac{C_{load-INV}}{k_{nINV}(V_{DD} - V_{T0n})} \left[\frac{V_{T0n}}{(V_{OH} - V_{T0n})} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OH} + V_{OL-INV}} - 1 \right) \right]$$

$$C_{load-NR2} = 2(C_{gd} + C_{db}) + C_{int} + C_{gb}$$


For the NR2:

$$\tau_{PHL-INV} \rightarrow \tau_{PHL-NR2}$$



➡

$C_{load-INV} \rightarrow C_{load-NR2}$	(Case 1 or Case 2)
$V_{OL-INV} \rightarrow V_{OL-NR2}$	(Case 1 or Case 2)
$k_{nINV} \rightarrow k_{nEQV-NR2}$	(Case 1 or Case 2)

n INPUT NOR (NRn)

 
  
$$I_L = \begin{cases} \sum_{m(ON)} \frac{k'_{n,d}}{2} \left(\frac{W}{L}\right)_m [2(V_{GS,m} - V_{T0,n}) V_{out} - (V_{out})^2] & LIN \\ \sum_{m(ON)} \frac{k'_{n,d}}{2} \left(\frac{W}{L}\right)_m [(V_{GS,m} - V_{T0,n})^2] & SAT \end{cases}$$




ASSUMING ALL nMOS DRIVERS HAVE IDENTICAL, (W/L) & $V_{GSi} = V_{GS}$
 $= V_{DD}$ for all $i = 1, 2, \dots, m \leq n$; otherwise $V_{GSi} = V_{OL}$

$$I_{DL} = \begin{cases} \frac{k'_{n,d}}{2} \left(\sum_{m(ON)} \left(\frac{W}{L} \right)_m \right) [2(V_{GS} - V_{TO,n}) V_{out} - (V_{out})^2] & \text{LIN} \\ \frac{k'_{n,d}}{2} \left(\sum_{m(ON)} \left(\frac{W}{L} \right)_m \right) (V_{GS} - V_{TO,n})^2 & \text{SAT} \end{cases}$$

$$G_{EQV} = \sum_{i=1}^m G_i = mG \quad \text{where } m \leq n = \text{number of nMOS} \rightarrow \text{ON}$$
 
$$\left(\frac{W}{L} \right)_{EQV-NRn} = \sum_{m(ON)} \left(\frac{W}{L} \right)_m = m \left(\frac{W}{L} \right) \quad \text{pattern dependent}$$



NRn DESIGN STRATEGY

$$\left(\frac{W}{L}\right)_{EQV} = \sum_{m(ON)} \left(\frac{W}{L}\right)_m = m \left(\frac{W}{L}\right)$$

1. Design V_{OL} for worst case: $V_k = V_{DD}$, $V_i = V_{OL}$ for all $i \neq k$.

Set $(W/L)_1 = (W/L)_2 = \dots = (W/L)_n = (W/L) = (W/L)_{EQV-NRn}$.

WHERE for EQV INV

$$k_{nEQV-NRn} R_L = \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL-NRn} + V_{OL-NRn}^2}$$

2. Design for delay for worst case: $V_k = V_{DD}$, $V_i = V_{OL}$ for all $i \neq k$
i.e. one input switching L->H and all other inputs set at V_{OL} .

$$\tau_{PHL-INV} = \frac{C_{load-INV}}{k_{nINV}(V_{DD} - V_{T0n})} \left[\frac{V_{T0n}}{(V_{OH} - V_{T0n})} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OH} + V_{OL-INV}} - 1 \right) \right]$$



$$C_{load-INV} \Rightarrow C_{load-NRn} = n(C_{gd} + C_{db}) + C_{int} + C_{gb}$$

For the NRn:

$$\tau_{PHL-INV} \rightarrow \tau_{PHL-NORn}$$

→
$$\begin{cases} C_{load-INV} \rightarrow C_{load-NRn} \\ V_{OL-INV} \rightarrow V_{OL-NRn} \\ k_{nINV} \rightarrow k_{nEQV-NRn} \end{cases}$$

2-INPUT NAND GATE (ND2)

  

V_A	V_B	V_{out}
LOW	LOW	HIGH
LOW	HIGH	HIGH
HIGH	LOW	HIGH
HIGH	HIGH	LOW

Let $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)$



CALCULATION OF V_{OH}

WHEN $V_A = 0$ and/or $V_B = 0 \Rightarrow I_L = I_{D1} = I_{D2} = 0$

$$V_{OH} = V_{DD}$$

FOR ALL 3 INPUT CASES

V_{OL}: V_A = V_{DD}, V_B = V_{DD}

  

$$G_{EQV-ND2} = \frac{1}{\frac{1}{G} + \frac{1}{G}} = \frac{1}{2}G \Rightarrow k_{EQV-ND2} = \frac{1}{2}k_n$$

$$\Rightarrow \left(\frac{W}{L}\right)_{EQV-ND2} = \frac{1}{2} \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$


ND2 GATE WITH TWO nMOS (W/L):

$$k_{nEQV-ND2}R_L = \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL-ND2} + V_{OL-ND2}^2}$$

In Pull-Up C_{load} & τ_{PLH} are input pattern dependent

CASE1: $V_1 = V_{OH}$
 $V_2 = V_{OH} \rightarrow V_{OL}$

CASE2: $V_1 = V_{OH} \rightarrow V_{OL}$
 $V_2 = V_{OH}$

 

CASE1:

$$\begin{aligned} C_{load} &= C_{gd1} + C_{gs1} + C_{db1} + C_{sb1} + C_{db2} + C_{gd2} + C_{int} + C_{gb} \quad (\text{worst case}) \\ &\approx [C_{db1} + C_{sb1} + C_{db2}] + C_{int} + C_{gb} \quad (\text{worst case}) \\ &= 3C_{db} \end{aligned}$$

CASE2:

$$\begin{aligned} C_{load} &= C_{gd1} + C_{db1} + C_{int} + C_{gb} \\ &\approx C_{db1} + C_{int} + C_{gb} \end{aligned}$$

$$\tau_{PLH1} > \tau_{PLH2}$$

In Pull-Down C_{load} & τ_{PHL} are input pattern dependent

CASE1:

$$\begin{aligned} V_1 &= V_{\text{OH}} \\ V_2 &= V_{\text{OL}} \rightarrow V_{\text{OH}} \end{aligned}$$

CASE2:

$$\begin{aligned} V_1 &= V_{\text{OL}} \rightarrow V_{\text{OH}} \\ V_2 &= V_{\text{OH}} \end{aligned}$$

CASE1:

$$C_{\text{load}} = C_{gd1} + C_{gs1} + C_{db1} + C_{sb1} + C_{db2} + C_{gd2} + C_{int} + C_{gb} \quad (\text{worst case})$$


$$\approx [C_{db1} + C_{sb1} + C_{db2}] + C_{int} + C_{gb} \quad (\text{worst case})$$

$$= 3C_{db}$$

CASE2:


$$C_{\text{load}} = C_{gd1} + C_{db1} + C_{int} + C_{gb}$$

$$\approx C_{db1} + C_{int} + C_{gb}$$

 

$$\begin{aligned} V_{\text{out}} &= \text{high} \rightarrow \text{low} \\ V_x &= \text{high} \rightarrow \text{low} \\ V_x &= \text{low} \end{aligned}$$
 
$$\tau_{\text{PHL1}} > \tau_{\text{PHL2}}$$



ND2 DESIGN STRATEGY

$$G_{EQV-ND2} = \frac{1}{\frac{1}{R_L} + \frac{1}{G}} = \frac{1}{2} G \Rightarrow k_{EQV-ND2} = \frac{1}{2} k_n$$

$$\Rightarrow \left(\frac{W}{L}\right)_{EQV-ND2} = \frac{1}{2} \left(\frac{W}{L}\right)$$

FOR DESIGN:

1. Determine R_L and $(W/L)_{EQV-ND2}$
2. Set $(W/L)_1 = (W/L)_2 = (W/L) = 2(W/L)_{EQV-ND2}$

$$k_n R_L = \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL} + V_{OL}^2}$$

$$\text{where } k_n = k_n \left(\frac{W}{L} \right)$$


ND2 GATE WITH TWO nMOS (W/L):


$$k_{nEQV-ND2} R_L = \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL-ND2} + V_{OL-ND2}^2} \quad \text{where } k_n = 2k_{EQV-ND2}$$

$$\tau_{PHL-ND2} = \frac{C_{load-ND2}}{k_{nEQV-ND2}(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OH} + V_{OL-ND2}} - 1 \right) \right]$$

$$C_{load-ND2} = 2C_{gd} + 2C_{db} + C_{gs} + C_{sb} + C_{int} + C_{gb} \quad (\text{worst case})$$

n INPUT NAND GATE (NDn)

 

 

Worst-case H-L: $V_1 = V_2 = \dots = V_{n-1} = V_{OH}$ and $V_n = V_{OL} \Rightarrow V_{OH} \Rightarrow V_{out} = V_{OH} \Rightarrow V_{OL}$
 and $V_{x1} = \text{high} \rightarrow \text{low}; V_{x2} = \text{high} \rightarrow \text{low}; \dots; V_{xn-1} = \text{high} \rightarrow \text{low}$

Worst-case L-H: $V_1 = V_2 = \dots = V_{n-1} = V_{OH}$ and $V_n = V_{OH} \Rightarrow V_{OL} \Rightarrow V_{out} = V_{OL} \Rightarrow V_{OH}$
 and $V_{x1} = \text{low} \rightarrow \text{high}; V_{x2} = \text{low} \rightarrow \text{high}; \dots; V_{xn-1} = \text{low} \rightarrow \text{high}$

$$\begin{aligned}
 C_{\text{load-NDn}} &\approx [C_{db1} + C_{db2} + \dots + C_{dbn} + C_{sb1} + C_{sb2} + \dots + C_{sbn-1}] + C_{\text{int}} + C_{\text{gb}} \quad (\text{worst case}) \\
 &= (2n - 1)C_{db}
 \end{aligned}$$

ND_n DESIGN STRATEGY

$$\left(\frac{W}{L}\right)_{EQV-NDn} \approx \frac{1}{n} \left(\frac{W}{L}\right)$$

- > Find (W/L) ratio for EQV-ND_n INVERTER to satisfy V_{OL} SPEC, i.e. for R_L find (W/L)_{EQV-NDn}.
- > Set all (W/L) = n(W/L)_{EQV-NDn}.

WHERE for EQV INV

$$k_{nEQV-NDn} R_L \approx \frac{2(V_{DD} - V_{T0n})}{2(V_{DD} - V_{T0n})V_{OL-NDn} + V_{OL-NDn}^2}$$

2. Design for delay for worst case C_{load-NDn}.

$$\tau_{PHL-NDn} \approx \frac{C_{load-NDn}}{k_{nEQV-NDn}(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OH} + V_{OL-NDn}} - 1 \right) \right]$$

$$\begin{aligned} C_{load-NDn} &\approx [C_{db1} + C_{db2} + \dots + C_{dbn} + C_{sb1} + C_{sb2} + \dots + C_{sbn-1}] + C_{int} + C_{gb} \text{ (worst case)} \\ &= (2n - 1)C_{db} \end{aligned}$$

