
 


Digital IC Design and Architecture

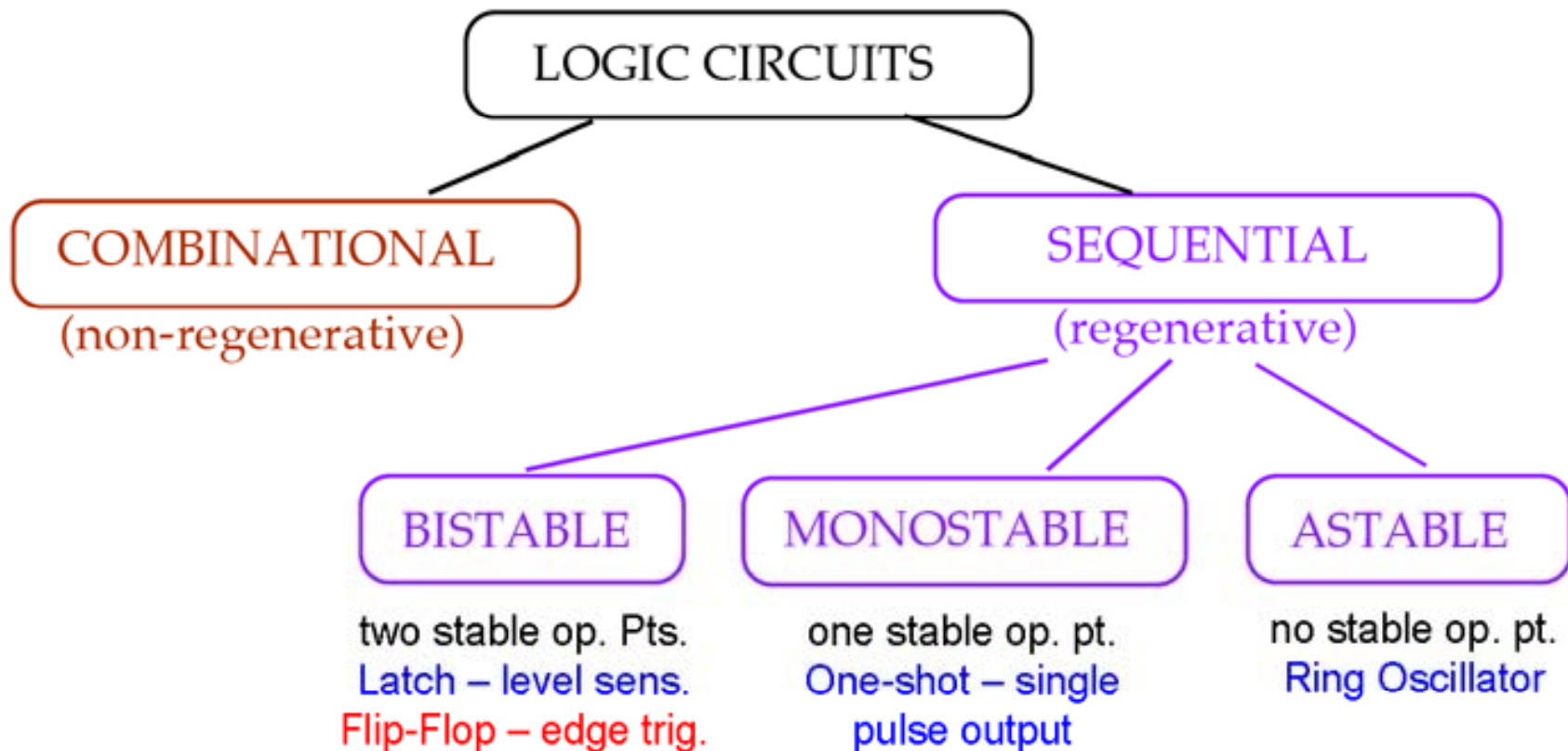

Sequential Circuits


Classes of Logic Circuits



Combinational Circuits: Current Output(s) depend ONLY on Current Inputs.


Sequential Circuits: Current Output(s) depend on Current Inputs and PAST Output(s).

Functions Using Sequential Operations

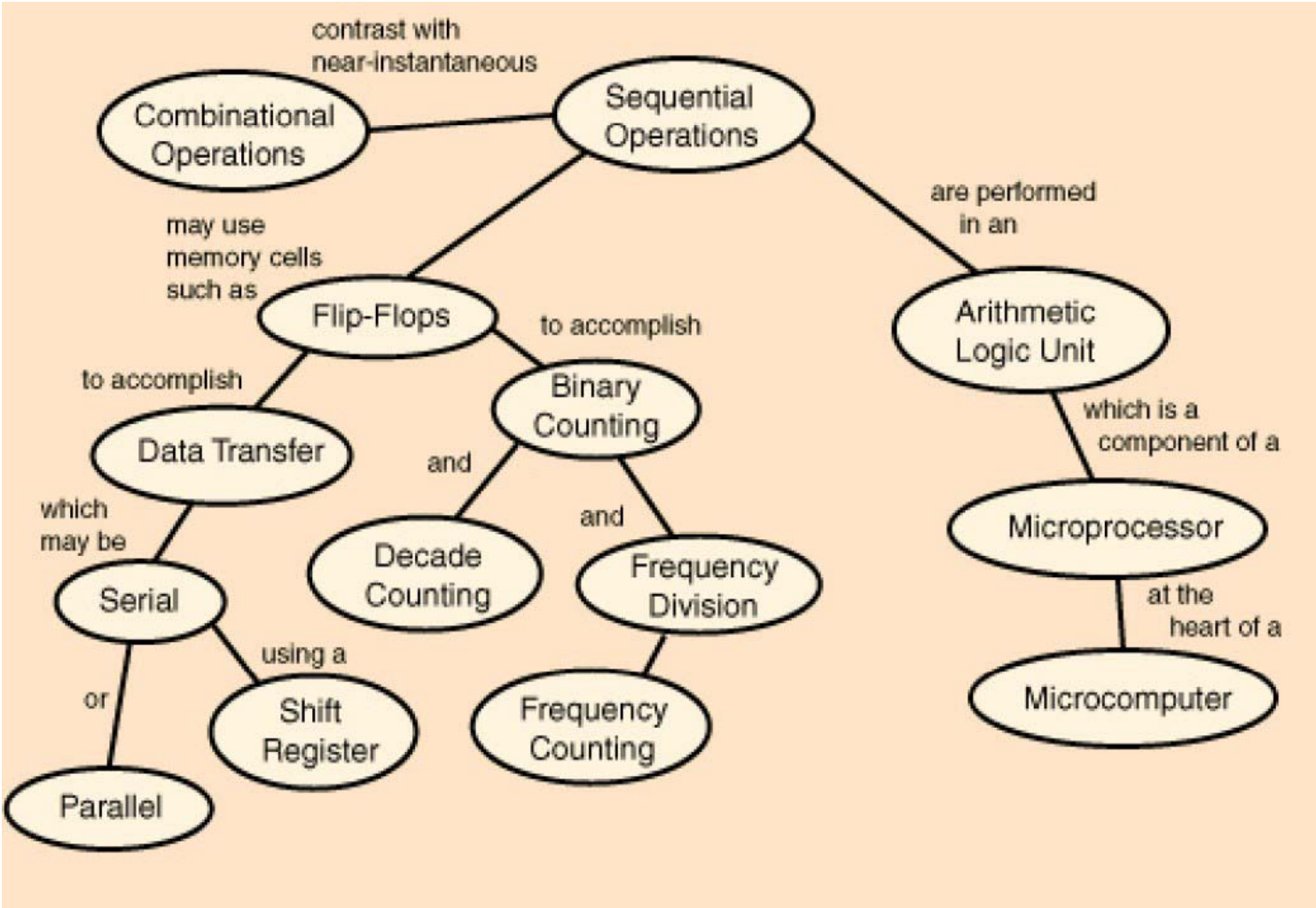

Sequential Circuit Construct


4

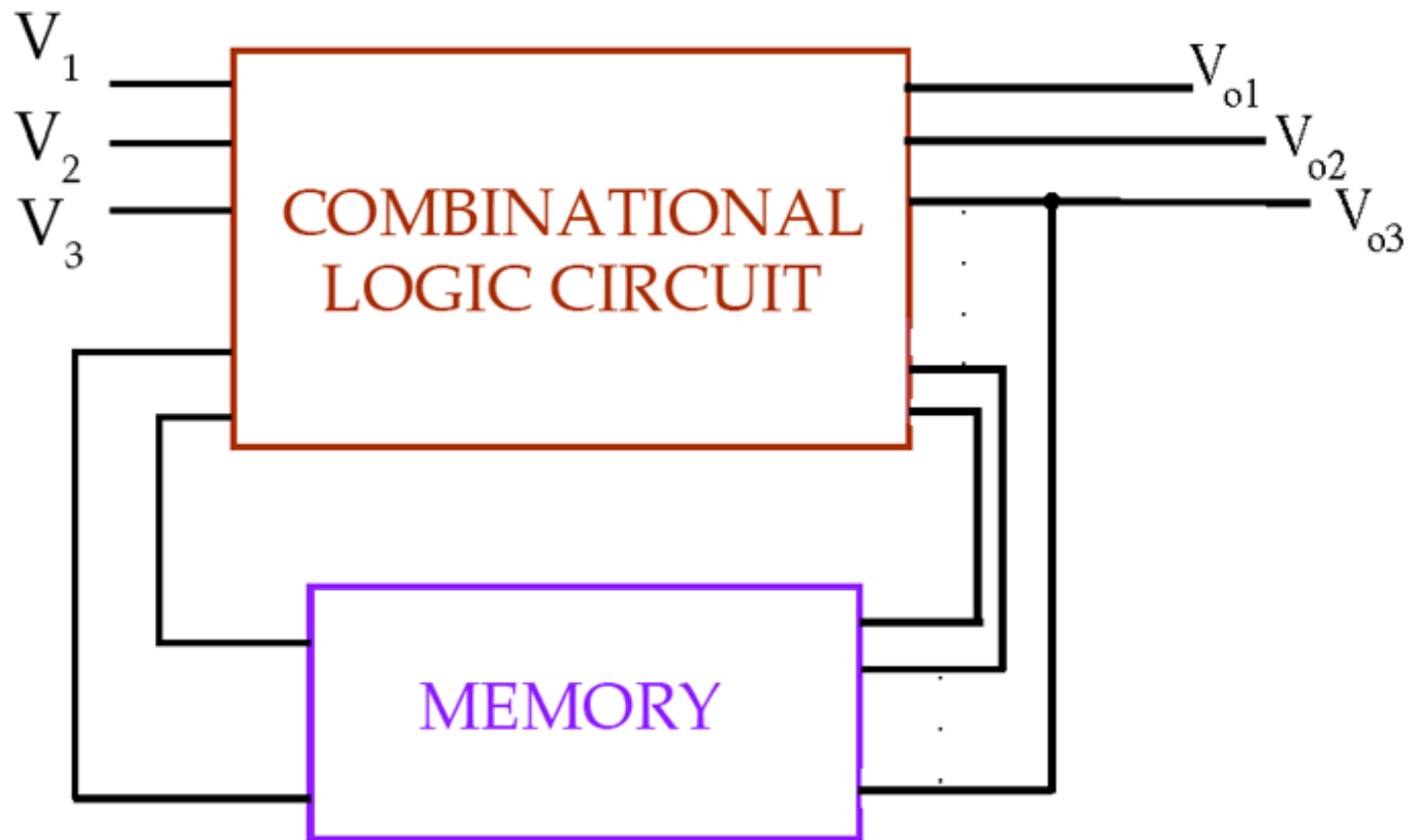


- > Sequential Circuits: Current Output(s) depend on Current Inputs and PAST inputs (via the feedback of some past State(s) and Output(s) to inputs).
- > Memory is used to Store Past Values of State(s) and Output(s).

Bistable Sequential Circuits

Basic Cross-coupled Inverter pair


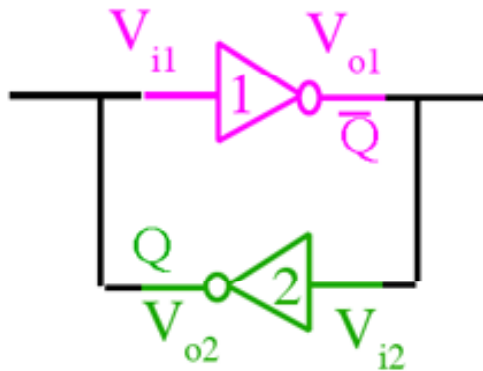


BISTABLE BEHAVIOR

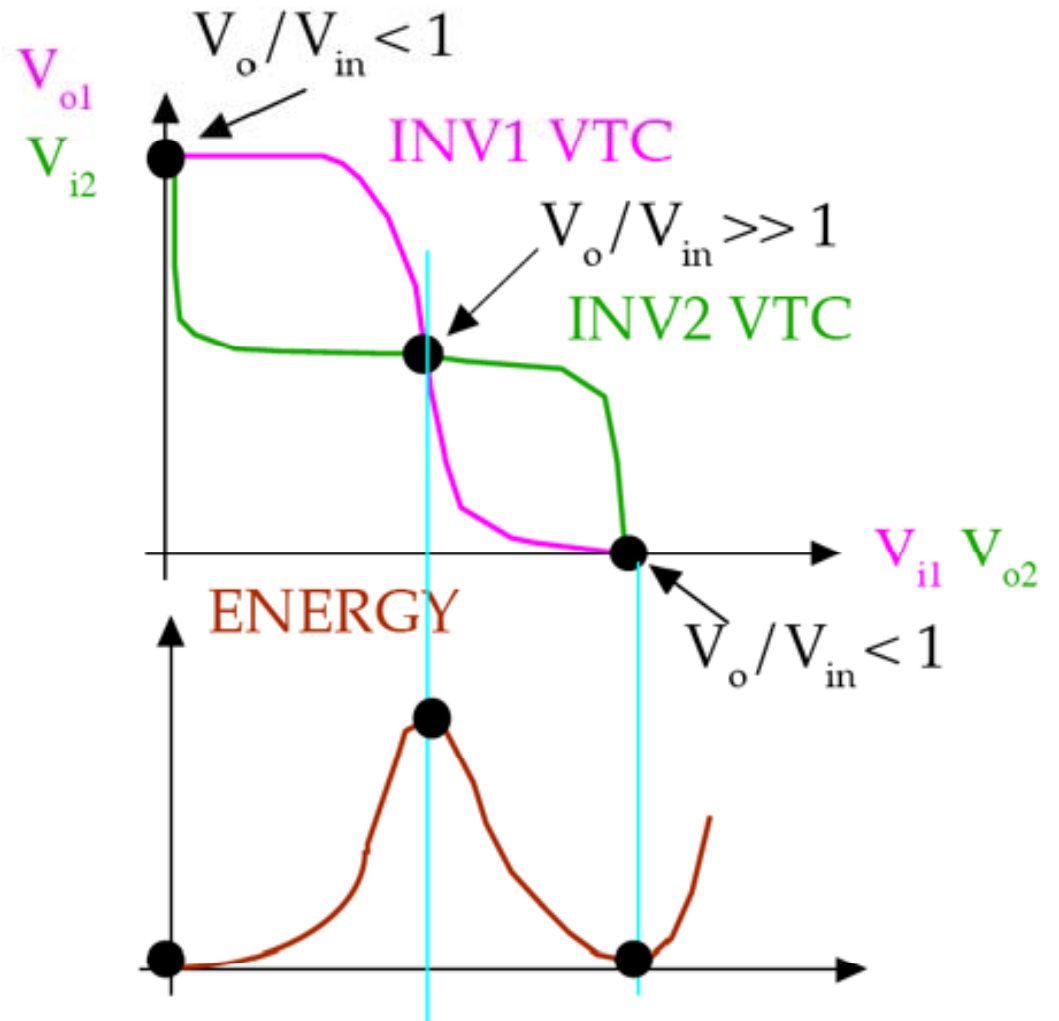

Bistable Sequential Circuits - cont.


6

 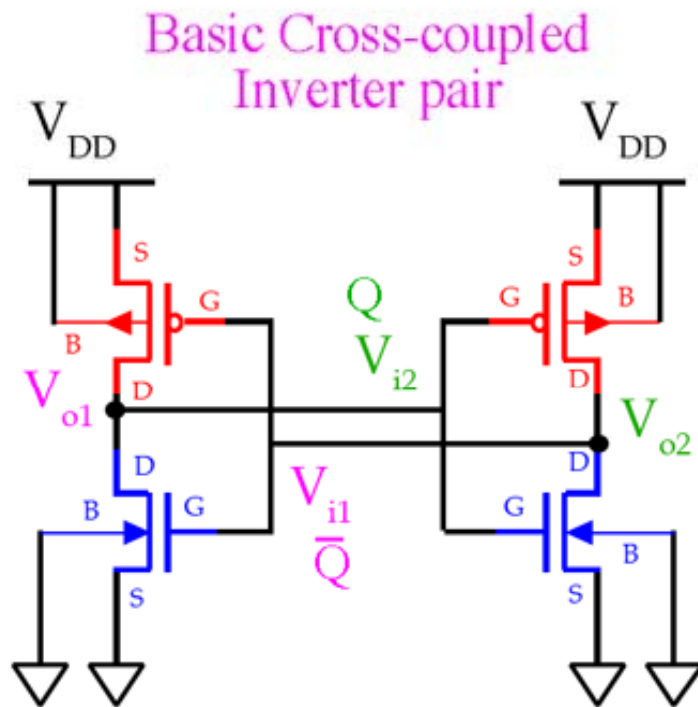

STATIC: V_{DD} is required to maintain stable state.

Basic Bistable Cross-coupled Inverter Pair has no means to apply input(s) to change the circuit's State.

Unclocked Latch Circuits

 

$t = t_1 > t = t_0$


S_{t_1}	R_{t_1}	Q_{t_1}	\bar{Q}_{t_1}	Operation
0	0	Q_n	\bar{Q}_n	hold
1	0	1	0	set*
0	1	0	1	reset*
1	1	0	0	NOT allowed

ACTIVE HIGH

*Data is written by over powering the feedback loop using S, R inputs.

Unlocked Latch Circuits


Full CMOS Asynchronous SR Latch

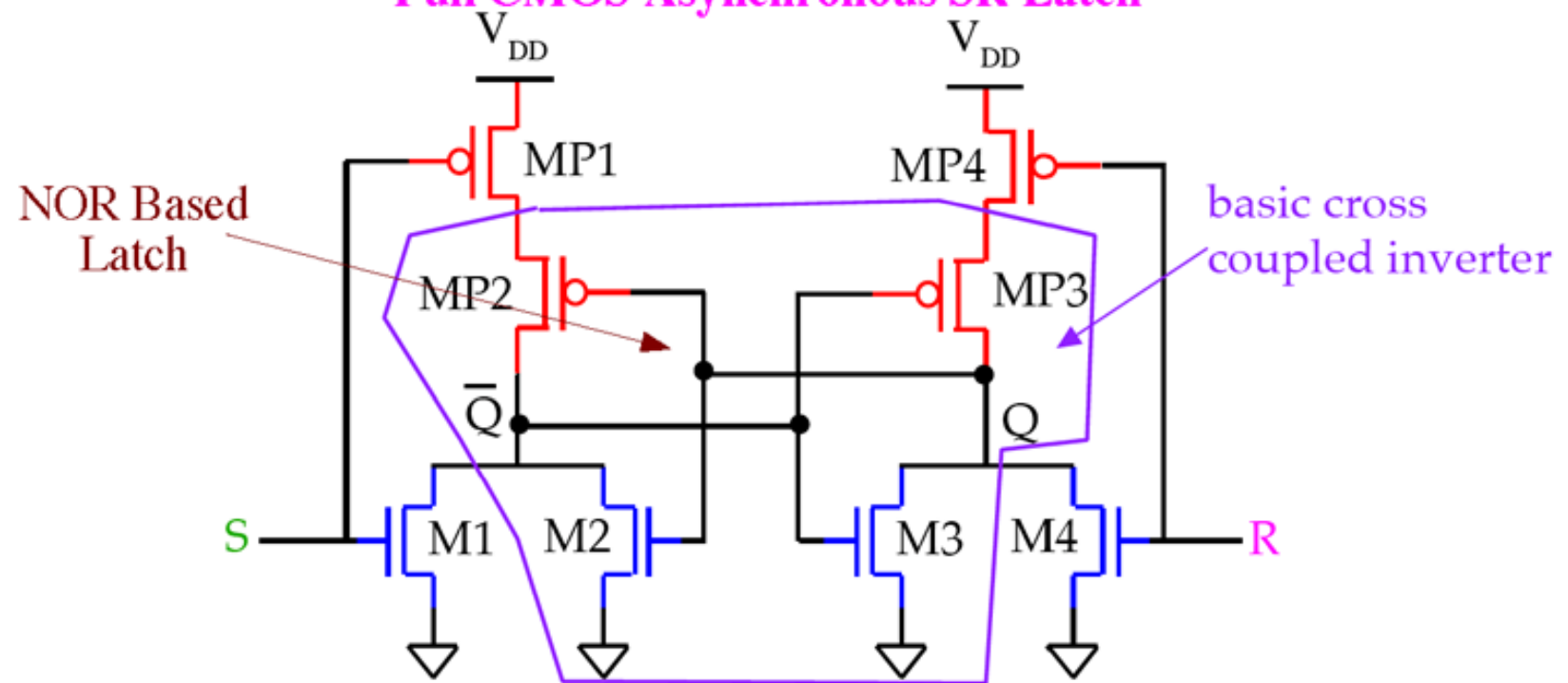

STATE OF LATCH can be EXTERNALLY SWITCHED between the 2 STABLE STATES

- SET STATE: $S_{t1} = 1, R_{t1} = 0 \Rightarrow Q_{t1} = 1, \bar{Q}_{t1} = 0$
 - RESET STATE: $S_{t1} = 0, R_{t1} = 1 \Rightarrow Q_{t1} = 0, \bar{Q}_{t1} = 1$
 - HOLD: $S_{t1} = 0, R_{t1} = 0 \Rightarrow Q_{t1} = Q_{t0}, \bar{Q}_{t1} = \bar{Q}_{t0}$
 (two cross-coupled Inverters)
 (M2, MP2 and M3, MP3)
- $t - t1 > t - t0$
- NOT ALLOWED: $S = 1, R = 1 \rightarrow$ state Q_{n+1}, \bar{Q}_{n+1} is indeterminate

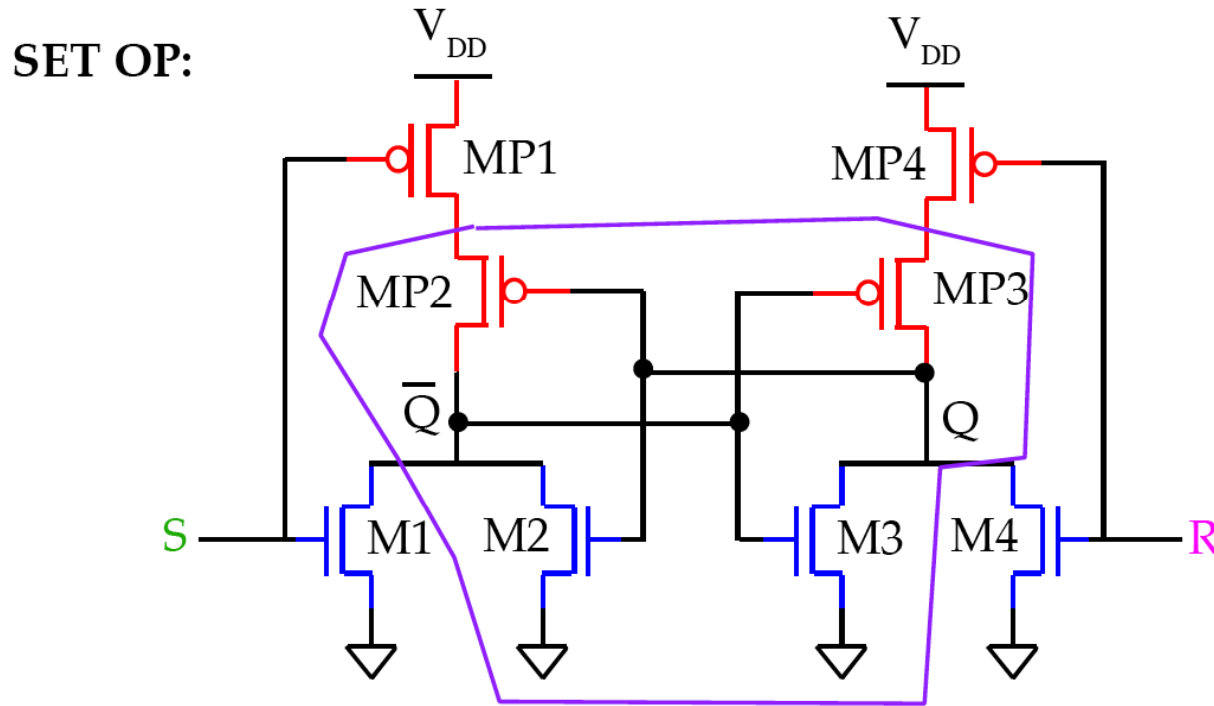Unclocked CMOS NOR Based SR Latch Operation



Let at $t = t_0$: $Q_{t_0} = 0, \bar{Q}_{t_0} = 1$


At $t = t_1 > t_0$

1. $S_{t_1} = V_{DD} \Rightarrow$ **M1 ON, MP1 OFF** $\Rightarrow \bar{Q}_{t_1} = 0$

2. $R_{t_1} = 0$ and $\bar{Q}_{t_1} = 0 \Rightarrow$ **M4 OFF, M3 OFF, MP3 ON, MP4 ON** $\Rightarrow Q_{t_1} = V_{DD}$

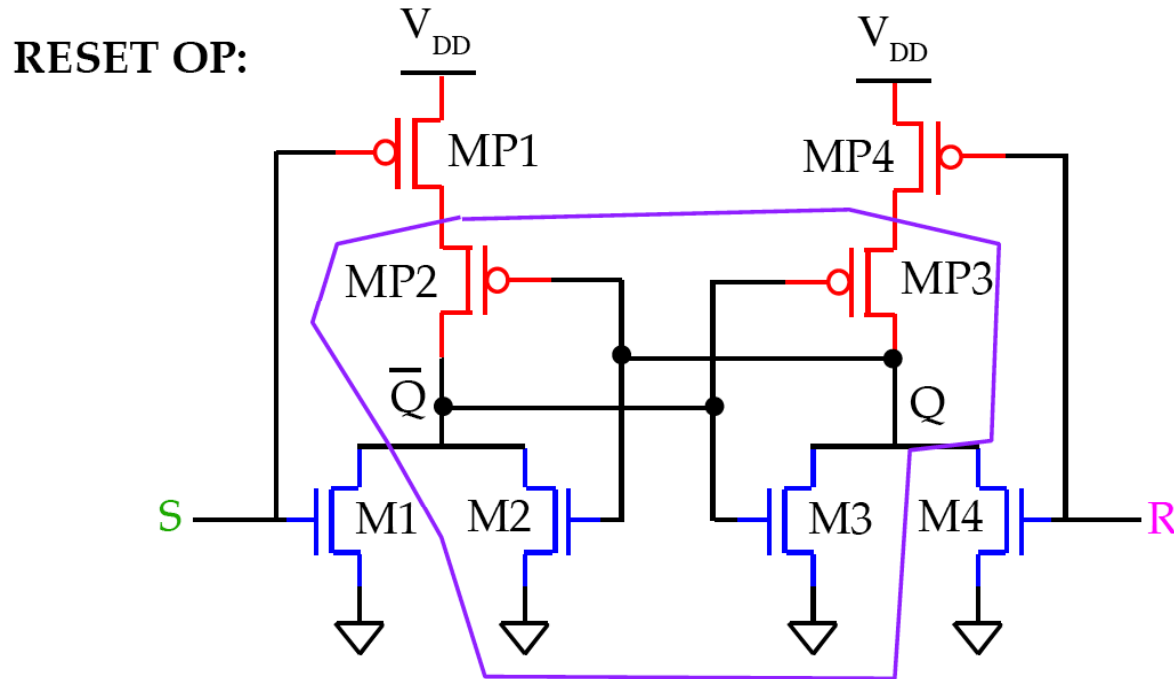3. $Q_{t_1} = V_{DD} \Rightarrow$ **M2 ON, MP2 OFF** $\Rightarrow \bar{Q}_{t_1} = 0$

Unclocked CMOS NOR Based SR Latch Operation - cont.




Let at $t = t_0$: $Q_{t_0} = 1, \bar{Q}_{t_0} = 0$

At $t = t_1 > t_0$

1. $R_{t_1} = 1 \Rightarrow M4 \text{ ON}, MP4 \text{ OFF} \Rightarrow Q_{t_1} = 0$
2. $S_{t_1} = 0$ and $Q_{t_1} = 0 \Rightarrow M1 \text{ OFF}, M2 \text{ OFF}, MP1 \text{ ON}, MP2 \text{ ON} \Rightarrow \bar{Q}_{t_1} = V_{DD}$
3. $\bar{Q}_{t_1} = V_{DD} \Rightarrow M3 \text{ ON}, MP3 \text{ OFF} \Rightarrow Q_{t_1} = 0$

Unclocked CMOS NOR Based SR Latch

Operation - cont.

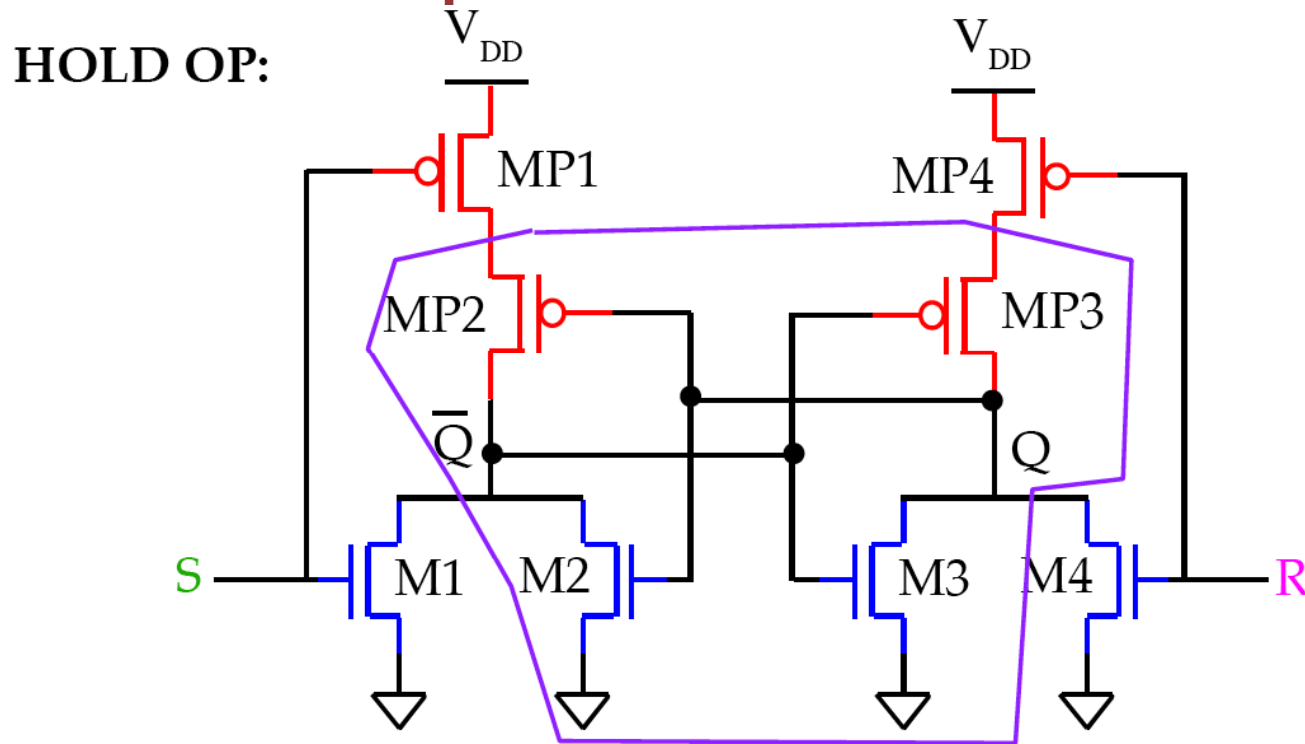

At $t = t_1 > t_0$


1. $S_{t_1} = 0 \Rightarrow M1 \text{ OFF, } MP1 \text{ ON; } R_{t_1} = 0 \Rightarrow M4 \text{ OFF, } MP4 \text{ ON}$

2a. $Q_{t_1} = Q_{t_0} = V_{DD}, \quad \bar{Q}_{t_1} = \bar{Q}_{t_0} = 0 \Rightarrow M2 \text{ ON, } MP2 \text{ OFF, } M3 \text{ OFF, } MP3 \text{ ON}$

or

2b. $Q_{t_1} = Q_{t_0} = 0, \quad \bar{Q}_{t_1} = \bar{Q}_{t_0} = V_{DD} \Rightarrow M2 \text{ OFF, } MP2 \text{ ON, } M3 \text{ ON, } MP3 \text{ OFF}$

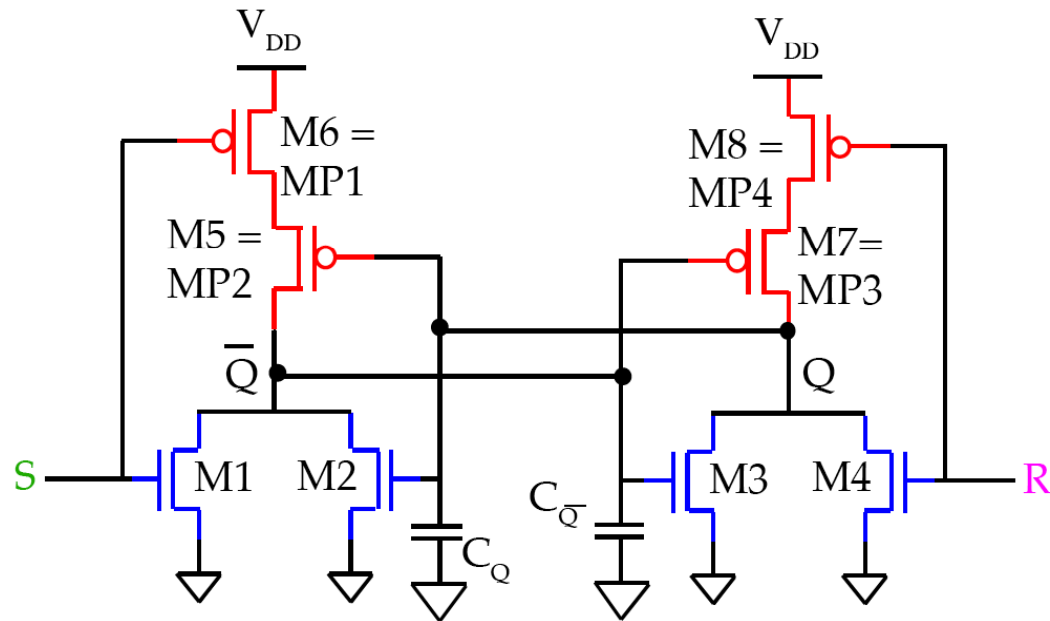Unclocked CMOS NOR Based SR Latch Operation - cont.



12

$$C_Q = C_{gb2} + C_{gb5} + C_{db3} + C_{db4} + C_{db7} + C_{sb7} + C_{db8}$$

$$C_{\bar{Q}} = C_{gb3} + C_{gb7} + C_{db1} + C_{db2} + C_{db5} + C_{sb5} + C_{db6}$$



Estimate time to simultaneously switch Q & \bar{Q} : **solution of two coupled differential equations.**

Conservative Estimate: Assume Q & \bar{Q} switch in sequence

$$\tau_{\text{rise},Q}(\text{SR-latch}) = \tau_{\text{rise},Q}(\text{NOR } 2) + \tau_{\text{fall},\bar{Q}}(\text{NOR } 2) \text{ at } t = 0: S \rightarrow 1, R \rightarrow 0$$

12

  Unclocked CMOS NAND Based SR Latch Circuit - cont



$t = t_1 > t = t_0$


S_{t_1}	R_{t_1}	Q_{t_1}	\bar{Q}_{t_1}	Operation
0	0	0	0	NOT allowed
0	1	1	0	set
1	0	0	1	reset
1	1	Q_{t_0}	\bar{Q}_{t_0}	hold

SR- Latches

- + Simplest form of latch
- Asynchronous
- Not Allowed Input Sequence

ASYNCHRONOUS NAND BASED SR LATCH

13

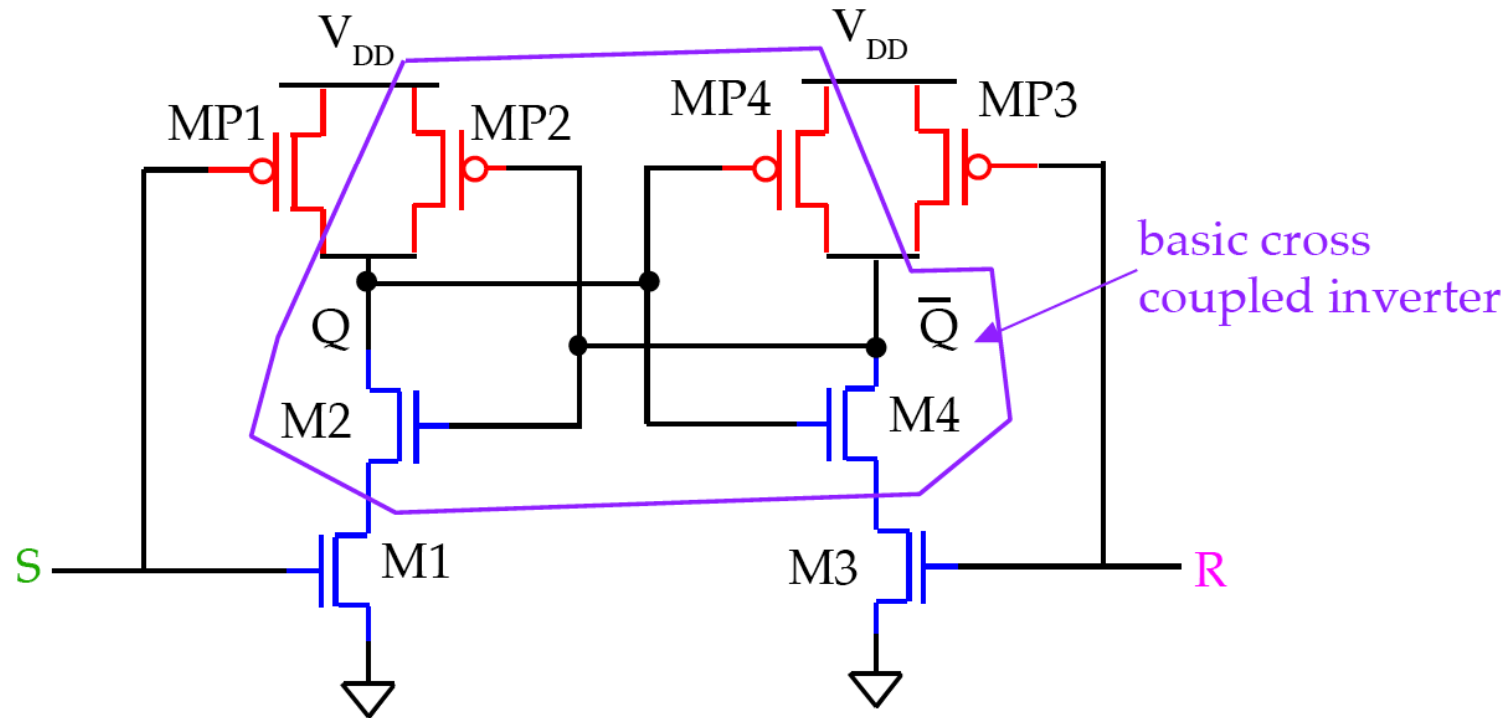

$t = t_1 > t = t_0$


S_{t1}	R_{t1}	Q_{t1}	\bar{Q}_{t1}	Operation
0	0	0	0	NOT allowed
0	1	1	0	set
1	0	0	1	reset
1	1	Q_{t0}	\bar{Q}_{t0}	hold

ACTIVE
LOW

Unclocked CMOS NAND Based SR Latch Circuit

ASYNCHRONOUS NAND BASED SR LATCH

13

 


$t = t_1 > t = t_0$

S_{t_1}	R_{t_1}	Q_{t_1}	\bar{Q}_{t_1}	Operation
0	0	0	0	NOT allowed
0	1	1	0	set
1	0	0	1	reset
1	1	Q_{t_0}	\bar{Q}_{t_0}	hold

ACTIVE LOW

Clocked CMOS Latch Circuits

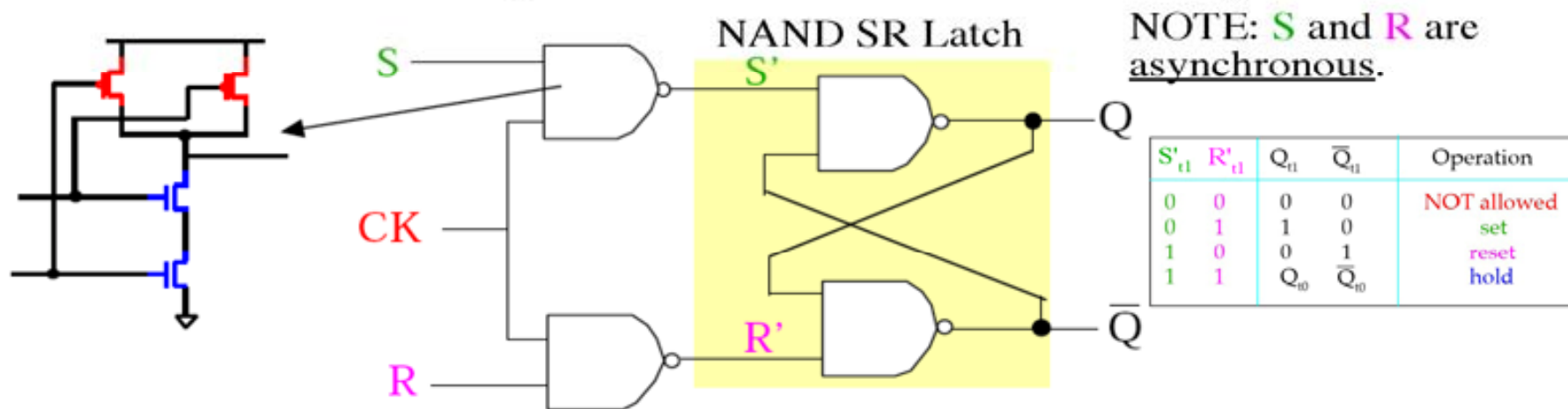CLOCKED SR LATCH: Synchronization is introduced through clock CK.



When $CK = 0$, $S' = R' = 1$ independent of the values of S and $R \Rightarrow$ **HOLD**

HOLD STATE: $CK = 0, S = x, R = x \Rightarrow Q_{n+1} = Q_n, \bar{Q}_{n+1} = \bar{Q}_n$

SET STATE: $CK = 1, S = 1, R = 0 \Rightarrow Q_{n+1} = 1, \bar{Q}_{n+1} = 0$


RESET STATE: $CK = 1, S = 0, R = 1 \Rightarrow Q_{n+1} = 0, \bar{Q}_{n+1} = 1$

NOT ALLOWED: $CK = 1, S = 1, R = 1 \Rightarrow S' = 0, R' = 0$

“ACTIVE HIGH”

Clocked CMOS Latch Circuits - cont.

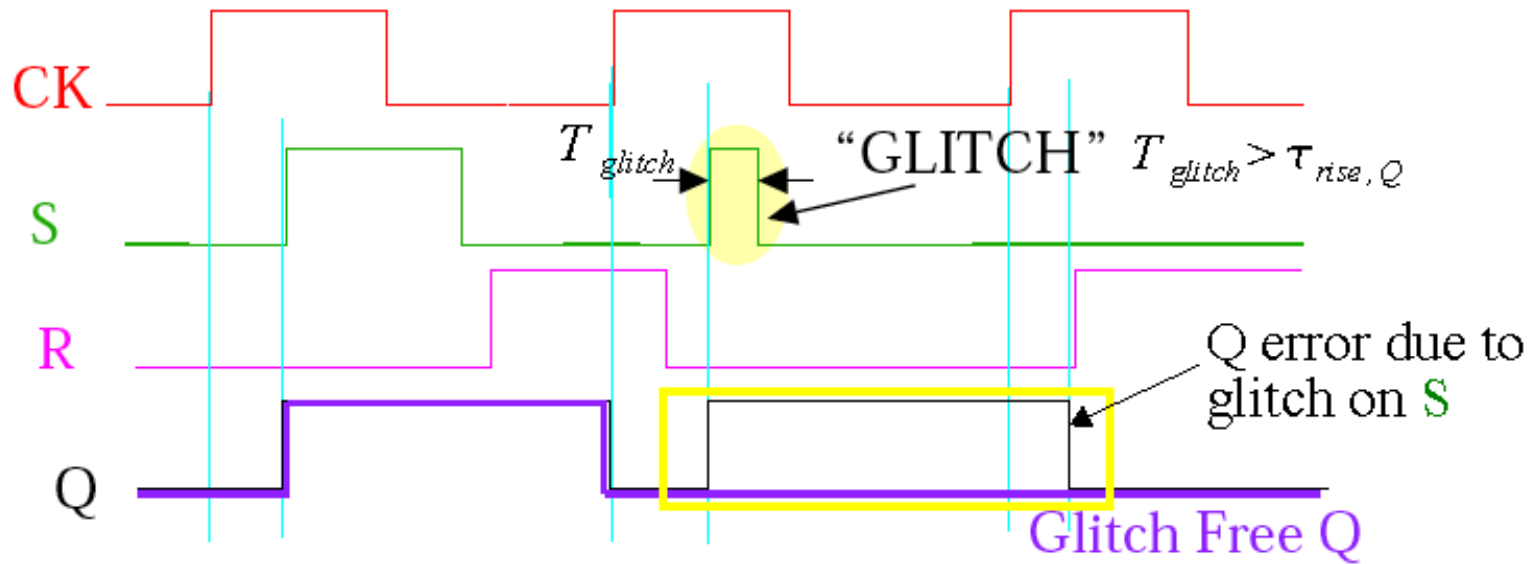HOLD STATE: $CK = 0, S = x, R = x \Rightarrow Q_{n+1} = Q_n, \bar{Q}_{n+1} = \bar{Q}_n$
SET STATE: $CK = 1, S = 1, R = 0 \Rightarrow Q_{n+1} = 1, \bar{Q}_{n+1} = 0$
RESET STATE: $CK = 1, S = 0, R = 1 \Rightarrow Q_{n+1} = 0, \bar{Q}_{n+1} = 1$
NOT ALLOWED: $CK = 1, S = 1, R = 1$




WHEN "GLITCH" ON S (OR R) OCCURS DURING $CK = 1$, Q IS SET (OR RESET)

LEVEL SENSITIVE: WHEN $CK = 1$, ANY CHANGES IN S, R WILL EFFECT Q.

Clocked CMOS Latch Circuits - cont.

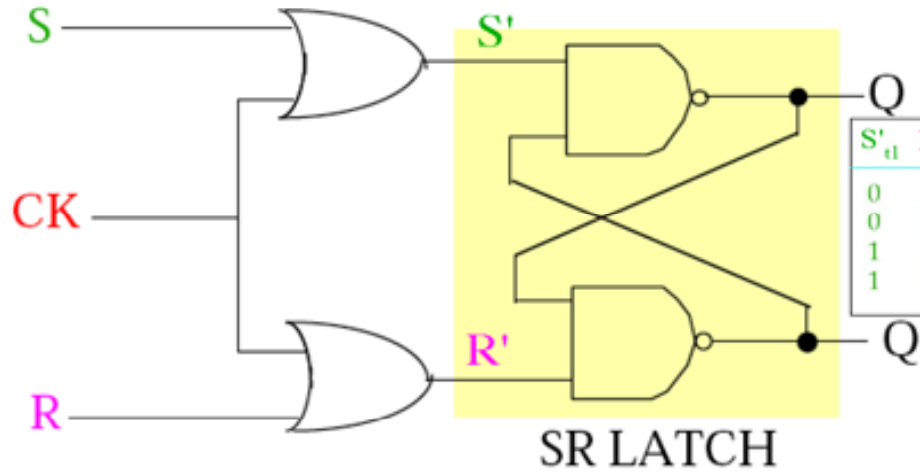Another Gate Level schematic of a Clocked NAND Based SR Latch



S'_{cl}	R'_{cl}	Q_{cl}	\bar{Q}_{cl}	Operation
0	0	0	0	NOT allowed
0	1	1	0	set
1	0	0	1	reset
1	1	Q_{n0}	\bar{Q}_{n0}	hold

When $CK = 1$, $S' = R' = 1$ independent of the values of S and $R \Rightarrow$ HOLD


“ACTIVE LOW”

CK	S	R	Q_{n+1}	\bar{Q}_{n+1}	Operation
0	0	0	0	0	NOT allowed
0	0	1	1	0	set
0	1	0	0	1	reset
1	x	x	Q_n	\bar{Q}_n	hold

$S' = R' = 0$

Clocked CMOS Latch Circuits - cont.

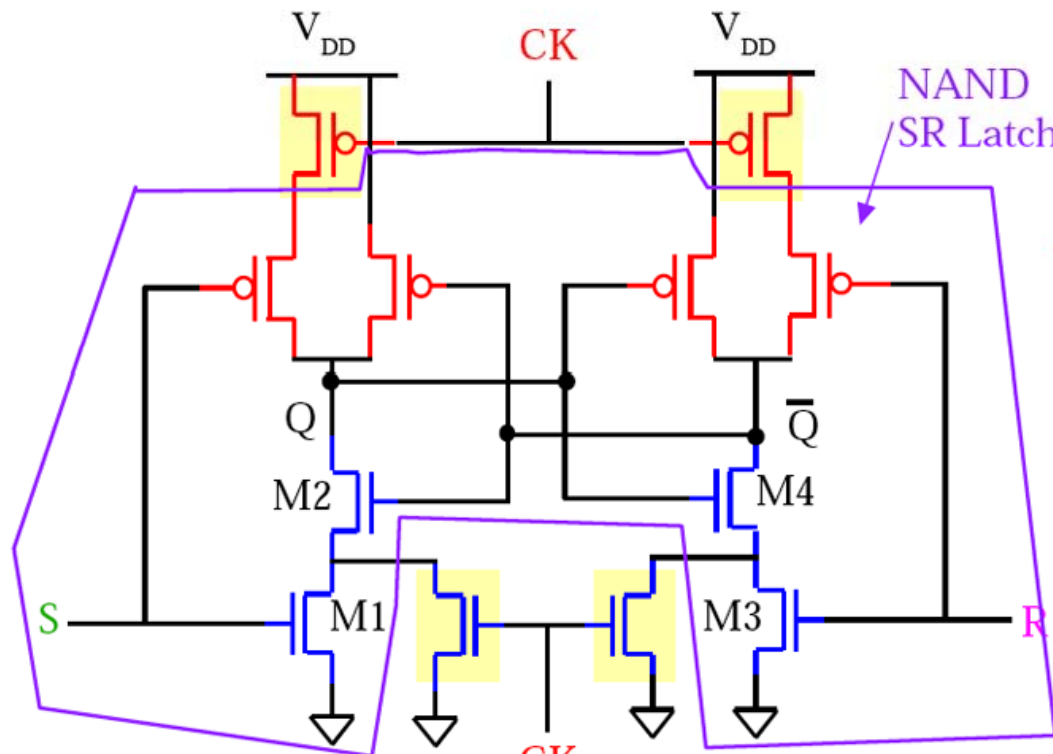CMOS Clocked NAND Based SR Latch or Flip-Flop




CK	S	R	Q_{n+1}	\bar{Q}_{n+1}	Operation
0	0	0	0	0	NOT allowed
0	0	1	1	0	set
0	1	0	0	1	reset
1	x	x	Q_n	\bar{Q}_n	hold


“ACTIVE LOW”

- + Synchronous operation CK
- Level Sensitive
- Not Allowed Input Sequence

CMOS Clocked Latch Circuits - cont.

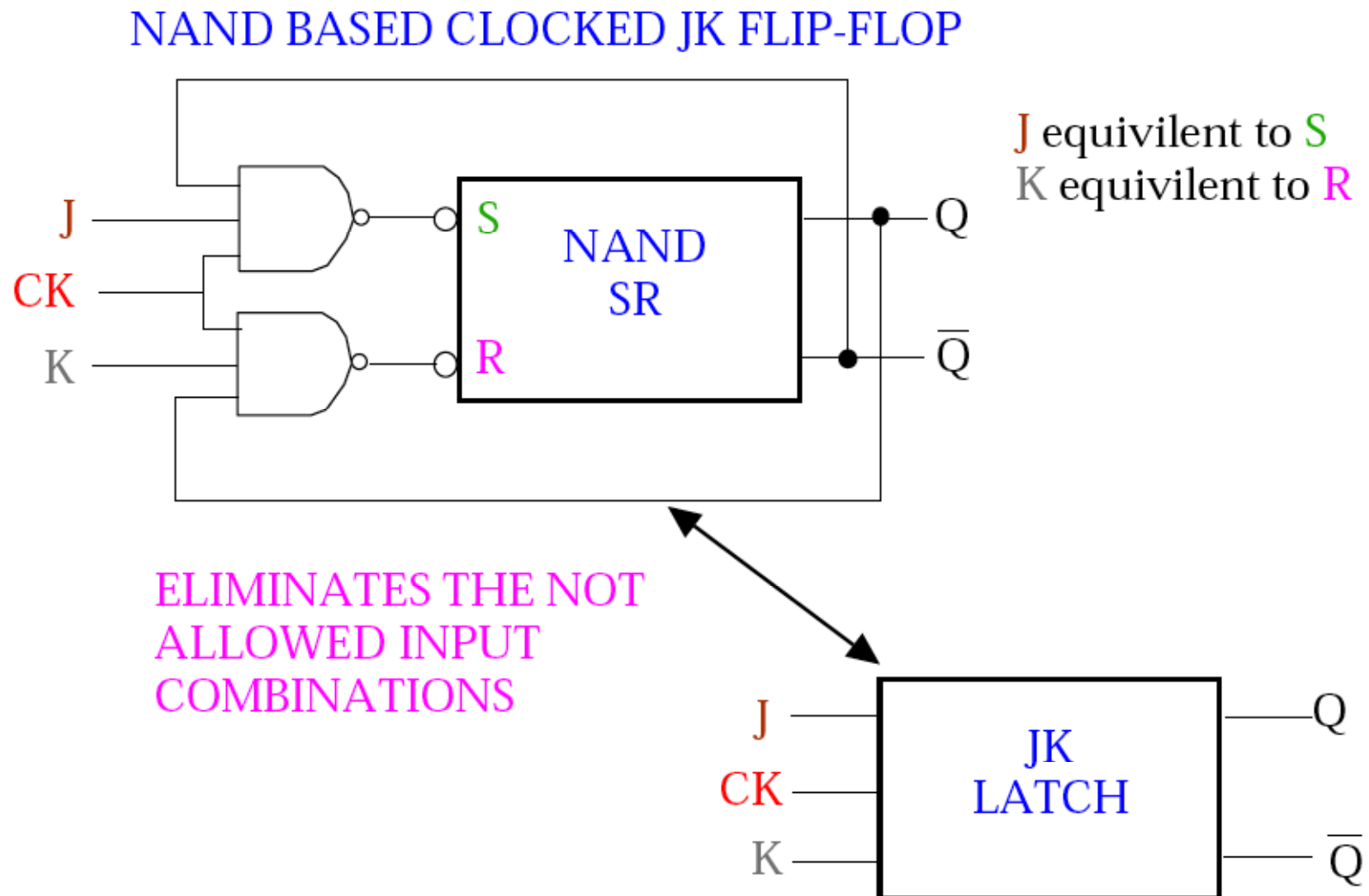

Clocked NAND Based JK Latch Operation

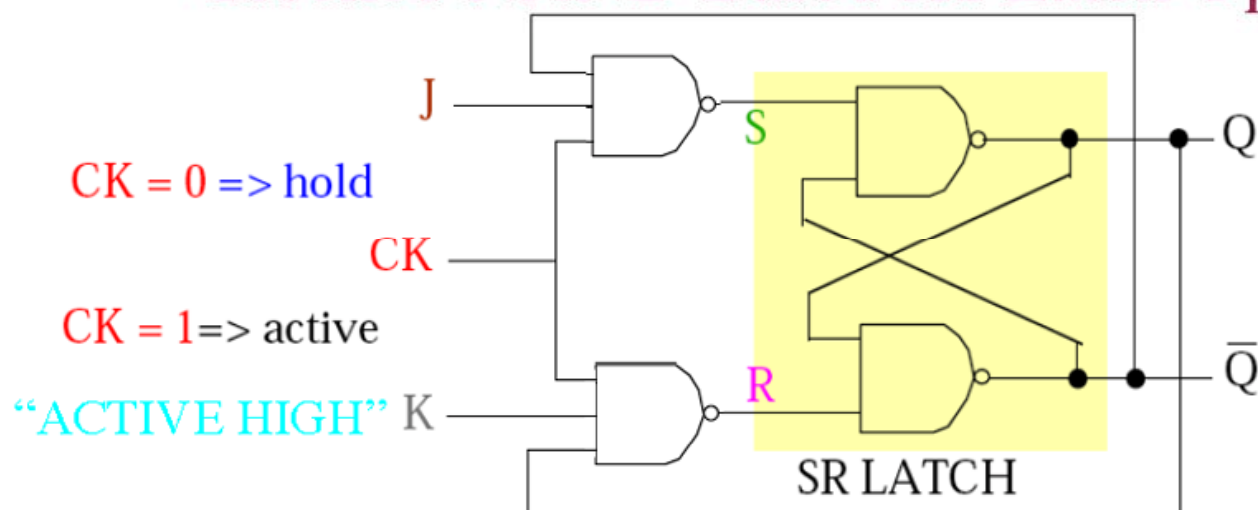

CK = 1

J	K	Q_n	\bar{Q}_n	S	R	Q_{n+1}	\bar{Q}_{n+1}	Operation
0	0	0	1	1	1	0	1	hold
0	0	1	0	1	1	1	0	hold
0	1	0	1	1	1	0	1	reset (hold)
0	1	1	0	1	0	0	1	reset
1	0	0	1	0	1	1	0	set
1	0	1	0	1	1	1	0	set (hold)
1	1	0	1	0	1	1	0	toggle
1	1	1	0	1	0	0	1	toggle

The not-allowed S, R values $S = R = 0$ do not occur for any values of J, K, CK.

OSC → not desirable, but the state Q_{n+1}, \bar{Q}_{n+1} is determinate


Clocked NAND Based JK Latch Operation

J	K	Q_n	\bar{Q}_n	S	R	Q_{n+1}	\bar{Q}_{n+1}	Operation
0	0	0	1	1	1	0	1	hold
0	0	1	0	1	1	1	0	hold
0	1	0	1	1	1	0	1	reset
0	1	1	0	1	0	0	1	reset
1	0	0	1	0	1	1	0	set
1	0	1	0	1	1	1	0	set
1	1	0	1	0	1	1	0	toggle
1	1	1	0	1	0	0	1	toggle

CK = 1

OSC

TO PREVENT OSCILLATION WHEN $J = K = 1$:

 


(high speed clock may be impractical)

τ_{JKP} = INPUT-OUTPUT PROP DELAY OF JK LATCH
 (CK 1 \rightarrow 0 BEFORE Q, \bar{Q} CAN SWITCH 2nd TIME)

CLOCKED SR FLIP FLOP: Negative Edge Triggered.

19

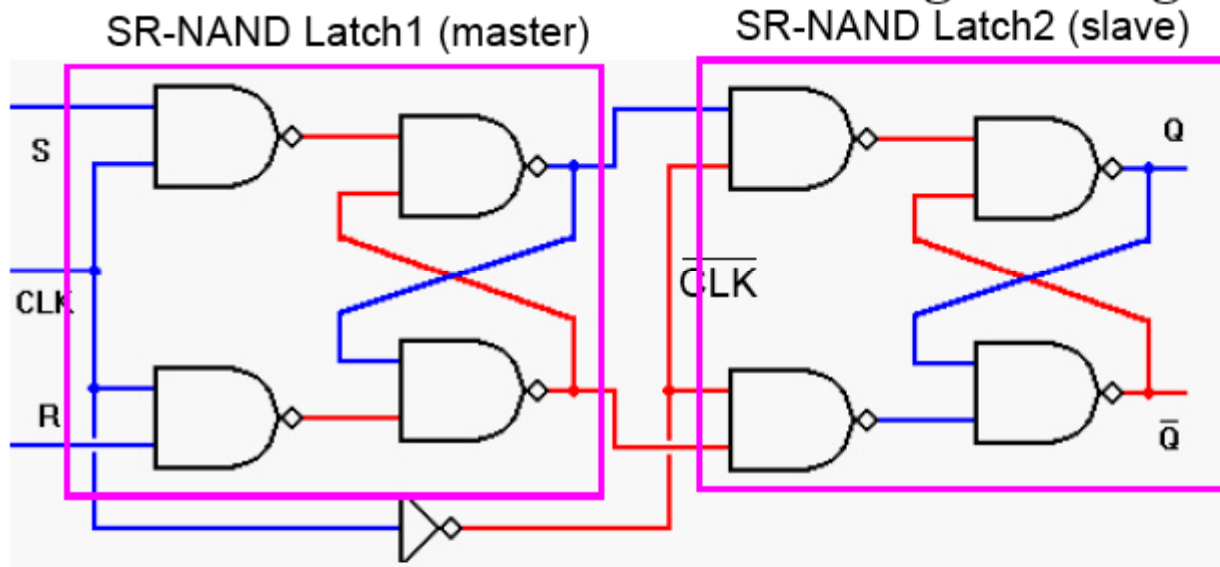

- + Synchronous operation
- + Not Level Sensitive
- Not Allowed S, R Sequence

- Start with $CLK = 0$, the S, R inputs are disconnected from the input Latch1.
- Changes in S, R cannot affect the state of Q, \bar{Q} .


When $CLK = 1$, S, R are able to control the state of Latch1.

- Inverted CLK applied to Latch2 prevents the state of Latch1 from effecting Q, \bar{Q} .
- Any changes to R, S are tracked by Latch1 while $CLK = 1$, but not reflected at Q, \bar{Q} .

When $CLK = 0$, S, R are again isolated from Latch1.

- Inverted CLK allows the current state of Latch1 to reach Latch2.
- Q, \bar{Q} can only change state when the CLK signal falls from 1 to 0.
- This is the falling (negative) edge of the CLK signal.

CLOCKED EDGE TRIGGERED JK FLIP-FLOP

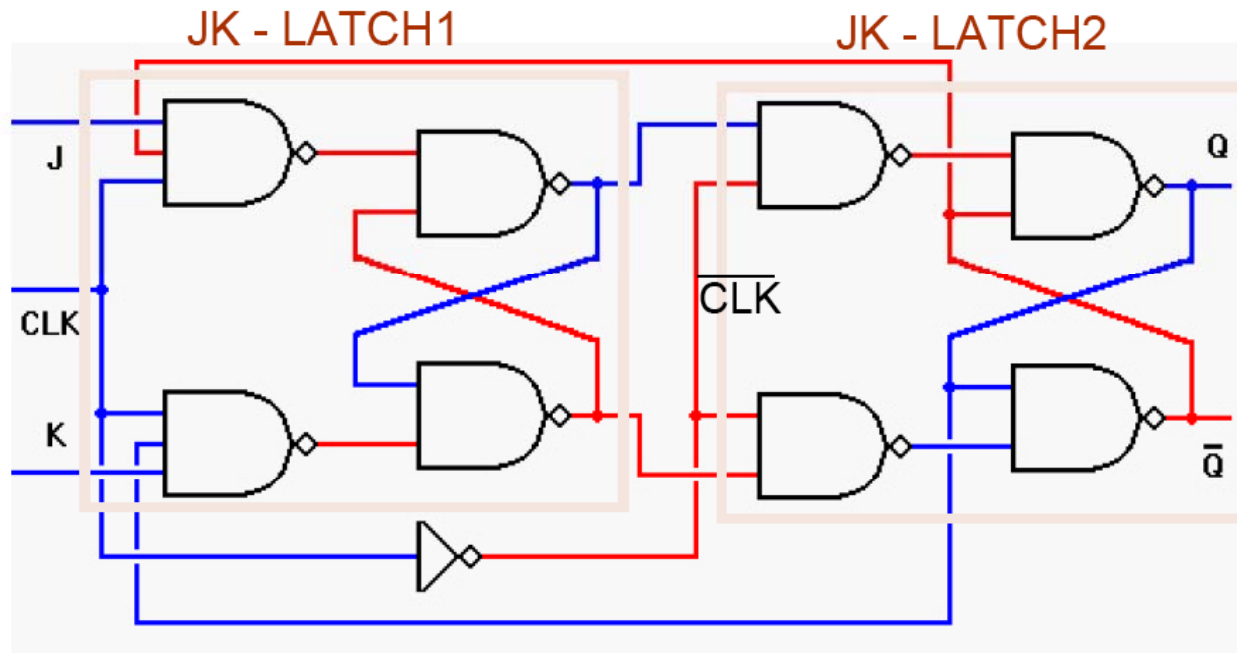


- + Synchronous Operation
- + No Not-Allowed Inputs
- + Not Level Sensitive
- + No Q , \bar{Q} Oscillation when $J = K = 1$

Since the behavior of the JK flip-flop is completely predictable under all conditions, it is the preferred type of flip-flop for most logic circuit designs.


CMOS D-Latch

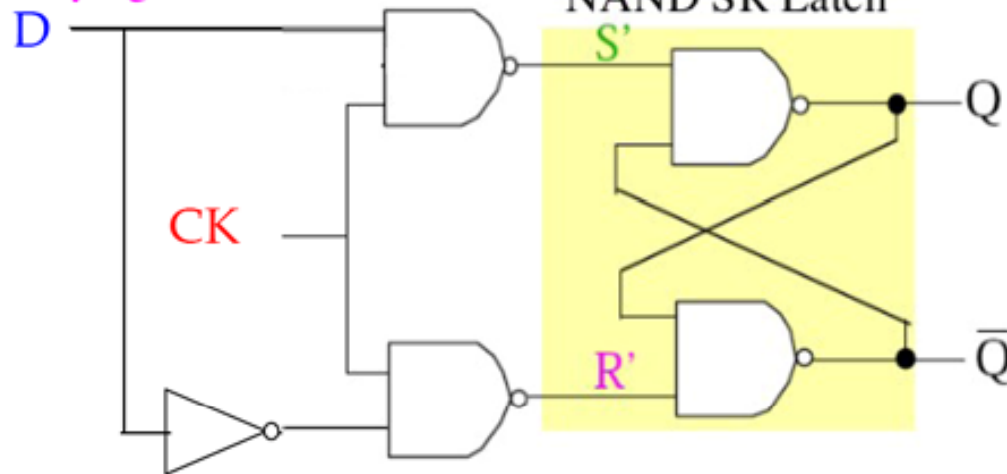gate level implementation
modifying an SR latch




CK	D	S'	R'	Q_{n+1}	Q_{n+1}	
1	1	0	1	1	0	SR-Set
1	0	1	0	0	1	SR-Reset
0	x	0	0	Q_n	Q_n	SR-Hold

 If CK = 1: $Q_{n+1} = D$
 If CK = 0: $Q_{n+1} = Q_n$




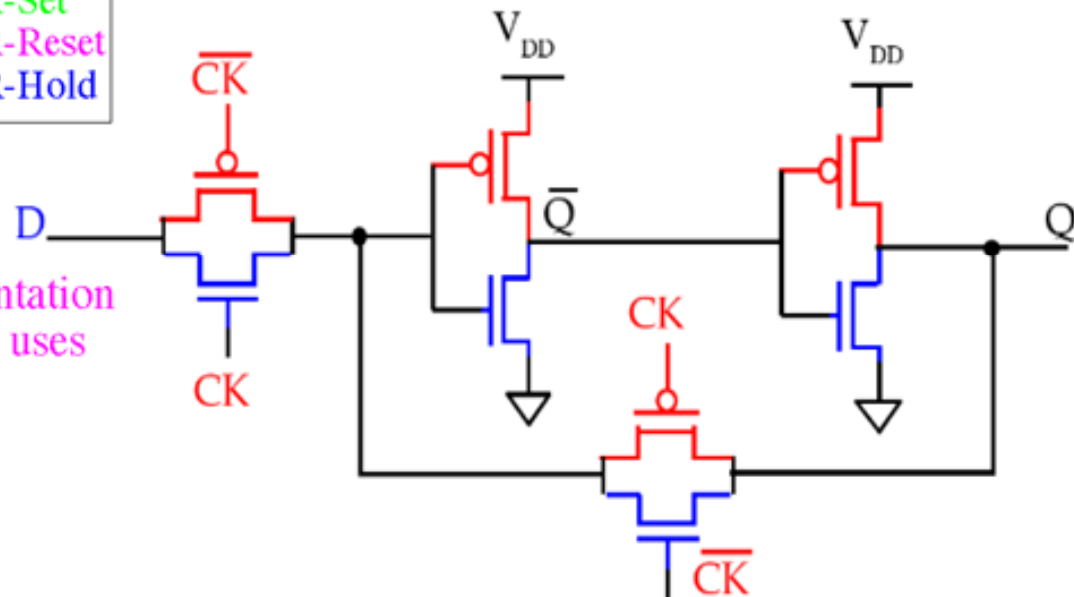transistor level implementation
using transmission gates uses
fewer transistors



CMOS D-Latch Operation


25

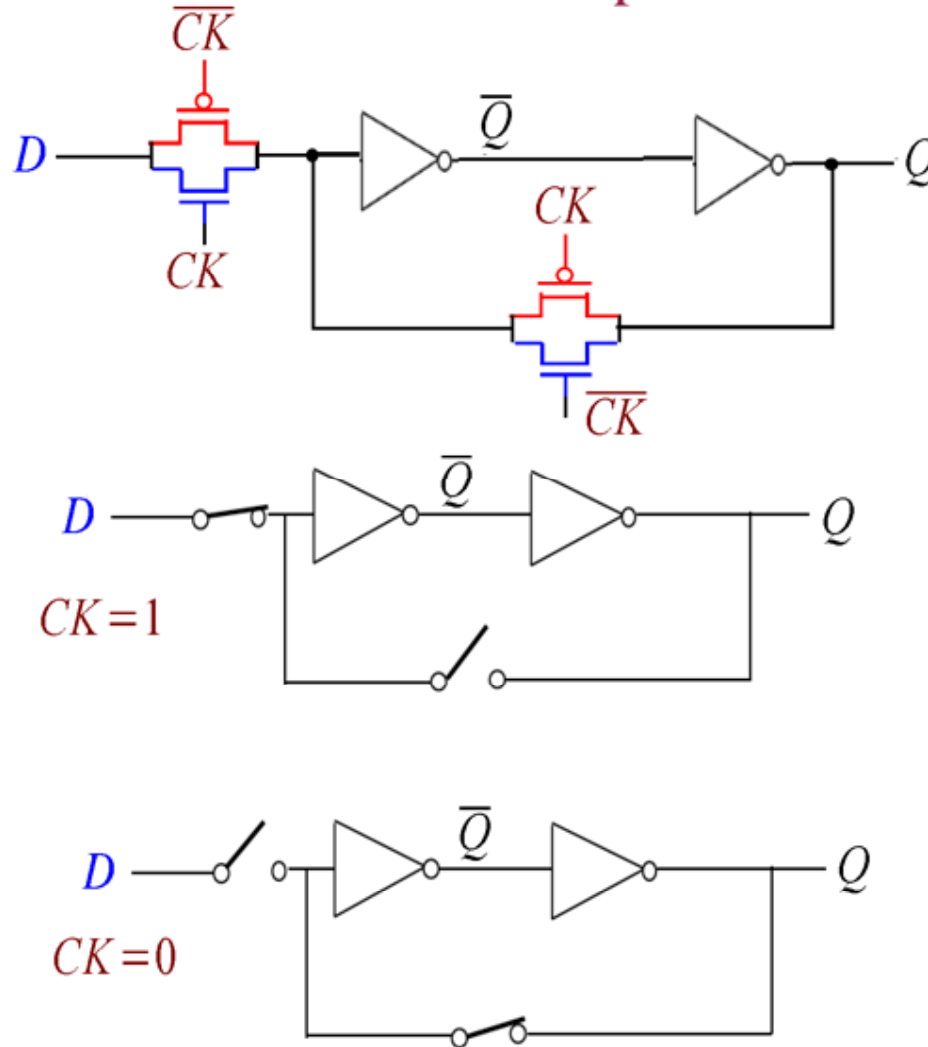

- + Much simpler than JK Latch.
- + Does not require Edge Triggering for Safe Operation.

CMOS D-Latch - cont.

26

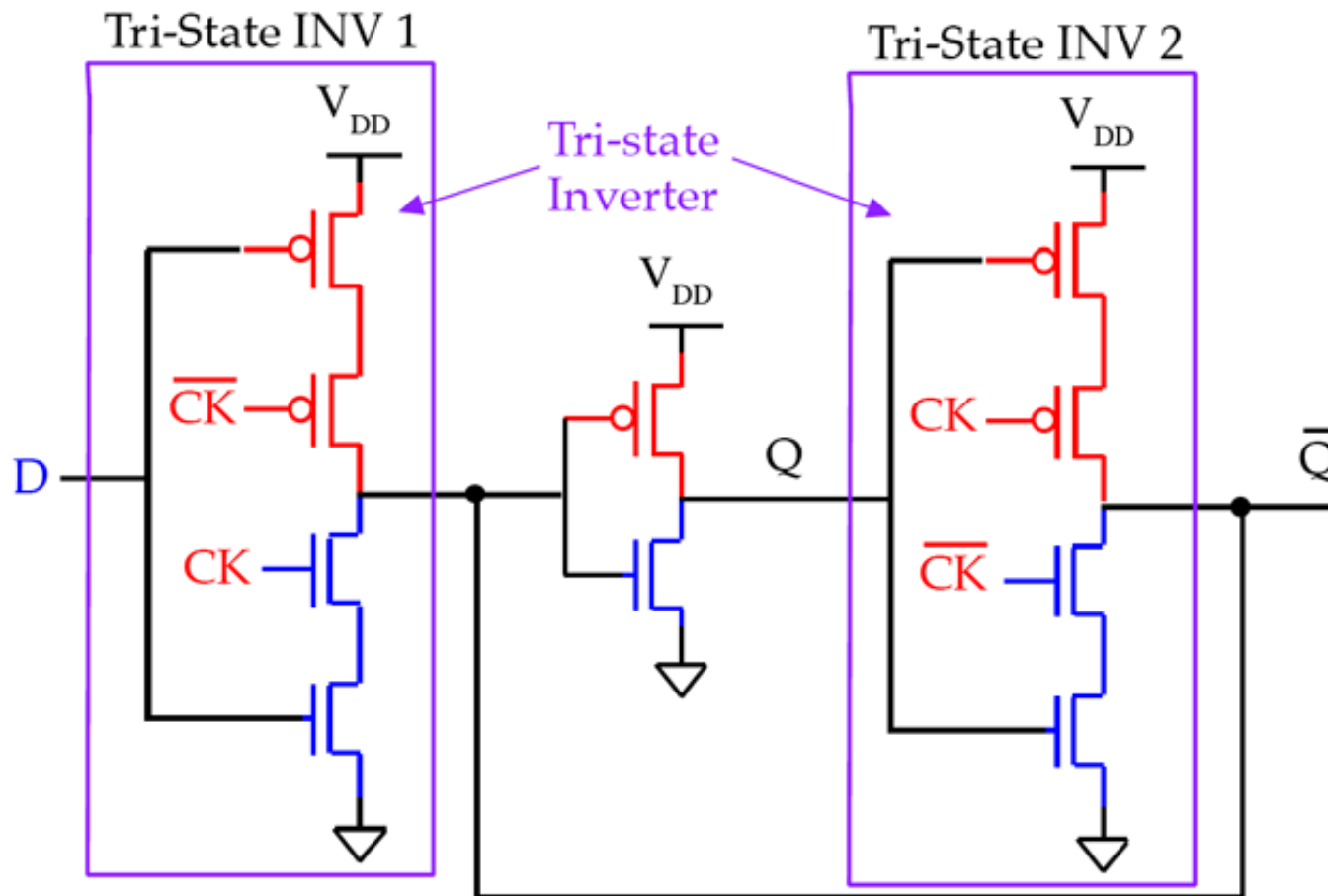


alternative implementation using clocked tri-state inverters

- $CK = 1$: Tri-state INV 1 is active, Tri-state INV 2 is Hi-Z and $Q_n = D_n$
- $CK = 0$: Tri-state INV 1 is Hi-Z, Tri-state INV 2 is active and Q_n and \overline{Q}_n are held

D-Latch Timing Requirements

28

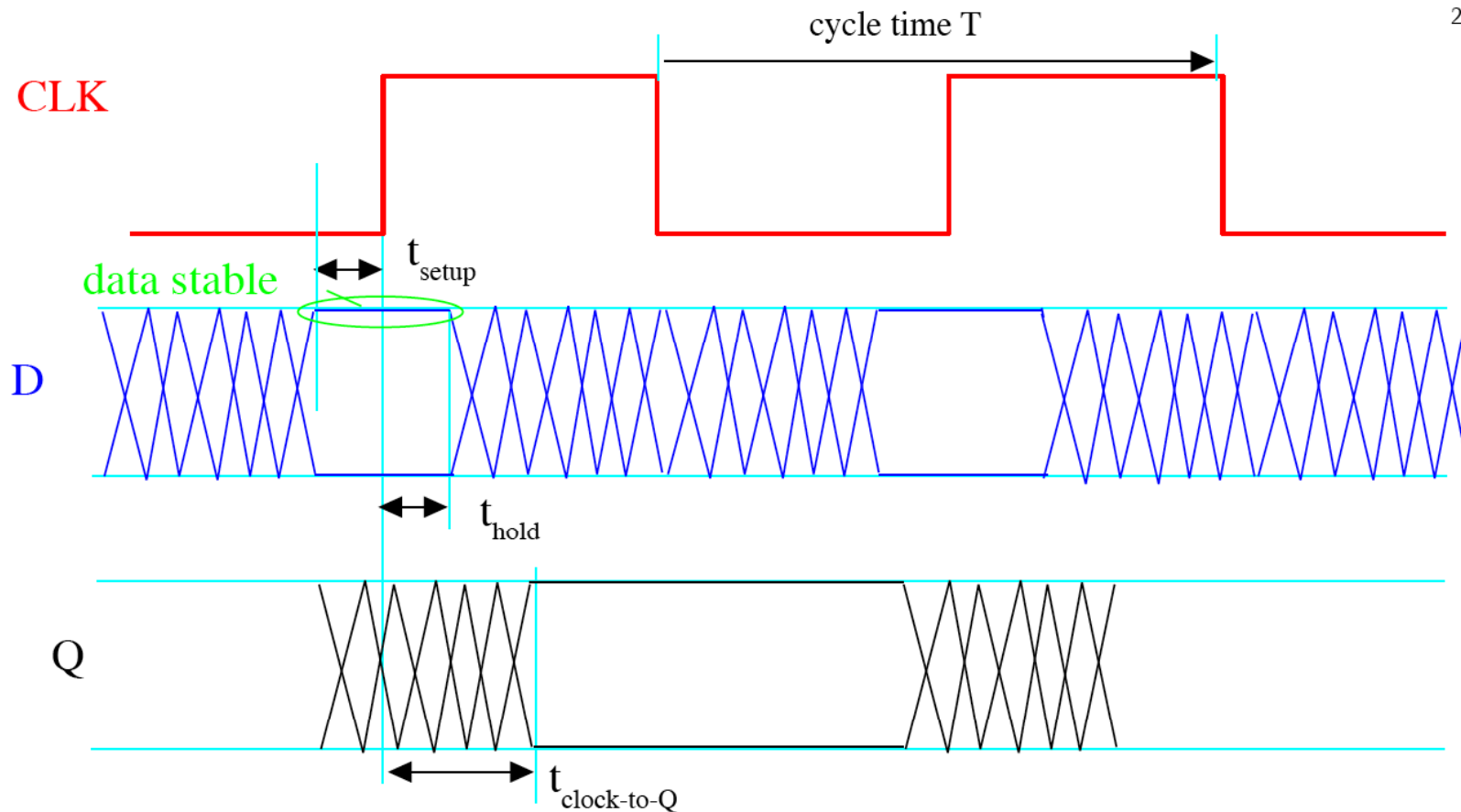

t_{setup} - time before the POS(neg)-CLK edge the D-input has to be stable.

t_{hold} - time after POS(neg)-CLK edge that the D-input has to remain stable.

$t_{\text{clock-to-Q}}$ - Delay from the POS(neg)-CLK edge to new stable value of Q output.

28


METASTABILITY AND SYNCHRONIZATION FAILURES

29

If **data and clock do not satisfy the setup & hold time constraints** of a register, then **synchronization failure may occur**. This due to **inherent analog nature** of storage elements.

METASTABLE STATE - **indeterminate state** between "1" & "0", i.e. latch is perfectly balanced between making decision for "1" or "0". In practice noise will eventually **arbitrarily push latch output** to "0" or "1".

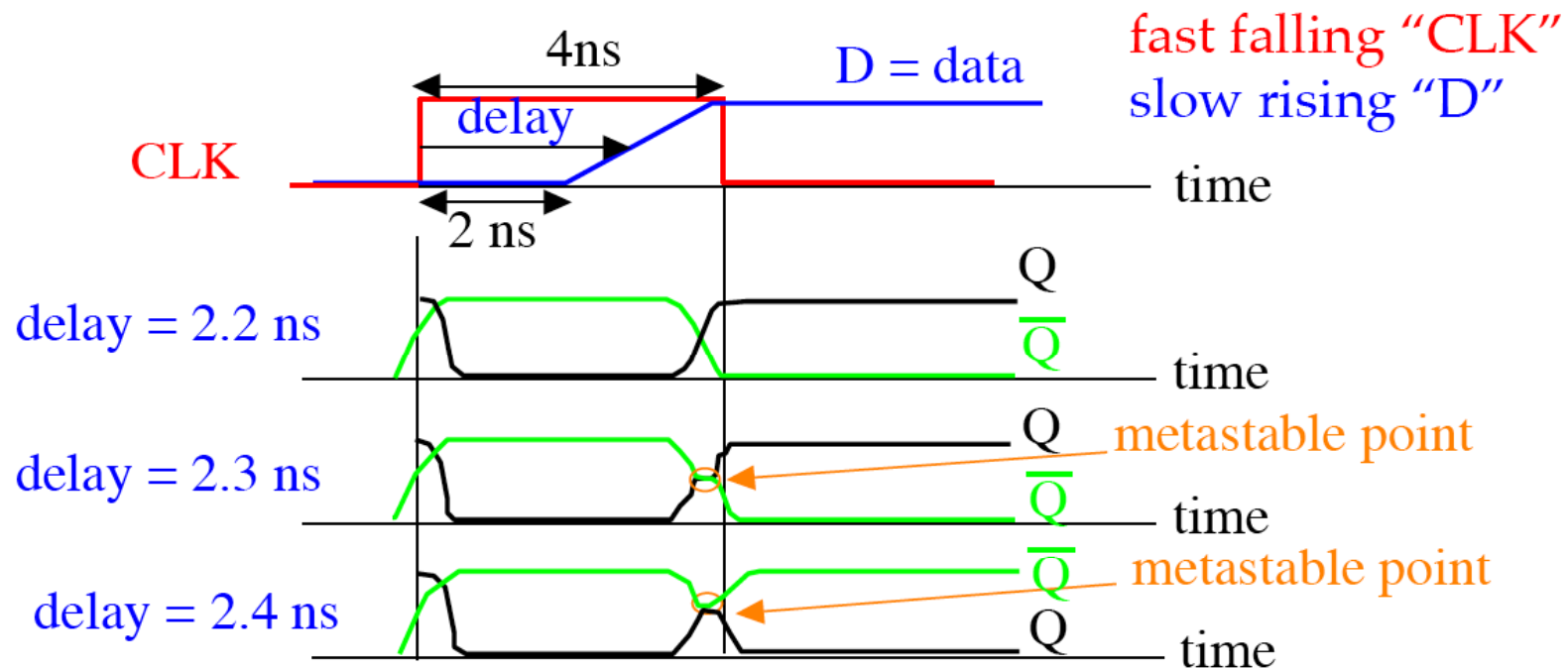Example: register entering metastable state (shown for negative edge trigger case)






29




CMOS D Flip-Flop

29

Positive D - Latch

   


Negative D - Latch

   


D Flip-Flop = Positive D-Latch + Negative D-Latch

CMOS D Flip-Flop – Positive Edge Triggered


30

 

FOR CLK = 0

 


FOR CLK = 1

 

1. **CLK = 0**: master Q_m tracks input D ; slave $Q_s = \text{previous } D_{n-1}$ sample (Q_s is transparent to variations in D).
2. **CLK = 0 \rightarrow 1**: master stores $Q_m = D_n$ (new D sample).
3. **CLK = 1**: master passes $Q_m = D_n$ to slave output Q_s (Q_m and Q_s are transparent to variations in D).
4. **CLK = 1 \rightarrow 0**: slave locks in new D_n .
5. **CLK = 0**: master Q_m begins tracking D . (Q_s is transparent to variations in D)
6. **CLK = 0 \rightarrow 1**: master stores $Q_m = D_{n+1}$.

CMOS Dynamic D Flip-Flop

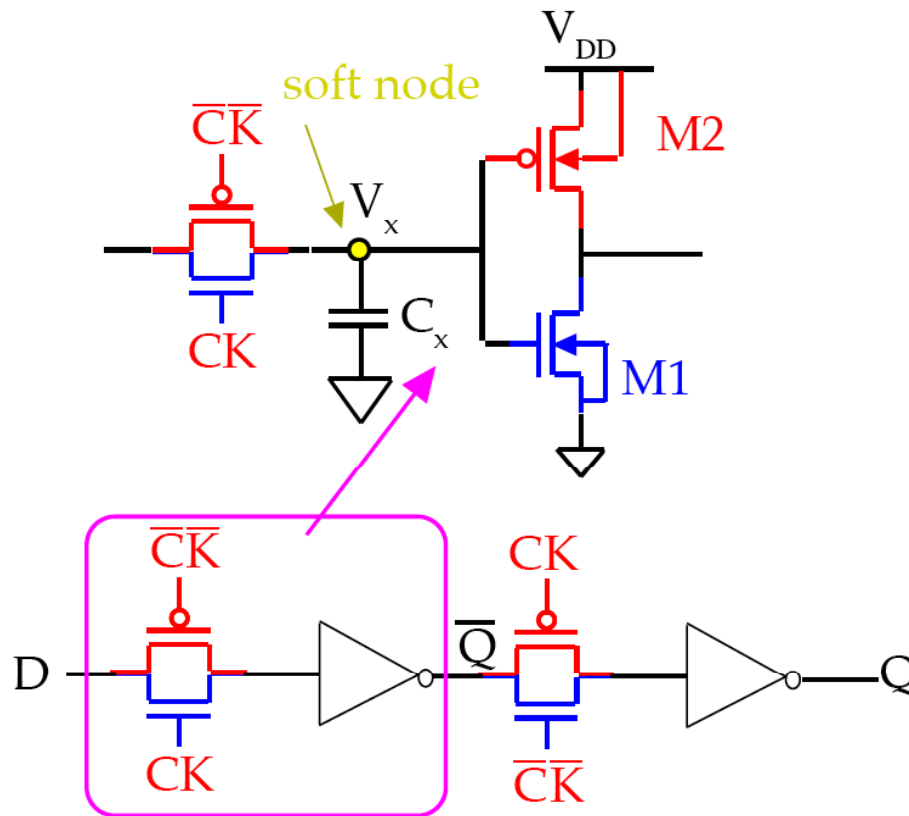

1. NO FEEDBACK REGENERATIVE FEEDBACK LOOP
2. STATES STORED ON SOFT NODES