

CMOS Digital Integrated Circuits



Lec 7

CMOS Inverters: Dynamic Analysis and Design



CMOS Inverters – Dynamic Analysis and Design


■ Goals

- Understand the detail dynamic analysis of the CMOS inverter.
- Understand one set of design form CMOS equations.
- Understand the basic CMOS design process using the CMOS static and CMOS design form dynamic equations.



CMOS Dynamic Analysis

Capacitance Model for CMOS

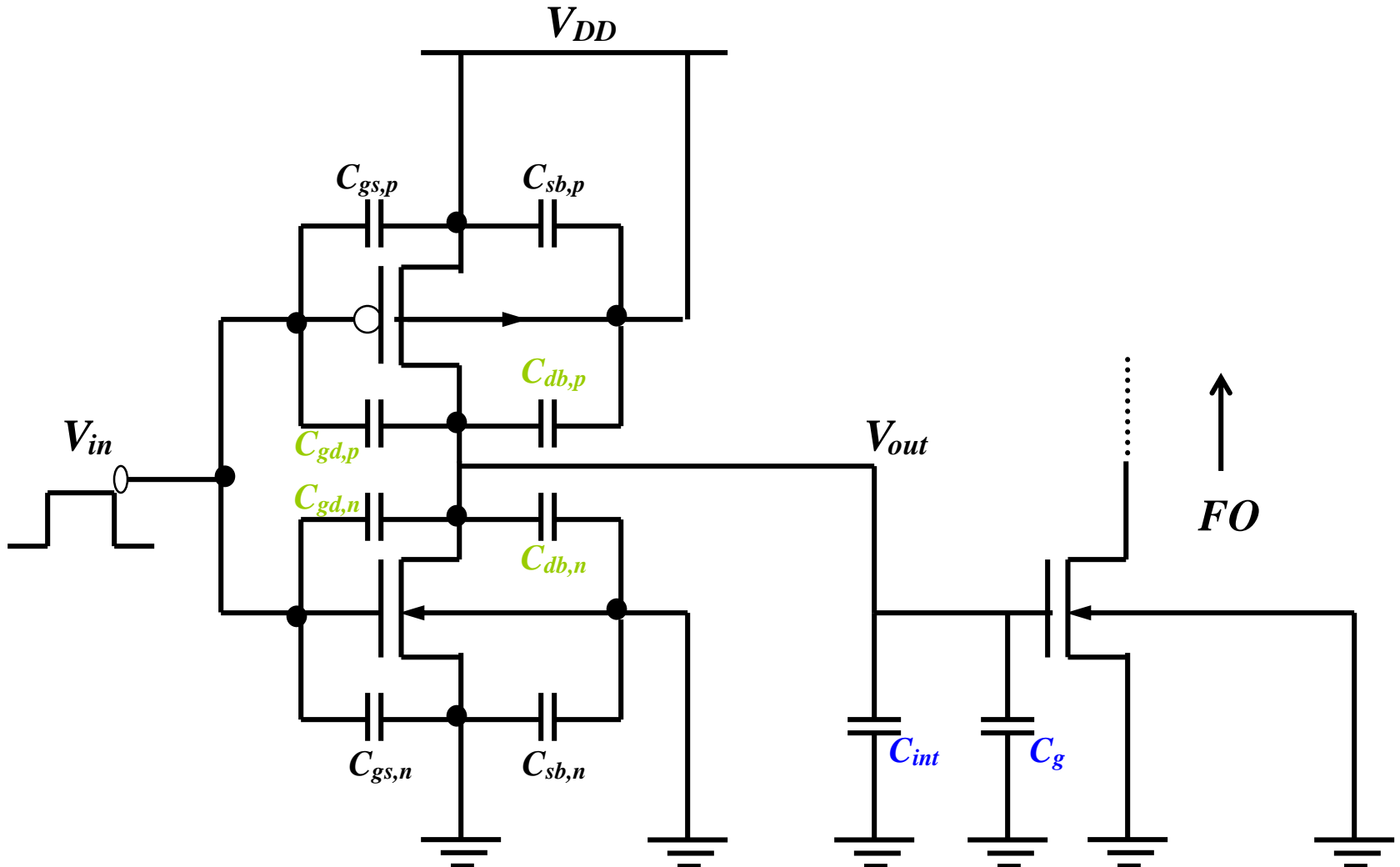

CMOS Dynamic Analysis

Capacitance Model for CMOS

- The aggregate capacitance driven by the output node of a CMOS inverter is in detail working from left to right,

- $C_{load} = C_{input} + C_{int} + C_g$

in which

$$C_{input} = C_{gd,n} + C_{gd,p} + C_{db,n} + C_{db,p} \text{ (intrinsic component)}$$

C_{int} = interconnect capacitance


C_g = thin-oxide capacitance over the gate area

} (extrinsic component)




CMOS Dynamic Analysis

Delay-Time Definitions

 

$$V_{50\%} = V_{OL} + (V_{OH} - V_{OL})/2$$


$$= (V_{OH} + V_{OL})/2$$

 

$$\tau_{PHL} = t_1 - t_0$$

$$\tau_{PLH} = t_3 - t_2$$

$$\tau_P = (\tau_{PHL} + \tau_{PLH})/2$$

 

$$V_{10\%} = V_{OL} + 0.1(V_{OH} - V_{OL})$$

$$V_{90\%} = V_{OL} + 0.9(V_{OH} - V_{OL})$$

$$\tau_{fall} = t_B - t_A$$

$$\tau_{rise} = t_C - t_D$$



CMOS Dynamic Analysis

Delay-Time Calculation (*First Order Estimates*)

- The simplest approach of calculating the propagation delay is based on estimating the *average capacitance current* during charge down/up.

$$\tau_{PHL} = \frac{C_{load}(V_{OH} - V_{50\%})}{I_{avg,HL}}$$

$$\tau_{PLH} = \frac{C_{load}(V_{50\%} - V_{OL})}{I_{avg,LH}}$$

where

$$I_{avg,HL} = \frac{1}{2} [i_C(V_{in} = V_{OH}, V_{out} = V_{OH}) + i_C(V_{in} = V_{OH}, V_{out} = V_{50\%})]$$


$$I_{avg,LH} = \frac{1}{2} [i_C(V_{in} = V_{OL}, V_{out} = V_{50\%}) + i_C(V_{in} = V_{OL}, V_{out} = V_{OL})]$$




CMOS Dynamic Analysis

Delay-Time Calculation (*More Accurate*)(1/4)

 - The propagation delay can be found more accurately by solving the state equation of the output node. The current flowing through C_{load} is a function V_{out} as



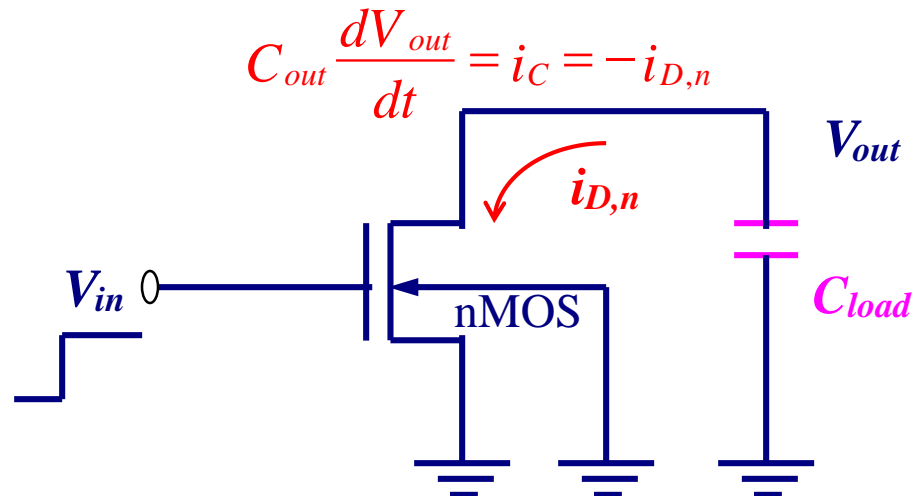
- τ_{PHL} : PMOS is off. The equivalent circuit during high-to-low output transition is



CMOS Dynamic Analysis

Delay-Time Calculation (2/4)

 The nMOS operates in two regions, *saturation* and *linear*, during the interval of τ_{PHL} .



- *Saturation Region*

$$i_{D,n} = (k_n/2)(V_{in} - V_{T,n})^2 = (k_n/2)(V_{OH} - V_{T,n})^2$$

» Plug $i_{D,n}$ into $C_{load} dV_{out}/dt = -i_{D,n}$, and integrate both sides, we get

$$t_1' - t_0 = 2C_{load}V_{T,n}/[k_n(V_{OH} - V_{T,n})^2]$$



CMOS Dynamic Analysis

Delay-Time Calculation (3/4)

- *Linear Region*

$$i_{D,n} = (k_n/2)[2(V_{in} - V_{T,n})V_{out} - V_{out}^2]$$


$$= (k_n/2)[2(V_{OH} - V_{T,n})V_{out} - V_{out}^2]$$

» Plug $i_{D,n}$ into $C_{load} dV_{out}/dt = -i_{D,n}$, and integrate both sides, we have

$$t_1 - t'_1 = \frac{C_{load}}{K_n(V_{DD} - V_{T,n})} \ln\left(\frac{4(V_{DD} - V_{T,n})}{V_{50\%}}\right)$$

- Finally, since $V_{OH} = V_{DD}$ and $V_{OL} = 0$, we have

 
$$\tau_{PHL} = \frac{C_{load}}{K_n(V_{DD} - V_{T,n})} \left[\frac{2V_{T,n}}{V_{DD} - V_{T,n}} + \ln\left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1\right) \right]$$



CMOS Dynamic Analysis

Delay-Time Calculation (4/4)

 - τ_{PLH} : NMOS is off. The equivalent circuit during low-to-high output transition is



With the similar way ($t_0 \rightarrow t_1' \rightarrow t_1/0 \rightarrow |V_{T,p}| \rightarrow V_{50\%}$ *linear* \rightarrow *saturation*), we can have

$$\tau_{PLH} = \frac{C_{load}}{K_p(V_{DD} - |V_{T,p}|)} \left[\frac{2|V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$



CMOS Inverter Design


- Design for Performance
 - **Keep capacitance small**
 - **Increase transistor size**
 - » *Watch out for self-loading!*
 - **Increase V_{DD} (????)**



CMOS Inverter Design


Delay as a Function of V_{DD}

 - V_{DD} increases $\rightarrow \tau_{PHL}/\tau_{PLH}$ decreases. However, the power consumption also increases.



CMOS Inverter Design

Device Sizing (1/5)

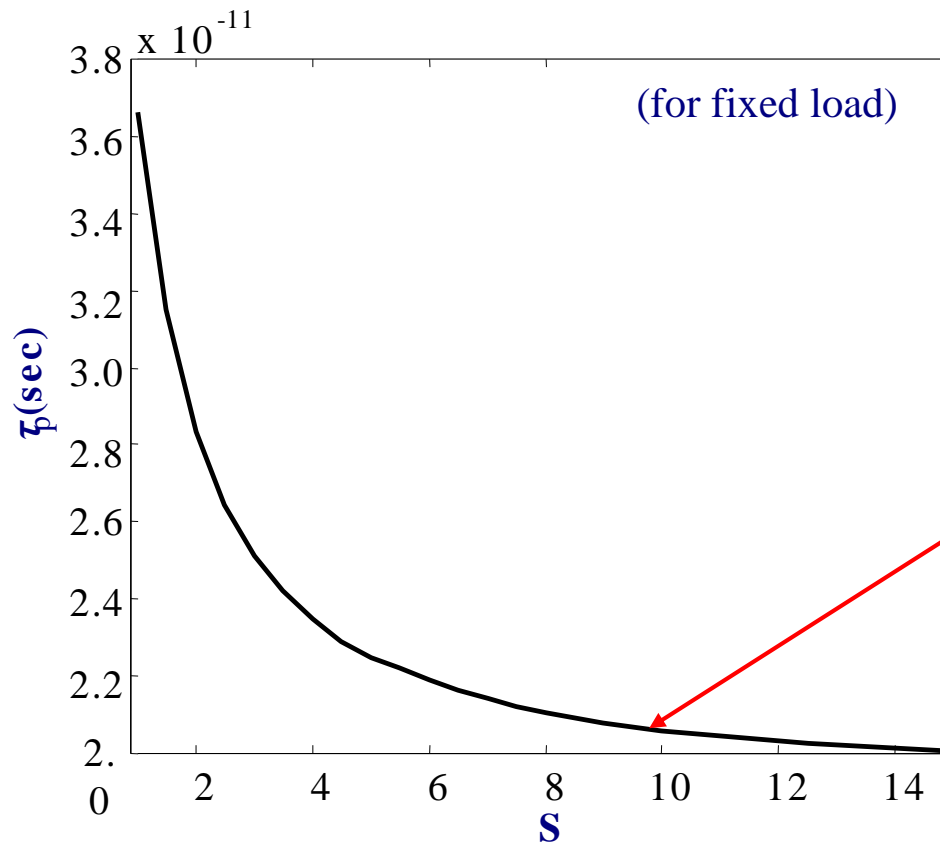


Self-loading effect:
Intrinsic capacitances
dominate



CMOS Inverter Design Device Sizing (2/5)

■ NMOS/PMOS Ratio

 

$$R = W_p / W_n$$



CMOS Inverter Design

Device Sizing (3/5)

Self-Loading Effect

$$C_{load} = C_{gd,n}(W_n) + C_{gd,p}(W_p) + C_{db,n}(W_n) + C_{db,p}(W_p) + C_{int} + C_g$$

$$= f(W_n, W_p)$$

- Using the junction capacitance expressions in Chapter 3, we have

$$C_{db,n} = (W_n D_{drain} + x_j D_{drain}) C_{j0,n} K_{eq,n} + (W_n + 2D_{drain}) C_{jsw,n} K_{eq,n}$$

$$C_{db,p} = (W_p D_{drain} + x_j D_{drain}) C_{j0,p} K_{eq,p} + (W_p + 2D_{drain}) C_{jsw,p} K_{eq,p}$$

- Therefore, C_{load} can be rewritten as

$$C_{load} = \alpha_0 + \alpha_n W_n + \alpha_p W_p$$

where

$$\alpha_0 = D_{drain} (2C_{jsw,n} K_{eq,n} + 2C_{jsw,p} K_{eq,p} + x_j C_{j0,n} K_{eq,n} + x_j C_{j0,p} K_{eq,p}) + C_{int} + C_g$$

$$\alpha_n = K_{eq,n} (C_{j0,n} D_{drain} + C_{jsw,n})$$

$$\alpha_p = K_{eq,p} (C_{j0,p} D_{drain} + C_{jsw,p})$$



CMOS Inverter Design

Device Sizing (4/5)

- Therefore, τ_{PHL} and τ_{PLH} are

$$\tau_{PHL} = \left(\frac{\alpha_0 + \alpha_n W_n + \alpha_p W_p}{W_n} \right) \times \left(\frac{L_n}{\mu_n C_{ox} (V_{DD} - V_{T,n})} \right) \times \left[\frac{2V_{T,n}}{V_{DD} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH} = \left(\frac{\alpha_0 + \alpha_n W_n + \alpha_p W_p}{W_p} \right) \times \left(\frac{L_p}{\mu_n C_{ox} (V_{DD} - |V_{T,p}|)} \right) \times \left[\frac{2|V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$

- The ratio between the channel widths W_n and W_p is usually dictated by other design constraints such as noise margins and the logic inversion threshold. Let's this transistor *aspect ratio* be defined as $R \equiv W_p/W_n$. Then, the propagation delay can be represented as

$$\tau_{PHL} = \Gamma_n \left(\frac{\alpha_0 + (\alpha_n + R\alpha_p)W_n}{W_n} \right)$$

$$\tau_{PLH} = \Gamma_p \left(\frac{\alpha_0 + \left(\frac{\alpha_n}{R} + \alpha_p \right) W_p}{W_p} \right)$$



CMOS Inverter Design

Device Sizing (5/5)

- As we continue increase the values of W_n and W_p , the propagation delay will asymptotically approach a limit value for larger W_n and W_p ,

$$\tau_{PHL}^{limit} = \Gamma_n(\alpha_n + R\alpha_p)$$


$$\tau_{PLH}^{limit} = \Gamma_p\left(\frac{\alpha_n}{R} + \alpha_p\right)$$

- The propagation delay times cannot be reduced beyond the above limits, and the limit is *independent* of the extrinsic capacitances.



CMOS Inverter Design

Impact of Rise Time on Delay

 

$$\tau_{PHL} = \sqrt{\tau_{PHL(\text{step input})}^2 + \left(\frac{\tau_r}{2}\right)^2}$$

$$\tau_{PLH} = \sqrt{\tau_{PLH(\text{step input})}^2 + \left(\frac{\tau_f}{2}\right)^2}$$

Propagation delay increases since both PMOS and NMOS are on during the charge-up and charge-down events.



CMOS Inverter Design

Impact of Channel Velocity Saturation

- The drain current is *linearly dependent on V_{GS}*

$$I_{sat} = \kappa W_n (V_{GS} - V_T)$$

- Propagation delay only has a weak dependence on the supply voltage V_{DD}

$$\tau_{PHL} \approx \frac{C_{load} V_{50\%}}{I_{sat}} = \frac{C_{load} (V_{DD} / 2)}{\kappa W_n (V_{DD} - V_T)}$$



CMOS Dynamic Analysis

Dynamic Power Dissipation (1/2)

- The dynamic power dissipation can be derived as follows.

$$P_{dyn,avg} = V_{DD} I_{DD,avg}$$

- With $I_{DD,avg}$ taken over one clock period T . The capacitance current which equals the current from the power supply (assuming $I_{Dn} = 0$ during charging) is

$$I_D = C_{load} \frac{dV_{out}}{dt}$$

- Rearranging and integrating over one clock period T

$$\int_0^T I_D dt = \int_0^{V_{DD}} C_{load} dV_{out}$$

- Gives

$$I_{DD,avg} T = C_{load} V_{DD}$$



CMOS Dynamic Analysis

Dynamic Power Dissipation (2/2)

- Solving for $I_{DD,avg}$ and substituting in P_{avg} :

$$P_{avg} = \frac{1}{T} C_{load} V_{DD}^2 = C_{load} V_{DD}^2 f$$

- It should be noted here the our simple C_{load} may underestimate the power dissipated.
- In terms of SPICE simulation, the authors' offer a circuit called power meter.

