

CMOS Digital Integrated Circuits




Lec 11

Sequential CMOS Logic Circuits



Sequential Logic

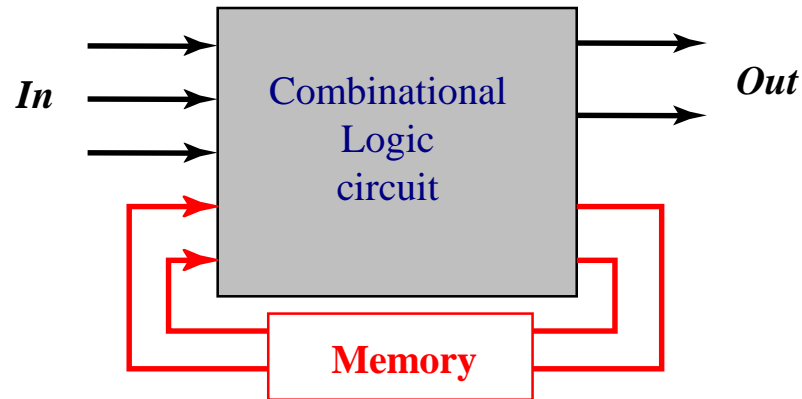

Sequential

The output is determined by

- Current inputs
- Previous inputs

$$\text{Output} = f(\text{In}, \text{Previous In})$$

- The regenerative behavior of sequential circuits is due to either a **direct** or an **indirect feedback** connection between the output and input




Critical Components of Sequential Circuits

Basic Regenerative Circuits

Categories of Basic Regenerative Circuits

 - 1. Bistable Circuits:** Two stable states or operation modes, each of them can be attained under certain input and output conditions. **The most widely used** and the most important class which is used for the basic latch, flip-flop circuits, registers, and memory elements.
- 2. Monostable Circuits:** One stable state or operation mode
- 3. Astable Circuits:** No stable operating point or state which the circuit can preserve for a certain time period. The output oscillates without settling into a stable operating mode.





Behavior of Bistable Elements (1/7)

Two Identical Cross-Coupled Inverter Circuit



- Voltage Transfer Curves

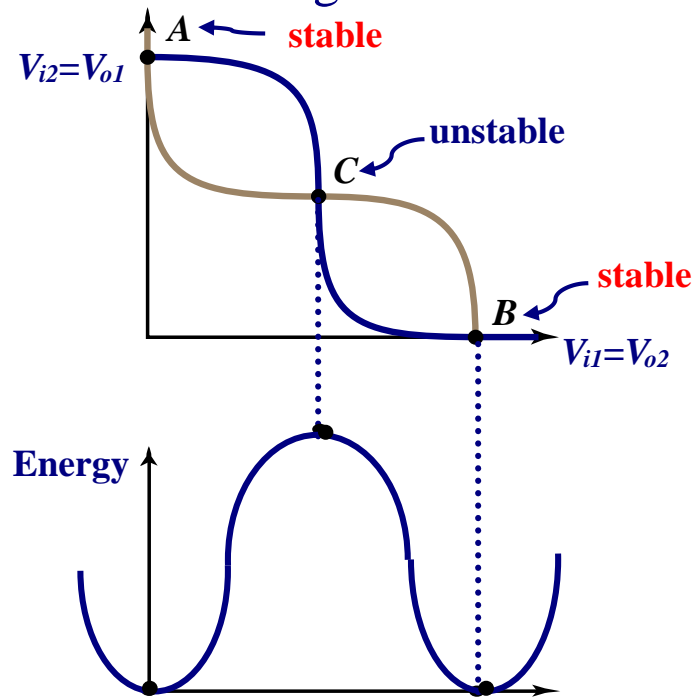 - » The output voltage of inverter (1) is equal to the input voltage of inverter (2), and the output voltage of inverter (2) is equal to the input voltage of inverter (1).
- » **A and B are stable points:** If the circuit is initially operating at one of them, it will preserve this state. The gain is smaller than **unity**.



Behavior of Bistable Elements (2/7)


- » **C is an unstable point:** The voltage gains of both inverters are larger than unity. A small voltage perturbation at this operating point will be amplified \Rightarrow the operating point will move to one of the stable operating points, **A** or **B**.
- **Energy Levels:**
 - » The potential energy is at its minimum at **A** and **B**, since the voltage gains of both inverters are equal to zero.
 - » The potential energy is at its maximum at **C**, since the voltage gains of both inverters are maximum. (all four transistors are in saturation modes)

  

Behavior of Bistable Elements (3/7)

Analysis of the Output Voltages

 - Let the initially operating point is at $v_{o1}=v_{o2}=V_{th}$, and assume that the gate capacitance (C_g) of each inverter is much larger than the drain capacitance (C_d).
- The drain current of each inverter is equal to the gate current of the other inverter.



$$\begin{aligned} i_{g1} &= i_{d2} = g_m v_{g2} \\ i_{g2} &= i_{d1} = g_m v_{g1} \end{aligned} \quad (\text{Eq. A})$$

g_m is the small-signal transconductance of the inverter.

- The gate voltages can be expressed by gate charges, q_1 and q_2

$$\begin{aligned} v_{g1} &= q_1 / C_g \\ v_{g2} &= q_2 / C_g \end{aligned} \quad (\text{Eq. B})$$

- Also the small-signal gate currents can be expressed as

$$\begin{aligned} i_{g1} &= C_g \cdot dv_{g1} / dt \\ i_{g2} &= C_g \cdot dv_{g2} / dt \end{aligned} \quad (\text{Eq. C})$$




Behavior of Bistable Elements (4/7)

Analysis of the Output Voltages

- Combine Eq. A and C, we have

$$g_m v_{g2} = C_g \frac{dv_{g1}}{dt}$$

$$g_m v_{g1} = C_g \frac{dv_{g2}}{dt}$$

 

- Replace the gate voltages by Eq. B, we obtain

$$\frac{g_m}{C_g} q_2 = \frac{dq_1}{dt}$$

$$\frac{g_m}{C_g} q_1 = \frac{dq_2}{dt}$$

- The above equations can be simplified to

$$\frac{g_m}{C_g} q_1 = \frac{C_g}{g_m} \frac{d^2 q_1}{dt^2} \Rightarrow \frac{d^2 q_1}{dt^2} = \left(\frac{g_m}{C_g} \right)^2 q_1 = \frac{1}{\tau_0^2} q_1; \quad \tau_0 = \frac{C_g}{g_m}$$



Behavior of Bistable Elements (5/7)

Analysis of the Output Voltages

- Therefore,

$$q_1(t) = \frac{q_1(0) - \tau_0 q_1'(0)}{2} e^{-\frac{t}{\tau_0}} + \frac{q_1(0) + \tau_0 q_1'(0)}{2} e^{\frac{t}{\tau_0}}$$

where $q_1(0) = C_g \cdot v_{g1}(0)$

- Replace the gate charge pf both inverters with the corresponding out-put voltages variables, we have

$$v_{o2}(t) = \frac{v_{o2}(0) - \tau_0 v_{o2}'(0)}{2} e^{-\frac{t}{\tau_0}} + \frac{v_{o2}(0) + \tau_0 v_{o2}'(0)}{2} e^{\frac{t}{\tau_0}}$$

≈ 0 for t >> τ₀

$$v_{o1}(t) = \frac{v_{o1}(0) - \tau_0 v_{o1}'(0)}{2} e^{-\frac{t}{\tau_0}} + \frac{v_{o1}(0) + \tau_0 v_{o1}'(0)}{2} e^{\frac{t}{\tau_0}}$$

≈ 0 for t >> τ₀

- For large values of t , the above equations can be approximated as

$$v_{o1}(t) \approx \frac{1}{2} (v_{o1}(0) + \tau_0 v_{o1}'(0)) e^{\frac{t}{\tau_0}}$$


$$v_{o2}(t) \approx \frac{1}{2} (v_{o2}(0) + \tau_0 v_{o2}'(0)) e^{\frac{t}{\tau_0}}$$



Behavior of Bistable Elements (6/7)

Analysis of the Output Voltages

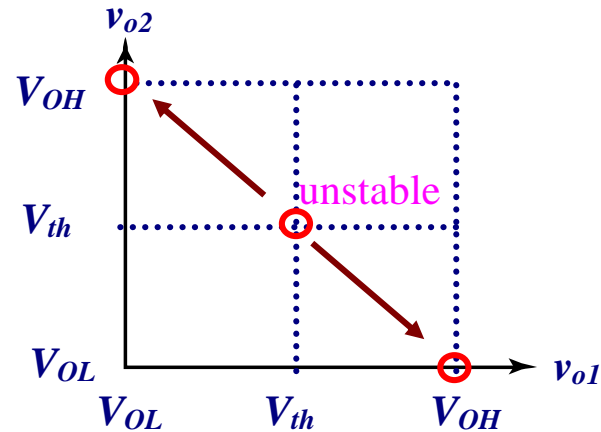- Depending on the polarity of the initial small perturbations $dv_{o1}(0)$ and $dv_{o2}(0)$, the v_{o1} and v_{o2} will diverge from their initial values of V_{th} to either V_{OL} and V_{OH} .
- The polarity of dv_{o1} must always be **opposite** to that of dv_{o2} , because of the **charge-conservation principle**. Therefore, v_{o1} and v_{o2} always diverge into opposite directions.



Phase-plane Representation

$v_{o1}: V_{th} \rightarrow V_{OH} \text{ or } V_{OL}$


$v_{o2}: V_{th} \rightarrow V_{OL} \text{ or } V_{OH}$



Behavior of Bistable Elements (7/7)

Analysis of the Output Voltages

 
- As a bistable circuit settles from unstable operating point to its stable point, a signal travels around **2 INV loop n times**.



$$v_{o1}(t)/v_{o1}(0) \approx e^{t/\tau_0}$$

- If during interval $t = T$, the signal travels around the loop n times

$$A^n \approx e^{T/\tau_0}$$

 

Naming Conventions



- ❑ A latch is level sensitive
- ❑ A register is edge-triggered
- ❑ There are many different naming conventions
 - For instance, many books call edge-triggered elements flip-flops



Latch versus Register



❑ Latch

stores data when
clock is low

  

❑ Register

stores data when
clock rises

  



© Digital Integrated Circuits^{2nd}

CMOS Digital Integrated Circuits





Latches

Positive Latch

  


Negative Latch

  

SR Latch Circuit

- The two cross-coupled inverters can perform a simple memory function of *holding* its state. However, the two-inverter circuit alone has no provision for allowing its state to be changed externally from one stable operating point to other.
- In order to allow such a change of state, we need to *add simple switches* which can be used to force or trigger the circuit from one operating point to the other.

 


Schematic Diagram of SR Latch



SR Latch Circuit (Cont.)

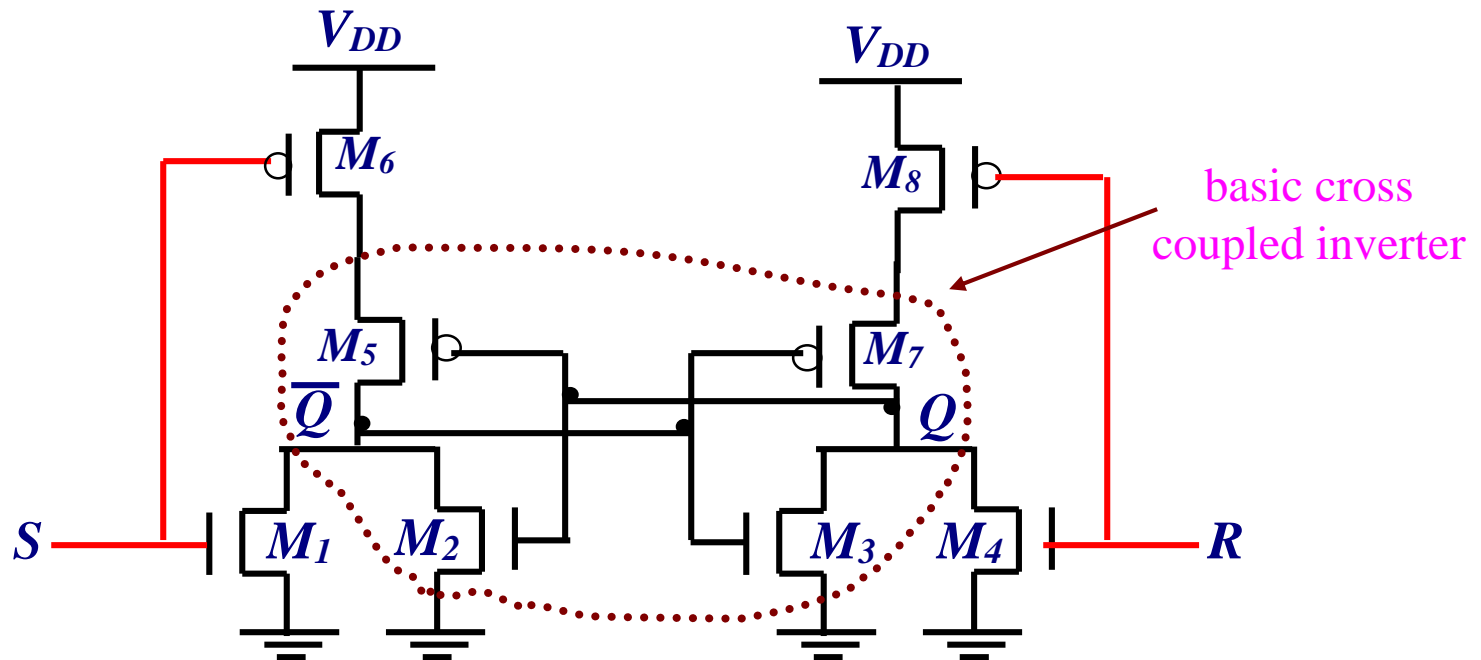- The below circuit shows the simple CMOS SR latch which consists of two triggering inputs, S (*set*) and R (*reset*).
- The SR Latch consists of two CMOS NOR2 gates. One of the input terminals of each NOR gate is used to cross-couple to the output of the other NOR gate. The second input enables triggering of the circuit.



SR Latch Circuit

Truth Table

- **Set:** $S=1, R=0 \Rightarrow Q_{n+1}=1, \overline{Q_{n+1}}=0$. The SR latch will be *set* regardless of its previous state.
- **Reset:** $S=0, R=1 \Rightarrow Q_{n+1}=0, \overline{Q_{n+1}}=1$. The SR latch will be *reset* regardless of its previous state.
- **Hold:** $S=0, R=0 \Rightarrow Q_{n+1}=Q_n, \overline{Q_{n+1}}=\overline{Q_n}$. The previous states will be *held*.
- **Not Allow:** $S=0, R=0 \Rightarrow Q_{n+1}=0, \overline{Q_{n+1}}=0$

S	R	Q_{n+1}	$\overline{Q_{n+1}}$	Operation
0	0	Q_n	$\overline{Q_n}$	<i>Hold</i>
1	0	1	0	<i>Set</i>
0	1	0	1	<i>Reset</i>
1	1	0	0	<i>Not Allowed</i>

active high →


Truth Table of NOR-based (*active high inputs*) SR latch



SR Latch Circuit

Operation Modes of the Transistors

S	R	Q_{n+1}	\overline{Q}_{n+1}	Operation	
				NMOS	PMOS
V_{OH}	V_{OL}	$V_{OH}^{(2)}$	$V_{OL}^{(1)}$	$M_1^{(1)}, M_2^{(3)}$ on; $M_3^{(2)}, M_4^{(1)}$ off	$M_7^{(2)}, M_8^{(1)}$ on; $M_5^{(3)}, M_6^{(1)}$ off
V_{OL}	V_{OH}	$V_{OL}^{(1)}$	$V_{OH}^{(2)}$	$M_1^{(1)}, M_2^{(2)}$ off; $M_3^{(3)}, M_4^{(1)}$ on	$M_7^{(3)}, M_8^{(1)}$ off; $M_5^{(2)}, M_6^{(1)}$ on
V_{OL}	V_{OL}	V_{OH}	V_{OL}	M_1, M_4 off; M_2 , on	M_6, M_8 on; M_7 , on
V_{OL}	V_{OL}	V_{OL}	V_{OH}	M_1, M_4 off; M_3 , on	M_6, M_8 on; M_5 , on

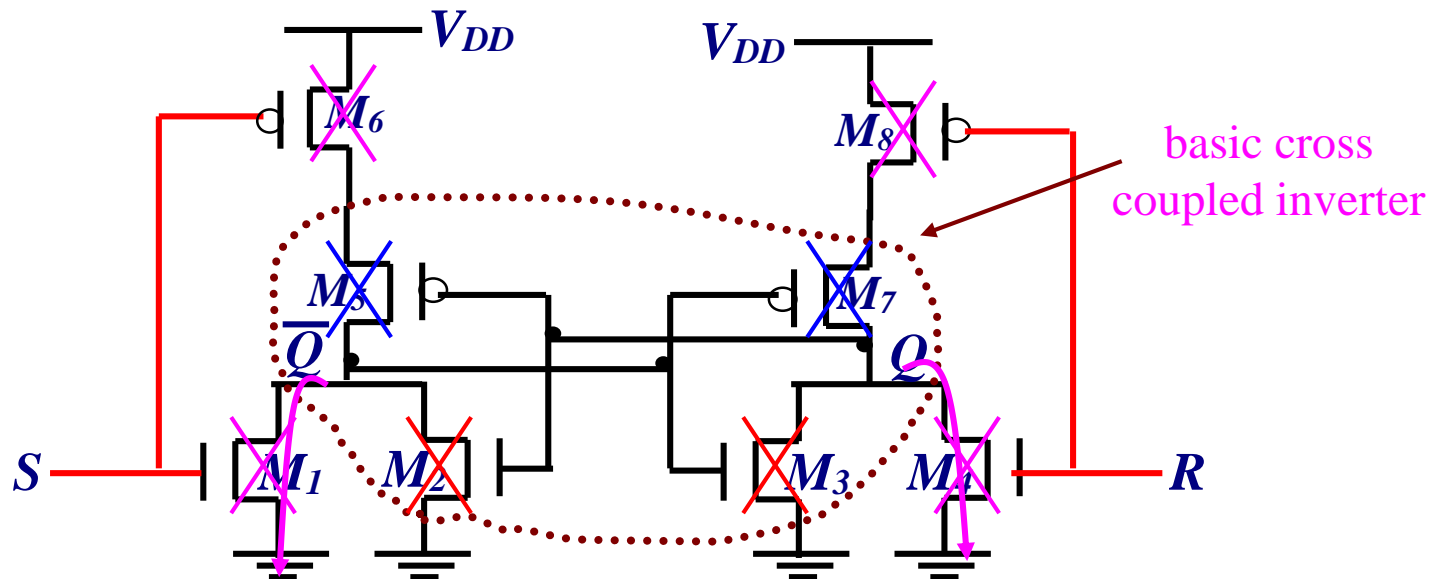

SR Latch Circuit

Transient Analysis

- For transient analysis, we have to consider an event which results in a state change, **reset** \Rightarrow **set**, or **set** \Rightarrow **reset**
- In either case, we note that both of the output nodes undergo simultaneous voltage transitions. One is from logic-low to logic-high, and the other is from logic-high to logic-low.
- The exact transient analysis need to solve two coupled differential equations.
- For simplicity, we can assume that the *two events take place in sequence rather than simultaneously*. (**overestimation**)

Switching Time Calculation

- The total lumped capacitance at each output node can be approximated as

$$C_Q = C_{gb,2} + C_{gb,5} + C_{db,3} + C_{db,4} + C_{db,7} + C_{sb,7} + C_{db,8}$$

$$C_{\bar{Q}} = C_{gb,3} + C_{gb,7} + C_{db,1} + C_{db,2} + C_{db,5} + C_{sb,5} + C_{db,6}$$




SR Latch Circuit

Transient Analysis (Cont.)


- Assuming that the latch is initially reset and that a set operation is being performed, the rise time associated with node Q can be estimated as
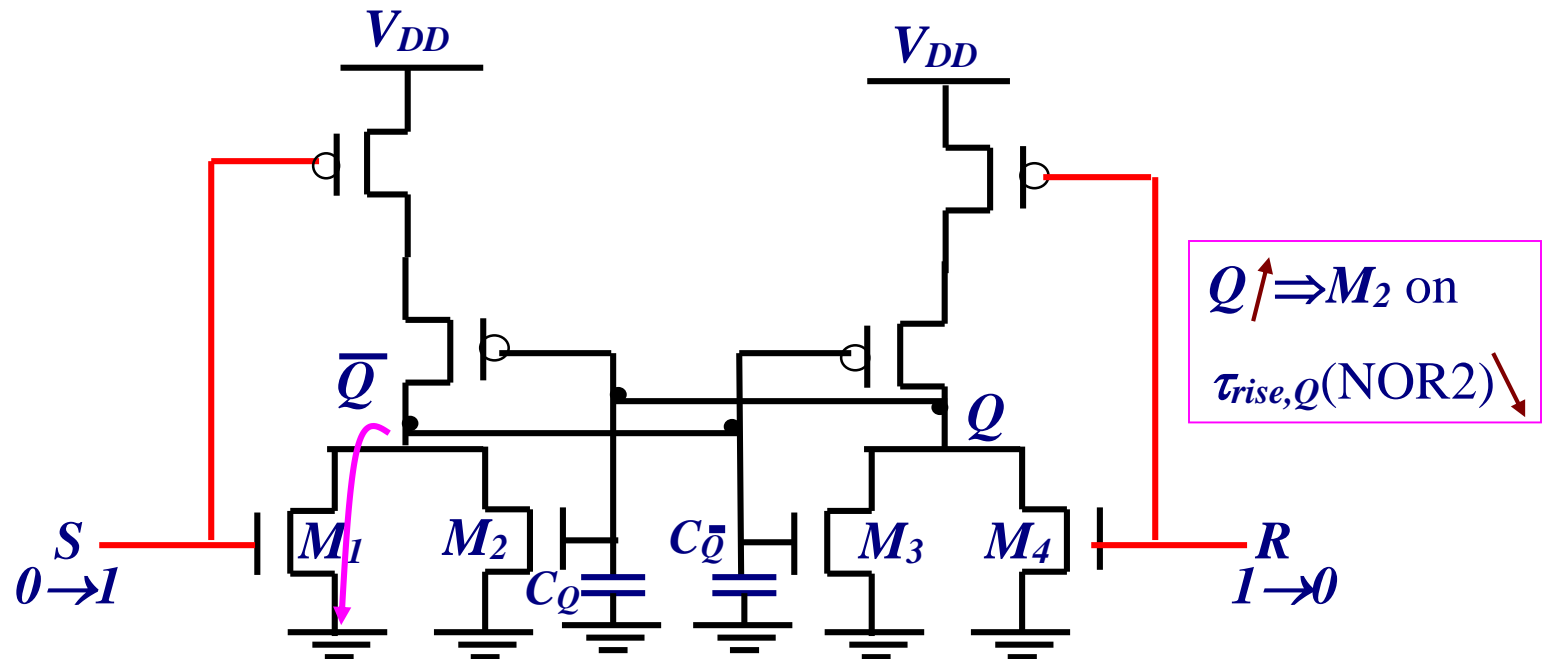
$$\tau_{rise,Q}(SR-latch) = \tau_{rise,Q}(NOR2) + \tau_{fall,\bar{Q}}(NOR2)$$



SR Latch Circuit

NAND-based (active low signals)

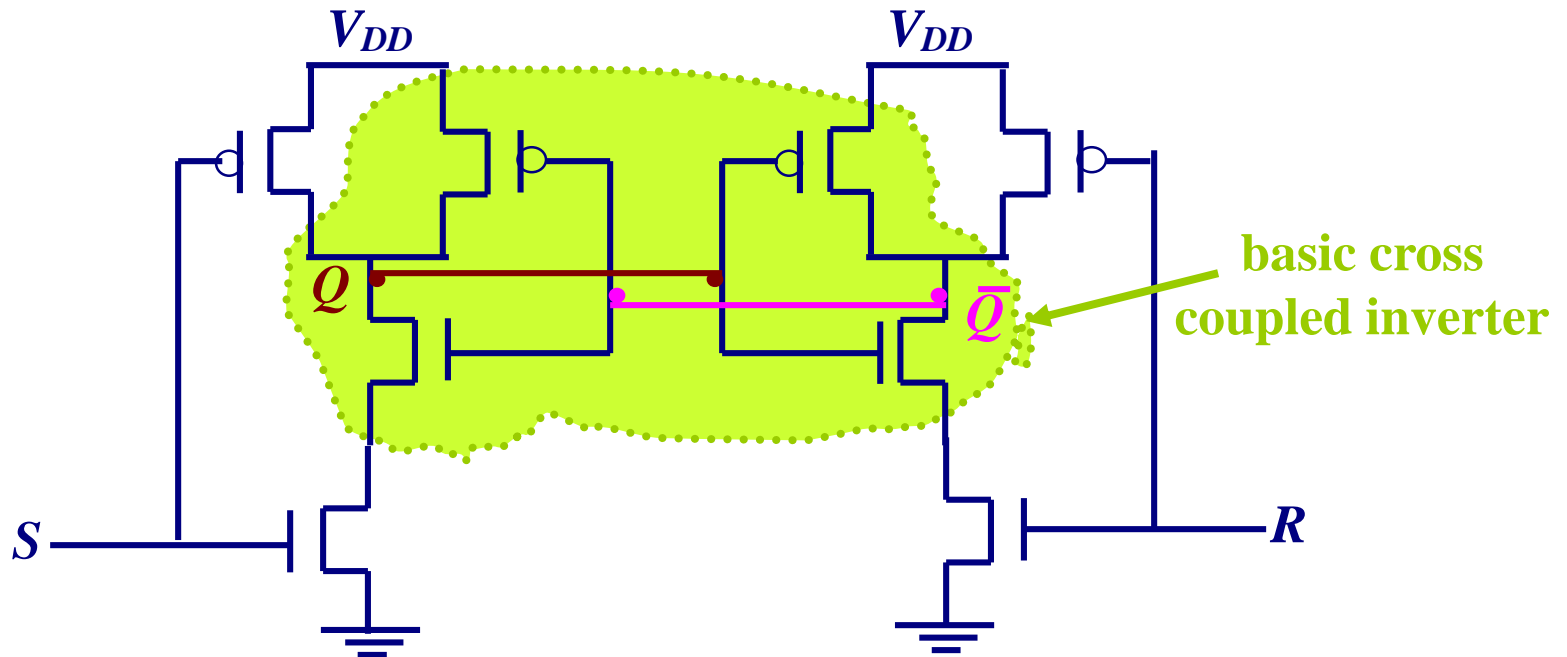


S	R	Q_{n+1}	$\overline{Q_{n+1}}$	Operation
0	0	1	1	<i>Not Allowed</i>
0	1	1	0	<i>Set</i>
1	0	0	1	<i>Reset</i>
1	1	Q_n	$\overline{Q_n}$	<i>Hold</i>

active low



Clocked Latch and Flip-Flop Circuits

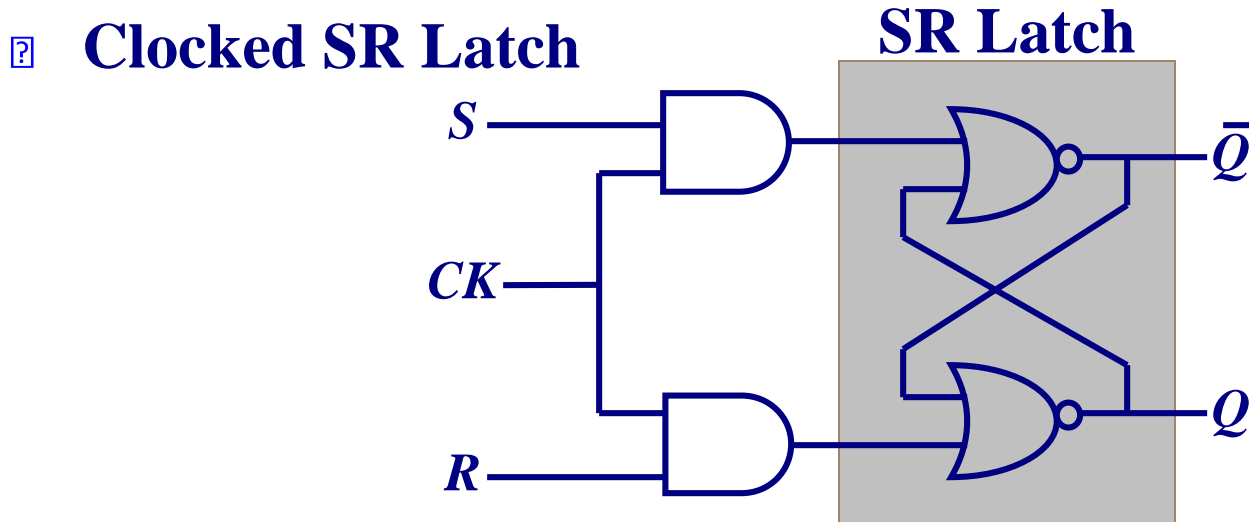The previous SR latch circuits are *asynchronous* sequential circuits. The *synchronization* can be introduced through **clock CK**, which the outputs will respond to the input levels only during the active period of a clock pulse.




- When $CK=0$, S , R have no influence of Q , $\bar{Q} \Rightarrow$ *Hold*
Set State: $CK=1$, $S=1$, $R=0 \Rightarrow Q_{n+1}=1$, $\bar{Q}_{n+1}=0$
Reset State: $CK=1$, $S=0$, $R=1 \Rightarrow Q_{n+1}=0$, $\bar{Q}_{n+1}=1$
Not Allowed: $CK=1$, $S=1$, $R=1$

Active “High”




AOI-based Implementation of Clocked NOR-based SR Latch

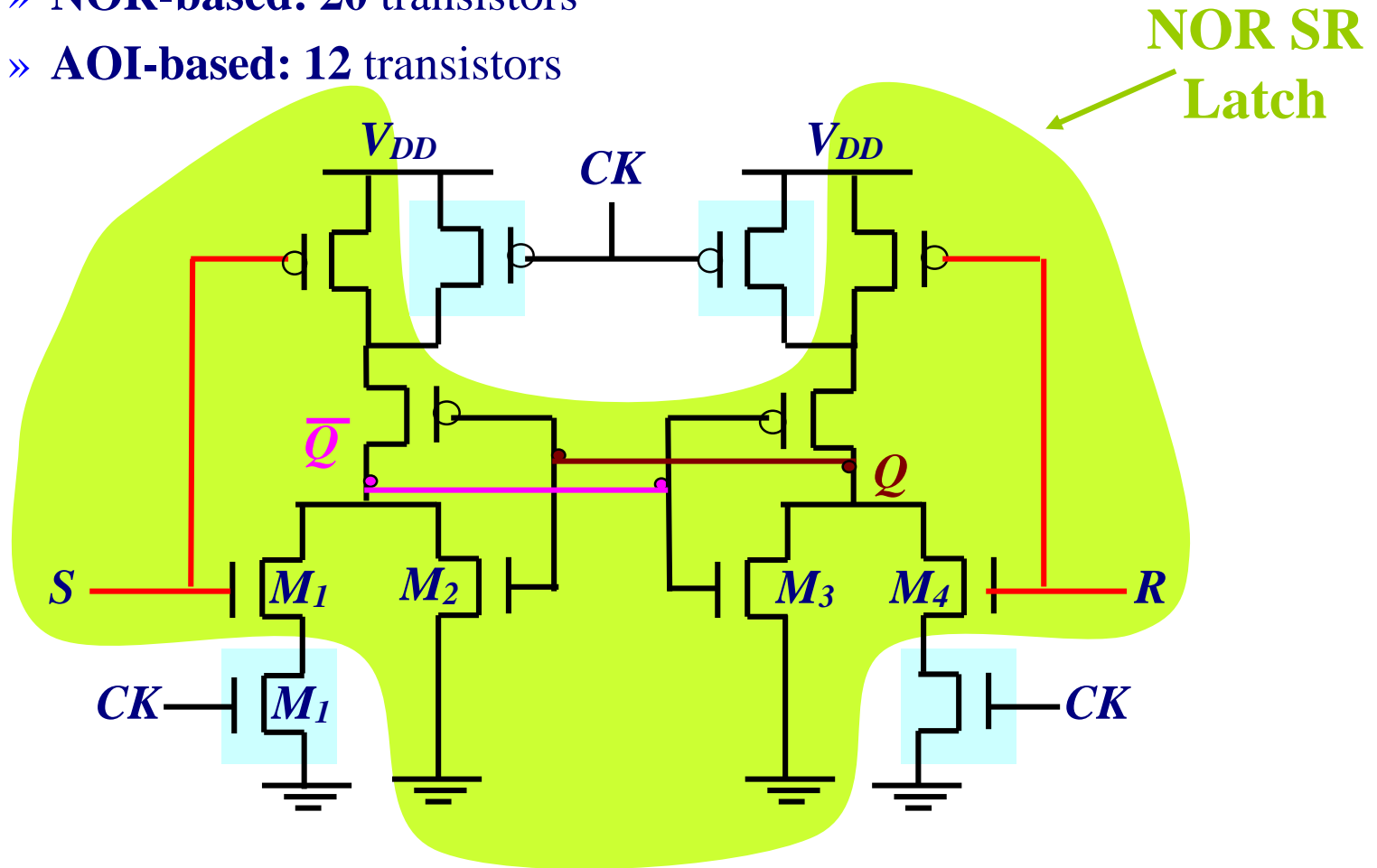- The AOI-based implementation need a very small transistor count, compared with the circuit consisting of two AND2 and two NOR2 gates
 - » **NOR-based: 20** transistors
 - » **AOI-based: 12** transistors



Operation of Clocked SR Latch


Operation	CK	S	R	Q_{n+1}	$\overline{Q_{n+1}}$
<i>Hold</i>	0	X	X	Q_n	$\overline{Q_n}$
<i>Set</i>	1	1	0	1	0
<i>Reset</i>	1	0	1	0	1
<i>Not Allow</i>	1	1	1	1	1

 

- When “Glitch” ON S (or R) occurs during $CK = 1$, Q is set (or reset).
- **Level Sensitive:** When $CK = 1$, any changes in S , R will effect Q .



Clocked NAND-based SR Latch

 


- When $CK = 1$, S and R have no influence of Q and $\bar{Q} \Rightarrow \text{Hold}$

Operation	CK	S	R	Q_{n+1}	$\overline{Q_{n+1}}$
<i>Hold</i>	1	X	X	Q_n	$\overline{Q_n}$
<i>Set</i>	0	0	1	1	0
<i>Reset</i>	0	1	0	0	1
<i>Not Allow</i>	0	0	0	0	0



OAI-based Implementation of Clocked NAND-based SR Latch

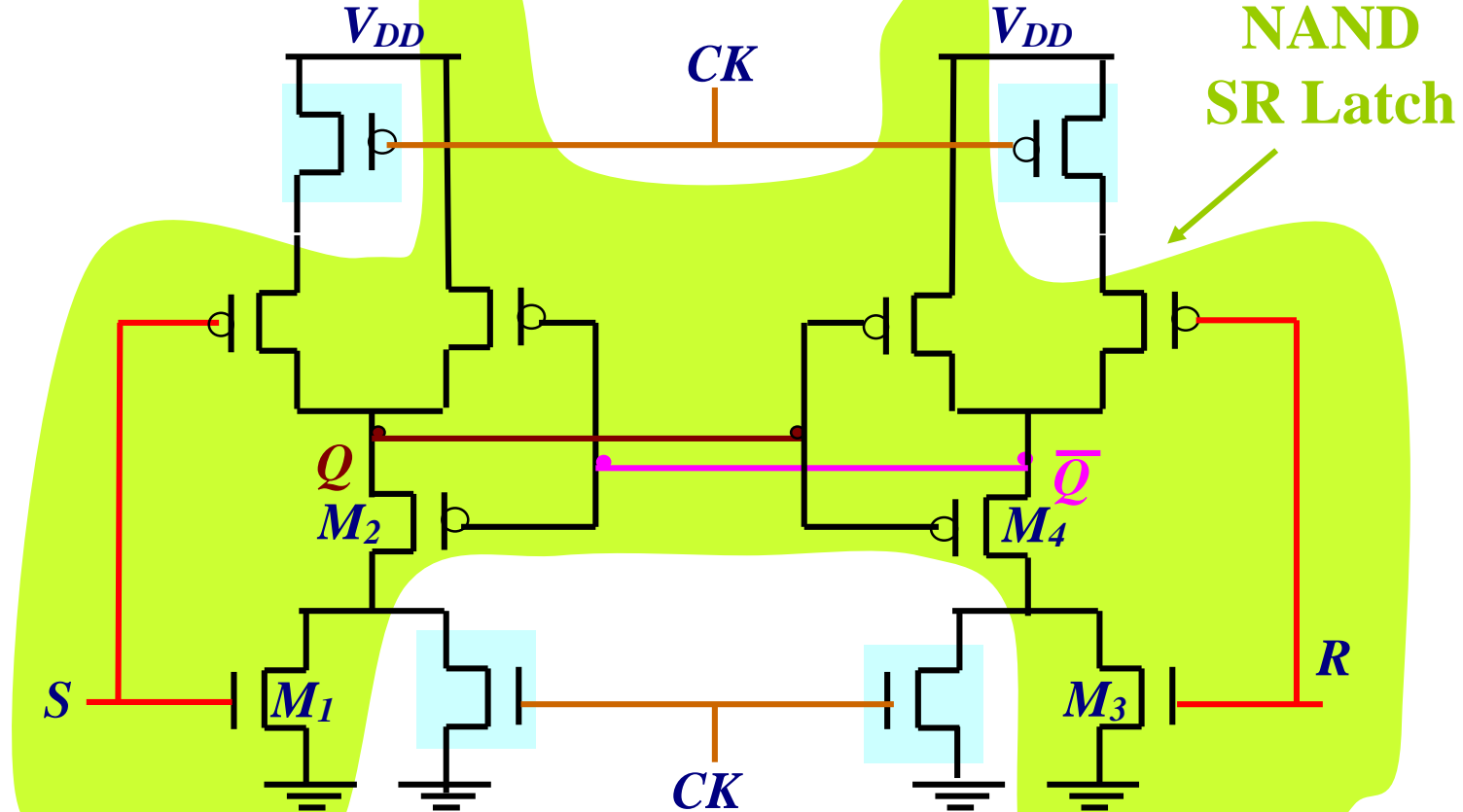- The OAI-based implementation need a very small transistor count, compared with the circuit consisting of two OR2 and two NAND2 gates




- Synchronous operation**
- Level sensitive** (any changes in S and R as $CK=1$ will be reflected onto outputs)
- Not allowed input sequence**



Clocked JK Latch

NAND SR

 

$CK = 0 \Rightarrow hold$

$CK = 1 \Rightarrow active$

No not allowed combination

J	K	Q_n	\overline{Q}_n	S	R	Q_{n+1}	\overline{Q}_{n+1}	Operation
0	0	0	1	1	1	0	1	Hold
0	0	1	0	1	1	1	0	Hold
0	1	0	1	1	1	0	1	Reset
0	1	1	0	1	0	0	1	Reset
1	0	0	1	0	1	1	0	Set
1	0	1	0	1	1	1	0	Set
1	1	0	1	0	1	1	0	Toggle
1	1	1	0	1	0	0	1	Toggle


$CK = 1$

OSC




AOI-based Implementation of NOR-based Clocked JK Latch

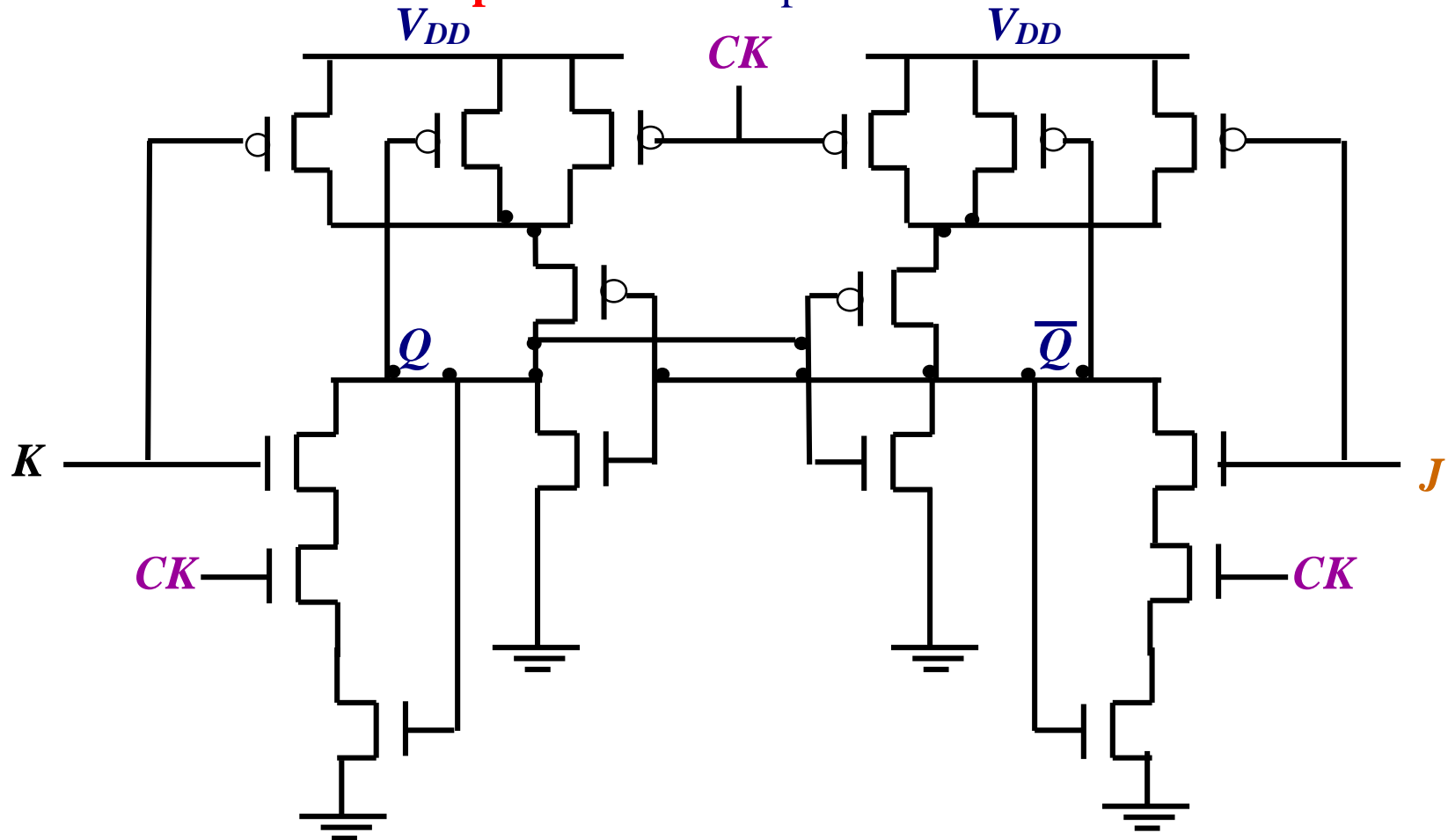- The AOI-based implementation has a **very small transistor count**, and a **more compact** circuit compared to all-NAND realization.



JK Toggle Switch


$$J = K = 1$$

 

- Iff $\tau_{JKP} > T_1$ (awkward to implement)
Output Q changes only once per clock period
 - » No not allowed input
 - » Timing issues
 - » Level sensitive



Master-Slave Flip-Flop

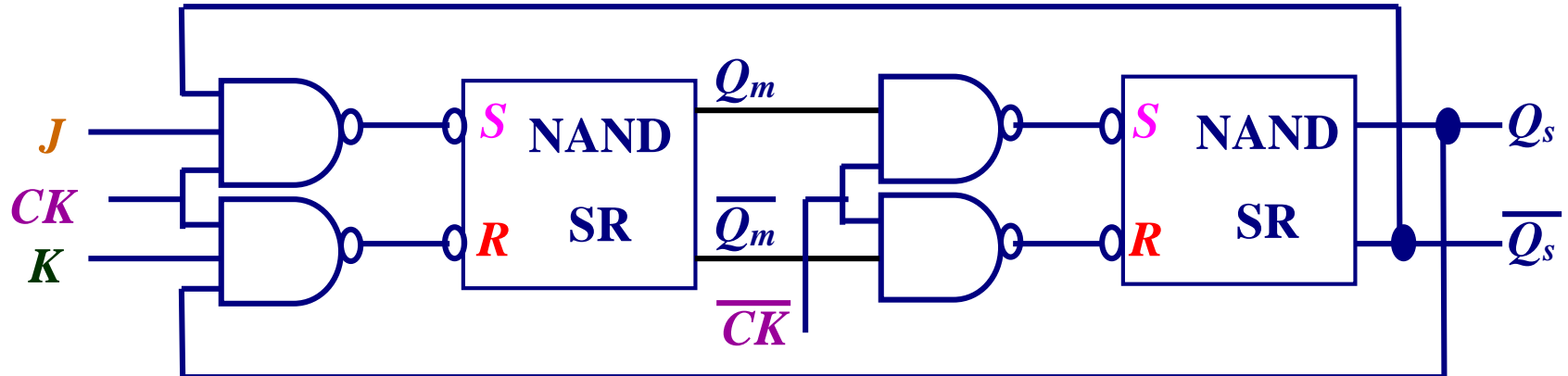


- Two cascaded latches operating on opposite clock phases insures that the flip-flop is *never transparent*; i.e., a change occurring in the primary inputs is never reflected directly to the outputs.
- Eliminates oscillations when $J = K = 1$.
- Still level sensitive.
- Number of transistors:
 - » **NAND-based: 36**
 - » **AOI-based: 28**



D-Latch

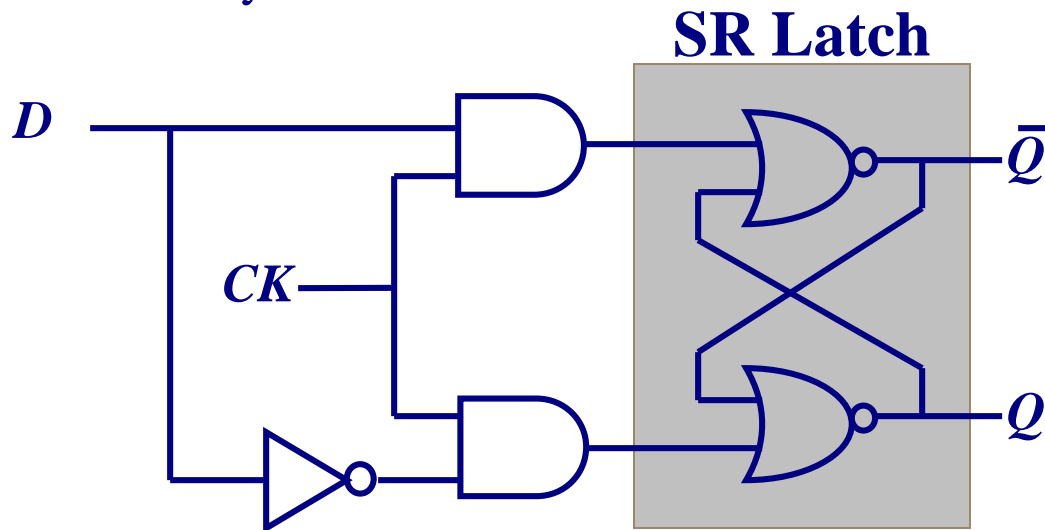- D-latch is obtained by modifying the clocked NOR-based SR latch circuit. The circuit has a single input D which is connected to S input, and D is also inverted and connected to R input.
- The applications of D-latch are primarily for temporary storage of data or as a delay element.



If $CK=1 \Rightarrow Q_{n+1} = D$


If $CK=0 \Rightarrow Q_{n+1} =$

Q_n




D-Latch (Cont.)

 - D-latch is a mux-based latch which can be represented as



$$Q = CK \cdot Q + \overline{CK} \cdot In$$

 Negative latch
(transparent when $CK = 0$)



$$Q = \overline{CK} \cdot Q + CK \cdot In$$


Positive latch
(transparent when $CK = 1$)



D-Latch

Implementation with Transmission Gates

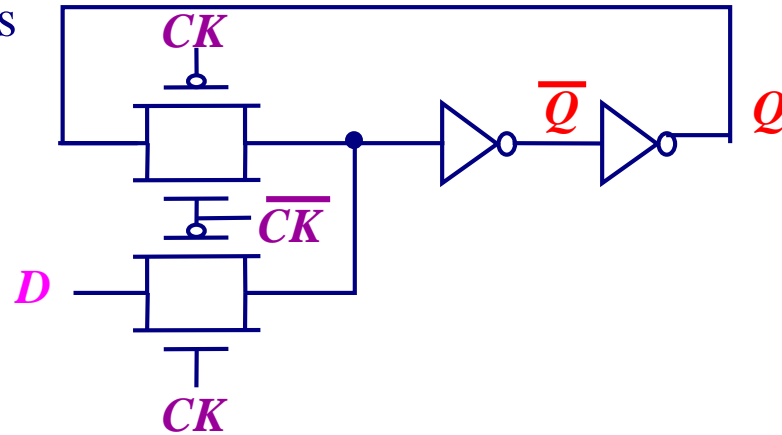- Transmission gate **D-latch**: Use switch-like properties of transmission gates



- Operation: For $CK = 1$, $\overline{Q_{n+1}} = \overline{D}$ and $Q_{n+1} = D$. A bit is loaded. For $CK = 0$, $\overline{Q_{n+1}} = \overline{Q_n}$ and $Q_{n+1} = Q_n$. Thus, a bit is stored. Note that Propagation delay to Q is less than delay to \overline{Q} . What about changes in D relative to changes in CK ?


Setup time and *Hold time* relative to CK : $1 \rightarrow 0$

- Device counts for TG-based reduced from AOI/OAI
 - » **AOI-based: 14**
 - » **TG-based: 8 (plus 2 to invert clock)**




D-Latch

Implementation with Three-State

 

 
- Similar to the TG-based implementation, except as if connection between n and pFETs in a driving inverter and input side of a driven transmission gate is served. Require addition of inverter at input first.



D-Latch


Implementation with Three-State (Cont.)

 - The first three-state inverter acts as the **input switch**. Accept the input signal when **CK** is high, the second three-state inverter is at its high impedance state, and $Q = D$.
- The first three-state inverter is **inactive** when the **CK** goes low, and the second three-state inverter completes the two-inverter loop, which preserves its state ($Q_{n+1} = Q_n$)



D-Latch

Setup Time and Hold Time


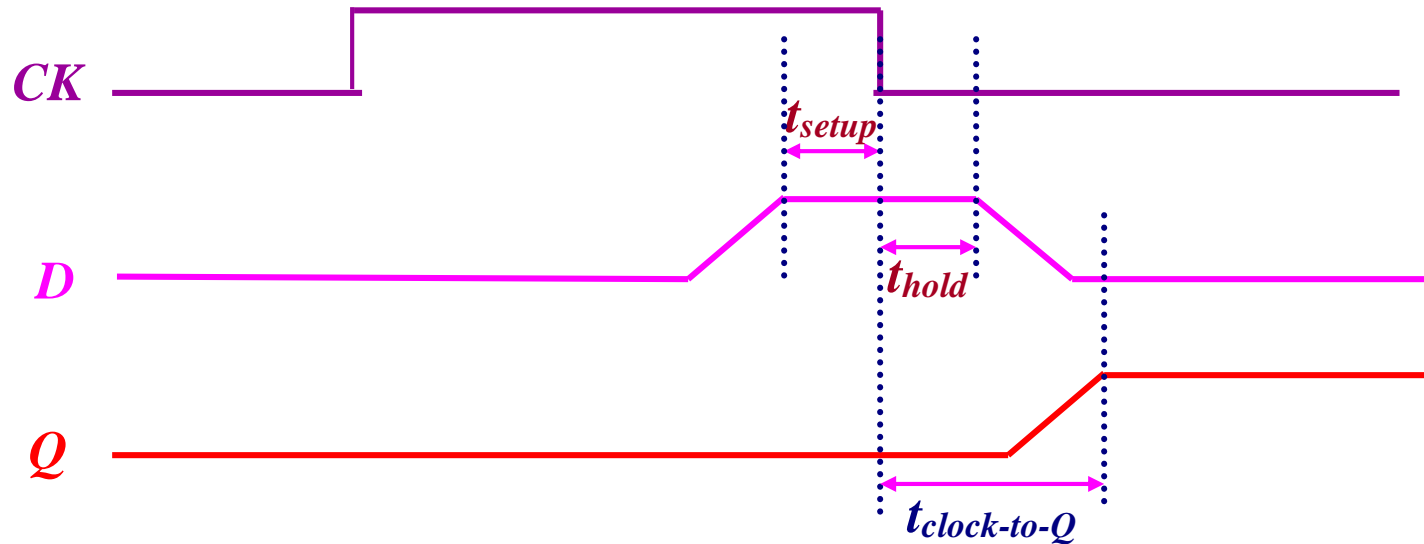


- T_{setup} : time before the negative-CK edge the **D-input** has to be stable
 - » The setup time is the delay between the data input of the register and the storage element. As the data takes a finite time to travel to the storage point, the clock cannot be changed until the correct data value appears.
- T_{hold} : time after the negative-CK edge **D-input** has to remain stable
 - » The hold time relates to the delay between the clock input to the register and the storage element. That is, the data has to be held for this period while the clock travels to the point of storage.
- $T_{clock-to-Q}$: Delay from the negative-CK edge to new value of Q output





Edge Triggered Master-Slave Operation


❑ Negative D-Latch

  


❑ Positive D-Latch

  

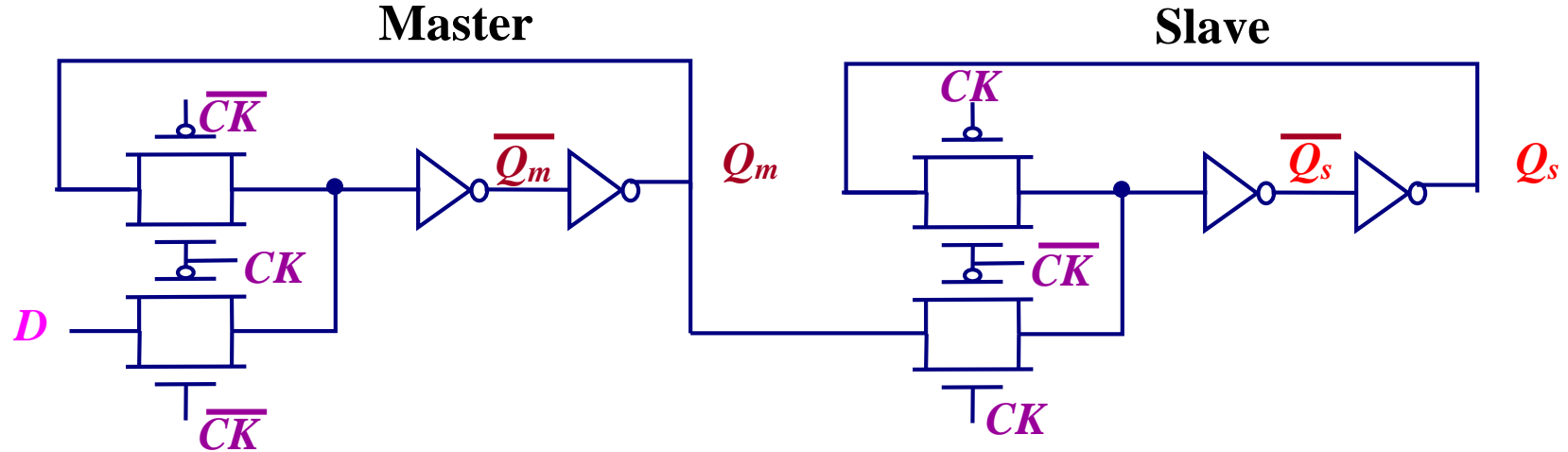Positive Edge Triggered Master-Slave Flip-Flop




For $CK=0$

 

1. $CK=0$: Master Q_m tracks current D ;
Slave Q_s =previous D sample
2. $CK=0 \rightarrow 1$: Master stores $Q_m = D$ (new D sample).

For $CK=1$

 

3. $CK=1$: Master passes $Q_m = D$ to Slave output Q_s
4. $CK=1 \rightarrow 0$: Slave locks in new D , and Master Q_m begins tracking D .

DFF Transient Response


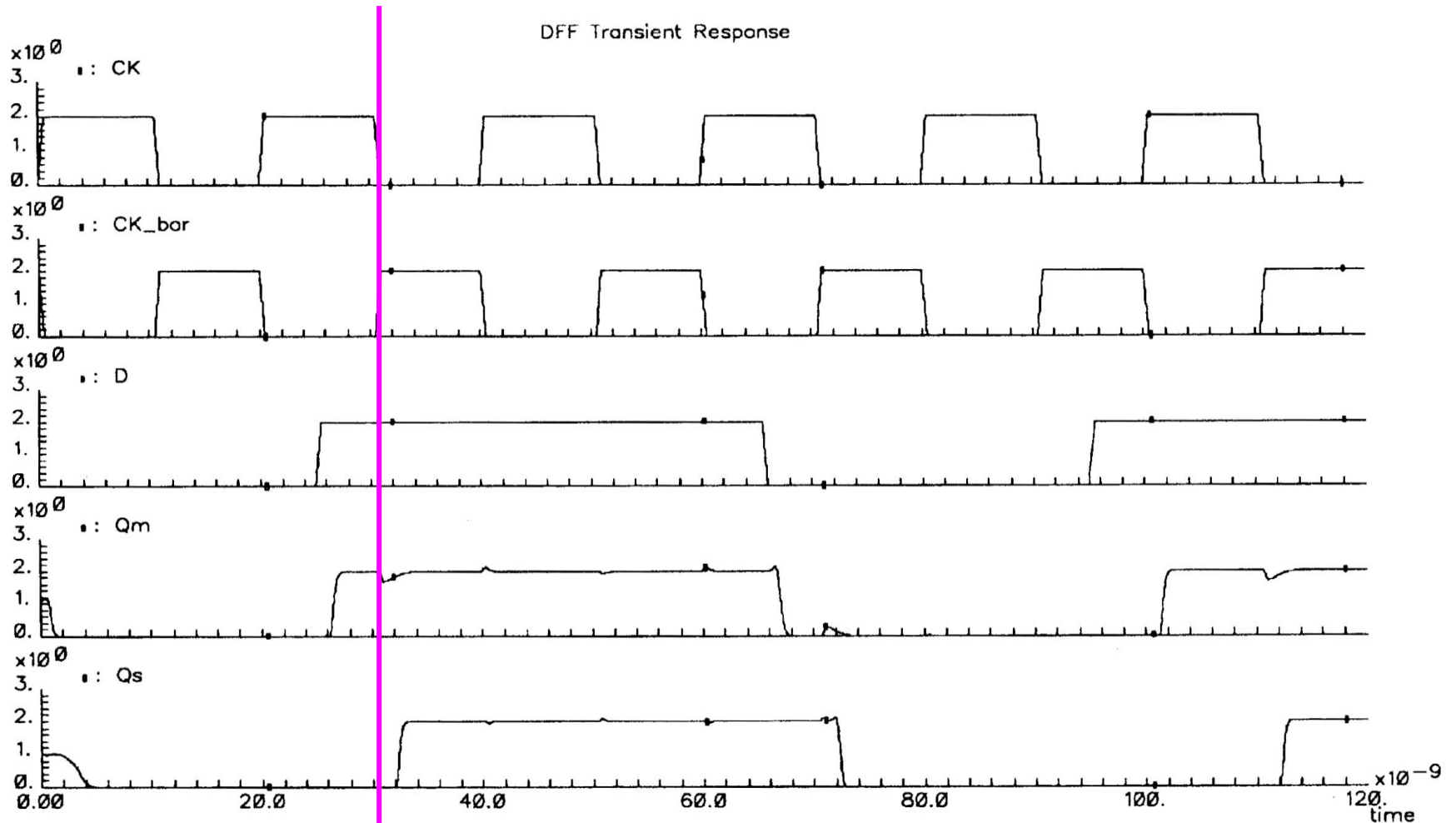


Figure 8.31 Simulated input and output waveforms of the CMOS DFF circuit in Fig. 8.30.

 


DFF Transient Response with Setup Time Violation



D Flip-Flop

Clock Skew Issues

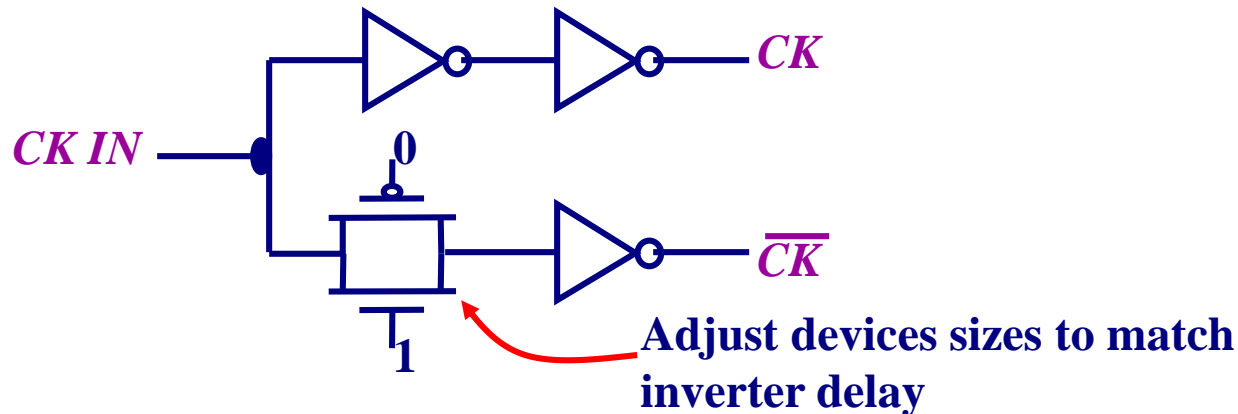- In a TG or three-state implemented flip-flop, if CK and \overline{CK} changes are *skewed (misaligned) enough*, then a change in Master can immediately propagate into Slave violating the master-slave (edge-triggered) concept.
- If global or shared drivers used, can use the following to reduce skew:





- For the global case, skew can also arise due to interconnect delay.



Non-Bistable Sequential Schmitt Trigger

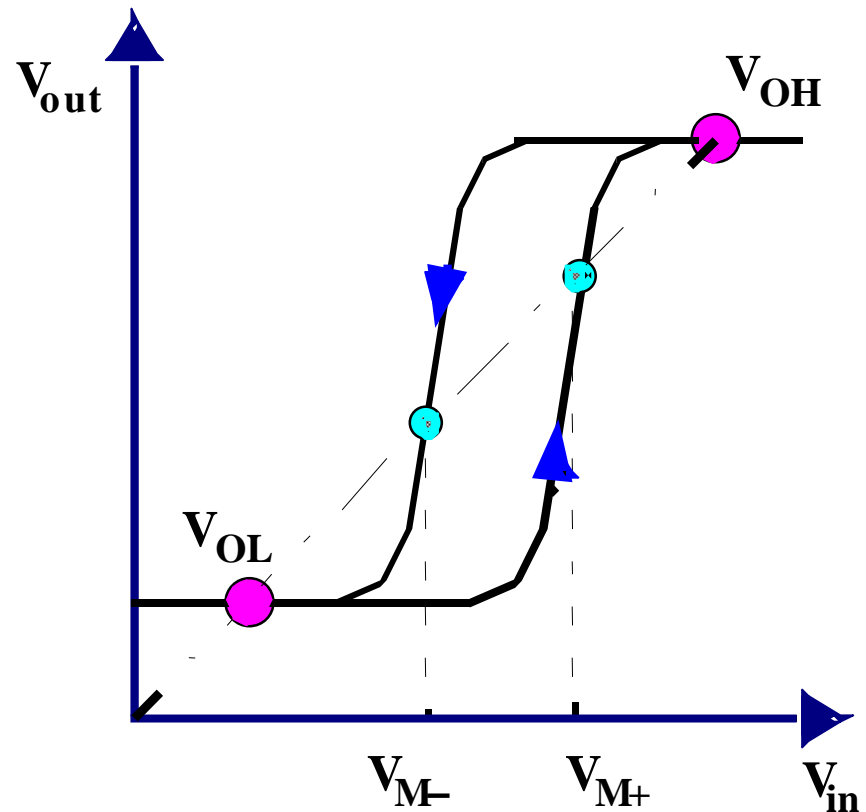 - The Schmitt trigger has an *inverter-like* voltage transfer characteristic, but with *two different threshold voltages* for increasing and decreasing input signals.




- VTC with hysteresis
- Restores signal slopes (positive feedback)




Schmitt Trigger Application

Noise Suppression

 

Schmitt Trigger


The Circuit(1)

 


Moves switching threshold of the first inverter



Schmitt Trigger Simulated VTC

 

 Voltage-transfer characteristics with hysteresis.




The effect of varying the ratio of the PMOS device M_4 . The width is $k \cdot 0.5 \mu\text{m}$.




Schmitt Trigger


The Circuit(2)

 


Multivibrator Circuits

 

 Bistable Multivibrator
flip-flop, Schmitt Trigger



Monostable Multivibrator
one-shot

 


Astable Multivibrator
oscillator


© Digital Integrated Circuits^{2nd}




Transition-Triggered Monostable

 

Astable Multivibrators (Oscillators)

 

Ring Oscillator

 

simulated response of 5-stage oscillator

© Digital Integrated Circuits^{2nd}

CMOS Digital Integrated Circuits

