



Course Title and Code Number:
 VLSI Modeling and Design (EE432)
 Fourth Year (Communications and Electronics)
 Time Allowed: 3 Hrs

اسم المقرر والرقم الكودي له: نمذجة و تصميم
 الدوائر المتكاملة ذات الكثافة العالية جداً (EE432)
 السنة الدراسية الرابعة (اتصالات و الكترونيات)
 الزمن: ٣ ساعات

MOSIS Scalable Design Rules and Verilog Quick Reference Card Are Allowed

Answer All Questions:

(75 marks)

Question One:

(15 marks)

For the layout shown in Figure 1:

- Extract the circuit schematic.
- Write the output equation. What logic function does it represent?
Hint: Construct the truth table of the circuit to realize its function.
- Respecting the design rules, estimate the layout height and width.

 


Figure 1: CMOS circuit layout

Question Two:

(15 marks)

For the CMOS inverter shown in Figure 2:

- Sketch the cross-sectional view of the inverter at the location indicated.
- Sketch the set of masks used to fabricate the inverter ordered in the fabrication sequence.
- Construct a table indicating each layer of the inverter and the fabrication processes used to create it.

 


Figure 2: CMOS inverter layout

Question Three:

(15 marks)

Write a Verilog description of the following:

- A magnitude comparator that compares between two 4-bit inputs A and B and yields two outputs: A_GT_B and A_LT_B. Use continuous assignments to build the comparator.
- Use the 4-bit comparator module developed in (a) in hierarchical fashion to build an 8-bit magnitude comparator that compares between two 8-bit inputs A and B and yields three outputs: A_GT_B, A_LT_B, and A_EQ_B. You can only use structural and dataflow modeling to build the comparator.
- A testbench to functionally verify the 8-bit comparator developed in (b).

Question Four:

(15 marks)

- Write a Verilog description of a 4-bit bidirectional counter module with asynchronous reset and synchronous load signal. Asserting the reset signal RST forces the output Q to 0 while asserting the load signal LD forces the output Q to the initial count D_IN. The following are the ports of the module:

CLK	1-bit clock input (synchronous actions performed on rising edge)
RST	1-bit reset (asynchronous reset)
UP_DOWN	1-bit input (if '1', then count up, if '0', then count down)
LD	1-bit load enable input, loads synchronized with CLK rising edge
D_IN	4-bit input data for loading counter value
Q	4-bit output

- Write a verilog procedural block to swap contents of two 8-bit registers using a temporary register. Rewrite the block to swap the two registers without using a temporary register. Declare the used registers.

Hint: Blocking Vs. Nonblocking assignments.

- Using case statement, design a 4-function ALU that has 4-bit inputs A and B and a 2-bit input select signal S, clock signal CLK, and a 5-bit output OUT. The ALU implements functions shown in Table based on the signal select. Ignore any overflow or underflow bits.

Select signal	Function
2'b00	OUT = A + B
2'b01	OUT = A - B
2'b10	OUT = A / B
2'b11	OUT = A % B

Question Five:

(15 marks)

Figure 3 shows a 4-bit rotate-right network. The input bits are $a_3a_2a_1a_0$, and the output bits are $f_3f_2f_1f_0$. The network uses four bits Ror_0, Ror_1, Ror_2, and Ror_3 to specify an n-bit right rotation ($n=0,1,2,3$).

- Modify the circuit to perform a shift-right operation that forces 0 into the empty space. Rename the control bits Ror_0 to 3 as Shr_0 to 3.
- Construct a colored stick diagram for the shifter network, Make the horizontal interconnections in Metal-1 and the vertical interconnection in Metal-2.
- Write a Verilog description of a parametric general shifter/rotator network as shown in Figure 4 .

The function of the combinational module is as follows: $f = \text{shift/rotate } (a) \text{ to the right/left by } (s) \text{ bits.}$

The following are the ports of the module:

- a n-bit input data, where $n = 2, 4, 8, \dots$
- f n-bit output data
- s m-bit input representing the shift/rotation amount, where $m = \log_2(n)$
- SH/RO 1-bit input specifying rotate or shift operation ('0' \equiv rotate and '1' \equiv shift)
- R/L 1-bit input specifying right or left shift/rotation ('0' \equiv right and '1' \equiv left)

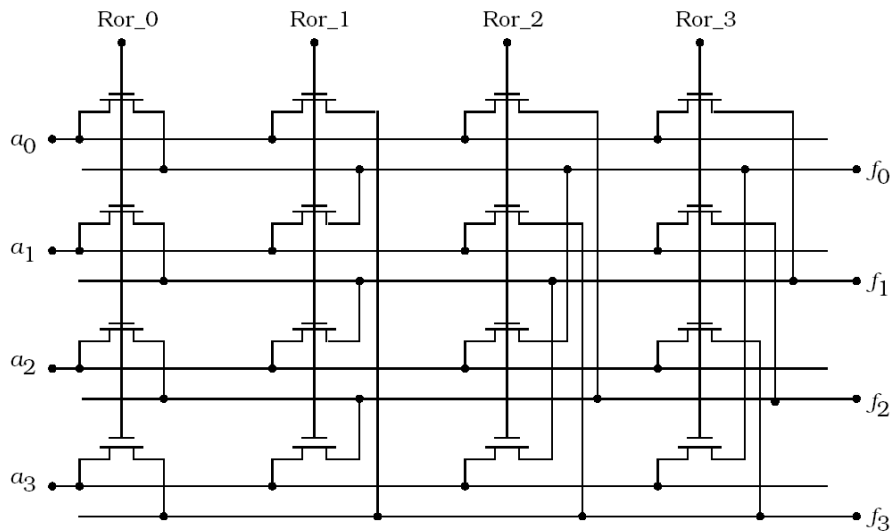


Figure 3: Rotate-right network

 


Figure 4: General shifter/rotator module

Good Luck

Examiner: *Dr. Mohammed Morsy*