



Course Title and Code Number:
 VLSI Modeling and Design (EE432)
 Fourth Year (Communications and Electronics)
 Time Allowed: 1.5 Hrs

اسم المقرر والرقم الكودي له: نمذجة و تصميم
 الدوائر المتكاملة ذات الكثافة العالية جداً (EE432)
 السنة الدراسية الرابعة (اتصالات و الكترونيات)
 الزمن: ساعة ونصف

MOSIS Scalable Design Rules Are Allowed

Answer All Questions:

(25 marks)

1. For the Layout shown below:


(5 marks)

a. What structure does it represent?

 b. The structure is to be fabricated in a scalable 1.2μm n-well CMOS process having the following parameters:

$\lambda=0.6 \mu\text{m}$, Gate-to-Channel capacitance = $1.6 \text{ fF}/\mu\text{m}^2$, Metal-to-Substrate capacitance = $0.03 \text{ fF}/\mu\text{m}^2$, Polysilicon-to-Substrate capacitance = $0.06 \text{ fF}/\mu\text{m}^2$ ($f \equiv \text{femto} \equiv 10^{-15}$).

Estimate the total capacitance associated with the structures as seen from Metal1 layer to ground. Note that the substrate is connected to ground.



2. In a scalable 0.5 μm CMOS process, it is intended to realize a resistor in a polysilicon layer. The process has the following parameters:

(5 marks)

$\lambda=0.25 \mu\text{m}$, Poly sheet resistance $R_s=25\Omega$, Poly-to-Substrate capacitance = $0.12 \text{ fF}/\mu\text{m}^2$.

If the chip area allocated for the resistor is $10 \mu\text{m} \times 10 \mu\text{m}$,

- Layout the poly layer in this area in such a way that a maximum resistance is attained (use λ -based design rules).
- Calculate the maximum attainable resistance and the associated parasitic capacitance. Note that a straight-square has a resistance R_s while a corner-square has a resistance of $0.65R_s$.
- Estimate the propagation delay time of such a structure.

Password: Snake

3. Consider the AOI logic function:

(7 marks)


$$f = \overline{a \cdot (b + c \cdot (d + e))}$$

- Design a CMOS circuit realizing this function using the fewest number of transistors.
- Is it possible to find an equivalent nFET and pFET Euler paths for the circuit? If so, construct a colored stick diagram layout. If not, find a layout strategy and construct the corresponding stick diagram.
- Determine the transistor sizes relative to β_n and β_p such that the logic circuit has approximately the same propagation delays as an inverter with $\beta_n = \beta_p$.

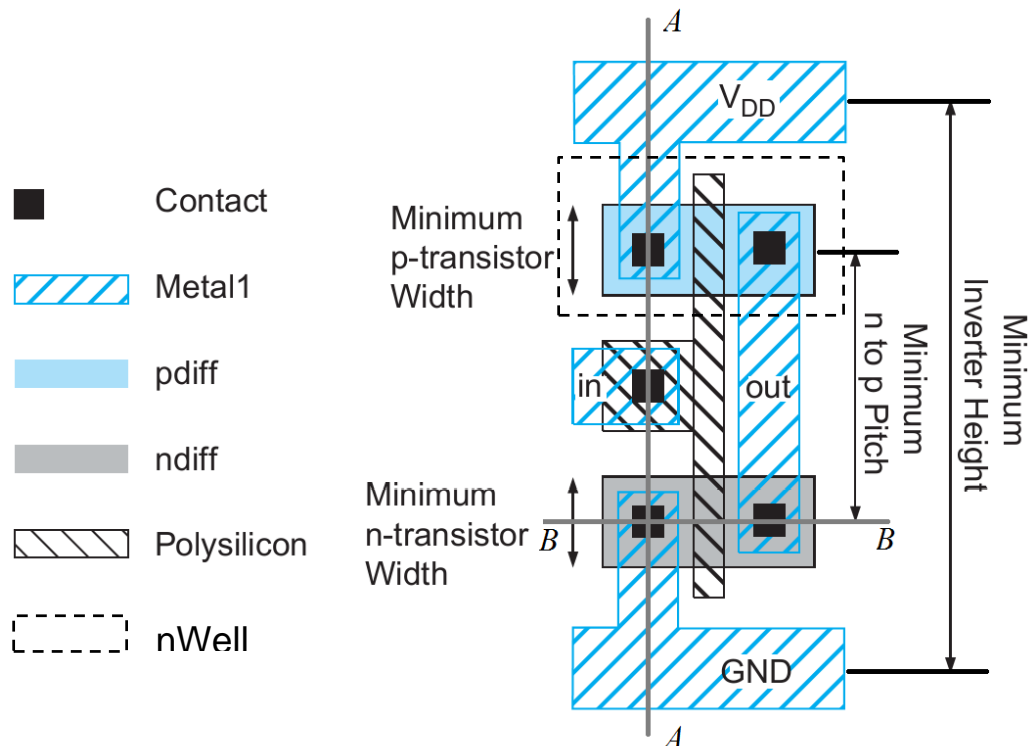4. For the Layouts shown in Figure 3:

(8 marks)

- Sketch the cross-sectional views of the layouts at the locations indicated.
- Calculate the minimum n to p pitch and the minimum inverter height with and without the poly contact to the gate (in). Use MOSIS scalable design rules.
- Briefly describe the physical limitations and potential problems associated with four design rules of different classes.



Good Luck

Examiner: Dr. Mohammed Morsy