




MOSIS Scalable Design Rules Are Allowed

Answer Only Two Questions:

(25 marks)

 1. The following Figure shows an example of using the fingering strategy to layout MOSFETs with large aspect ratio. This strategy is used to get a square-shape layout. **(15 marks)**
 - a. Draw a schematic representation of this layout and explain how it is equivalent to a MOSFET with large aspect ratio.
 - b. Sketch the layout of a MOSFET with aspect ratio of 9 using the fingering strategy.
 - Attempt to keep the layout aspect ratio near to 1.
 - Minimize the layout area while respecting MOSIS design rules.
 - c. The structure is to be fabricated in a scalable 1.2 μm n-well CMOS process having the following parameters:
 - Gate-to-Channel capacitance =1.6 fF/ μm^2 , Metal1-to-Substrate capacitance=0.03 fF/ μm^2 , Metal1-to-Poly capacitance=0.05 fF/ μm^2 , and Polysilicon-to-Substrate capacitance=0.06 fF/ μm^2 .
 - Substrate sheet resistance=100 Ω , Active sheet resistance=10 Ω , Poly sheet resistance=4 Ω , Metal1 sheet resistance=2 Ω , and contact resistance=1 Ω .

Draw the transistor equivalent circuit indicating approximate values of the resistors and capacitors. Assume that the substrate and source are connected to ground.



2. Consider the following logical function. (15 marks)

$$w_1 = \overline{a + b.c + d.e}, \quad w_2 = \overline{f \oplus g}$$

$$result = \overline{w_1 . w_2 . h}$$

The inputs are $a, b, c, d, e, f, g,$ and $h,$ the output is $result,$ and w_1 and w_2 are internal signals. Exclusive-OR is shown as \oplus .

- Design a CMOS circuit realizing this function using the fewest number of transistors.
- Is it possible to find an equivalent nFET and pFET Euler paths for individual circuits? If so, construct a colored stick diagram layout. If not, find a layout strategy and construct the corresponding stick diagram. You can use two-layer of metals if needed.

Follow these I/O constraints exactly:


- Please make Vdd and GND run horizontally across the circuit in metal1.
- Please make the inputs, a; b; c; d; e come from the left in metal1
- Please make the inputs, f; g; h come from the right in metal 1
- Please make the output "result" exit to the right in metal 1

(Note: Please use an entire page for the stick diagram.)

- Can you layout the $result$ logical function in a smaller area? If so, explain without plotting how to do that.

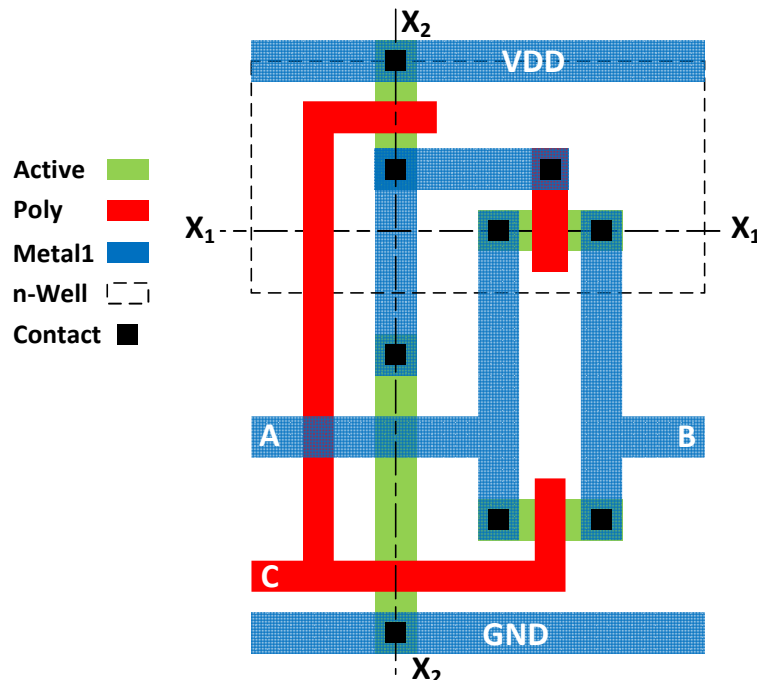3. For the Layouts shown in the following Figure: (10 marks)

- Draw the schematic representation and write the logical function equation.
- Sketch the cross-sectional views of the layouts at the locations indicated.
- Calculate the minimum cell height and width. Use MOSIS scalable design rules.



Good Luck

Examiner: **Dr. Mohammed Morsy**