



GENERAL VLSI SYSTEM COMPONENTS


Dr. Mohammed M. Farag




Faculty of Engineering
Alexandria University




Multiplexers

 

Gate-level NAND 2:1 multiplexor.

 


(a) TG circuit

 


(b) Pass transistors

Multiplexor using switch logic.

 

(a) Symbol

(b) Logic diagram


 


Gate-level 4:1 MUX

A 4:1 MUX using instanced 2:1 devices.



Multiplexers (2)

  


4:1 MUX using nFET pass transistors.

Simple 4:1 pass-FET MUX layout.




Multiplexers (3)

 


Split-array 4:1 MUX for full-rail output.



Multiplexers (4)

 


(a) Symbol

 

(b) Bit-level realization


A vector 2:1 MUX.

 


Single-bit cell tiling for an 8-bit 2:1 MUX.



Decoders

 

(a) Symbol and table

 


(b) NOR2 implementation


An active-high 2/4 decoder.



Decoders (2)

 

(a) Symbol and table


 


(b) NAND2 implementation

Active low 2/4 decoder.





Comparators

 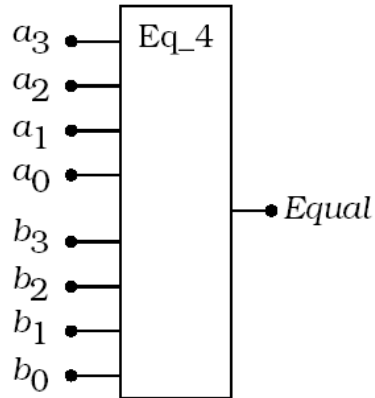


a 4-bit equality detector.

8-bit equality detector.

  



Comparators (2)

 



4-bit magnitude comparator logic.

Comparator output summary.

Condition	GT	LT
$a > b$	1	0
$a < b$	0	1
$a = b$	0	0



Comparators (3)

  


Comp 8 logic diagram.

Additional logic for A_EQ_B
and Enable features.




Comparators (4)

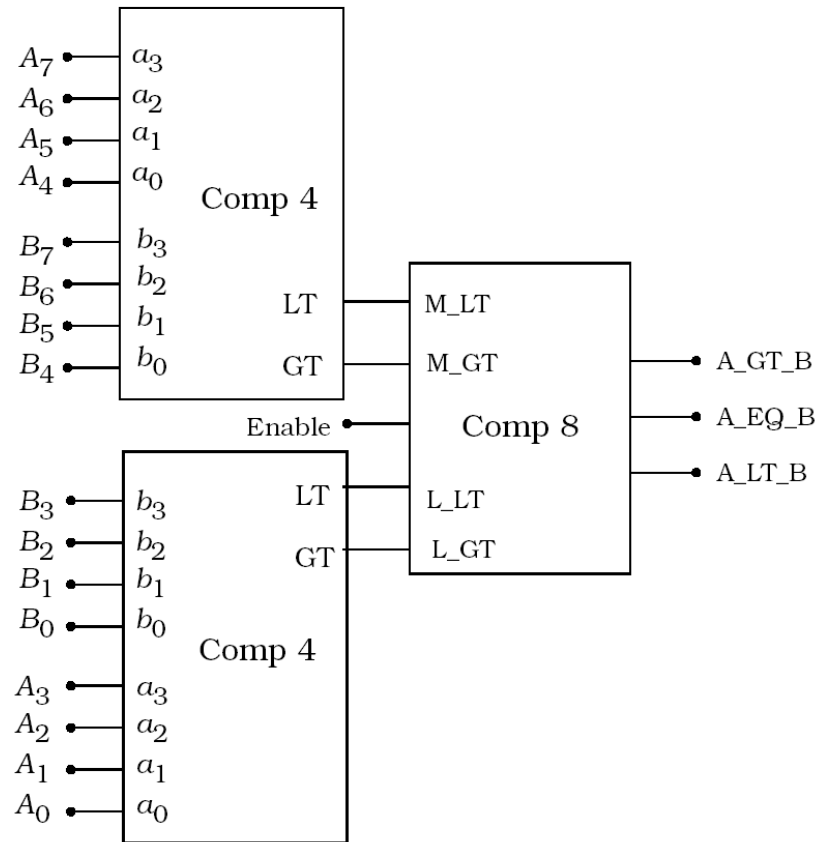

8-bit comparator system.



Encoders

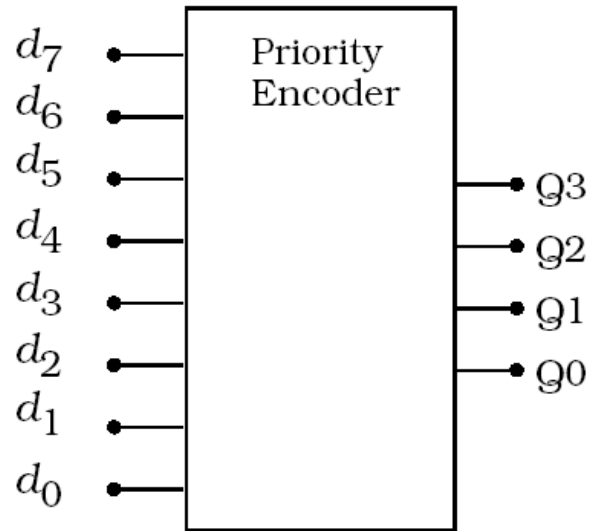

d_7	d_6	d_5	d_4	d_3	d_2	d_1	d_0	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	0	0	1	1	0	0	0
0	0	0	0	0	0	1	-	1	0	0	1
0	0	0	0	0	1	-	-	1	0	1	0
0	0	0	0	1	-	-	-	1	0	1	1
0	0	0	1	-	-	-	-	1	1	0	0
0	0	1	-	-	-	-	-	1	1	0	1
0	1	-	-	-	-	-	-	1	1	1	0
1	-	-	-	-	-	-	-	1	1	1	1
0	0	0	0	0	0	0	0	0	0	0	0

d_7 has highest priority
 d_0 has lowest priority


$Q_3 = 1$ when $d_i = 1$
 for any $i = 0, \dots, 7$

Symbol for priority encoder

Function table for an 8-bit priority encoder.




Encoders (2)

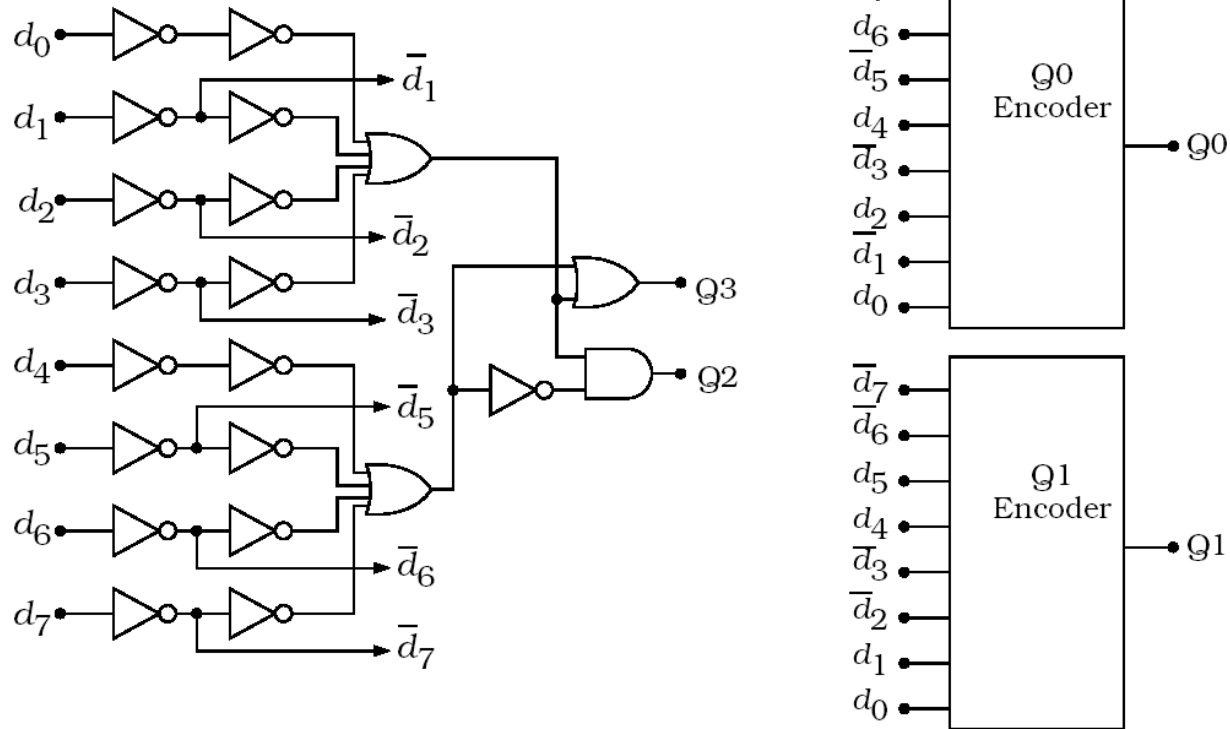


Logic diagram for the priority encoder.



Encoders (3)

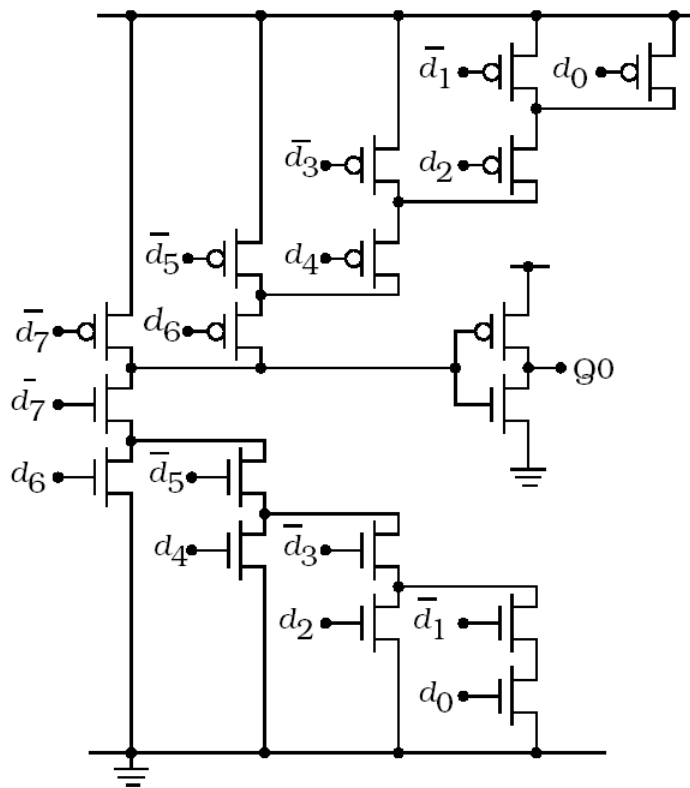

(a) Q0 circuit

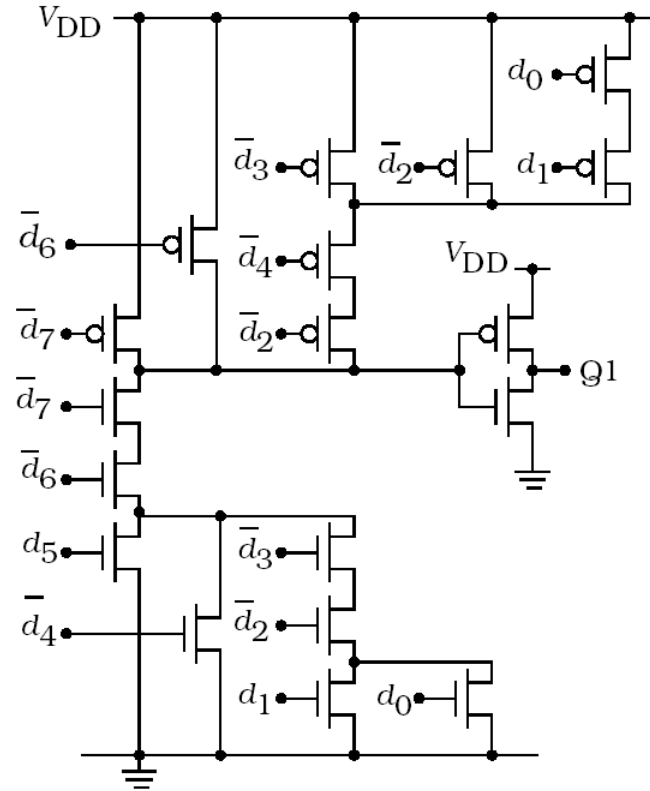


(b) Q1 circuit


Q0 and Q1 circuits for the 8-bit priority encoder.



Rotators and Shifters

 


General rotator.

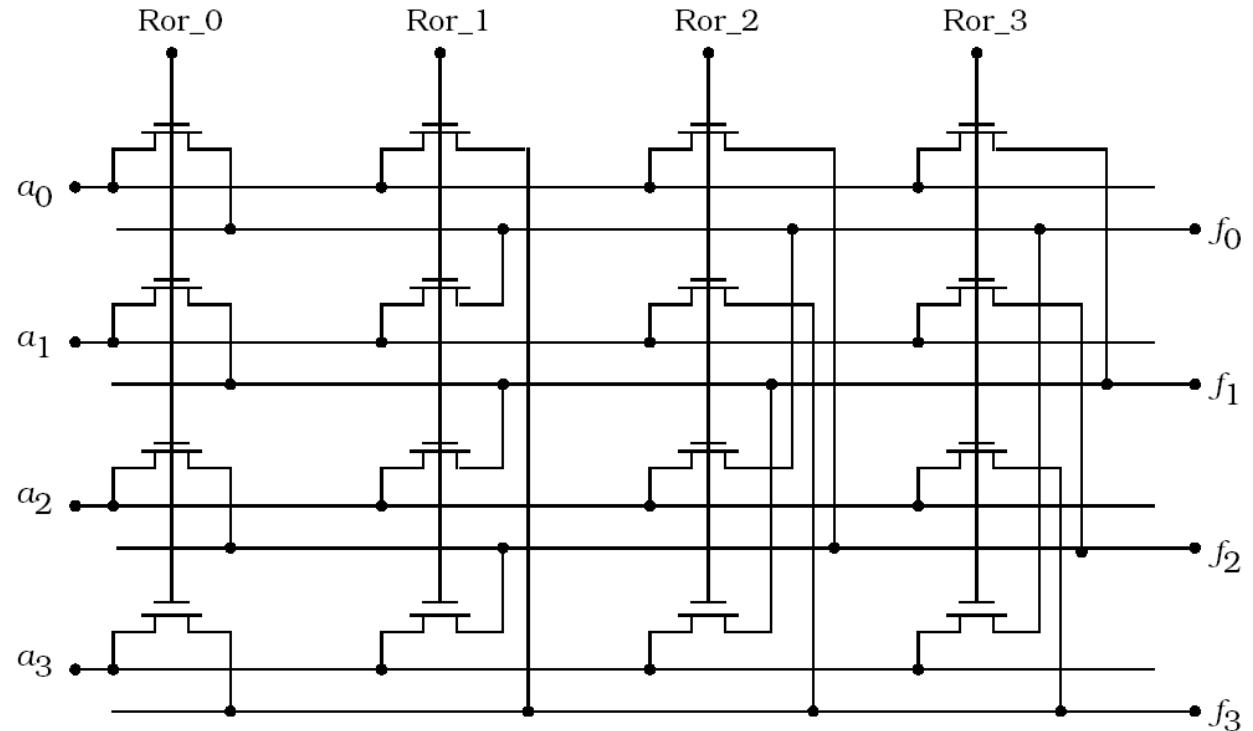

A 4-bit rotate-right network.




Rotators and Shifters (2)

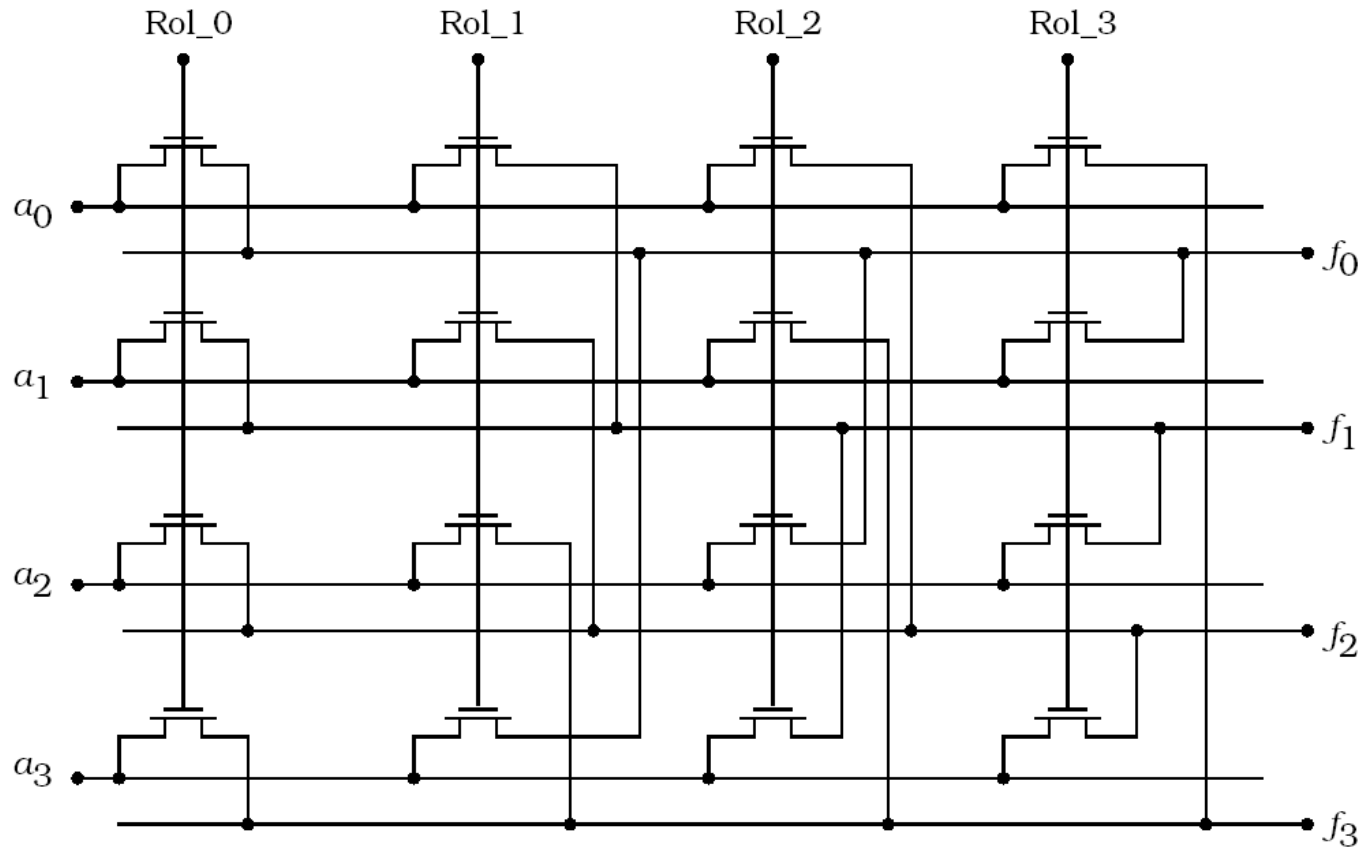


Left-rotate switching array.



Rotators and Shifters (3)

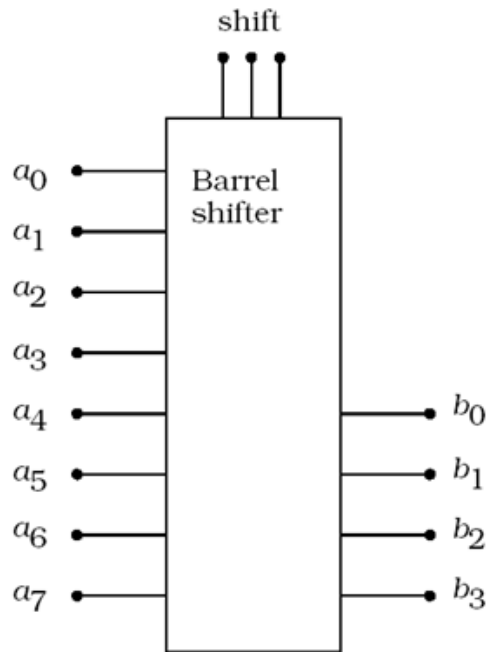

shift	$b_0b_1b_2b_3$
0	$a_0a_1a_2a_3$
1	$a_1a_2a_3a_4$
2	$a_2a_3a_4a_5$
3	$a_3a_4a_5a_6$
4	$a_4a_5a_6a_7$

 


An 8 X 4 barrel shifter.


FET-array barrel shifter.




Latches and Flip-Flops

 

(a) Symbol

 


(b) Logic diagram

 


CMOS circuit for a D-latch.


D-latch.

 

(a) Symbol

 

(b) Logic diagram

 


Gated D-latch with Enable control.


AOI CMOS gate for D-latch with Enable.



Latches and Flip-Flops (2)


 


(a) Bistable circuit

 


(b) Ring oscillator

Closed-loop inverter configurations.

  

(a) Stable states

 


(b) CMOS circuit


Operation of a bistable circuit.



Latches and Flip-Flops (3)

 


(a) Receiver circuit

 


 (b) Controlled loading

Adding an input node to the bistable circuit.



(a) CMOS TG version

 


(b) nFET pass gates


D-latch using oppositely phased switches.



Latches and Flip-Flops (4)

 

(a) Load with $C = 1$

 


(b) Hold with $C = 0$


Operation of the D-latch.



Latches and Flip-Flops (5)

 

(a) C²MOS static latch


 


(b) Dynamic latch


C²MOS-based D-latch circuits.




Latches and Flip-Flops (6)

 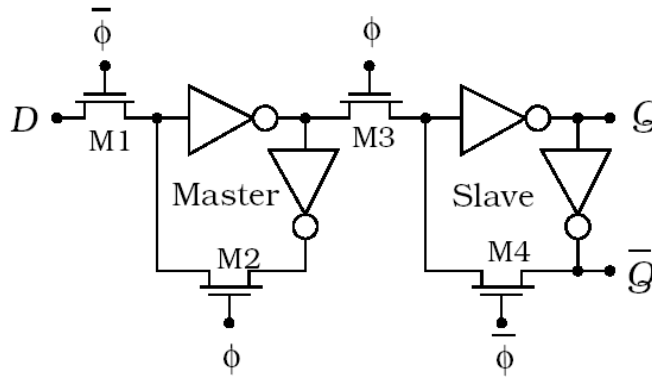

Master-slave D-type flip-flop.

 

(a) Positive edge-triggered DFF

 


(b) Negative edge-triggered DFF

Edge-triggered DFF symbols.





Latches and Flip-Flops (7)

 



Alternate circuitry for the master-slave DFF.



Latches and Flip-Flops (8)

  

(a) DFF with direct Clear

  


(b) DFF with direct Clear and Set

DFF circuits with assert-low Clear and Clear/Set controls.




Latches and Flip-Flops (9)

 


DFF modified to a TFF circuit using feedback.



Latches and Flip-Flops (10)

 

(a) Wiring diagram

 


(b) Symbol


D-type flip-flop with *Load* control.




Latches and Flip-Flops (II)

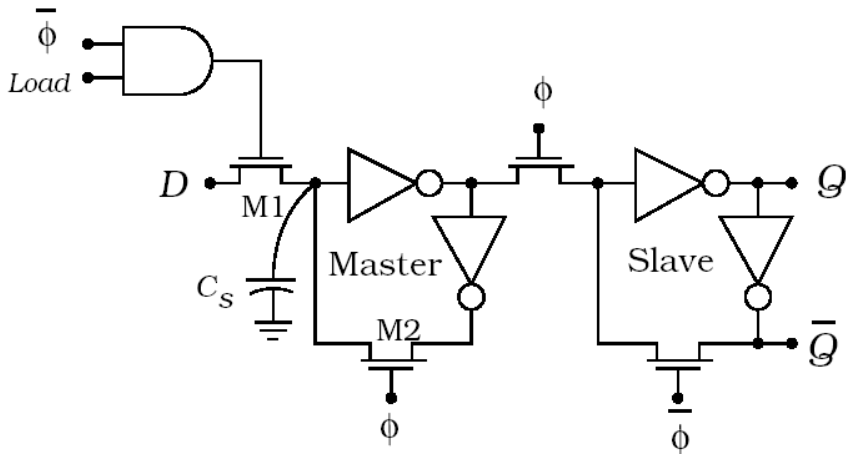


CMOS master-slave FF with Load control.

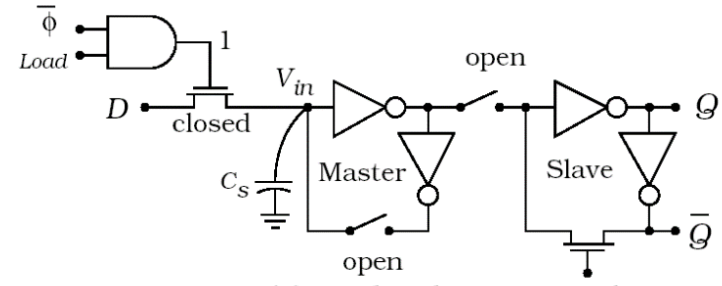

(a) Load with $\phi = 0$, Load = 1

 

(b) Hold with $\phi = 1$, Load = 0

 


(c) Hold with $\phi = 0$, Load = 0


Operation of the CMOS DFF with load control.



Registers

 

(a) Internal construction

 


(b) Basic symbol

Construction of an n -bit register.



Registers (2)

 

One-bit static multiport register circuit.

An n -bit static multiport register.

