



# SYSTEM SPECIFICATIONS USING VERILOG HDL

Dr. Mohammed M. Farag



**Faculty of Engineering  
Alexandria University**



# Static Random Access Memory, SRAM

- SRAM : cells use a simple bi-stable circuit to hold a data bit
  - ▣ Three states: hold, write, and read operations



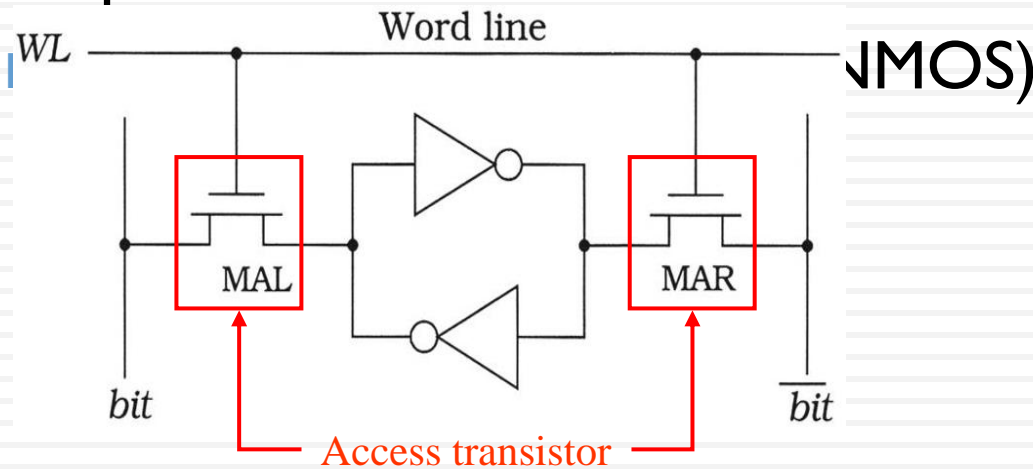


Figure 13.1 General SRAM cell

 

(a) 6T cell

 

(b) 4T cell with poly resistors

Figure 13.2 CMOS SRAM circuits



# SRAM (1/2)


 



Figure 13.3 6T SRAM cell design parameters

 

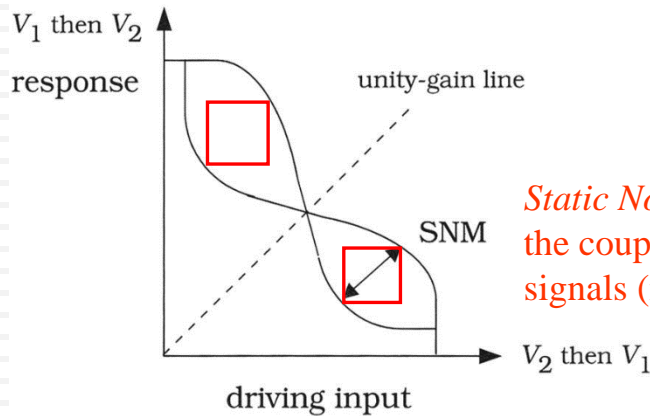(a) Write 1 operation


Write 1: in worst case,  
 $V_1 = 0, V_2 = V_{DD}$   
 $\rightarrow (\beta_A / \beta_n = 2)$   
 Why??

$$\frac{(W/L)_{nA}}{(W/L)_n} \quad (13.1)$$



**Static Noise Margin: immunity**  
 the coupled electromagnetic  
 signals (noise)

Figure 13.4 Butterfly plot

 

(b) Resistor model

Figure 13.5 Writing to an SRAM



# SRAM (2/2)

S: Source  
D: Drain

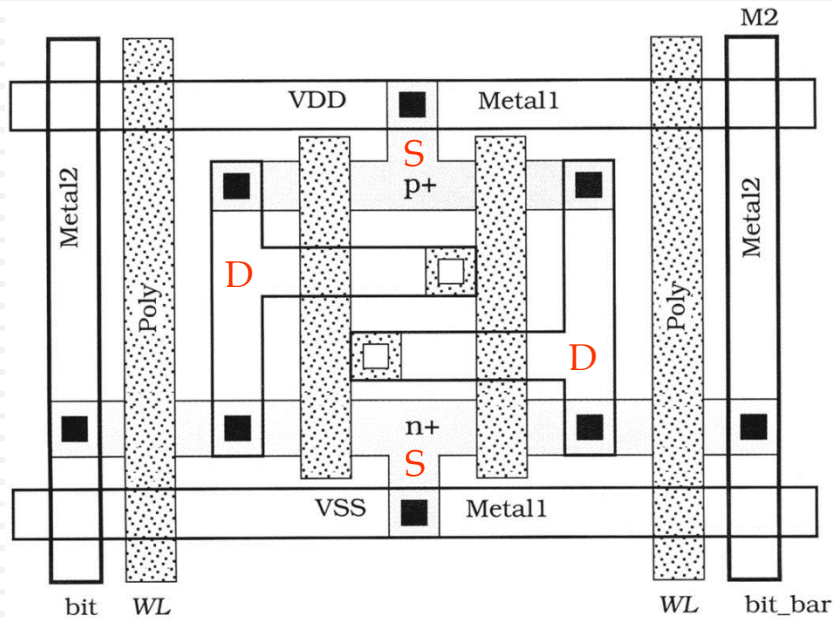


Figure 13.6 Example of a basic 6-T SRAM cell layout

 


Figure 13.7 A 2-port CMOS SRAM cell

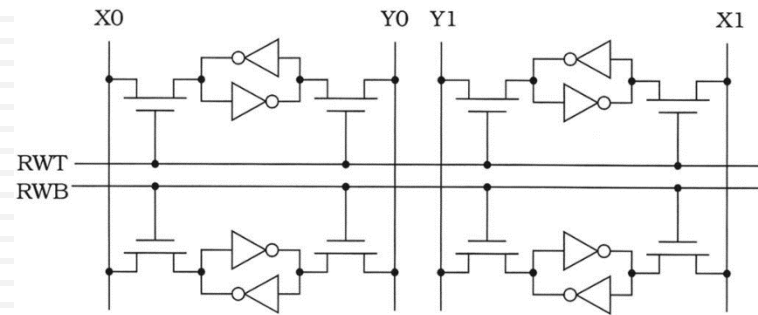


Figure 13.8 4-cell SRAM group



# Outline

- The Static RAM
- **SRAM Arrays**
- Dynamic RAM
- ROM Arrays
- Logic Arrays



# SRAM Arrays (1/4)

 


Figure 13.9 High-level view of an SRAM

 


Figure 13.11 Cell arrangement in a core region

 


Figure 13.10 Central SRAM block architecture

 


Figure 13.12 Row driver circuit



# SRAM Arrays (2/4)

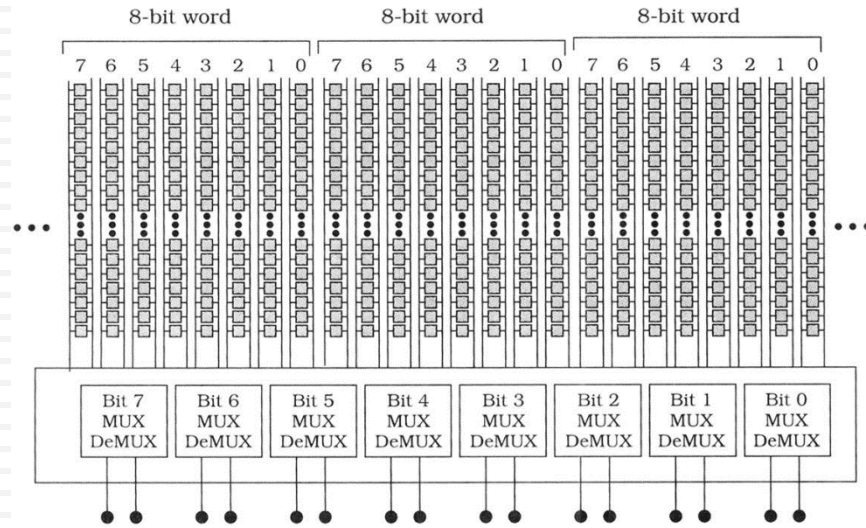


Figure 13.13 Column MUX/DeMUX network for 8-bit words

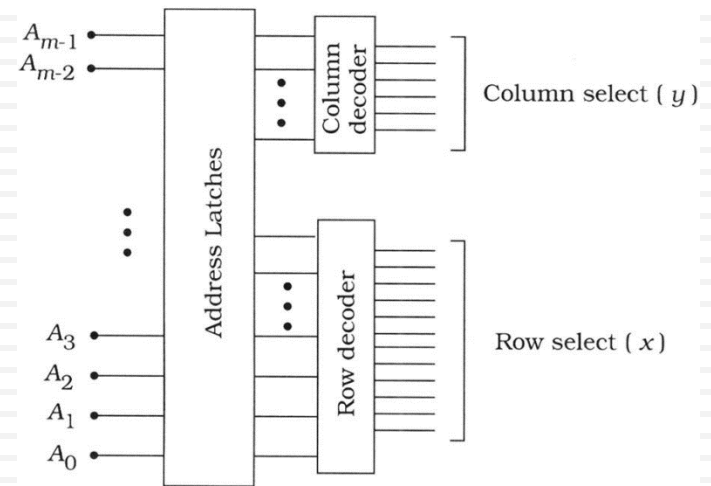


Figure 13.15 Basic addressing scheme

 


Figure 13.14 Logic 1 column driver

 


Figure 13.16 Address latch circuit



# SRAM Arrays (3/4)

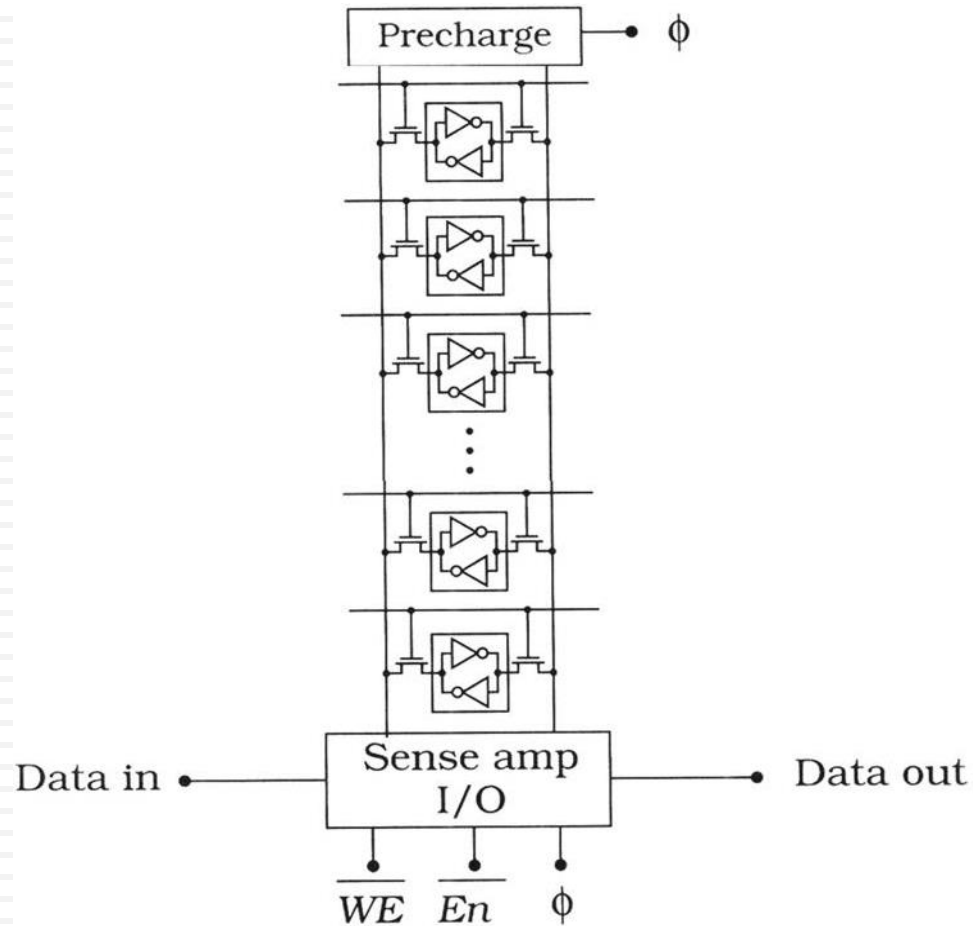


Figure 3.17 Pre-charge and I/O circuit for a single column





# SRAM Arrays (4/4)

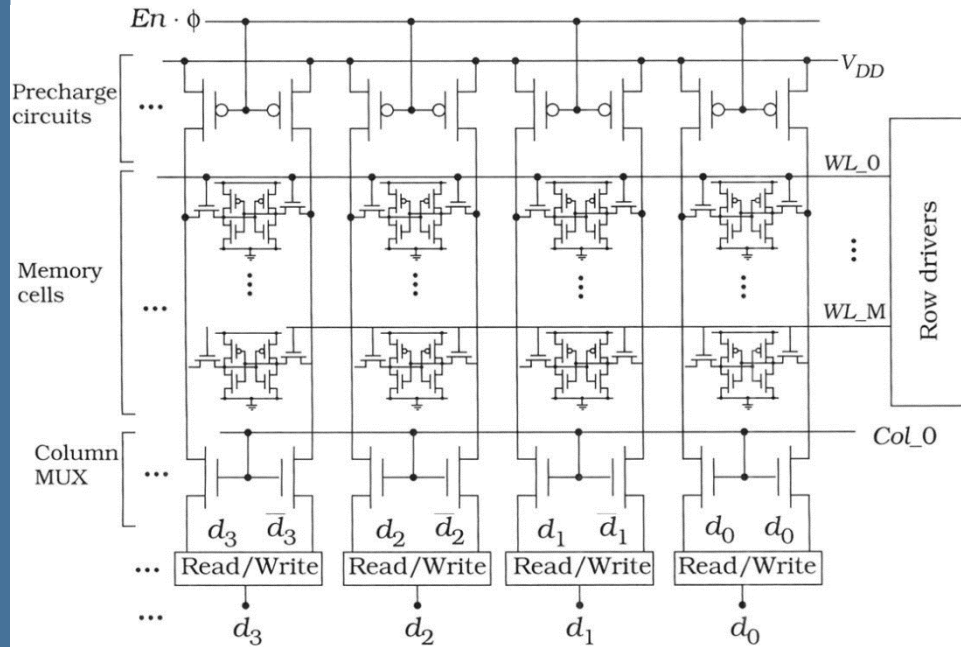


Figure 3.18 Expanded view of column circuitry

 


Figure 13.19 Write circuitry example



# Sensing Operation


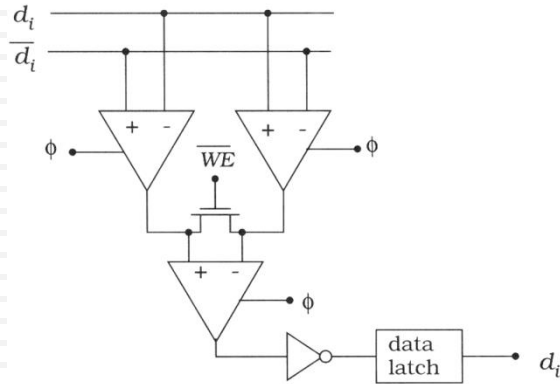


Figure 3.20 Example of a sensing scheme for the read operation

$$v_d = (v^+ - v^-) \quad (13.5)$$

$$v_{out} = Av_d = A(v^+ - v^-) \quad (13.6)$$
 
$$I_{SS} = I_{D1} + I_{D2} \quad (13.7)$$



(a) Circuit diagram

(b) Current flow

Figure 3.21 Single-ended differential amplifier


 


Figure 3.22 Dual-amplifier scheme for the sense amplifier network

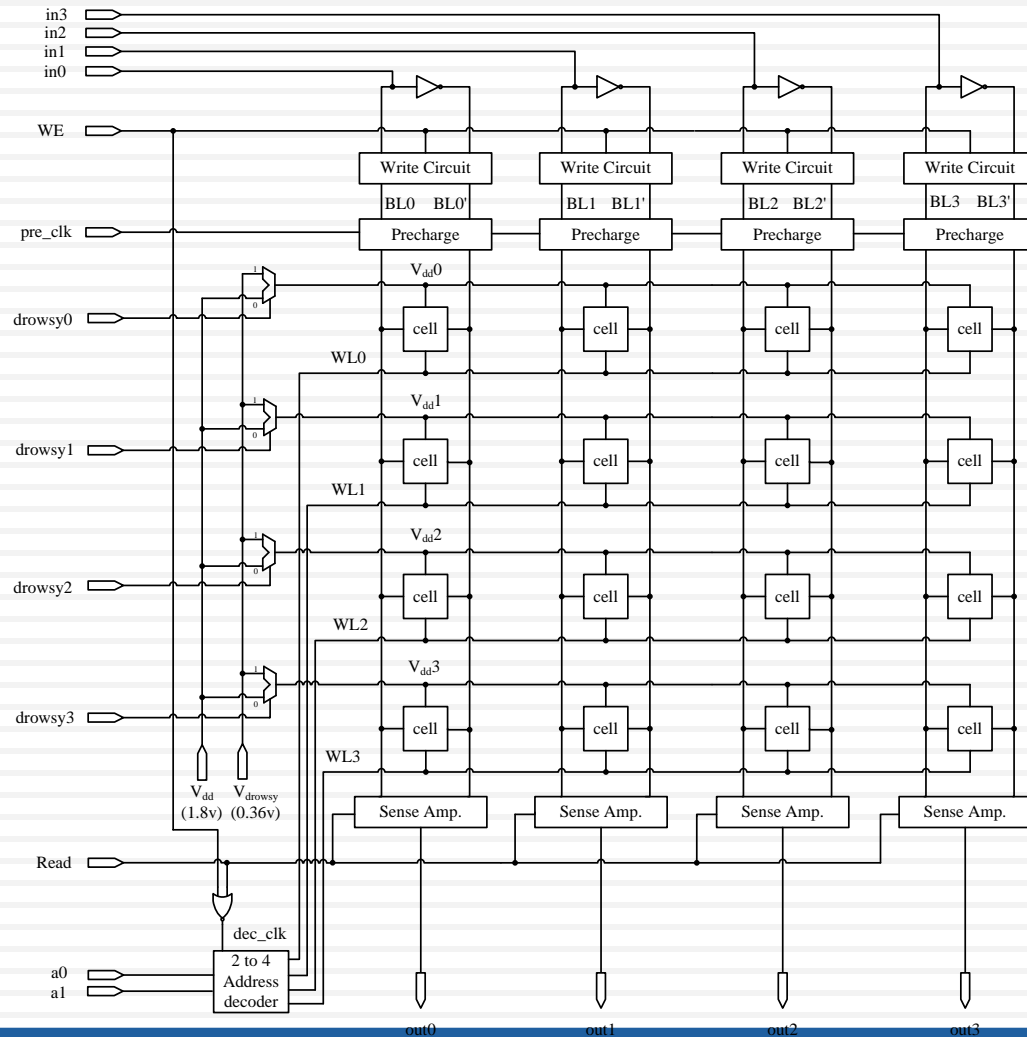

# An example: A Drowsy SRAM





# Outline

- The Static RAM
- SRAM Arrays
- **Dynamic RAM**
- ROM Arrays
- Logic Arrays



# DRAM (1/3)

## Dynamic RAM (DRAM)

- Smaller than SRAM cells
- Higher density storage arrays

As the central system memory in microcomputer systems

$$Q_s = C_s V_s \quad (13.8)$$

For writing 1,  $V_s = V_{max} = V_{DD} - V_{Tn}$  (13.9)

$$V_s = V_{max} = V_{DD} - V_{Tn} \quad (13.9)$$

Require more peripheral circuitry (13.10)


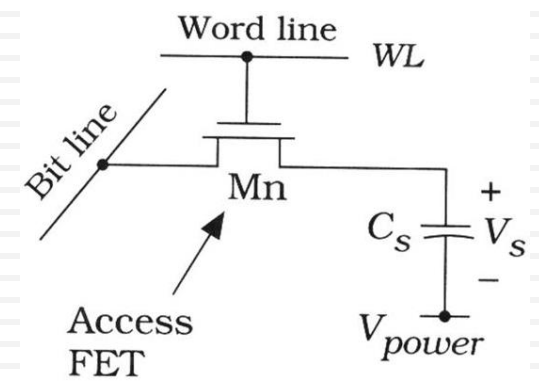


Figure 13.23 1T DRAM cell

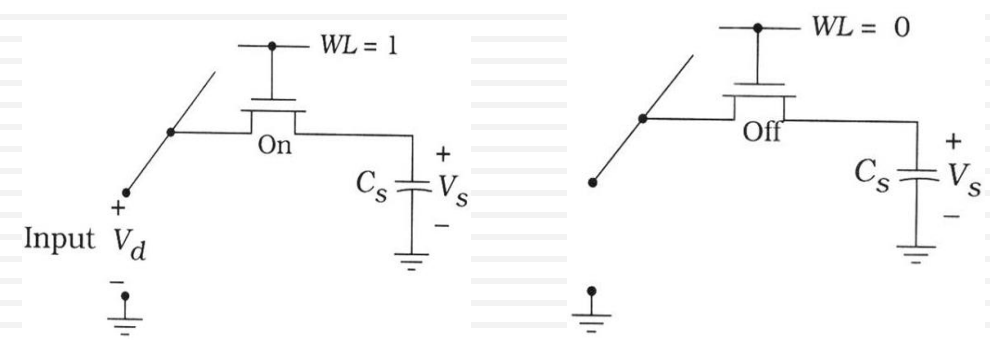

(a) Write operation

(b) Hold

Figure 3.24 Write and hold operations in a DRAM cell



# DRAM (2/3)

□ **Charge Leakage:** When  $V_G < V_T$ , a MOSFET is cutoff but still admits small leakage currents

$$I_L = -\left(\frac{dQ_s}{dt}\right) \quad (13.11)$$

$$I_L = -C_s \left(\frac{dV_s}{dt}\right) \quad (13.12)$$

$$I_L \approx -C_s \left(\frac{\Delta V_s}{\Delta t}\right) \quad (13.13)$$

$$t_h = |\Delta t| \approx \left(\frac{C_s}{I_L}\right) (\Delta V_s) \quad (13.14) \text{ (hold time or retention time)}$$

$$t_h = \left(\frac{50 \times 10^{-15}}{1 \times 10^{-9}}\right) (1) = 0.5 \mu s \quad (13.15) \text{ (} I_L = 1 \text{ nA, } C_s = 50 \text{ fF, and } \Delta V_s = 1 \text{ V)}$$

$$f_{refresh} \approx \frac{1}{2t_h} \quad (13.16) \text{ (refresh frequency)}$$

 


Figure 3.25 Charge leakage in a DRAM cell

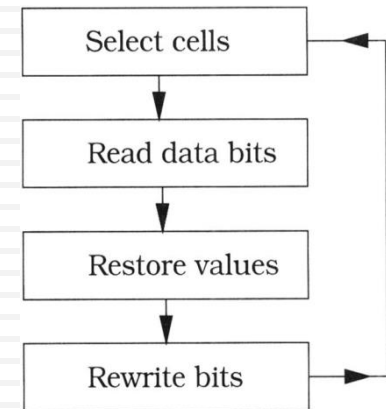


Figure 3.26 Refresh operation summary



# DRAM (3/3)

 


Figure 3.26 Read operation in a DRAM cell

$$Q_s = C_s V_s \quad (13.17)$$

$$Q_s = C_s V_f + C_{bit} V_f \quad (13.18)$$

$$V_f = \left( \frac{C_s}{C_s + C_{bit}} \right) V_s \quad (13.19)$$

 


Figure 3.28 A DRAM cell using a trench capacitor


 


Figure 13.29 Visualization of stacked capacitor structure

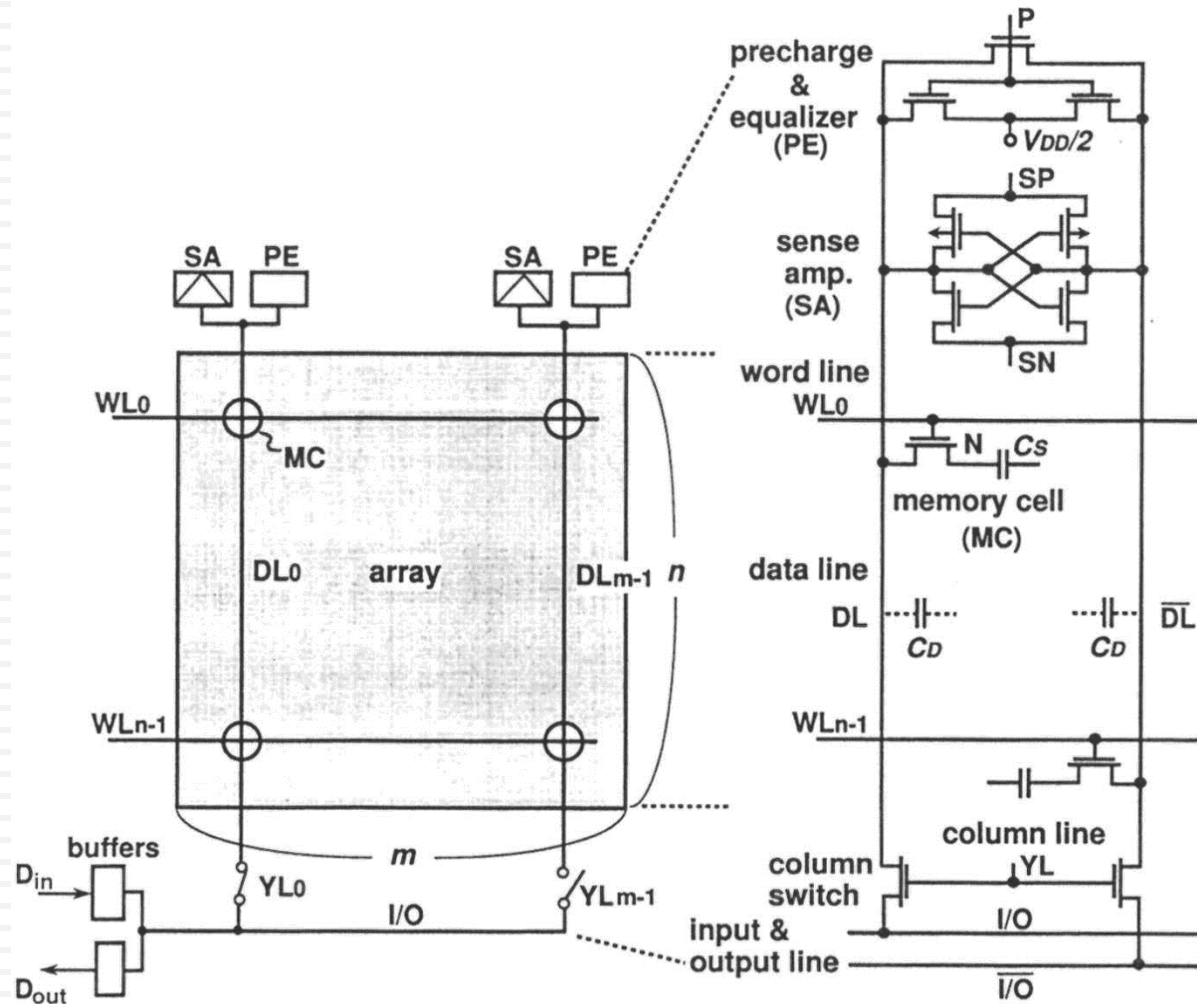

# DRAM Array and Peripheral Circuit







# Divided-Word Line Architectures

 


Figure 13.30 Basic for a divided-word line architecture RAM layout

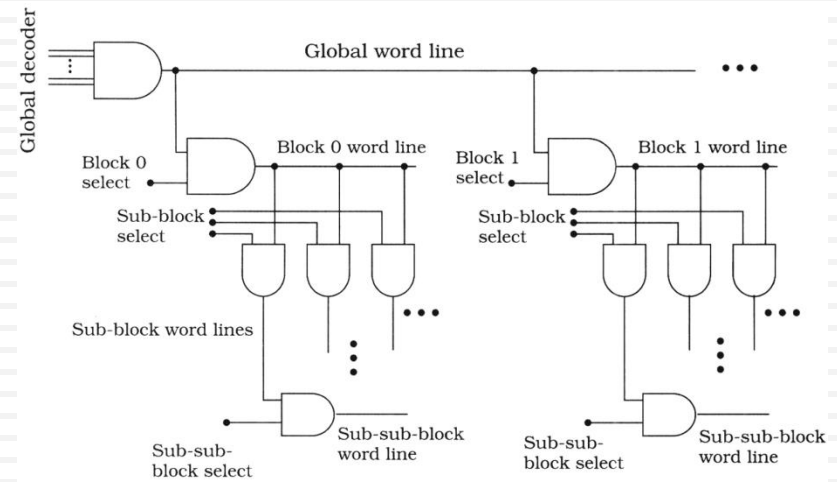


Figure 13.31 Logic for a DWL design



# Outline

- The Static RAM
- SRAM Arrays
- Dynamic RAM
- **ROM Arrays**
- Logic Arrays



# ROM

 


Figure 13.33 Logic diagram for a NOR-based ROM

 


Figure 13.35 Map for ROM layout

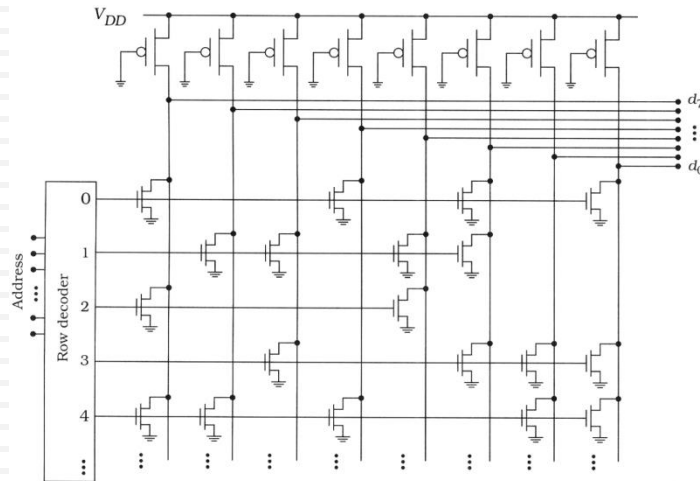


Figure 13.34 ROM array using pseudo-nMOS circuitry


 


Figure 13.36 ROM layout based on FET map

 


# User-Programmable ROMs


- Electrically-erasable EPROMs (E<sup>2</sup>PROMs) are used to store the BIOS code in PC, and allow the user to up




(a) Symbol

 

(b) Structure

 

(a) Normal  $V_{Tn}$  state

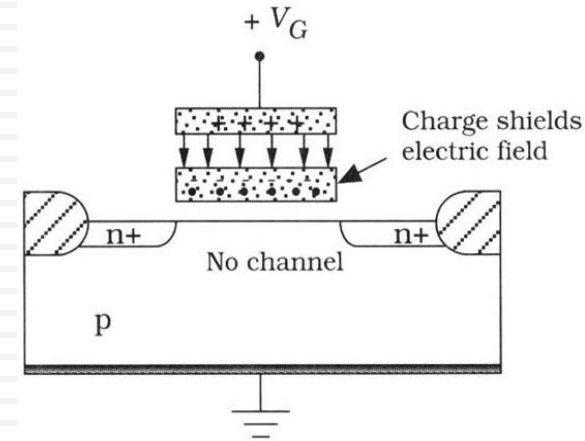

(b) Increased  $V_{Tn,H}$  state

Figure 13.33 Logic diagram for a NOR-based ROM



# E<sup>2</sup>PROMs

 


Figure 13.39 A E<sup>2</sup>PROM word using floating-gate nFETs

 


Figure 13.41 Fowler-Nordheim tunnelling

 


Figure 13.40 Programming a floating-gate FET

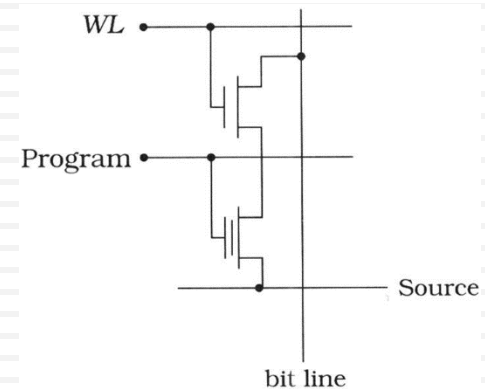


Figure 13.42 EEPROM cell with write line



# Outline

- The Static RAM
- SRAM Arrays
- Dynamic RAM
- ROM Arrays
- **Logic Arrays**



# Programmable Logic Array, PLA (1/2)

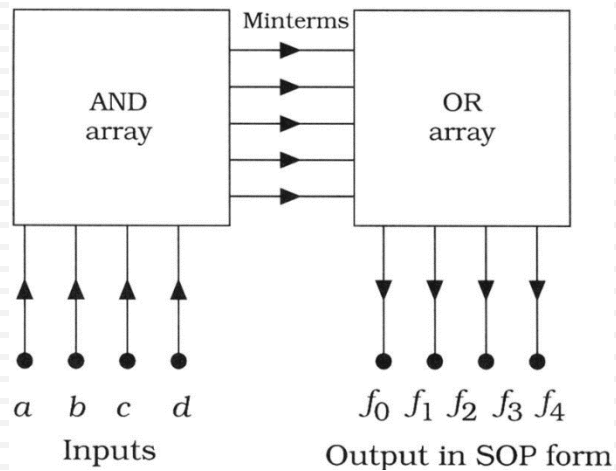


Figure 13.43 Structure of an AND-OR PLA


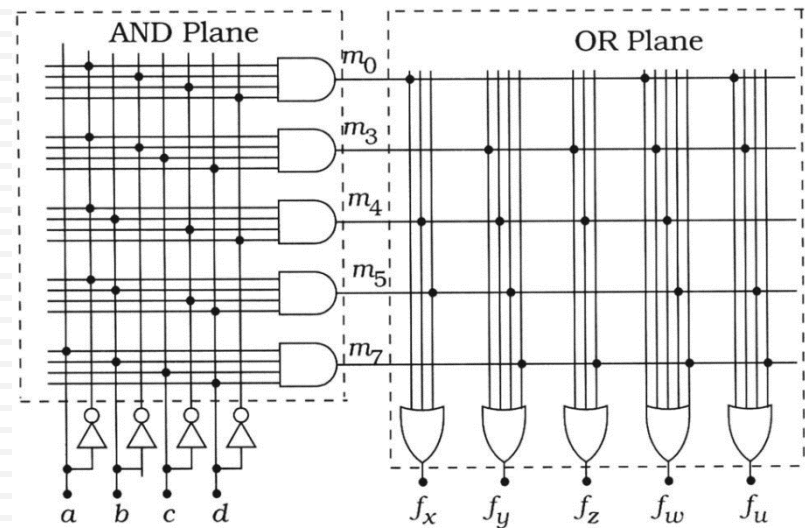



Figure 13.44 Logic gate diagram of the PLA

 

# Programmable Logic Array, PLA (2/2)



(a) AND-OR logic

 

(b) NOR-based logic

Figure 13.45 NOR-gate PLA logic

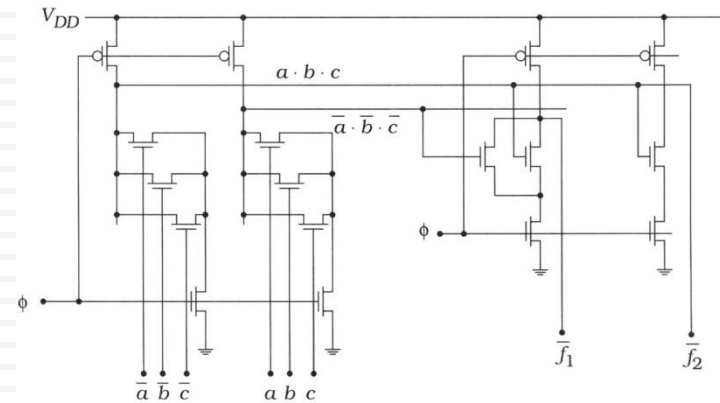


Figure 13.46 A dynamic CMOS PLA based on NOR gates


 


Figure 13.47 Generic NOR-based logic plane

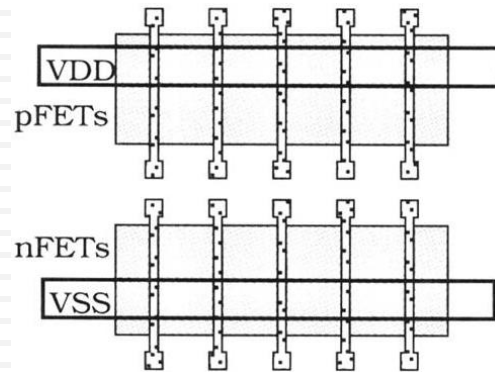





# Gate Array




(a) Gate array based

 


(a) Structure

 

(b) Metal-active

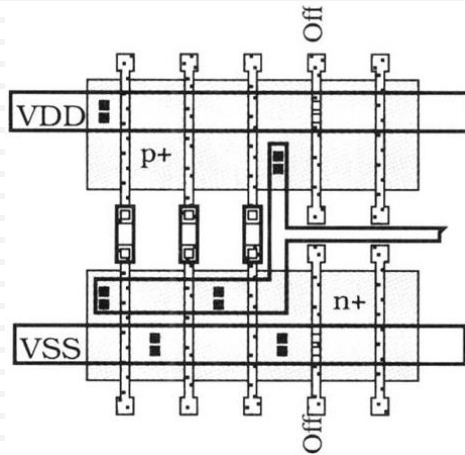

(b) NOR3 gate wiring

 

(c) Metal-metal

Figure 13.45 NOR-gate PLA logic