

# Circuit Modeling with Hardware Description Languages

Prof. Hubert Kaeslin  
Microelectronics Design Center  
ETH Zürich

Morgan Kaufmann “Top-Down Digital VLSI Design” Chapter 4


last update: July 18, 2014

# Content
 
## You will learn

to write high-quality HDL models for circuit synthesis and simulation.

- ▶ Why hardware synthesis?
- ▶ Key concepts behind hardware description languages
  - ▶ What sets HDLs apart from a programming language
  - ▶ Essential VHDL and/or SystemVerilog language constructs
- ▶ Putting HDLs to service for hardware synthesis
  - ▶ Synthesis subset
  - ▶ Patterns for registers and finite state machines
  - ▶ Timing constraints
  - ▶ How to establish a register transfer level model
- ▶ VHDL versus SystemVerilog



*Simulation and testbench coding are postponed to chapter 5 "Functional Verification".*

# Subject

## Motivation and background

## Why hardware synthesis?

Current situation for VLSI designers:

- ▶ Buyers ask for more and more functions on a single chip.
- ▶ Technology supports ever higher integration densities (Moore's law).
- ▶ Market pressure vetoes dilation of development times.

## Why hardware synthesis?

Current situation for VLSI designers:

- ▶ Buyers ask for more and more functions on a single chip.
- ▶ Technology supports ever higher integration densities (Moore's law).
- ▶ Market pressure vetoes dilation of development times.

Hardware description languages (HDL) and design automation come to the rescue in four ways:

- ▶ Move design entry to higher levels of **abstraction**.
- ▶ Allow designers to **focus on functionality** as synthesis tools automate the construction of structural and physical views.
- ▶ **Facilitate reuse** by capturing a circuit description in a parametrized, technology- and platform-independent form.
- ▶ Make **functional verification** more efficient by supporting stimuli generation, automatic response checking, assertion-based verification, etc.

## Languages for modeling digital hardware I

VHDL	An HDL that not only supports structural and behavioral circuit models but testbench models too. A subset is synthesizable. Syntactically similar to Ada.
Verilog	Conceptually similar to VHDL, no type checking and more limited capabilities for design abstraction. A subset is synthesizable. Syntactically similar to C. Superseded by ...
System-Verilog	A superset of Verilog that includes many advanced features from VHDL and from specialized verification languages (OpenVera, PLS). A subset is synthesizable. Supports object-oriented programming.
SystemC	Extends C++ with class libraries and a simulation kernel. Adds <b>clocking</b> information to C++ functions. Intended for software/hardware co-design and co-simulation. Does not support any <b>timing</b> finer than one clock cycle. Synthesis path is via translation to RTL VHDL or Verilog.

## Languages for modeling digital hardware II

Criterion	VHDL	Verilog	SystemVerilog
Synthesis support	yes	yes	growing
Parametrization & abstract modeling	good	poor	good
Type checking & scoping rules	strong	none	loose
Deterministic event queue mechanism	yes	not really	not really
Modeling of electric phenomena	9-valued	4-valued	4-valued
High-level verification support	limited	poor	excellent

## Languages for modeling digital hardware II


Criterion	VHDL	Verilog	SystemVerilog
Synthesis support	yes	yes	growing
Parametrization & abstract modeling	good	poor	good
Type checking & scoping rules	strong	none	loose
Deterministic event queue mechanism	yes	not really	not really
Modeling of electric phenomena	9-valued	4-valued	4-valued
High-level verification support	limited	poor	excellent

*For me, I find VHDL is like swimming with a lifeguard on duty, whereas Verilog is like swimming with a lifebuoy hanging by the poolside. (Blogger on EETimes 2011)*

- ▶ Many companies currently use **VHDL** for synthesis and **SystemVerilog** for system-level verification.
- ▶ Will **SystemVerilog** one day supersede Verilog and **VHDL**, and reconcile their user communities?



# HDLs shown in the Y-chart

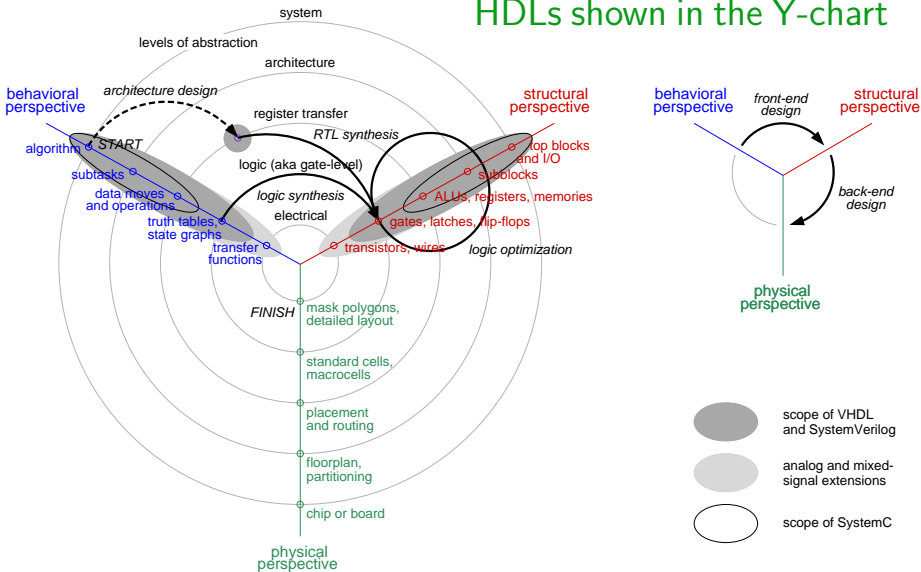

## The genesis of VHDL

- 1983 US DoD commissions IBM, Intermetrics and Texas Instruments to define a HDL for documentation purposes. Ada is taken as a starting point. There are **no plans for automatic synthesis**.
- 1986 Military restrictions lifted, rights transferred to IEEE.
- 1987 Language accepted as IEEE 1076 standard. Event-based **simulation tools begin to appear**.
- 1993 Language standard significantly revised to become IEEE 1076-93. Nine-valued logic system accepted as IEEE 1164 standard. Though confined to a language subset, **synthesis begins to catch on**.
- 1999 A major extension towards modeling of analog and mixed-signal circuits is accepted as separate a standard IEEE 1076.1.
- 2002 Standard slightly revised to become IEEE 1076-2002.
- 2008 IEEE 1076-2008 brings enhanced generics, source code encryption, embedding of IEEE 1850 Property Specification Language, and more.

## The genesis of SystemVerilog

1984 Gateway Design Autom. develops Verilog for a proprietary logic simulator.

1989 Gateway acquired by Cadence.

1990 Verilog made an **open standard**.

1995 Verilog accepted as IEEE 1364 standard. (questionable politics involved)

2001 IEEE 1364-2001 brings major extensions for circuit modeling.

2005 IEEE 1364-2005 is a minor revision.

**SystemVerilog**, created by the Accellera consortium, is accepted as a separate standard named **IEEE 1800**. (more politics involved)

Quiz: "What do Sausage and EDA Standards have in common?"

## The genesis of SystemVerilog

1984 Gateway Design Autom. develops Verilog for a proprietary logic simulator.

1989 Gateway acquired by Cadence.

1990 Verilog made an **open standard**.

1995 Verilog accepted as IEEE 1364 standard. (questionable politics involved)

2001 IEEE 1364-2001 brings major extensions for circuit modeling.

2005 IEEE 1364-2005 is a minor revision.

**SystemVerilog**, created by the Accellera consortium, is accepted as a separate standard named **IEEE 1800**. (more politics involved)

Quiz: "What do Sausage and EDA Standards have in common?"

Answer: "Those who like sausage or EDA standards should never watch either one be made!" (Stuart Sutherland).

2009 IEEE 1800-2009 standard brings improvements mostly for verification, Verilog gets absorbed into the SystemVerilog standard.

2013 IEEE 1800-2012 version released.

## Why bother learning hardware description languages? I

Idea: View HDLs as nothing more than intermediate formats for exchanging data between system design tools and VLSI CAE/CAD suites. Have electronic system-level tools generate code from specs automatically.

# Why bother learning hardware description languages? I

Idea: View HDLs as nothing more than intermediate formats for exchanging data between system design tools and VLSI CAE/CAD suites. Have electronic system-level tools generate code from specs automatically.

- △ Software for system design has a focus, there is no universal tool.
  - Transformational systems as found in signal processing and telecommunications.
  - Reactive system as found in controllers and interface protocols.
  - Specific applications such as data networks, image processing, instruction set computers, etc.
  - HDL generators typically restricted to few predefined architectural patterns.
  
- △ HDL code generated by most ESL tools is nothing else than a translation of software code and inadequate for circuit synthesis.
  
- △ HDLs are indispensable for modeling library cells and virtual components.

## Why bother learning hardware description languages? II

△ HDLs are being used all along digital VLSI design flows.

Design stage & model	Main purpose	Level of abstraction	Timing	Predominant languages
1. Algorithmic model	system-level simulation	behavioral	none	C, MATLAB
			tentative	VHDL, SysVer
2. RTL model	simulation	register transfer	optional fake delays	VHDL, SysVer
	synthesis		constraints in Tcl	
3. Post-synthesis netlist	simulation, timing analysis, place & route	gate level	estimated with wire load models	Verilog, (VHDL&VITAL)
4. Post-layout netlist	simulation, timing analysis, sign-off	gate level	extracted from layout and back-annotated	Verilog, (VHDL&VITAL)

## Why bother learning hardware description languages? II

△ HDLs are being used all along digital VLSI design flows.

Design stage & model	Main purpose	Level of abstraction	Timing	Predominant languages
1. Algorithmic model	system-level simulation	behavioral	none	C, MATLAB
			tentative	VHDL, SysVer
2. RTL model	simulation	register transfer	optional fake delays	VHDL, SysVer
	synthesis		constraints in Tcl	
3. Post-synthesis netlist	simulation, timing analysis, place & route	gate level	estimated with wire load models	Verilog, (VHDL&VITAL)
4. Post-layout netlist	simulation, timing analysis, sign-off	gate level	extracted from layout and back-annotated	Verilog, (VHDL&VITAL)

### Conclusion

For the foreseeable future, VHDL and SystemVerilog are bound to remain prominent hubs for all VLSI design activities.



# Requirements for HDLs

*Show around a motherboard or some other mounted PCB.*

*What features must a formal language have to capture the essence of electronic circuitry?*

# A first look at VHDL and SystemVerilog

In a nutshell, HDLs can be characterized as follows:

- HDL = Structured programming language
- + circuit hierarchy and connectivity
  - + interacting concurrent processes
  - + a discrete replacement for electrical signals
  - + an event-driven scheme of execution
  - + model parametrization facilities
  - + verification aids

VHDL      SysVer

- |   |   |
|---|---|
| ✓ | ✓ |
| ✓ | ✓ |
| ✓ | ✓ |
| ✓ | ✓ |
| ✓ | ✓ |

*Chapter 5*

# A first look at VHDL and SystemVerilog

In a nutshell, HDLs can be characterized as follows:

- HDL = Structured programming language
- + circuit hierarchy and connectivity
  - + interacting concurrent processes
  - + a discrete replacement for electrical signals
  - + an event-driven scheme of execution
  - + model parametrization facilities
  - + verification aids

VHDL      SysVer



*Chapter 5*

Limitation:

- No way to express timing constraints

## Two words of caution ...

Linguistic ambiguity in the context of hardware modeling:

Meaning of “sequential” with reference to	Synonym	Antonyms
○ program execution during simulation	step-by-step	concurrent, parallel
○ nature of circuit being modeled	memorizing	combinational, memoryless

## ... before we go into the details

Teaching follows two threads:

**Lab hours** Become acquainted with software tools and acquire coding skills.

**Lectures** Understand the underlying concepts and mechanisms.

- ▶ modeling of electrical phenomena
- ▶ simulation cycle
- ▶ testbench design
- ▶ synthesis procedure
- ▶ handling of macrocells (RAM)
- ▶ delay modeling, timing checks, timing constraints
- ▶ code portability
- ▶ ...

## ... before we go into the details

Teaching follows two threads:

**Lab hours** Become acquainted with software tools and acquire coding skills.

**Lectures** Understand the underlying concepts and mechanisms.

- ▶ modeling of electrical phenomena
- ▶ simulation cycle
- ▶ testbench design
- ▶ synthesis procedure
- ▶ handling of macrocells (RAM)
- ▶ delay modeling, timing checks, timing constraints
- ▶ code portability
- ▶ ...

**Both are needed!** Circuit design is neither pure theory nor ignorant hacking.

A fool with a tool is still a fool.

## Subject

# Key concepts and constructs of VHDL

*For a SystemVerilog course, skip the next 95 or so slides.*

# Hardware description language requirements

## HDL requirement no.1

Means for expressing how circuits are being composed from subcircuits and how those subcircuits connect to each other.



## 1st HDL capability: Circuit hierarchy and connectivity


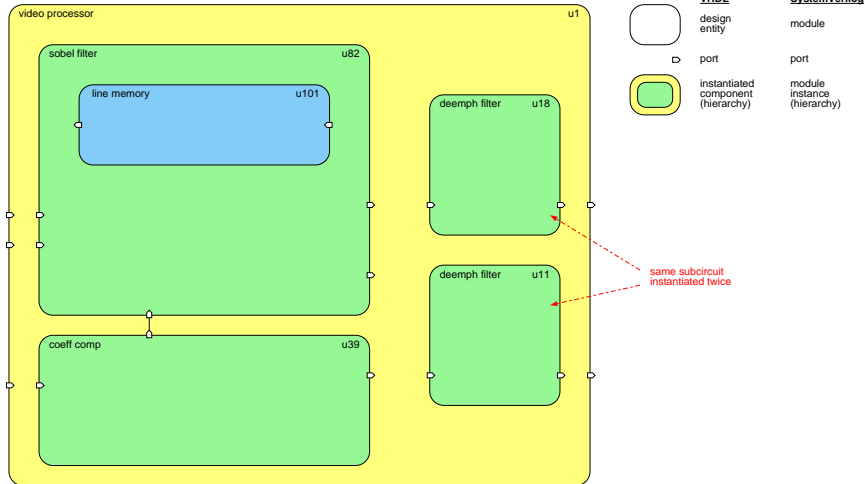


Figure: Hierarchical composition ...
 
## Entity declaration

Specifies the external interface of a design entity (small or large).

```
-- entity declaration
entity lfsr4 is
  port (
    Clk_CI : in std_logic;
    Rst_RBI : in std_logic; -- reset is active low
    Ena_SI : in std_logic;
    Oup_DO : out std_logic );
end lfsr4;
```



- ▶ A port list declares all signals of an entity that are accessible from outside (i.e. the terminals of a circuit as opposed to its inner nodes).

## Architecture body I: a structural circuit model

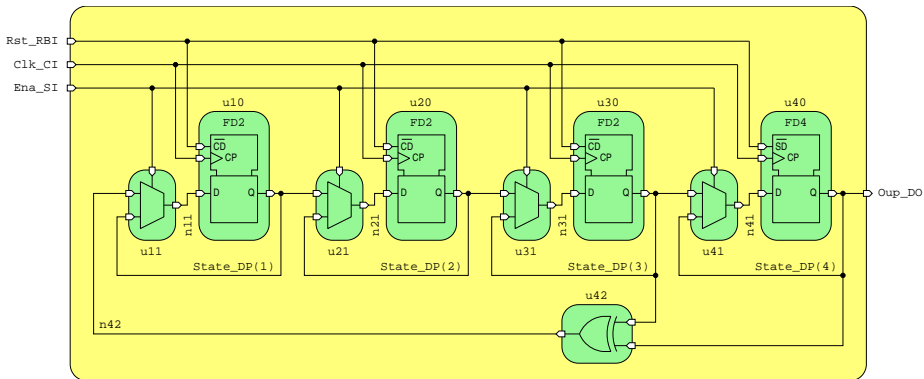


Figure: Linear-feedback shift register circuit to be described.

## Architecture body I: a structural circuit model

*Refer to transparency lfsr4struc.vhd for code!*

Describes a circuit or netlist assembled from components and wires.

1. Declare all components to be used.
2. Declare all signals that run back and forth unless they are already known from the port clause.
3. Instantiate components specifying all terminal-to-signal connections.

## How to compose a circuit from components

How do you proceed when asked to fit a circuit board with components?

1. Think of a part's exact name, e.g. GTECH\_FD2
2. Fetch a copy and assign it some unique identifier it, e.g. u10
3. Solder its terminals to existing metal pads on the board

The component instantiation statement does exactly that. Example:

```
u10 : GTECH_FD2
  port map( D  => n11,
            CP => Clk_CI,
            CD => Rst_RBI,
            Q  => State_DP(1) );
```

### Note

The association operator => does not indicate an assignment but an association of two signals that stands for an electrical connection.

## The essence of structural circuit modeling

- ▶ VHDL can describe the hierarchical composition of a circuit by
  - ▶ instantiating components or entities and by
  - ▶ interconnecting them with the aid of signals.
- ▶ Structural HDL models hold the same information as circuit netlists do.
- ▶ Manually writing structural HDL models is not particularly attractive.
- ▶ Most structural models are in fact obtained from RTL models by automatic synthesis.

## The essence of structural circuit modeling

- ▶ VHDL can describe the hierarchical composition of a circuit by
  - ▶ instantiating components or entities and by
  - ▶ interconnecting them with the aid of signals.
- ▶ Structural HDL models hold the same information as circuit netlists do.
- ▶ Manually writing structural HDL models is not particularly attractive.
- ▶ Most structural models are in fact obtained from RTL models by automatic synthesis.

### HDL requirement no.2

Means for expressing circuit behavior including the combined effects of multiple subcircuits that operate jointly and concurrently.

## 2nd HDL capability: Interacting concurrent processes

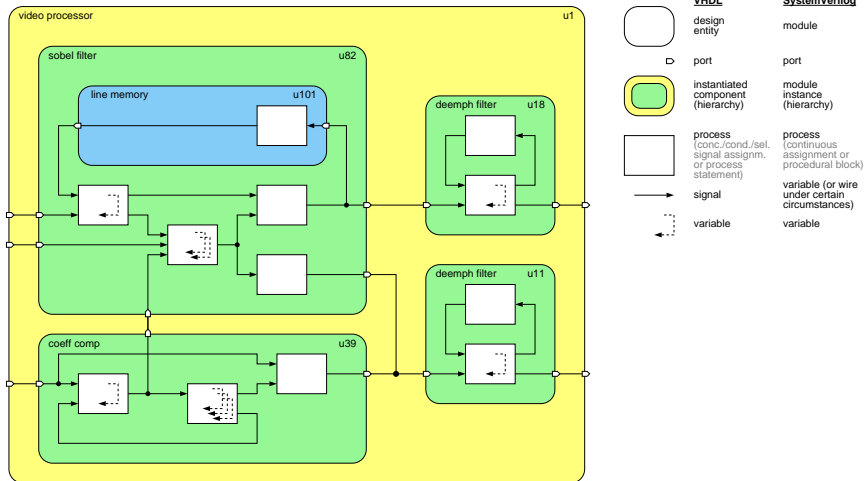


Figure: ... plus behavior modeled with the aid of concurrent processes ...



## Constants, variables, and signals

What everyone knows from software languages:

- ▶ Constant declaration

Example `constant FERMAT_PRIME_4 : integer := 65537;`

- ▶ Variable declaration

Examples `variable Brd : real := 2.48678E5;`  
`variable Ddr : real := 1.08179E5;`

- ▶ Variable assignment

Example `Brd := Brd + Ddr;`

## Constants, variables, and signals

What everyone knows from software languages:

- ▶ Constant declaration

Example `constant FERMAT_PRIME_4 : integer := 65537;`

- ▶ Variable declaration

Examples `variable Brd : real := 2.48678E5;`  
`variable Ddr : real := 1.08179E5;`

- ▶ Variable assignment

Example `Brd := Brd + Ddr;`

... plus a special vehicle for exchanging information between processes:

- ▶ Signal declaration

Example `signal Error_D, Actual_D, Wanted_D : integer := 0;`

- ▶ Signal assignment.

Example `Error_D <= Actual_D - Wanted_D;`

## Practical advice

### Hints

- ▶ VHDL is case-insensitive, e.g. `clk_ci = CLK_CI` (except for extended identifiers written between backslashes, e.g. `\clk_ci\`  $\neq$  `\CLK_CI\`).
- ▶ Naming a signal or a port In or Out is all too tempting, yet these are reserved words in VHDL. We recommend `Inp` and `Outp` instead.
- ▶ Two distinct symbols are being used for variable assignment `:=` and for signal assignment `<=`.
- ▶ Code is easier to read when `signals` can be told from variables by their visual appearance. We append an underscore followed by a suffix of upper-case letters to signals, e.g. `Carry_DB`, `AddrCnt_SN`, `Irq_AMI`.

*Details of our naming convention are to follow in chapter 6 “The Case for Synchronous Design”.*

## How to describe combinational logic behaviorally I

### 1. Concurrent signal assignment:

- ▶ Syntactically simplest form of a process.
- ▶ Drives one signal.

Example:

```
signal Aa_D, Bb_D, Cc_D, Oup_D : std_logic;
```

```
.....
```

```
Oup_D <= Aa_D xor (Bb_D and not Cc_D)
```

- ▶ Typically used to model some combinational behavior (such as an arithmetic or logic operation) when there is no need for branching.

Glimpse ahead: A concurrent/selected/conditional signal assignment gets activated by any change of any signal on the right-hand side.

## How to describe combinational logic behaviorally II

### 2. Selected signal assignment. Example:

```
type month is (JANUARY, FEBRUARY, MARCH, APRIL, MAY, JUNE, JULY,  
              AUGUST, SEPTEMBER, OCTOBER, NOVEMBER, DECEMBER);  
signal ThisMonth_D : month;  
type quarter is (Q1ST, Q2ND, Q3RD, Q4TH);  
signal ThisQuarter_D : quarter;  
.....  
with ThisMonth_D select  
    ThisQuarter_D <= Q1ST when JANUARY | FEBRUARY | MARCH,  
                   Q2ND when APRIL | MAY | JUNE,  
                   Q3RD when JULY | AUGUST | SEPTEMBER,  
                   Q4TH when others;
```

- ▶ This is a form of conditional execution reminiscent of a multiplexer.

Note: The | symbol separates choices, it does not express a logic or operation.

## How to describe combinational logic behaviorally III

### 3. Conditional signal assignment. Example:

```
subtype day is integer range 1 to 31;  
signal ThisDay_D is day;  
signal Spring_D is boolean;  
.....
```

```
Spring_D <= true when (ThisMonth_D=MARCH and ThisDay_D>=21) or  
                    ThisMonth_D=APRIL or ThisMonth_D=MAY or  
                    (ThisMonth_D=JUNE and ThisDay_D<=20)  
                    else false;
```

- ▶ This is a syntactically different form of conditional execution.

Note: There are two <= symbols here. One stands for a signal assignment, the other for a comparison operator.

## How to describe combinational logic behaviorally IV

### 4. Process statement.

Example:

```
memless1: process (all)
begin
    Spring_D <= false;    -- execution begins here
    if ThisMonth_D=MARCH and ThisDay_D>=21 then Spring_D <= true; end if;
    if ThisMonth_D=APRIL then Spring_D <= true; end if;
    if ThisMonth_D=MAY then Spring_D <= true; end if;
    if ThisMonth_D=JUNE and ThisDay_D<=20 then Spring_D <= true; end if;
end process memless1;    -- process suspends here
```

## Process statement versus signal assignments

When compared to a concurrent/selected/conditional signal assignment, a process statement

- ▶ is capable of updating **two or more signals at a time**,
- ▶ captures the instructions for doing so in a **sequence of statements** that may not only include branching but also loops,
- ▶ gives the liberty to make use of **variables for temporary storage**,
- ▶ provides more detailed control over the **conditions for activation**.



## Process statement versus signal assignments

When compared to a concurrent/selected/conditional signal assignment, a process statement

- ▶ is capable of updating **two or more signals at a time**,
- ▶ captures the instructions for doing so in a **sequence of statements** that may not only include branching but also loops,
- ▶ gives the liberty to make use of **variables for temporary storage**,
- ▶ provides more detailed control over the **conditions for activation**.

### Observation

The process statement is best summed up as being concurrent outside and sequential inside.

## How to describe a register behaviorally

- ▶ Code example of an edge-triggered register that features
  1. an asynchronous reset,
  2. a synchronous load, and
  3. an enable.

```
p_memzing : process (Clk_C,Rst_RB)
begin
  -- activities triggered by asynchronous reset
  if Rst_RB='0' then
    State_DP <= (others => '0'); -- shorthand for all bits zero
  -- activities triggered by rising edge of clock
  elsif Clk_C'event and Clk_C='1' then
    -- when synchronous load is asserted
    if Lod_S='1' then
      State_DP <= (others => '1'); -- shorthand for all bits one
    -- else assume new value iff enable is asserted
    elsif Ena_S='1' then
      State_DP <= State_DN; -- admit next state into state register
    end if;
  end if;
end process p_memzing;
```

## Architecture body II: a behavioral circuit model

Describes how concurrent processes interact via signals and how they alter them.




```
-- architecture body
architecture behavioral of lfsr4 is
    signal State_DP, State_DN : std_logic_vector(1 to 4);
    -- for present and next state respectively
begin

    -- computation of next state using concatenation of bits
    State_DN <= (State_DP(3) xor State_DP(4)) & State_DP(1 to 3);

    -- updating of state
    process (Clk_CI, Rst_RBI)
    begin
        -- activities triggered by asynchronous reset
        if Rst_RBI='0' then
            State_DP <= "0001";
        -- activities triggered by rising edge of clock
        elsif Clk_CI'event and Clk_CI='1' then
            if Ena_SI='1' then
                State_DP <= State_DN; -- admit next state into state register
            end if;
        end if;
    end process;

    -- updating of output
    Oup_DO <= State_DP(4);

end behavioral;
```

   

## The essence of behavioral circuit modeling


In VHDL, the behavior of a digital circuit typically gets described by a collection of concurrent processes that

- ▶ execute simultaneously, that
- ▶ communicate via signals, and where
- ▶ each such process represents some subfunction.

### Hint for RTL synthesis

- ▶ Model each register with a process statement.
- ▶ Prefer concurrent, selected, and conditional signal assignments for describing the combinational logic in between.

## Hardware modeling styles

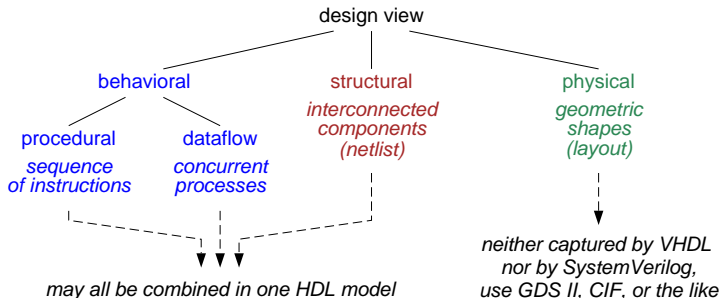

### Observation

VHDL allows for procedural, dataflow, and structural modeling styles to be freely combined in a single model.

# Procedural, dataflow, and structural models compared I


*Refer to transparency fulladd.vhd for code!*

Compare in terms of

1. number of processes
2. number of internal signals
3. number of variables
4. impact of ordering of statements
5. interaction with event queue
6. portability of source code

Note: Adders are normally synthesized from algebraic expressions, a full-adder has been chosen here for its simplicity and obviousness.

## Procedural, dataflow, and structural models compared II

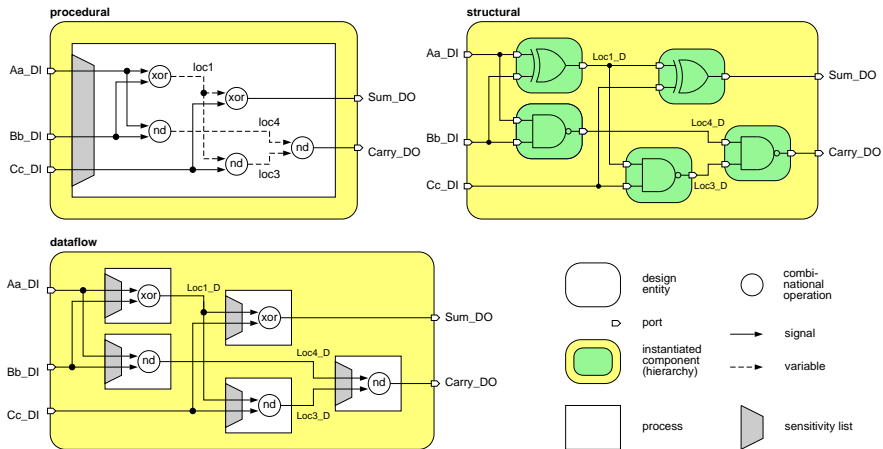

**Figure:** Modeling styles illustrated with a full adder as example.

## Example: The ones counter

*Refer to transparency onescnt.vhd for code!*

### Observe

1. In spite of its name, this is a memoryless subfunction that finds applications in large adder circuits.
2. The output is a 3 bit number that indicates how many of the four input bits are 1 (logic high).
3. The great diversity of modeling styles to express exactly the same functionality.



## Example: The ones counter

*Refer to transparency onescnt.vhd for code!*

### Observe

1. In spite of its name, this is a memoryless subfunction that finds applications in large adder circuits.
2. The output is a 3 bit number that indicates how many of the four input bits are 1 (logic high).
3. The great diversity of modeling styles to express exactly the same functionality.

### Observation

Some code examples are compact and easy to understand, others are more cryptic or tend to grow exponentially.

## 3rd capability: A discrete replacement for electrical signals

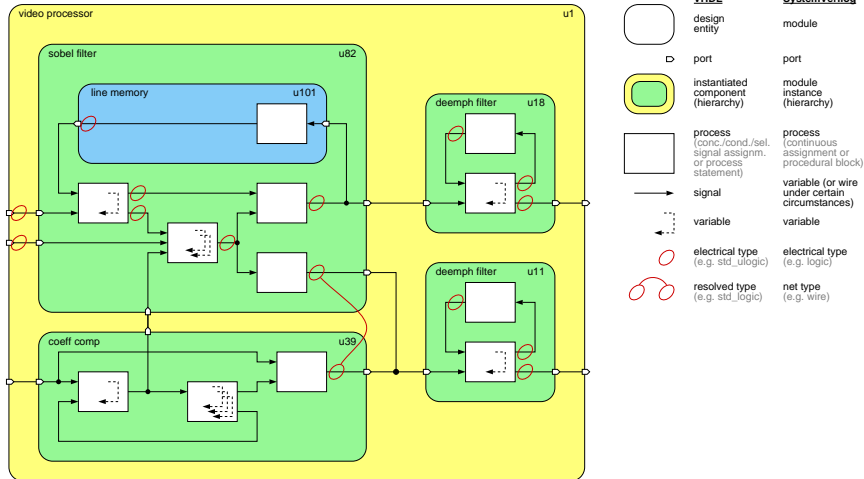


Figure: ... plus data types for modeling electrical phenomena ...

# What you ought to know about bidirectional busses I

 


Figure: Memory read and write transfers in a computer.

## What you ought to know about bidirectional busses II

### Requirements:

- ▶ Each bidirectional line is to be driven from multiple places, so one needs a **multi-driver signal** (as opposed to a single-driver signal).
- ▶ Driving alternates.
- ▶ Buffers must be able to **electrically release** the line hence the name “three-state” output (0, 1, disabled output = high-impedance state).
- ▶ Requires some kind of access control mechanism (centralized or distributed).

## What you ought to know about bidirectional busses II

### Requirements:

- ▶ Each bidirectional line is to be driven from multiple places, so one needs a **multi-driver signal** (as opposed to a single-driver signal).
- ▶ Driving alternates.
- ▶ Buffers must be able to **electrically release** the line hence the name “three-state” output (0, 1, disabled output = high-impedance state).
- ▶ Requires some kind of access control mechanism (centralized or distributed).

### Failure modes:

- ▶ Stationary drive conflict  $\mapsto$  functional failure or damage.
- ▶ Floating voltage  $\mapsto$  electrically undesirable condition.

*Presentation focusses on HDL modeling, remedies to be discussed in chapter 10 "Gate- and Transistor-Level Design".*

## Why do binary types not suffice to model digital circuits?

Digital circuits exhibit characteristics and phenomena such as

- ▶ transients,
- ▶ three-state outputs,
- ▶ drive conflicts, and
- ▶ power-up

that can not be modeled with 0 and 1 alone.

## Why do binary types not suffice to model digital circuits?

Digital circuits exhibit characteristics and phenomena such as

- ▶ transients,
- ▶ three-state outputs,
- ▶ drive conflicts, and
- ▶ power-up

that can not be modeled with 0 and 1 alone.

### HDL requirement no.3

A multi-valued logic system capable of capturing the effects of both node voltage and source impedance.

## The IEEE 1164 logic system I

Voltage is quantized into three logic states

- low                      logic low, that is below  $U_l$ .
- high                     logic high, that is above  $U_h$ .
- unknown                either “low”, “high” or anything in between  
e.g. as a result from a short between two drivers.



# The IEEE 1164 logic system I

**Voltage** is quantized into three logic states

- low                      logic low, that is below  $U_l$ .
- high                     logic high, that is above  $U_h$ .
- unknown                either “low”, “high” or anything in between  
e.g. as a result from a short between two drivers.

Source impedance gets mapped onto three **drive strengths**

- strong                    as exhibited by a driving output
- high-impedance        as exhibited by a disabled three-state output
- weak                     somewhere between “strong” and “high-impedance”  
e.g. as exhibited by a passive pull-up/down resistor.

## The IEEE 1164 logic system II

No charge retention in high-impedance state  $\rightsquigarrow$

- charged low
- charged high
- charged unknown

are all merged into a single value of undetermined state (voltage).

## The IEEE 1164 logic system II

No charge retention in high-impedance state  $\rightsquigarrow$

- charged low
- charged high
- charged unknown

are all merged into a single value of undetermined state (voltage).

Two extra logic values are added, namely:

- uninitialized      **signal has never been assigned any value since power-up**  
(applicable to simulation only).
- don't care      **don't care condition for logic minimization,**  
distinction between "low" or "high" immaterial  
(applicable to synthesis only).

## The IEEE 1164 logic system III

Uses a total of nine logic values to model electrical signals.

logic value → ↓	logic state		
	low	unknown	high
uninitialized		U	
strong	0	X	1
strength  weak	L	W	H
high-impedance	Z	Z	Z
don't care		-	

Defines two data types that share the above set of values:

- `std_ulogic`           type                           *Difference to be*
- `std_logic`            subtype                           *explained soon*

## Illustrations

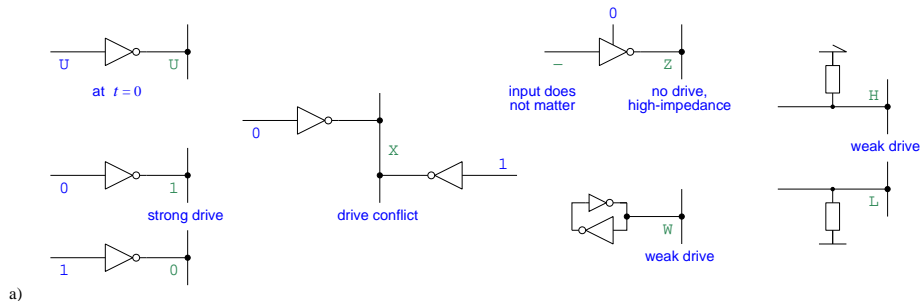


Figure: The IEEE 1164 standard MVL-9 illustrated.

## Collapsing of logic values during synthesis

L and H are not normally honored by synthesis software. Most synthesis tools collapse “meaningless” (to them) values to more sensible ones, e.g.

- ▶  $L \mapsto 0$
- ▶  $H \mapsto 1$
- ▶  $X \text{ or } W \mapsto -$

## Collapsing of logic values during synthesis

L and H are not normally honored by synthesis software. Most synthesis tools collapse “meaningless” (to them) values to more sensible ones, e.g.

- ▶  $L \mapsto 0$
- ▶  $H \mapsto 1$
- ▶  $X$  or  $W \mapsto -$

### Hint for RTL synthesis

For the sake of clarity and portability, do not use logic values other than 0, 1, Z and - in VHDL source code that is intended for synthesis.

## How to model a bidirectional line in VHDL I

Want to model a circuit node that can be driven from multiple subcircuits?  
↪ Use two or more conditional signal assignments.

Example:

```
signal Com_DZ, Aa_D, Bb_D, SelA_S, SelB_S : std_logic;


.....
Com_DZ <= not Aa_D when SelA_S='1' else 'Z';
.....
Com_DZ <= not Bb_D when SelB_S='1' else 'Z';
.....
```

### Note

Node Com\_DZ is left floating when neither of the two drivers is enabled.



 
## How to model a bidirectional line in VHDL II




single-driver signals `Pp_DZ` and `Qq_DZ`  
may assume distinct logic values,  
no difference between `std_ulogic` and `std_logic`

b)

 


if multi-driver signal `Com_DZ` is of type  
`std_ulogic` then an error message gets issued  
`std_logic` then the conflict is resolved to `Com_DZ = 1`
 
## How to model a bidirectional line in VHDL II



single-driver signals `Pp_DZ` and `Qq_DZ`  
may assume distinct logic values,  
no difference between `std_ulogic` and `std_logic`

b)

 

if multi-driver signal `Com_DZ` is of type  
`std_ulogic` then an error message gets issued  
`std_logic` then the conflict is resolved to `Com_DZ = 1`

### Observation

The distinction between types `std_ulogic` and `std_logic` matters only when simulating a multi-driver node:

<code>std_logic</code>	tacitely resolves all conflicts that might occur
<code>std_ulogic</code>	generates a message in case of conflict

## The IEEE 1164 standard resolution function

```
-----  
-- resolution function "resolved"  
-----  
constant resolution_table : stdlogic_table := (  
--  
-- | U   X   0   1   Z   W   L   H   -   | |  
--  
-- ( 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U' ), -- | U |  
-- ( 'U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' ), -- | X |  
-- ( 'U', 'X', '0', 'X', '0', '0', '0', '0', '0', 'X' ), -- | 0 |  
-- ( 'U', 'X', 'X', '1', '1', '1', '1', '1', '1', 'X' ), -- | 1 |  
-- ( 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', 'X' ), -- | Z |  
-- ( 'U', 'X', '0', '1', 'W', 'W', 'W', 'W', 'X' ), -- | W |  
-- ( 'U', 'X', '0', '1', 'L', 'W', 'L', 'W', 'X' ), -- | L |  
-- ( 'U', 'X', '0', '1', 'H', 'W', 'W', 'H', 'X' ), -- | H |  
-- ( 'U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' ) -- | - |  
);
```

- ▶ This is the default resolution function, others can be added.

## Data type `std_logic` versus `std_ulogic`

- ▶ Signals of type `std_logic` can accommodate multiple drivers whereas those of type `std_ulogic` can not.
- ▶ An error message will tell should a `std_ulogic`-type signal accidentally get involved in a naming conflict, so this is the more conservative choice.
- ▶ A signal is allowed to be driven from multiple processes iff a resolution function is defined that determines the outcome.
- ▶ There can be no such thing as a resolution function for variables, neither for `bit`, `bit_vector`, `integer`, `real`, and similar data types.

## Data types for modeling single-bit signals

data type defined in value set per binary digit	bit VHDL 2	std_ulogic ieee.std_logic_1164 9	std_logic
for simulation purposes			
modeling of power-up phase	no	yes	yes
modeling of weakly driven nodes	no	yes	yes
modeling of multi-driver nodes	no	yes	yes
handling of drive conflicts	n.a.	reported	resolved
for synthesis purposes			
three-state drivers	no	yes	yes
don't care conditions	no	yes	yes

## Data types for modeling multi-bit signals

data type(s)	integer, natural, positive	bit_ vector	std_logic _vector	signed, unsigned	signed, unsigned
defined in	VHDL	VHDL	ieee. std_logic _1164	ieee. numeric _bit	ieee. numeric _std
value set per binary digit word width	2 32 bit	2	9	2	9
		at the programmer's discretion			
arithmetic operations	yes	no	no	yes	yes
logic operations	no	yes	yes	yes	yes
access to subwords or bits	no	yes	yes	yes	yes
modeling of electrical effects	no	no	yes	no	yes

## Data types for modeling multi-bit signals

data type(s)	integer, natural, positive	bit_ vector	std_logic _vector	signed, unsigned	signed, unsigned
defined in	VHDL	VHDL	ieee. std_logic _1164	ieee. numeric _bit	ieee. numeric _std
value set per binary digit word width	2 32 bit	2	9	2	9
		at the programmer's discretion			
arithmetic operations	yes	no	no	yes	yes
logic operations	no	yes	yes	yes	yes
access to subwords or bits	no	yes	yes	yes	yes
modeling of electrical effects	no	no	yes	no	yes

- ▶ VHDL is **strongly typed** = extensive type checking is performed  
 ↪ must convert before assignment or comparison across types.

## Converting between data types

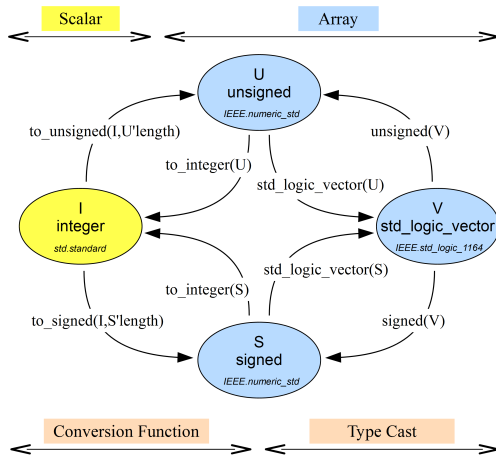


Figure: VHDL type conversion paths (chart courtesy of Dr. Jürgen Wassner).



## Orientation of binary vectors

### Hint

Any vector that contains a data item coded in some positional number system should consistently be declared as  $(i_{MSB} \text{ downto } i_{LSB})$  where  $2^i$  is the weight of the binary digit with index  $i$ .

The MSB so has the highest index assigned to it and appears in the customary leftmost position because  $i_{MSB} \geq i_{LSB}$ .

Example `signal Hour_D : unsigned(4 downto 0) := "10111";`

## Orientation of binary vectors

### Hint

Any vector that contains a data item coded in some positional number system should consistently be declared as  $(i_{MSB} \text{ downto } i_{LSB})$  where  $2^i$  is the weight of the binary digit with index  $i$ .

The MSB so has the highest index assigned to it and appears in the customary leftmost position because  $i_{MSB} \geq i_{LSB}$ .

Example `signal Hour_D : unsigned(4 downto 0) := "10111";`

Types unsigned and signed are for integer numbers:

unsigned ii...i.

signed si...i. in 2's complement format

## Orientation of binary vectors

### Hint

Any vector that contains a data item coded in some positional number system should consistently be declared as  $(i_{MSB} \text{ downto } i_{LSB})$  where  $2^i$  is the weight of the binary digit with index  $i$ .

The MSB so has the highest index assigned to it and appears in the customary leftmost position because  $i_{MSB} \geq i_{LSB}$ .

Example `signal Hour_D : unsigned(4 downto 0) := "10111";`

Types unsigned and signed are for integer numbers:

unsigned `ii...i.`

signed `si...i.` in 2's complement format

What about fractional parts `.ff...f` ?

## Data types for fractional and floating point numbers

Introduced with the IEEE 1076-2008 revision.

type prefix	unresolved_			unresolved resolved
data type	ufixed	sfixed	float	
defined in	fixed_ generic_ pkg		float_ generic_ pkg	
arithmetics	fixed point unsigned   signed		floating point	
word width	at the programmer's discretion			
arithmetic operations	yes			
logic operations	yes			
access to subwords or bits	yes			
modeling of electrical effects	yes (resolved)			

## Data types for fractional numbers

Both signed and unsigned formats exist; 2'C format used for signed numbers.

Unsigned example

```
signal HourWithQuarter_D : ufixed(4 downto -2) := "1011111";
```

`iiii. ff` (  $\mapsto$  range 0 to  $11111.11_2 = 31.75_{10}$   
in steps of  $\frac{1}{4}$ , initial value =  $10111.11_2 = 23.75_{10}$ )

## Data types for fractional numbers

Both signed and unsigned formats exist; 2'C format used for signed numbers.

Unsigned example

```
signal HourWithQuarter_D : ufixed(4 downto -2) := "1011111";
```

`iiii. ff` (  $\mapsto$  range 0 to  $11111.11_2 = 31.75_{10}$   
in steps of  $\frac{1}{4}$ , initial value =  $10111.11_2 = 23.75_{10}$ )

Signed example

```
signal HourWithQuarter_D : sfixed(4 downto -2) := "1011111";
```

`siiii. ff` (  $\mapsto$  range  $10000.00_2 = -16.00_{10}$  to  $01111.11_2 = 15.75_{10}$   
in steps of  $\frac{1}{4}$ , initial value =  $10111.11_2 = -9.75_{10}$ )

## Data types for fractional numbers

Both signed and unsigned formats exist; 2'C format used for signed numbers.

Unsigned example

```
signal HourWithQuarter_D : ufixed(4 downto -2) := "1011111";  
iiii. ff (  $\mapsto$  range 0 to 11111.112 = 31.7510  
in steps of  $\frac{1}{4}$ , initial value = 10111.112 = 23.7510)
```

Signed example

```
signal HourWithQuarter_D : sfixed(4 downto -2) := "1011111";  
siiii. ff (  $\mapsto$  range 10000.002 = -16.0010 to 01111.112 = 15.7510  
in steps of  $\frac{1}{4}$ , initial value = 10111.112 = -9.7510)
```

- ▶ For maximum versatility, some arithmetic aspects are kept user-adjustable via generics:
  - ▶ Rounding behavior. (round  $\approx$  vs. truncate  $\downarrow$ ).
  - ▶ Overflow behavior (saturate  $\text{---}\diagup$  vs. wrap around  $\text{---}\diagup\diagdown$ ).
  - ▶ Number of guard bits for division operation  
(extra digit positions used to reduce the roundoff error)

## Data types for floating point numbers

Floating point numbers include a sign bit and an exponent by definition.

- ▶ Formats adhere to the principles of the IEEE 754 standard, except # of bits for exponent and mantissa are defined in type declaration.
- ▶ Mantissa is coded as a fractional number in 2'C format.
- ▶ Exponent is coded in O-B (offset-binary) format.



## Data types for floating point numbers

Floating point numbers include a sign bit and an exponent by definition.

- ▶ Formats adhere to the principles of the IEEE 754 standard, except **# of bits for exponent and mantissa are defined in type declaration.**
- ▶ Mantissa is coded as a fractional number in 2'C format.
- ▶ Exponent is coded in O-B (offset-binary) format.

Example `signal ToyFloat_D : float(5 downto -8);`

The number format so specified is `seeeee.fffffff` where

- ▶  $\#e = 5$  and  $\#f = 8$
- ▶ `s` stands for the sign bit (of the mantissa)
- ▶ each `e` stands for one bit of the exponent (with an offset  $2^{\#e-1} - 1 = 15$ )
- ▶ each `f` stands for one bit of the mantissa (normalized to the interval  $[1...2)$  and with binary weights from  $\frac{1}{2}$  all the way down to  $\frac{1}{256}$ )

Online translators available on the Internet!

## 4th HDL capability: An event-based model of time

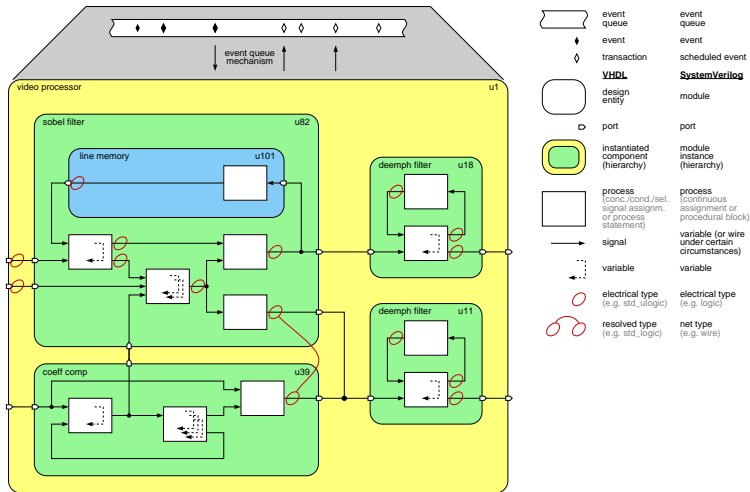


Figure: ... plus an event queue mechanism that governs process activation ...

## How does VHDL simulation work? I

Please recall:

A signal's value can be altered by any of ...

- ▶ Concurrent **signal assignment** (simplest)
- ▶ Selected **signal assignment**
- ▶ Conditional **signal assignment**
- ▶ **process statement** (most powerful).

### Make sure to understand

- ▶ All the above constructs are **concurrent processes** aka threads of execution (in the sense of the German “nebenläufiger Prozess”).
- ▶ “**process statement**”, in contrast, refers to a specific VHDL language construct (identified by the presence of the reserved word **process**).

## How does VHDL simulation work? II

- ▶ A typical circuit model comprises many many processes.
- ▶ No more than a few processor cores are normally available for running the simulation code.
- ▶ Yet, simulation is to yield the same result as if all processes were operating simultaneously.

## How does VHDL simulation work? II

- ▶ A typical circuit model comprises many many processes.
- ▶ No more than a few processor cores are normally available for running the simulation code.
- ▶ Yet, simulation is to yield the same result as if all processes were operating simultaneously.

### HDL requirement no.4

A mechanism that schedules processes for sequential execution and that combines their effects such as to perfectly mimic concurrency.

## Notions of time

- Simulation time** is to an HDL what physical time is to the hardware being modeled. The simulator can be thought to maintain some kind of stop watch that registers the progress of simulation time.
- Execution time** (aka wall clock) refers to the time a computer takes to execute statements from the program code during simulation.

## Notions of time

**Simulation time** is to an HDL what physical time is to the hardware being modeled. The simulator can be thought to maintain some kind of stop watch that registers the progress of simulation time.

**Execution time** (aka wall clock) refers to the time a computer takes to execute statements from the program code during simulation.

- ▶ In VHDL simulation, **the continuum of time gets subdivided by events** each of which occurs at a precise moment of simulation time.
- ▶ An event is said to happen whenever the value of a `signal` changes.

# Event-driven simulation I


Event-driven simulation works in cycles where three stages alternate:

1. Advance simulation time to the next transaction thereby making it the current one.
2. Set all signals that are to be updated at the present moment of time to the target value associated with the current transaction.
3. Invoke all processes that need to respond to the new situation. Every signal assignment there supposed to modify a signal's value causes a transaction to be entered into the event queue at that point in the future when the signal is anticipated to take on its new value.

Go to 1. and start a new simulation cycle.



## The event-queue mechanism

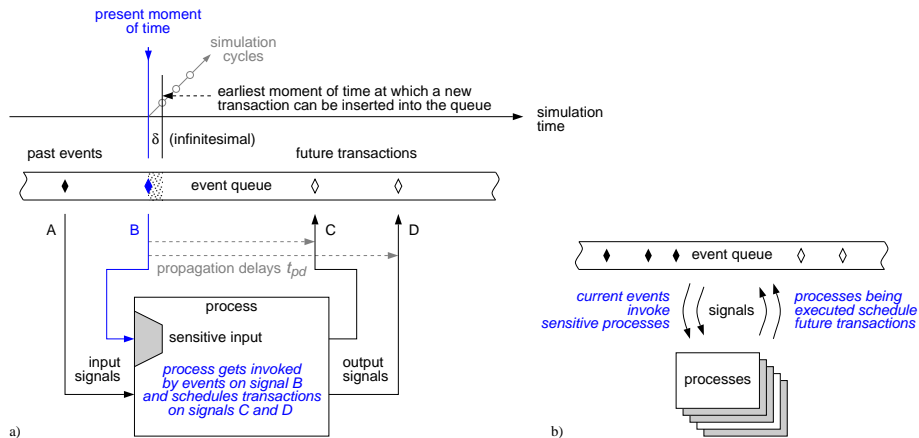

**Figure:** Interactions between the event queue and processes in VHDL.

## Event-driven simulation II

- ▶ Simulation stops when the event queue becomes empty or when simulation time reaches some predefined final value.
- ▶ As nothing happens between transactions, an event-driven simulator essentially skips from one transaction to the next.  
    ↪ No computational resources are wasted while models sit idle.

## Event-driven simulation II

- ▶ Simulation stops when the event queue becomes empty or when simulation time reaches some predefined final value.
- ▶ As nothing happens between transactions, an event-driven simulator essentially skips from one transaction to the next.  
    ↪ No computational resources are wasted while models sit idle.

### Note the analogy between event queue and agenda

- ▶ Events are observable from the past evolution of a `signal`'s value.
- ▶ Transactions reflect future plans that may or may not materialize.

## Delay modeling for simulation I

Delays are captured in an optional `after` clause in a signal assignment.

Example

```
Oup_D <= InpA_D + InpB_D after TPD;
```

Contamination delay can be modeled using two `after` clauses.

Example

```
Oup_D <= 'X' after TCD, InpA_D + InpB_D after TPD;
```

- ▶ Ramps can not be modeled.

## Delay modeling for simulation II

In the absence of an `after` clause, delay is assumed to be zero and the transaction is scheduled for the next simulation cycle ( $\delta$  delay).

Example

```
Oup_D <= InpA_D + InpB_D;
```

Example

```
Oup_D <= InpA_D + InpB_D after 0 ns;
```

### Observation

The  $\delta$  delay serves to maintain a consistent order of transactions in models that include zero delays.

## Delay modeling for simulation II

In the absence of an `after` clause, delay is assumed to be zero and the transaction is scheduled for the next simulation cycle ( $\delta$  delay).

Example

```
Oup_D <= InpA_D + InpB_D;
```

Example

```
Oup_D <= InpA_D + InpB_D after 0 ns;
```

### Observation

The  $\delta$  delay serves to maintain a consistent order of transactions in models that include zero delays.

When simulating models with no delays (other than  $\delta$ ), it becomes difficult to distinguish between cause and effect from waveform output as the respective events appear to coincide.

### Hint

Fake delays help to visually tell apart cause and effect.

Example

```
Oup_D <= InpA_D + InpB_D after FAKEDELAY;
```

## Signal versus variable I

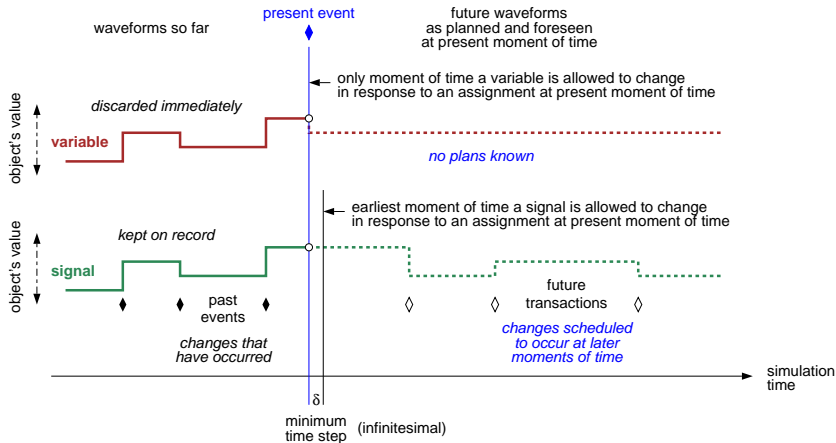


Figure: The past, present and future of VHDL variables and signals.

## Signal versus variable II

### VHDL property

- ▶ VHDL signals convey time-varying information between processes via the event queue. They are instrumental in process invocation which is directed by the same mechanism.
- ▶ As opposed to this, variables are confined to within a process statement or a subprogram and do not interact with the event queue in any way.



## Watch out, frequent misconception!

Effects of variable and signal assignments.

**Variable assignment ( $:=$ )** Effect felt immediately, that is, in the next statement exactly as in any programming language.

## Watch out, frequent misconception!

Effects of variable and signal assignments.

**Variable assignment** (`:=`) Effect felt immediately, that is, in the next statement exactly as in any programming language.

**Signal assignment** (`<=`) Does not become effective before the delay specified in the `after` clause has expired.

In the absence of an explicit indication, there is a delay of one simulation cycle, so **the effect can never be felt in the next statement.**

## Event-driven simulation III

A process is either active or suspended at any time. Simulation time is stopped while the code of the processes presently active is being carried out.

This implies:

- ▶ All active processes are executed concurrently with respect to simulation time.
- ▶ All sequential statements inside a process statement are executed in zero simulation time.

### Note

The order of process invocation with respect to execution time is undetermined.

## Insight gained

In software languages:

- ▶ Execution strictly follows the order of statements in the source code.

During VHDL simulation:

- ▶ No fixed ordering for carrying out processes  
(including concurrent signal assignments and assertion statements).

### Important observation

When to invoke a process gets determined solely by events on the signals that run back and forth between processes.

## Further details on process activation

### VHDL property

Concurrent, selected or conditional signal assignments have no sensitivity list. Any signal on the right-hand side of the assignment activates the process.

```
Spring_D <= true when (ThisMonth_D=MARCH and ThisDay_D>=21) or  
                    ThisMonth_D=APRIL or ThisMonth_D=may or  
                    (ThisMonth_D=JUNE and ThisDay_D<=20)  
                    else false;
```

- ▶ ThisMonth\_D and ThisDay\_D act as **wake-up signals** here.

*On to the tricky process statement ...*

## Process statement with sensitivity list

### VHDL property

The process statement provides a special clause, termed sensitivity list, where all wake-up signals must be declared.

```
memless2: process (ThisMonth_D, ThisDay_D) <-- sensitivity list
begin
    Spring_D <= false;    -- execution begins here
    if ThisMonth_D=MARCH and ThisDay_D>=21 then Spring_D <= true; end if;
    if ThisMonth_D=APRIL then Spring_D <= true; end if;
    if ThisMonth_D=may then Spring_D <= true; end if;
    if ThisMonth_D=JUNE and ThisDay_D<=20 then Spring_D <= true; end if;
end process memless2;    -- process suspends here
```

- ▶ Upon activation by a wake-up signal, instructions are executed one after the other until the end process statement is reached.
- ▶ The process then reverts to its suspended state.

## A process statement may or may not exhibit memory

What happens if signal `ThisDay_D` is omitted from the sensitivity list?

```
memwhat: process (ThisMonth_D) <-- this sensitivity list is incomplete
begin
    Spring_D <= false;    -- execution begins here
    if ThisMonth_D=MARCH and ThisDay_D>=21 then Spring_D <= true; end if;
    if ThisMonth_D=APRIL then Spring_D <= true; end if;
    if ThisMonth_D=MAY then Spring_D <= true; end if;
    if ThisMonth_D=JUNE and ThisDay_D<=20 then Spring_D <= true; end if;
end process memwhat;    -- process suspends here
```

## A process statement may or may not exhibit memory

What happens if signal `ThisDay_D` is omitted from the sensitivity list?

```
memwhat: process (ThisMonth_D) -- this sensitivity list is incomplete
begin
    Spring_D <= false;    -- execution begins here
    if ThisMonth_D=MARCH and ThisDay_D>=21 then Spring_D <= true; end if;
    if ThisMonth_D=APRIL           then Spring_D <= true; end if;
    if ThisMonth_D=MAY             then Spring_D <= true; end if;
    if ThisMonth_D=JUNE  and ThisDay_D<=20 then Spring_D <= true; end if;
end process memwhat;    -- process suspends here
```

- ▶ Events on `ThisDay_D` are unable to activate the process and, hence, no longer update signal `Spring_D`. Its current state then depends on **past** values of `ThisDay_D`.

The above code implies sequential circuit behavior!



## A process statement may include wait statements

provided it features no sensitivity list.

- ▶ Process execution suspends when a wait statement is reached.
- ▶ The wait statement comes in **four flavors** that differ in the nature of the condition for process reactivation.

statement	wake-up condition
wait on ...	an event (value change) on any of the signals listed
wait until ...	<i>idem</i> plus the logic conditions specified here
wait for ...	a predetermined lapse of time as specified here
wait	none, sleep forever as no wake-up condition is given

## Process statement with a wait

as an alternative syntax for memless2:

```
memless3: process    <-- no sensitivity list here
begin
    Spring_D <= false;    -- execution begins here
    if ThisMonth_D=MARCH and ThisDay_D>=21 then Spring_D <= true end if;
    if ThisMonth_D=APRIL          then Spring_D <= true end if;
    if ThisMonth_D=MAY            then Spring_D <= true end if;
    if ThisMonth_D=JUNE  and ThisDay_D<=20 then Spring_D <= true end if;
    wait on ThisMonth_D, ThisDay_D;    -- process suspends here until reactivated
                                        -- by an event on any of these signals
end process memless3;    -- execution continues with first statement
```

- ▶ Functionally interchangeable with process memless2 shown before.
- ▶ Process execution does not terminate with the end process statement but resumes at the top of the process body.
- ▶ wait placed at the end because all processes get activated once until they suspend during initialization at simulation time zero.

## Not all process statements are amenable to synthesis

► Accepted coding styles for synthesis:

process statement with sensitivity list	universally supported
with 1 wait	<i>idem</i>
with $\geq 2$ waits	not normally supported

## Not all process statements are amenable to synthesis

► Accepted coding styles for synthesis:

process statement with sensitivity list	universally supported
with 1 wait	<i>idem</i>
with $\geq 2$ waits	not normally supported

Reason:

Each `wait` statement is allowed to carry its own condition as to when process execution is to resume. Depending on the details, this may imply synchronous or asynchronous behavior.

*More detailed reasons follow in the synthesis section.*

## What makes a VHDL process statement exhibit sequential behavior?

A process statement implies memory iff one or more of the conditions below apply.

- ▶ The process includes **multiple wait on or wait until statements**.
- ▶ The process evaluates **input signals that have no wake-up capability**.
- ▶ The process includes **variables that get assigned no value before being used**.
- ▶ The process **fails to assign a value to its output signals for every possible combination of values of its inputs**.

⇒ Circuit synthesized will or will not include flip-flops and/or latches.

## Beware of frequent oversights!

If a process statement is to model combinational logic

- ▶ Assign to each output for all possible combinations of input values.  
If a signal's value does not matter, assign a don't care.  
**Not assigning anything implies memory!**
- ▶ Enumerate all inputs in the sensitivity list.

A syntax option introduced with the IEEE 1076-2008 revision helps:

```
memless1: process (all) <-- This is shorthand for a complete sensitivity list
begin
  Spring_D <= false;    -- execution begins here
  if ThisMonth_D=MARCH and ThisDay_D>=21 then Spring_D <= true; end if;
  if ThisMonth_D=APRIL      then Spring_D <= true; end if;
  if ThisMonth_D=MAY        then Spring_D <= true; end if;
  if ThisMonth_D=JUNE  and ThisDay_D<=20 then Spring_D <= true; end if;
end process memless1;    -- process suspends here
```

## Insight gained

VHDL knows of no specific language constructs and of no reserved words that could tell

- ▶ a **sequential** model from a **combinational** one,
- ▶ a **synchronous** from an **asynchronous** circuit,
- ▶ one type of finite state machine from a different one (Mealy, Moore and Medvedev).

### VHDL property

What makes the difference is the detailed construction of the source code!

### Hint

Make your intentions explicit in the source code (comments and process labels) to facilitate code understanding and the interpretation of EDA tool reports (presence of latches, number of flip-flops, through paths).

## How to safely code sequential circuits

### Recommendation

To be safe and universally accepted for synthesis, any process statement that models memorizing behavior must be organized as follows:

```
process (Clk_C, Rst_R) <----- sensitivity list, no more signals accepted!  
begin  
  <----- no other statement allowed here!  
  -- activities triggered by asynchronous active-high reset  
  if Rst_R='1' then  
    PresentState_DP <= STARTSTATE;  
    .....
```

-- activities triggered by rising edge of clock

```
  elsif Clk_C'event and Clk_C='1' then <----- no more term allowed here!  
    <----- extra subconditions, if any, accepted here.  
    PresentState_DP <= NextState_DN; -- admit next state into state register  
    .....
```

<----- no further elsif or else clause allowed here!

```
  end if;  
  <----- no statement allowed here!  
end process;
```



## Granularity of VHDL processes

Whether the subfunction being modeled by a concurrent process is simple or complex is entirely open. A single process statement can be made to capture almost anything between

- ▶ a humble piece of wire or
- ▶ an entire image compression circuit, for instance.

### Hint

For the sake of modularity and legibility, do not cram too much functionality into a concurrent process.

## Signal/variable initialization vs. hardware reset facility

VHDL supports assigning an initial value in a declaration statement.

Example `signal Acceleration_D : integer := 0;`

Example `variable Speed : real := 1.25E2;`

- ▶ The initial value defines the objects' state at  $t = 0$ , just before the simulator enters the first simulation cycle.

## Signal/variable initialization vs. hardware reset facility

VHDL supports assigning an initial value in a declaration statement.

Example `signal Acceleration_D : integer := 0;`

Example `variable Speed : real := 1.25E2;`

- ▶ The initial value defines the objects's state at  $t = 0$ , just before the simulator enters the first simulation cycle.
- ▶ A hardware reset mechanism remains ready to reconduct the circuit into a predetermined start state **at any time**  $t \geq 0$  using a dedicated reset signal distributed to all bistables concerned.

### Observation

These are two totally different things. An initialized signal or variable will neither model a reset facility nor synthesize into one.

*A code example for how to model a reset has been given just a few slides back.*

## Detecting clock edges and other signal events

VHDL provides a **signal attribute** to detect signal transitions.

Example: `if Clk_C'event and Clk_C='1' then ... endif;`  
↳ will synthesize into (edge-triggered) flip-flops.

Alternative syntax: `if rising_edge(Clk_C) then ... endif;`  
(defined in IEEE 1164 std for `std_logic` and `std_ulogic`)

## Detecting clock edges and other signal events

VHDL provides a **signal attribute** to detect signal transitions.

Example: `if Clk_C'event and Clk_C='1' then ... endif;`  
↳ will synthesize into (edge-triggered) flip-flops.

Alternative syntax: `if rising_edge(Clk_C) then ... endif;`  
(defined in IEEE 1164 std for `std_logic` and `std_ulogic`)

Signal attribute: a named characteristic of a signal, e.g.

- ▶ `'event` ↳ typically the only one supported for synthesis
- ▶ `'transaction`
- ▶ `'driving`
- ▶ `'last_value`
- ▶ `'stable` ↳ most useful in simulation models
- ▶ ...
- ▶ user-defined

## How to check timing conditions

Please recall:

- ▶ Latches, flip-flops, RAMs, etc. impose timing requirements that must not be violated, otherwise circuit behavior becomes unpredictable.

## How to check timing conditions

Please recall:

- ▶ Latches, flip-flops, RAMs, etc. impose timing requirements that must not be violated, otherwise circuit behavior becomes unpredictable.

↪ A simulation model is in charge of two things:

1. Check whether input waveforms indeed conform with timing requirements (if any).
2. Evaluate input data to update outputs and/or state.

VHDL supports this plan with

- ▶ signal attribute 'stable and
- ▶ assertion statements.

## How to check timing conditions

Please recall:

- ▶ Latches, flip-flops, RAMs, etc. impose timing requirements that must not be violated, otherwise circuit behavior becomes unpredictable.

↪ A simulation model is in charge of two things:

1. Check whether input waveforms indeed conform with timing requirements (if any).
2. Evaluate input data to update outputs and/or state.

VHDL supports this plan with

- ▶ signal attribute 'stable and
- ▶ assertion statements.

**Concurrent assertion statement** A passive process capable of checking user-defined properties and of generating a message but not of updating signals.



## Example: Setup and hold time checks

```
architecture behavioral of setff is
    signal State_DP : std_logic;    -- state signal
begin

    assert (not (Clk_CI'event and Clk_CI='1' and not Dd_DI'stable(1.09 ns)))
        report "setup time violation" severity warning;
    assert (not (Dd_DI'event and Clk_CI='1' and not Clk_CI'stable(0.60 ns)))
        report "hold time violation" severity warning;

    memzing: process (Clk_CI, Rst_RBI)
    begin
        if Rst_RBI='0' then
            State_DP <= '0';
        elsif Clk_CI'event and Clk_CI='1' then
            State_DP <= Dd_DI;
        end if;
    end process memzing;

    Qq_DO <= State_DP after 0.92 ns;

end behavioral;
```

## Inspecting the event queue to check for timing violations

 


Figure: Done by searching the event queue for past events.

### Observation

Any inspection of the event queue for compliance with timing requirements must necessarily look backward in time.

# 5th HDL capability: Facilities for model parametrization

 


Figure: ... plus parametrization with adjustable quantities and conditional items.

## Why it pays to keep HDL models parametrized

1. Imagine you have devised a synthesis model for a datapath unit
  - ▶ 16 data registers
  - ▶ 17 arithmetic and logic operations
  - ▶ 32 bit word width

## Why it pays to keep HDL models parametrized

1. Imagine you have devised a synthesis model for a datapath unit
  - ▶ 16 data registers
  - ▶ 17 arithmetic and logic operations
  - ▶ 32 bit word width
2. In addition, you need a similar unit for address computations
  - ▶ 5 data registers
  - ▶ 8 arithmetic and logic operations
  - ▶ 24 bit word width

## Why it pays to keep HDL models parametrized

1. Imagine you have devised a synthesis model for a datapath unit
  - ▶ 16 data registers
  - ▶ 17 arithmetic and logic operations
  - ▶ 32 bit word width
2. In addition, you need a similar unit for address computations
  - ▶ 5 data registers
  - ▶ 8 arithmetic and logic operations
  - ▶ 24 bit word width

Easy to derive model 2. by modifying the existing HDL code, **but**

- ▶ maintenance effort doubled
- ▶ what if you later needed a third and a fourth model?

### HDL requirement no.5

Means for accommodating distinct architecture choices and parameter settings within a single piece of code.

## Generics

```
component parityoddw    -- w-input odd parity gate
  generic (
    WIDTH : natural range 2 to 32;    -- number of inputs with supported range
    TCD   : time := 0 ns,             -- contamination delay with default value
    TPD   : time := 1.0 ns );        -- propagation delay with default value
  port (
    Inp_DI : in  std_logic_vector(WIDTH-1 downto 0);
    Oup_DO : out std_logic );
end component;


.....
constant NUMBITS : natural = 12;
.....
-- component instantiation statement
u173: parityoddw
  generic map ( WIDTH => NUMBITS, TCD => 0.05 ns, TPD => (NUMBITS * 0.1 ns) )
  port map ( Inp_DI => DataVec_D , Oup_DO => Parbit_D );
```

- Signals** carry time-varying info between processes and design entities.
- Generics** serve to disseminate time-invariant details to design entities, they **do not have any direct hardware counterpart**.

 
## Conditional spawning of processes I

Consider a cellular automaton: Game of Life by John H. Conway (1970)

Show <http://www.bitstorm.org/gameoflife/>



2D array of identical cells

 




 
## Conditional spawning of processes I

Consider a cellular automaton: Game of Life by John H. Conway (1970)

Show <http://www.bitstorm.org/gameoflife/>



2D array of identical cells

 

### HDL requirement no.5'

Means for varying the number of processes (and of components too) as a function of parameter settings made **after the source code is frozen**.

## Conditional spawning of processes II

### The generate statement

- ▶ allows to decide on the number of concurrent processes immediately before simulation or synthesis begins with no changes to the basic code
- ▶ produces processes under control of constants and generics
- ▶ comes in two flavors

`if ... generate`

to capture the conditional presence or absence  
of a process

`for ... generate`

to capture a number of replications of a process  
where the number is subject to change

## Example: Game of Life

```
.....
-- spawn a process for each cell in the array
row : for ih in HEIGHT-1 downto 0 generate -- repetitive generation
  cell : for iw in WIDTH-1 downto 0 generate -- repetitive generation
    memzing: process(Clk_C)
      subtype live_neighbors_type is integer range 0 to 8;
      variable live_neighbors : live_neighbors_type;
    begin
      if Clk_C'event and Clk_C='1' then
        live_neighbors := live_neighbors_at(ih,iw);
        if State_DP(ih,iw)='0' and live_neighbors=3 then
          State_DP(ih,iw) <= '1'; -- birth
        elsif State_DP(ih,iw)='1' and live_neighbors<=1 then
          State_DP(ih,iw) <= '0'; -- death from isolation
        elsif State_DP(ih,iw)='1' and live_neighbors>=4 then
          State_DP(ih,iw) <= '0'; -- death from overcrowding
        end if;
      end if;
    end process memzing;
  end generate cell;
end generate row;
.....
```

## Conditional instantiation of components

The generate mechanism also works for component instantiation.

*Refer to transparency `binary2gray.vhd(structural)` for code!*

As usual:

1. Declare all components to be used.
2. Declare all signals that run back and forth unless they are already known from the port clause.
3. Instantiate components specifying all terminal-to-signal connections.

New:

4. Use `if ... generate` and `for ... generate` statements to make instantiation conditional.

## Multiple models for one circuit block


VHDL accepts multiple architecture bodies for the same entity declaration.  
Why would you want that?

## Multiple models for one circuit block

VHDL accepts multiple architecture bodies for the same entity declaration.  
Why would you want that?

- ▶ Because over a design cycle the same functionality needs to be modeled at distinct levels of detail.
  1. Algorithmic model (purely behavioral)
  2. RTL model (for simulation and synthesis)
  3. Post synthesis gate-level netlist (timing estimated)
  4. Post layout gate-level netlist (timing back-annotated)
  
- ▶ To evaluate different circuit implementations for one block (in terms of  $A$ ,  $t_{lp}$ ,  $E$ , etc.).
 
# Entity declaration versus architecture body




- bold** identifier, i.e. name of entity or architecture
- $\square$  ports convey dynamic i.e. time-varying information
- ~* generics convey static i.e. time-invariant information
- italic* type of information conveyed

external view one entity declaration  
 internal view one or more architecture bodies

higher level of abstraction  
 next lower level of abstraction

typically used for synthesis

**behavioral**

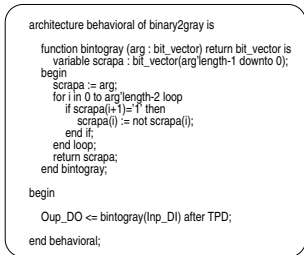


as the design progresses



**structural**

typically used for place & route

 

## Configuration specification and binding

With multiple architecture bodies, there must be a way to indicate which one to use for simulation and synthesis

↪ configuration specification statement.

```
for u113: binary2gray use entity binary2gray(behavioral);  
for u188: binary2gray use entity binary2gray(structural);
```

The mechanism is more general. A component instantiated under one name can be bound to an entity with a different name, and this binding does not need to be the same for all instances of that component.

```
for all: xnor2_gate use entity GTECH_XNOR2(behavioral);  
for all: inverter_gate use entity GTECH_NOT(behavioral);
```



## Configuration specification and binding

With multiple architecture bodies, there must be a way to indicate which one to use for simulation and synthesis

↪ configuration specification statement.

```
for u113: binary2gray use entity binary2gray(behavioral);  
for u188: binary2gray use entity binary2gray(structural);
```

The mechanism is more general. A component instantiated under one name can be bound to an entity with a different name, and this binding does not need to be the same for all instances of that component.

```
for all: xnor2_gate use entity GTECH_XNOR2(behavioral);  
for all: inverter_gate use entity GTECH_NOT(behavioral);
```

### Warning

Do not pack two functionally distinct behaviors into two architecture bodies that belong to the same entity declaration as this is extremely confusing!

## Insight gained

VHDL provides a range of constructs for writing parametrized circuit models:

- ▶ generic quantities
- ▶ `for...generate` and `if...generate` statements
- ▶ multiple architecture bodies for a single entity
- ▶ configurations along with the pertaining declaration and specification statements

### VHDL property

It is possible to establish a model without committing the code to any specific number of processes and/or instantiated components.

## Insight gained

VHDL provides a range of constructs for writing parametrized circuit models:

- ▶ generic quantities
- ▶ `for...generate` and `if...generate` statements
- ▶ multiple architecture bodies for a single entity
- ▶ configurations along with the pertaining declaration and specification statements

### VHDL property

It is possible to establish a model without committing the code to any specific number of processes and/or instantiated components.

↪ A preparatory step must take place before simulation or synthesis can begin  $\mapsto$  elaboration and binding.



## What you ought to know about programming

Proven concepts from safe and modular programming include

- ▶ Structured flow control statements (no goto)
- ▶ Typing and type checking
- ▶ Data structures (enumerated types, arrays, records)
- ▶ Subprograms
- ▶ Packages (collections of type declarations and subprograms)
- ▶ Information hiding (declaration module vs. implementation module)

## What you ought to know about programming

Proven concepts from safe and modular programming include

- ▶ Structured flow control statements (no goto)
- ▶ Typing and type checking
- ▶ Data structures (enumerated types, arrays, records)
- ▶ Subprograms
- ▶ Packages (collections of type declarations and subprograms)
- ▶ Information hiding (declaration module vs. implementation module)

### HDL requirement no.6

Make those ideas available to HDL model developers too.

*No graphic illustration at this point.*

## Concepts borrowed from programming languages

- ▶ Structured flow control statements
  - ▶ `if...then...elsif...else`, `case`
  - ▶ `loop`, `exit`, `next`
- ▶ Strong typing (`type`, `subtype`, type checking at compile time)
- ▶ Enumerated types
- ▶ Composite data types (`array`, `record`)
- ▶ Subprograms (`function`, `procedure`)
- ▶ Packages (`package`)
- ▶ Information hiding
  - ▶ declaration module (`entity` declaration, `package` declaration)
  - ▶ implementation module (`architecture body`, `package body`)

## Data types and subtypes

A data type defines a set of values and a set of operations. Users may declare their own data types or use predefined ones. Type declaration.

Example `type month is (JANUARY, FEBRUARY, ... , DECEMBER);`

### VHDL property

VHDL is strongly typed. Extensive type checking is performed.  
Types must be made to match prior to assignment or comparison.



## Data types and subtypes

A data type defines a set of values and a set of operations. Users may declare their own data types or use predefined ones. Type declaration.

Example `type month is (JANUARY, FEBRUARY, ... , DECEMBER);`

### VHDL property

VHDL is strongly typed. Extensive type checking is performed.  
Types must be made to match prior to assignment or comparison.

A subtype shares the operations with its parent type, but differs in that it takes on a subset of data values only. Subtype declaration.

Example `subtype day is integer range 1 to 31;`

### Hint

It is good practice to indicate an upper and a lower bound when using integers for hardware modeling. On-line range checking (simulation) and economic sizing of circuits (synthesis) otherwise remain elusive.

## Package declaration and package body

A package is a named collection of types and/or subprograms that is made visible by referring to it in a use clause. Example:

```
-- package declaration
package calendar is
  type month is (JANUARY, FEBRUARY, MARCH, APRIL, MAY, JUNE, JULY,
                AUGUST, SEPTEMBER, OCTOBER, NOVEMBER, DECEMBER);
  subtype day is integer range 1 to 31;
  function nextmonth (given_month : month) return month;
  function nextday (given_day : day) return day;
end calendar;

-- package body
package body calendar is

  function nextmonth (given_month : month) return month is
  begin
    if given_month=month'right then return month'left;
    else return month'rightof(given_month);
    end if;
  end nextmonth;

  function nextday (given_day : day) return day is
  .....
  end nextday;

end calendar;
```

## Predefined packages

**standard package** defines data types and subtypes of VHDL along with the pertaining logic and arithmetic operations and a few more features.

Always gets precompiled into design library `std`.

Users do not normally need to care much about it.

**textio package** defines subprograms related to the reading and writing of ASCII files (obviously not intended for synthesis).

Always gets precompiled into design library `std`.

Source code must include the line `use std.textio.all;` to make definitions immediately available.

## Design unit, design file and design library

### VHDL property

VHDL supports information hiding and incremental compilation.


**Design unit** a language construct amenable to compilation on its own.

- package declaration,
- package body,
- entity declaration,
- architecture body, and
- configuration declaration.

**Design file** a file that holds one or more design units.

**Design library** a named repository for a collection of design units after compilation on a host computer.  
Specific for a platform (host computer and software product).  
Can accommodate many design files and design units.

# VHDL source code and intermediate data

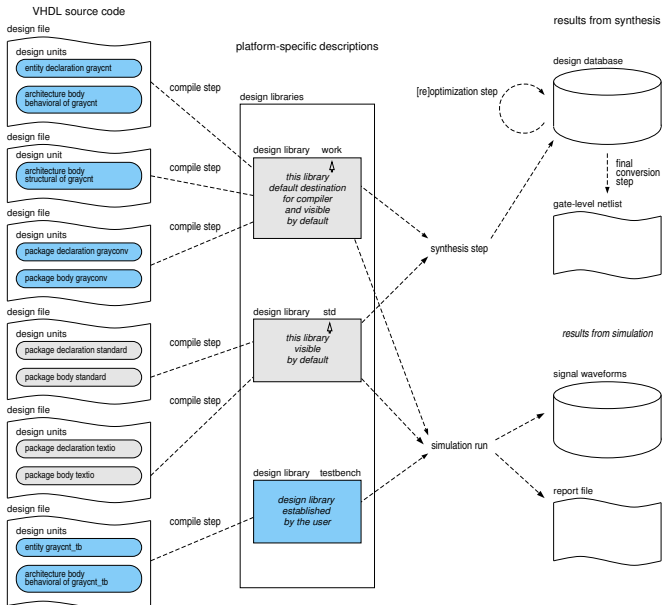

## Subject

# Key concepts and constructs of SystemVerilog

*For a VHDL course, skip the next 75 or so slides.*

# Hardware description language requirements

## HDL requirement no.1

Means for expressing how circuits are being composed from subcircuits and how those subcircuits connect to each other.

# 1st HDL capability: Circuit hierarchy and connectivity

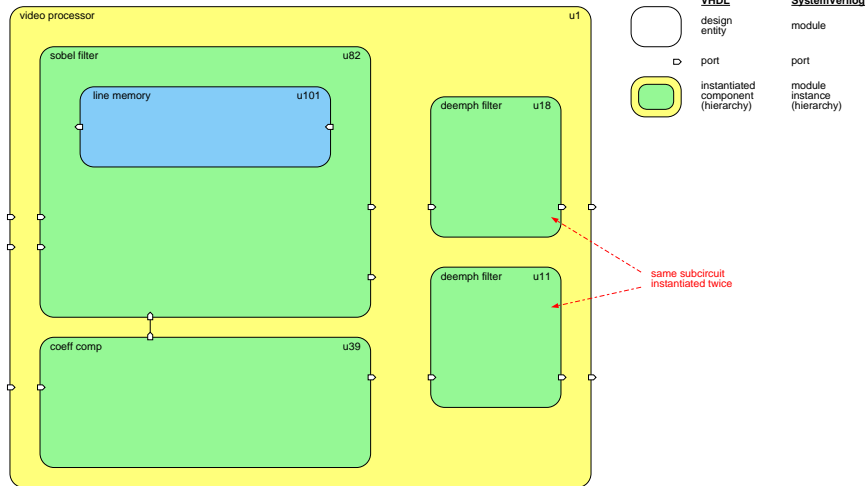



Figure: Hierarchical composition ...


 
## Module header

Specifies the external interface of a (sub)circuit (small or large).

```
// module header with external interface
module lfsr4
  ( output logic Oup_DO,
    input logic Clk_CI, Rst_RBI, Ena_SI ) ;
  ...
endmodule
```



- ▶ The port list declares all signals of a module that are accessible from outside (i.e. the terminals of a circuit as opposed to its inner nodes).

## Module body I: a structural circuit model

 


Figure: Linear-feedback shift register circuit to be described.

## Module body I: a structural circuit model

*Refer to transparency `lfsr4struc.sv` for code!*

Describes a circuit or netlist assembled from components and wires.

1. Declare all `modules` to be used.
2. Declare all variables that run back and forth unless they are already known from the port list.
3. Instantiate `modules` specifying all terminal-to-signal connections.

## Practical advice

### Hints

- ▶ SystemVerilog is case-sensitive, e.g. `clk_ci`  $\neq$  `CLK_CI`.
- ▶ Naming a variable `input` or `output` is all too tempting, yet these are reserved words in SystemVerilog. We recommend `Inp` and `Outp` instead.

## Practical advice

### Hints

- ▶ SystemVerilog is case-sensitive, e.g. `clk_ci`  $\neq$  `CLK_CI`.
- ▶ Naming a variable `input` or `output` is all too tempting, yet these are reserved words in SystemVerilog. We recommend `Inp` and `Oup` instead.

No rule without exceptions. Case-**insensitive** are

- ▶ the letters `d`, `h`, `o` and `b` that indicate the base in decimal, hexadecimal, octal and binary numbers,
- ▶ the hex digits `A` through `F`, and
- ▶ the logic values `X` and `Z`.

Example:

```
16'hFE39 // casing of a 16-bit hexadecimal number for max. legibility
```

## How to compose a circuit from components

How do you proceed when asked to fit a circuit board with components?

1. Think of a part's exact name, e.g. GTECH\_FD2
2. Fetch a copy and assign it some unique identifier it, e.g. u10
3. Solder its terminals to existing metal pads on the board

The module instantiation statement does exactly that. Example:

```
GTECH_FD2 u10
  ( .D(n11),           // port map begins here
    .CP(Clk_C),
    .CD(Rst_RB),
    .Q(State_DP[1]) ); // port map ends here
```

### Note

Each `.instance_terminal(circuit_node)` item stands for an electrical connection.

## The essence of structural circuit modeling

- ▶ SystemVerilog can describe the hierarchical composition of a circuit by
  - ▶ instantiating modules and by
  - ▶ interconnecting them with the aid of wires normally modeled as variables.
- ▶ Structural HDL models hold the same information as circuit netlists do.
- ▶ Manually writing structural HDL models is not particularly attractive.
- ▶ Most structural models are in fact obtained from RTL models by automatic synthesis.

## The essence of structural circuit modeling

- ▶ SystemVerilog can describe the hierarchical composition of a circuit by
  - ▶ instantiating modules and by
  - ▶ interconnecting them with the aid of wires normally modeled as variables.
- ▶ Structural HDL models hold the same information as circuit netlists do.
- ▶ Manually writing structural HDL models is not particularly attractive.
- ▶ Most structural models are in fact obtained from RTL models by automatic synthesis.

### HDL requirement no.2

Means for expressing circuit behavior including the combined effects of multiple subcircuits that operate jointly and concurrently.



## 2nd HDL capability: Interacting concurrent processes

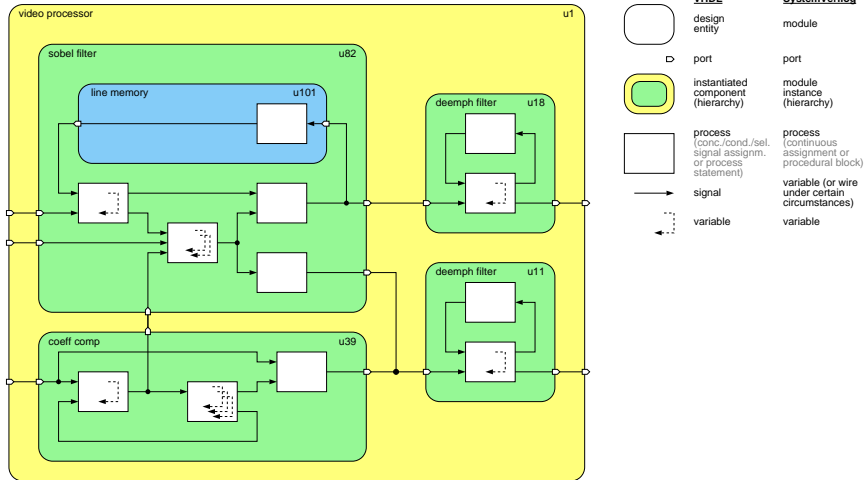


Figure: ... plus behavior modeled with the aid of concurrent processes ...

## Constants and variables

What everyone knows from software languages:

- ▶ Constant declaration

Example

```
const integer FERMAT_PRIME_4 = 65537;
```

- ▶ Variable declaration

Examples

(keyword `var` is optional)

```
var real Brd = 2.48678E5;
```

```
real Ddr := 1.08179E5;
```

- ▶ Variable assignment (procedural assignment)

Example

```
Brd = Brd + Ddr;
```

## Constants and variables

What everyone knows from software languages:

- ▶ Constant declaration

Example

```
const integer FERMAT_PRIME_4 = 65537;
```

- ▶ Variable declaration

Examples

(keyword `var` is optional)

```
var real Brd = 2.48678E5;
```

```
real Ddr := 1.08179E5;
```

- ▶ Variable assignment (procedural assignment)

Example

```
Brd = Brd + Ddr;
```

... plus an HDL particularity:

- ▶ Variable assignment (continuous assignment)

Example

```
assign Brd = Brd + Ddr;
```

# How to describe combinational logic behaviorally I

## Continuous assignment

- ▶ Syntactically simplest form of a process.
- ▶ Drives one variable.

Example:

```
logic Aa_D, Bb_D, Cc_D, Oup_D;  
.....  
assign Oup_D = Aa_D ^ (Bb_D & ~Cc_D);
```

- ▶ Typically used to model some combinational behavior (such as an arithmetic or logic operation) when there is no need for branching.

---

<sup>0</sup>Logic operators: ^=XOR, &=AND, |=OR, ~=NOT

## How to describe combinational logic behaviorally II

Continuous assignment **with a condition operator included**

Example:

```
logic Add_S, Aa_D, Bb_D, Oup_D;  
.....  
assign Oup_D = Add_S ? (Aa_D + Bb_D) : (Aa_D - Bb_D);
```

Syntax: conditional\_expression ? then\_expression : else\_expression

Glimpse ahead: A continuous assignment gets activated by any change of any signal on the right-hand side.

## How to describe combinational logic behaviorally III

### Procedural blocks

- ▶ `always_comb`, `always_ff`, `always_latch`  $\mapsto$  for circuit modeling.
- ▶ `always`, `initial`, `final`  $\mapsto$  for testbench design.

## How to describe combinational logic behaviorally III

### Procedural blocks

- ▶ `always_comb`, `always_ff`, `always_latch`  $\mapsto$  for circuit modeling.
- ▶ `always`, `initial`, `final`  $\mapsto$  for testbench design.
- ▶ There is a special construct for combinational circuitry.

Example:

```
always_comb
```

```
begin
```

```
    Spring_D = 0;    // execution begins here
```

```
    if (ThisMonth_D==MARCH & ThisDay>=21) Spring_D = 1;
```

```
    if (ThisMonth_D==APRIL)                Spring_D = 1;
```

```
    if (ThisMonth_D==MAY)                  Spring_D = 1;
```

```
    if (ThisMonth_D==JUNE & ThisDay<=20) Spring_D = 1;
```

```
end    // process suspends here
```

## Procedural block versus continuous assignment

When compared to a continuous assignment, a procedural block

- ▶ is capable of updating **two or more variables at a time**,
- ▶ captures the instructions for doing so in a **sequence of statements** that are going to be executed one after the other,
- ▶ gives the liberty to make use of variables **for temporary storage**,
- ▶ provides more detailed control over the **conditions for activation**.



## Procedural block versus continuous assignment

When compared to a continuous assignment, a procedural block

- ▶ is capable of updating **two or more variables at a time**,
- ▶ captures the instructions for doing so in a **sequence of statements** that are going to be executed one after the other,
- ▶ gives the liberty to make use of variables **for temporary storage**,
- ▶ provides more detailed control over the **conditions for activation**.

### Observation

Procedural blocks are best summed up as being concurrent outside and sequential inside.

- ▶ They are indispensable to model memorizing circuit behavior.

# How to describe a register behaviorally I

## Procedural blocks (revisited)

- ▶ `always_comb`, `always_ff`, `always_latch`  $\mapsto$  for circuit modeling.
- ▶ `always`, `initial`, `final`  $\mapsto$  for testbench design.
- ▶ There is a special construct for edge-triggered circuitry and a separate one for level-sensitive circuitry.

$\mapsto$  A net progress over Verilog and VHDL.


## How to describe a register behaviorally II

Example of an edge-triggered register that features

1. an asynchronous reset,
2. a synchronous load, and
3. an enable.

```
always_ff @(posedge Clk_C, negedge Rst_RB) // sensitivity list
// activities triggered by asynchronous reset
if (~Rst_RB)
    State_DP <= '0; // shorthand for all bits zero
// activities triggered by rising edge of clock
else
    // when synchronous load is asserted
    if (Lod_S)
        State_DP <= '1; // shorthand for all bits one
    // otherwise assume new value iff enable is asserted
    else if (Ena_S)
        State_DP <= State_DN; // admit next state into state register
```

# More than just VHDL nostalgia

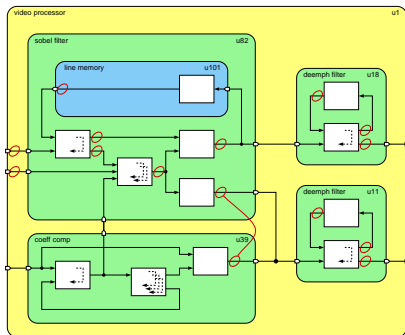

VHDL	SystemVerilog
design entity	module
port	port
instantiated component (hierarchy)	module instance (hierarchy)
process (cond./sel. signal assignm. or process statement)	process (continuous assignment or procedural block)
signal	variable (or wire under certain circumstances)
variable	variable
electrical type (e.g. std_logic)	electrical type (e.g. logic)
resolved type (e.g. std_logic)	net type (e.g. wire)

## Suggestion

Code is easier to read when when “signals” can be told from local variables. We append an underscore followed by a suffix of upper-case letters to those variables that convey information between concurrent processes, e.g. Carry\_DB, AddrCnt\_SN, Irq\_AMI.

*Details of our naming convention are to follow in chapter 6 “The Case for Synchronous Design”.*

## Module body II: a behavioral circuit model

Describes how concurrent processes interact via signals and how they alter them.

```
// external interface of module
module lfsr4 (
    input logic Clk_CI, Rst_RBI, Ena_SI, // reset is active low
    output logic Oup_DO );




// behavioral model for module

// declare internal variables
logic [1:4] State_DP, State_DN; // for present and next state

// computation of next state using concatenation of bits
assign State_DN = {(State_DP[3] ^ State_DP[4]), State_DP[1:3]};

// updating of state
always_ff @(posedge Clk_CI, negedge Rst_RBI)
// activities triggered by asynchronous reset
if (~Rst_RBI)
    State_DP <= 4'b0001;
// activities triggered by rising edge of clock
else
    if (Ena_SI)
        State_DP <= State_DN; // admit next state into state register

   // updating of output
assign Oup_DO = State_DP[4];
endmodule
```



## The essence of behavioral circuit modeling


In SystemVerilog, the behavior of a digital circuit typically gets described by a collection of concurrent processes that

- ▶ execute simultaneously, that
- ▶ communicate via variables, and where
- ▶ each such process represents some subfunction.

### Hint for RTL synthesis

- ▶ Model each register with an `always_ff` statement (or an `always_latch` if level-sensitive rather than edge-triggered).
- ▶ Prefer continuous assignments for describing the combinational logic in between.

## Hardware modeling styles

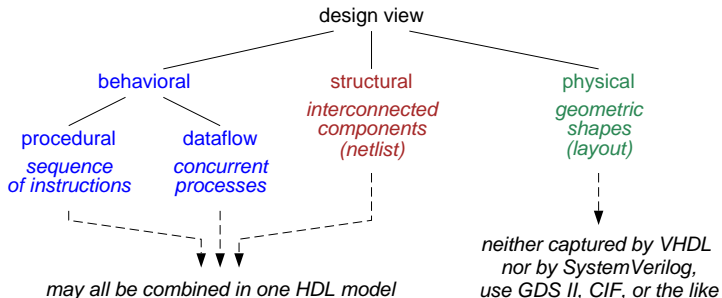

### Observation

SystemVerilog allows for procedural, dataflow, and structural modeling styles to be freely combined in a single model.

# Procedural, dataflow, and structural models compared I

*Refer to transparency [fulladd.sv](#) for code!*


Compare in terms of

1. number of processes
2. number of variables that communicate between processes
3. number of variables confined to within one process
4. impact of ordering of statements
5. interaction with event queue
6. portability of source code

Note: Adders are normally synthesized from algebraic expressions, a full-adder has been chosen here for its simplicity and conciseness.



## Procedural, dataflow, and structural models compared II

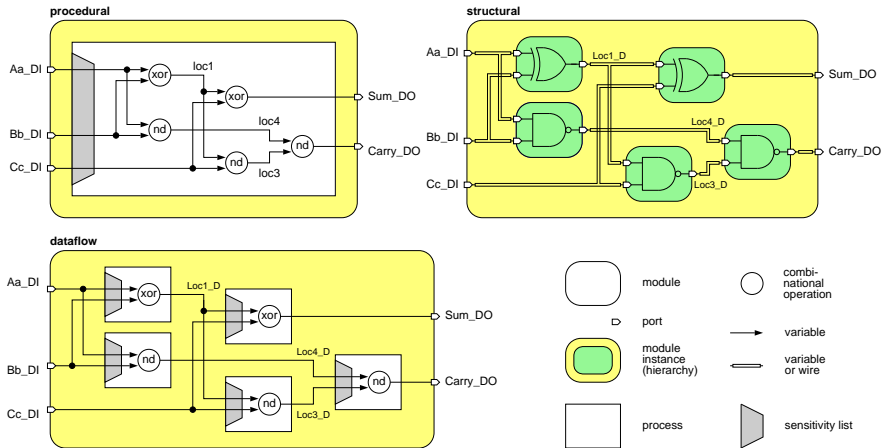

**Figure:** Modeling styles illustrated with a full adder as example.

## Example: The ones counter

*Refer to transparency onescnt.sv for code!*

### Observe

1. In spite of its name, this is a memoryless subfunction that finds applications in large adder circuits.
2. The output is a 3 bit number that indicates how many of the four input bits are 1 (logic high).
3. The great diversity of modeling styles to express exactly the same functionality.

## Example: The ones counter

*Refer to transparency onescnt.sv for code!*

### Observe

1. In spite of its name, this is a memoryless subfunction that finds applications in large adder circuits.
2. The output is a 3 bit number that indicates how many of the four input bits are 1 (logic high).
3. The great diversity of modeling styles to express exactly the same functionality.

### Observation

Some code examples are compact and easy to understand, others are more cryptic or tend to grow exponentially.

## 3rd capability: A discrete replacement for electrical signals

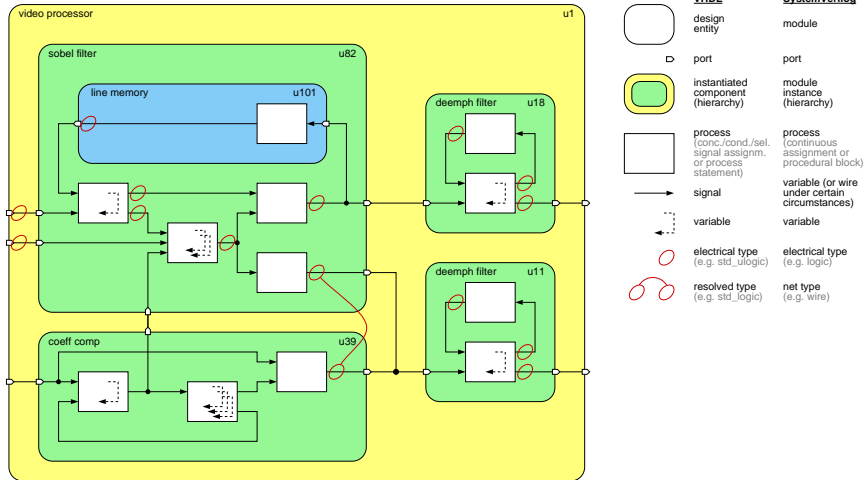


Figure: ... plus data types for modeling electrical phenomena ...

# What you ought to know about bidirectional busses I

 


Figure: Memory read and write transfers in a computer.

## What you ought to know about bidirectional busses II

### Requirements:

- ▶ Each bidirectional line is to be driven from multiple places, so one needs a **multi-driver signal** (as opposed to a single-driver signal).
- ▶ Driving alternates.
- ▶ Buffers must be able to **electrically release** the line hence the name “three-state” output (0, 1, disabled output = high-impedance state).
- ▶ Requires some kind of access control mechanism (centralized or distributed).

## What you ought to know about bidirectional busses II

### Requirements:

- ▶ Each bidirectional line is to be driven from multiple places, so one needs a **multi-driver signal** (as opposed to a single-driver signal).
- ▶ Driving alternates.
- ▶ Buffers must be able to **electrically release** the line hence the name “three-state” output (0, 1, disabled output = high-impedance state).
- ▶ Requires some kind of access control mechanism (centralized or distributed).

### Failure modes:

- ▶ Stationary drive conflict  $\mapsto$  functional failure or damage.
- ▶ Floating voltage  $\mapsto$  electrically undesirable condition.

*Presentation focusses on HDL modeling, remedies to be discussed in chapter 10 "Gate- and Transistor-Level Design".*

## Why do binary types not suffice to model digital circuits?

Digital circuits exhibit characteristics and phenomena such as

- ▶ transients,
- ▶ three-state outputs,
- ▶ drive conflicts, and
- ▶ power-up

that can not be modeled with 0 and 1 alone.



## Why do binary types not suffice to model digital circuits?

Digital circuits exhibit characteristics and phenomena such as

- ▶ transients,
- ▶ three-state outputs,
- ▶ drive conflicts, and
- ▶ power-up

that can not be modeled with 0 and 1 alone.

### HDL requirement no.3

A multi-valued logic system capable of capturing the effects of both node voltage and source impedance.

# The SystemVerilog logic system I

**Voltage** is quantized into three logic states

- low                      logic low, that is below  $U_l$ .
- high                     logic high, that is above  $U_h$ .
- unknown                either “low”, “high” or anything in between  
e.g. as a result from a short between two drivers.

# The SystemVerilog logic system I

**Voltage** is quantized into three logic states

- low                      logic low, that is below  $U_l$ .
- high                     logic high, that is above  $U_h$ .
- unknown                either “low”, “high” or anything in between  
                                 e.g. as a result from a short between two drivers.

Source impedance gets mapped onto two **drive strengths**

- driven                    as exhibited by a driving output
- high-impedance        as exhibited by a disabled three-state output

- ▶ Note the absence of drive strength “weak”  
as exhibited by a passive pull-up/-down resistor or a snapper.

## The SystemVerilog logic system II

No charge retention in high-impedance state  $\rightsquigarrow$

- charged low
- charged high
- charged unknown

are all merged into a single value of undetermined state (voltage).

## The SystemVerilog logic system II

No charge retention in high-impedance state  $\rightsquigarrow$

- charged low
- charged high
- charged unknown

are all merged into a single value of undetermined state (voltage).

Two extra conditions ought to be distinguished, namely:

- uninitialized      **signal has never been assigned any value since power-up**  
(applicable to simulation only).
- don't care      **don't care condition for logic minimization,**  
distinction between "low" or "high" immaterial  
(applicable to synthesis only).

## The SystemVerilog logic system II

No charge retention in high-impedance state  $\rightsquigarrow$

- charged low
- charged high
- charged unknown

are all merged into a single value of undetermined state (voltage).

Two extra conditions ought to be distinguished, namely:

- uninitialized      **signal has never been assigned any value since power-up**  
(applicable to simulation only).
- don't care      **don't care condition for logic minimization,**  
distinction between “low” or “high” immaterial  
(applicable to synthesis only).

Oddities:

- ▶ No attempt to distinguish between “unknown” and “uninitialized”.
- ▶ Same symbol X is used as for “unknown” and “don't care”.

## The SystemVerilog logic system III

Uses a total of four logic values to model electrical signals.

logic value → ↓	logic state		
	low	unknown	high
uninitialized		X	
strength driven	0	X	1
high-impedance	Z	Z	Z
don't care		X	

Defines two data types that share the above set of values:

- o `logic` *Difference to be*
- o `wire` *explained soon*

## Illustrations

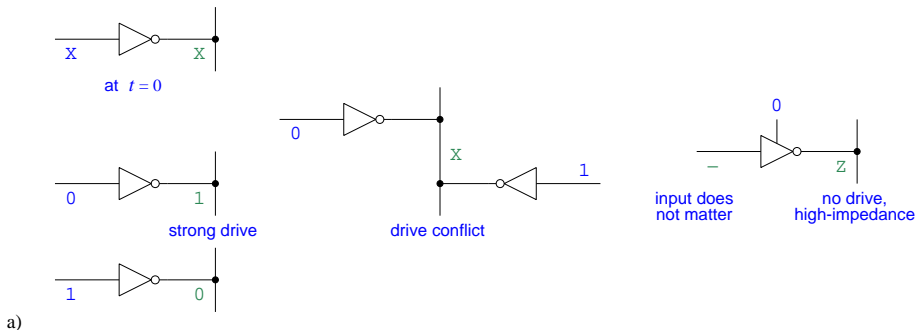


Figure: The SystemVerilog MVL-4 illustrated.



## How to model a bidirectional line in SystemVerilog I

Want to model a circuit node that can be driven from multiple subcircuits?  
↪ Use a wire and two or more continuous assignments with a condition.


Example:

```
wire Com_DZ;  
logic Aa_D, Bb_D, SelA_S, SelB_S;  
  
.....  
assign Com_DZ = SelA_S ? ~Aa_D : 1'bZ;  
.....  
assign Com_DZ = SelB_S ? ~Bb_D : 1'bZ;  
.....
```

### Note


Node Com\_DZ is left floating when neither of the two drivers is enabled.
 
## How to model a bidirectional line in SystemVerilog II




single-driver signals `Pp_DZ` and `Qq_DZ`  
may assume distinct logic values,

 - b) no difference between `logic` and `wire`




if multi-driver signal `Com_DZ` is of type  
`logic` then an error message gets issued  
`wire` then the conflict is resolved to `Com_DZ = 1`
 
## How to model a bidirectional line in SystemVerilog II



single-driver signals `Pp_DZ` and `Qq_DZ`  
may assume distinct logic values,

 - b) no difference between `logic` and `wire`



if multi-driver signal `Com_DZ` is of type  
`logic` then an error message gets issued  
`wire` then the conflict is resolved to `Com_DZ = 1`

### Observation

Use `wire` for multi-driver nodes exclusively. When simulating

`wire` tacitly resolves all conflicts that might occur

`logic` supports no multiple drivers, generates an error message

## The SystemVerilog built-in resolution function

	X	0	1	Z
X	X	X	X	X
0	X	0	X	0
1	X	X	1	1
Z	X	0	1	Z

- ▶ This is the default resolution function for type `wire`, others can be added.
- ▶ There can be no resolution function for type `logic` nor for `integer` or any other type of variable.

## Data types for modeling single-bit signals

data type	bit	logic	wire
for simulation purposes			
modeling of power-up phase	no	passable	passable
modeling of weakly driven nodes	no	no	no
modeling of multi-driver nodes	no	no	yes
handling of drive conflicts	n.a.	n.a.	resolved
for synthesis purposes			
three-state drivers	no	yes	yes
don't care conditions	no	yes	yes

## Data types for modeling multi-bit signals

data type(s)	byte, shortint, int, longint	integer	bit vector	logic vector	wire vector
value set per binary digit word width	2 8/16/32/64	4 32	2 at the programmer's discretion	4	4
arithmetic operations default signed/unsigned	yes signed	yes signed	yes unsign.	yes unsign.	yes unsign.
logic operations	yes	yes	yes	yes	yes
access to subwords or bits	yes	yes	yes	yes	yes
modeling of electrical effects	no	passable*	no	passable*	passable

\* Multiple drivers not allowed with this data type.

## Orientation of binary vectors

### Hint

Any vector that contains a data item coded in some positional number system should consistently be declared as  $(i_{MSB} \text{ downto } i_{LSB})$  where  $2^i$  is the weight of the binary digit with index  $i$ .

The MSB so has the highest index assigned to it and appears in the customary leftmost position because  $i_{MSB} \geq i_{LSB}$ .

Example

```
logic [4:0] Hour_D = 5'b10111;
```

## Orientation of binary vectors

### Hint

Any vector that contains a data item coded in some positional number system should consistently be declared as  $(i_{MSB} \text{ downto } i_{LSB})$  where  $2^i$  is the weight of the binary digit with index  $i$ .

The MSB so has the highest index assigned to it and appears in the customary leftmost position because  $i_{MSB} \geq i_{LSB}$ .

Example

```
logic [4:0] Hour_D = 5'b10111;
```

Numerical data types can be declared as unsigned or signed with a modifier.

Example:

```
int unsigned ii...i.
```

```
int signed si...i. in 2's complement format
```



## A word of advice

### Hint

Rather than silently relying on defaults to keep the code as terse as possible, make your intentions reasonably explicit in the code.

- ▶ Not only improves code quality but also accelerates debugging and code maintenance.
- ▶ Defaults are rather unsystematic in SystemVerilog.
- ▶ SystemVerilog is **weakly typed** = little type checking is performed.
  - △ data words get tacitely extended or slashed in width to make things fit
  - ± almost no obligation to include type conversions
  - impossible for tools to find suspect code fragments during compilation

## 4th HDL capability: An event-based model of time

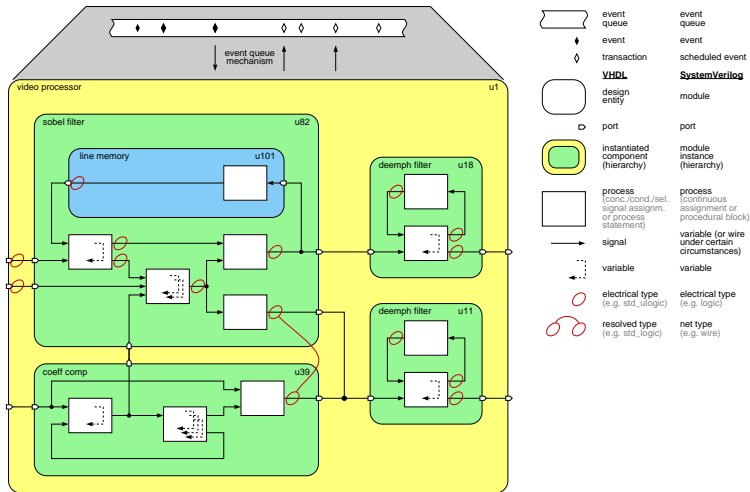


Figure: ... plus an event queue mechanism that governs process activation ...

## How does SystemVerilog simulation work? I

Please recall:

A variable's (or a wire's) value can be altered by any of ...

- ▶ continuous assignment.
- ▶ `always_comb`, `always_ff`, and `always_latch` block (for circuit modeling).
- ▶ `always`, `initial`, and `final` blocks (for testbenches).

### Make sure to understand

- ▶ All the above constructs are **concurrent processes** aka threads of execution (in the sense of the German "nebenläufiger Prozess").
- ▶ "Procedural block", in contrast, refers only to the `always_`, `always`, `initial`, and `final` blocks.

## How does SystemVerilog simulation work? II

- ▶ A typical circuit model comprises many many processes.
- ▶ No more than a few processor cores are normally available for running the simulation code.
- ▶ Yet, simulation is to yield the same result as if all processes were operating simultaneously.

## How does SystemVerilog simulation work? II

- ▶ A typical circuit model comprises many many processes.
- ▶ No more than a few processor cores are normally available for running the simulation code.
- ▶ Yet, simulation is to yield the same result as if all processes were operating simultaneously.

### HDL requirement no.4

A mechanism that schedules processes for sequential execution and that combines their effects such as to perfectly mimic concurrency.

## Notions of time

- Simulation time** is to an HDL what physical time is to the hardware being modeled. The simulator can be thought to maintain some kind of stop watch that registers the progress of simulation time.
- Execution time** (aka wall clock) refers to the time a computer takes to execute statements from the program code during simulation.

## Notions of time

**Simulation time** is to an HDL what physical time is to the hardware being modeled. The simulator can be thought to maintain some kind of stop watch that registers the progress of simulation time.

**Execution time** (aka wall clock) refers to the time a computer takes to execute statements from the program code during simulation.

- ▶ In SystemVerilog simulation, **the continuum of time gets subdivided by events** each of which occurs at a precise moment of simulation time.
- ▶ An update event is said to happen whenever the value of a variable (or wire) changes.

# Event-driven simulation I


Event-driven simulation works in cycles where three stages alternate:

1. Advance simulation time to the next scheduled event thereby making it the current one.
2. Set all variables that are to be updated at the present moment of time to the target value associated with the current event.
3. Invoke all processes that need to respond to the new situation.  
Every assignment there supposed to modify a variable's value causes an event to be entered into the event queue at that point in the future when the variable is anticipated to take on its new value.

Go to 1. and start a new simulation cycle.



## Basic event-queue mechanism

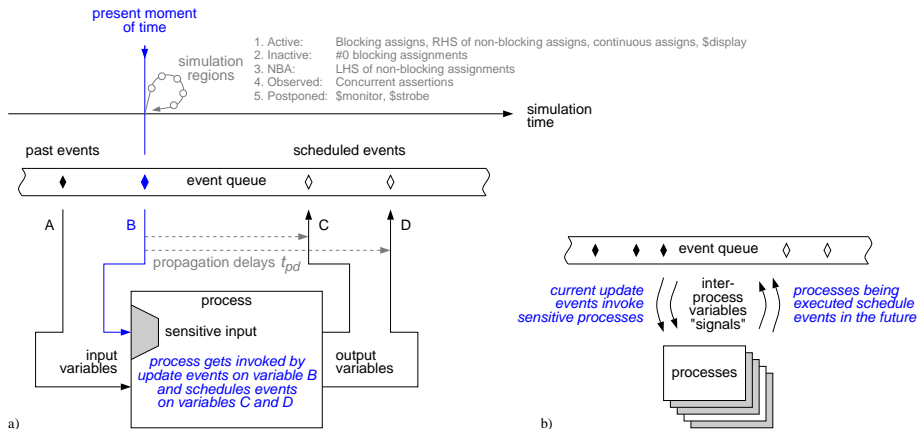

**Figure:** Interactions between the event queue and processes in SystemVerilog.

## Event-driven simulation II

- ▶ Simulation stops when the event queue becomes empty or when simulation reaches a `$stop` or `$finish` instruction.
- ▶ As nothing happens between events, an event-driven simulator essentially skips from one scheduled event to the next.
  - ↔ No computational resources are wasted while models sit idle.

## Event-driven simulation II

- ▶ Simulation stops when the event queue becomes empty or when simulation reaches a `$stop` or `$finish` instruction.
- ▶ As nothing happens between events, an event-driven simulator essentially skips from one scheduled event to the next.
  - ↔ No computational resources are wasted while models sit idle.

### Note the analogy between event queue and agenda

- ▶ Update events are observable from the past evolution of a variable's value.
- ▶ Scheduled events reflect future plans that may or may not materialize.

## Event-driven simulation II

- ▶ Simulation stops when the event queue becomes empty or when simulation reaches a `$stop` or `$finish` instruction.
- ▶ As nothing happens between events, an event-driven simulator essentially skips from one scheduled event to the next.
  - ↪ No computational resources are wasted while models sit idle.

### Note the analogy between event queue and agenda

- ▶ Update events are observable from the past evolution of a variable's value.
- ▶ Scheduled events reflect future plans that may or may not materialize.

### This was just a first order approximation

The exact operation of the SystemVerilog “stratified event queue” is much more complicated as each cycle is organized into 17 ordered “regions”.

## Event-driven simulation III

A process is either active or suspended at any time. Simulation time is stopped while the code of the processes presently active is being carried out.

This implies:

- ▶ All active processes are executed concurrently with respect to simulation time.
- ▶ All sequential statements inside a procedural block (`always`, `initial`, `final`) are executed in zero simulation time.

### Note

The order of process invocation with respect to execution time is undetermined.

## Insight gained

In software languages:

- ▶ Execution strictly follows the order of statements in the source code.

During SystemVerilog simulation:

- ▶ No fixed ordering for carrying out processes  
(including continuous assignments and assertion statements).

### Important observation

When to invoke a process gets determined solely by events on the variables (and wires) that run back and forth between processes.

## Sensitivity list, process suspension and activation I

- ▶ A matching event (value change) on any signal in the sensitivity list (re-)activates the process. Example:

```
//          vvvvvv  sensitivity list  vvvvvv  
always_ff @(posedge Clk_C, negedge Rst_RB)  
    .....
```

- ▶ Constructs for temporarily suspending a process and for stating when it is to resume include:

Statement	Wake-up condition
@(...)	an update event on any of the signals listed here
wait (...)	<i>idem</i> plus the logic conditions specified here
#...	a predetermined lapse of time as specified here

## Sensitivity list, process suspension and activation II

### SystemVerilog property

Continuous assignments have no sensitivity list.  
Any variable on the right-hand side of the assignment activates the process.

Example:

```
assign Out_D = InpA_D + InpB_D;
```

- ▶ InpA\_D and InpB\_D act as wake-up signals here.



## Delay modeling for simulation

Delays are captured with an optional # term in a continuous assignment.

Example

```
assign #TPD Outp_D = InpA_D + InpB_D;
```

## Delay modeling for simulation

Delays are captured with an optional # term in a continuous assignment.

Example `assign #TPD Oup_D = InpA_D + InpB_D;`

Contamination delay must be modeled using a procedural block.

Example:

```
always_comb
begin
    Oup_D <= #TCD '{default:1'bX}; // revert all bits to unknown after tcd
    Oup_D <= #TPD InpA_D + InpB_D; // propagate result to output after tpd
end
```

- Ramps can not be modeled.

## Event-driven simulation IV

 


Figure: The past, present and future of SystemVerilog variables.

- ▶ SystemVerilog variables can convey time-varying information between processes via the event queue. They are instrumental in process invocation which is directed by the same mechanism.

## Blocking versus nonblocking assignments

### SystemVerilog property

How variables interact with the event queue depends on how exactly the assignment is coded.

Assignment Operator Delay term	Continuous assign ... =		Procedural			
	none	non-zero	= (blocking) none	= (blocking) non-zero	<= (nonblocking) none	<= (nonblocking) non-zero
Execution of process	suspends until next update event on a right-hand operand		continues	suspends for delay specified	continues	
Effect on variable	immediate	deferred by delay specified	immediate	deferred by delay specified	following simultan. blocking assignm.	deferred by delay specified

## No binding order of execution for simultaneous events

### SystemVerilog aberration

A simulator is free to execute processes scheduled for the same simulation time in arbitrary order  $\rightsquigarrow$  nondeterminism and race conditions loom.

∅ As opposed to VHDL, SystemVerilog knows of no  $\delta$  delay.

## No binding order of execution for simultaneous events

### SystemVerilog aberration

A simulator is free to execute processes scheduled for the same simulation time in arbitrary order  $\rightsquigarrow$  nondeterminism and race conditions loom.

∅ As opposed to VHDL, SystemVerilog knows of no  $\delta$  delay.

### Rules for writing safe RTL synthesis models

1. Prefer continuous assigns for uncomplicated combinational functions.
2. Do not use procedural blocks other than `always_comb`, `always_ff` and `always_latch`. (Use `always` block only where not for synthesis.)
3. In an `always_comb` block, always use blocking assignments (`=`).
4. In `always_ff` and `always_latch` blocks, use nonblocking assignments (`<=`) only.
5. Do not make `#0` (zero delay expression) procedural assignments.

## Signal/variable initialization vs. hardware reset facility

SystemVerilog supports assigning an initial value in a declaration statement.

Example

```
integer Acceleration_D = 0;
```

- ▶ The initial value defines the objects's state at  $t = 0$ , just before the simulator enters the first simulation cycle.

## Signal/variable initialization vs. hardware reset facility

SystemVerilog supports assigning an initial value in a declaration statement.

Example `integer Acceleration_D = 0;`

- ▶ The initial value defines the objects's state at  $t = 0$ , just before the simulator enters the first simulation cycle.
- ▶ A hardware reset mechanism remains ready to reconduct the circuit into a predetermined start state **at any time**  $t \geq 0$  using a dedicated reset signal distributed to all bistables concerned.

### Observation

These are two totally different things. An initialized variable will neither model a reset facility nor synthesize into one.

*A code example for how to model a reset has been given earlier, another one is to follow shortly.*



## How to check timing conditions

Please recall:

- ▶ Latches, flip-flops, RAMs, etc. impose timing requirements that must not be violated, otherwise circuit behavior becomes unpredictable.

## How to check timing conditions

Please recall:

- ▶ Latches, flip-flops, RAMs, etc. impose timing requirements that must not be violated, otherwise circuit behavior becomes unpredictable.

↪ A simulation model is in charge of two things:

1. Check whether input waveforms indeed conform with timing requirements (if any).
2. Evaluate input data to update outputs and/or state.

SystemVerilog supports this plan with

- ▶ the `specify` block and
- ▶ twelve specialized constructs among which `$setup`, `$hold`, `$width` and `$period`.

## Example: Setup and hold time checks

```
// simulation model of a single-edge-triggered flip-flop with hardcoded timing
module setff
  ( input logic Clk_CI, logic Rst_RBI, logic Dd_DI,
    output logic Qq_D0 );

  logic State_DP; // state variable

  specify
    $setup ( Dd_DI, posedge Clk_CI, 1.09ns ); // data evt, clock evt, min. sep.
    $hold ( posedge Clk_CI, Dd_DI, 0.60ns ); // clock evt, data evt, min. sep.
  endspecify

  always_ff @(posedge Clk_CI, negedge Rst_RBI)
    if (~Rst_RBI)
      State_DP <= 1'b0;
    else
      State_DP <= Dd_DI;

  assign #0.92ns Qq_D0 = State_DP;

endmodule
```

## 5th HDL capability: Facilities for model parametrization

 


Figure: ... plus parametrization with adjustable quantities and conditional items.

## Why it pays to keep HDL models parametrized

1. Imagine you have devised a synthesis model for a datapath unit
  - ▶ 16 data registers
  - ▶ 17 arithmetic and logic operations
  - ▶ 32 bit word width

## Why it pays to keep HDL models parametrized

1. Imagine you have devised a synthesis model for a datapath unit
  - ▶ 16 data registers
  - ▶ 17 arithmetic and logic operations
  - ▶ 32 bit word width
2. In addition, you need a similar unit for address computations
  - ▶ 5 data registers
  - ▶ 8 arithmetic and logic operations
  - ▶ 24 bit word width

## Why it pays to keep HDL models parametrized

1. Imagine you have devised a synthesis model for a datapath unit
  - ▶ 16 data registers
  - ▶ 17 arithmetic and logic operations
  - ▶ 32 bit word width
2. In addition, you need a similar unit for address computations
  - ▶ 5 data registers
  - ▶ 8 arithmetic and logic operations
  - ▶ 24 bit word width

Easy to derive model 2. by modifying the existing HDL code, **but**

- ▶ maintenance effort doubled
- ▶ what if you later needed a third and a fourth model?

### HDL requirement no.5

Means for accommodating distinct architecture choices and parameter settings within a single piece of code.

## Parameters

```
// w-input odd parity gate
module parityoddw
  #( parameter WIDTH,    // number of inputs
    parameter TCD = 0ns, // contamination delay with default value
    parameter TPD = 1.0ns ) // propagation delay with default value
  ( input logic [WIDTH-1:0] Inp_DI,
    output logic Oup_DO );
  ...
endmodule

.....
// module instantiation statement
parityoddw #( .WIDTH(NUMBITS), .TCD(0.05ns), .TPD(NUMBITS * 0.1ns) )
  u173 ( .Inp_DI(DataVec_D) , .Oup_DO(Parbit_D) );
.....
```

**Ports** carry time-varying information between modules.


**Parameters** serve to disseminate time-invariant details to modules (e.g. word widths, active-low/high signaling, timing quantities), they **do not have any direct hardware counterpart**.



 
## Conditional spawning of processes I

Consider a cellular automaton: Game of Life by John H. Conway (1970)

Show <http://www.bitstorm.org/gameoflife/>




2D array of identical cells

 

 
## Conditional spawning of processes I

Consider a cellular automaton: Game of Life by John H. Conway (1970)

Show <http://www.bitstorm.org/gameoflife/>



2D array of identical cells

 

### HDL requirement no.5'

Means for varying the number of processes (and of components too) as a function of parameter settings made **after the source code is frozen**.

## Conditional spawning of processes II

### The generate statement

- ▶ allows to decide on the number of concurrent processes immediately before simulation or synthesis begins with no changes to the basic code
- ▶ produces processes under control of constants and parameters
- ▶ comes in two flavors

`generate if`

to capture the conditional presence or absence of a process

`generate for`

to capture a number of replications of a process where the number is subject to change

## Example: Game of Life

```
.....  
// spawn a process for each cell in the array  
generate  
for (genvar ih = 0; ih<HEIGHT; ih++)  
  for (genvar iw = 0; iw<WIDTH; iw++)  
    always_ff @(posedge Clk_C) begin // sensitivity list  
      integer live_neighbors;  
      live_neighbors = live_neighbors_at(ih,iw);  
      if (State_DP[ih][iw]== 'b0 && live_neighbors==3)  
        State_DP[ih][iw] <= 'b1; // birth  
      else if (State_DP[ih][iw]== 'b1 && live_neighbors<=1)  
        State_DP[ih][iw] <= 'b0; // death from isolation  
      else if (State_DP[ih][iw]== 'b1 && live_neighbors>=4)  
        State_DP[ih][iw] <= 'b0; // death from overcrowding  
    end // always_ff  
endgenerate  
.....
```

## Multiple models for one circuit block

SystemVerilog allows multiple modules for the same circuit  
Why would you want that?

## Multiple models for one circuit block

SystemVerilog allows multiple modules for the same circuit

Why would you want that?

- ▶ Because over a design cycle the same functionality needs to be modeled at distinct levels of detail.
  1. Algorithmic model (purely behavioral)
  2. RTL model (for simulation and synthesis)
  3. Post synthesis gate-level netlist (timing estimated)
  4. Post layout gate-level netlist (timing back-annotated)
  
- ▶ To evaluate different circuit implementations for one block (in terms of  $A$ ,  $t_{lp}$ ,  $E$ , etc.).

## Conditional compilation of source code

With multiple modules for one subcircuit, there must be a way to indicate which one to use for simulation and synthesis  $\rightsquigarrow$  'ifdef statement.

```
// parametrized binary to Gray code converter
module binary2gray
  #( parameter ...) // parameters
  (.....); // inputs and outputs

  `ifdef usebehavioral
    // module body with behavioral model follows here
    .....
  `else
    // module body with structural model follows here
    .....
  `endif
endmodule
```

## Conditional compilation of source code

With multiple modules for one subcircuit, there must be a way to indicate which one to use for simulation and synthesis  $\rightsquigarrow$  'ifdef statement.

```
// parametrized binary to Gray code converter
module binary2gray
  #( parameter ...) // parameters
  (.....); // inputs and outputs

  `ifdef usebehavioral
    // module body with behavioral model follows here
    .....
  `else
    // module body with structural model follows here
    .....
  `endif
endmodule
```

### Warning

Warning: Do not give two modules with functionally distinct behaviors identical names as this is extremely confusing!



## Insight gained

SystemVerilog provides a range of constructs for writing parametrized circuit models:

- ▶ parameter quantities
- ▶ `generate...for` and `generate...if` statements
- ▶ `'define`, `'undef`, `'ifdef` and other compiler directives.

### SystemVerilog property

It is possible to establish a model without committing the code to any specific number of processes and/or instantiated components.

## Insight gained

SystemVerilog provides a range of constructs for writing parametrized circuit models:

- ▶ parameter quantities
- ▶ `generate...for` and `generate...if` statements
- ▶ `'define`, `'undef`, `'ifdef` and other compiler directives.


### SystemVerilog property

It is possible to establish a model without committing the code to any specific number of processes and/or instantiated components.

↪ A preparatory step must take place before simulation or synthesis can begin  $\mapsto$  elaboration and binding.

 
### Delay calculation from layout

- outside the scope of VHDL or SystemVerilog



 
### HDL simulation flow

- circuit models plus testbench
- full language supported


 
### RTL synthesis flow

- circuit models exclusively
- subset of language only



## What you ought to know about programming

Proven concepts from safe and modular programming include

- ▶ Structured flow control statements (no goto)
- ▶ Typing and type checking
- ▶ Data structures (enumerated types, arrays, records)
- ▶ Subprograms
- ▶ Packages (collections of type declarations and subprograms)
- ▶ Information hiding (declaration module vs. implementation module)

## What you ought to know about programming

Proven concepts from safe and modular programming include

- ▶ Structured flow control statements (no goto)
- ▶ Typing and type checking
- ▶ Data structures (enumerated types, arrays, records)
- ▶ Subprograms
- ▶ Packages (collections of type declarations and subprograms)
- ▶ Information hiding (declaration module vs. implementation module)

### HDL requirement no.6

Make those ideas available to HDL model developers too.

*No graphic illustration at this point.*

## Concepts borrowed from programming languages

- ▶ Structured flow control statements
  - ▶ `if ... else if ... else, case...endcase`
  - ▶ `for, while, repeat`
- △ Little type checking  $\mapsto$  almost anything compiles!
- ▶ Enumerated types (`enum`)
- ▶ Composite data types (`struct`)
- ▶ Subprograms (`function, task`)
- ▶ Packages (`package`)
- △ Limited information hiding, no separation into declaration and implementation module.

## Package

A package is a named collection of types and/or subprograms that is made visible by referring to it in an `import` clause. Example:

```
package calendar;
```

```
typedef enum {JANUARY, FEBRUARY, MARCH, APRIL, MAY, JUNE, JULY,  
             AUGUST, SEPTEMBER, OCTOBER, NOVEMBER, DECEMBER} month;  
typedef logic unsigned [4:0] day;
```

```
function month nextmonth (month given_month);  
    return given_month.next; // wraps around at the end  
endfunction
```

```
function day nextday (day given_day);  
    .....  
endfunction
```

```
endpackage: calendar
```

## System tasks I

System tasks are commands to the simulator and not for synthesis. Examples:

```
$display("Simulation ended after %4d checks and with %4d error(s).",  
        checkcnt, errorcnt);  
  
int simvectorfile = $fopen("../simvectors/moore6st_simvector.asc", "r");  
  
$fclose(simvectorfile);  
  
while( !$feof(simvectorfile)) begin  
    void'($fgets(readstr, simvectorfile));  
    fmatch = $sscanf(readstr, "%b %b %b",  
        StimuliRec.Clr_S, StimuliRec.Inp_D, ExpRespRec.Oup_D );  
    ...  
end  
  
$readmemh("../sim/vectors/stim.txt", stimuli);  
  
$error("Expected 'b%b does not match actual 'b%b", expresp, ActResp_D);  
  
assert (simvectorfile) else $fatal("Could not open simvector file.");
```



## System tasks II, incomplete overview

Command	Action
Formatted text output	
\$write	write line to standard output immediately with no newline character
\$display	write line to standard output immediately preceded by a newline character
\$strobe	<i>idem</i> at the end of current time slot, i.e. before advancing simulation time
\$monitor	<i>idem</i> when specified events occur
File operations	
\$fopen	open a file
\$fclose	close a file
\$fread	read from a file
\$fgets	read characters from a file and assembles them into a string
\$sscanf	parse formatted text from a string
\$feof	return a non-zero value when end of file found and 0 if not so
\$fwrite	same as \$write for writing to a file
Memory load and dump	
\$readmemb/h	load memory from a text file in binary/hex format
\$writememb/h	dump memory to a text file in binary/hex format
Simulation control	
\$stop	suspend simulation
\$finish	terminate simulation
Run time information with severity levels (standalone and for use in assertions)	
\$info	print argument to simulator window and continue
\$warning	print argument to simulator window, count as warning, and continue
\$error	print argument to simulator window, count as error, and continue
\$fatal	print argument to simulator window and terminate simulation
Random number generation (for use in stimuli preparation)	
\$random	return a random signed integer
\$urandom	return a random unsigned integer
Enquiries about the event queue (for use in properties and assertions)	
\$rose	return 1 iff argument has changed to 1
\$fell	return 1 iff argument has changed to 0
\$stable	return 1 iff argument had not changed value
\$past	return argument's value a specified number of clock cycles earlier

## Subject

# Circuit synthesis from HDL models

## HDL synthesis overview

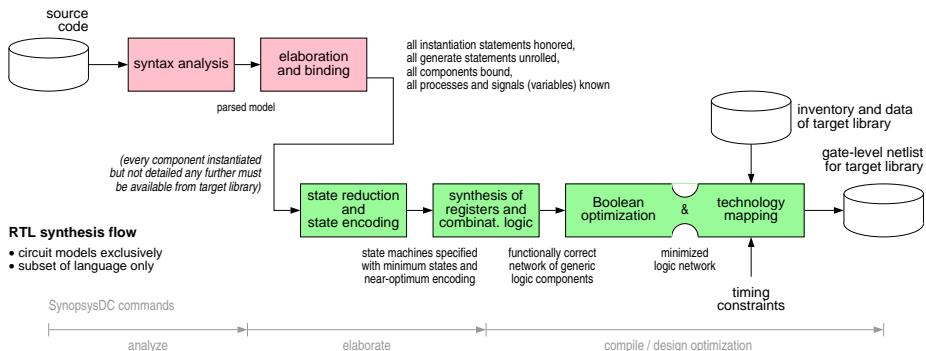


Figure: Major steps of automated RTL synthesis.

- Syntax analysis is different for VHDL and for SystemVerilog models. After that, the synthesis process becomes essentially the same.

## Synthesis subset

The predominant HDLs have not originally been intended for synthesis.

- ▶ While almost all **VHDL** simulators support the full IEEE 1076 standard, **only a subset of the legal language constructs is amenable to synthesis.**
- ▶ The same holds for **SystemVerilog** and the IEEE 1800 standard.

↪ Good HDL code is written such as to be portable across platforms and synthesis tools.

### Guiding principle

Limit yourself to safe, unambiguous, and universally accepted constructs!

## Synthesis subset

The predominant HDLs have not originally been intended for synthesis.

- ▶ While almost all **VHDL** simulators support the full IEEE 1076 standard, **only a subset of the legal language constructs is amenable to synthesis.**
- ▶ The same holds for **SystemVerilog** and the IEEE 1800 standard.

↪ Good HDL code is written such as to be portable across platforms and synthesis tools.

### Guiding principle

Limit yourself to safe, unambiguous, and universally accepted constructs!

- ▶ Apart from that, the impact of coding style on combinational random logic is fairly small (surprisingly perhaps as it is often overstated).

# Not all data types are amenable to synthesis

## VHDL

### Supported:

- + integer
- + boolean and bit
- + std\_logic and std\_ulogic
- + unsigned and signed
- + enumerated type
- + ufixed, sfixed and float
- + array and record of fixed size

## SystemVerilog

- + integer, shortint, int, longint
- + bit
- + logic and wire
- + byte
- + enumerated type
- + array and struct of fixed size

## Not all data types are amenable to synthesis

### VHDL

#### Supported:

- + integer
- + boolean and bit
- + std\_logic and std\_ulogic
- + unsigned and signed
- + enumerated type
- + ufixed, sfixed and float
- + array and record of fixed size

#### Not supported:

- real
- time
- character
  
- file

### SystemVerilog

- + integer, shortint, int, longint
- + bit
- + logic and wire
- + byte
- + enumerated type
  
- + array and struct of fixed size

- real
- time-related data types
- string, queue, and other dynamic data types
- file-related data types

## Hardware-compatible wake-up conditions

- ▶ While HDLs allow the modeling of arbitrary behavior (as long as it is causal, discrete in value, and discrete in time), automatic synthesis only supports synchronous clock-driven subcircuits and — at a higher level — conglomerates of such subcircuits.

### Observation

Any process that is supposed to model a piece of hardware must execute upon activation, return to the same instruction, and suspend there.



## Hardware-compatible wake-up conditions

- ▶ While HDLs allow the modeling of arbitrary behavior (as long as it is causal, discrete in value, and discrete in time), automatic synthesis only supports synchronous clock-driven subcircuits and — at a higher level — conglomerates of such subcircuits.

### Observation

Any process that is supposed to model a piece of hardware must execute upon activation, return to the same instruction, and suspend there.

### Why?

- ▶ Each `wait` or `similar` statement is allowed to carry its own condition as to when process execution is to resume.
  - ↳ Depending on the details, this may imply asynchronous behavior.
  - ↳ Extremely difficult, if not impossible, to implement in a physical circuit.

# Formalisms for describing finite state machines

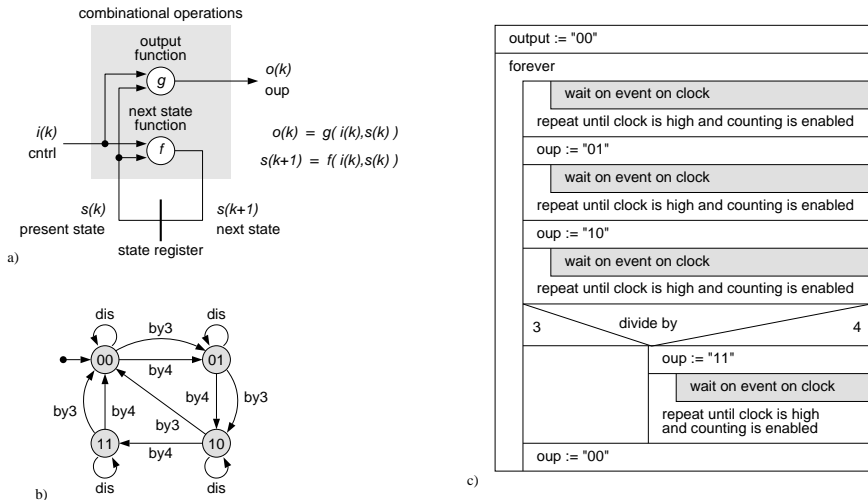


Figure: Data dependency graph (a), state chart (b), Nassi-Shneiderman diagram (c).

## Explicit versus implicit state models

modeling style	explicit state		implicit state
	computed state	enumerated state	
inspired from	data dependency graph or schematic diagram	state chart, state graph, or state table	Nassi-Shneiderman diagram
synchronization mechanism	sensitivity list or single wait statement (semantically equivalent)		multiple wait statements
state variable	declared explicitly as signal or variable and thus of user-defined type		hidden in pointer to current statement
states captured by	(subrange of) integer or vector of bits	enumerated type	multiple wait statements
state transitions captured by	arithmetic and/or logic operations	one-to-one translation from state table	control flow
output function captured by	arithmetic and/or logic operations	one-to-one translation from state table	assignment statements
immediate hardware equivalent	yes		depending on wait conditions
synchronous	yes		<i>idem</i>
synthesizable	yes		no


## What you ought to know from automata theory

**Mealy machine** output is a function of both state and input

$$o(k) = g(i(k), s(k))$$

$$s(k + 1) = f(i(k), s(k))$$

 ⇒ latency 0, through path, hazards likely.




**Moore machine** output is a function of state exclusively

$$o(k) = g(s(k))$$

$$s(k + 1) = f(i(k), s(k))$$

 ⇒ latency 1, no through path, hazards likely.




**Medvedev machine** subclass of Moore with identity as output function


$$o(k) = s(k)$$

$$s(k + 1) = f(i(k), s(k))$$

 ⇒ latency 1, no through path, hazard-free.


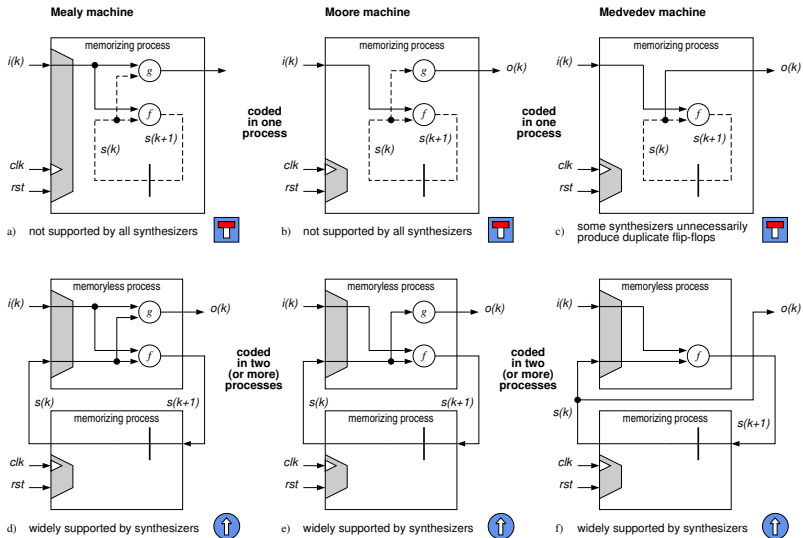
# How to capture a finite state machine in HDL



## How to write portable synthesis code (VHDL)

For the sake of code portability and trouble-free synthesis ...

### Good VHDL synthesis code shall

- ▶ model circuits at the RTL (register transfer level) throughout,
- ▶ collect combinational and sequential logic in separate processes,
- ▶ have all memorizing process statements conform with our skeleton,
- ▶ prefer concurrent, conditional and selected signal assignments for combinational logic,
- ▶ have all memoryless process statements coded according to the rules.

## How to write portable synthesis code (VHDL)

For the sake of code portability and trouble-free synthesis ...

### Good VHDL synthesis code shall

- ▶ model circuits at the RTL (register transfer level) throughout,
- ▶ collect combinational and sequential logic in separate processes,
- ▶ have all memorizing process statements conform with our skeleton,
- ▶ prefer concurrent, conditional and selected signal assignments for combinational logic,
- ▶ have all memoryless process statements coded according to the rules.

### Warning

The emergence of unplanned for latches or other bistables during synthesis always points to bad code.

## How to write portable synthesis code (SystemVerilog)

For the sake of code portability and trouble-free synthesis ...

### Good SystemVerilog synthesis code shall

- ▶ model circuits at the RTL (register transfer level) throughout,
- ▶ collect combinational and sequential logic in separate processes,
- ▶ use `always_ff` blocks exclusively for memorizing behavior (`always_latch` blocks for level-sensitive clocking),
- ▶ use continuous assigns or `always_comb` blocks for combinational logic.



## How to write portable synthesis code (SystemVerilog)

For the sake of code portability and trouble-free synthesis ...

### Good SystemVerilog synthesis code shall

- ▶ model circuits at the RTL (register transfer level) throughout,
- ▶ collect combinational and sequential logic in separate processes,
- ▶ use `always_ff` blocks exclusively for memorizing behavior (`always_latch` blocks for level-sensitive clocking),
- ▶ use continuous `assigns` or `always_comb` blocks for combinational logic.

### Warning

The emergence of unplanned for latches or other bistables during synthesis always points to bad code.

## Example: a Mealy-type state machine

*Refer to transparency mealy5st.vhd or .sv for code!*

Observe

1. The enumerated type for states.
2. The default state and output assignments.
3. The **when state if input then action** construct that assigns values to output and next state.
4. The tying up of parasitic states.

## Example: a Moore-type state machine

*Refer to transparency moore6st.vhd or .sv for code!*

### Observe

1. The combination of symbolic state identifiers and one-hot state codes imposed by the user.
2. The default state and output assignments (as before).
3. The placement of all output assignments outside the `if input then` clauses throughout.  
This makes the code describe a Moore machine!
4. Output assignments can be stated before or after each of the `if input then` clauses with no difference.
5. The tying up of parasitic states (as before).

## Example: a Medvedev-type state machine

*Refer to transparencies `graycnt.vhd` and `grayconv.vhd` or `.sv` for code!*

### Observe

1. The simplicity and elegance of the combinational process.
2. The usage of two functions `bintogray` and `graytobin` for code conversion described in a user-defined package `grayconv.vhd`.
3. The clause `use work.grayconv.all` that makes that package available.

## More on good FSM coding practices

### Recommendation

- ▶ Try to decompose large FSMs into a bunch of smaller ones that cooperate.
- ▶ Adhere to hierarchical and modular design.
- ▶ Consider using counters instead of long state chains.

### Recommendation

The various processes that make up for an FSMs are best included in the same architecture body as the datapath they command.

Shutting the FSM into an entity of its own just inflates the code and the effort for coding and maintenance.

## Synthesis of ROMs

Innocent approach: Declare a storage array as if the code were intended for simulation and assume the synthesizer will take care of all the rest.

Example: 4bit-binary to seven-segment display decoder.

```
-- unsupported VHDL coding style
.....
-- address of array must be of type integer or natural
p_memless : process (Binary4Code_D)
    variable address : natural range 0 to 15;
    type array16by7 is array(0 to 15) of std_logic_vector(1 to 7)
    constant SEGMENT_LOOKUP_TABLE : array16by7 := -- segments ordered a...g
        ("1111110","0110000","1101101","1111001", -- digits 0,1,2,3,
         "0110011","1011011","0011111","1110000", --         4,5,6,7,
         "1111111","1110011","1110111","0011111", --         8,9,A,b,
         "1001110","0111101","1001111","1000111"); --         C,d,E,F;

begin
    -- use binary input as index, look up in table, and assign to segment output
    address := to_integer(unsigned(Binary4Code_D));
    Segment7Code_D <= SEGMENT_LOOKUP_TABLE(address);
end process p_memless;
.....
```

## Synthesis of RAMs I

Innocent approach: Declare a storage array as if the code were intended for simulation and assume the synthesizer will take care of all the rest.

Example: 64 byte read-write memory. – unsupported VHDL coding style

```
.....  
    type array64by8 is array(0 to 63) of std_logic_vector(7 downto 0);  
    signal Storage_D : array64by8;  
.....
```

- ▶ Will not synthesize into a RAM because the behavior so defined is a far cry from actual RAM macrocells and their interfaces. Automated synthesis would hardly churn out a safe and synchronous gate-level circuit either.

## Synthesis of RAMs II

Second attempt: Instantiate RAM, state macrocell generator to be used, pass on all further specifications in a generic map.

```
-- unsupported VHDL coding style
.....
u39: cmosram01
  generic map ( NUMBER_OF_WORDS => 64, WORD_WIDTH => 8,
                DATA_INPUT_OUTPUT_SEPARATE => false )
  port map ( CLK => Clk_C, WRENA => RamWrite_S,
             ADDR => RamAddress_D, DATIO => RamData_D );
.....
```

- ▶ Realistic, but not currently feasible due to the lack of standardization and the absence of interfaces between VHDL synthesis and proprietary macrocell generators.



## Synthesis of RAMs III (VHDL)

Final attempt: instantiate RAM macrocell like any other component.

```
-- supported VHDL coding style
.....
u39: myram64by8
    port map ( CLK => Clk_C, WRENA => RamWrite_S,
              ADDR => RamAddress_D, DATIO => RamData_D );
.....
```

### Observation

The necessary design views of a macrocell (simulation model, schematic icon, detailed layout, etc.) must be obtained from outside the VHDL environment.

The chip designer must either

- gain access to the process-specific macrocell generator software or
- commission the silicon foundry do so for him.

## Synthesis of RAMs III (SystemVerilog)

Final attempt: instantiate RAM macrocell like any other component.

```
// supported SystemVerilog coding style
.....
myram64by8 u39 ( .CLK(Clk_C), .WRENA(RamWrite_S),
                .ADDR(RamAddress_D), .DATIO(RamData_D) );
.....
```

### Observation

The necessary design views of a macrocell (simulation model, schematic icon, detailed layout, etc.) must be obtained from outside the SystemVerilog environment.

The chip designer must either

- gain access to the process-specific macrocell generator software or
- commission the silicon foundry do so for him.

## Synthesis of RAMs and ROMs

Look up table (LUT) (memoryless)		
desired hardware organization	random logic	ROM (tiled layout)
function must be modeled	as an array-type constant or with logic equations	by instantiating a ROM macrocell as a component
Data storage array (memorizing)		
desired hardware organization	register file built from flip-flops or latches	RAM (tiled layout)
function must be modeled	as an array of (clocked) storage registers	by instantiating a RAM macrocell as a component
Common characteristics of implemented circuit		
efficient when data quantity is	small	large
techn.-specific softw. required	no	macrocell generator
code amenable to retargeting	yes	manual rework needed
pre-synthesis simulation from	RTL source code	extra behavioral model
post-synthesis simulation from	gate-level model	<i>idem</i>

## Insight gained

A storage array can be implemented

- as on-chip macrocell,
- as off-chip part,
- as a RAM,
- assembled from flip-flops or
- from latches.

Deciding among those options has far-reaching consequences for circuit performance, system architecture, and design effort.

### Conclusion

Spontaneous incorporation of macrocells is neither a practical nor really a desirable proposition for RTL synthesis because it would deprive designers of control over a circuit's architecture.

## What is an “optimal” circuit?

- ▶ Meets all user-defined performance targets at the lowest hardware costs.

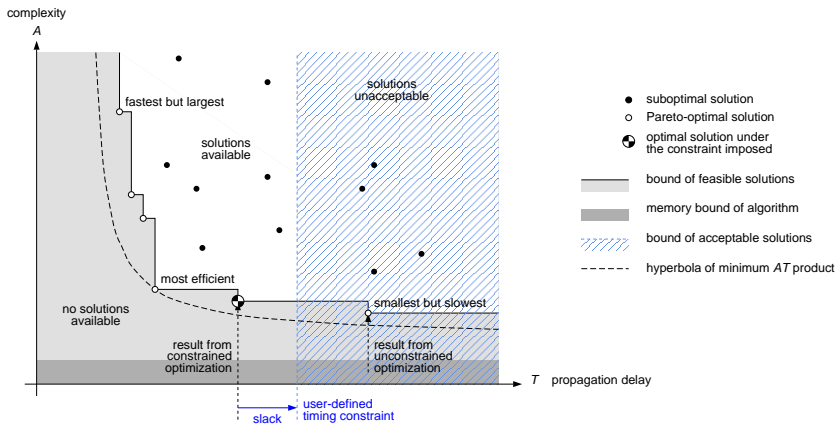


Figure: Trade-offs between size and performance for a hypothetical circuit.

## Timing quantities related to synthesis

**Timing constraint** User-defined bound (upper or lower) for a timing quantity (propagation delay, contamination delay, clock period, etc.) that the final circuit must meet.

**Slack** Difference between target specified and actual circuit delay, e.g.

$$t_{sl} = t_{lp\ max} - t_{lp} \text{ (combinational ckt) or}$$
$$t_{sl} = T_{clk} - t_{ss} \text{ (sequential ckt).}$$

## Timing quantities related to synthesis

**Timing constraint** User-defined bound (upper or lower) for a timing quantity (propagation delay, contamination delay, clock period, etc.) that the final circuit must meet.

**Slack** Difference between target specified and actual circuit delay, e.g.  
 $t_{sl} = t_{lp\ max} - t_{lp}$  (combinational ckt) or  
 $t_{sl} = T_{clk} - t_{ss}$  (sequential ckt).

**Negative slack** indicates synthesis has failed to meet timing target  $\rightsquigarrow$

1. Try varying synthesizer directives.
2. Rework RTL synthesis code.
3. Rework circuit architecture.

## Timing constraints are not part of the HDL standards ...

- ▶ All timing-related constructs get ignored during synthesis, e.g.
  - ▶ ... after tpd (VHDL)
  - ▶ wait for 3.9 ns *idem*
  - ▶ ... #3.9ns ... (SystemVerilog)

These serve to model the behavior of existing circuits,  
not to impose target requirements for the synthesis process.



## Timing constraints are not part of the HDL standards ...

- ▶ All timing-related constructs get ignored during synthesis, e.g.
  - ▶ ... after tpd (VHDL)
  - ▶ wait for 3.9 ns *idem*
  - ▶ ... #3.9ns ... (SystemVerilog)

These serve to model the behavior of existing circuits,  
not to impose target requirements for the synthesis process.

- ▶ Timing **constraints** that could guide synthesis and optimization  
have never been adopted in the IEEE 1076 and 1800 standards.

Unsupported constructs:

**VHDL:** `Oup_D <= Aa_D + Bb_D with_delay_no_more_than 1.7 ns;`

**SystemVerilog:** `assign #max#1.7ns Oup_D = Aa_D + Bb_D;`

## ... but must be expressed with scripting languages instead

- ▶ The HDL code is complemented with user-defined timing constraints along with other synthesis control statements.
- ▶ Proprietary language extensions or scripting languages such as Tcl must be used.

Tcl syntax examples for timing constraints:

```
create_clock -period 15 [get_ports Clk_CI]  
set_input_delay -max 6 -clock Clk_CI [get_ports Inp_DI]
```

## ... but must be expressed with scripting languages instead

- ▶ The HDL code is complemented with user-defined timing constraints along with other synthesis control statements.
- ▶ Proprietary language extensions or scripting languages such as Tcl must be used.

Tcl syntax examples for timing constraints:


```
create_clock -period 15 [get_ports Clk_CI]
set_input_delay -max 6 -clock Clk_CI [get_ports Inp_DI]
```

- ▶ Tcl requires time spans to be expressed as multiples of a predefined time unit, 1 ns in this example.
- ▶ The same timing constraints are to be reused later during design verification.

*For your first encounter with RTL synthesis, you may prefer to skip further details and come back later.*
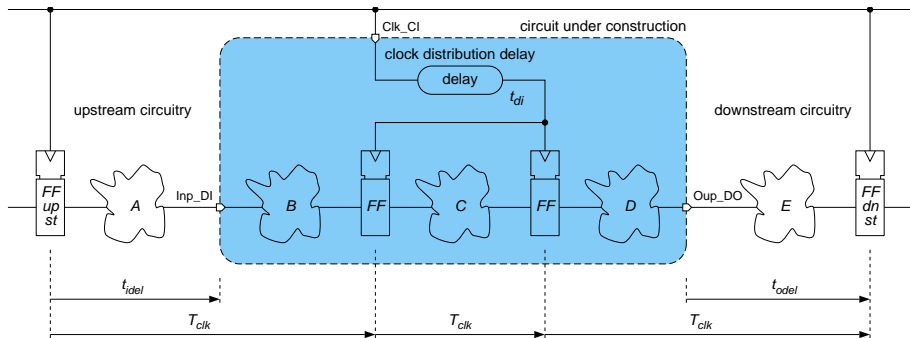
## How to formulate timing constraints I

- An upper bound for the delay from one register to the next gets imposed by  $T_{clk}$   $\rightsquigarrow$  Indicating a clock period is mandatory and straightforward.



a) `create_clock -period  $T_{clk}$  [get_ports Clk_CI]`

**Figure:** Most synthesis tools accept timing constraints in terms of  $T_{clk}$ ,  $t_{idel}$  and  $t_{odel}$ .

## How to formulate timing constraints II

- ▶ Constraining input- and output paths is more tricky because it is possible to look at input/output timing from two different perspectives:
  - “Egocentric” view indicates how much time is available to the circuit under construction.
  - “Altruistic” view quantifies the amount of time that must be set aside for the surrounding circuitry.

## How to formulate timing constraints II

- ▶ Constraining input- and output paths is more tricky because it is possible to look at input/output timing from two different perspectives:
  - “Egocentric” view indicates how much time is available to the circuit under construction.
  - “Altruistic” view quantifies the amount of time that must be set aside for the surrounding circuitry.


### Note


Most EDA tools adopt the “altruistic” view mainly because target clock can be altered without having to numerically readjust all I/O timing constraints.

### Caution

Do not get confused by inexpressive or ill-defined names!


## How to formulate input timing constraints

 data-valid window of upstream circuitry during which circuit under construction must catch data at its input

 time span left for input circuit under construction to settle (propagation through input logic plus register set-up)

③ data-valid window begins

② data-valid window ends

 

```
set_input_delay  $t_{idel}$  -clock Clk_CI [get_ports Inp_DI]
set_input_delay -max  $t_{idel\ max}$  -clock Clk_CI [get_ports Inp_DI]
b) set_input_delay -min  $t_{idel\ min}$  -clock Clk_CI [get_ports Inp_DI]
```


 
 


Figure: Input constraints  $t_{idel\ max}$  and  $t_{idel\ min}$  as understood by synthesis tools .
 
## How to formulate output timing constraints

- data-call window of downstream circuitry during which circuit under construction must provide valid output data
- time span left for output circuit under construction to settle (propagation delay through register and output logic)

- ④ data-call window begins
- ① data-call window ends



```
set_output_delay t_odel -clock Clk_CI [get_ports Oup_DO]
set_output_delay -max t_odel_max -clock Clk_CI [get_ports Oup_DO]
set_output_delay -min t_odel_min -clock Clk_CI [get_ports Oup_DO]
```

**Figure:** Output constraints  $t_{odel\ max}$  and  $t_{odel\ min}$  as understood by synthesis tools.



## Cross reference for I/O timing constraints

Event	Symbol	Quantity (altruistic view)	Synopsys term
relating to the interface with the upstream circuitry			
(3) data-valid window begins	$t_{su\ inp}$ $\leq T_{clk} - t_{pd\ upst}$	setup time of circuit under construction	
	$t_{pd\ upst} = t_{idel\ max}$	clock-to-output prop. delay of upstream circuitry	maximum input delay
(2) data-valid window ends	$t_{ho\ inp}$ $\leq t_{cd\ upst}$	hold time of circuit under construction	
	$t_{cd\ upst} = t_{idel\ min}$	clock-to-output cont. delay of upstream circuitry	minimum input delay
relating to the interface with the downstream circuitry			
(4) data-call window begins	$t_{pd\ oup}$ $\leq T_{clk} - t_{su\ dnst}$	clock-to-output prop. delay of circuit under construction	
	$t_{su\ dnst} = t_{odel\ max}$	setup time of downstream circuitry	maximum output delay
(1) data-call window ends	$t_{cd\ oup}$ $\geq t_{ho\ dnst}$	clock-to-output cont. delay of circuit under construction	
	$t_{ho\ dnst} = -t_{odel\ min}$	hold time of downstream circuitry	<u>minus</u> minimum output delay

## Dealing with special subcircuits I

- ▶ Adders, multipliers, and other (high-performance) arithmetic units.
- ▶ Padframe (core ↔ pads interconnect).
- ▶ Clock distribution network (typically buffered trees).
- ▶ Clock gating circuitry (for low power).
- ▶ Data synchronizers (at clock boundaries).
- ▶ Scan paths (auxiliary structures for circuit testing).

What do all these subcircuits have in common?

## Dealing with special subcircuits I

- ▶ Adders, multipliers, and other (high-performance) arithmetic units.
- ▶ Padframe (core ↔ pads interconnect).
- ▶ Clock distribution network (typically buffered trees).
- ▶ Clock gating circuitry (for low power).
- ▶ Data synchronizers (at clock boundaries).
- ▶ Scan paths (auxiliary structures for circuit testing).

What do all these subcircuits have in common?

Each **must conform to a precisely defined pattern at the gate level**, mimicking the desired behavior alone does not suffice!

Limitation: Boolean optimization tools are not designed to handle such “non-logic” circuits.

## Dealing with special subcircuits II

- ▶ What are the options when tight control is sought?  
(over a subcircuit's gate-level construction)
  - ▶ Use dedicated design automation tools,<sup>1</sup>
  - ▶ fall back to schematic entry, or
  - ▶ write a **parametrized structural VHDL** model.
- ▶ As for arithmetic circuits, take advantage of proven synthesis models (e.g. Synopsys DesignWare).

### Hint

Do not reoptimize subcircuits so obtained as critical properties may deteriorate. Use “Don't touch” synthesis directives to prevent logic optimization from altering structurally critical subcircuits.

---

<sup>1</sup>Example: Clock tree generation is postponed to the physical design phase and handled by specialized EDA software there.

## Why write RTL synthesis models?

- ▶ VHDL is perfectly suitable for coding a data processing algorithm.
- ▶ Yet, do not expect an EDA tool to accept a purely behavioral model and to turn that into a circuit design of acceptable performance, size, and energy efficiency.

### Conclusion

The fun and the burden of architecture design rests with the hardware developer.

# How to write an RTL model step by step I



## VHDL construct (SystemVerilog construct)

1. Draw a fairly detailed **block diagram** of the architecture devised.
2. Check where you can take advantage of DesignWare models.
3. Organize the design such as to confine **critical propagation paths** to within **design entities (modules)**.
4. Identify macrocells such as RAMs and ROMs and prepare for generating the necessary design views outside the HDL environment.
5. Identify **all** registers and loosely collect the combinational operations in between into clouds.
6. For each cloud, specify the operations in mathematical terms.
7. Specify what is to happen during each clock cycle (**schedule**).

## How to write an RTL model step by step II


8. For each FSM, find out what type is most appropriate.
9. Capture each register in a **memoryizing process statement** (**always\_ff** block).
10. For each cloud, decide how many processes to use.  
Prefer **concurrent signal assignments** (**continuous assignments**) for simpler operations.
11. Declare the data items that run back and forth between the various processes as **signals** (**variables**) and decide on appropriate types.
12. Only **now translate** your draft into actual HDL code.
  - Adhere to the code patterns established in this text.
  - Watch out for special signals such as clock, reset, enable etc.
  - The schedule defines the various subfunctions in full detail.
  - Fill in don't care entries wherever possible.
  - Follow the recommendations in this text.
  
# Translating an RTL diagram into HDL code (VHDL)




 
## Translating an RTL diagram into HDL code (SystemVerilog)



register



`always_ff`  
`block`

combinational  
 subfunction



`continuous assignment`  
 or  
`always_comb` block

macrocell



`module`  
`instantiation`  
`statement`

## Hardware model writing versus programming

- ▶ Writing code for HDL synthesis is not the same as writing software for a program-controlled computer!
- ▶ Always think in terms of circuit hierarchies and simultaneous activities (concurrent processes) rather than in terms of instruction sequences!

## Hardware model writing versus programming

- ▶ Writing code for HDL synthesis is not the same as writing software for a program-controlled computer!
- ▶ Always think in terms of circuit hierarchies and simultaneous activities (concurrent processes) rather than in terms of instruction sequences!

### Golden rule

- ▶ Establish a block diagram of your architecture first, then code what you see!

## Hardware model writing versus programming

- ▶ Writing code for HDL synthesis is not the same as writing software for a program-controlled computer!
- ▶ Always think in terms of circuit hierarchies and simultaneous activities (concurrent processes) rather than in terms of instruction sequences!

### Golden rule

- ▶ Establish a block diagram of your architecture first, then code what you see!

### Caution

Do not ignore warnings and error messages from the synthesizer unless you understand what they mean!


## Conclusions I

VHDL and SystemVerilog universally adopted due to paying benefits:

- + Top-down design methodology using a single standard language.
- + RTL synthesis does away with all lower-level schematic drawings in a typical VLSI design hierarchy.  $\mapsto$  Saves time and effort.
- + HDLs enable sharing, reusing and porting of subfunctions and -circuits in a parametrized form.  $\mapsto$  More useful than schematics.
- + Automatic technology mapping postpones the commitment to a specific fabrication process until late in the design cycle.
- + Allows for retargetting between field-programmable logic and ASICs.
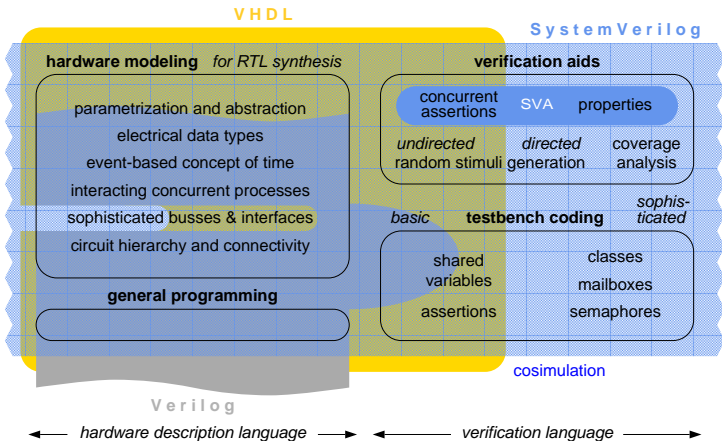
## Conclusions II

+ VHDL and SystemVerilog support the coding of simulation testbenches.



More on this in chapter 5 "Functional Verification".

## Conclusions III

The limitations are relatively minor:

- Learning to master VHDL or SystemVerilog may be daunting.
- ~ Only a subset is amenable to synthesis.  $\mapsto$  No serious problem.
- Lack of agreement between tool vendors on
  - ▶ what constructs the synthesis subset ought to include,
  - ▶ how to capture timing constraints and synthesis directives, and
  - ▶ when to support new constructs introduced with past std revisions.
- A gap remains between system design and actual hardware design. Manual translation from a behavioral model to RTL synthesis code is inefficient and prone to errors. Will high-level synthesis help?

## Conclusions III

The limitations are relatively minor:

- Learning to master VHDL or SystemVerilog may be daunting.
- ~ Only a subset is amenable to synthesis.  $\mapsto$  No serious problem.
- Lack of agreement between tool vendors on
  - ▶ what constructs the synthesis subset ought to include,
  - ▶ how to capture timing constraints and synthesis directives, and
  - ▶ when to support new constructs introduced with past std revisions.
- A gap remains between system design and actual hardware design. Manual translation from a behavioral model to RTL synthesis code is inefficient and prone to errors. Will high-level synthesis help?

### Concluding remark

HDL synthesis does not do away with architecture design!