

Lecture 6: Logical Effort


Outline

- Logical Effort
- Delay in a Logic Gate
- Multistage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary

Introduction

- ❑ Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?

 - ❑ Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries



Example


- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- ❑ Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors

- ❑ Ben needs to decide:

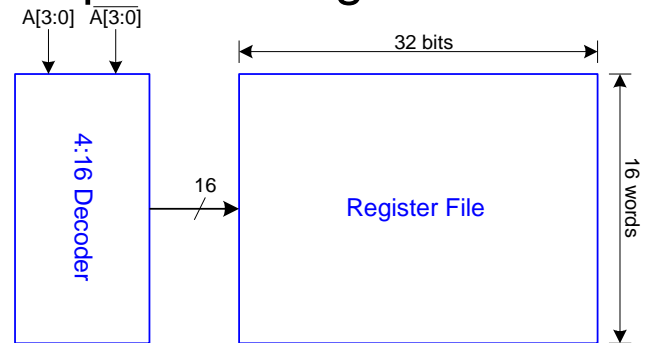- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?




Delay in a Logic Gate

- ❑ Express delays in process-independent unit $d = \frac{d_{abs}}{\tau}$
 - ❑ Delay has two components: $d = f + p$
 - ❑ f : effort delay = gh (a.k.a. stage effort)
 - Again has two components
 - ❑ g : logical effort
 - Measures relative ability of gate to deliver current
 - $g \equiv 1$ for inverter
 - ❑ h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
 - ❑ p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance
- $\tau = 3RC$
 $\approx 3 \text{ ps in } 65 \text{ nm process}$
 $60 \text{ ps in } 0.6 \mu\text{m process}$


Delay Plots

$$d = f + p$$
$$= gh + p$$

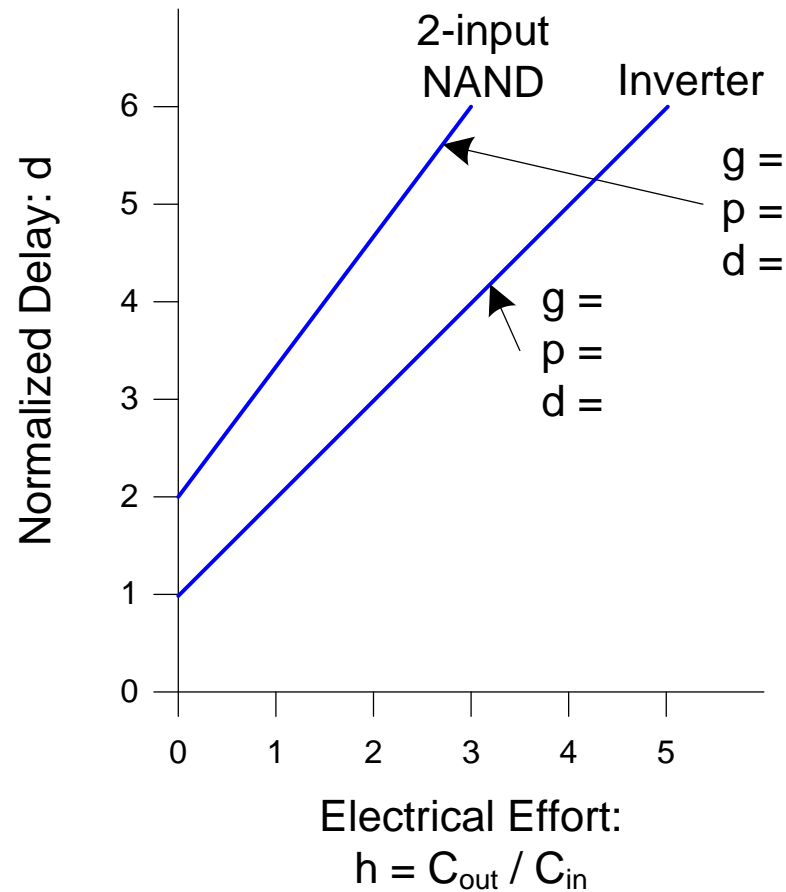


Computing Logical Effort

 
- ❑ DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- ❑ Measure from delay vs. fanout plots
- ❑ Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$


Catalog of Gates

□ Logical effort of common gates


Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

Computing Parasitic Delay

 
- ❑ DEF: The parasitic delay of a gate is the delay of the gate when it drives zero load.
- ❑ It can be estimated with Elmore RC delay models.
- ❑ An estimate is to count only diffusion capacitance on the output node (ignore internal node delays)



$$C_{out} = 3$$
$$p = 3/3$$

 

$$C_{out} = 6$$
$$p = 6/3$$

 

$$C_{out} = 6$$
$$p = 6/3$$

Catalog of Gates

- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	


Parasitic Delay Note

- ❑ This method of estimating parasitic delay is obviously crude.
- ❑ More refined estimates use the Elmore delay counting internal parasitics
- ❑ However, optimizing transistor size in a particular circuit is weakly dependent on the parasitic delay
- ❑ it is important to realize that parasitic delay grows more than linearly with the number of inputs in a real NAND or NOR circuit

 Example: NAND Gate

- n -input NAND gate parasitic delay


$$t_{pd} = R(3nC) + \sum_{i=1}^{n-1} \left(\frac{iR}{n}\right)(nC) = \left(\frac{n^2}{2} + \frac{5}{2}n\right)RC \quad (4.23)$$



- In practice, it is rarely advisable to construct a gate with more than four to five series transistors.

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$


Parasitic Delay: $p =$

Stage Delay: $d =$

Frequency: $f_{osc} =$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

Drive

- ❑ A standard cell library contains multiple sizes of each common gate.
- ❑ The sizes are typically labeled with their drive.
- ❑ For example, a unit inverter may be called `inv_1x`. An inverter of eight times unit size is called `inv_8x`. A 2-input NAND that delivers the same current as the inverter is called `nand2_1x`.
- ❑ If we redefine a unit inverter to have one unit of input capacitance, then the drive of an arbitrary gate is:

$$x = \frac{C_{in}}{g} \quad \rightarrow \quad d = \frac{C_{out}}{x} + p$$

Limitations to the Linear Delay Model

- ❑ Input and Output Slopes: inputs do not change abruptly
- ❑ Input arrival times: not all inputs arrive at the same instance
- ❑ Velocity saturation: Series transistors see less velocity saturation and hence have lower resistance than we estimate
- ❑ Voltage Dependence: delay will vary if the supply or threshold voltage is changed
- ❑ Gate-Source Capacitance: is not zero for internal nodes
- ❑ Bootstrapping: gate-drain capacitances couples input/output which increases the delay.


Multistage Logic Networks

- ❑ Logical effort generalizes to multistage networks

- ❑ *Path Logical Effort* $G = \prod g_i$

- ❑ *Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 - ❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$



Multistage Logic Networks

- ❑ Logical effort generalizes to multistage networks

- ❑ *Path Logical Effort* $G = \prod g_i$

- ❑ *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$

- ❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$

- ❑ Can we write $F = GH$?

Paths that Branch

❑ No! Consider paths that branch:

G =


H =

GH =

h_1 =

h_2 =

F =

 

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

Multistage Delays

- ❑ Path Effort Delay $D_F = \sum f_i$
- ❑ Path Parasitic Delay $P = \sum p_i$
- ❑ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is



- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



Example: 3-stage path

 

Logical Effort $G =$

Electrical Effort $H =$

Branching Effort $B =$

Path Effort $F =$

Best Stage Effort $\hat{f} =$

Parasitic Delay $P =$


Delay $D =$

Example: 3-stage path

- Work backward for sizes

$y =$


$x =$

 

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter


D =

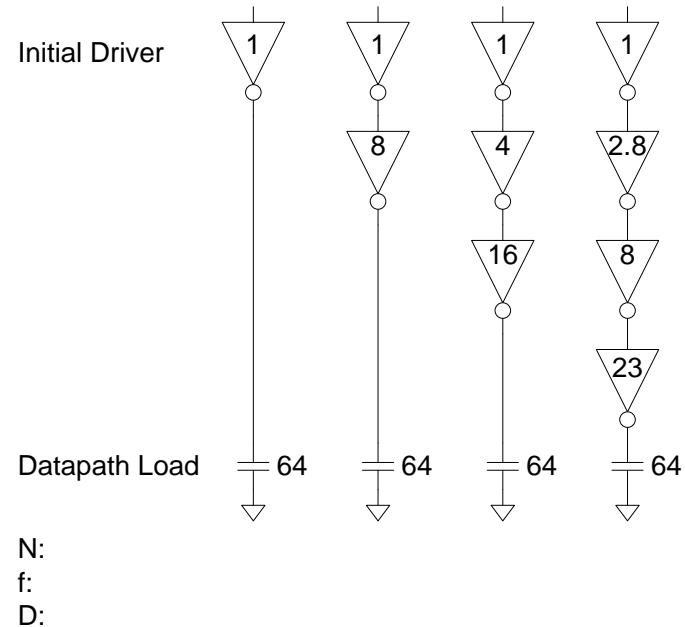

Derivation

- Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

Best Stage Effort

- ❑ $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- ❑ Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- ❑ For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

 - How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

Example, Revisited


- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- ❑ Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors

- ❑ Ben needs to decide:

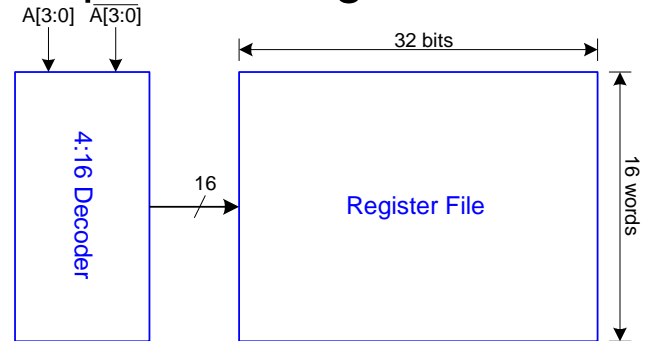- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort: $H =$

Branching Effort: $B =$

- ❑ If we neglect logical effort (assume $G = 1$)

Path Effort: $F =$

Number of Stages: $N =$

- ❑ Try a -stage design

Gate Sizes & Delay

Logical Effort: $G =$


Path Effort: $F =$

Stage Effort: $\hat{f} =$

Path Delay: $D =$

Gate sizes: $z =$

$y =$

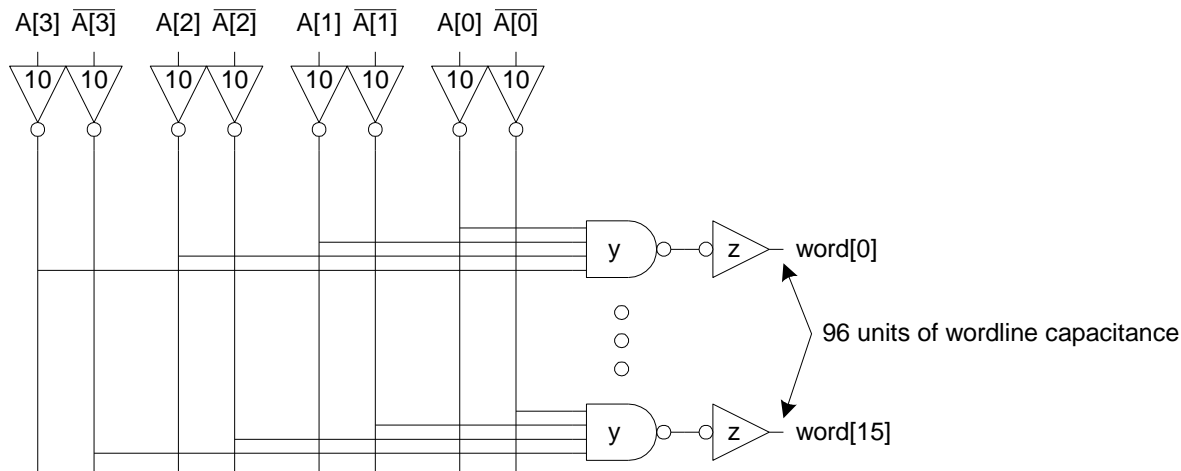

Comparison

- ❑ Compare many alternatives with a spreadsheet
- ❑ $D = N(76.8 G)^{1/N} + P$

Design	N	G	P	D
NOR4	1	3	4	234
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Limits of Logical Effort

- ❑ Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- ❑ Simplistic delay model
 - Neglects input rise time effects
- ❑ Interconnect
 - Iteration required in designs with wire
- ❑ Maximum speed only
 - Not minimum area/power for constrained delay


Iterative Solutions for Sizing

❑ Not all logical effort problems can be solved using the systematic steps.

❑ Example:

For the following circuit, write an expression for the arrival time of the output as a function of the gate drives.

 Determine the sizes to achieve minimum delay.



Solution

- The input capacitance of a gate with logical effort g and drive x is $C_{in} = gx$

$$d_1 = 1 + \frac{4}{3}x_2 + \frac{5}{3}x_3$$

$$d_2 = 2 + \frac{7}{3} \frac{x_4}{x_2}$$

$$d_3 = 2 + \frac{7}{3} \frac{x_4}{x_3}$$

$$d_4 = 3 + \frac{x_5}{x_4} + \frac{10}{x_4}$$

$$d_5 = 1 + \frac{12}{x_5}$$

- The arrival time can be expressed as:

$$a_1 = d_1$$

$$a_2 = a_1 + d_2$$

$$a_3 = a_1 + d_3$$

$$a_4 = \max\{a_2, a_3\} + d_4$$

$$a_5 = a_4 + d_5 = d_1 + \max\{d_2, d_3\} + d_4 + d_5$$

- Use an automatic solver to choose the drives to minimize the latest arrival time

Stage (i)	x_i	f_i	c_{in}	d_i	a_i
1: INV	1	4.85	1	5.85	5.85
2: NAND2	1.62	4.85	2.16	6.85	12.70
3: NOR2	1.62	4.85	2.70	6.85	12.70
4: NOR3	3.37	4.85	7.86	7.85	20.55
5: INV	6.35	1.89	6.35	2.89	23.44

Example Observations

- ❑ In paths that branch, each fork should contribute equal delay.
- ❑ If one fork were faster than the other, it could be downsized to reduce the capacitance it presents to the stage before the branch.
- ❑ The stage efforts, f , are equal for each gate in paths with no fixed capacitive loads, but may change after a load.
- ❑ To minimize delay, upsize gates on nodes with large fixed capacitances to reduce the effort borne by the gate, while only slightly increasing the effort borne by the predecessor.

Summary

- ❑ Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- ❑ Provides language for discussing fast circuits
 - But requires practice to master