

Lecture 7: Power

Outline

- Power and Energy
- Dynamic Power
- Static Power

Power and Energy

- ❑ Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip.
- ❑ Instantaneous Power: $P(t) =$
- ❑ Energy: $E =$
- ❑ Average Power: $P_{\text{avg}} =$

Power in Circuit Elements


$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$



$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$


 
$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t) dt = \int_0^{\infty} C \frac{dV}{dt} V(t) dt \\ &= C \int_0^{V_C} V(t) dV = \frac{1}{2} CV_C^2 \end{aligned}$$



Charging a Capacitor

- When the gate output rises
 - Energy stored in capacitor is


$$E_C = \frac{1}{2} C_L V_{DD}^2$$

- But energy drawn from the supply is

$$\begin{aligned} E_{V_{DD}} &= \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2 \end{aligned}$$


- Half the energy from V_{DD} is dissipated in the pMOS transistor as heat, other half stored in capacitor

 - When the gate output falls
 - Energy in capacitor is dumped to GND
 - Dissipated as heat in the nMOS transistor




Switching Waveforms

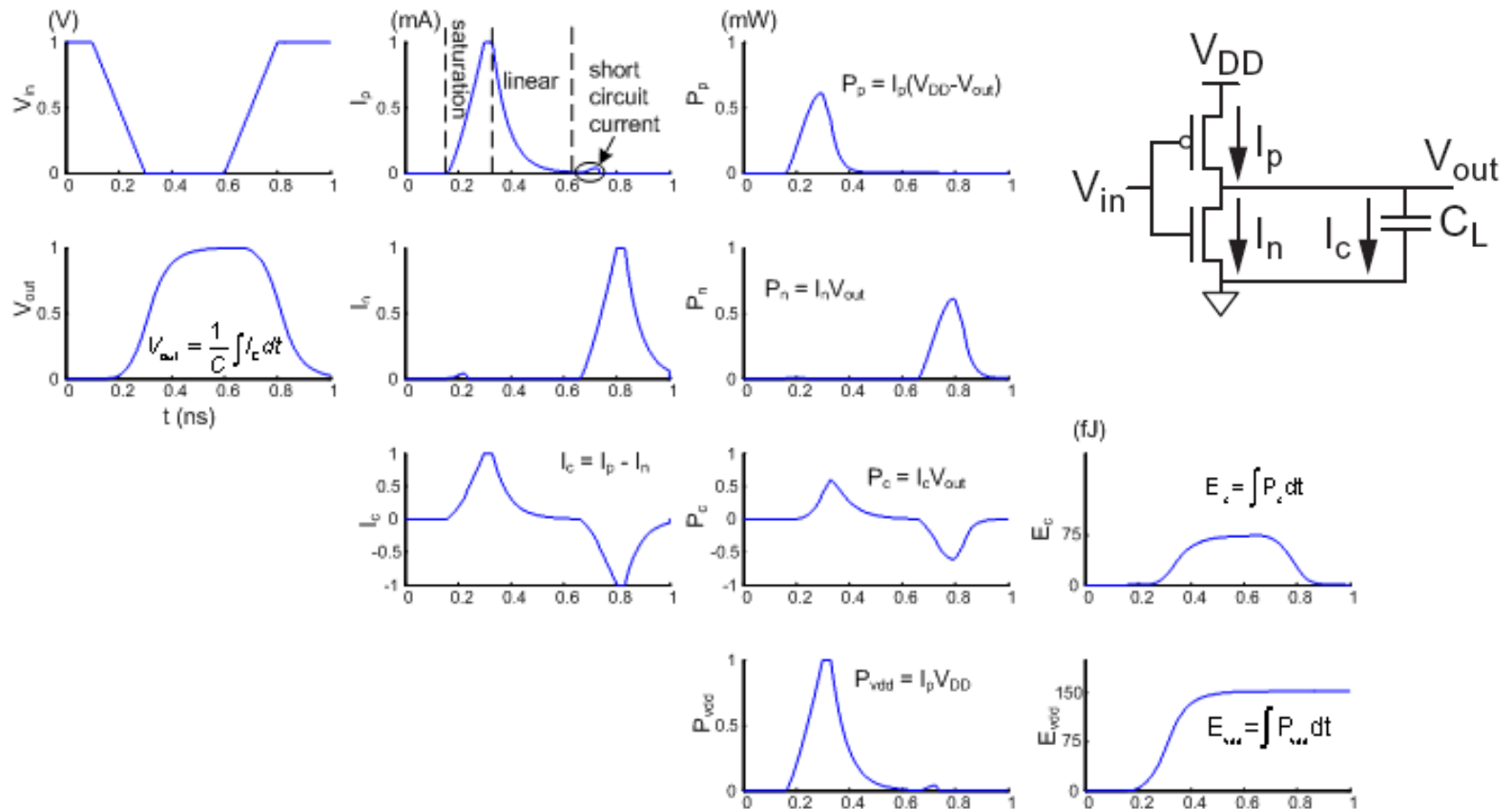□ Example: $V_{DD} = 1.0 \text{ V}$, $C_L = 150 \text{ fF}$, $f = 1 \text{ GHz}$



Switching Power
 
$$\begin{aligned} P_{\text{switching}} &= \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt \\ &= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt \\ &= \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}] \\ &= C V_{DD}^2 f_{\text{sw}} \end{aligned}$$



Activity Factor

- ❑ Suppose the system clock frequency = f
- ❑ Let $f_{sw} = \alpha f$, where α = activity factor
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = 1/2$

- ❑ Dynamic power:

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

Short Circuit Current

- ❑ When transistors switch, both nMOS and pMOS networks may be momentarily ON at once
- ❑ Leads to a blip of “short circuit” current.
- ❑ $< 10\%$ of dynamic power if rise/fall times are comparable for input and output
- ❑ We will generally ignore this component

Power Dissipation Sources

- ❑ $P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$
- ❑ Dynamic power: $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$
 - Switching load capacitances
 - Short-circuit current
- ❑ Static power: $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$
 - Subthreshold leakage
 - Gate leakage
 - Junction leakage
 - Contention current

Dynamic Power

- ❑ Consists of mainly switching power, short circuit power is neglected.
- ❑ To calculate dynamic power given V_{DD} and f , consider the capacitance of each node of the circuit including gate, diffusion, and wire capacitances.
- ❑ The effective capacitance is the true capacitance multiplied by the node activity factor.
- ❑ The switching power depends on the sum of the effective capacitances of all nodes.
- ❑ Activity factor is task-dependent.
- ❑ Low-power → minimize the power equation terms

Dynamic Power Example

- ❑ 1 billion transistor chip
 - 50M logic transistors
 - Average width: 12λ
 - Activity factor = 0.1
 - 950M memory transistors
 - Average width: 4λ
 - Activity factor = 0.02
 - 1.0 V 65 nm process
 - $C = 1 \text{ fF}/\mu\text{m}$ (gate) + $0.8 \text{ fF}/\mu\text{m}$ (diffusion)
- ❑ Estimate dynamic power consumption @ 1 GHz.
Neglect wire capacitance and short-circuit current.

Solution

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = [0.1C_{\text{logic}} + 0.02C_{\text{mem}}](1.0)^2 (1.0 \text{ GHz}) = 6.1 \text{ W}$$

Dynamic Power Reduction

- ❑ $P_{\text{switching}} = \alpha C V_{DD}^2 f$
- ❑ Try to minimize:
 - Activity factor
 - Capacitance
 - Supply voltage
 - Frequency

Activity Factor Estimation


- ❑ Let $P_i = \text{Prob}(\text{node } i = 1)$
 - $\bar{P}_i = 1 - P_i$
- ❑ $\alpha_i = \bar{P}_i * P_i$
- ❑ Completely random data has $P = 0.5$ and $\alpha = 0.25$
- ❑ Data is often not completely random
 - e.g. upper bits of 64-bit words representing bank account balances are usually 0
- ❑ Data propagating through ANDs and ORs has lower activity factor
 - Depends on design, but typically $\alpha \approx 0.1$

Switching Probability

Gate	P_Y
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

 
Example

- ❑ A 4-input AND is built out of two levels of gates
- ❑ Estimate the activity factor at each node if the inputs have $P = 0.5$
- ❑ Construct the truth table and calculate the probabilities




Clock Gating

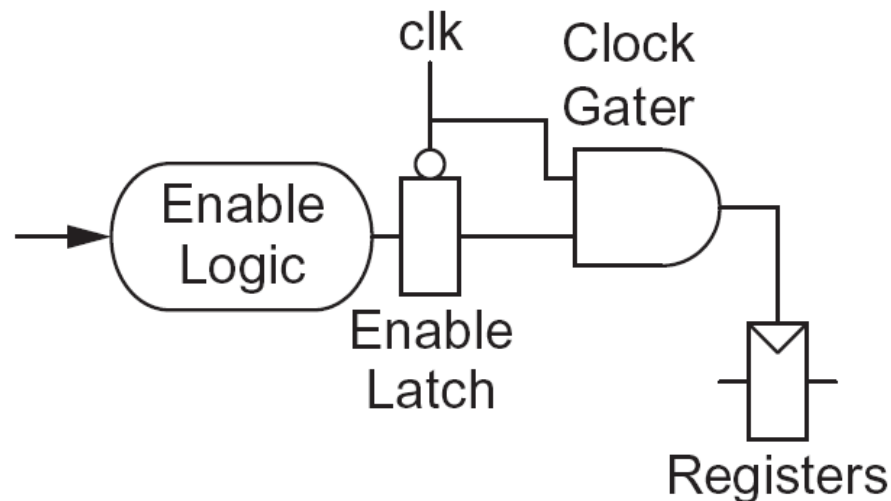- ❑ The best way to reduce the activity is to turn off the clock to registers in unused blocks
 - Saves clock activity ($\alpha = 1$)
 - Eliminates all switching activity in the block
 - Requires determining if block will be used



Glitches

 - ❑ gates sometimes make spurious transitions called glitches when inputs do not arrive simultaneously
- ❑ The glitches cause extra power dissipation
- ❑ Chains of gates are particularly prone to this problem
- ❑ Glitching can raise the activity factor of a gate above 1



Capacitance

- ❑ Gate capacitance
 - Fewer stages of logic
 - Small gate sizes
 - Large gates with higher activity factors can be downsized to reduce power (at the expense of increasing logical effort and delay)
- ❑ Wire capacitance
 - Good floorplanning to keep communicating blocks close to each other
 - Drive long wires with inverters or buffers rather than complex gates

Gate Sizing Under a Delay Constraint

- To compute energy in a circuit, consider:
 - a unit inverter has gate capacitance $3C$,
 - a gate with logical effort g , parasitic delay p , and drive x has gx times as much gate capacitance and px times as much diffusion capacitance.
 - The energy of the entire circuit is the sum of the energies of each gate:

$$\text{Energy} = 3CV_{DD}^2 \sum_{i \in \text{nodes}} \alpha_i \left(\frac{C_{\text{wire}_i}}{3C} + p_i x_i + \sum_{j \in \text{fanout}(i)} g_j x_j \right)$$

Gate Sizing Under a Delay Constraint (2)


- By normalizing the equation:

$$E = \sum_{i \in \text{nodes}} \alpha_i \left(c_i + p_i x_i + \sum_{j \in \text{fanout}(i)} g_j x_j \right) = \sum_{i \in \text{nodes}} \alpha_i x_i d_i$$

- The problem is formulated as an optimization problem to minimize E such that the worst-case arrival time is less than some delay D .
- The problem is still a posynomial and has a unique solution that can be found quickly by a good optimizer.

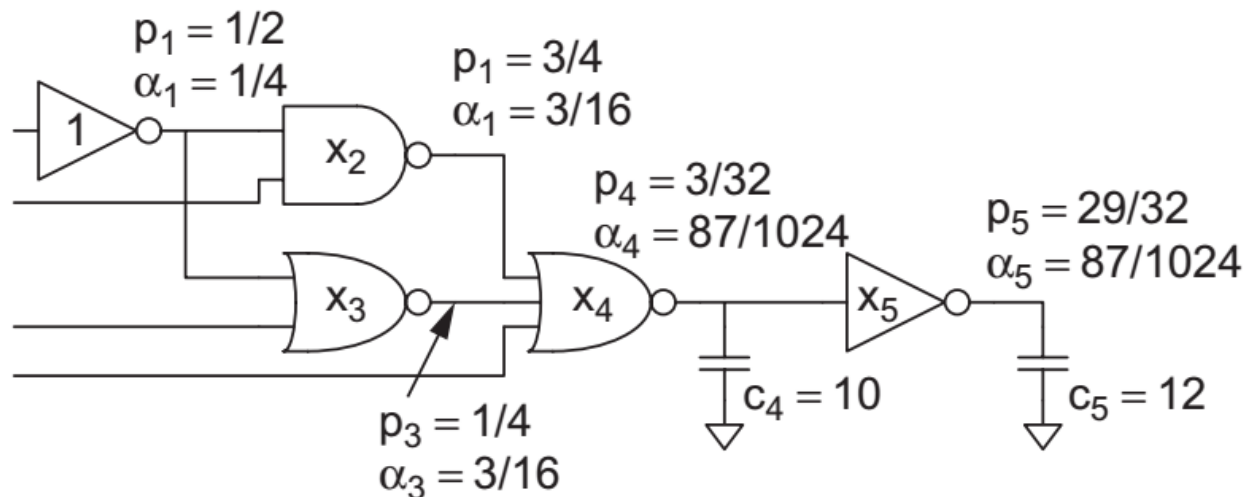Example

- Generate an energy-delay trade-off curve for the following circuit as delay varies from the minimum possible ($D_{\min} = 23.44 \tau$ to 50τ). Assume that the input probabilities are 0.5.




Solution

- ❑ The Energy of the circuit is:


$$E = \frac{1}{4} \left(1 + \frac{4}{3} x_2 + \frac{5}{3} x_3 \right) + \frac{3}{16} \left(2x_2 + \frac{7}{3} x_4 \right) + \frac{3}{16} \left(2x_3 + \frac{7}{3} x_4 \right) + \frac{87}{1024} \left(10 + 3x_4 + x_5 \right) + \frac{87}{1024} \left(12 + x_5 \right)$$

 - ❑ The energy-delay trade-off curve obtained by an automatic Solver is depicted
- ❑ The delay cannot be minimized unless the input inverter size is increased





Voltage Domains

- ❑ Run each block at the lowest possible voltage and frequency that meets performance requirements
- ❑ Voltage Domains
 - Provide separate supplies to different blocks
 - Level converters required when crossing from low to high V_{DD} domains
 - Voltage domains are associated with a large area of the floorplan
- ❑ Clustered Voltage Scaling (CVS) is an alternative approach to use two supply voltages in the same block with some constraints

 

Dynamic Voltage Scaling

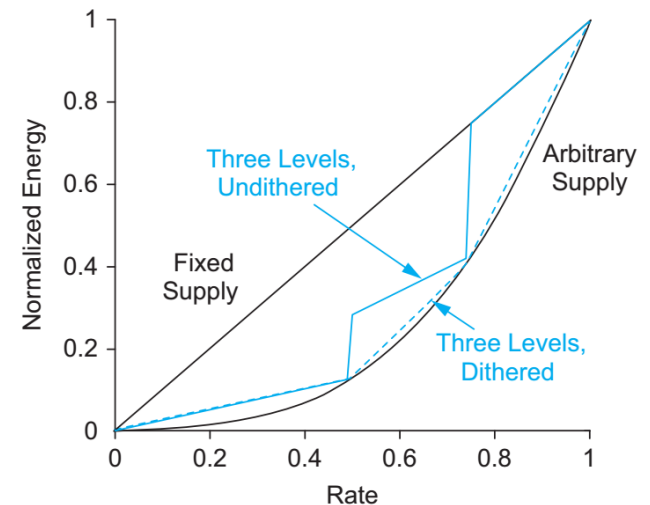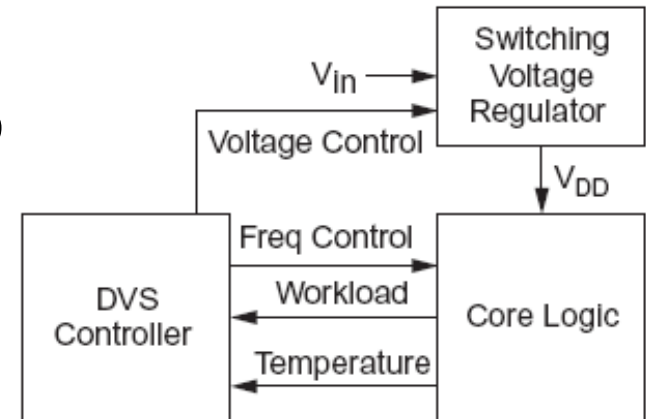- ❑ Dynamic Voltage Scaling (DVS)
 - Adjust V_{DD} and f according to workload
- ❑ DVFS
 - reducing the clock frequency to the minimum per task
 - reducing the supply voltage to the minimum necessary to operate at that frequency



Short-Circuit Current

- ❑ While the input switches, both pullup and pulldown networks are partially ON causing short-circuit current.
- ❑ It increases as the input edge rates become slower because both networks are ON for more time, and decreases as load capacitance increases.
- ❑ short-circuit current is a small fraction ($< 10\%$) of current to the load and can be ignored for sharp input edges.
- ❑ Short-circuit power is strongly sensitive to the ratio $v = V_t / V_{DD}$, for $v=0.5$ short circuit current is zero.

Static Power

- ❑ Static CMOS gates have no contention current
- ❑ Static power is consumed even when chip is quiescent.
 - Leakage draws power from nominally OFF devices
 - Ratioed circuits burn power in flight between ON transistors

Subthreshold Leakage

- For $V_{ds} > 50$ mV

$$I_{sub} \approx I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{DD}) - k_{\gamma} V_{sb}}{S}}$$

- I_{off} = leakage at $V_{gs} = 0$, $V_{ds} = V_{DD}$
 η : the DIBL coefficient
 K_{γ} : The body effect coefficient
 S : Subthreshold slope

- I_{off} is usually specified at 25 °C and increases exponentially with temperature

Typical values in 65 nm

$$I_{off} = 100 \text{ nA}/\mu\text{m} \text{ @ } V_t = 0.3 \text{ V}$$

$$I_{off} = 10 \text{ nA}/\mu\text{m} \text{ @ } V_t = 0.4 \text{ V}$$

$$I_{off} = 1 \text{ nA}/\mu\text{m} \text{ @ } V_t = 0.5 \text{ V}$$


$$\eta = 0.1$$

$$k_{\gamma} = 0.1$$

$$S = 100 \text{ mV/decade}$$

Stack Effect

 - Series OFF transistors have less leakage
 - V_x small, N_1 has low DIBL and small leak
 - $V_x > 0$, so N_2 has negative V_{gs}



$$I_{sub} = \underbrace{I_{off} 10^{\frac{\eta(V_x - V_{DD})}{S}}}_{N1} = \underbrace{I_{off} 10^{\frac{-V_x + \eta((V_{DD} - V_x) - V_{DD}) - k_\gamma V_x}{S}}}_{N2}$$

$$V_x = \frac{\eta V_{DD}}{1 + 2\eta + k_\gamma}$$

$$I_{sub} = I_{off} 10^{\frac{-\eta V_{DD} \left(\frac{1 + \eta + k_\gamma}{1 + 2\eta + k_\gamma} \right)}{S}} \approx I_{off} 10^{\frac{-\eta V_{DD}}{S}}$$

- Leakage through 2-stack reduces $\sim 10x$
- Leakage through 3-stack reduces further

Leakage Control

- ❑ Leakage and delay trade off
 - Aim for low leakage in sleep and low delay in active mode
- ❑ To reduce leakage:
 - Increase V_t : *multiple V_t*
 - Use low V_t only in critical circuits
 - Increase V_s : *stack effect*
 - *Input vector control* in sleep
 - Decrease V_b
 - *Reverse body bias* in sleep
 - Or forward body bias in active mode

Leakage Control (2)


- ❑ Other forms of leakage must be considered to reduce Subthreshold leakage.
- ❑ Raising the doping level to raise V_t by controlling DIBL and short-channel effects increases BTBT.
- ❑ Applying a reverse body bias to increase V_t also causes BTBT to increase.
- ❑ Applying a negative gate voltage to turn the transistor OFF more strongly increases GIDL.
- ❑ Silicon on Insulator (SOI) circuits are attractive for low-leakage designs because they have a sharper subthreshold current roll-off.

Gate Leakage


- ❑ Extremely strong function of t_{ox} and V_{gs}
 - Negligible for older processes
 - Approaches subthreshold leakage at 65 nm and below in some processes
- ❑ An order of magnitude less for pMOS than nMOS
- ❑ Control leakage in the process using $t_{\text{ox}} > 10.5 \text{ \AA}$
 - High-k gate dielectrics help
 - Some processes provide multiple t_{ox}
 - e.g. thicker oxide for 3.3 V I/O transistors
- ❑ Control leakage in circuits by limiting V_{DD}

Gate Leakage (2)

- ❑ Gate leakage also depends on the voltage across the gate
- ❑ For the example in the figure
 - If $N1$ is ON and $N2$ is OFF, $N1$ has $V_{gs} = V_{DD}$ and has full gate leakage.
 - On the other hand, if $N1$ is OFF and $N2$ is on, $N2$ has $V_{gs} = V_t$ and experiences negligible gate leakage
 - In both cases, the OFF transistor has no gate leakage.
 - Thus, gate leakage can be alleviated by stacking transistors such that the OFF transistor is closer to the rail

 

(a)

 


(b)

NAND3 Leakage Example

□ 100 nm process

$$I_{gn} = 6.3 \text{ nA} \quad I_{gp} = 0$$
 
$$I_{offn} = 5.63 \text{ nA} \quad I_{offp} = 9.3 \text{ nA}$$



Input State (ABC)	I_{sub}	I_{gate}	I_{total}	V_x	V_z
000	0.4	0	0.4	stack effect	stack effect
001	0.7	0	0.7	stack effect	$V_{DD} - V_t$
010	0.7	1.3	2.0	intermediate	intermediate
011	3.8	0	3.8	$V_{DD} - V_t$	$V_{DD} - V_t$
100	0.7	6.3	7.0	0	stack effect
101	3.8	6.3	10.1	0	$V_{DD} - V_t$
110	5.6	12.6	18.2	0	0
111	28	18.9	46.9	0	0

Data from [Lee03]

Junction Leakage

- ❑ From reverse-biased p-n junctions
 - Between diffusion and substrate or well
- ❑ Ordinary diode leakage is negligible
- ❑ Band-to-band tunneling (BTBT) can be significant
 - Especially in high- V_t transistors where other leakage is small
 - Worst at $V_{db} = V_{DD}$
- ❑ Gate-induced drain leakage (GIDL) exacerbates
 - Worst for $V_{gd} = -V_{DD}$ (or more negative)

Static Power Estimation

- ❑ Static CMOS circuits have no contention current.
- ❑ Some other families inherently draw current even while quiescent. (e.g. pseudo nMOS logic)
- ❑ Static current is estimated by:
 - Estimate total width of transistors that are leaking,
 - multiplying by the leakage current per width,
 - and multiplying by the fraction of transistors that are in their leaky state (usually one half).
 - Add the contention current if applicable.
 - The static power is the supply voltage times the static current.

Static Power Example

- ❑ Revisit power estimation for 1 billion transistor chip
- ❑ Estimate static power consumption
 - Subthreshold leakage
 - Normal V_t : 100 nA/ μm
 - High V_t : 10 nA/ μm
 - High V_t used in all memories and in 95% of logic gates
 - Gate leakage 5 nA/ μm
 - Junction leakage negligible

Solution

$$W_{\text{normal-}V_t} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(0.05) = 0.75 \times 10^6 \mu\text{m}$$

$$W_{\text{high-}V_t} = \left[(50 \times 10^6)(12\lambda)(0.95) + (950 \times 10^6)(4\lambda) \right] (0.025 \mu\text{m} / \lambda) = 109.25 \times 10^6 \mu\text{m}$$


$$I_{\text{sub}} = \left[W_{\text{normal-}V_t} \times 100 \text{ nA}/\mu\text{m} + W_{\text{high-}V_t} \times 10 \text{ nA}/\mu\text{m} \right] / 2 = 584 \text{ mA}$$

$$I_{\text{gate}} = \left[(W_{\text{normal-}V_t} + W_{\text{high-}V_t}) \times 5 \text{ nA}/\mu\text{m} \right] / 2 = 275 \text{ mA}$$

$$P_{\text{static}} = (584 \text{ mA} + 275 \text{ mA})(1.0 \text{ V}) = 859 \text{ mW}$$

Power Gating

- ❑ Turn OFF power to blocks when they are idle to save leakage
 - Use virtual V_{DD} (V_{DDV})
 - Gate outputs to prevent invalid logic levels to next block
- ❑ Voltage drop across sleep transistor degrades performance during normal operation
 - Size the transistor wide enough to minimize delay and voltage drop
 - Also, it should have low leakage during sleep
- ❑ Switching wide sleep transistor costs dynamic power
 - Only justified when circuit sleeps long enough

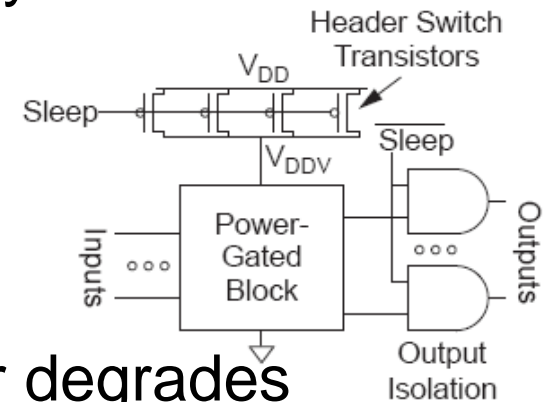

Power Gating Design

- ❑ It can be done externally with a disable input to a voltage regulator or internally with high- V_t header or footer switches
- ❑ On-chip power gating can use pMOS header switch transistors or nMOS footer switch transistors
- ❑ *Fine-grained power gating* can be applied to individual logic gates, but placing a switch in every cell has enormous area overhead
- ❑ Practical designs use *coarse-grained power gating* where the switch is shared across an entire block
- ❑ The switch is commonly sized to keep this delay to 5–10%

Multiple Threshold Voltages

- ❑ Multiple threshold voltages can keep performance on critical paths with low- V_t transistors while reducing leakage on others with high- V_t transistors.
- ❑ Good design practice starts with high- V_t devices everywhere and selectively introduces low- V_t devices where necessary.
- ❑ Using multiple thresholds requires additional implant masks that add to the cost of a CMOS process.
- ❑ Alternatively, designers can increase the channel length, which tends to raise the threshold voltage via the short channel effect.

Variable Threshold Voltage

- ❑ V_{sb} controls the threshold voltage via the body effect
- ❑ In *variable threshold CMOS* (VTCMOS), a body bias is applied to achieve high I_{on} and low I_{off}
- ❑ For example, low- V_t devices can be used and a *reverse body bias* (RBB) can be applied during sleep mode to reduce leakage
- ❑ Alternatively, higher- V_t devices can be used, and then a *forward body bias* (FBB) can be applied during active mode to increase performance
- ❑ Improper body biasing can increase leakage via BTBT and junction leakage