

Lecture 8: Wires

Outline


- Introduction
- Wire Resistance
- Wire Capacitance
- Wire RC Delay
- Crosstalk
- Wire Engineering
- Repeaters

Introduction

- ❑ Chips are mostly made of wires called *interconnect*
 - In stick diagram, wires set size
 - Transistors are little things under the wires
 - Many layers of wires
- ❑ Wires are as important as transistors
 - Speed
 - Power
 - Noise
- ❑ Alternating layers run orthogonally

Wire Geometry

 
- ❑ Pitch = $w + s$
- ❑ Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires




Layer Stack

- ❑ AMI 0.6 μm process has 3 metal layers
- ❑ Modern processes use 6-10+ metal layers
- ❑ Example:
 - Intel 180 nm process
 - ❑ M1: thin, narrow ($< 3\lambda$)
 - High density cells
 - ❑ M2-M4: thicker
 - For longer wires
 - ❑ M5-M6: thickest
 - For V_{DD} , GND, clk

Layer	T (nm)	W (nm)	S (nm)	AR
6	1720	860	860	2.0
	1000			
5	1600	800	800	2.0
	1000			
4	1080	540	540	2.0
	700			
3	700	320	320	2.2
	700			
2	700	320	320	2.2
	700			
1	480	250	250	1.9
	800			

 


Example

 

Intel 90 nm Stack

[Thompson02]

 


Intel 45 nm Stack

[Moon08]

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$


$R =$

 

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$

$$R = \frac{\rho}{t} \frac{l}{w}$$

 

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$


$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

□ $R_{\square} = \text{sheet resistance } (\Omega/\square)$

– \square is a dimensionless unit(!)

□ Count number of squares

 – $R = R_{\square} * (\# \text{ of squares})$



Choice of Metals


- ❑ Until 180 nm generation, most wires were aluminum
- ❑ Modern processes often use copper
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

Metal	Bulk resistivity ($\mu\Omega\cdot\text{cm}$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Molybdenum (Mo)	5.3

Copper Issues

- ❑ Copper wires diffusion barrier has high resistance
- ❑ Copper is also prone to *dishing* during polishing
- ❑ Effective resistance is higher
 
$$R = \frac{\rho}{(t - t_{\text{dish}} - t_{\text{barrier}})} \frac{l}{(w - 2t_{\text{barrier}})}$$



Example

- ❑ Compute the sheet resistance of a $0.22 \mu\text{m}$ thick Cu wire in a 65 nm process. The resistivity of thin film Cu is $2.2 \times 10^{-8} \Omega\cdot\text{m}$. Ignore dishing.

$$R_{\square} =$$

- ❑ Find the total resistance if the wire is $0.125 \mu\text{m}$ wide and 1 mm long. Ignore the barrier layer.

$$R =$$


Sheet Resistance

- Typical sheet resistances in 180 nm process

Layer	Sheet Resistance (Ω/\square)
Diffusion (silicided)	3-10
Diffusion (no silicide)	50-200
Polysilicon (silicided)	3-10
Polysilicon (no silicide)	50-400
Metal1	0.08
Metal2	0.05
Metal3	0.05
Metal4	0.03
Metal5	0.02
Metal6	0.02


Contacts Resistance

 - ❑ Contacts and vias also have 2-20 Ω
- ❑ Use many contacts for lower R
 - Many small contacts for current crowding around periphery



Wire Capacitance

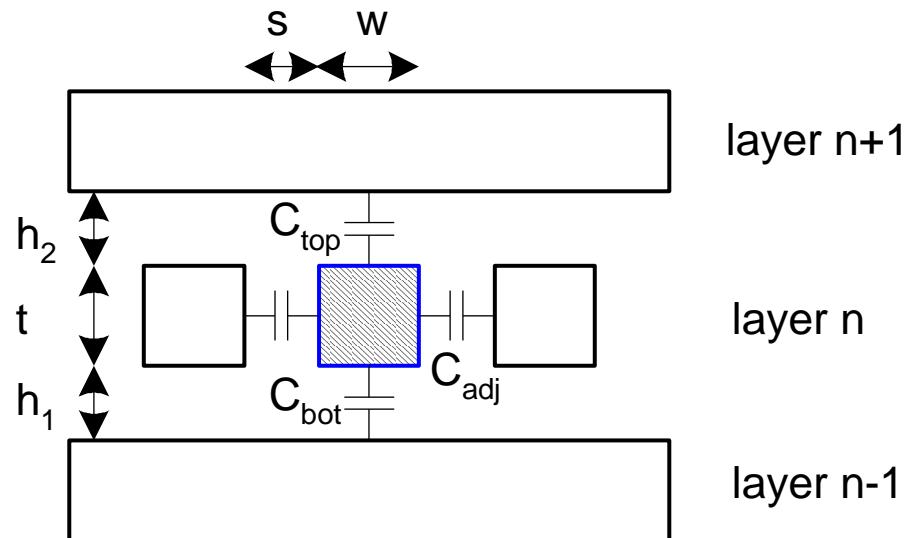- ❑ Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- ❑ $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$



Capacitance Trends


- ❑ Parallel plate equation: $C = \epsilon A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (W, t) increases capacitance
 - Increasing distance (s, h) decreases capacitance
- ❑ Dielectric constant
 - $\epsilon = k\epsilon_0$
- ❑ $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm
- ❑ $k = 3.9$ for SiO_2
- ❑ Processes are starting to use low- k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

Capacitance Formula

- ❑ Capacitance of a conductor above a ground plane can be approximated as


$$C_{tot} = \epsilon_{ox} l \left[\frac{w}{h} + 0.77 + 1.06 \left(\frac{w}{h} \right)^{0.25} + 1.06 \left(\frac{t}{h} \right)^{0.5} \right]$$

 - ❑ This empirical formula is accurate to 6% for $AR < 3.3$
- ❑ This formula does not account for neighbors in the same layer or higher layers




M2 Capacitance Data

 - Typical wires have ~ 0.2 fF/ μm
 - Compare to 2 fF/ μm for gate capacitance



S: normalized spacing

 


Diffusion & Polysilicon

- ❑ Diffusion capacitance is very high (about 2 fF/ μm)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion *runners* for wires!
- ❑ Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Lumped Element Models

 - ❑ Wires are a distributed system
 - Approximate with lumped element models




- ❑ 3-segment π -model is accurate to 3% in simulation
- ❑ L-model needs 100 segments for same accuracy!
- ❑ Use single segment π -model for Elmore delay

Example

- Metal2 wire in 180 nm process
 - 5 mm long
 - 0.32 μm wide
- Construct a 3-segment π -model
 - $R_{\square} =$
 - $C_{\text{permicron}} =$

 Example

- ❑ Metal2 wire in 180 nm process
 - 5 mm long
 - 0.32 μm wide
- ❑ Construct a 3-segment π -model
 - $R_{\square} = 0.05 \Omega/\square$ $\Rightarrow R = 781 \Omega$
 - $C_{\text{permicron}} = 0.2 \text{ fF}/\mu\text{m}$ $\Rightarrow C = 1 \text{ pF}$




Wire RC Delay

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example.
 - $R = 2.5 \text{ k}\Omega \cdot \mu\text{m}$ for gates
 - Unit inverter: $0.36 \mu\text{m}$ nMOS, $0.72 \mu\text{m}$ pMOS

- $t_{pd} =$

Wire RC Delay

 
- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example.
 - $R = 2.5 \text{ k}\Omega \cdot \mu\text{m}$ for gates
 - Unit inverter: $0.36 \mu\text{m}$ nMOS, $0.72 \mu\text{m}$ pMOS



– $t_{pd} = 1.1 \text{ ns}$

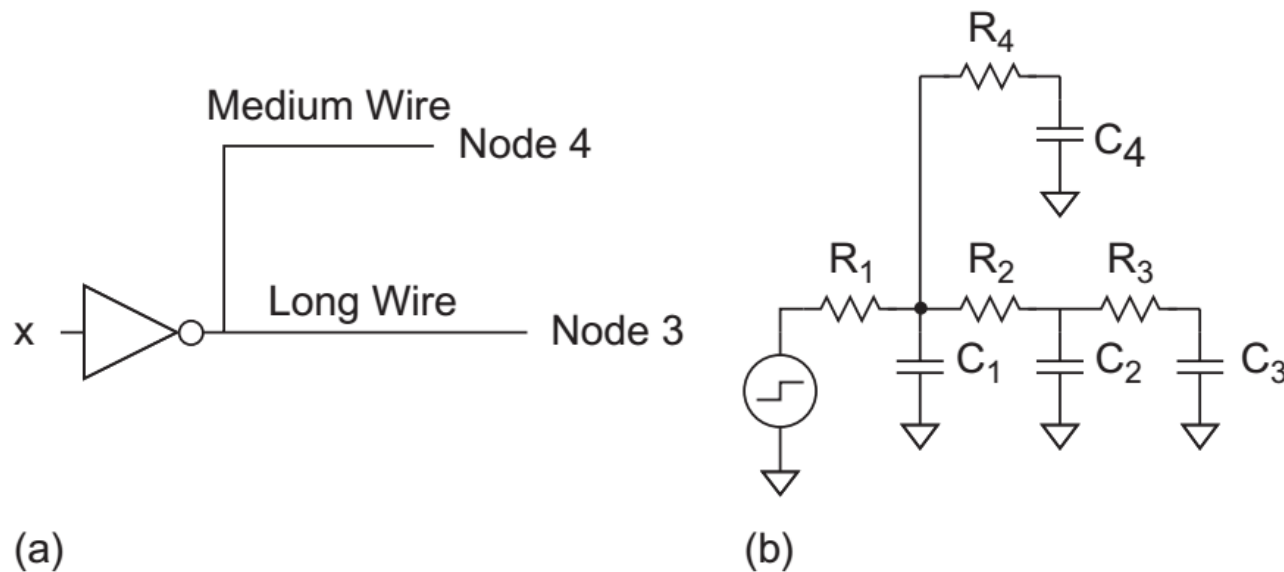Example 6.5

- A gate driving wires to two destinations:



$$T_{D_3} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + R_1 C_4$$

$$T_{D_4} = R_1 C_1 + R_1 (C_2 + C_3) + (R_1 + R_4) C_4$$

Crosstalk


- ❑ A capacitor does not like to change its voltage instantaneously.
- ❑ A wire has high capacitance to its neighbor.
 - When the neighbor switches from 1- \rightarrow 0 or 0- \rightarrow 1, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*.
- ❑ Crosstalk effects
 - Noise on nonswitching wires
 - Increased delay on switching wires

Crosstalk Delay

- ❑ Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$

- ❑ Effective C_{adj} depends on behavior of neighbors

 – *Miller effect: The charge delivered to the coupling capacitor is $Q = C_{\text{adj}} \Delta V$*




B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant			
Switching with A			
Switching opposite A			

Crosstalk Delay

- ❑ Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- ❑ Effective C_{adj} depends on behavior of neighbors
 - *Miller effect: Miller Coupling Factor*

(MCF)

 

B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant	V_{DD}	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	C_{gnd}	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2 C_{\text{adj}}$	2

Miller Coupling Factor

- ❑ The *Miller Coupling Factor* (MCF) describes how the capacitance to adjacent wires is multiplied to find the effective capacitance
- ❑ Some designers use $MCF = 1.5$ as a statistical compromise when estimating propagation delays before layout information is available.
- ❑ A conservative design methodology assumes neighbors are switching to compute propagation and contamination delays ($MCF = 2$ and 0 , respectively).
- ❑ A more aggressive methodology tracks the time and direction of switching between neighbor wires.

Example

- ❑ Two 1 mm lines has capacitance of 0.08 fF/ μm to ground and 0.12 fF/ μm to its neighbor
 - Each wire is driven by an inverter of 1K Ω resistance
 - Estimate the contamination and propagation delays of the path.

- ❑ Solution:

$$C_{\text{gnd}} = (0.08 \text{ fF}/\mu\text{m})(1000 \mu\text{m}) = 80 \text{ fF} , C_{\text{adj}} = 120 \text{ fF}$$

$$T_d = RC_{\text{eff}}$$


$$\text{Contamination delay (MCF=0)} \rightarrow C_{\text{eff}} = C_{\text{gnd}}$$

$$\text{Propagation delay (MCF=2)} \rightarrow C_{\text{eff}} = C_{\text{gnd}} + 2 C_{\text{adj}}$$

Crosstalk Noise

- ❑ Crosstalk causes noise on nonswitching wires
- ❑ If victim is floating:
 - model as capacitive voltage divider
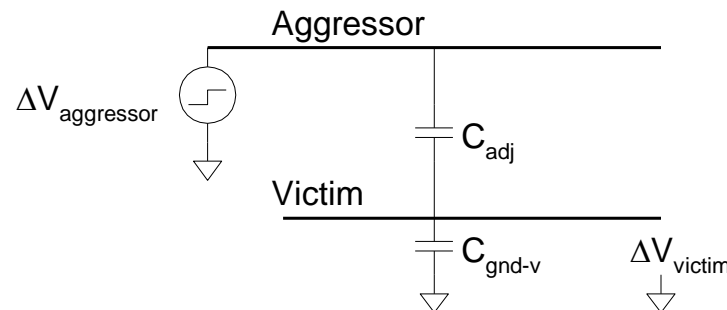
$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$




Driven Victims

- Usually victim is driven by a gate that fights noise
 - Noise depends on relative resistances
 - Victim driver is in linear region, agg. in saturation
 - If sizes are same, $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1+k} \Delta V_{\text{aggressor}}$$
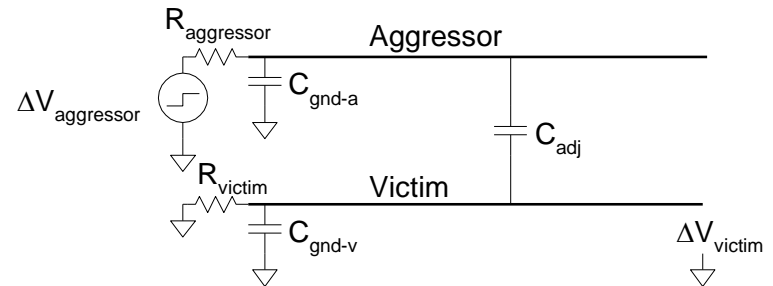
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$



Coupling Waveforms

 - Simulated coupling for $C_{adj} = C_{victim}$



Noise Implications



- ❑ *So what* if we have noise?
- ❑ If the noise is less than the noise margin, nothing happens
- ❑ Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- ❑ Dynamic logic never recovers from glitches
- ❑ Memories and other sensitive circuits also can produce the wrong answer

Wire Engineering

- ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:



Wire Engineering

  - ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:
 - Width
 - Spacing



Wire Engineering

  - ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:
 - Width
 - Spacing
 - Layer






Wire Engineering

❑ Goal: achieve delay, area, power goals with acceptable noise

❑ Degrees of freedom:

- Width
- Spacing
- Layer
- Shielding

   

Width, Spacing, and Layer



- ❑ The wire width, spacing, and layer usage are selected to trade off delay, bandwidth, energy, and noise.
- ❑ Minimum pitch wires are preferred for noncritical wires
- ❑ When the load is dominated by wire capacitance, increase spacing to reduce delay is by reducing the capacitance to nearby neighbors which also reduces the energy and coupling noise.
- ❑ When the delay is dominated by the gate capacitance and wire resistance, widening the wire reduces resistance and delay, reduces coupling noise, but increases the energy.

Repeaters

- ❑ R and C are proportional to l
- ❑ RC delay is proportional to l^2
 - Unacceptably great for long wires

Repeaters

  - ❑ R and C are proportional to l
- ❑ RC delay is proportional to l^2
 - Unacceptably great for long wires
- ❑ Break long wires into N shorter segments
 - Drive each one with an inverter or buffer




Repeater Design

- ❑ How many repeaters should we use?
- ❑ How large should each one be?
- ❑ Equivalent Circuit
 - Wire length l/N
 - Wire Capacitance $C_w * l/N$, Resistance $R_w * l/N$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W

Repeater Design

 - ❑ How many repeaters should we use?
- ❑ How large should each one be?
- ❑ Equivalent Circuit
 - Wire length l
 - Wire Capacitance $C_w * l$, Resistance $R_w * l$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W



Repeater Results

- Write equation for Elmore Delay
 - Differentiate with respect to W and N
 - Set equal to 0, solve

$$\frac{l}{N} = \sqrt{\frac{2RC'}{R_w C_w}}$$

$$\frac{t_{pd}}{l} = (2 + \sqrt{2}) \sqrt{RC'R_w C_w}$$

~60-80 ps/mm

in 180 nm process

$$W = \sqrt{\frac{RC_w}{R_w C'}}$$

Repeater Energy

- Energy / length $\approx 1.87C_w V_{DD}^2$
 - 87% premium over unrepeated wires
 - The extra power is consumed in the large repeaters
- If the repeaters are downsized for minimum EDP:
 - Energy premium is only 30%
 - Delay increases by 14% from min delay

Crosstalk Control

- ❑ The crosstalk is proportional to the ratio of coupling capacitance to total capacitance.
- ❑ For modern processes, the coupling capacitance contributes more than $\frac{3}{4}$ of the total capacitance.
- ❑ There are several approaches to control crosstalk:
 - Increase spacing to adjacent lines
 - Shield wires: usually clock signal is shielded
 - Ensure neighbors switch at different times: e.g. signals switch at different clock edges
 - Crosstalk cancellation: arrange wires to cancel the effects of crosstalk

Logical Effort with Wires

- ❑ The branching effort at a wire with capacitance C_{wire} driving a gate load of C_{gate} is $(C_{\text{gate}} + C_{\text{wire}}) / C_{\text{gate}}$
- ❑ This branching effort is not constant; it depends on the size of the gate being driven
- ❑ For short interconnect ($C_{\text{wire}} \ll C_{\text{gate}}$), C_{wire} can be ignored.
- ❑ Conversely, when the interconnect is long ($C_{\text{wire}} \gg C_{\text{gate}}$), the gate at the end can be ignored.
- ❑ The path can now be partitioned into two parts; the first part drives the wire while the second receives its input from the wire.

Logical Effort with Wires


- ❑ The most difficult problems occur when $C_{\text{wire}} \approx C_{\text{gate}}$.
- ❑ These wires introduce branching efforts that are a function of the size of the gates they drive
- ❑ Example:

$$d = \frac{x}{10} + \frac{y+50}{x} + \frac{100}{y} + P$$

Diff W.R.T x and y yields:

$$\frac{1}{10} - \frac{y+50}{x^2} = 0 \Rightarrow x^2 = 10y + 500$$
 
$$\frac{1}{x} - \frac{100}{y^2} = 0 \Rightarrow y^2 = 100x$$



$x=33$ fF and $y=57$ fF

The stage efforts are $(33/10) = 3.3$, $(57 + 50)/33 = 3.2$, and $(100/57) = 1.8$

Not equal as usual due to the wire capacitance