



Course Title and Code Number:
Principles and Applications of Electrical Engineering (05211)
Second Year (Agricultural Engineering)
Time Allowed: One hour

اسم المقرر والرقم الكودي له:
مبادئ الهندسة الكهربائية وتطبيقاتها (05211)
السنة الدراسية الثانية (هندسة زراعية)
الزمن: ساعة

Attempt All Questions:

(60 marks)

- In Figure 1, if $v_1 = v/8$ and the power delivered by the source is 8 mW, find R , v , v_1 , and i .
- Find the equivalent resistance between terminals a and b in the circuit of Figure 2.
- Using **node voltage analysis** in the circuit of Figure 3, find the three indicated node voltages.
- Using **mesh current analysis**, find the voltage, v , across the current source in the circuit of Figure 4.
- Find the voltage, v , across the 3Ω - resistor in the circuit of Figure 5 by replacing the remainder of the circuit with its **Thevenin equivalent**.
- Repeat problem 5 using **superposition**.

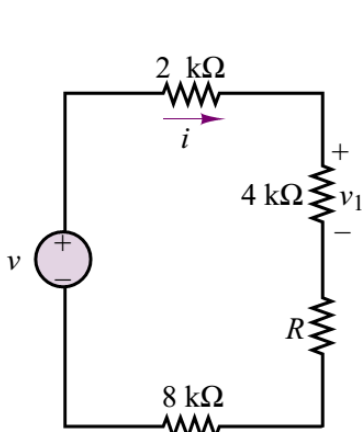


Figure 1

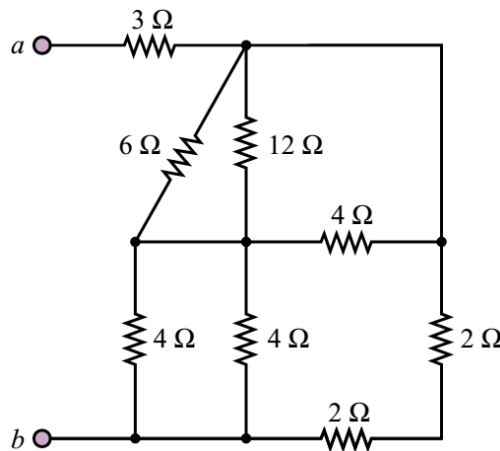


Figure 2

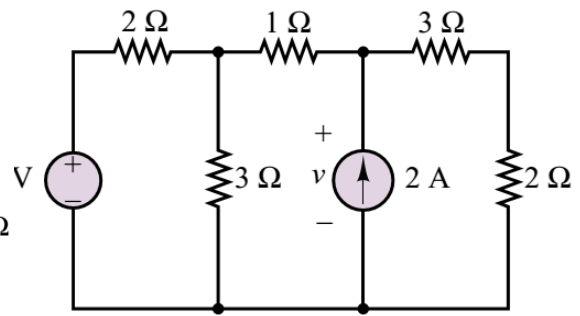


Figure 4

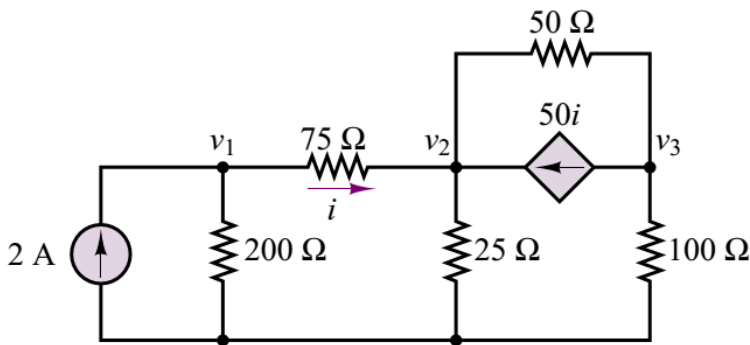


Figure 3

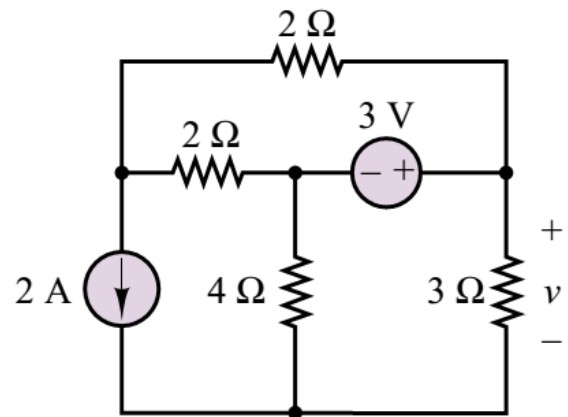


Figure 5

Good Luck

Examiner: Dr. Mohammed Morsy