

by

Prof. Dr. Osman SEVAİOĞLU

Electrical and Electronics Engineering Department



Basic Principles of Electricity

Course Syllabus

EE 209


Fundamentals of Electrical and Electronics Engineering (3-0)3

- Basic Principles of Electricity,
- Circuit Analysis,
- AC Circuits,
- AC Power,
- Phasors,
- Three Phase Systems,
- Transformers,
- Magnetic Circuits,
- Electrical Safety

(Offered to non-EE students only)

Prerequisite: PHYS 106 or consent of the department.

Book for the Course

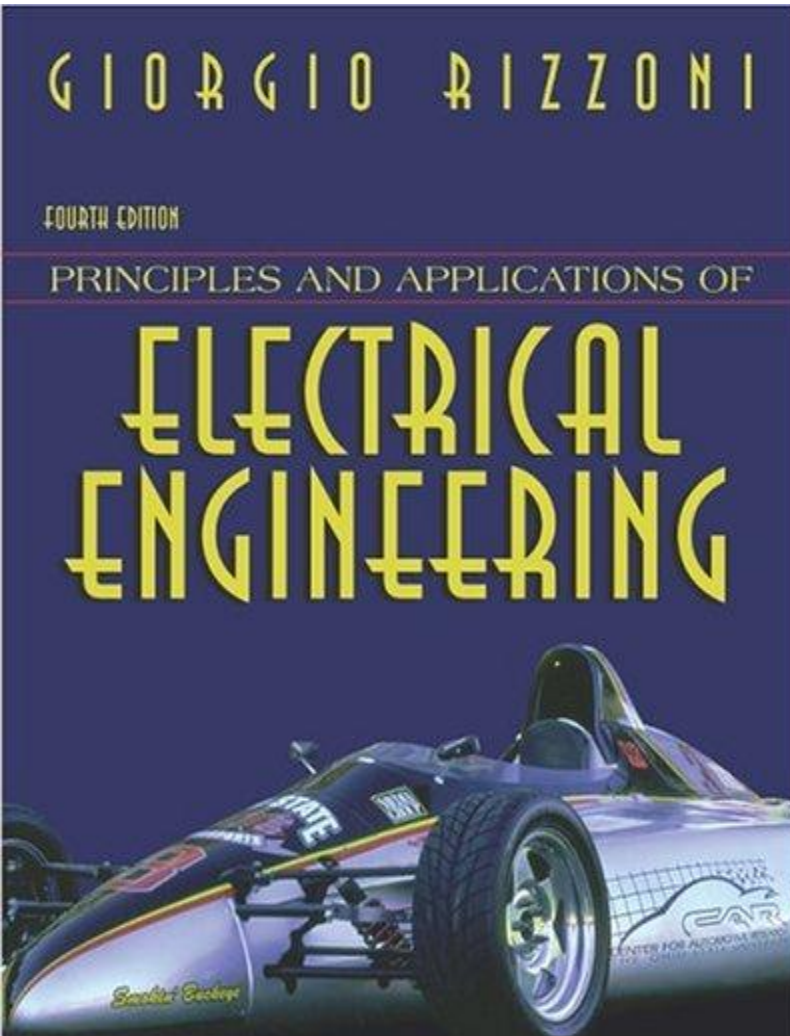

Principles and Applications of Electrical Engineering, 4/e

Giorgio Rizzoni
The Ohio State University

Mc. Graw Hill Book Company,


ISBN: 0072463473

Copyright year: 2003

999 Pages

*Available in Reserve Division of the
Middle East Technical University
Central Library*

Course Syllabus

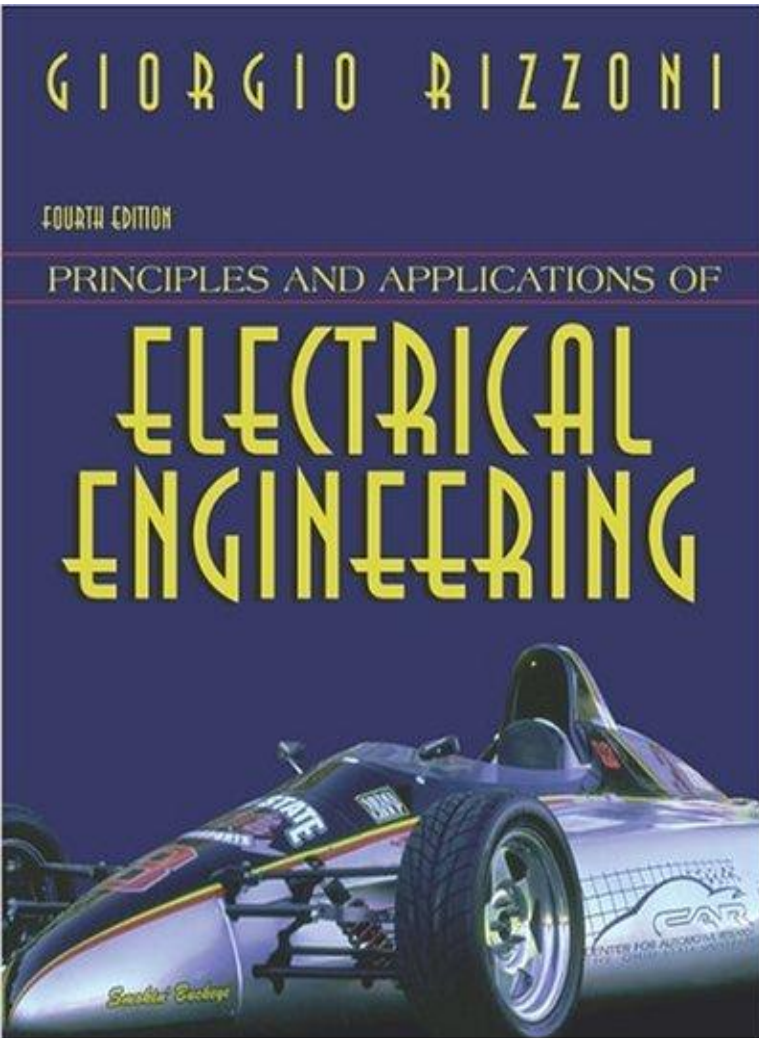

Chapters to be Covered

- Basic Principles of Electricity,
- Circuit Analysis,
- AC Circuits,
- AC Power,
- Phasors,
- Three Phase Systems,
- Transformers,
- Magnetic Circuits,
- Electrical Safety

Atom

Structure of atom



Electron is assumed to be negatively charged
Proton is assumed to be positive charged

Helium Atom

Electron

Proton

Neutron

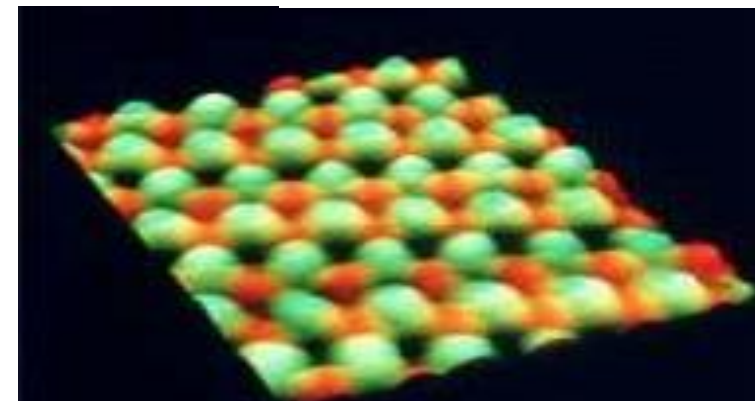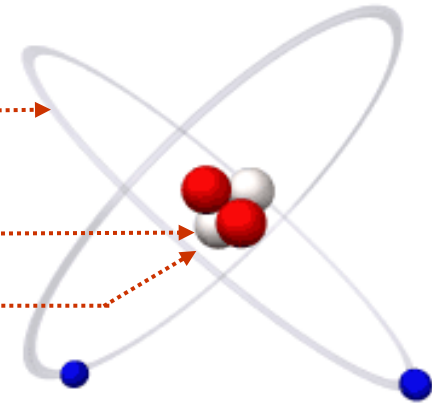

IBM Research/Peter Arnold, Inc.

Electrical Charge

Definition


Unit of Electrical Charge Coulomb

6.3×10^{18} electrons \triangleq 1 Coulomb

or

Electrical charge / electron = $1 / (6.3 \times 10^{18})$
Coulomb


$= 1.602 \times 10^{-19}$ Coulomb

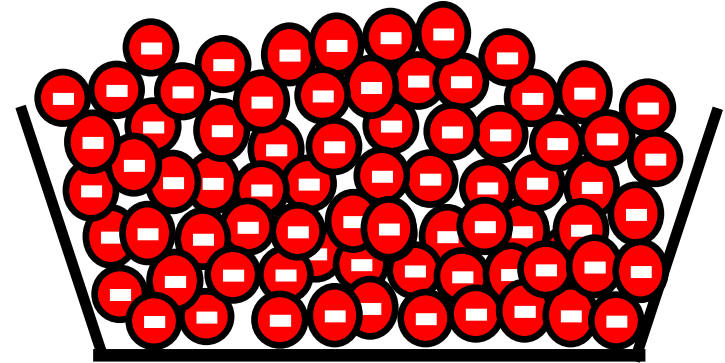


Basic Principle of Circuit

Mechanical Example

Inclined Surface

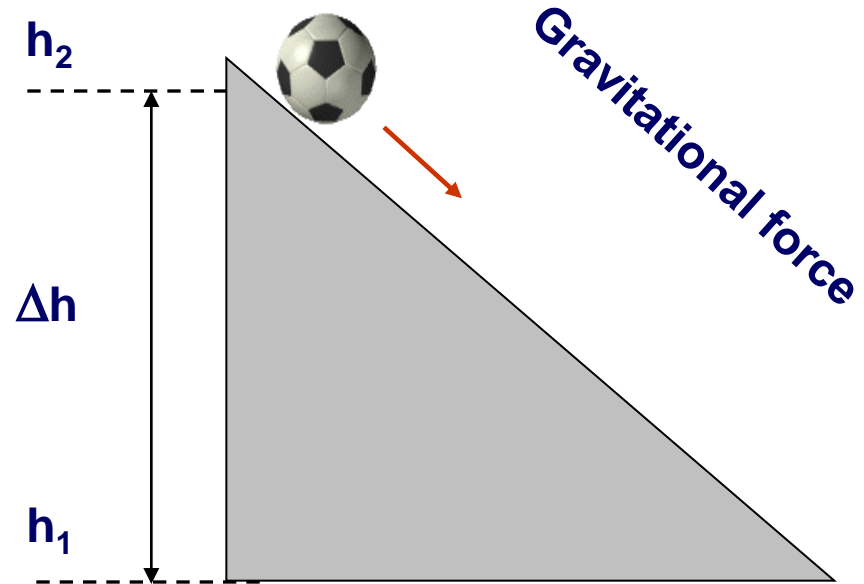


Water Circuit

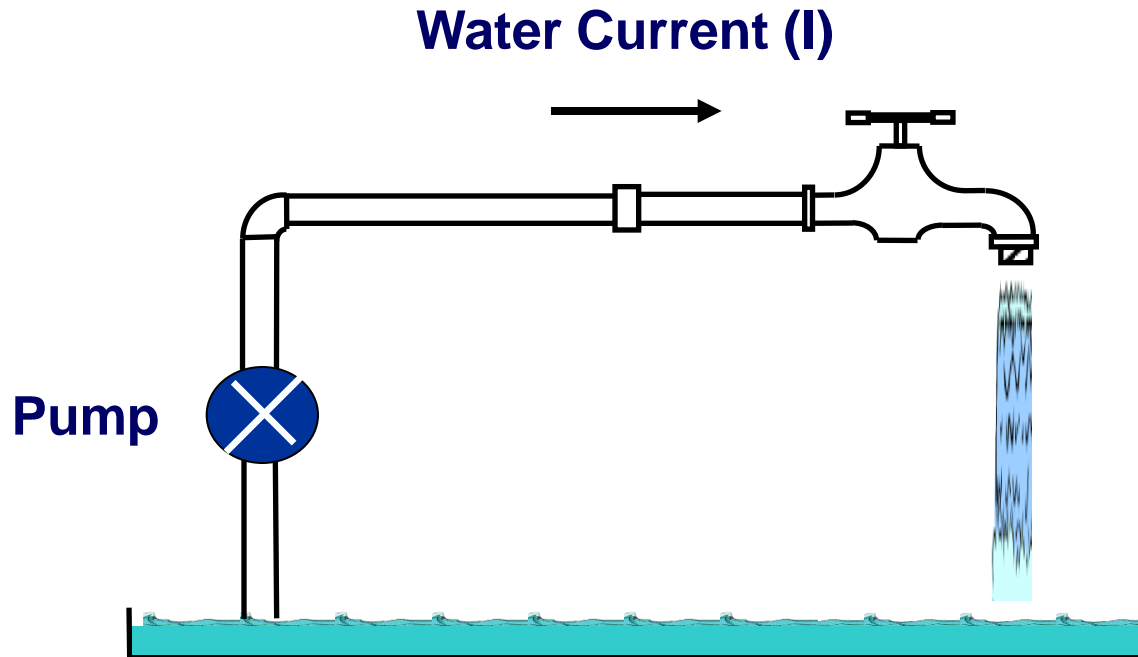


$$\text{Water Current} = \text{Volume (m}^3\text{)} / \text{sec}$$

Water Circuit

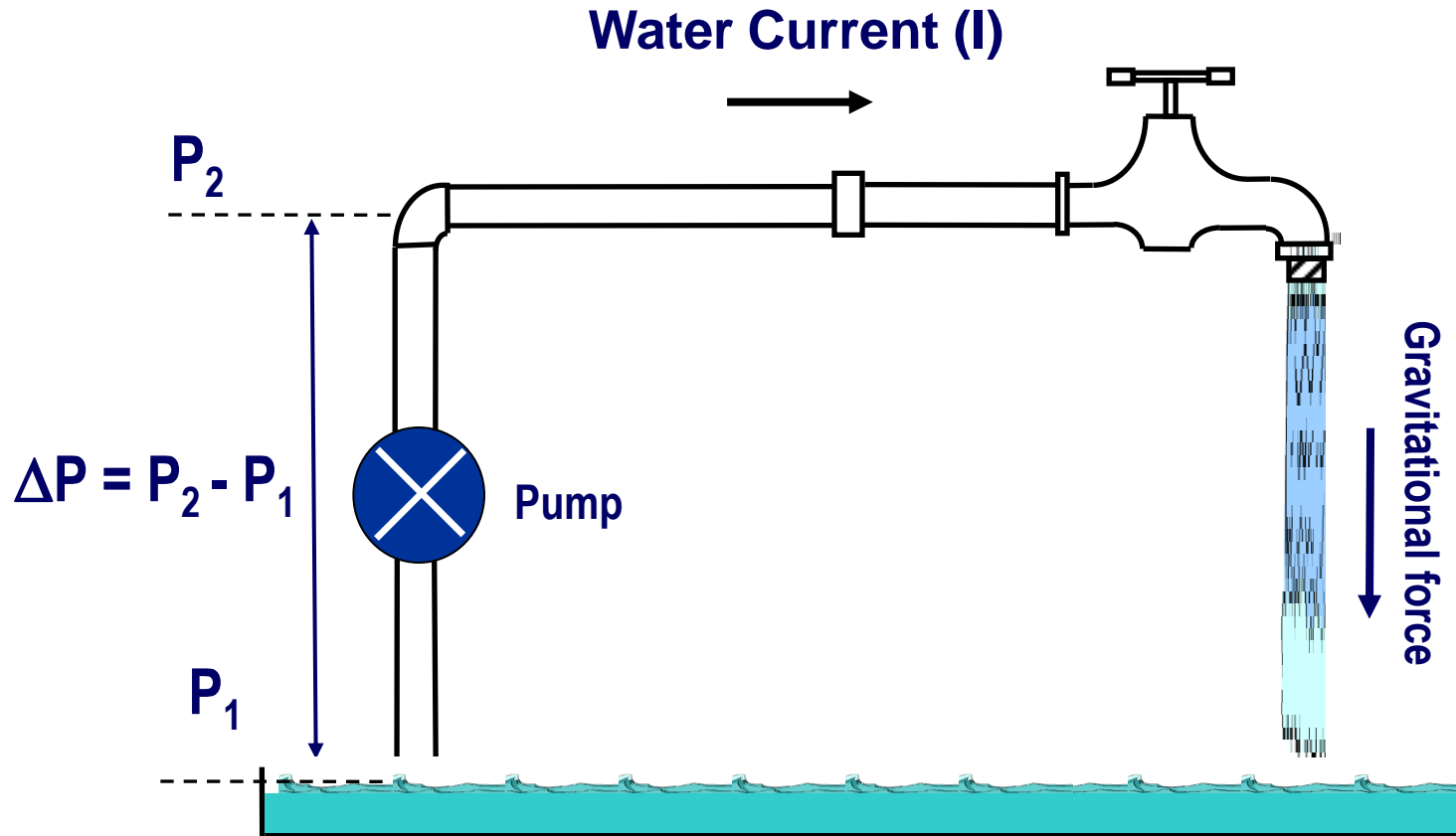

Electrical Circuit



Electrical Current (I)

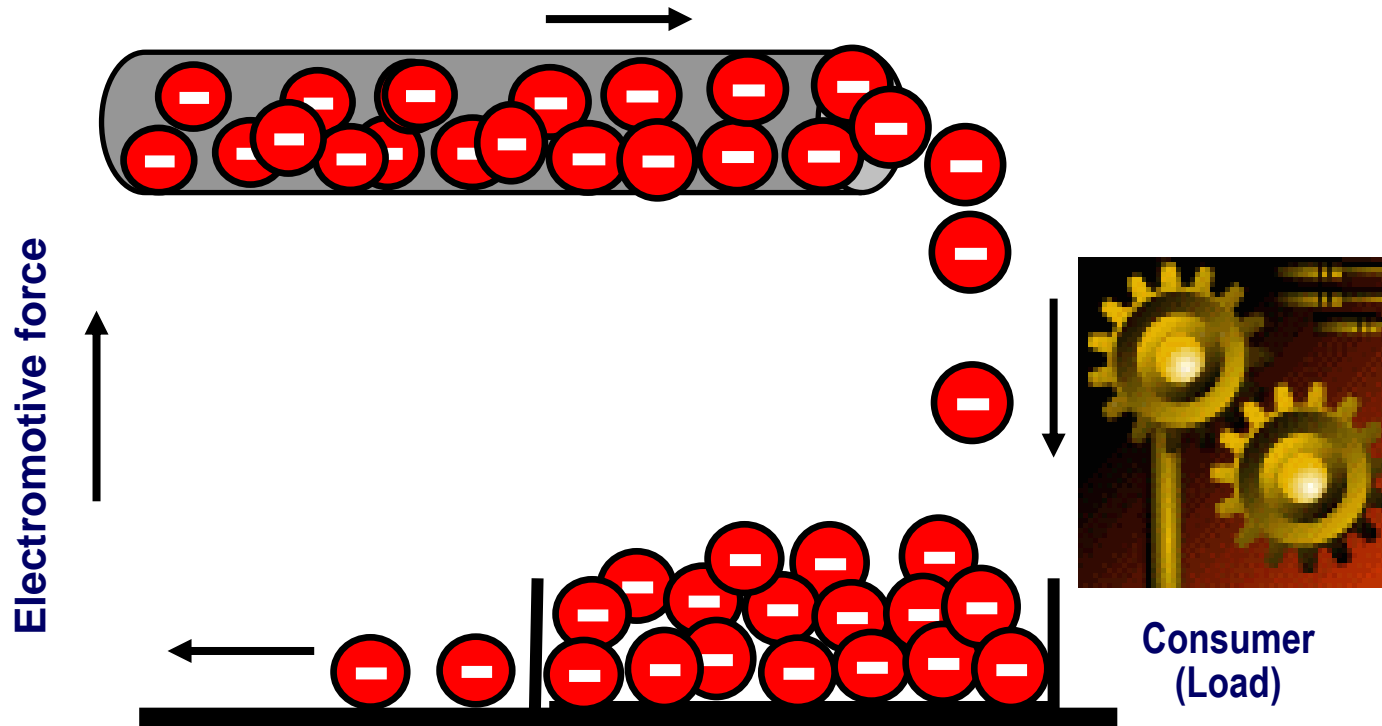

Electrical Current = No. of electrons / sec
= 1 Coulomb / sec
 6.3×10^{18} electrons / sec = 1 Amper


Electrical Circuit

Electrical Current (I)

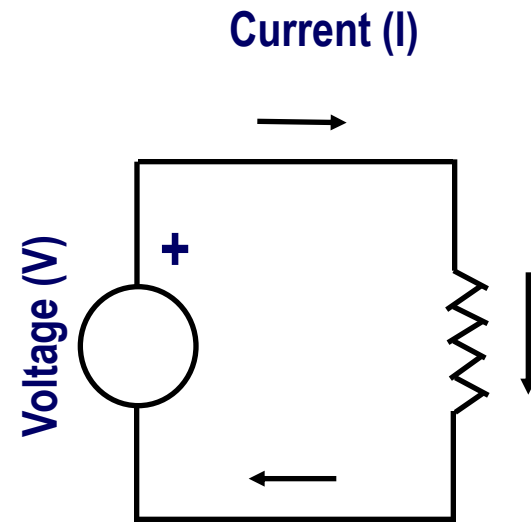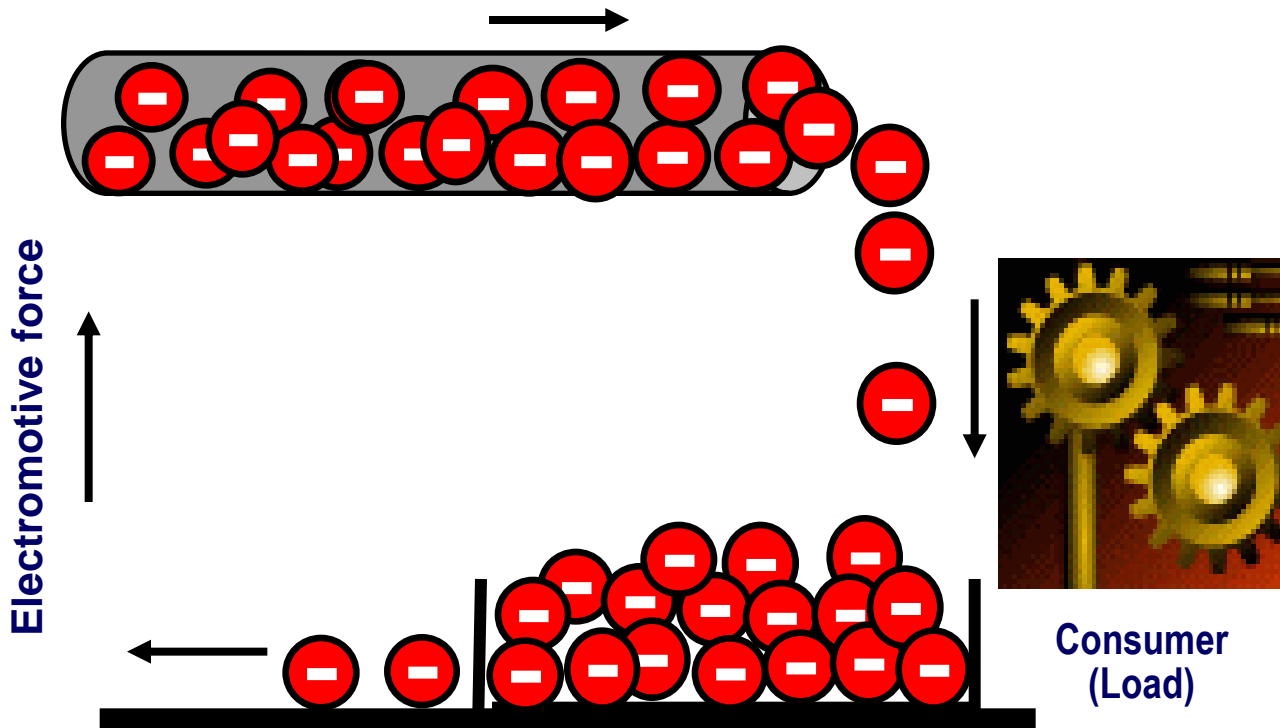


Voltage Difference

Pressure Difference

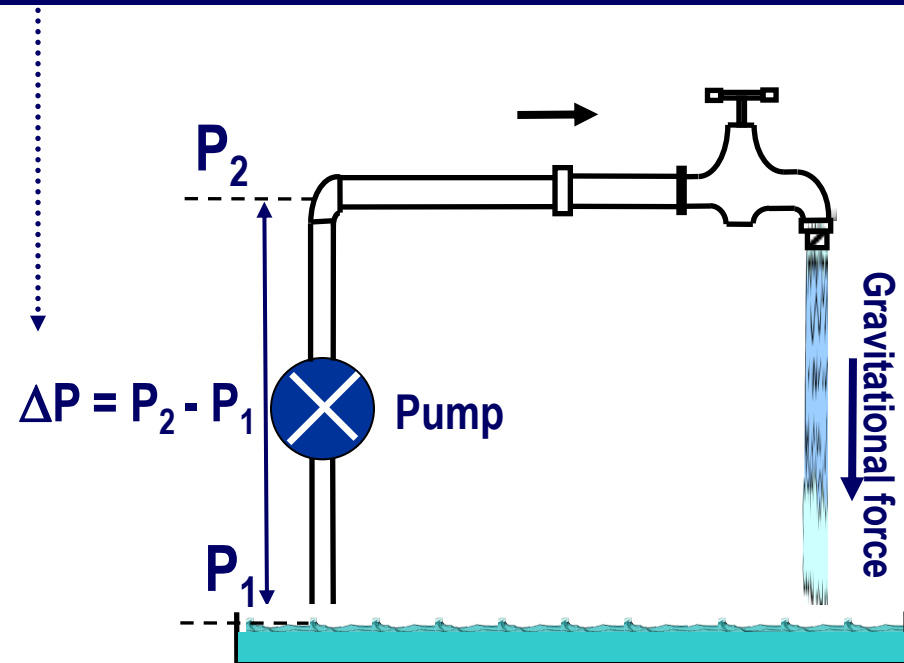

Voltage Difference

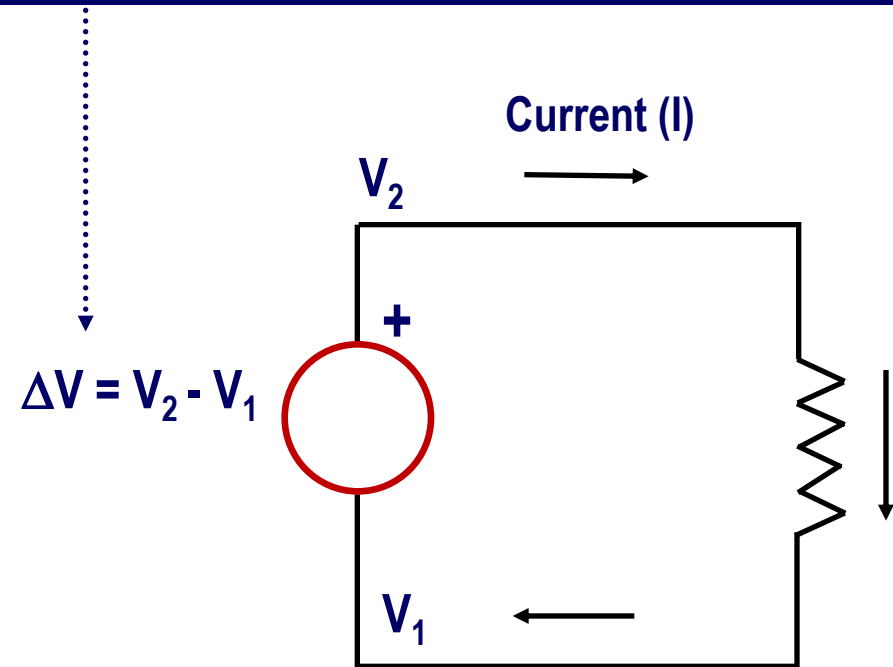

Ground Node (Earth Point)



Definition

Ground Node is the point (junction) at which the voltage is assumed to be zero

All other voltages takes their references with respect to this ground node

Representation

Ground Node

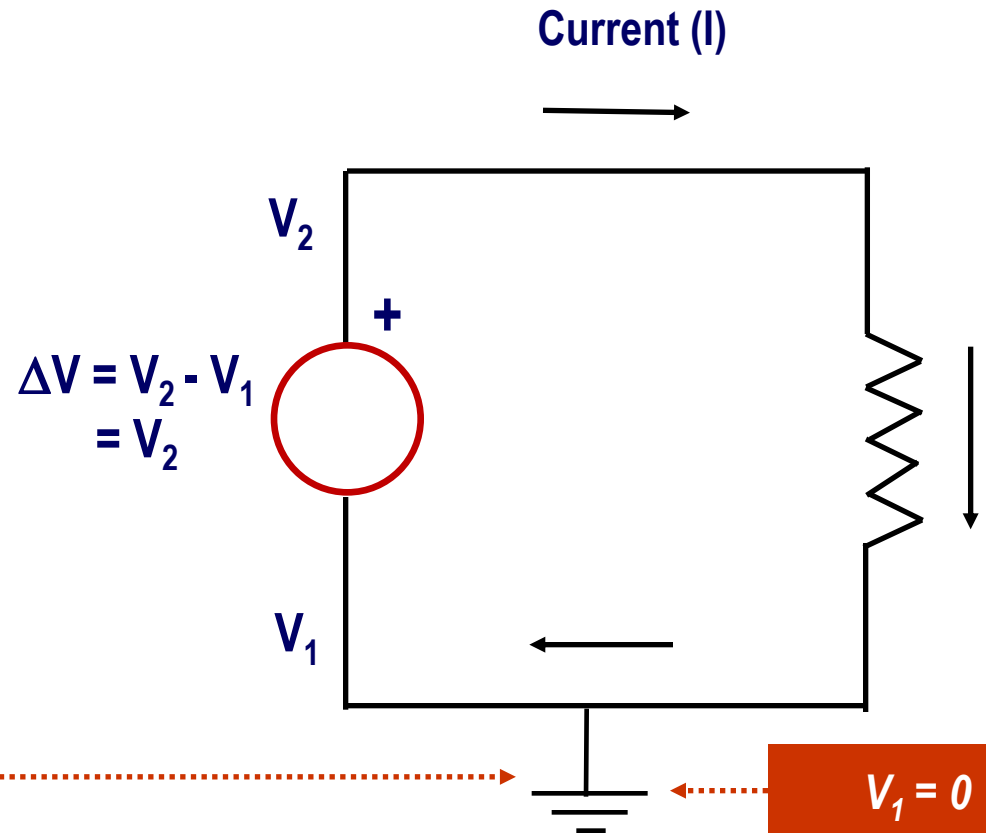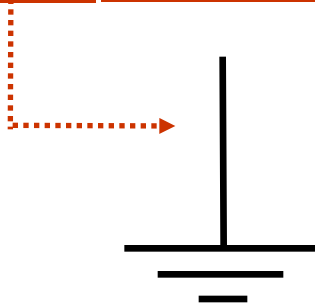


Ground Node (Earth Point)

Definition

Ground Node is the point (junction) at which the voltage is assumed to be zero

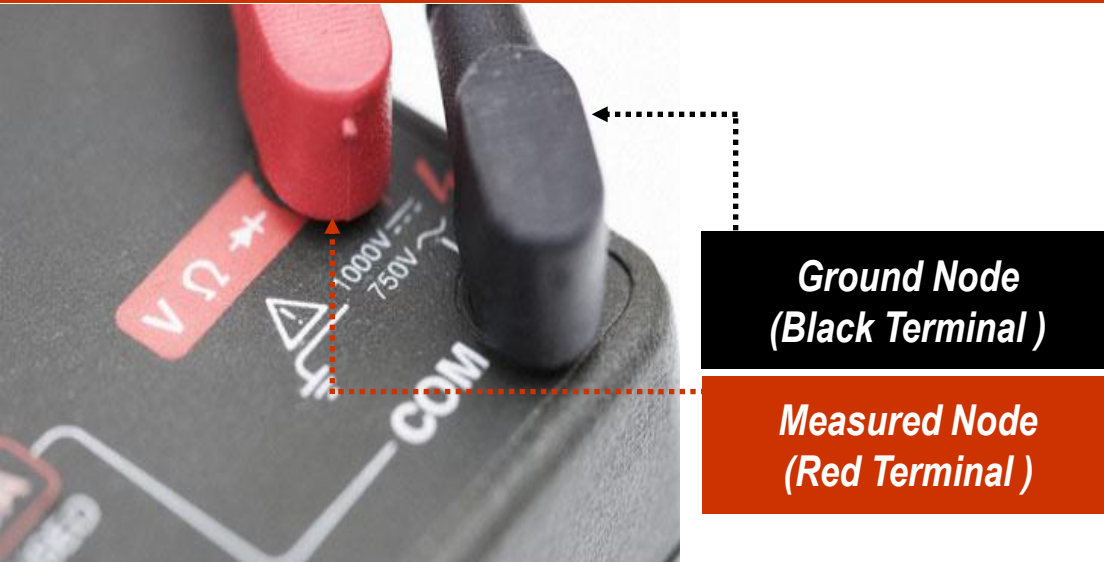All other voltages takes their references with respect to this ground node



Electrical Current


Current = no. of electrons transferred / time duration

$$I = \Delta Q / \Delta t$$

1 Amp = 1 Coulomb / 1 Seconds

Charge = Current x Time duration

$$\Delta Q = I \times \Delta t$$

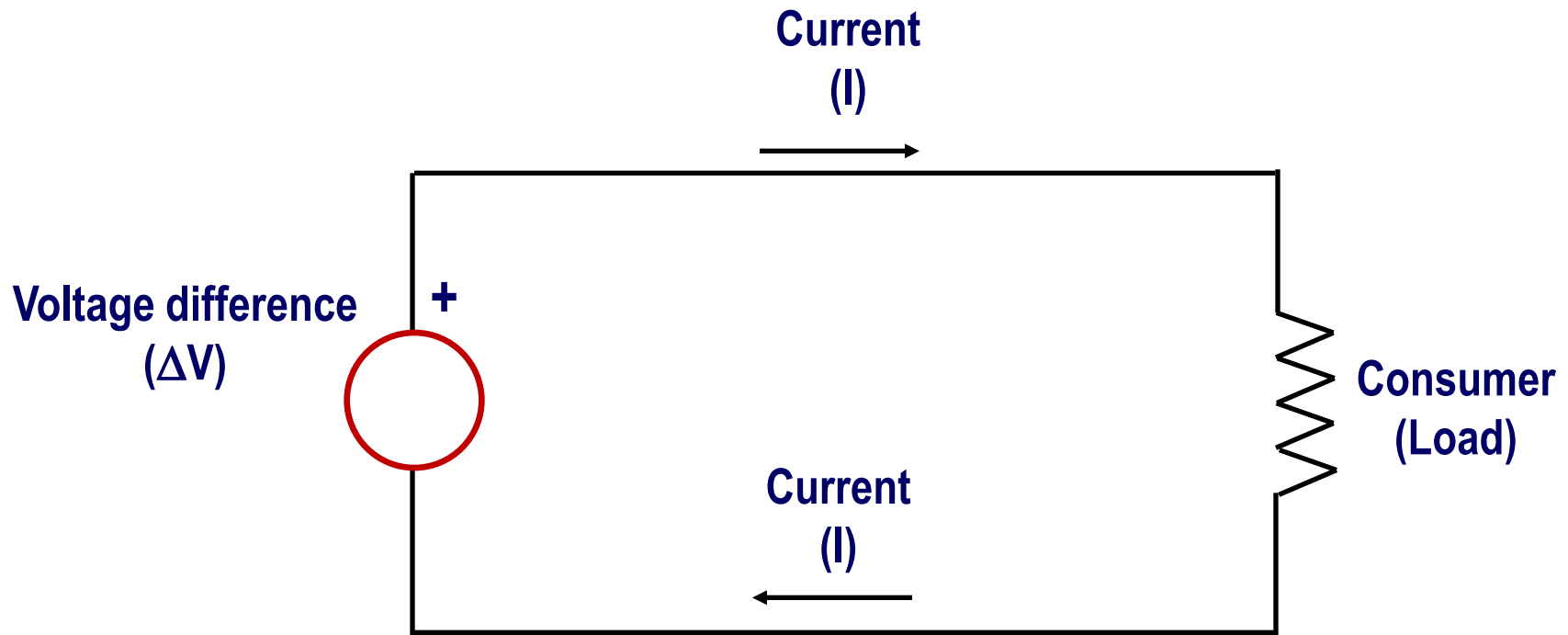

Traffic Current


Cars Flowing in a Highway




Traffic Current = Cars / minute

Water Current

Birecik Dam (672 MW)

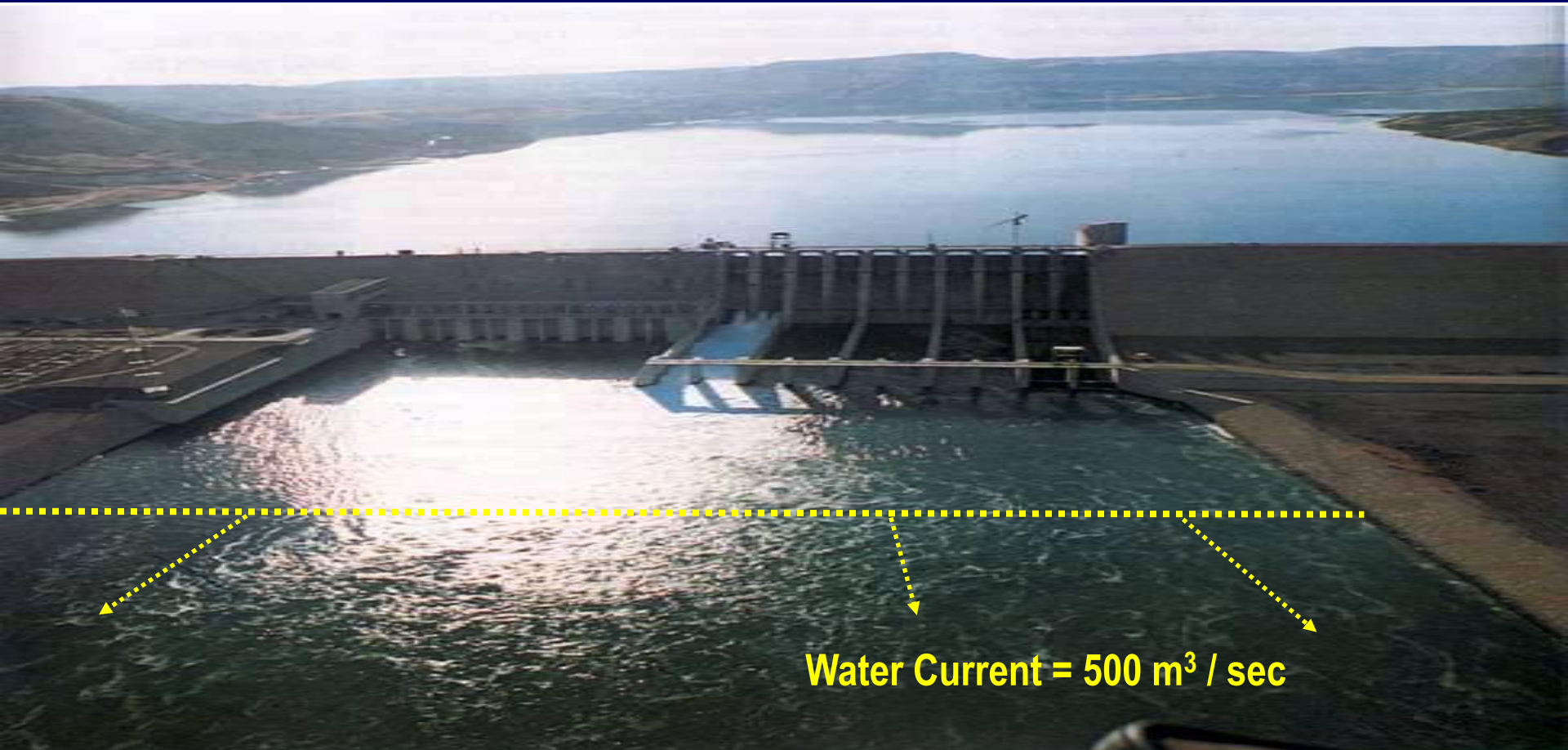

Example: Electrical Current

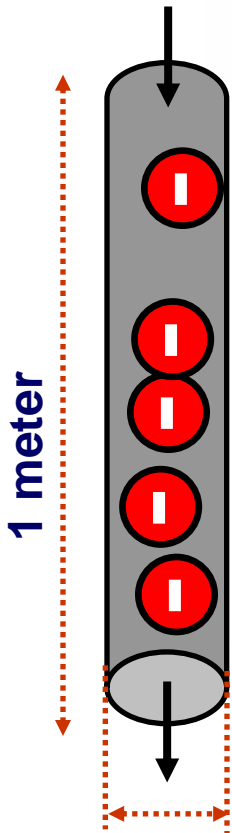

A cylindrical conductor is 1 m long and 2 mm in diameter and contains 10^{29} free carriers per cubic meter.

1. Find the total charge of the carriers in this wire.
2. If the wire is used in a circuit, find the current flowing in the wire if the average velocity of the carriers is 19.9×10^{-6} m/s.

2 mm diameter

Example: Electrical Current

Solution:

1. In order to compute the total charge contributed by the electrons, we first need to compute the volume of the conductor.

$$\text{Volume} = \text{Length} \times \text{Cross-sectional area}$$


$$= \pi r^2 L = \pi \left(\frac{2 \times 10^{-3}}{2} \right)^2 (1) \quad (1)$$

Next we compute the charge by determining the total number of charge carriers in the conductor as follows:

$$\text{Charge} = \text{Volume} \times \frac{\text{Charge}}{\text{Unit volume}}$$

$$Q = \pi \left(\frac{2 \times 10^{-3}}{2} \right)^2 (1) (-1.602 \times 10^{-19} \text{ C}) \left(10^{29} \frac{\text{carriers}}{\text{m}^3} \right)$$

$$= -50.33 \times 10^3 \text{ C}$$

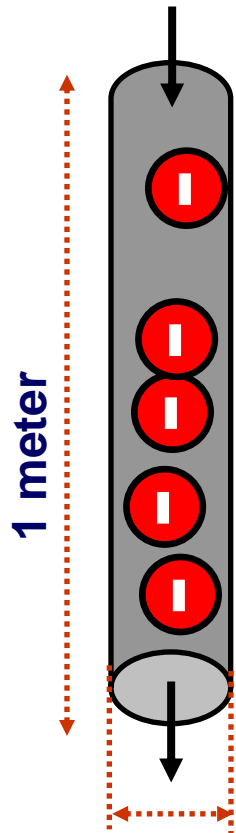


2 mm diameter

Electrical Current

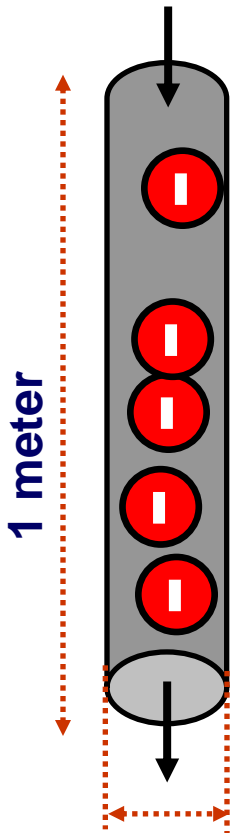
2. If the carriers move with an average velocity of 19.9×10^{-6} m/s, the magnitude of the total current flow in the wire can be computed by considering that current is the flow of charge per unit time:

$$\begin{aligned}
 \text{Current} &= \text{Charge density per unit length (C/m)} \times \text{Carrier velocity (m/s)} \\
 &= \frac{50.33 \times 10^3}{1} \times 19.9 \times 10^{-6} \\
 &= 1 \text{ A}
 \end{aligned}$$





2 mm diameter


Electrical Current - Basic Principle

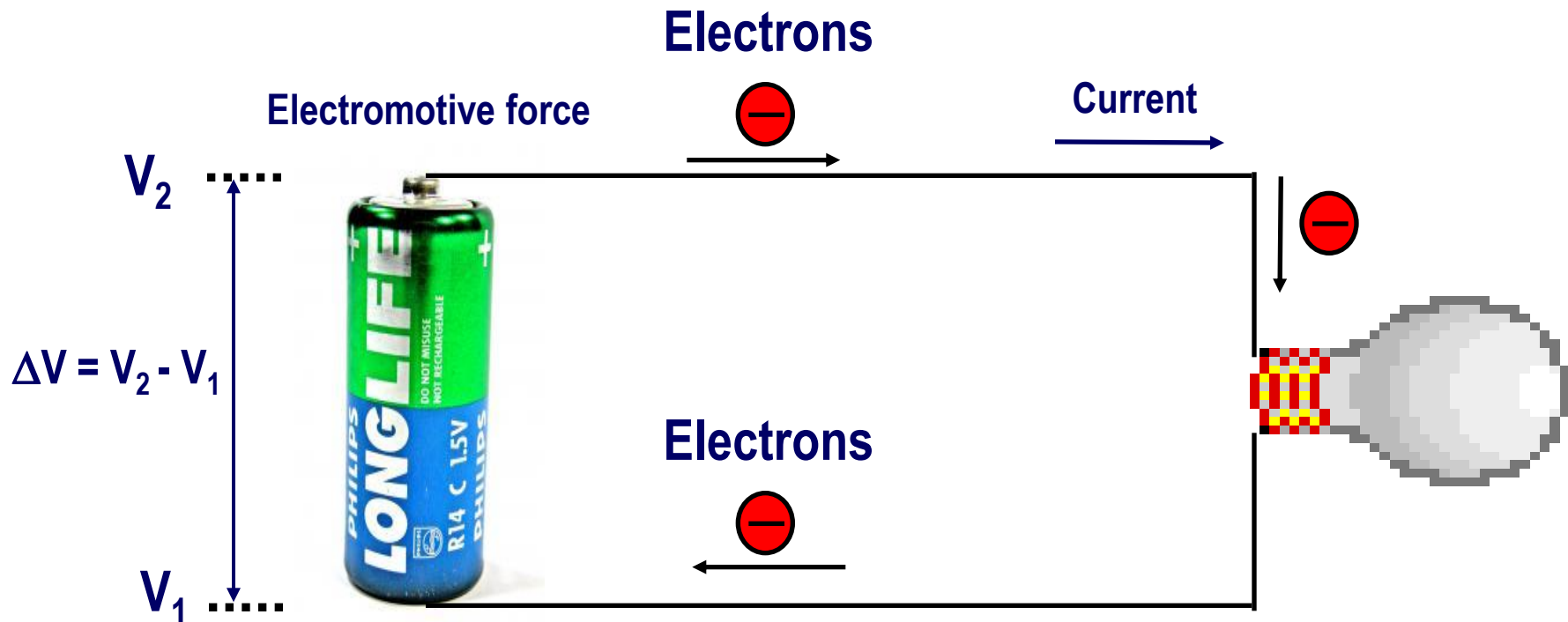

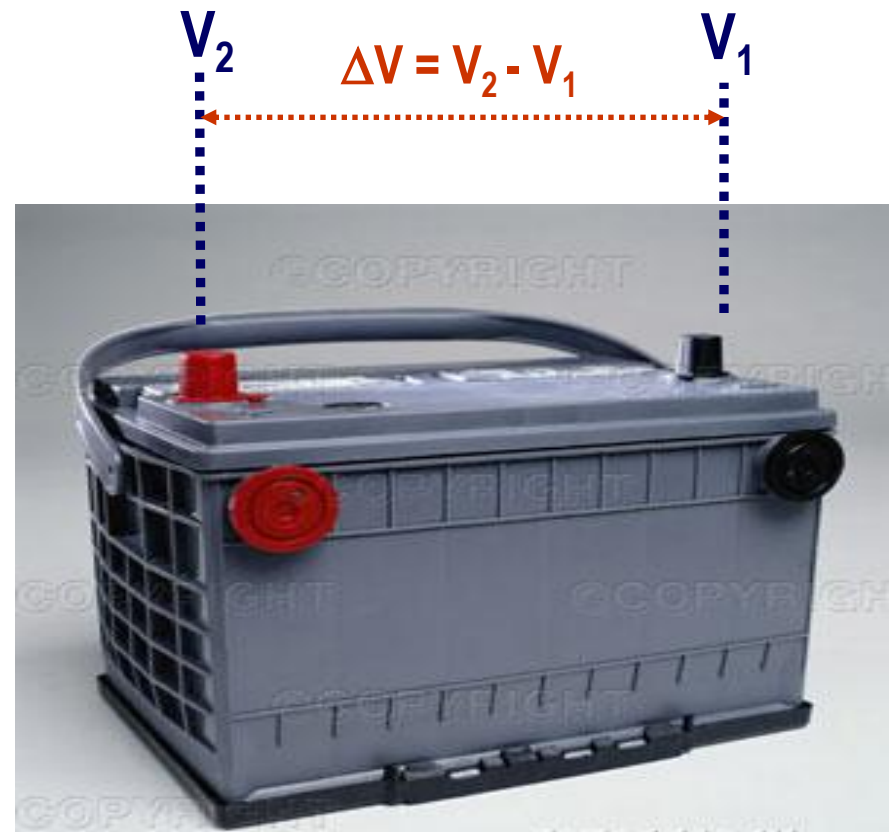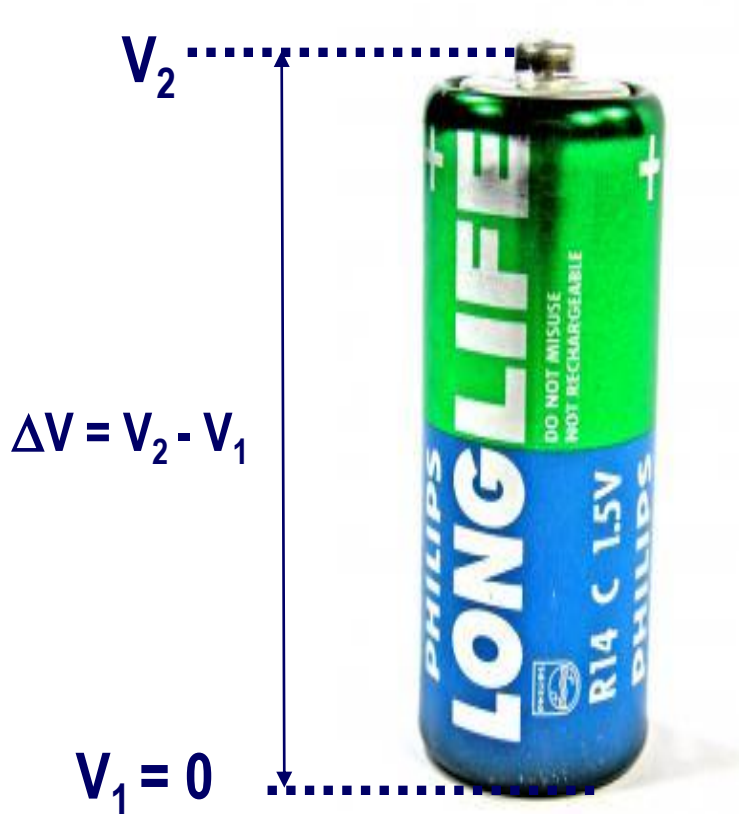Electrical Current DC (Direct Current) Sources



Simple AC Circuit

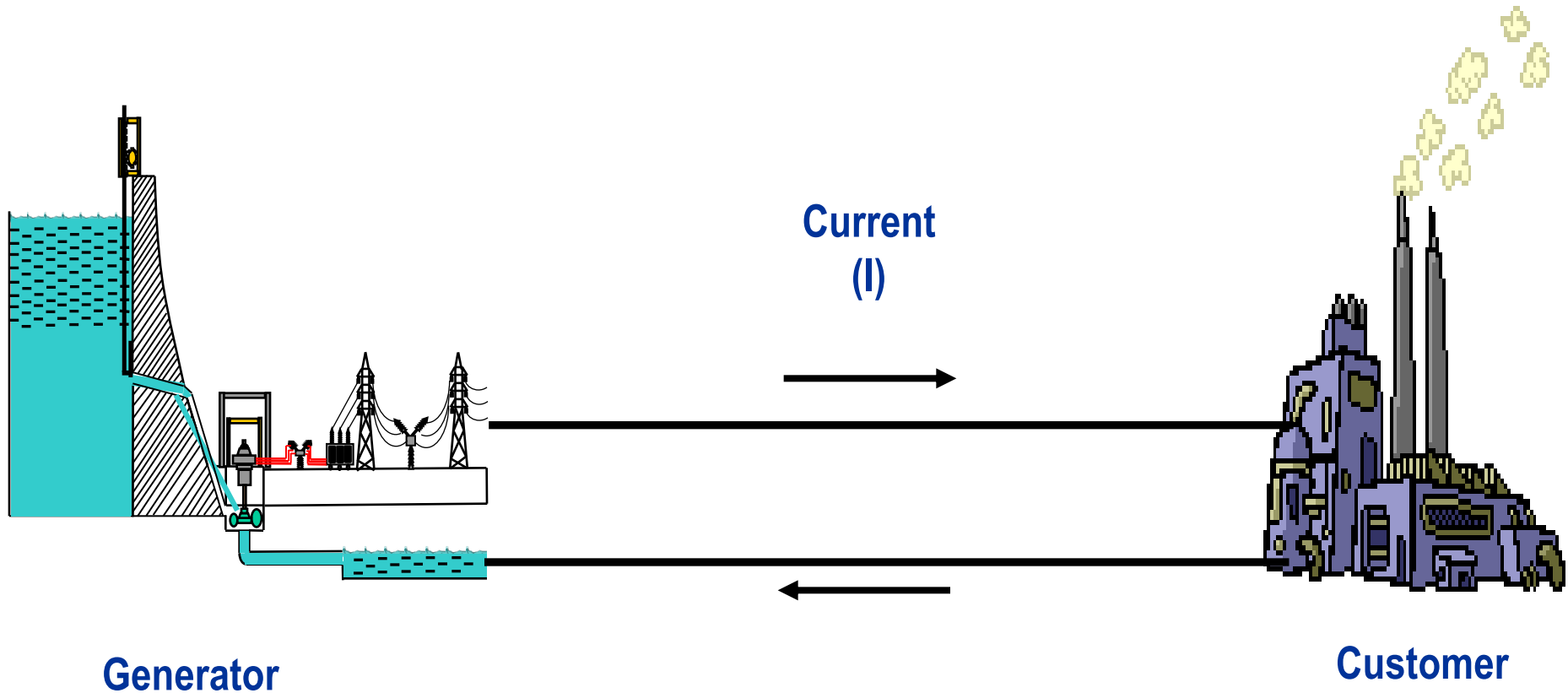

Basic Principles of Electricity

Kirchoff's Current Law (KCL)

Basic Principle

$$\Sigma \text{ Cars entering} = \Sigma \text{ Cars leaving}$$

Balance

Cars entering: 370

Cars leaving:

120


65

55


130

+

370

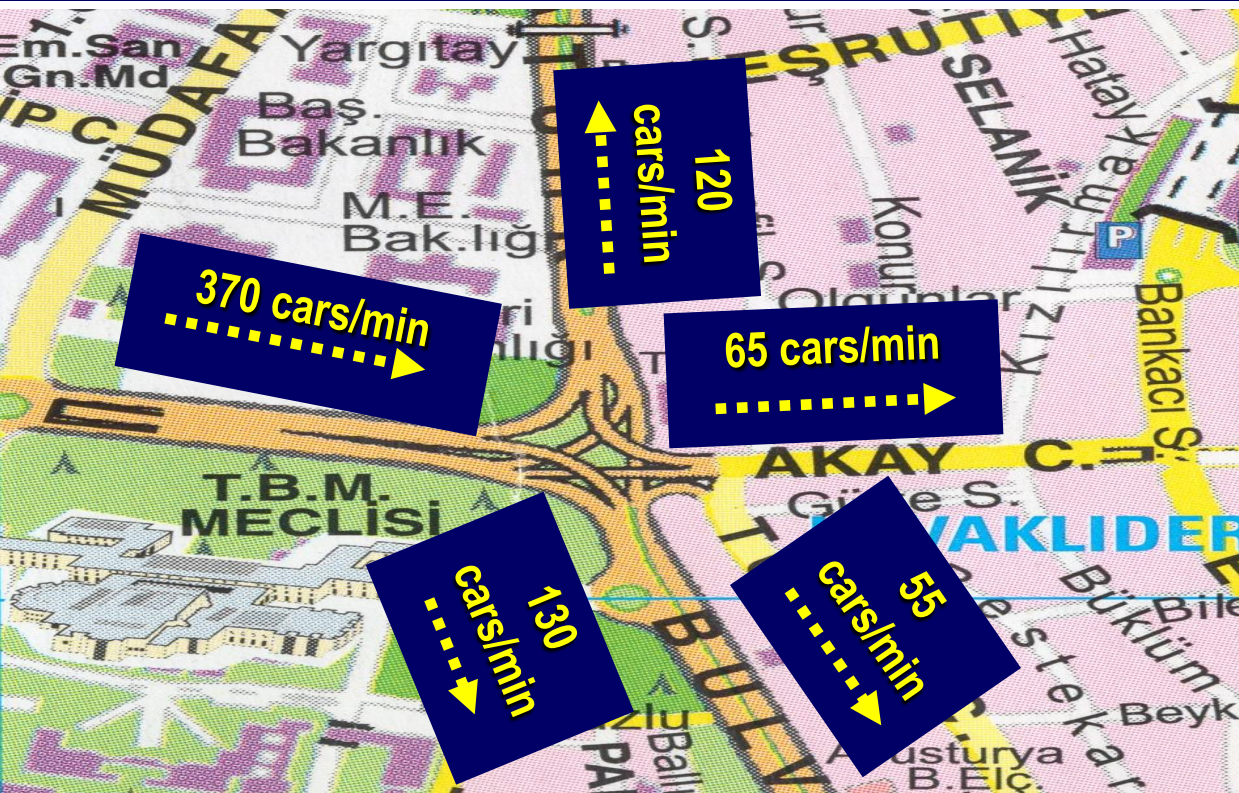

Kirchoff's Current Law (KCL)

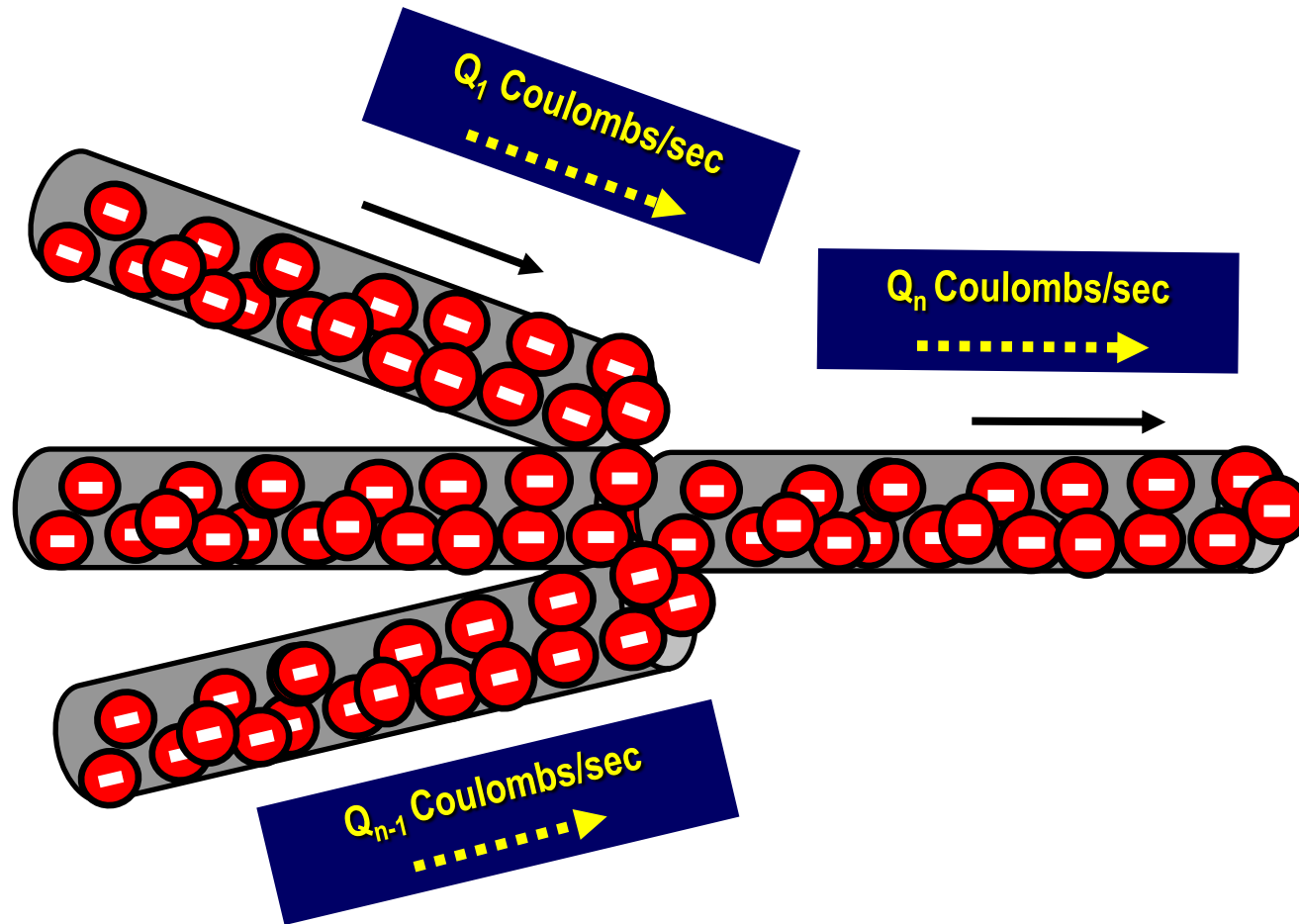

Charges entering

$$\begin{aligned}
 & Q_1 \\
 & Q_2 \\
 & Q_{n-1} \\
 & + \\
 & \text{-----} \\
 & Q_{in}
 \end{aligned}$$


Charges leaving

$$Q_{out} = Q_n$$

Balance

$$\begin{aligned}
 Q_{in} &= Q_{out} && \text{or} \\
 Q_{in} - Q_{out} &= 0 && \text{or} \\
 \sum Q &= 0
 \end{aligned}$$

Kirchoff's Current Law (KCL)

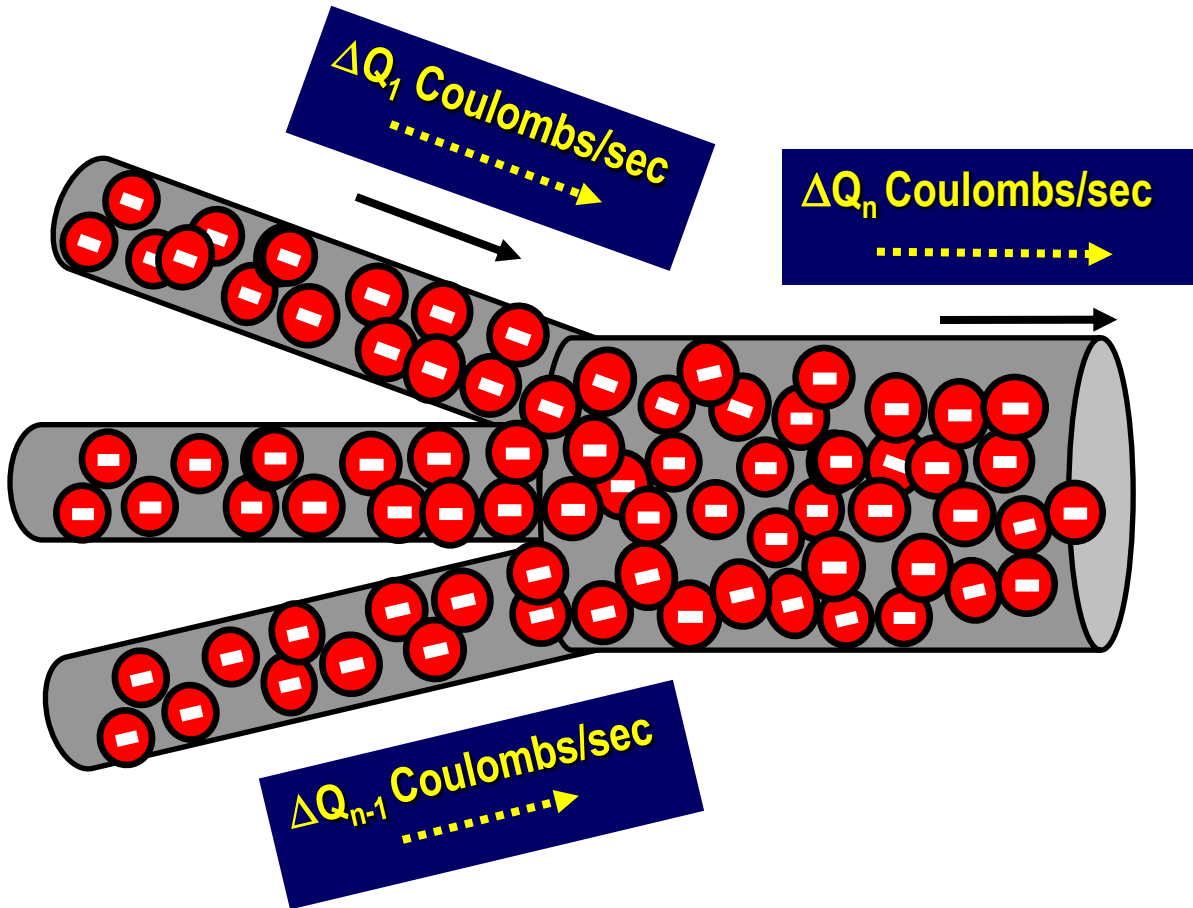

or

$$\sum \Delta Q = 0$$

or

$$\sum \Delta Q / \Delta t = 0$$

or

$$\sum_{i=1}^{i=n} I_i = 0$$

Kirchoff's First Law
 or
Kirchoffs Current Law

Mechanical Force

Definition



$$F = m \times a$$

Force needed to accelerate 1 kg of mass to 1 meter / sec² is defined as 1 Newton

$$1 \text{ Newton} = 1 \text{ kg} \times 1 \text{ meter} / \text{sec}^2$$

$$1000 \text{ Newton} = 1000 \text{ kg} \times 1 \text{ meter} / \text{sec}^2$$

Acceleration = 1 m/sec²

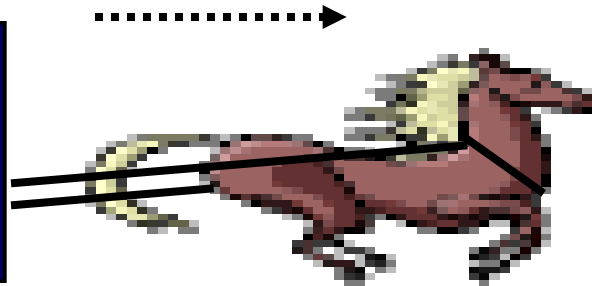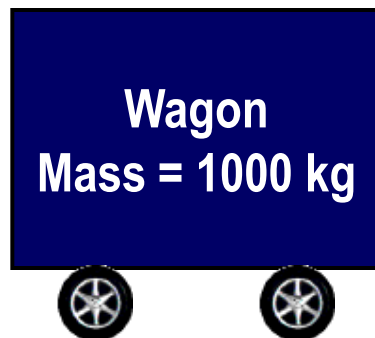

Force = 1000 Newton




Mechanical Energy

Definition

1 Joule is the energy needed to move a mass 1 meter by using 1 Newton force
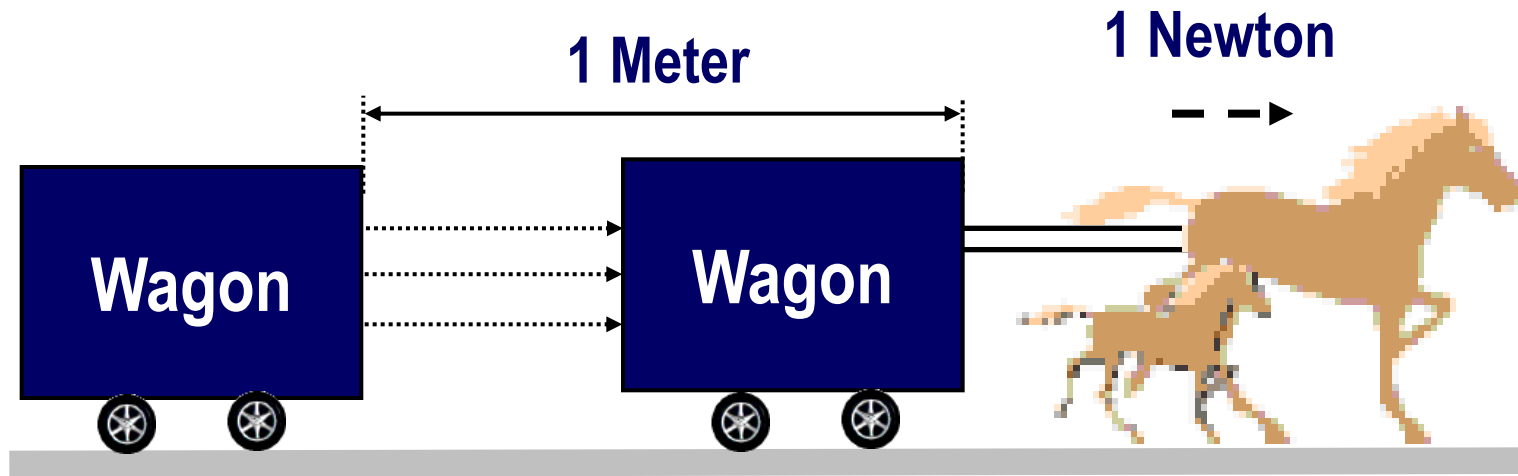
$$1 \text{ Joule} = 1 \text{ Newton} \times 1 \text{ Meter}$$



Power

Definition


Power is the work done within a certain unit of time, i.e. one second or one hour

$$\text{Power} = \text{Energy} / \text{Duration}$$


$$= 1 \text{ Joule} / \text{sec}$$

Please note that force (and hence power) of the weak horse shown below is half of the first, but the work done (energy spent) is the same, i.e.
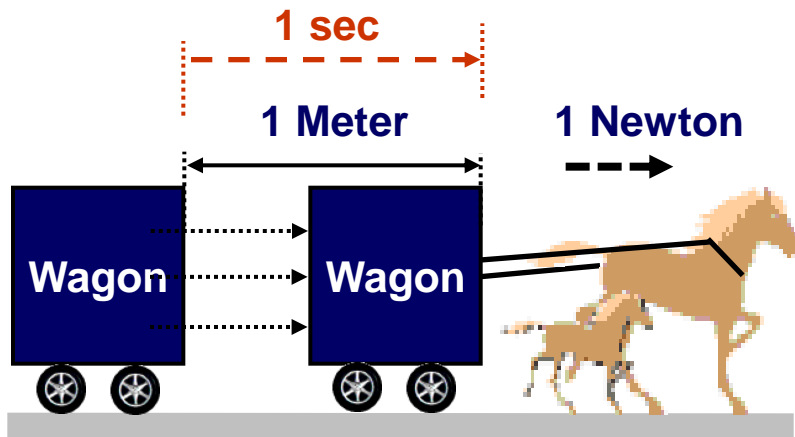
$$\text{Energy} = 2 \text{ seconds} \times 0.5 \text{ Newton} \times 1 \text{ meter}$$



Energy = 1 Joule, Power = 1 Joule / sec.

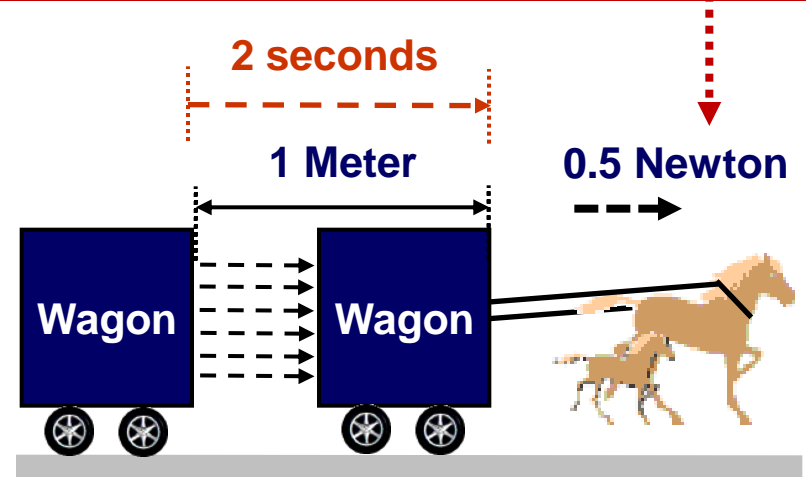

Energy = 1 Joule, Power = 1 Joule / 2 sec.


Mechanical Energy vs Electrical Energy

Equivalence


Mechanical Energy = Electrical Energy

Mechanical Work = Electrical Work

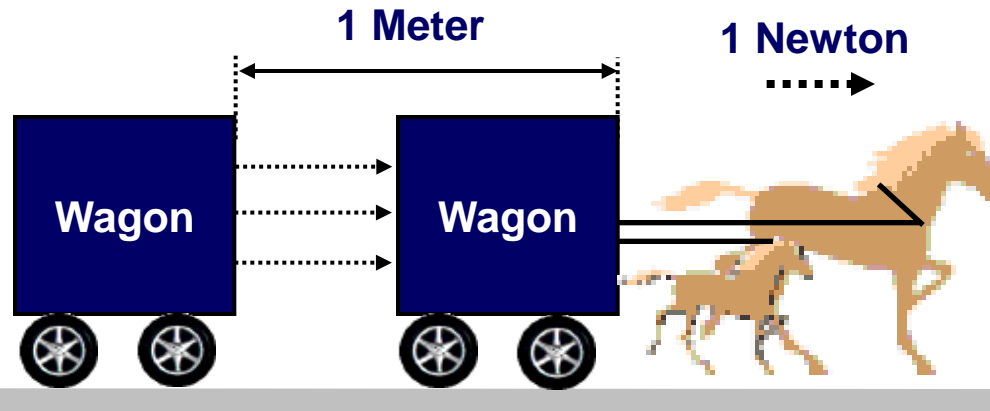The same amount of energy may be spent out by using electricity



Mechanical Energy (Work) = 1 Joule

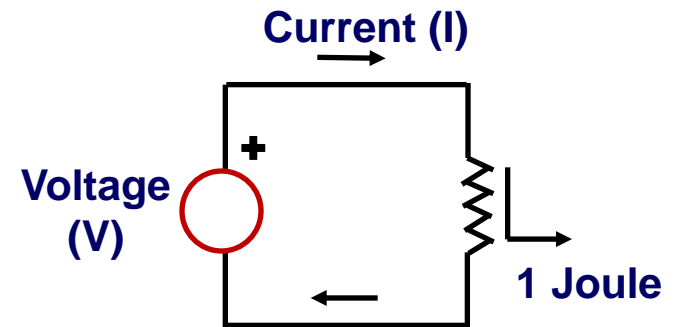


Electrical Energy (Work) = 1 Joule

Electrical Power


Definition

Similar to mechanical power, electrical power is the work done within a certain unit of time, i.e. one second or one hour
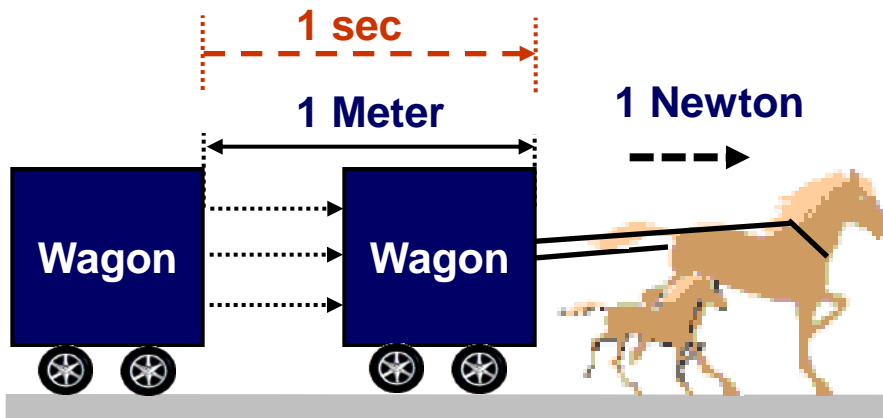
$$\text{Electrical Power} = \text{Electrical Energy} / \text{Duration} \\ = 1 \text{ Joule} / \text{sec}$$



Mechanical Power = 1 Joule / sec.

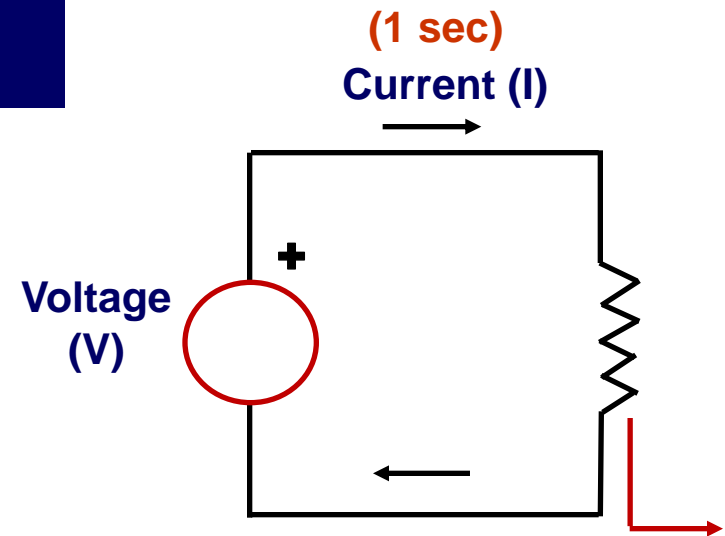


Electrical Power = 1 Joule / sec.


Equivalence of Mechanical and Electrical Powers

Equivalence

Mechanical Power = Electrical Power

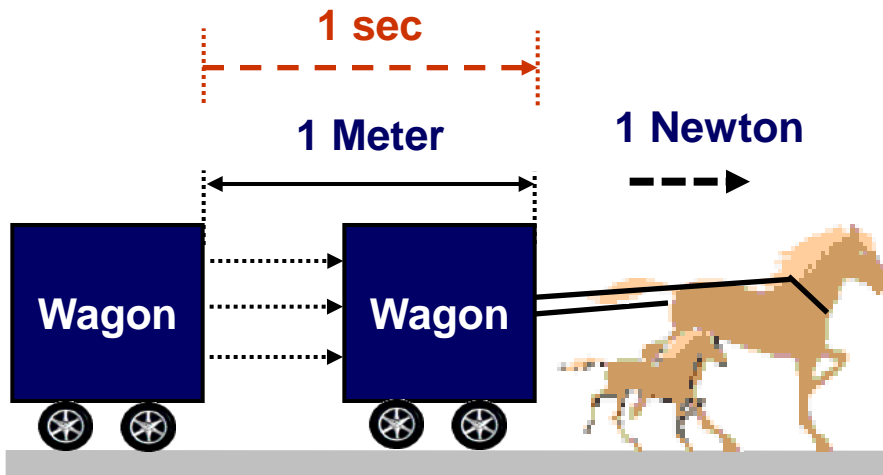

Mechanical Power = 1 Joule / sec.

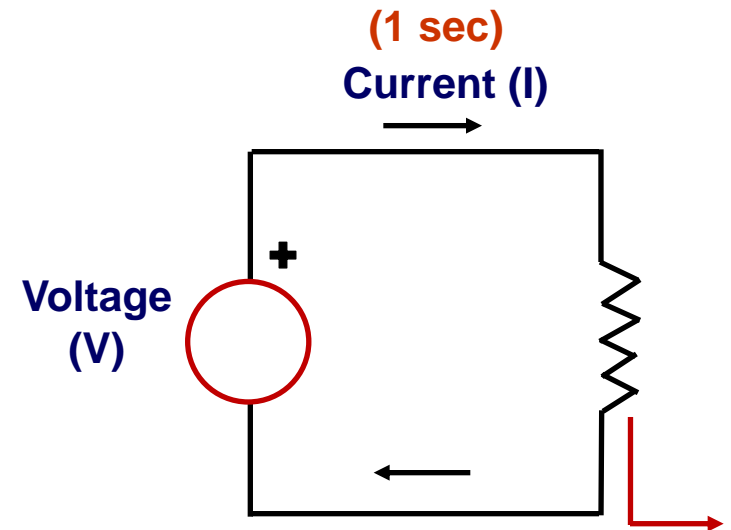

Electrical Power = 1 Joule / sec.


Electrical Power

Definition


$$1 \text{ Joule} = 1 \text{ Watt} \times \text{second}$$

$$1 \text{ Horse Power} = 746 \text{ Watts} \\ = 0.746 \text{ kWatt}$$

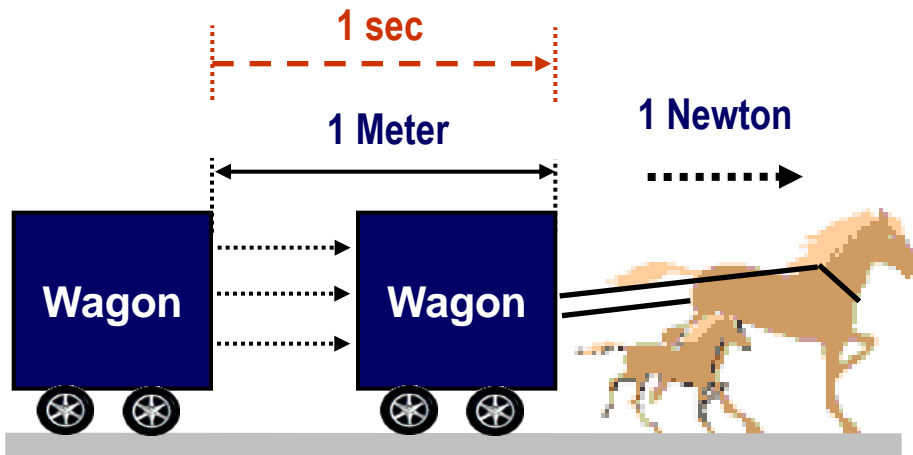1 Joule / second = 1 Watt
(1 Joule energy is spent within 1 second)


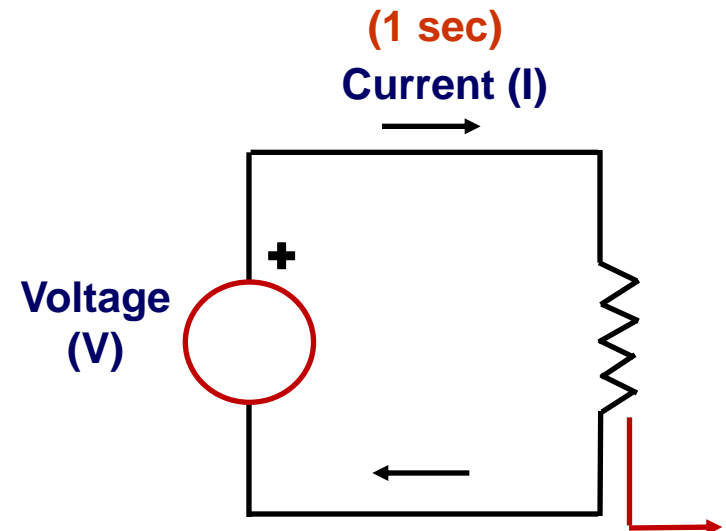
$$1 \text{ Joule} / \text{sec} = 1 \text{ Watt}$$



$$\text{Electrical Power} = 1 \text{ Joule} / \text{sec.} = 1 \text{ Watt}$$


Electrical Power

Definition

$$P = V \times I$$

(Watt) = (Volt) x (Amp)

$$Power = Voltage \times Current$$

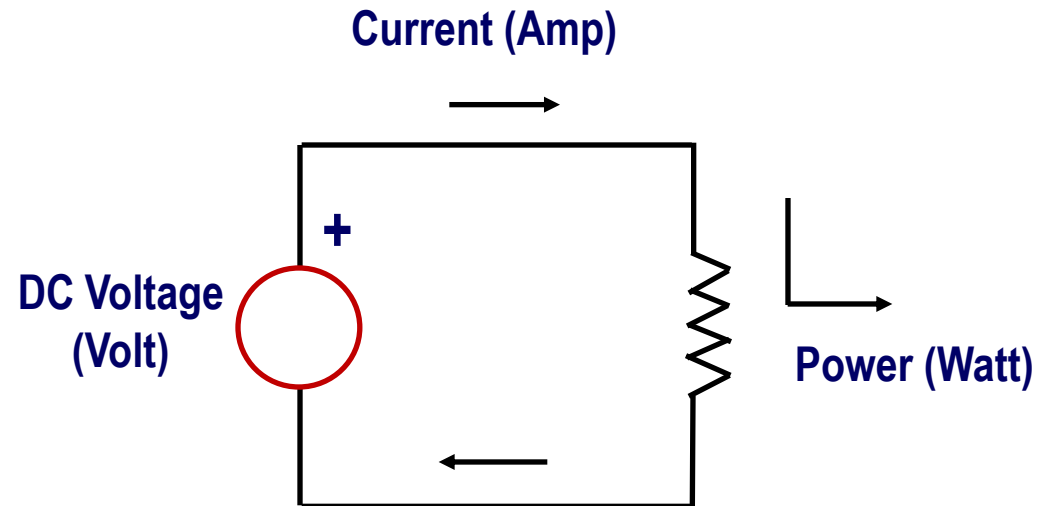

Voltage

Definition

Power = Voltage x Current


or

$$P = V \times I$$

Voltage = Power / Current

or

$$V = P / I$$

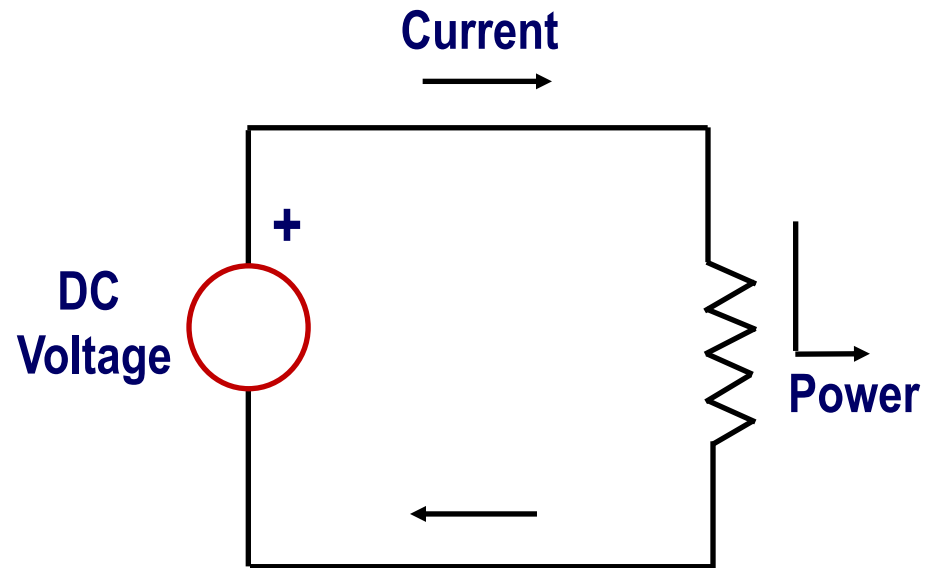

Voltage

Definition

$$\text{Power} = \text{Voltage} \times \text{Current}$$


or

$$\text{Voltage} = \text{Power} / \text{Current}$$

or

$$V = P / I$$

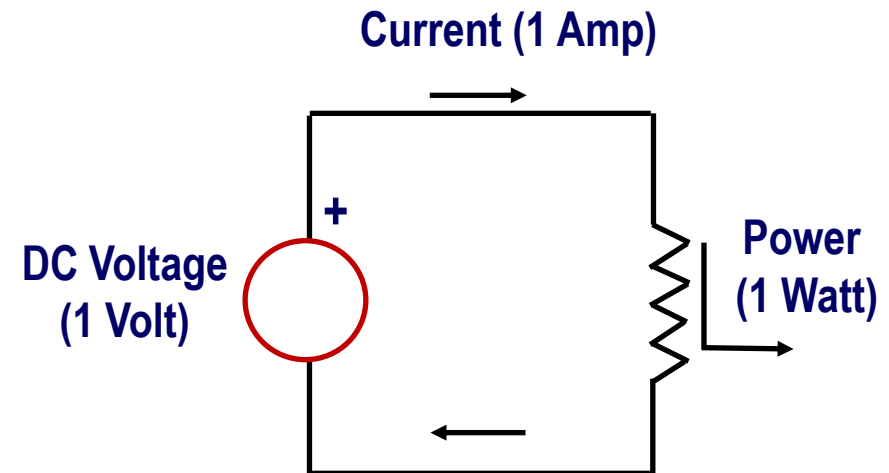
$$\underline{1 \text{ Volt} = 1 \text{ Watt} / 1 \text{ Amp}}$$



Electrical Energy

Definition
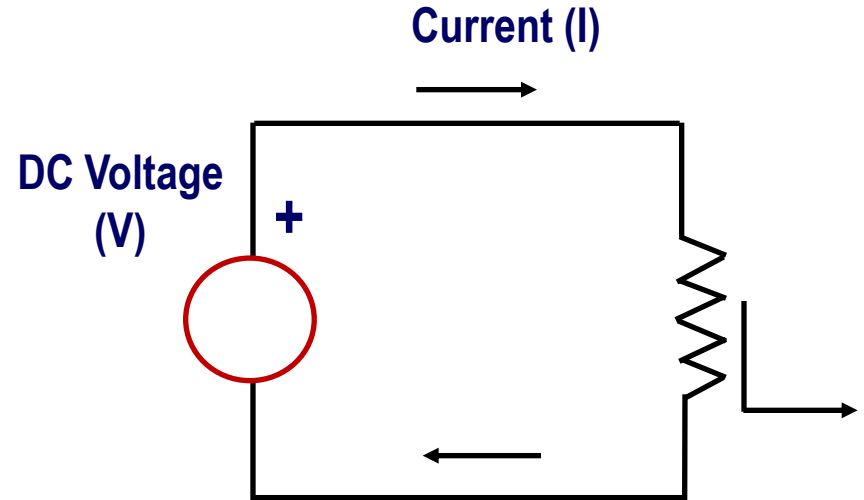
$$\begin{array}{l} \text{Energy} = \text{Power} \times \text{Time} \\ (\text{Watt-sec}) \quad (\text{Watt}) \quad (\text{second}) \end{array}$$



$$\text{Energy} = \text{Power} \times \text{Time}$$

Unit of Electrical Energy

Definition

$$\text{Energy} = \text{Power} \times \text{Time}$$

(Watt-sec) (Watt) (second)

$$\text{Energy} = \text{Power} \times \text{Time}$$

(KiloWatt-hour) (KiloWatt) (hour)

x 1000

x 1000


x 3600

$$1 \text{ KiloWatt - hour} = 1000 \times 3600 \text{ Watt} \times \text{seconds}$$

$$= 3\,600\,000 \text{ Joules}$$

$$1 \text{ KiloWatt} = 1000 \text{ Watts}$$
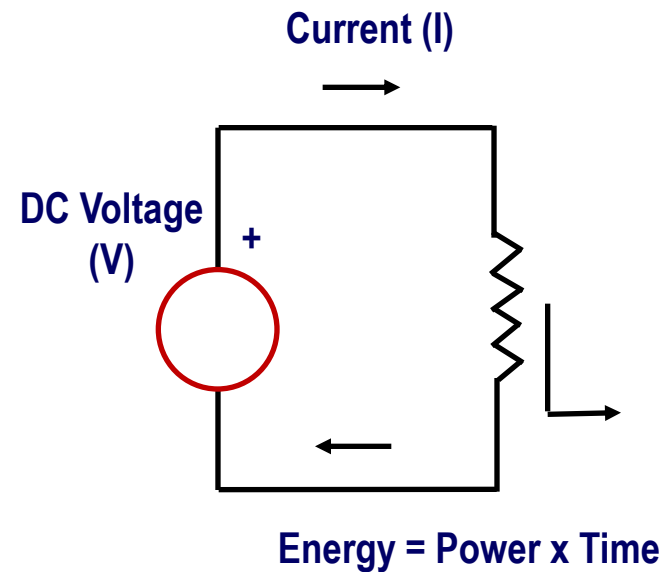
$$1 \text{ Hour} = 3600 \text{ seconds}$$



Electrical Energy

Example

Calculate the monthly payment for the energy consumed by the lamp shown on the RHS

Source voltage is 220 Volt

Current drawn by the lamp is 5 Amp

Price of electrical energy is 12 Cents / kWh

$$\text{Power} = \text{Voltage} \times \text{Current}$$

$$P = V \times I$$

$$P = 220 \times 5 = 1100 \text{ Watts}$$

$$\text{Energy} = P \times \Delta t$$

$$= 1100 \text{ Watts} \times (24 \text{ hours / day} \times 30 \text{ days/month})$$


$$= 792000 \text{ Watt hours} = 790.2 \text{ kWh}$$

$$\text{Monthly payment} = 790.2 \times 12 \text{ Cents / month}$$

$$= 90.504 \text{ USD} = 122.1 \text{ YTL / month}$$



$V = 220 \text{ V}$

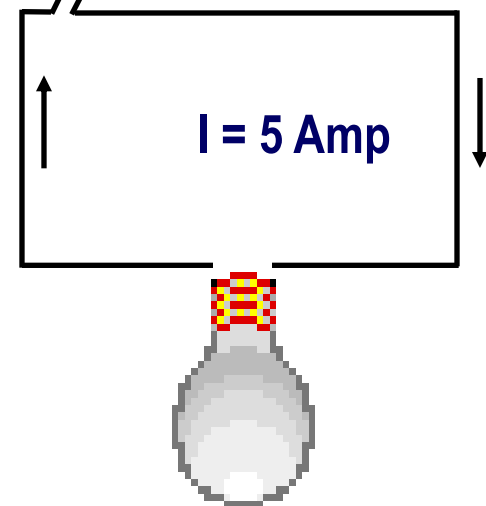


Alternative Definition of Voltage

$$\begin{aligned} 1 \text{ Volt} &= 1 \text{ Watt} / 1 \text{ Amp} \\ &= (1 \text{ Joule} / \text{sec}) / 1 \text{ Amp} \\ &= 1 \text{ Joule} / (1 \text{ Amp} \times \text{sec}) \\ &= 1 \text{ Joule} / 1 \text{ Coulomb} (*) \end{aligned}$$

(*) Remember that $1 \text{ Amp} = 1 \text{ Coulomb} / 1 \text{ sec}$

1 Volt is the voltage needed;

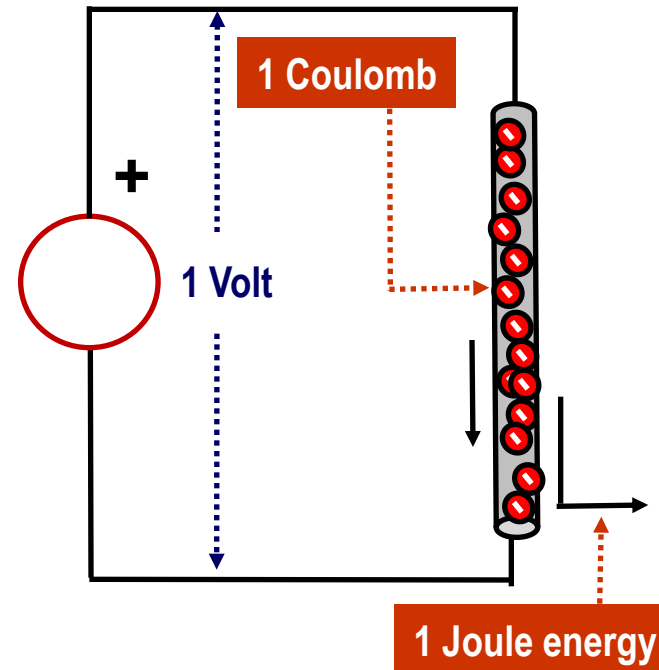- to move 1 Coulomb of electrical charge,
- to spend 1 Joule of energy for this movement in a conductor



Alternative Definition of Voltage

$$1 \text{ Volt} = 1 \text{ Joule} / 1 \text{ Coulomb}$$

Please note that time parameter does not appear in the above equation, implying that it is arbitrary

Case-1

Let $t = 1 \text{ sec}$

Then, $I = 1 \text{ Coulomb} / 1 \text{ sec} = 1 \text{ Amp}$

$$P = V \times I = 1 \text{ Volt} \times 1 \text{ Amp} = 1 \text{ Watt}$$

$$\text{Energy} = P \times t = (1 \text{ Joule} / \text{sec}) \times \text{sec} = 1 \text{ Joule}$$

Case-2


Let now $t = 2 \text{ sec}$

Then, $I = 1 \text{ Coulomb} / 2 \text{ sec} = 0.5 \text{ Amp}$

$$P = V \times I = 1 \text{ Volt} \times 0.5 \text{ Amp} = 0.5 \text{ Watt}$$

$$= \text{Energy} / 2 = 0.5 \text{ Joule} / \text{sec}$$
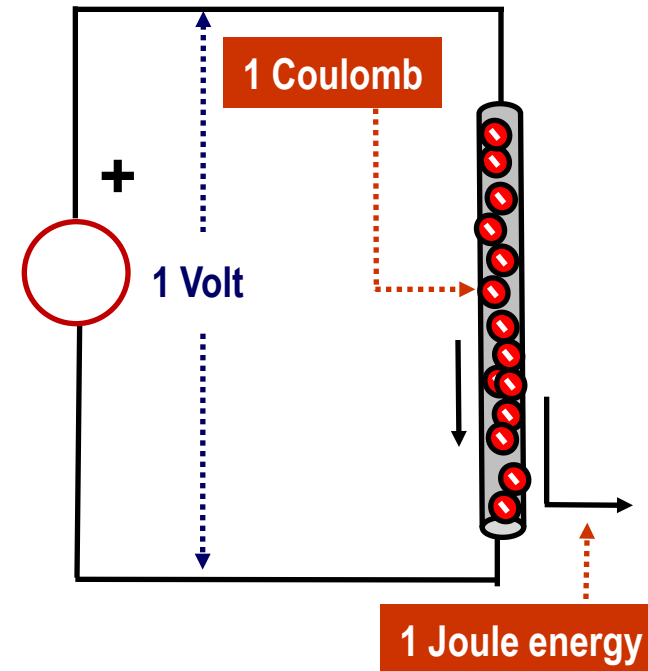
$$\text{Energy} = P \times t = 0.5 \times 2 = 1 \text{ Joule} \quad \text{again}$$



Resistance



Definition

Resistance is the reaction of a pipe against water flow

Resistance R_1

$R_1 > R_2$

Resistance R_2

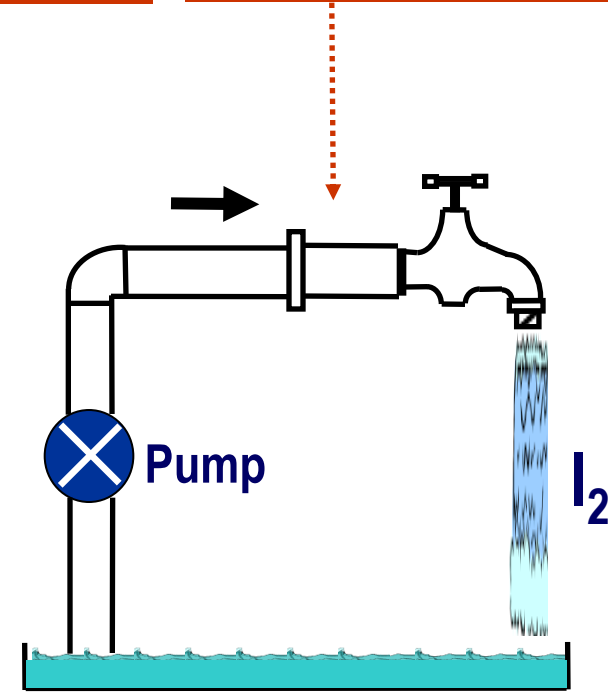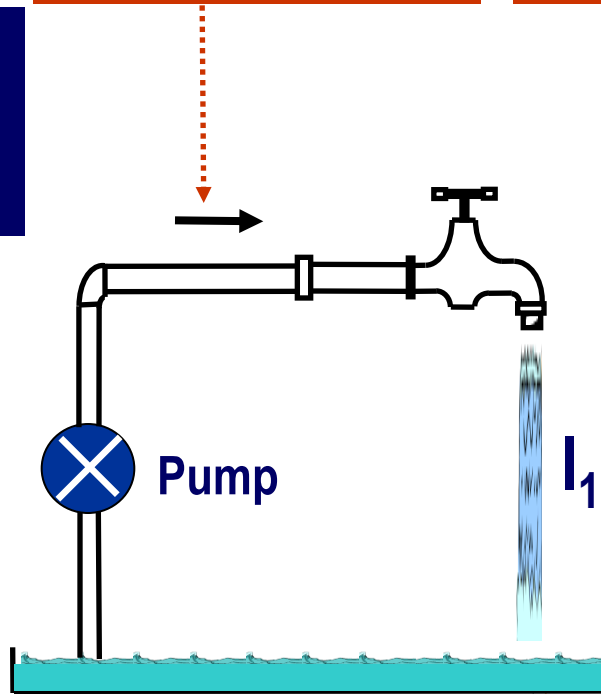

Current I_1

$I_2 > I_1$

Current I_2

Resistance

Definition

Resistance is the reaction of a conductor against electrical current



Resistance R_1
Current I_1



$$R_1 > R_2$$

Resistance R_2
Current I_1




$$I_1 < I_2$$

Ohm Law

Basic Principles

Current flowing in the circuit is;

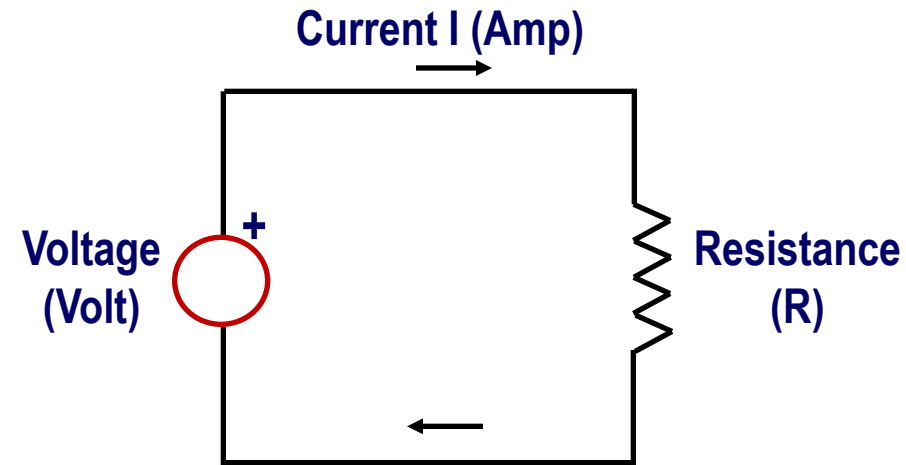- proportional to voltage,
- inversely proportional to resistance



Hence

Unit of resistance is Ohm

1 Ohm is the resistance that allows 1 Amper to pass at 1 Volts voltage;

1 Ohm = 1 Volt / 1 Amper

$$I = V / R$$

(Amp) (Volt) (Ohm)

or

$$V = R \times I$$

(Volt) (Ohm) (Amp)

Ohm Law


Two circuits with different Resistances, identical voltage sources

Resistance R_1


$R_1 > R_2$

Resistance R_2

Current (I_1)

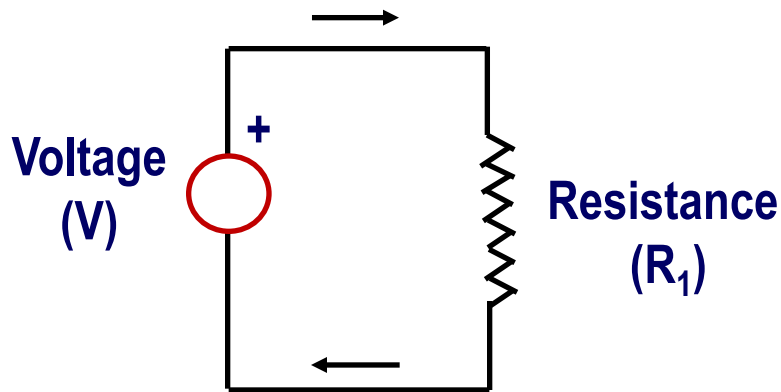

Current (I_2)

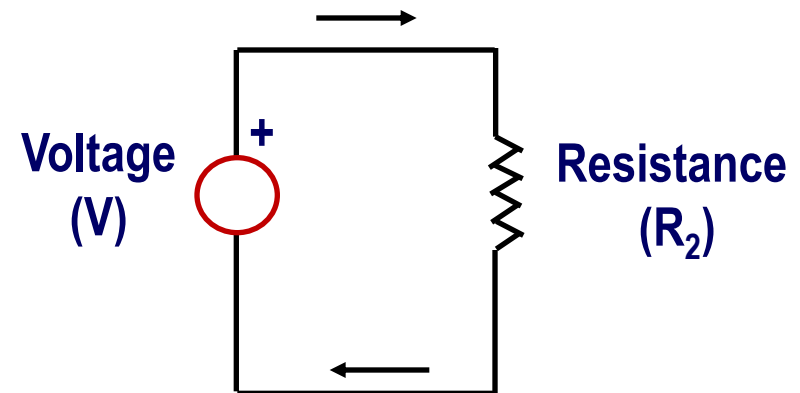


$$V/R_1 = I_1$$

$$I_1 < I_2$$

$$V/R_2 = I_2$$


Basic Principles of Electricity

Ohm Law V-I Characteristics

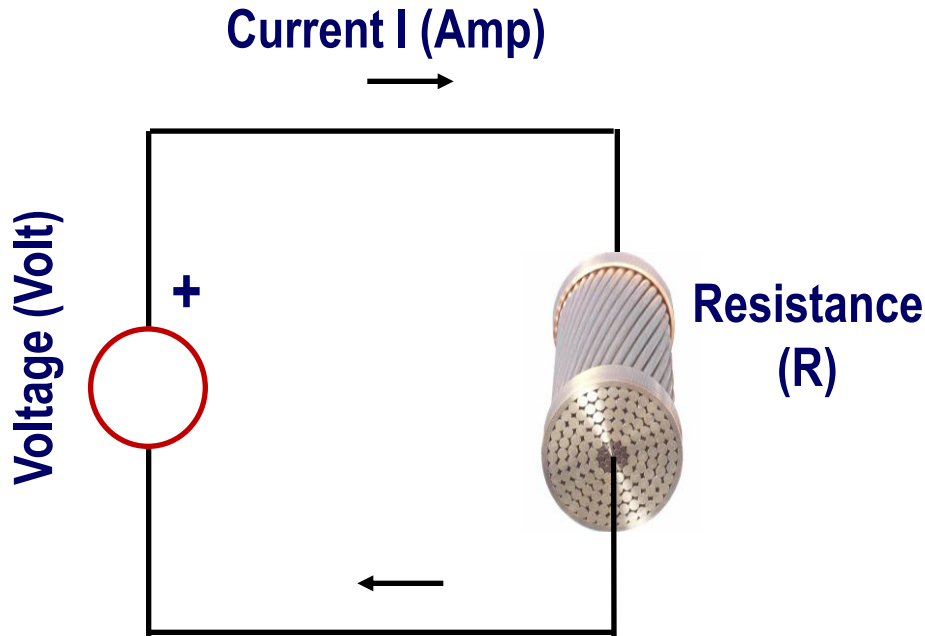

$$V = R \times I$$

(Volt) (Ohm) (Amp)

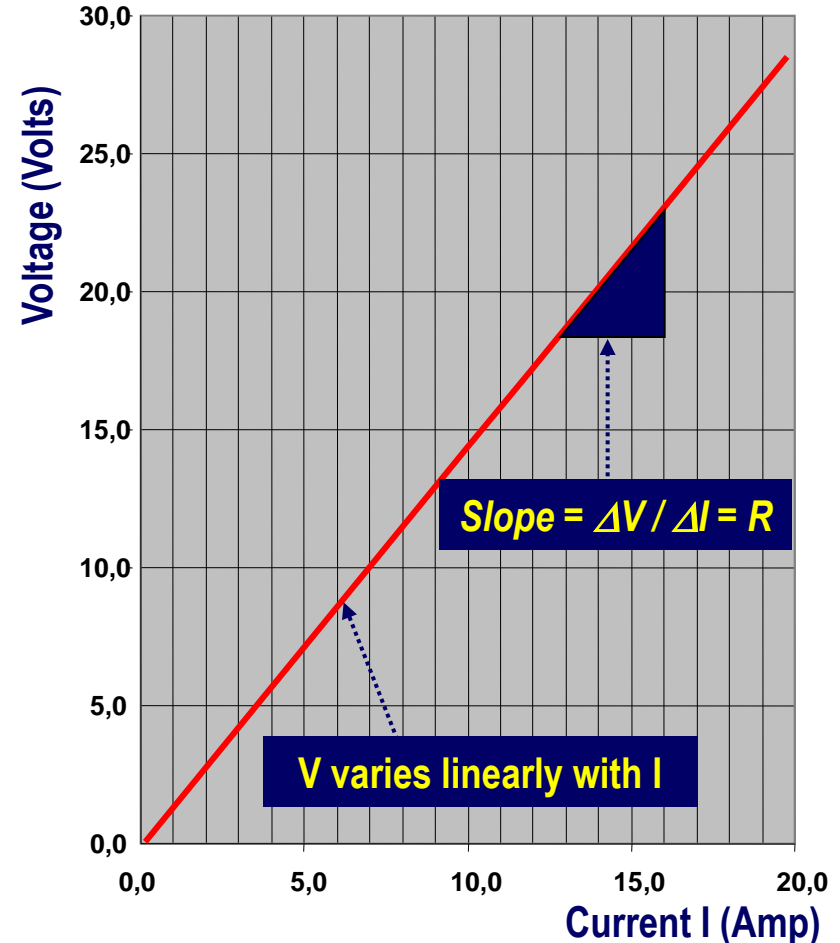




Ohm Law - Example

Question

Calculate the current flowing in the circuit shown on the RHS

$$\begin{aligned} V &= R \times I \\ (\text{Volt}) &= (\text{Ohm}) \times (\text{Amp}) \end{aligned}$$
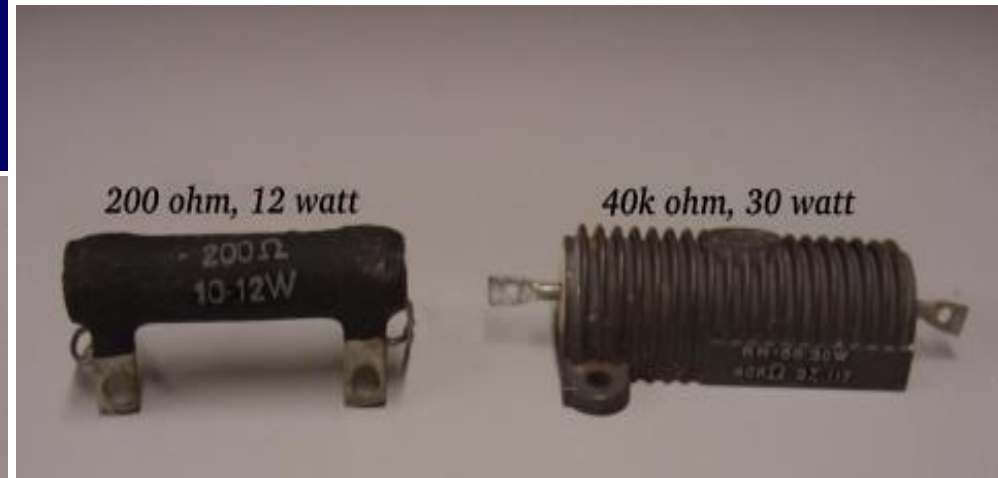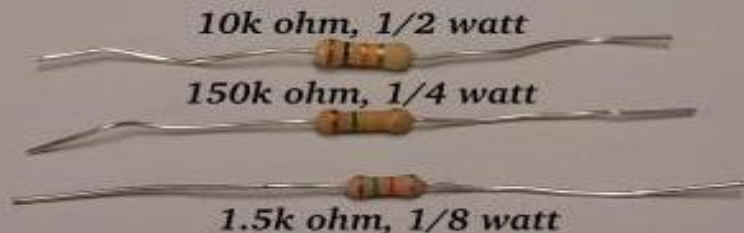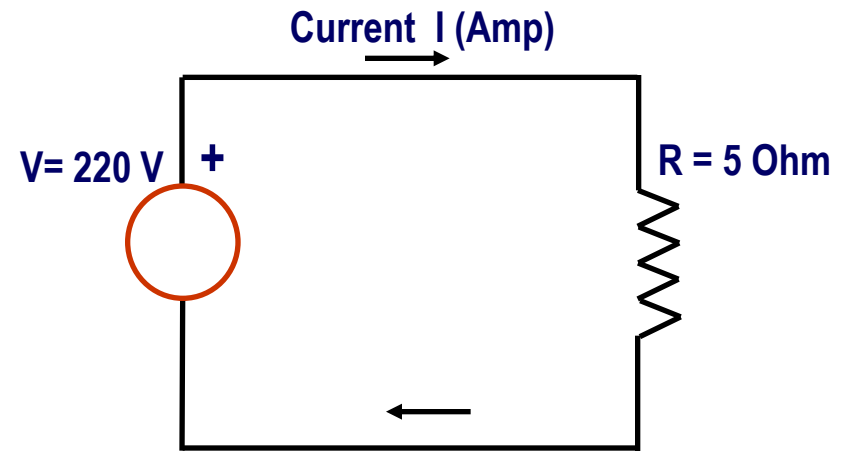
$$\begin{aligned} I &= V / R \\ &= 220 / 5 = 44 \text{ Amps} \end{aligned}$$



Ohm Law

Nonlinear V-I Characteristics

$$V = R \times I$$

(Volt) (Ohm) (Amp)



$$R = R_0 (1 + \alpha \Delta t)$$

$$\Delta t = T - 23^\circ \text{C}$$

$R_0 = \text{Resistance at } 23^\circ \text{C}$

$\alpha = \text{The temperature coeff. of the metal}$

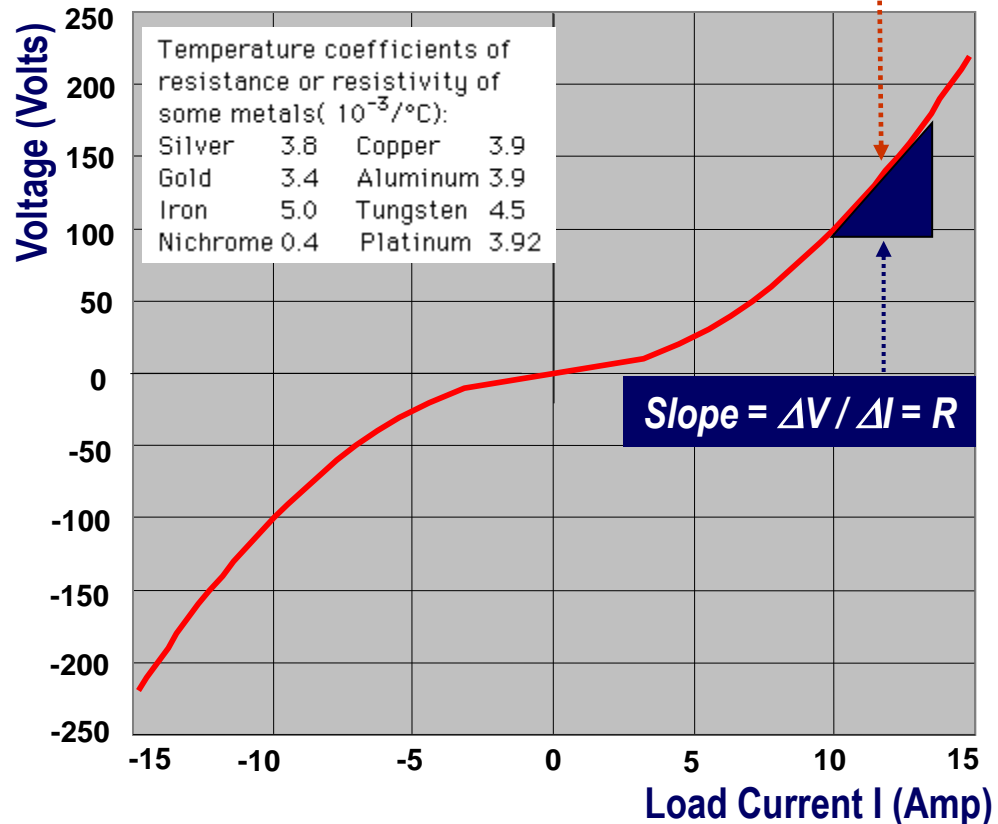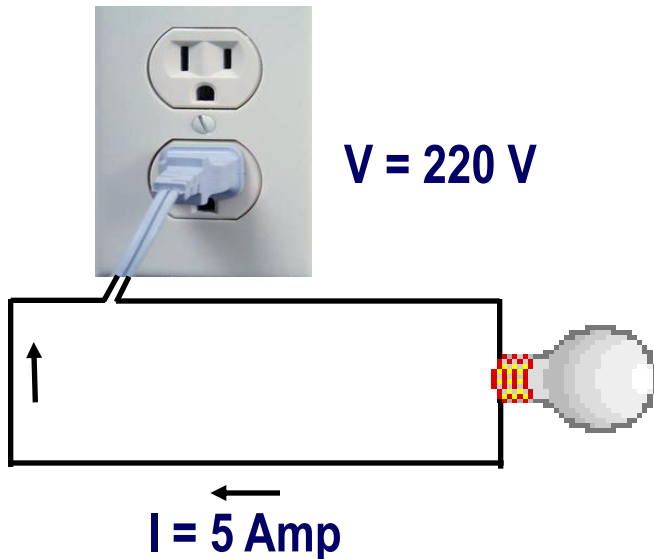Note that resistance increases with temperature, hence current is reduced



Resistance Formula

Resistance Formula

$$R = \rho l / A$$

where, R is the resistance of conductor,

ρ is the resistivity coefficient,

$\rho = 1 / 56 \text{ Ohm-mm}^2/\text{m}$ (Copper)

$1 / 32 \text{ Ohm-mm}^2/\text{m}$ (Aluminum)


l (m) is the length of the conductor

A (mm^2) is the cross sectional area of the conductor

ACSR Conductor
(Aluminum Conductor Steel Reinforced)

l (meter)

A (mm^2)

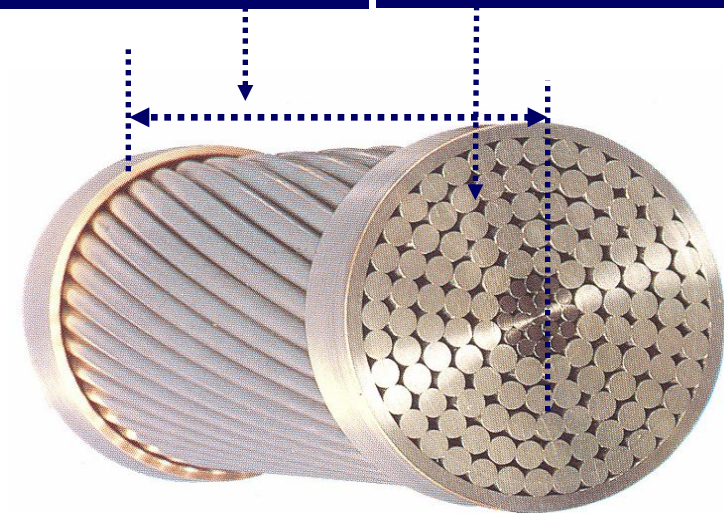

Resistance Formula

Resistance Formula

Resistance of a cable is proportional to the length and inversely proportional to the cross sectional area of the cable

$$R = \rho l / A$$

where, R is the resistance of conductor,

ρ is the resistivity coefficient,

$\rho = 1 / 56 \text{ Ohm-mm}^2/\text{m}$ (Copper)

$1 / 32 \text{ Ohm-mm}^2/\text{m}$ (Aluminum)

l (m) is the length of the conductor

A (mm^2) is the cross sectional area of the conductor



Resistance Formula

Resistance Formula

Example

Calculate the resistance of a copper cable with length 3200 meters and cross section 240 mm²

Solution

$$R = (1 / 56) 3200 / 240 \\ = 0.238 \text{ Ohms}$$

Aluminum Conductors

All Aluminium Conductors (AAC)
Tam Alüminyum İletkenler (AAC)

Aluminium Conductors Steel Reinforced (ACSR)
Çelik Özlü Alüminyum İletkenler (ACSR)

All Aluminium Alloy Conductors (AAAC)
Tam Alışimli Alüminyum İletkenler (AAAC)

0,6-1 kV Aluminium Cables
0,6-1 kV Alüminyum Kablo (APEK)

OPGW
Composite Fiber Optic Overhead Ground Wire
Fiber Optikli Koruma İletkeni

Steel Wire Rope
Çelik Halat



Resistance Formula

Resistance Formula


Example

Calculate the resistance of a copper cable with length 3200 meters and cross section 240 mm^2

Solution

$$R = (1 / 56) 3200 / 240 = 0.238 \text{ Ohms}$$

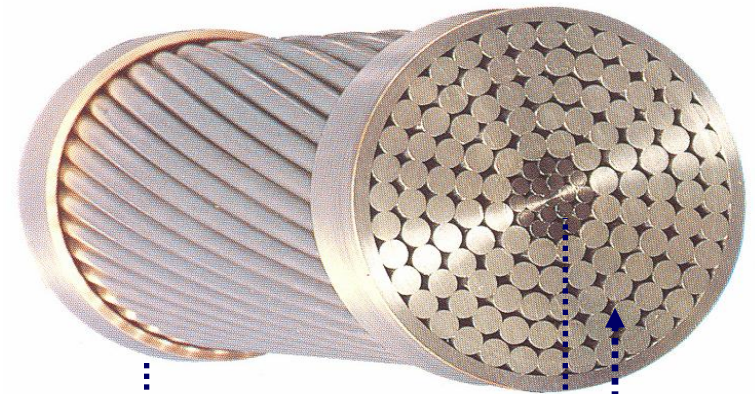ACSR Conductor
(Aluminum Conductor Steel Reinforced)



$l = 3200 \text{ (m)}$

$A = 240 \text{ (mm}^2\text{)}$

Resistivity Coefficients of Various Metals

Formula

$$\rho = 1 / 56 \text{ Ohms/meter (Copper)}$$

$$= 0.0178571 \text{ Ohm-mm}^2/\text{m}$$

$$R = \rho l / A$$


where, R is the resistance of conductor,
 ρ is the resistivity coefficient,
 $\rho = 1 / 56 \text{ Ohm-mm}^2/\text{m}$ (Copper)
 $1 / 32 \text{ Ohm-mm}^2/\text{m}$ (Aluminum)
 l (m) is the length of the conductor
 A (mm²) is the cross sectional area
of the conductor

Resistivity Coefficients

Material	Resistivity Coefficient	Resistance
	Ohm-mm ² /m	Ohms/feet
Silver	0.0162	0.00094
Copper	0.0172	0.00099
Gold	0.0244	0.00114
Aluminum	0.0282	0.00164
Mercury	0.9580	
Brass	0.0700	0.00406
Nickel	0.7800	0.00452
Iron	0.1000	0.00579
Platinum	0.1000	0.00579
Steel	0.1180	0.00684
Lead	0.2200	0.01270

Color Codes for Resistances

Rule

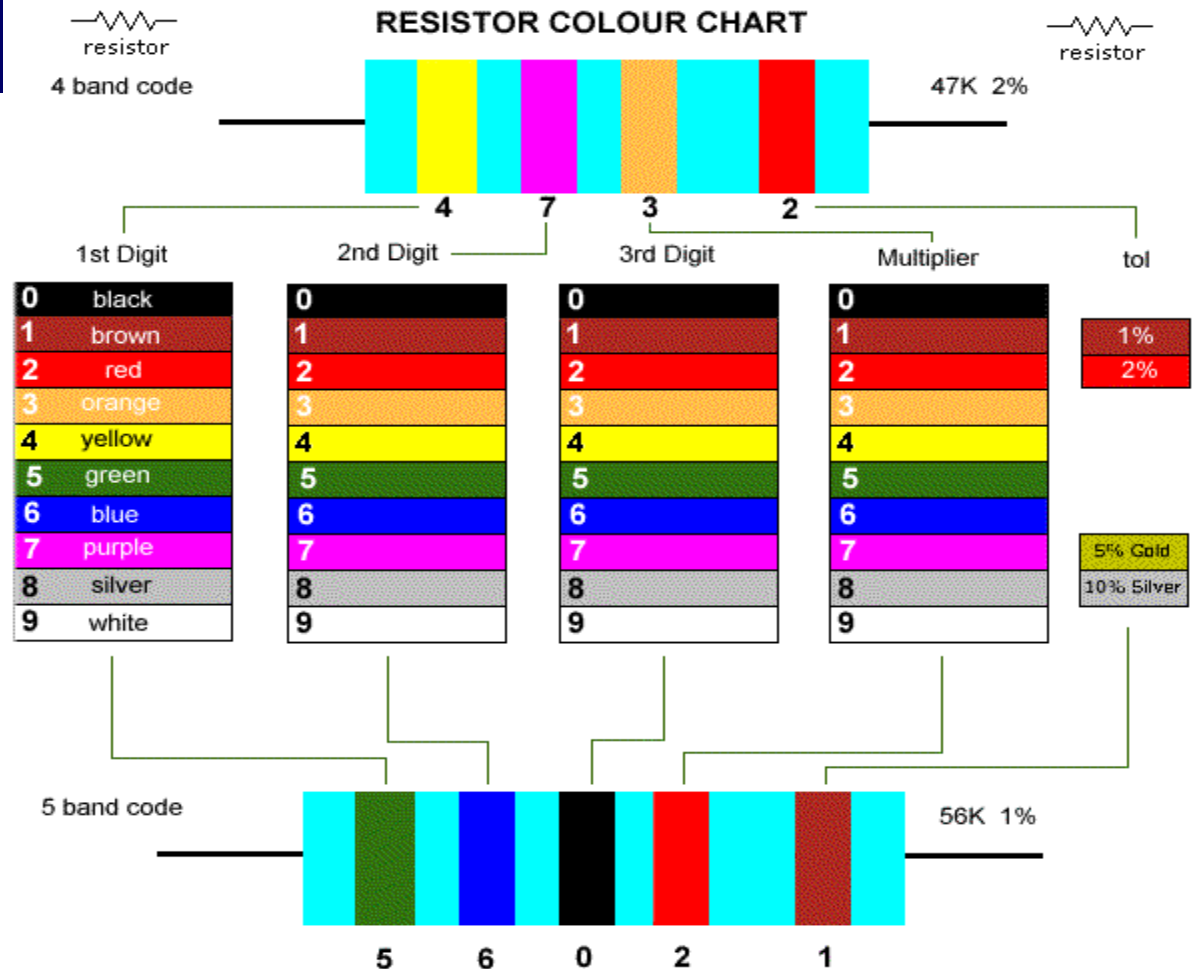

Insulator

Insulator

Insulator is a material with almost infinite resistance

Insulators are used to support HV lines and conductors

In practice, all materials have resistances. Hence, they conduct a certain amount of current when a voltage is applied to the terminals.

Insulator are materials that conduct only a very small amount of current, even when an extremely high voltage is applied to the terminals.

HV side

Ground side



Power dissipation in a Resistance

$$V = R \times I$$

(Volt) = (Ohm) (Amp)

On the other hand, it was shown in this lecture that;


$$\text{Power} = \text{Voltage} \times \text{Current}$$

or

$$P = V \times I$$


Hence, power dissipation in resistance R is
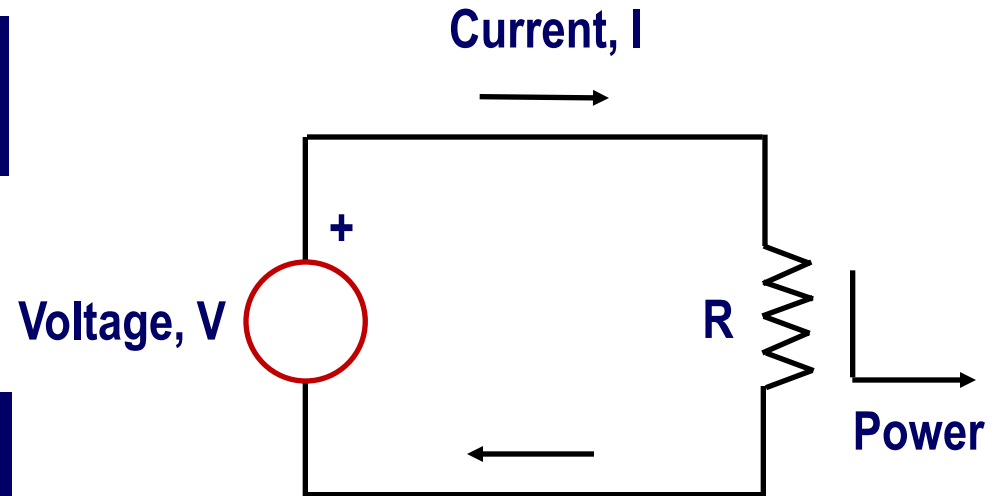
$$\text{Power} = R \times I \times I$$
$$= R \times I^2 \quad \text{Watt}$$



Series Connected Resistances

Equivalent Resistance Formula

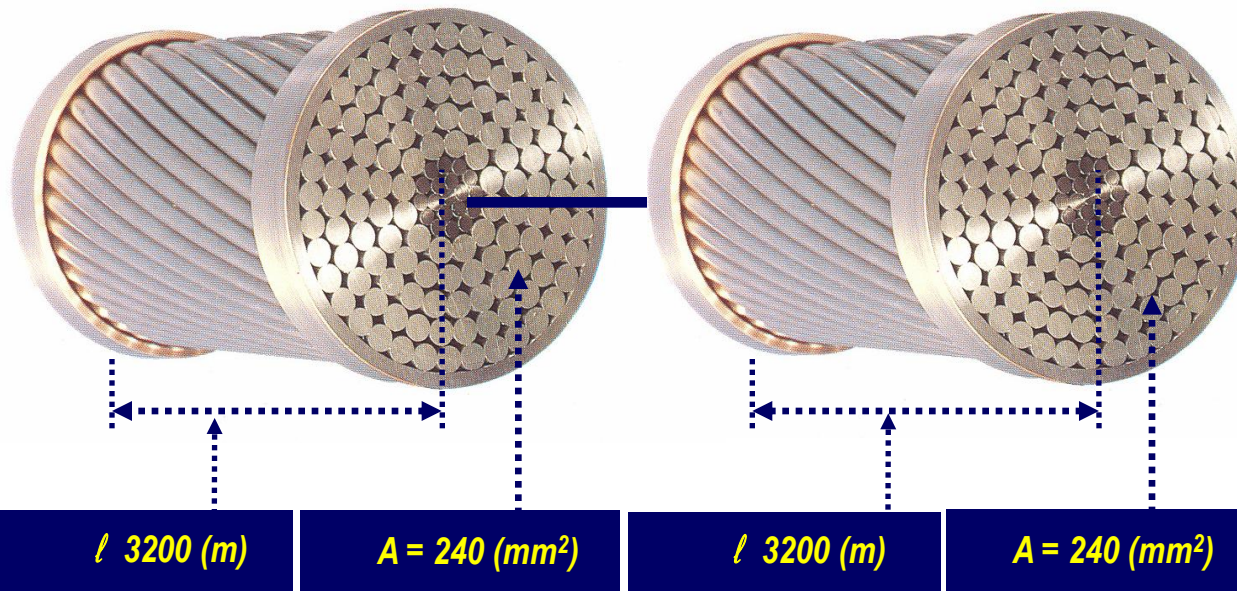

$$R_1 = \rho l_1 / A_1$$

$$R_2 = \rho l_2 / A_2$$

$$\text{Let } A_1 = A_2$$

Hence;

$$l_{\text{total}} = l_1 + l_2$$


$$\begin{aligned} R_{\text{total}} &= \rho l_{\text{total}} / A \\ &= \rho (l_1 + l_2) / A \\ &= \rho l_1 / A + \rho l_2 / A \\ &= R_1 + R_2 \end{aligned}$$

Series Connected Resistances

Equivalent Resistance Formula

$$R_{total} = R_1 + R_2$$

Series connected resistances are added

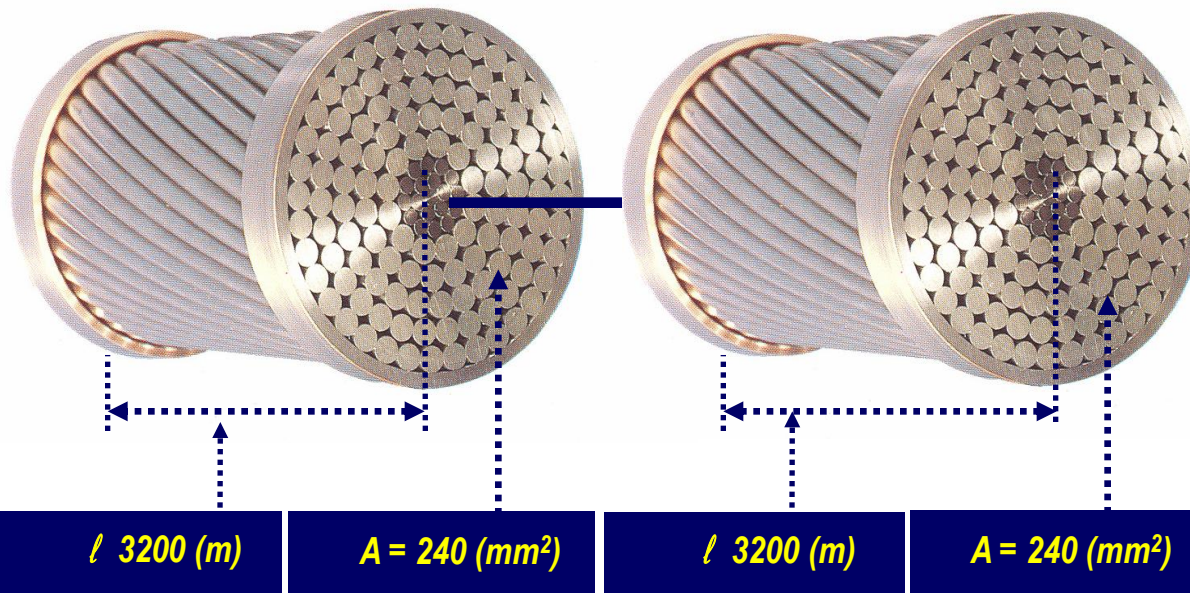

$$R_{total} = R_1 + R_2 + \dots + R_k$$

Ohm Law for Series Resistances


$$V = R_{total} \times I$$

(Volt) (Ohm) (Amp)


$$V = R_1 \times I + R_2 \times I$$

(Volt) (Volt) (Volt)


Current I (Amp)

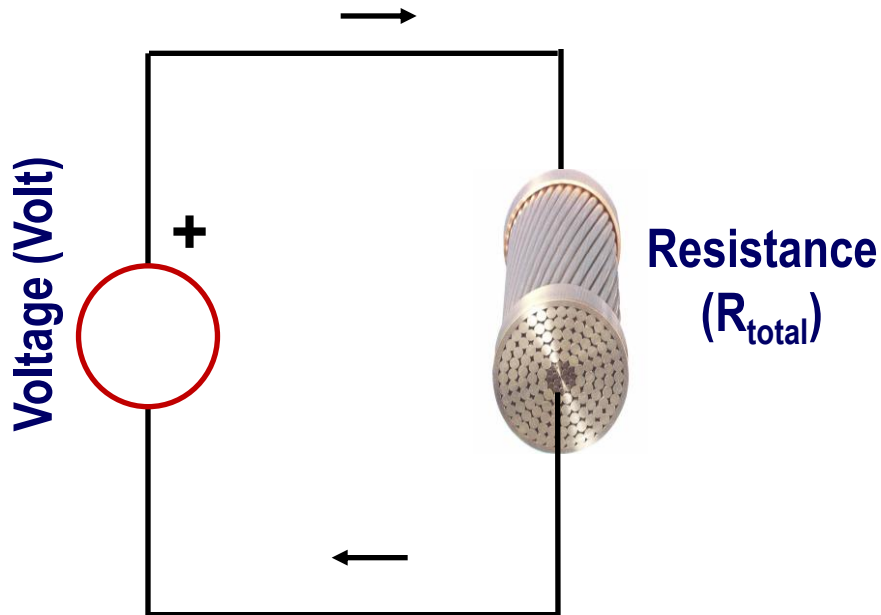

Current I (Amp)

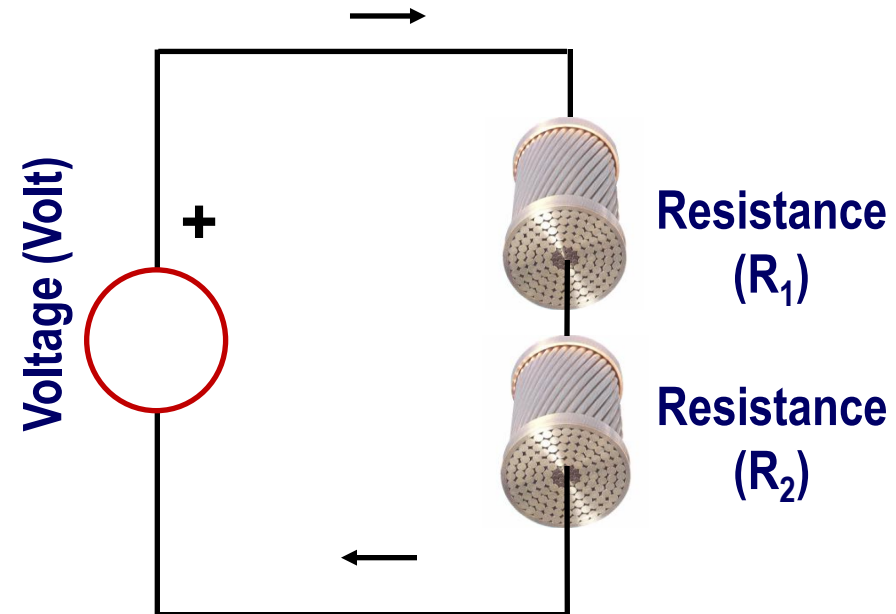


Ohm Law for Series Resistances

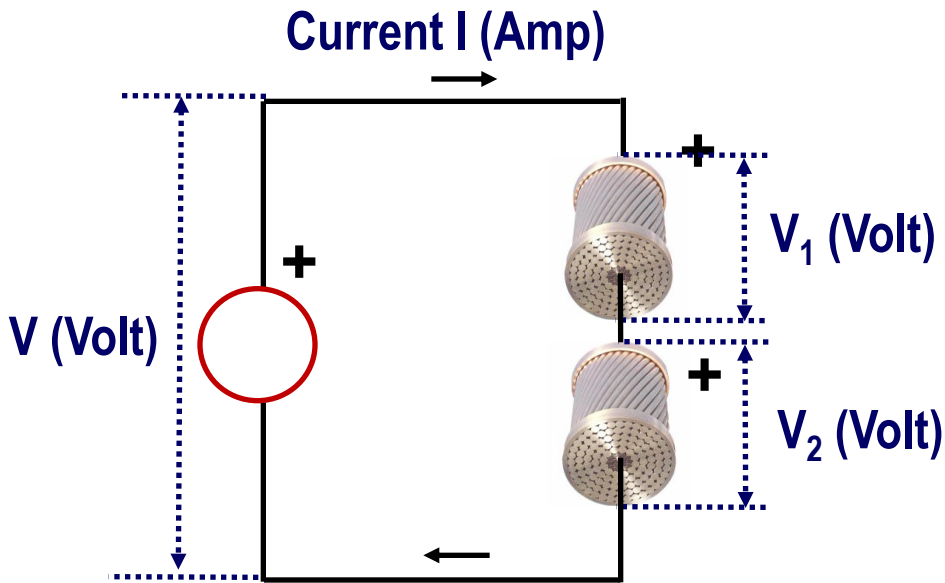

$$\begin{aligned} V &= R_1 \times I + R_2 \times I \\ (\text{Volt}) & \quad (\text{Volt}) \quad (\text{Volt}) \\ &= V_1 + V_2 \end{aligned}$$

Aluminum Cables and Conductors

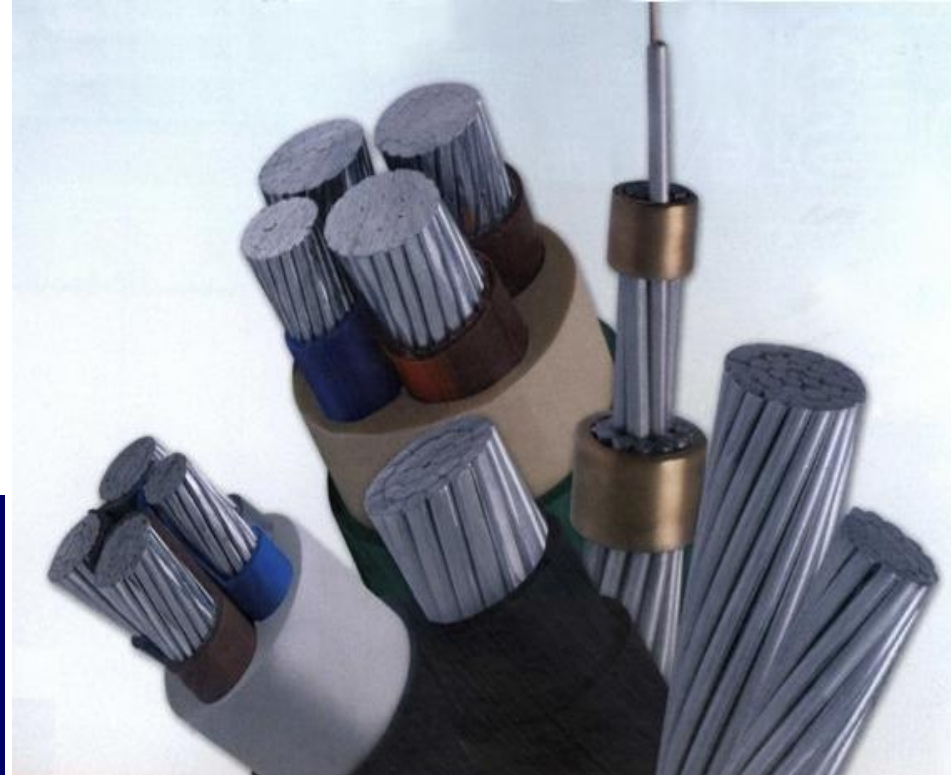

Admittance

Definition

Inverse of resistance is called “Admittance”

$$g = 1 / R$$



(Siemens) (1 / Ohm)

Unit of “Admittance” is Siemens

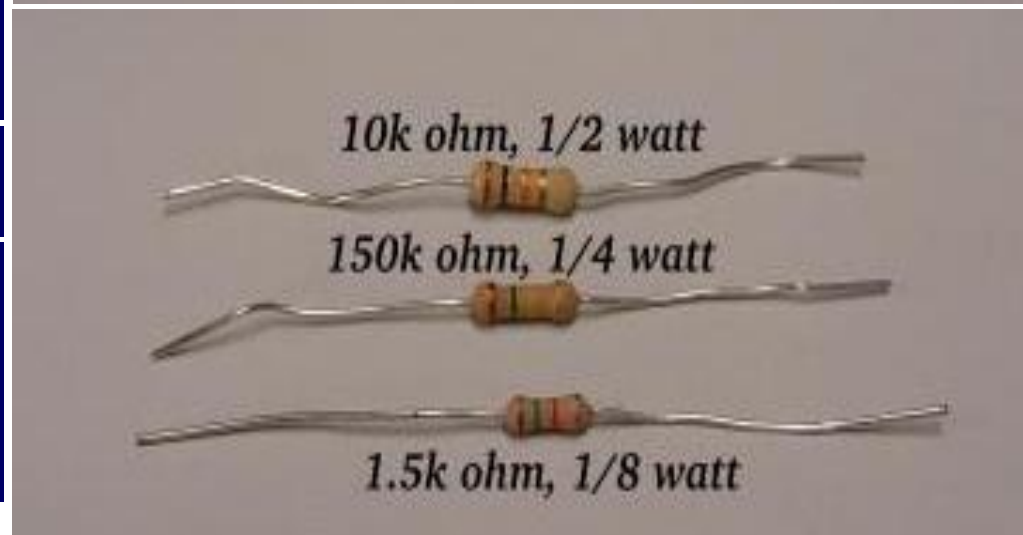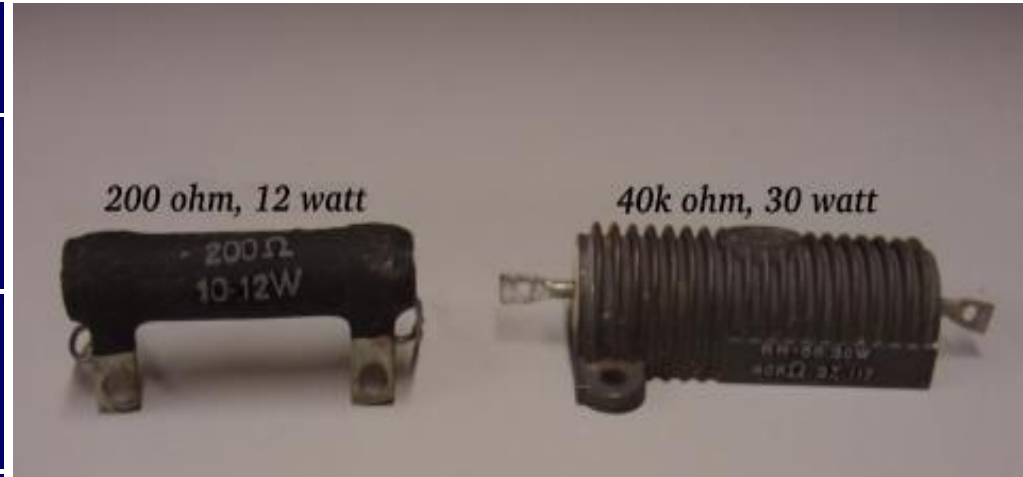Example



Calculate the admittance of 10 k Ω resistance shown on the RHS

$$g = 1 / 10^4 = 10^{-4} \text{ Siemens}$$




Shunt Connected Resistances

Equivalent Resistance Formula

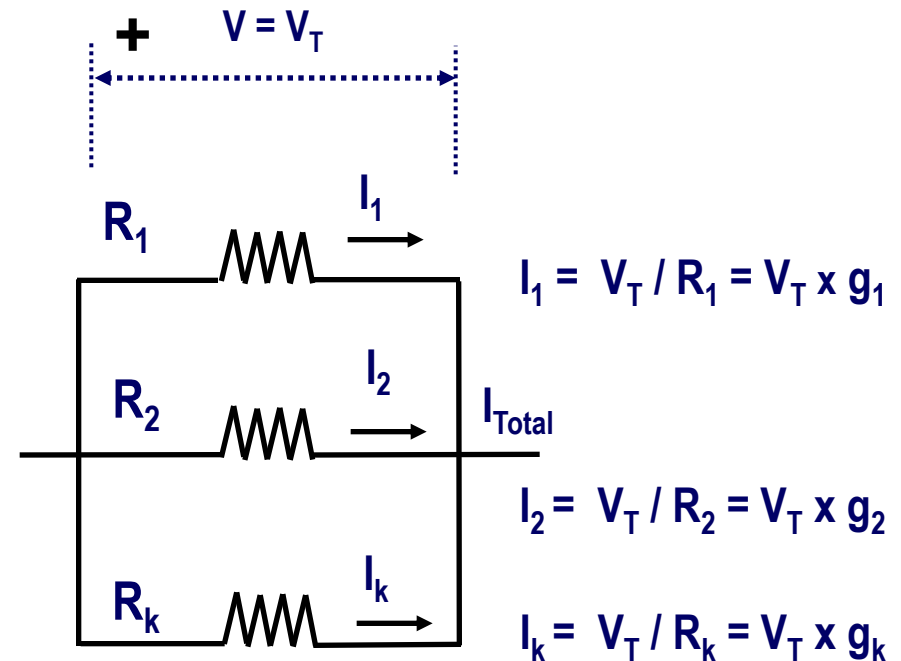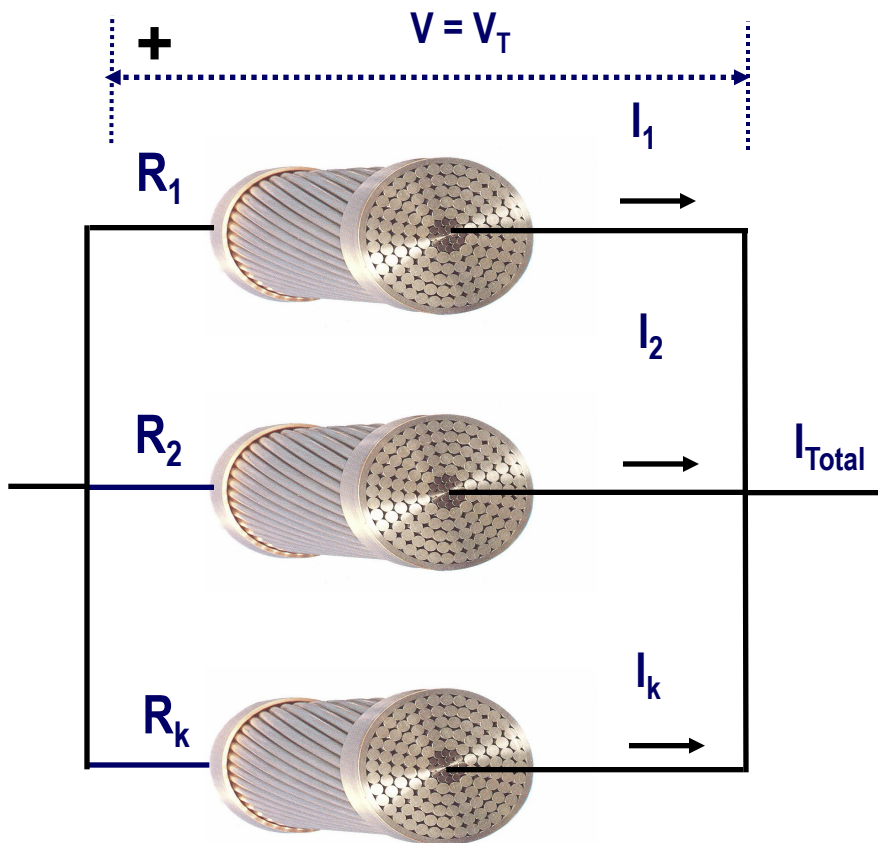

Shunt Connected Resistances

Equivalent Resistance Formula

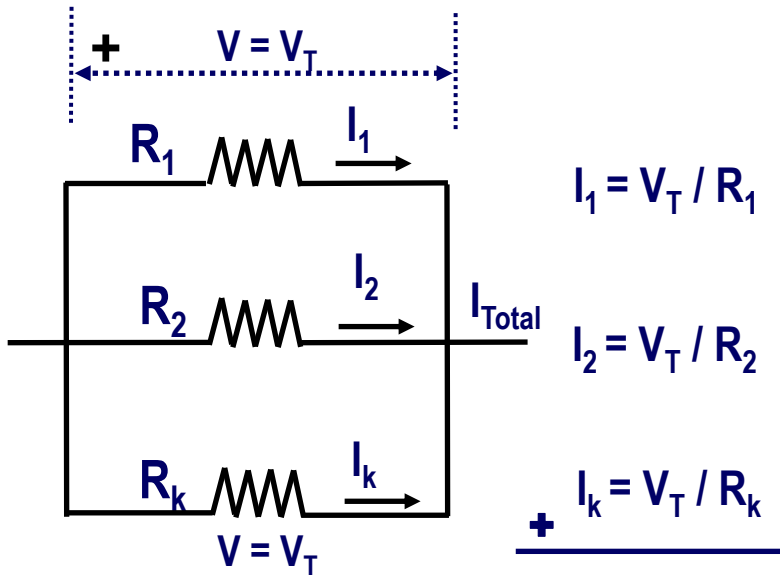

$$I_1 = V_T / R_1$$

$$I_2 = V_T / R_2$$

$$+ \quad I_k = V_T / R_k$$

$$I_{total} = V_T(1 / R_1 + 1 / R_2 + \dots + 1 / R_k) = V_T / R_{equivalent}$$


Hence,

$$R_{equiv} = \frac{1}{1 / R_1 + 1 / R_2 + \dots + 1 / R_k}$$

Shunt Connected Resistances

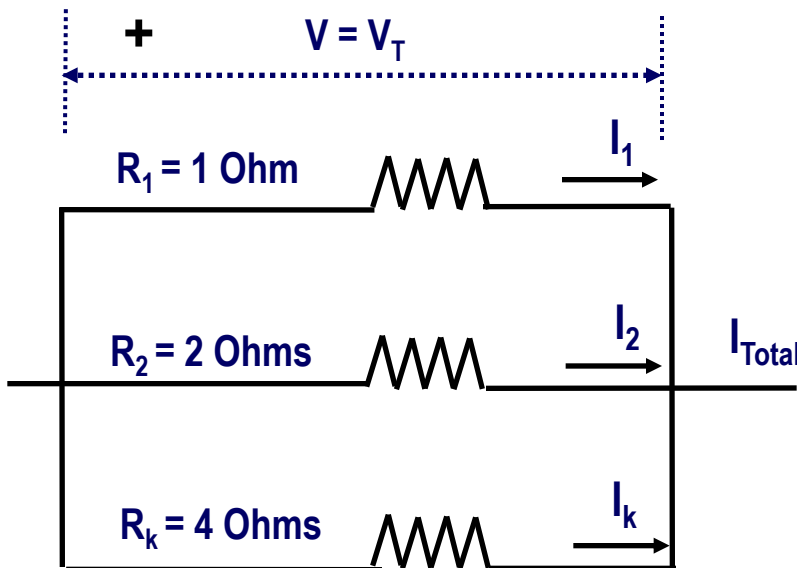Example

Find the equivalent resistance of the following connection




$$R_{\text{equiv}} = \frac{1}{1/R_1 + 1/R_2 + \dots + 1/R_k}$$

$$R_{\text{equiv}} = \frac{1}{1/1 + 1/2 + 1/4} = 1 / (7/4) = 4/7 = \underline{0.5714 \text{ Ohm}}$$

Shunt Connected Resistances

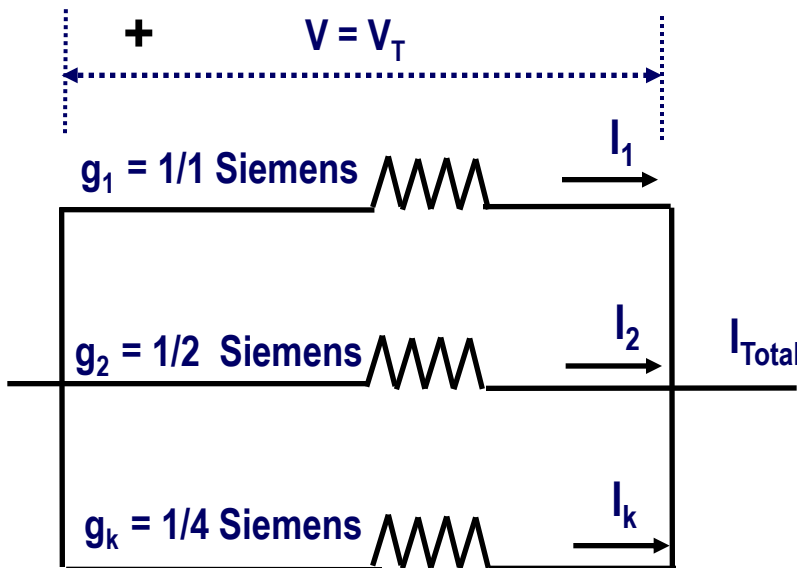Example

Find the equivalent admittance of the following connection



$$R_{equiv} = \frac{1}{1/R_1 + 1/R_2 + \dots + 1/R_k}$$

or

$$1/g_{equiv} = \frac{1}{g_1 + g_2 + \dots + g_k}$$

$$\begin{aligned} g_{equiv} &= g_1 + g_2 + g_3 \\ &= 1/1 + 1/2 + 1/4 \\ &= 7/4 \\ &= 1.75 \text{ Siemens} \end{aligned}$$

Basic Principles of Electricity



Voltages on Series Connected Elements

Voltages on series connected elements are added

$$V \text{ (Volt)} = V_1 \text{ (Volt)} + V_2 \text{ (Volt)}$$

or
generalizing
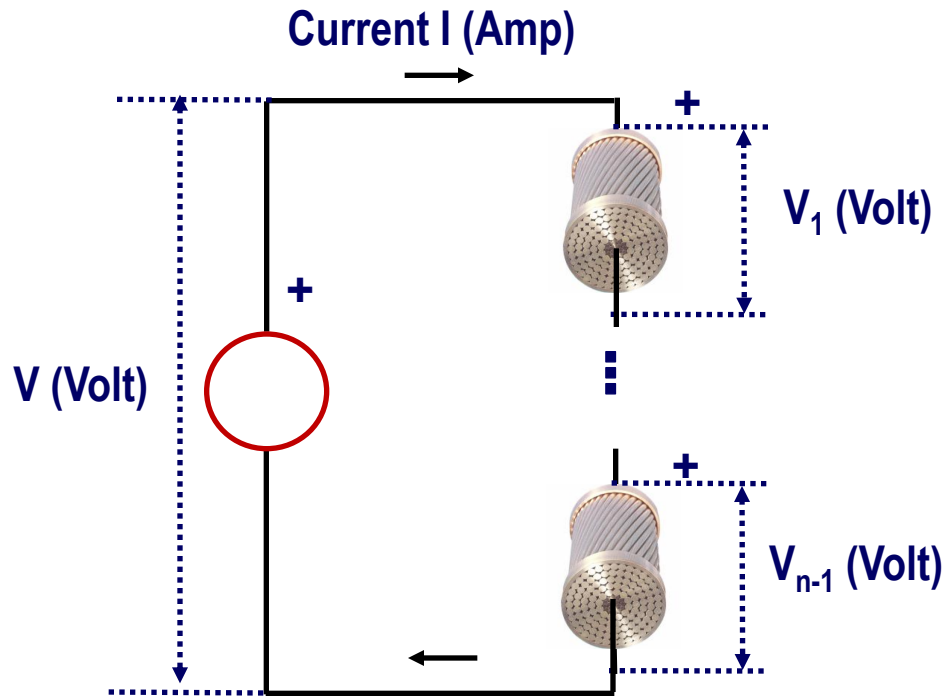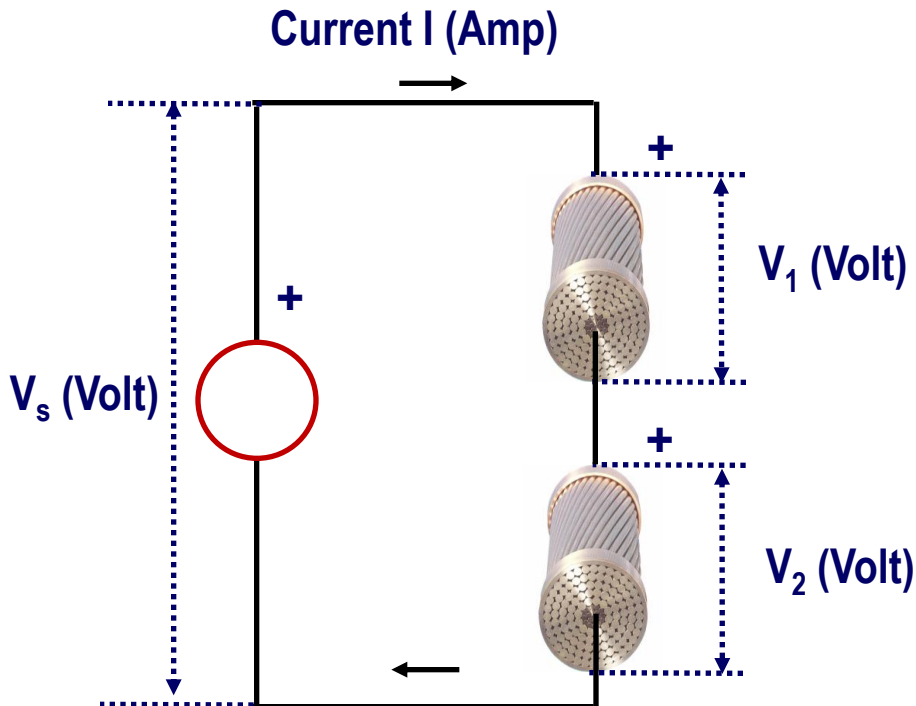
$$V \text{ (Volt)} = V_1 \text{ (Volt)} + \dots + V_{n-1} \text{ (Volt)}$$



Basic Principles of Electricity

Voltages on Series Connected Elements


Voltages on series connected elements are added

$$V \text{ (Volt)} = V_1 \text{ (Volt)} + \dots + V_{n-1} \text{ (Volt)}$$

$$V = \sum_{i=1}^{i=n-1} V_i$$

$$V_n - \sum_{i=1}^{i=n-1} V_i = 0$$

$$\sum_{i=1}^{i=n} V_i = 0$$

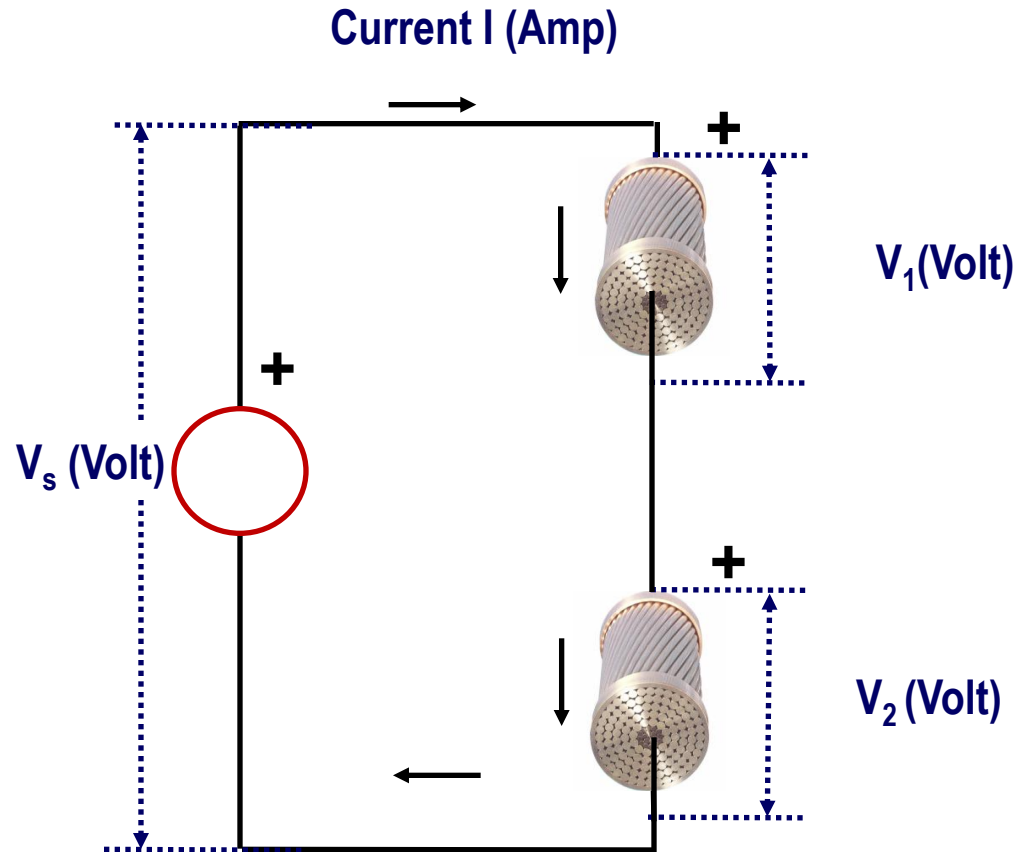

Kirchoff's Voltage Law (KVL)

Statement


The above result may be expressed as;

Sum of voltages in a closed loop is zero

or

$$\sum_{i=1}^{i=n} V_i = 0$$

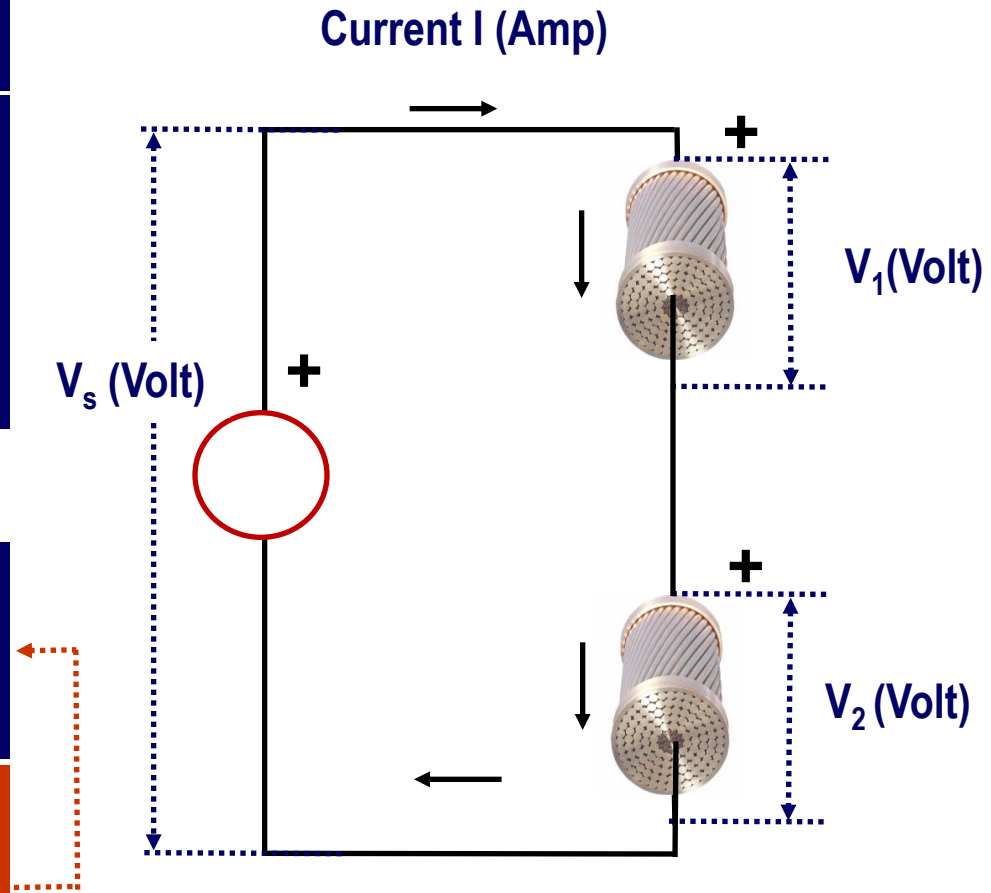Kirchoff's Second Law
or
Kirchoff's Voltage Law



Kirchoff's Voltage Law (KVL)


Example

$$\sum_{i=1}^{i=n} V_i = 0$$

$$V_s = 220 \text{ Volts}$$

$$V_s - V_1 - V_2 = 0$$

$$220 - 100 - 120 = 0$$


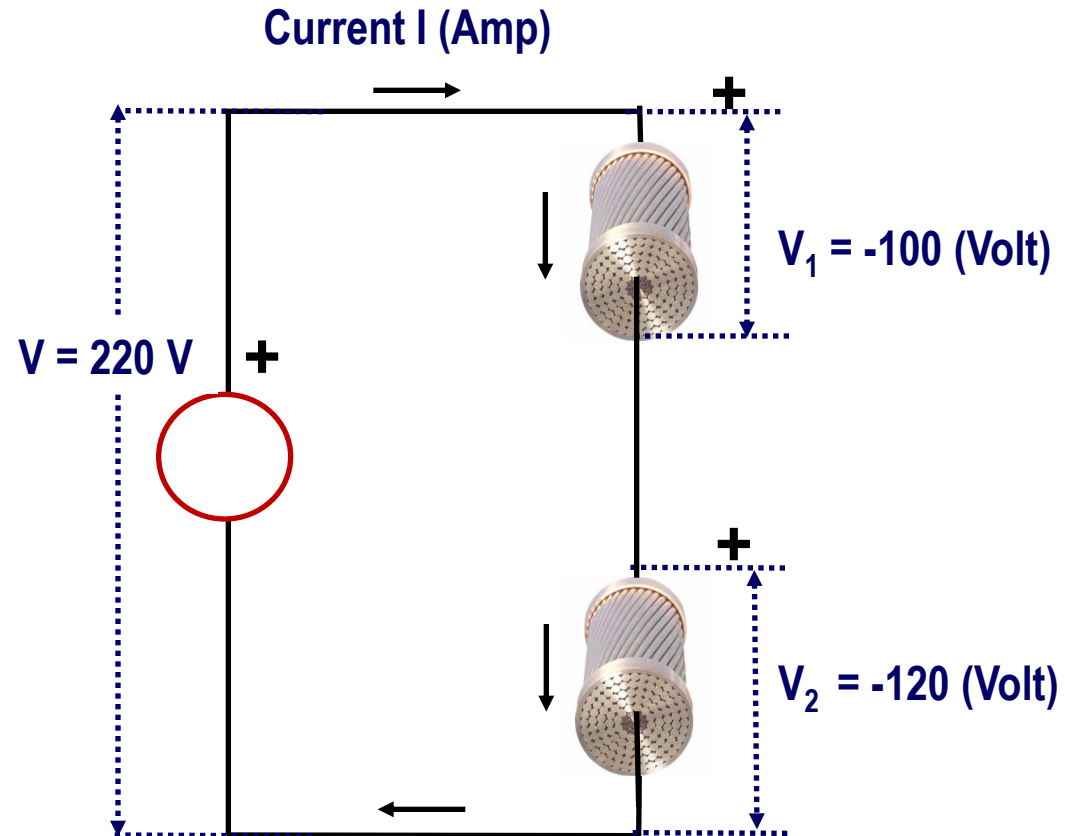


Kirchoff's Voltage Law (KVL)

Simple Rules

Head (pinpoint) of the arrow is negative,
Tail of the arrow is positive

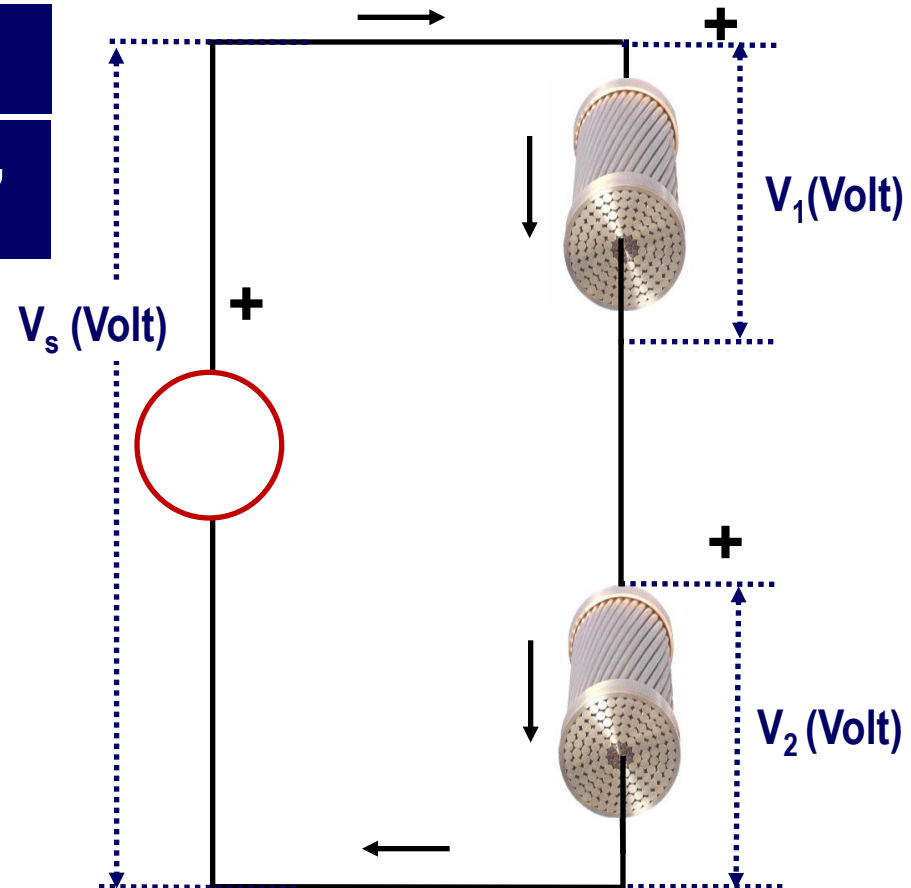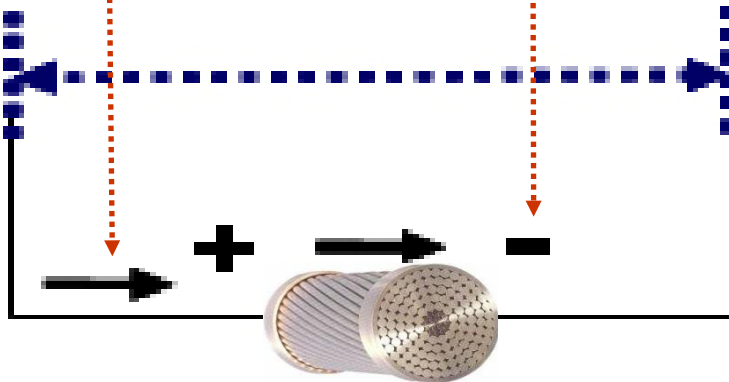
This current is assigned
such a direction that it
always enters from the '+'
side of the resistance



A Simple Rule for applying Kirchoff's Voltage Law (KVL)

A Simple Rule

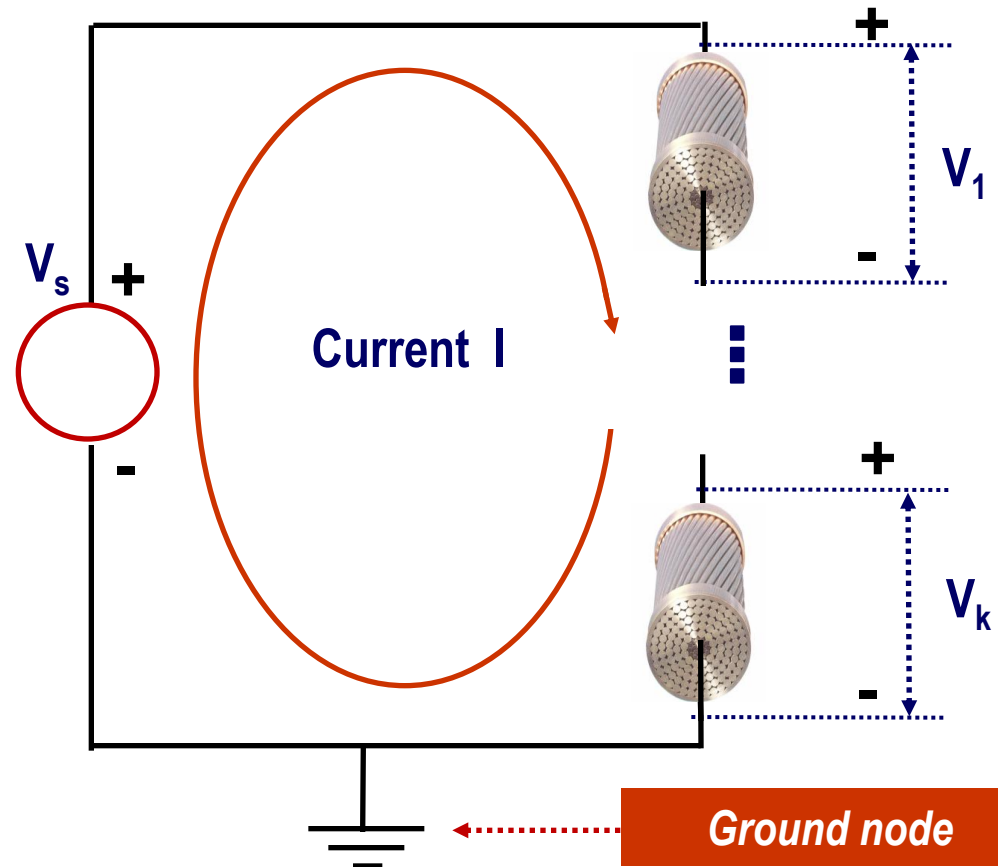- Choose a ground node,
- Assume that current I flows clockwise,
- Starting from the ground node, assign “+” and “-” signs to those passive elements (i.e. those elements other than source) in such a direction that the current enters to “+” side and the leaves from the “-” side,
- Assign “+” sign to the that side of the source from which current is leaving




A Simple Rule for applying Kirchoff's Voltage Law (KVL)

A Simple Rule

- Then write down the voltages on each element by using Ohm Law on a path in a clockwise direction,
- Assign “+” sign to those voltage terms in the equation that you pass from “-” to “+”,
- Assign “-” sign to those voltage terms in the equation that you pass from “+” to “-”,
- Stop and equate it to zero when you come again to the ground node that you have started

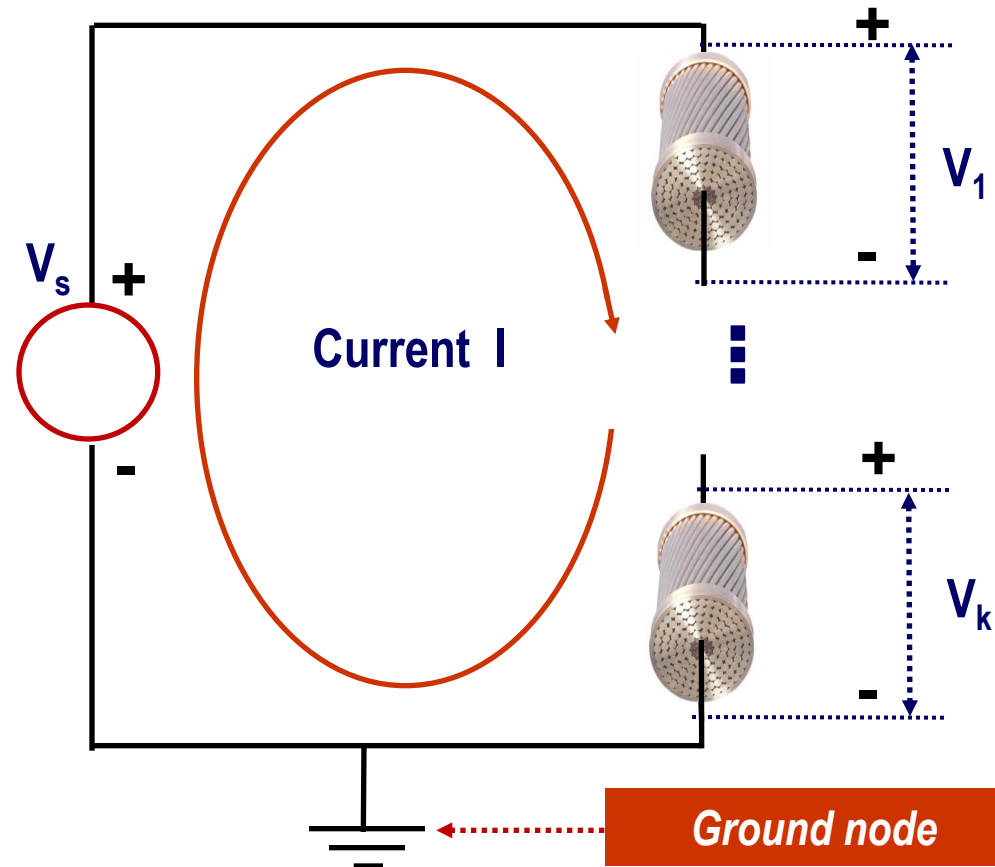Example;

$$+V_s - V_1 - V_2 = 0 \rightarrow V_s = V_1 + V_2$$



Summary of Kirchoff's Laws

Kirchoff's Current Law (KCL)



Algebraic sum of currents entering a junction is zero

$$\sum_{i=1}^{i=n} I_i = 0$$

Kirchoff's Voltage Law (KVL)

Algebraic sum of voltages in a closed loop is zero

$$\sum_{i=1}^{i=n} V_i = 0$$

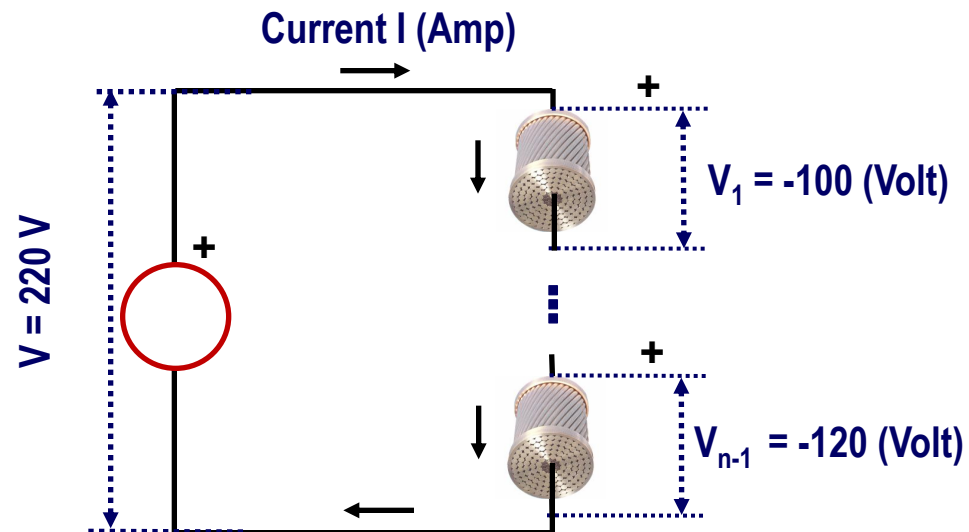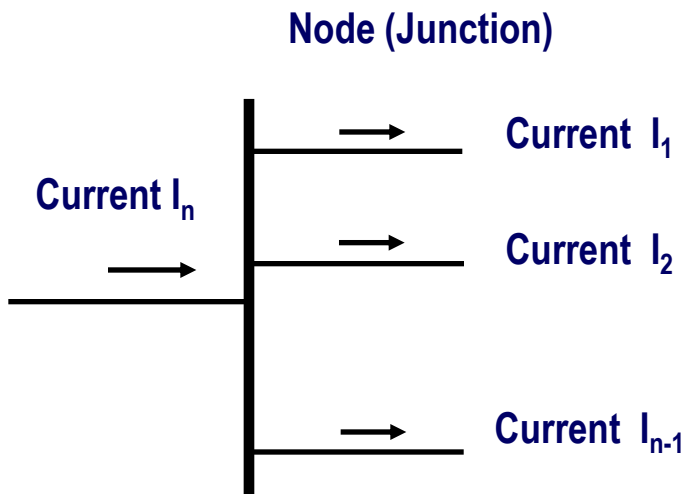

Voltage Division Principle

$$V_1 = R_1 \times I$$

$$V_2 = R_2 \times I$$

...

$$V_k = R_k \times I$$


+

$$V_s = V_1 + V_2 + \dots + V_k$$

$$= (R_1 + \dots + R_k) \times I$$

$$V_k / V_s = R_k / (R_1 + \dots + R_k)$$
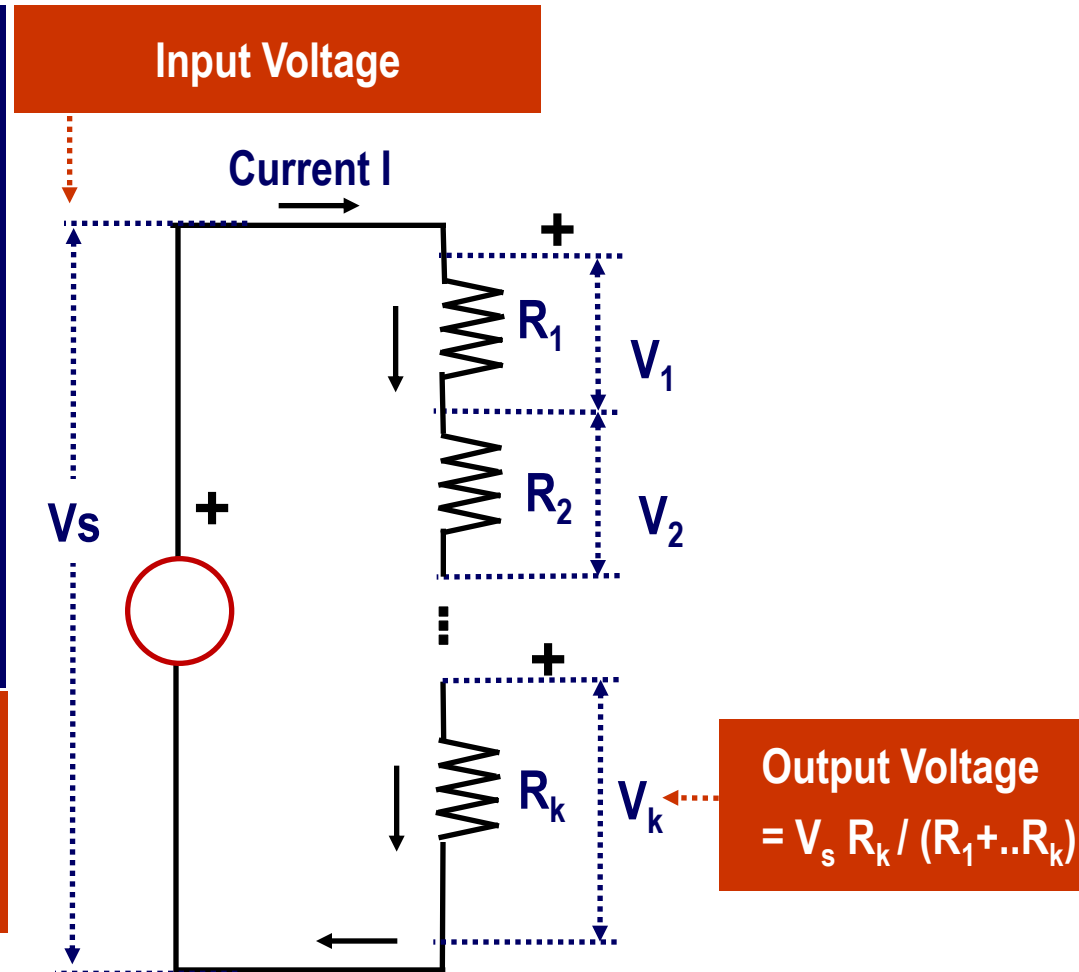
$$\text{Voltage Division Ratio} = \frac{R_k}{R_1 + \dots + R_k}$$





Potentiometer (Voltage Divider)

Principle

Input voltage is divided and a certain fraction is given to the output

$$V_k = \frac{R_k}{R_1 + \dots + R_k} V_s$$
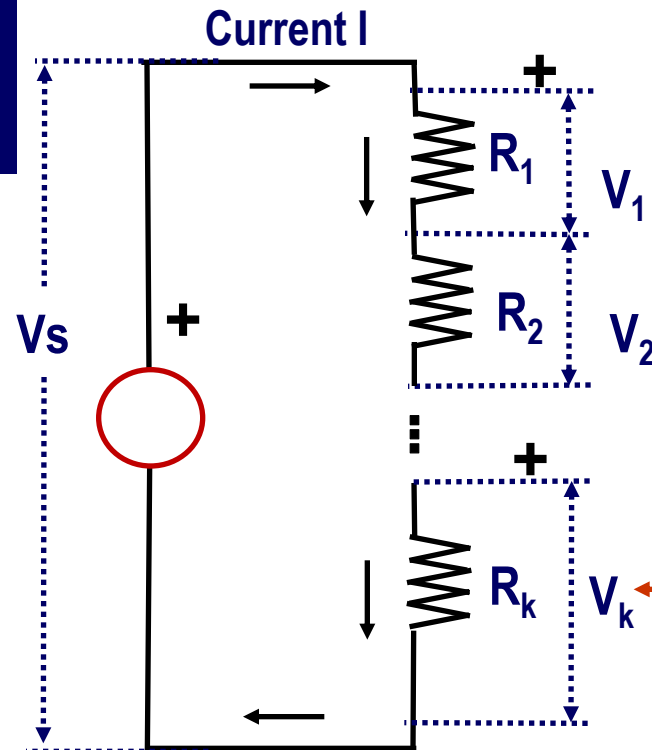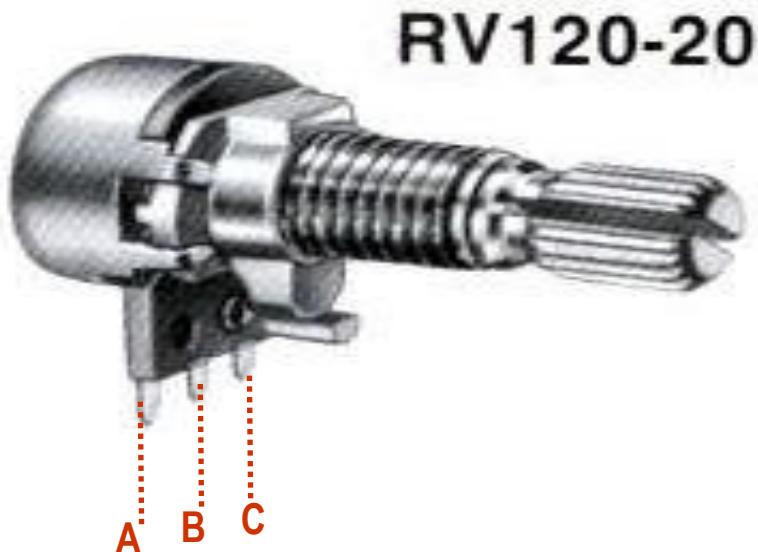
$$\text{Division Ratio} = \frac{R_k}{R_1 + \dots + R_k}$$




Potentiometer (Voltage Divider)

Circuit Arrangement

Rotary Potentiometer
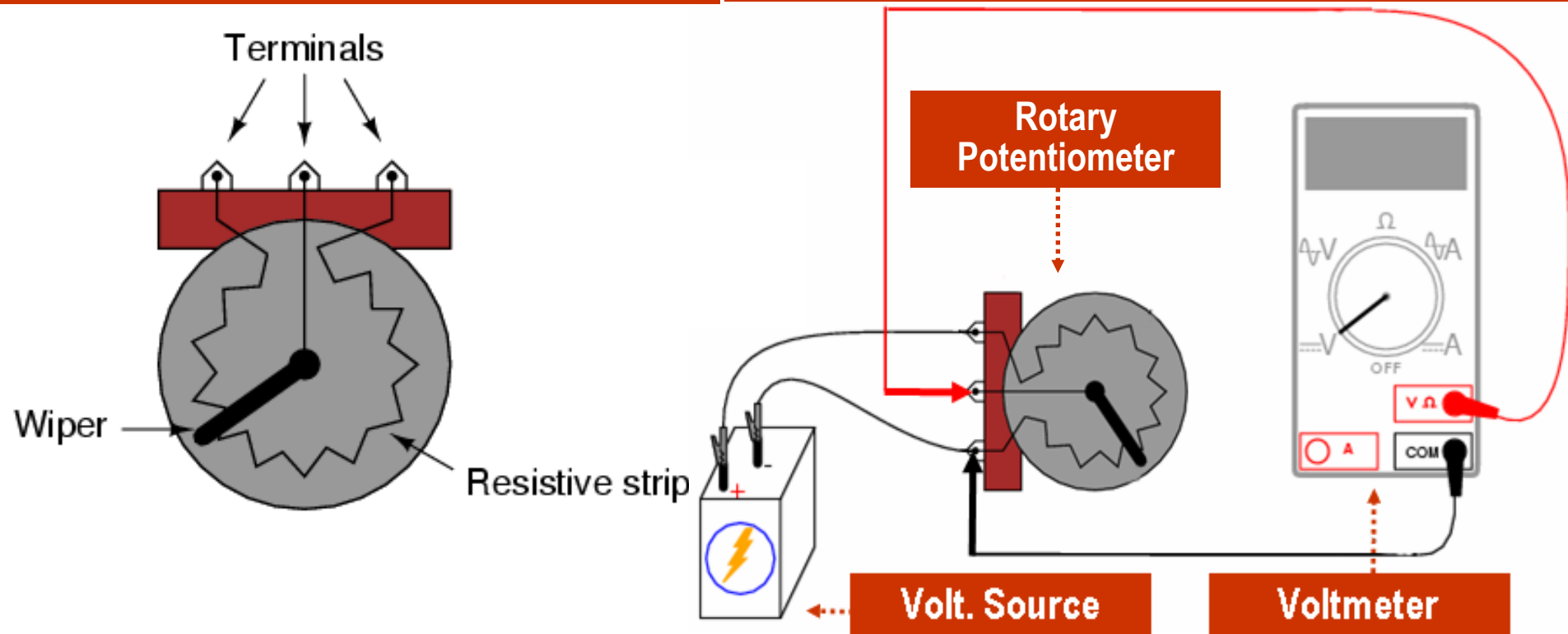
$$\text{Division Ratio} = \frac{R_k}{R_1 + \dots + R_k}$$



Current Division Principle

$$V_T \times g_1 = I_1$$

$$V_T \times g_2 = I_2$$

...

$$V_T \times g_k = I_k$$

+-----

$$V_T (g_1 + \dots + g_k) = I_1 + \dots + I_k$$


or

$$V_T (g_1 + \dots + g_k) = I_s$$

$$I_k / I_s = g_k / (g_1 + \dots + g_k)$$

$$I_k = \frac{g_k}{g_1 + \dots + g_k} I_s$$
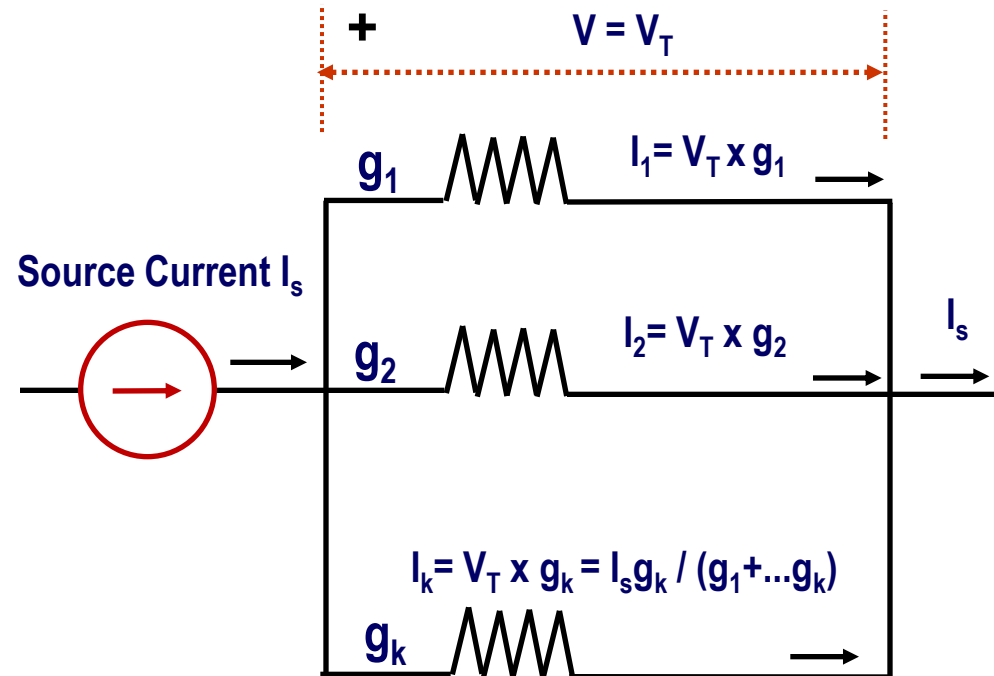
$$\text{Division Ratio} = \frac{g_k}{g_1 + \dots + g_k}$$



Voltage Sources

Definition



Voltage source is an element which creates a voltage difference at its terminals

A simple Rule:

Current is assigned such a direction that it always leaves the '+' side of the voltage or current source.

Voltage Source

DC Voltage Source

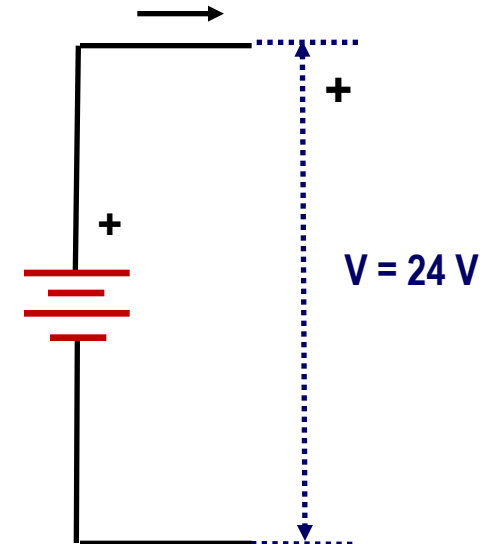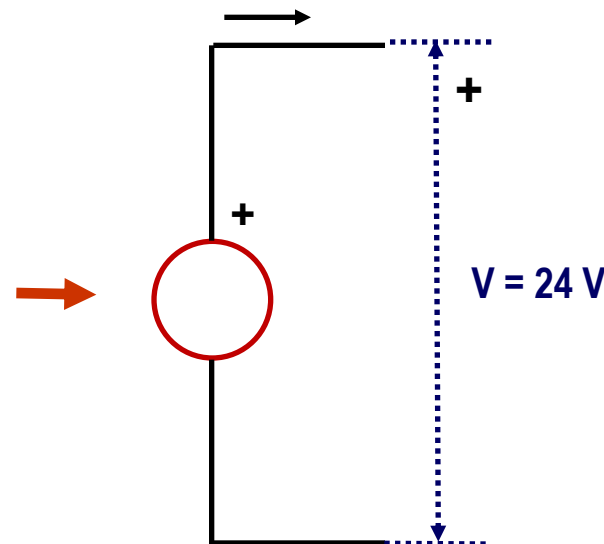

Ideal Voltage Source



Definition

An ideal voltage source is the one that the terminal voltage does not change with the current drawn

An ideal voltage source has zero internal resistance



Battery

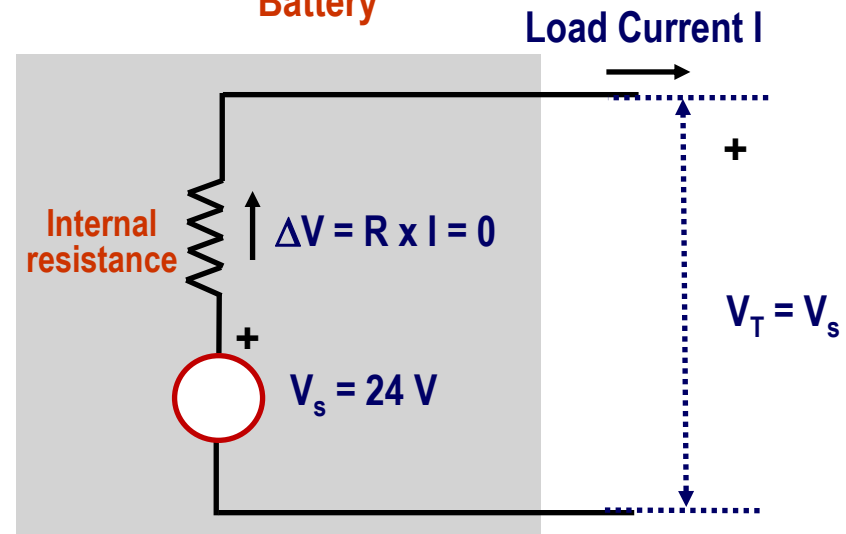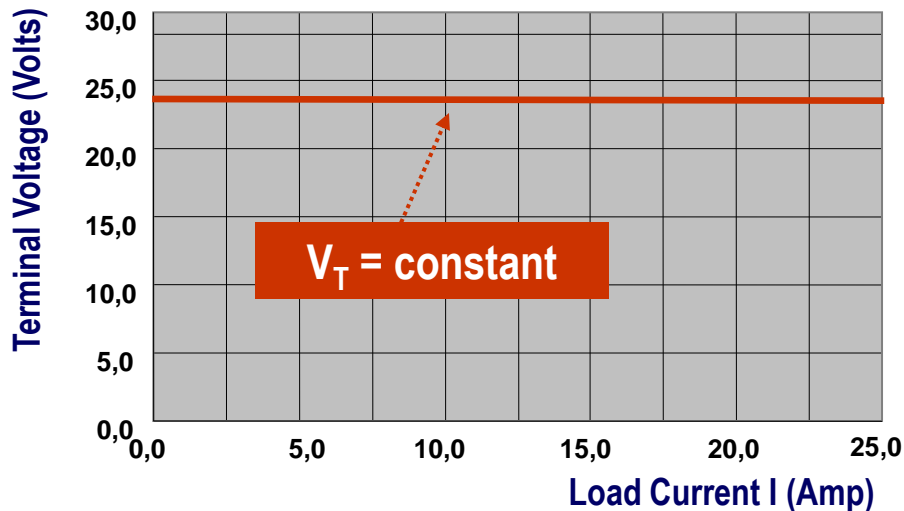

Non-Ideal (Real) Voltage Sources

Definition

A voltage source always has an internal resistance R connected in series with the source

Writing down KVL for the above cct;

$$V_s - \Delta V - V_T = 0$$

or


$$V_T = V_s - \Delta V$$

where,

$$\Delta V = R \times I$$

is called “internal voltage drop”

Terminal voltage V_T is reduced by ΔV

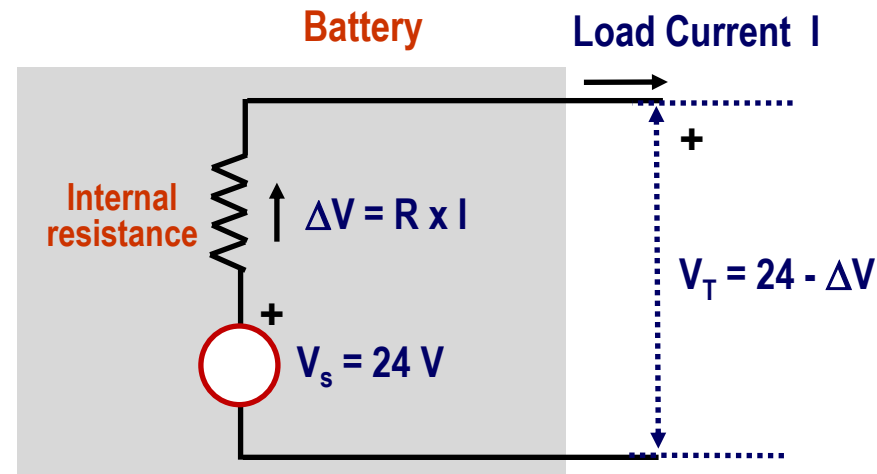



Non-Ideal (Real) Voltage Sources

Definition

Writing down KVL for the above cct;

$$V_T = V_s - \Delta V$$

$$= V_s - R \times I$$

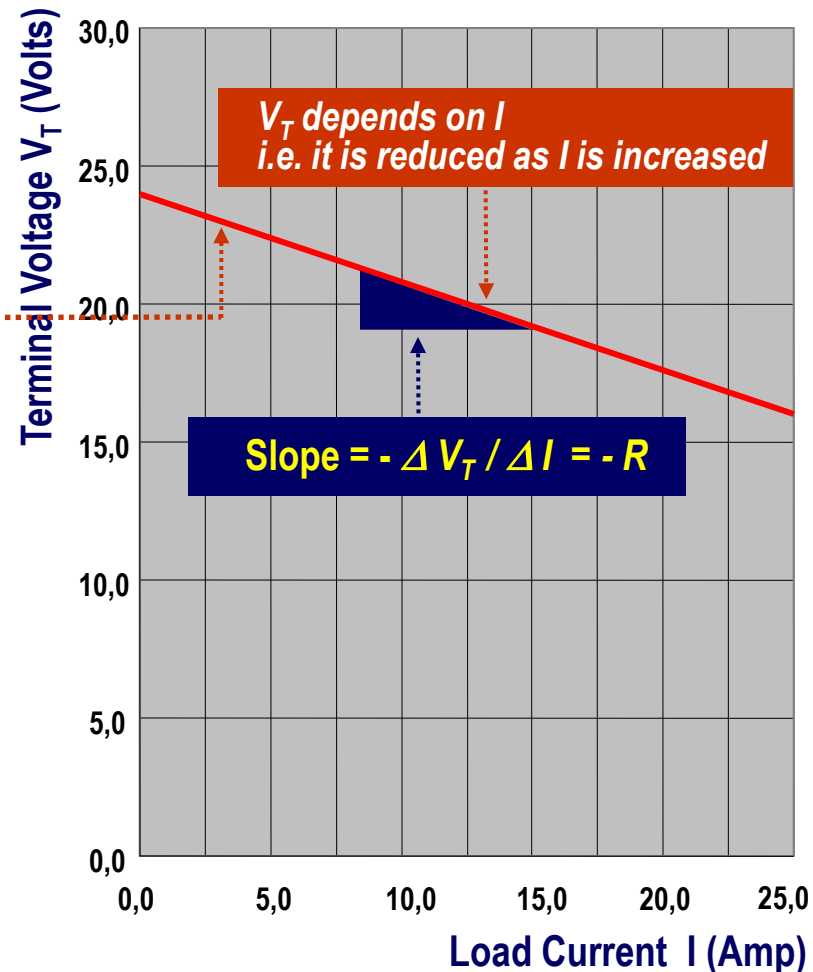
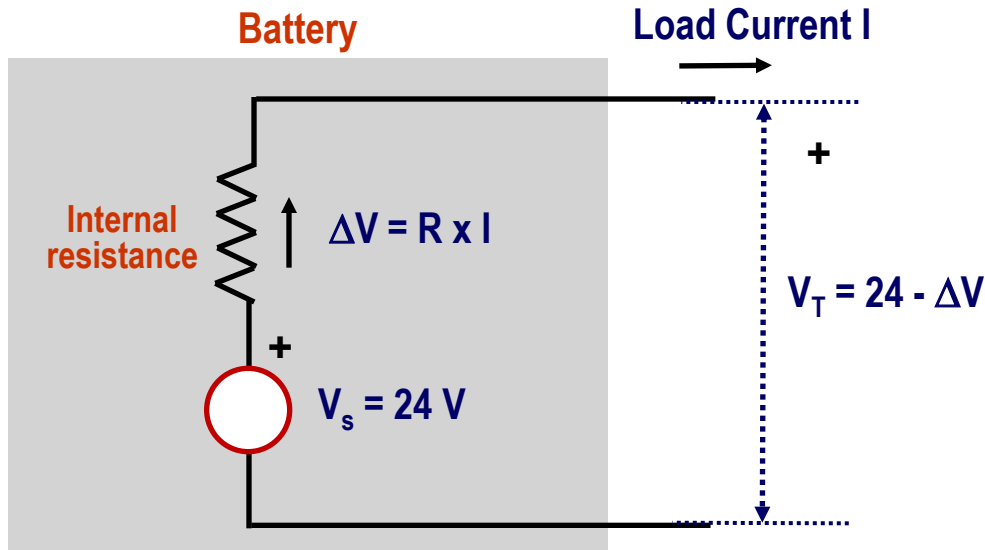


Ideal Current Source

Definition

Ideal Current Source

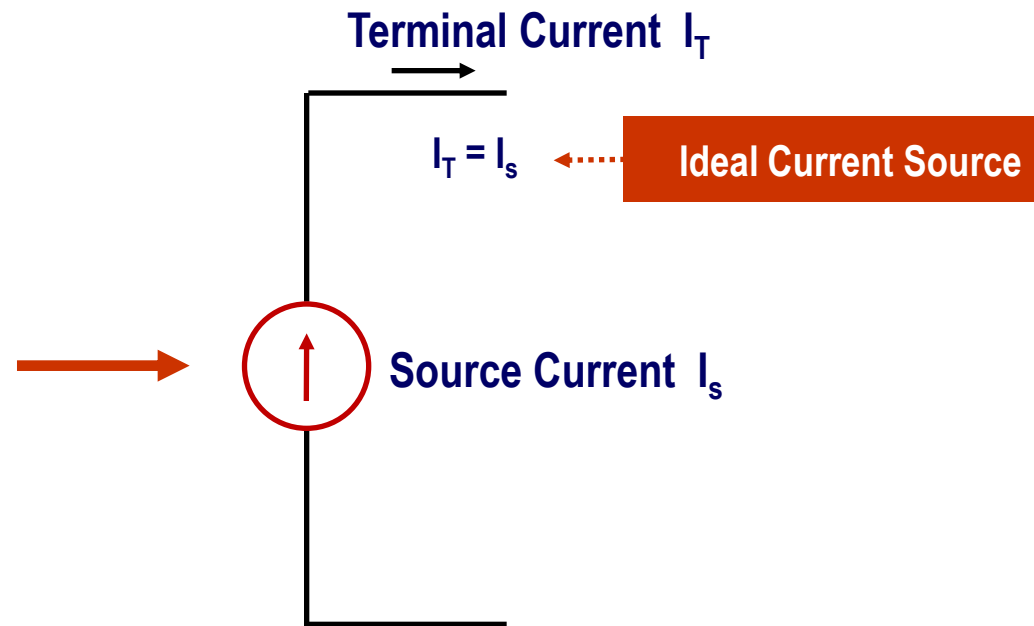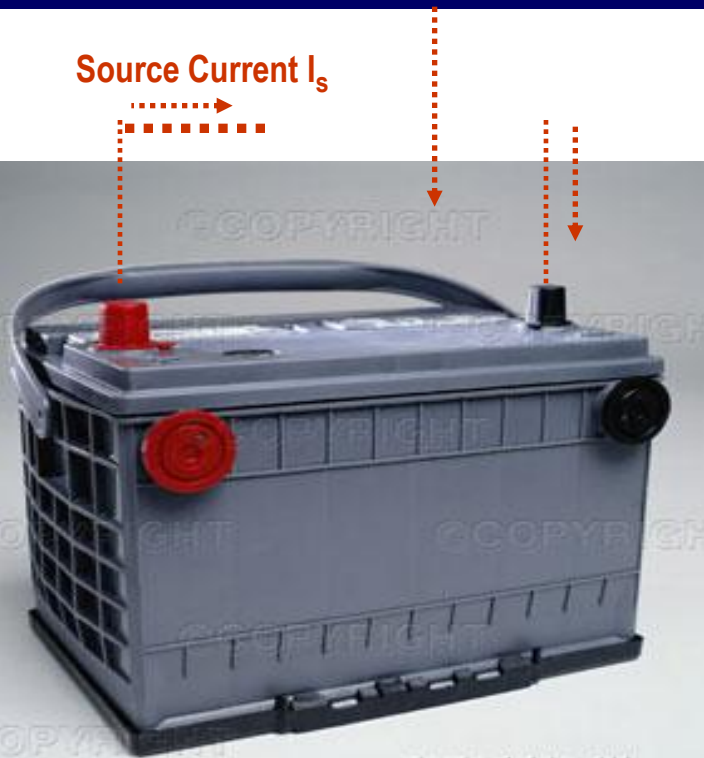An ideal current source is an element providing a constant current from its terminals



Non-Ideal (Real) Current Source

Definition


Non-Ideal Current Source

A non ideal current source is an element with a current depending on terminal voltage

Terminal Current I_T

$$I_T = I_s - \Delta I$$

$$I_T = I_s - g \times V_T$$

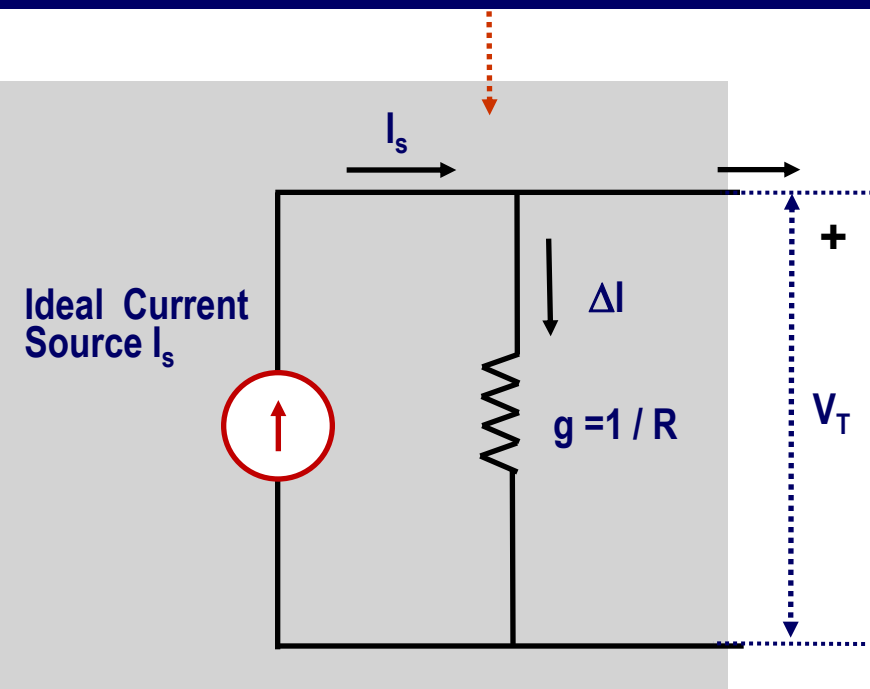

Current Source I_s




Non-Ideal (Real) Current Source

Definition: Non-Ideal Current Source

A non ideal current source is an element with a current depending on terminal voltage


Non-Ideal Current Source

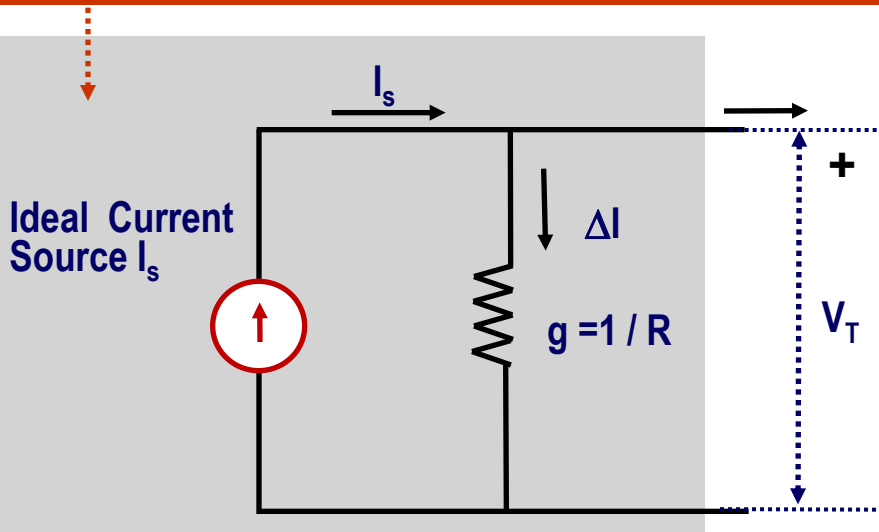

Terminal Current I_T

$$I_T = I_s - \Delta I$$

$$I_T = I_s - g \times V_T$$

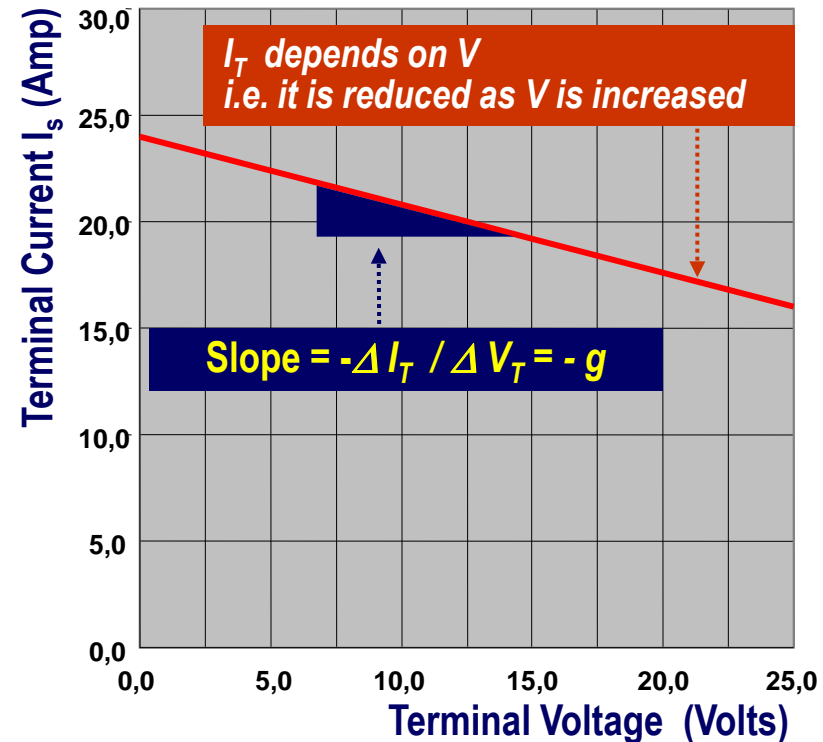


Controlled (Dependent) Sources

Definition: Controlled Sources

A controlled source is an element with a current or voltage depending on any other voltage or current in the circuit

*Controlled Source: Current $I_s = A V_x$
 $A =$ Amplification coefficient*

Voltage Controlled Current Source

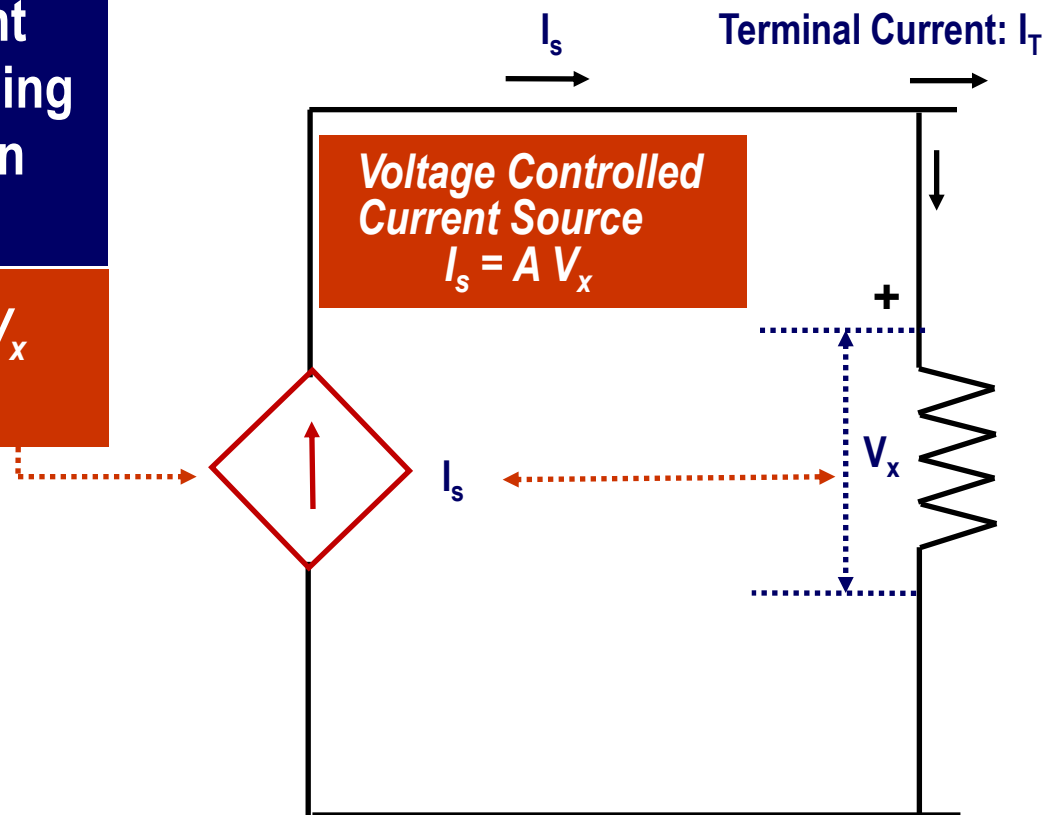


Controlled (Dependent) Sources

Definition: Controlled Sources

A controlled source is an element with a current or voltage depending on any other voltage or current in the circuit

Controlled Source: Current $I_s = A I_x$

Current Controlled Current Source

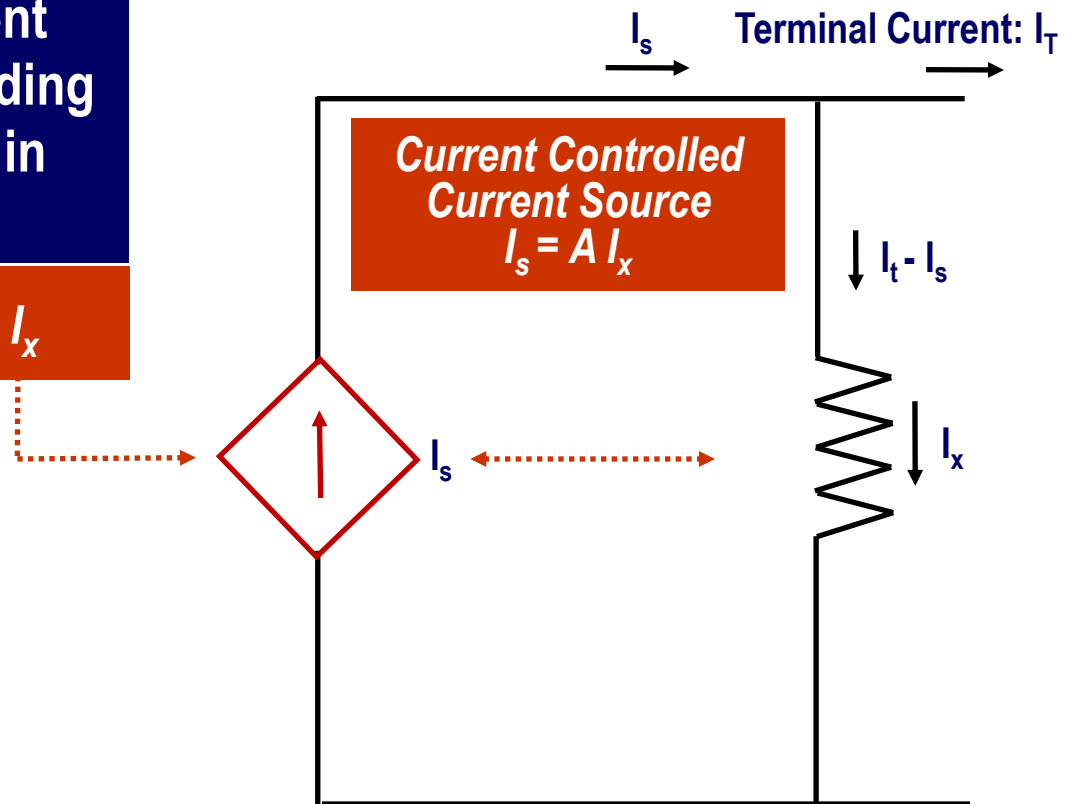


Controlled (Dependent) Sources

Definition: Controlled Sources

A controlled source is an element with a current or voltage depending on any other voltage or current in the circuit

Controlled Source: Voltage $V_s = A V_x$

Voltage Controlled Voltage Source

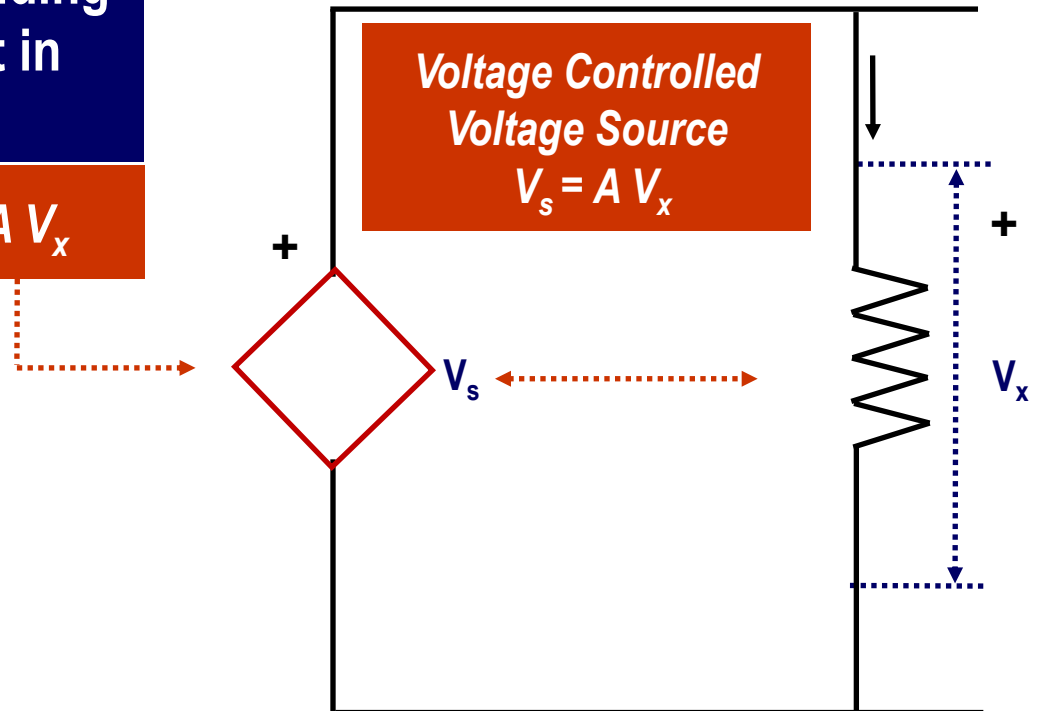


Controlled (Dependent) Sources

Definition: Controlled Sources

A controlled source is an element with a current or voltage depending on any other voltage or current in the circuit

Controlled Source: Voltage $V_s = A I_x$

Current Controlled Voltage Source

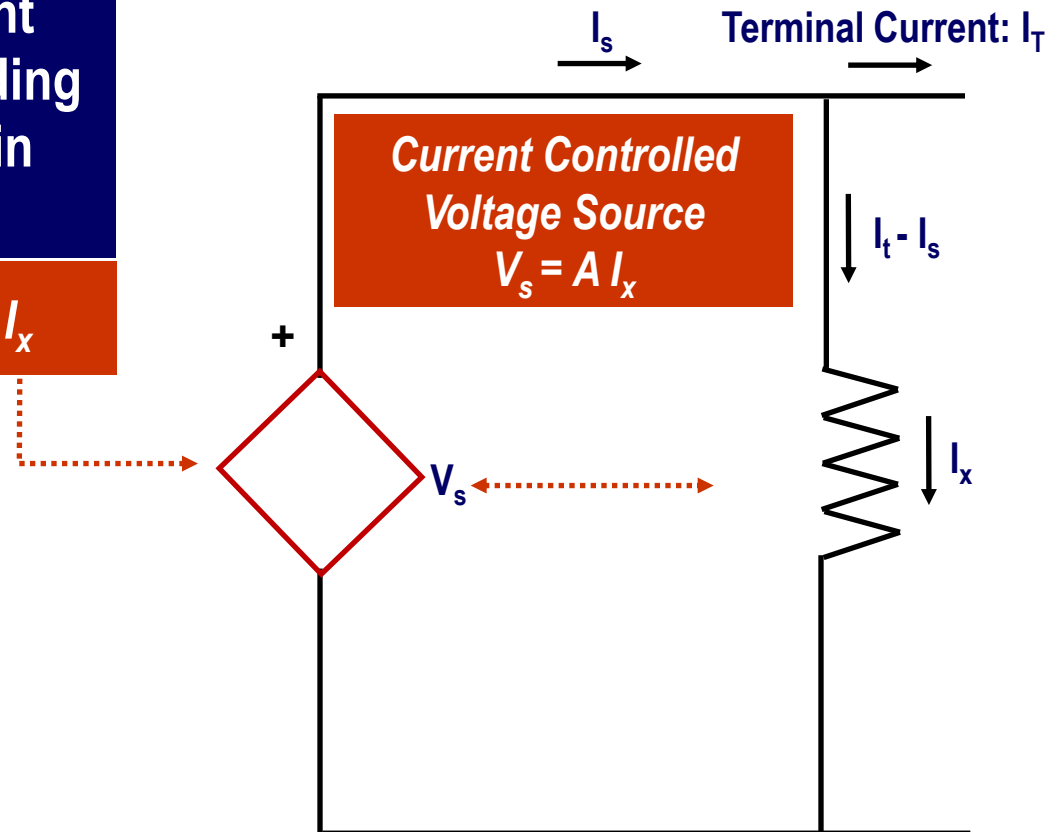

Example

Question

Solve the circuit on the RHS for current I_x

Solution


Write down KVL;

$$V_s - 10 - 2 I_x = 0$$

$$10 I_x - 10 - 2 I_x = 0$$

$$8 I_x = 10 \rightarrow I_x = 10 / 8 = 1.25 \text{ Amp}$$


Current Controlled Voltage Source

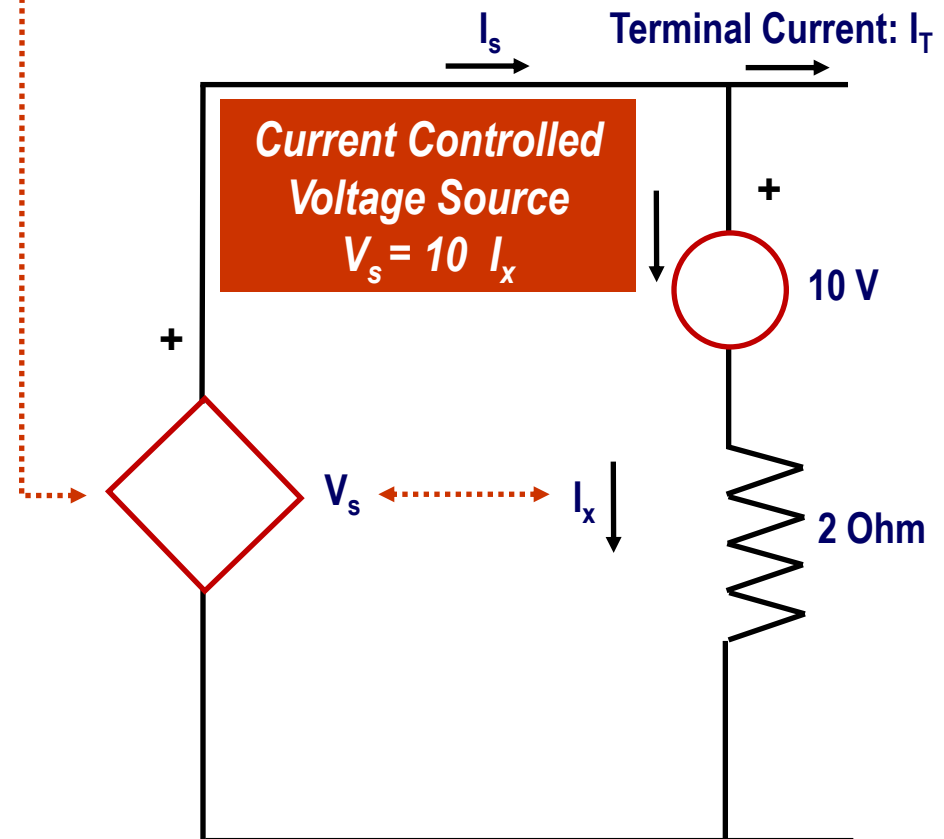

Measuring Devices - Ammeter

An ammeter is a measuring instrument used to measure the flow of electric current in a circuit. Electric currents are measured in amperes, hence the name. The word "**ammeter**" is commonly misspelled or mispronounced as "ampmeter" by some.

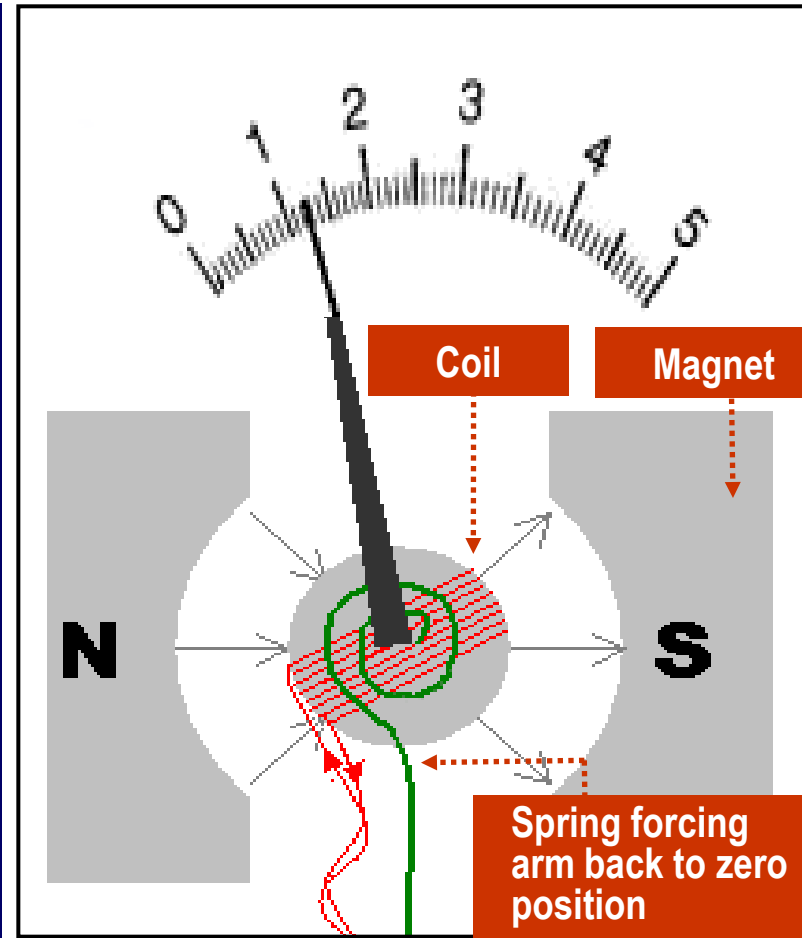The earliest design is the D'Arsonval galvanometer. It uses magnetic deflection, where current passing through a coil causes the coil to move in a magnetic field. The voltage drop across the coil is kept to a minimum to minimize resistance in any circuit into which the meter is inserted.




Measuring Devices - Ammeter

Ampere - Volt - Ohm (AVO)Meter




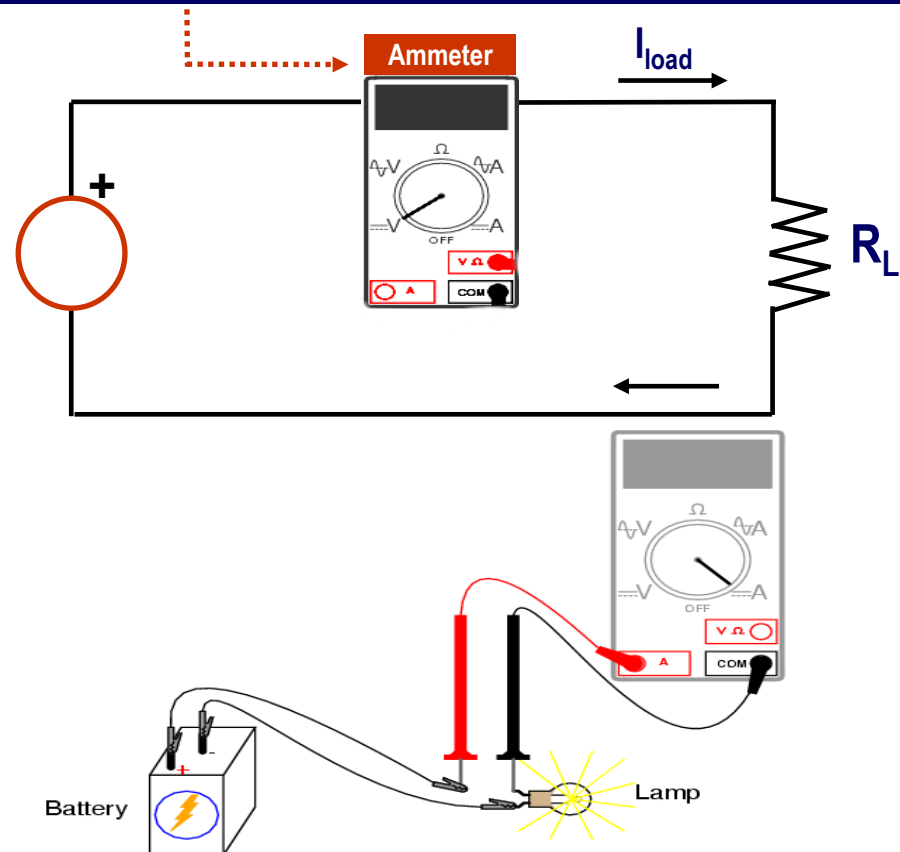
An ammeter is always series connected in the circuit measured



Measuring Devices - Ammeter

An ammeter is always series connected in the circuit measured

Internal Resistance of Ammeter

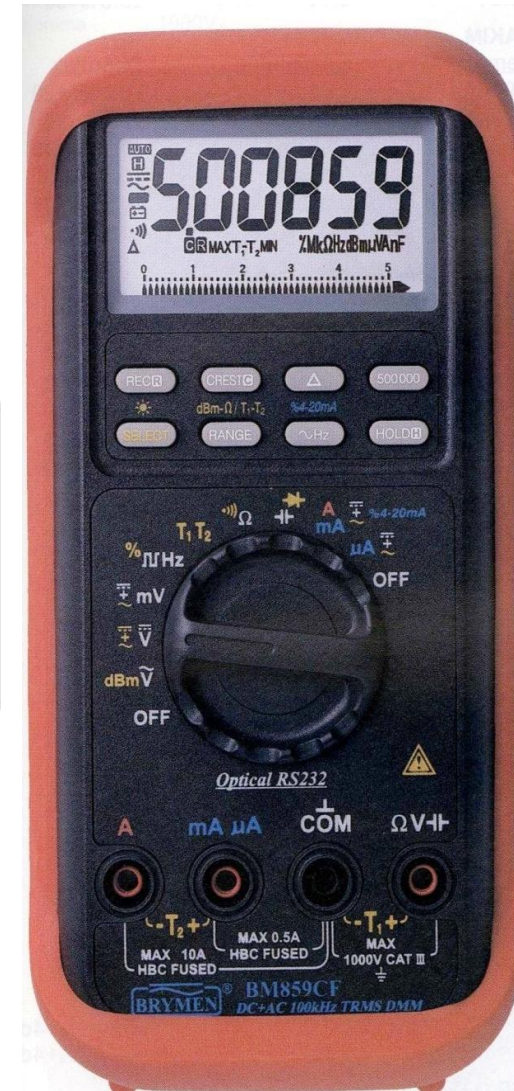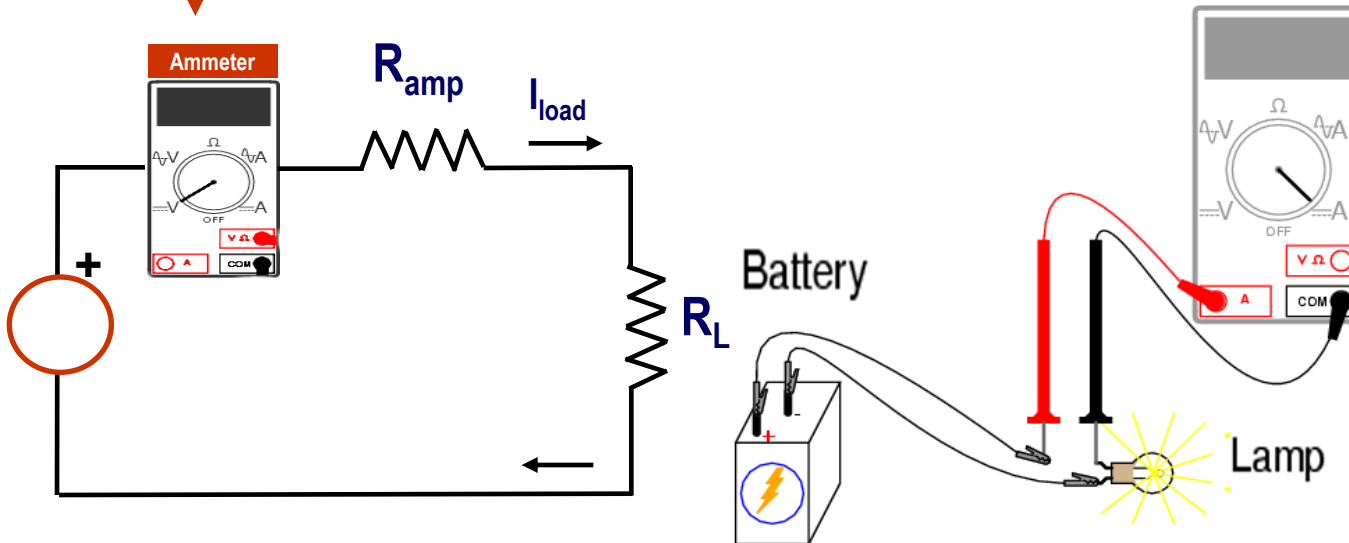


Ideal Ammeter

Definition

An ideal ammeter is the one with zero internal resistance (Short Circuit)

- An ideal ammeter behaves as a short circuit, i.e. $R_{amp} \cong 0$.
- An ideal ammeter has zero resistance so that the measured current is not influenced

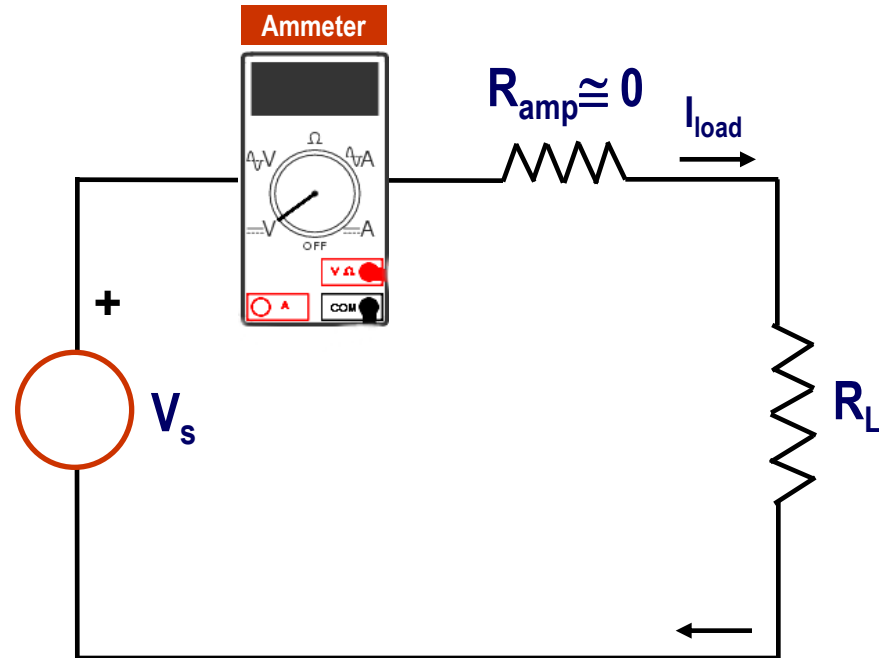No ammeter can ever be ideal, and hence all ammeters have some internal resistance




Ideal Ammeter

An ammeter should not influence the current measured

$$I = V_s / (R + R_{amp})$$
$$R_{amp} \cong 0$$

Hence,
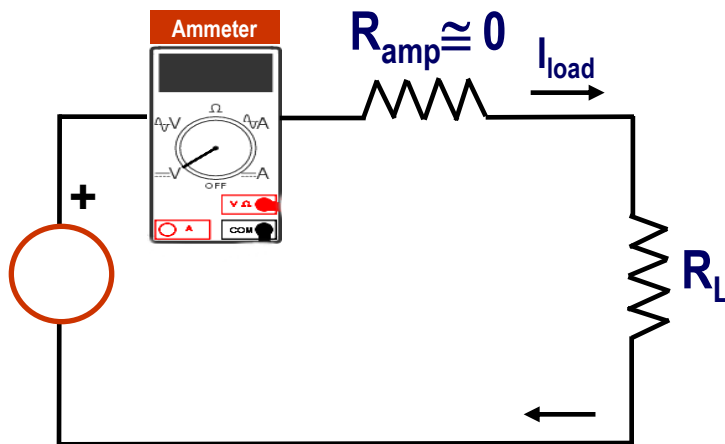
$$I = V_s / (R + R_{amp}) \cong V_s / R$$



Non-Ideal (Real) Ammeter


Definition

No ammeter can ever be ideal, and hence all ammeters have some internal resistance

A real (non-ideal) ammeter has always an internal resistance in series

- A non ideal ammeter behaves as a series resistance with: $R_{amp} \neq 0$
- Hence the the measured current is influenced (reduced)
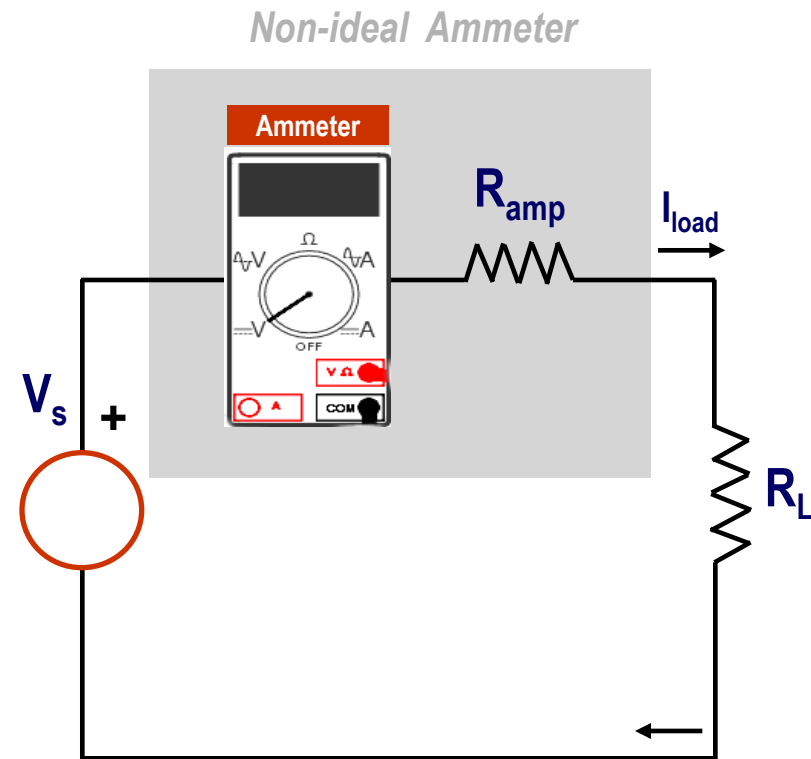
$$\left. \begin{aligned} I_{load} &= V_s / (R + R_{amp}) \\ I_{load} &= V_s / R \end{aligned} \right\} \rightarrow I_{load} < I_{ideal}$$




Measuring Devices – Clamp Ammeter

The Need for Clamp Ammeter

Sometimes the electrical service carried out by the circuit may be so vital that it can not be interrupted by breaking the line for a series connection of the ammeter

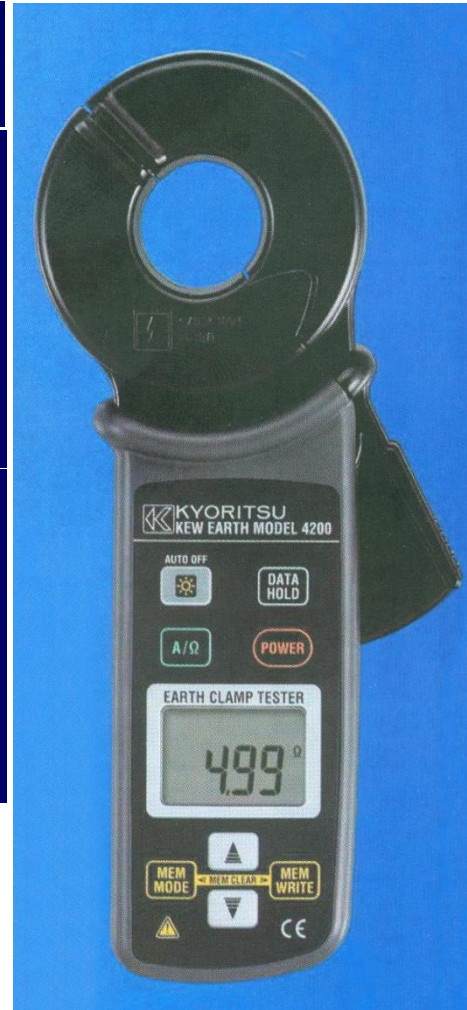Ammeter shown on the RHS is a particular design for such circuits to measure current flowing in the circuit as well as resistance without braeking the circuit




Measuring Devices - Voltmeter

A voltmeter has a high internal resistance so that it passes only a small current

An ideal voltmeter has a very large resistance so that the the circuit in which it has been placed is not disturbed

An ideal voltmeter is an open circuit

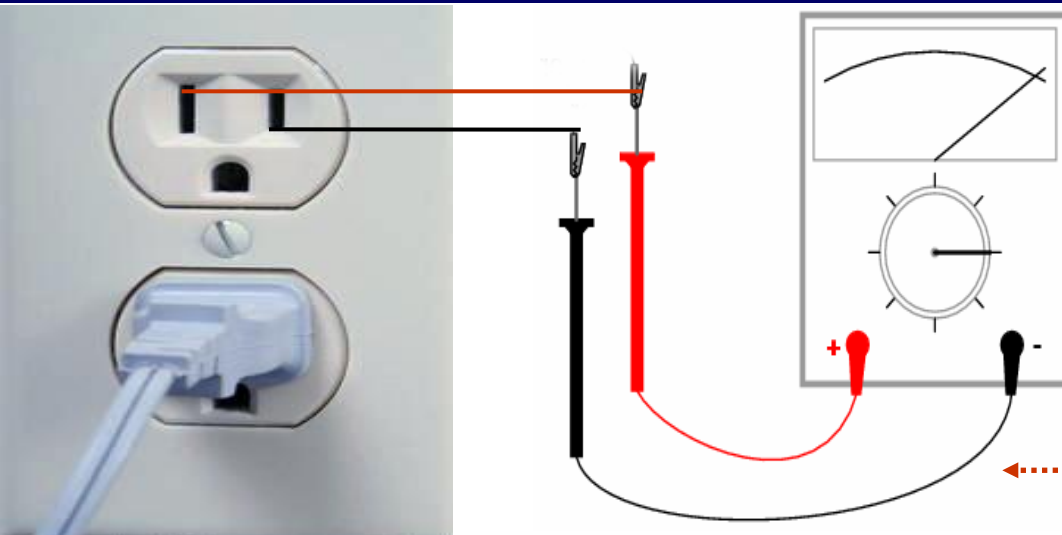However, no voltmeter can ever be ideal, and therefore all voltmeters draw some small current



Voltmeter is always parallel connected to the terminals measured

Measuring Devices - Voltmeter


A voltmeter has a high internal resistance so that it passes only a small current

A voltmeter is always shunt (parallel) connected in the circuit that it measures

Measured voltage;

$$V_o = V_s \frac{R_L}{R_1 + R_L}$$

Red lines are not part of the circuit

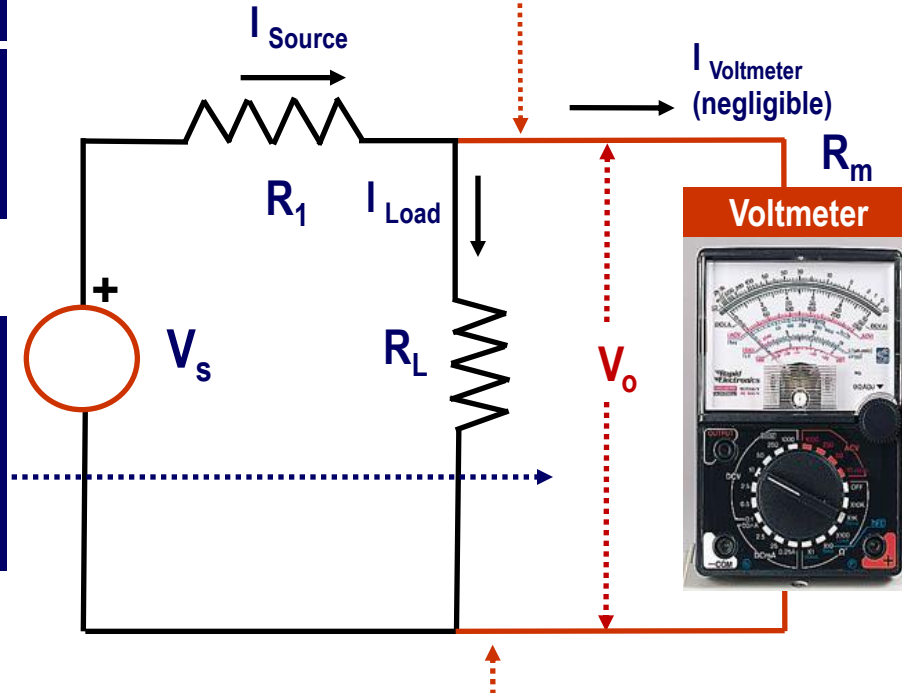

Voltmeter is always parallel connected to the terminals measured

Ideal Voltmeter


Definition

An ideal voltmeter is the one with infinite internal resistance (Open circuit)

An ideal voltmeter has a very large resistance, $R_m \cong \infty$. i.e. it behaves as an open circuit, so that the the measured circuit is not influenced

However, no voltmeter can ever be ideal, and therefore all voltmeters draw some current

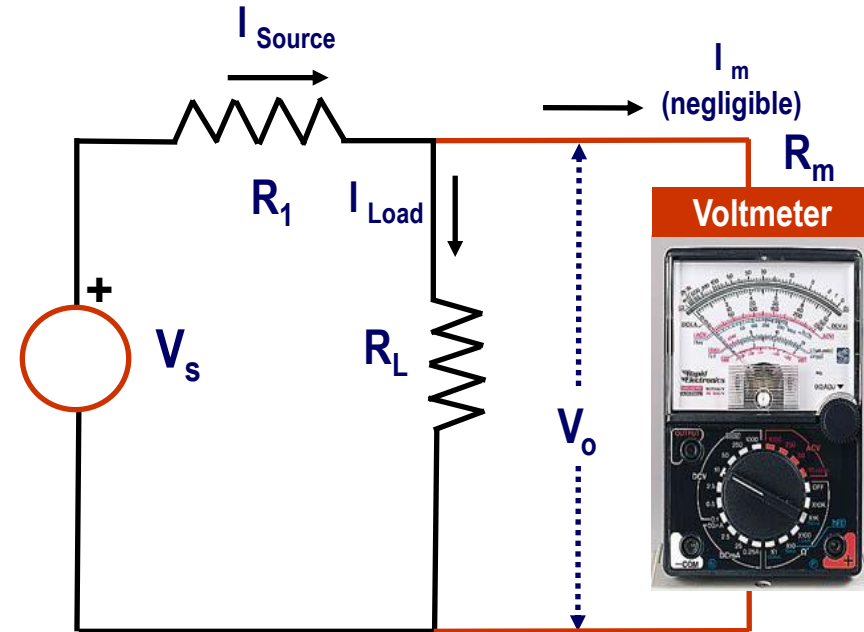A real voltmeter has a certain internal resistance so that it passes a certain current



Ideal Voltmeter

No voltmeter can ever be ideal, and therefore all voltmeters draw some current.

$$R_m \cong \infty \quad \text{i.e.} \quad R_m \gg R_L$$

$$I_m \ll I_{Load}$$


$$I_{Source} = I_{Load} + I_m \cong I_{Load}$$

$$V_o = R_L (I_{source} - I_m)$$

$$= R_L I_{Source} - R_L I_m$$

$$\cong R_L I_{Source}$$

Negligible

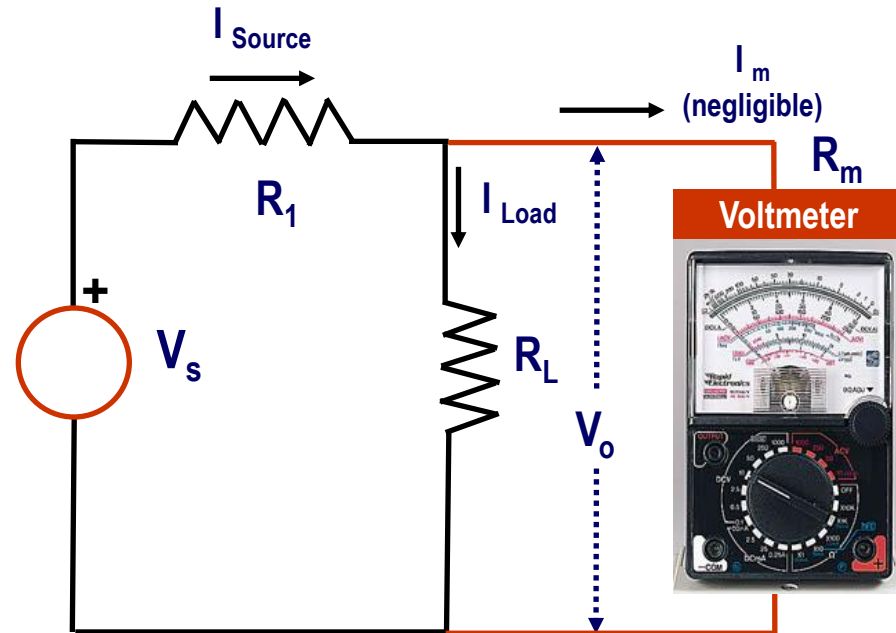

Example


Problem

Calculate the internal admittance g_m of a voltmeter, if it reads 11.81 Volts when connected to a 0.48 mA current source with an internal admittance of $g_s = 4 \times 10^{-5}$ Siemens

Siemens = $1/\Omega$

Ideal Voltmeter

$I_m \approx 0$

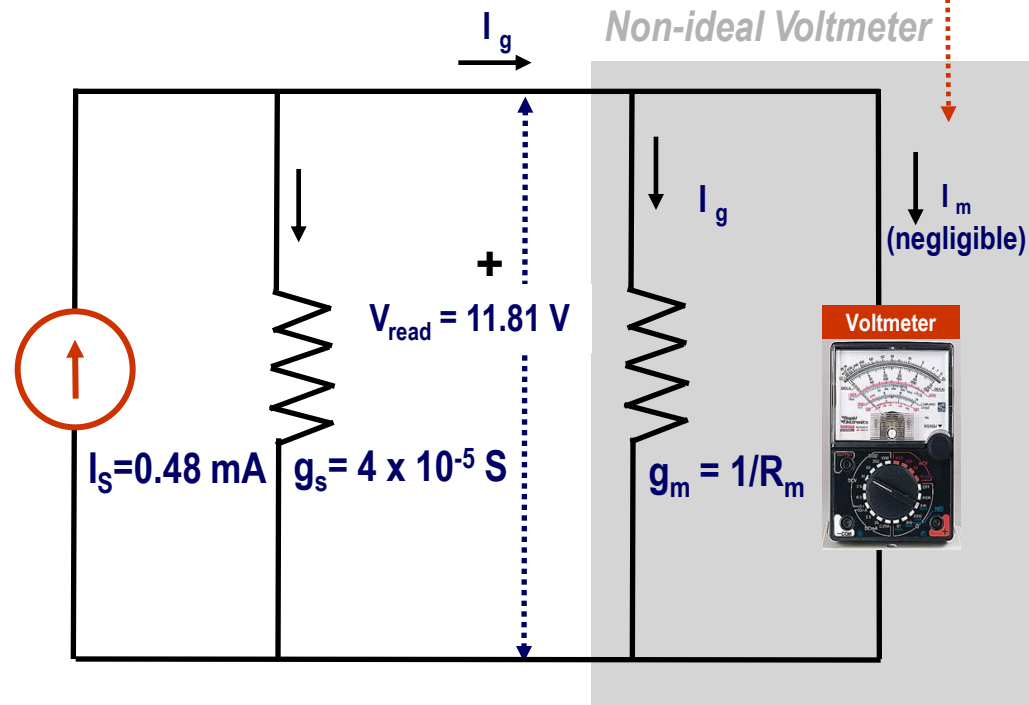

Example

Problem

$$R_s = 1/g_s = 1/(4 \times 10^{-5}) \text{ Siemens} \\ = 10^5 / 4 = 25 \text{ k}\Omega$$

$$I_s \times R_{eq} = V_{read} = 11.81 \text{ Volts}$$

Hence,

$$R_{eq} = V_{read} / I_s = 11.81 / (0.48 \times 10^{-3}) \\ = 24607.17 \Omega$$

$$R_{eq} = R_s // R_m$$


Hence,

$$R_{eq} = (R_s \times R_m) / (R_s + R_m) = 24607.17 \Omega$$

$$R_m = 155.39 \text{ M}\Omega$$

Ideal Voltmeter

$$I_m \approx 0$$

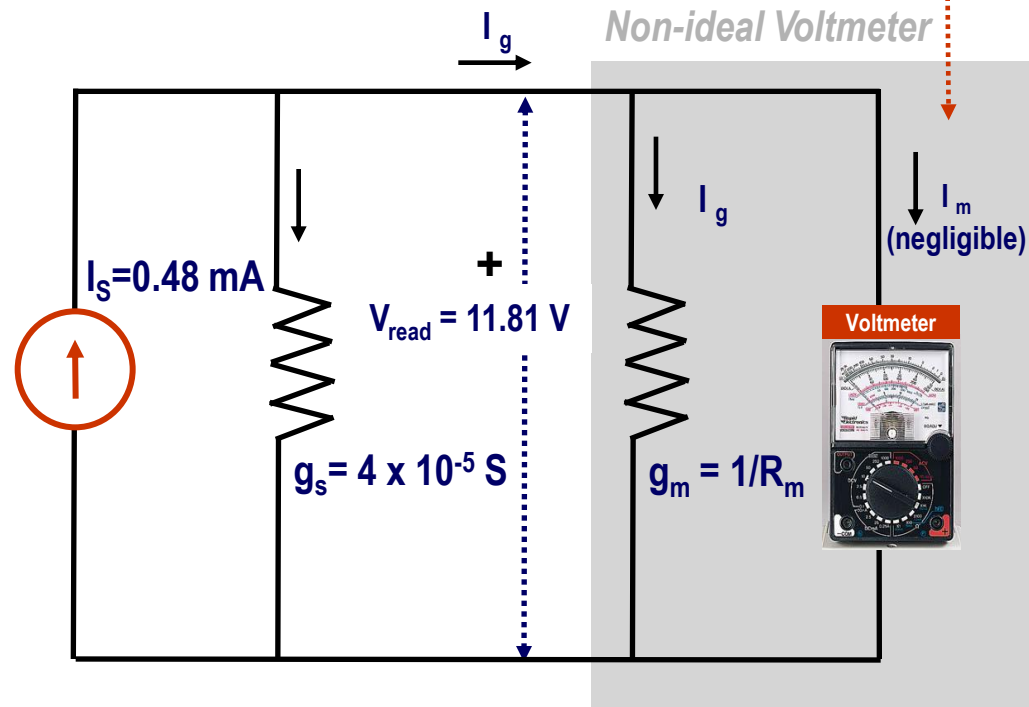

Advanced Measuring Devices

Power Quality Analyzer

GÜÇ KALİTESİ ANALİZÖRÜ



Fluke 43Basic
Fluke 43B
Fluke 43Kit




Power Quality Analyzer
Power Quality Analyzer
Power Quality Analyzer



Wheatstone Bridge

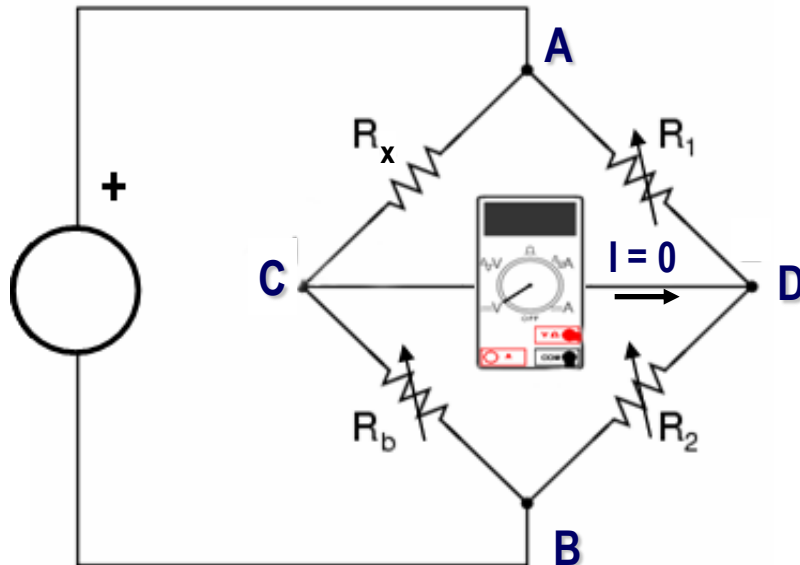The Wheatstone Bridge is an electrical circuit used to determine an unknown resistance R_x by adjusting the values of known resistances, so that the current measured in the line connecting the terminals C and D is zero



Wheatstone Bridge

Principle


Adjust the resistances R_1 , R_2 and R_b such that the ammeter connected between the terminals C and D reads zero current

Hence, the voltage difference between the terminals C and D is zero

$$\Delta V_{CD} = 0$$

or

$$V_C = V_D$$

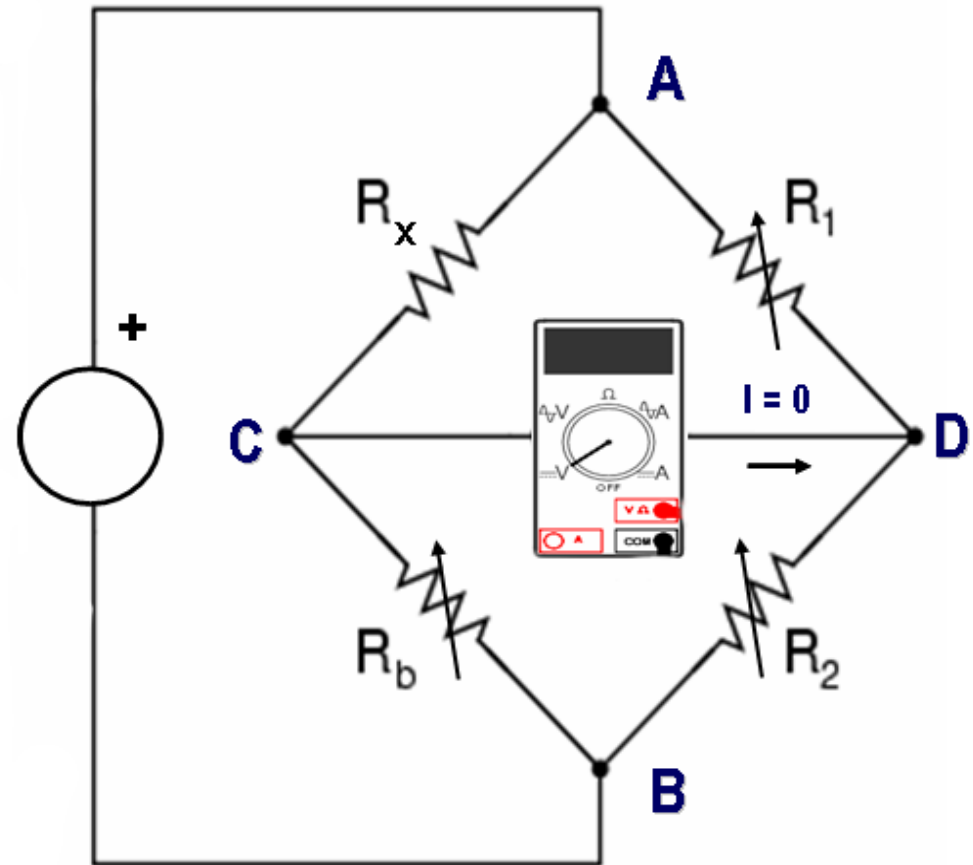

Wheatstone Bridge

Principle

$$V_C = V_D$$

$$V_C = V_s R_b / (R_x + R_b)$$

$$V_D = V_s R_2 / (R_1 + R_2)$$

$$V_s R_b / (R_x + R_b) = V_s R_2 / (R_1 + R_2)$$

or


$$R_b / (R_x + R_b) = R_2 / (R_1 + R_2)$$

$$R_b (R_1 + R_2) = R_2 (R_x + R_b)$$

$$R_b R_1 + R_b R_2 = R_2 R_x + R_2 R_b$$

or

$$R_x = R_b \times R_1 / R_2$$

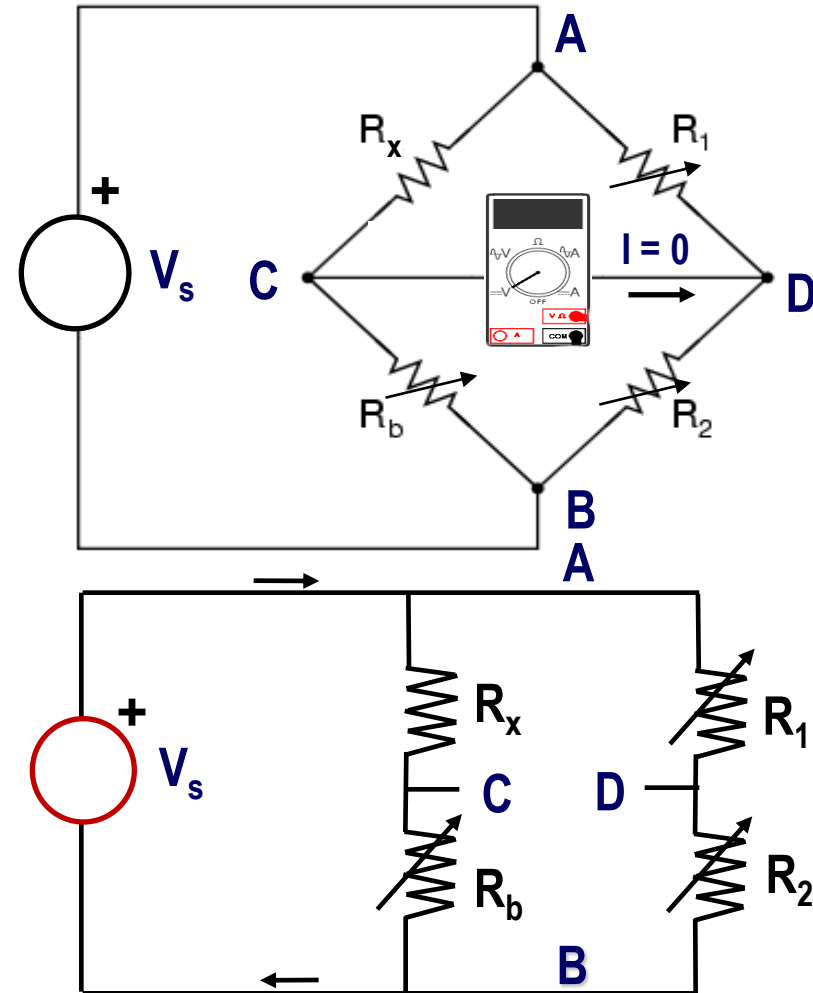


Wheatstone Bridge

Basic Rule

Cross multiplication branch resistances must be equal at balance condition

$$R_x \times R_2 = R_b \times R_1$$

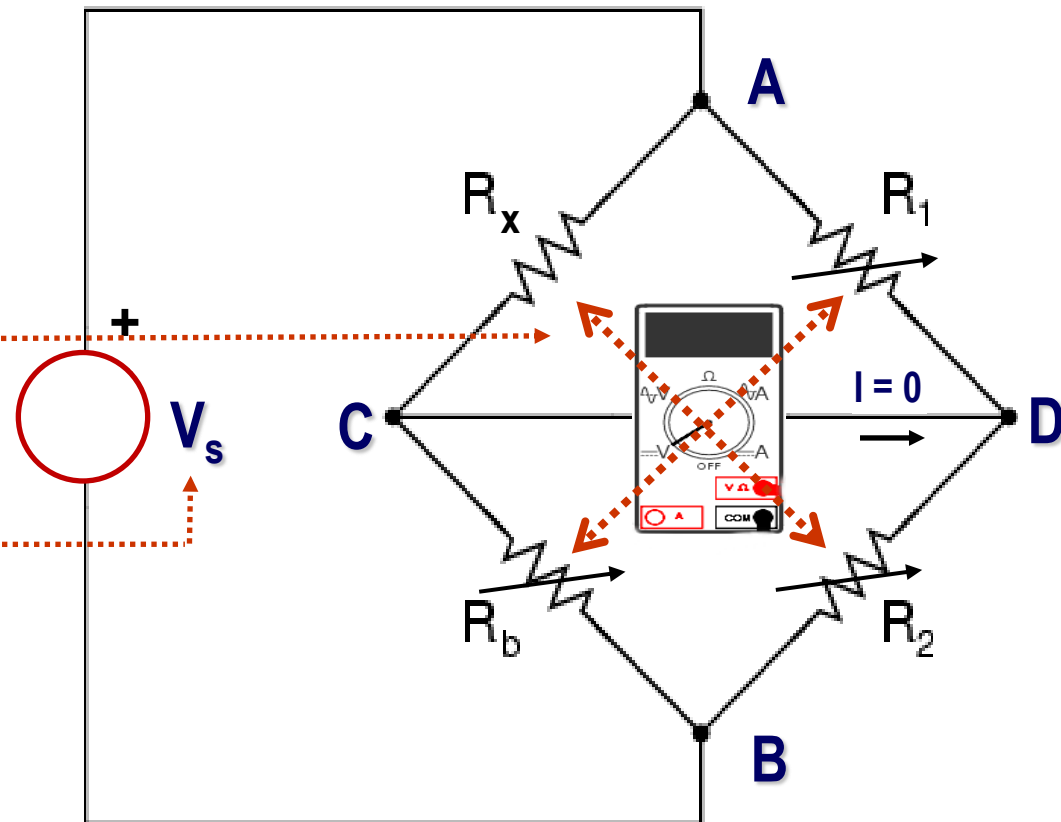Please note that voltage V_s is neither used, nor needed in the above equation, i.e. its value is arbitrary



Wheatstone Bridge

Example


Calculate the value of unknown resistance R_x in the balanced Wheatstone Bridge shown on the RHS

Cross multiplication of branch resistances must be equal at balance condition:

$$R_x \times R_2 = R_b \times R_1$$


$$R_x = R_b \times R_1 / R_2$$
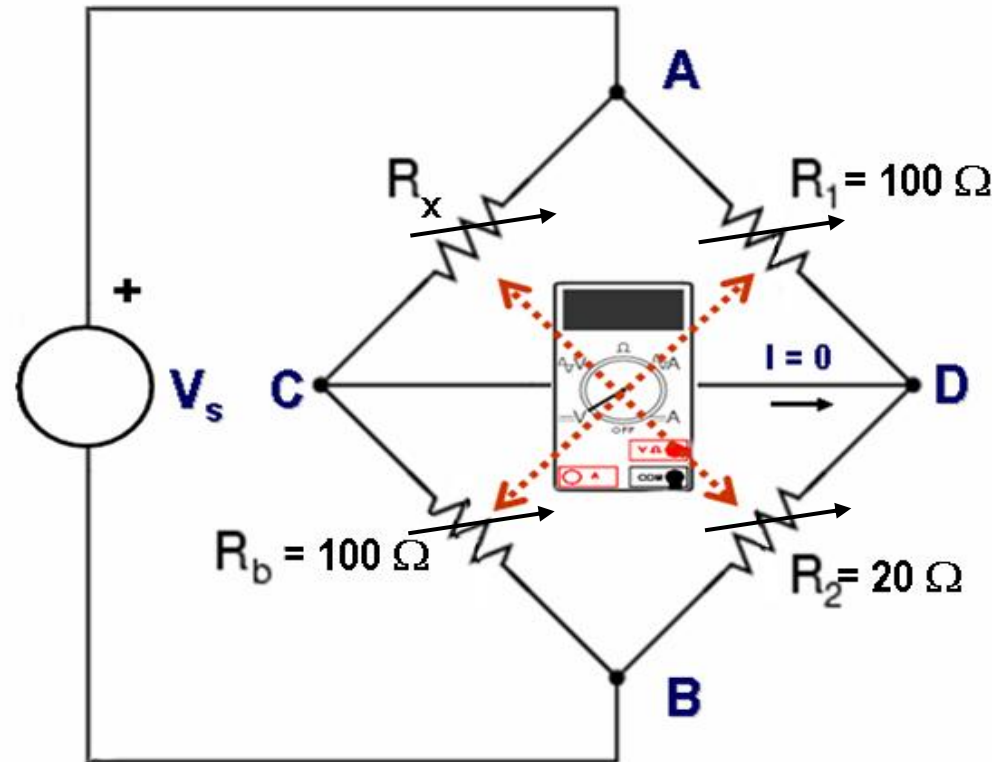
$$= 100 \times 100 / 20 = 500 \text{ Ohm}$$




Switch - Circuit Breaker

Switch or Circuit Breaker

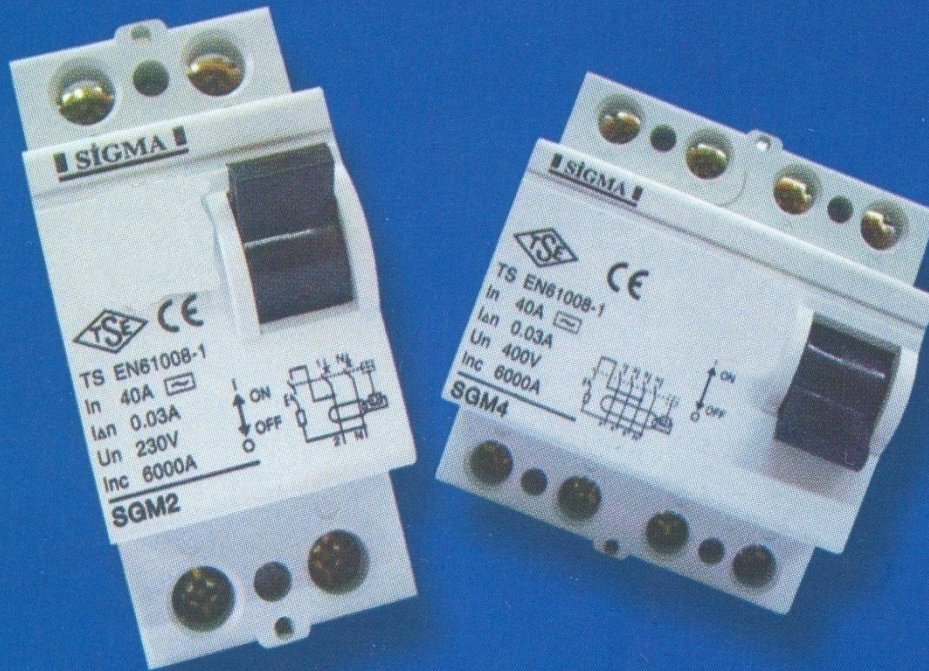

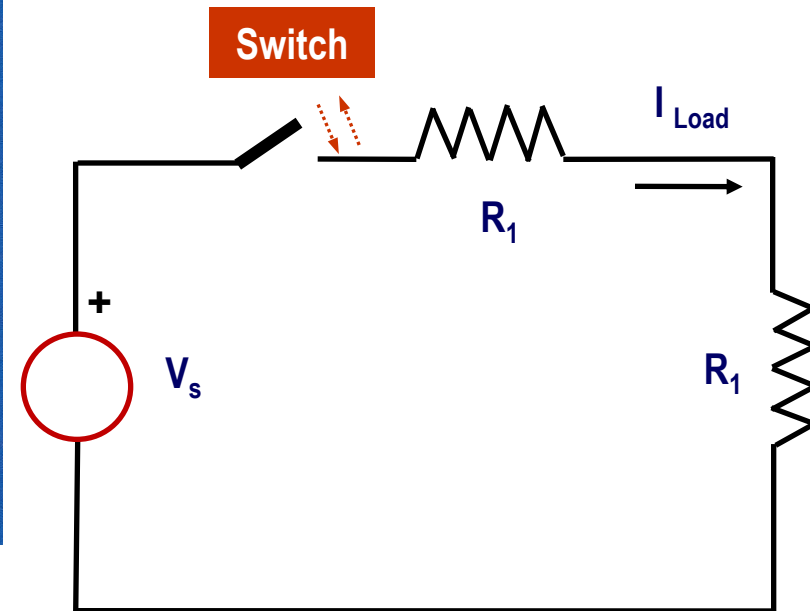Switch or circuit breaker is a device used to open an electrical circuit manually or automatically by an electronic relay system






Open
"Off"




Closed
"On"

Meaning of “Open” and “Closed” (Highly Important)

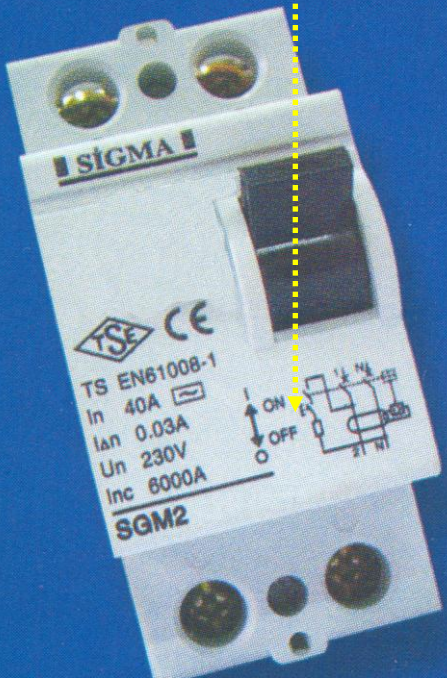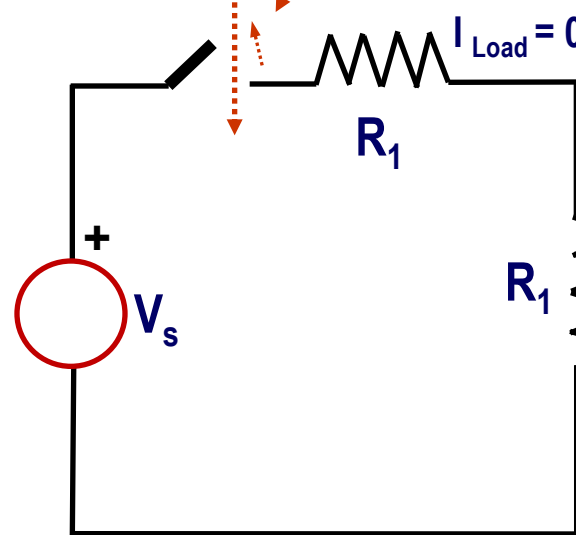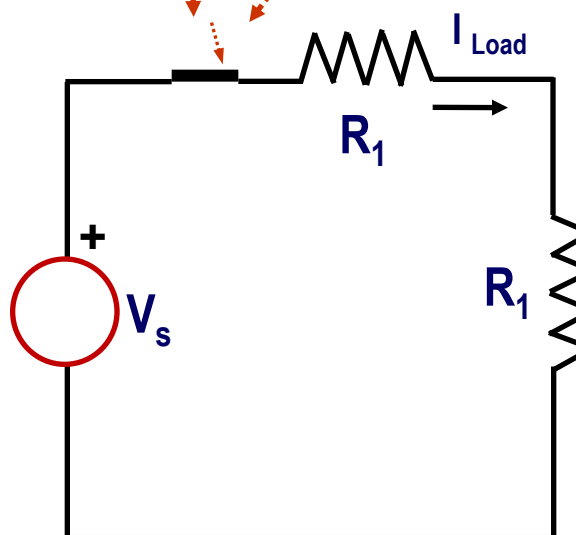Breaker	Open Circuit or Switch		Closed Circuit or Switch	
Open (On), Closed (Off)	Open Circuit	Open (Off) Switch	Closed Circuit	Closed (On) Switch
				
<p><u>“Closed Switch (On)” does NOT mean that there is no voltage (current) in the circuit !</u></p>				

Thermal-Magnetic Circuit Breaker

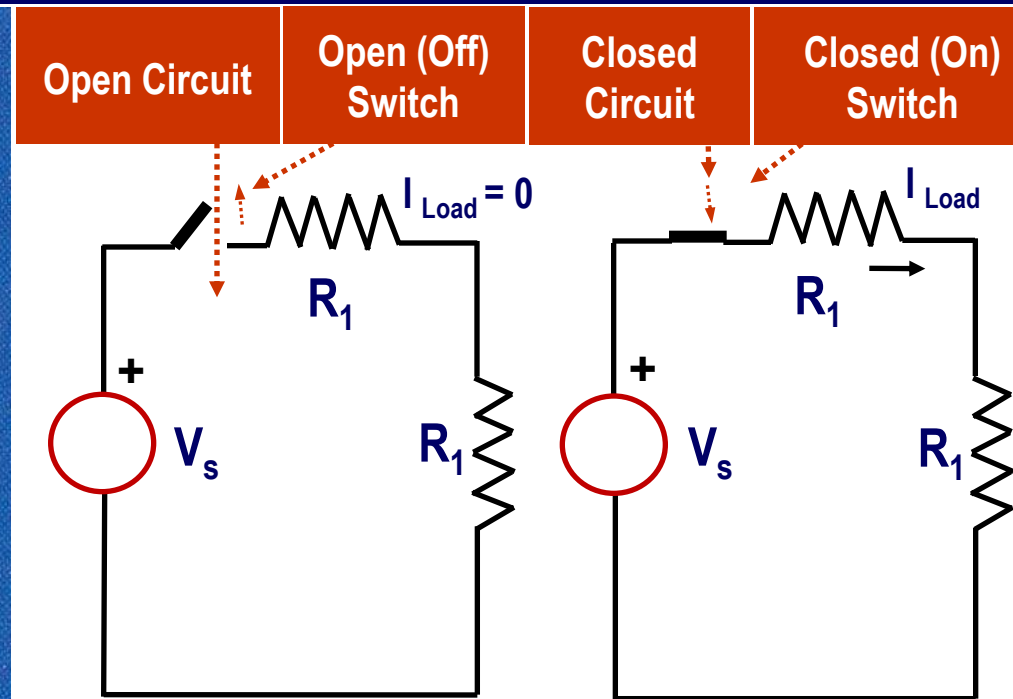
220 Volt, 63 Amp. Thermal-Magnetic (Molded-Case) Breaker



“Closed Switch (On)” does NOT mean that there is no voltage (current) in the circuit !

Medium Voltage (36 kV) Vacuum Circuit Breaker

Open Circuit

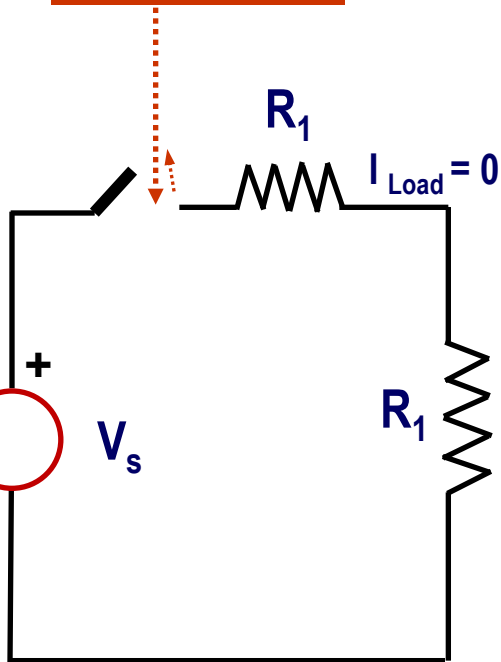

Vacuum tube enclosing
breaker poles

Tripping buttons

Spring handle (taken off)

