





Course Title and Code Number:
Principles and Applications of Electronic Engineering
Second Year (Agricultural Engineering)
Time Allowed: Two hours

اسم المقرر والرقم الكودي له:
مبادئ الهندسة الإلكترونية وتطبيقاتها
السنة الدراسية الثانية (هندسة زراعية)
الزمن: ساعتين


Answer All Questions (Each Question is 30 marks):

(180 marks)

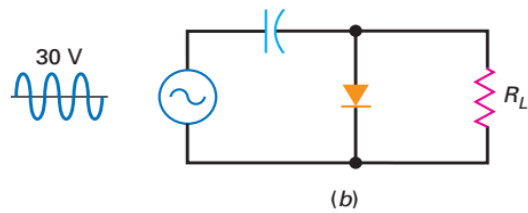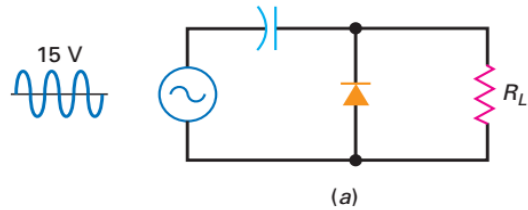
1. For the circuit shown in Figure 1:
 - a. Sketch the output waveform of Figure (a). What is the maximum positive and negative voltages?
 - b. Sketch the output waveform of Figure (b). What is the maximum positive voltage? The maximum negative?
 - c. Sketch the output waveform of the clamper and final output in Figure (c). What is the DC output voltage with ideal diodes? To a second approximation?




1

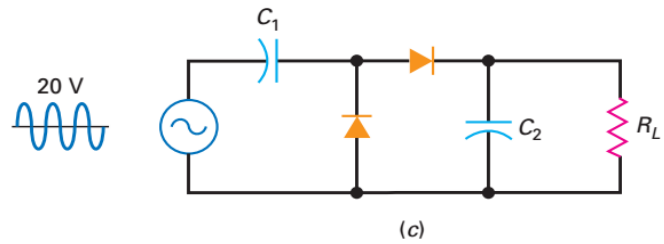

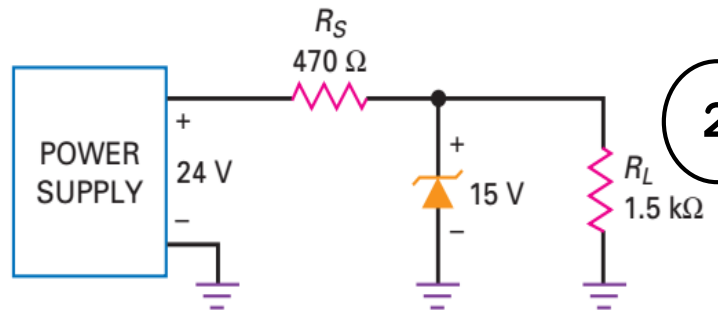
2. For the circuit shown in Figure 2:
 - a. Calculate all three currents.
 - b. If the Zener diode is disconnected, what is the load voltage?
 - c. If the Zener diode has a resistance of 14Ω , and the power supply has a ripple of $1 V_{p-p}$, what is the ripple across the load resistor?



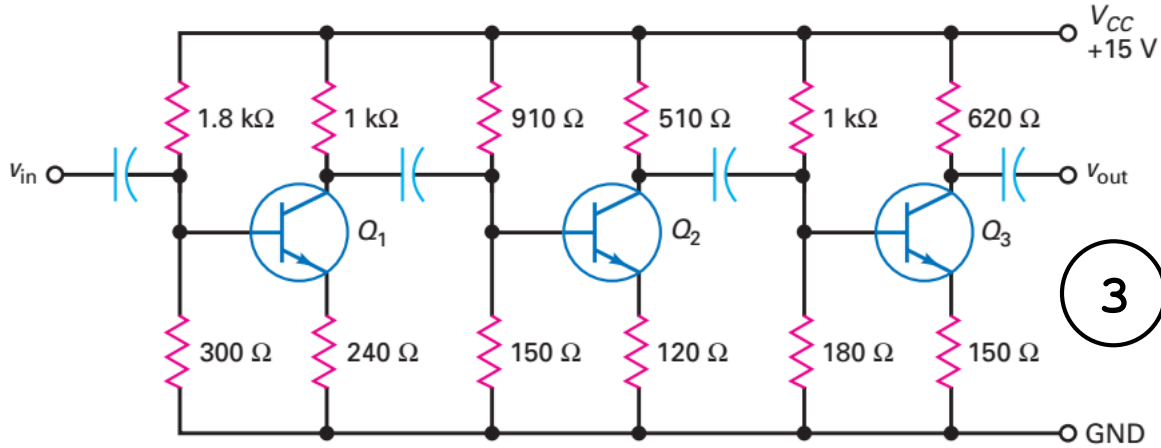3. Determine the mode of operation and calculate the collector voltage for each transistor in Figure 3 ($\beta=100$ for Q_1, Q_2, Q_3). Calculate the output voltage v_{out} for input voltage v_{in} of 0V. What is the name of this biasing method?



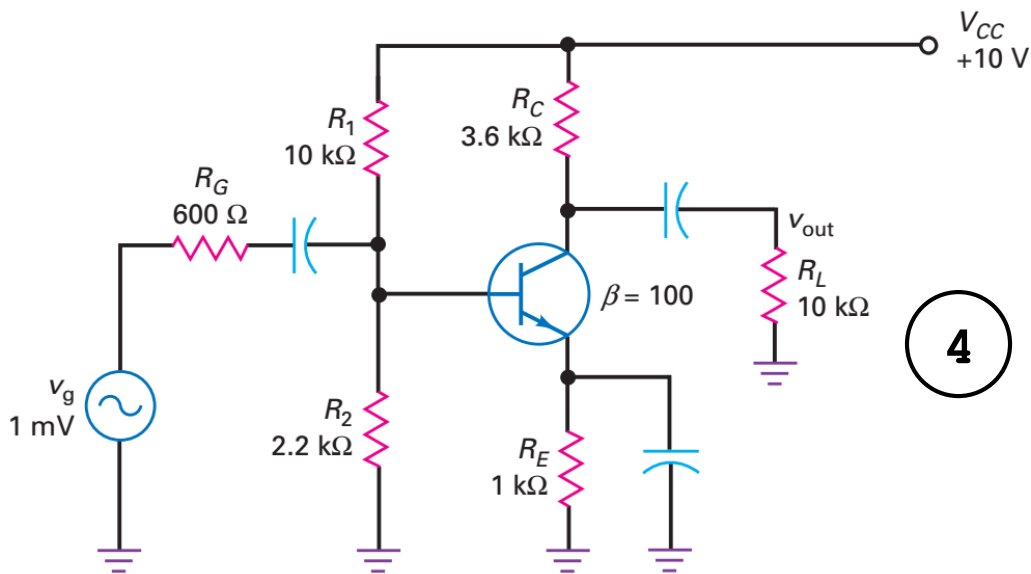4. For the circuit shown in Figure 4:
- Draw the load line. What is the collector current at the saturation point? The collector-emitter voltage at the cutoff point?
 - What is the ac resistance of the emitter diode?
 - What is the input impedance of the base?
 - Draw the ac-equivalent circuit of this amplifier and find the output voltage and ac voltage gain.



5. For the circuit shown in Figure 5:
- Is this an inverting or non-inverting amplifier?
 - Find the voltage gain v_o/v_{in}
 - Calculate the voltage gain v_o/v_{in} for $R_1=10\text{ k}\Omega$, $R_2 = 100\text{ k}\Omega$
 - Find the input resistance

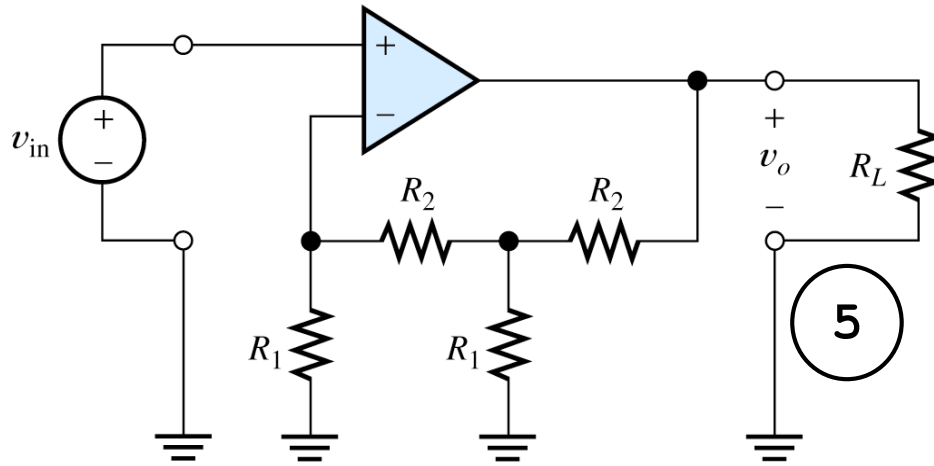


Figure 14.15 Circuit for Exercise 14.6.

6. Find the voltage gain $A_v = v_o/v_{in}$ and input impedance for the amplifier shown in Figure 6.
- With the switch open
 - With the switch closed
 - Is this an inverting or non-inverting amplifier?

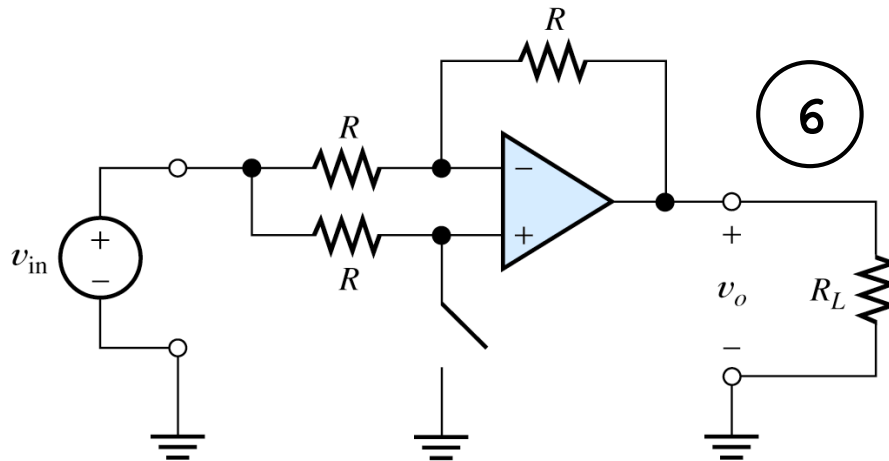


Figure 14.13 Inverting or noninverting amplifier. See Exercise 14.4.