

MALVINO & BATES

**Electronic
PRINCIPLES**

SEVENTH EDITION



Introduction




Topics Covered in Chapter 1

- **Three kinds of formulas**
- **Approximations**
- **Voltage sources**
- **Current sources**
- **Thevenin's Theorem**
- **Norton's Theorem**
- **Troubleshooting**

Three kinds of formulas


The definition: Invented for a new concept

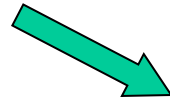
$$C = \frac{Q}{V} \quad \left\{ \begin{array}{l} \text{defines what capacitance is} \\ \text{does not require verification} \end{array} \right.$$

The law: Summarizes a relationship that exists in nature



$$f = K \frac{Q_1 Q_2}{d^2} \quad \{ \text{verified by experiment} \}$$

The derivation: Obtained by manipulating other formulas using mathematics

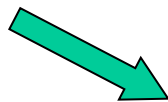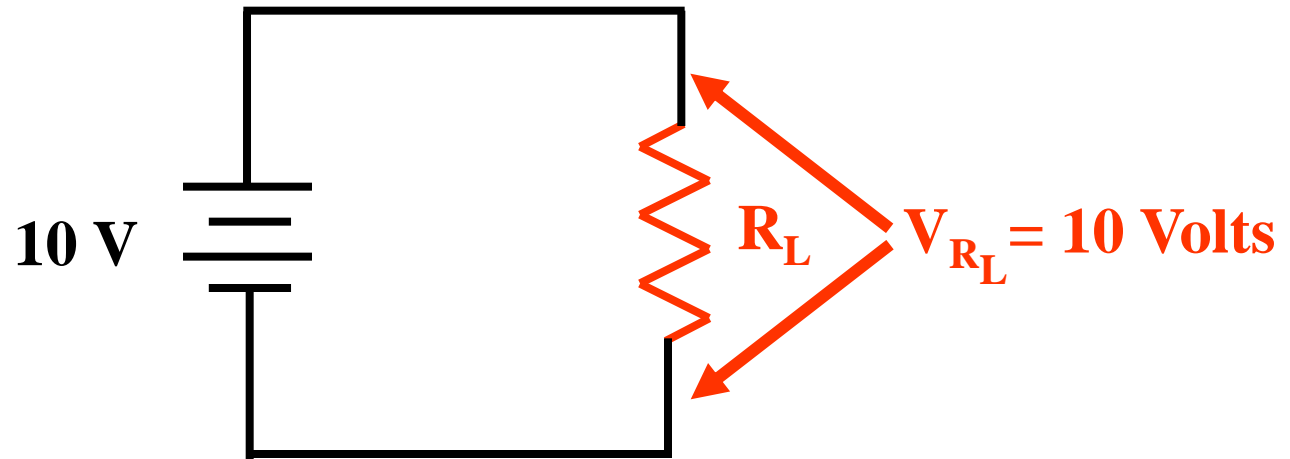
$$Q = CV$$

Ideal voltage source

Maintains a constant output voltage, regardless of the value of R_L .



The ideal model can be called
the first approximation.

Approximations


- **Widely used in industry**
- **Useful for troubleshooting**
- **Useful for circuit calculations**

Voltage Sources

- An **ideal** source has no internal resistance
- The **second** approximation of a voltage source has internal resistance
- A stiff voltage source has an internal resistance that is **1/100** of load resistance

Real Voltage Source

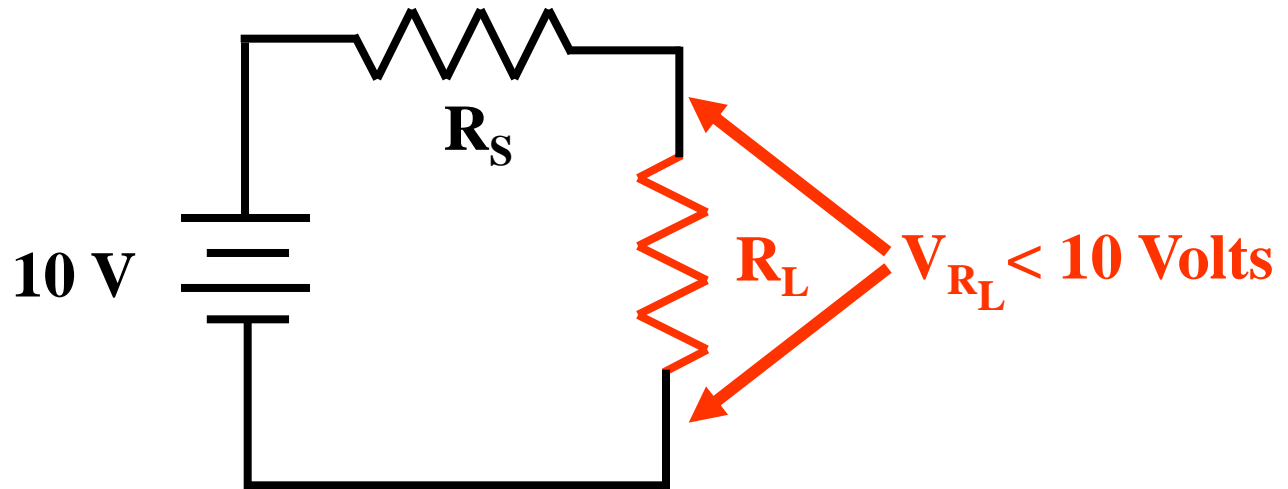Has an internal resistance in series with the source




This model is called the
the second approximation.

When R_L is equal to or greater than 100 times R_S , a real voltage source is *stiff* and the first approximation can be used.

Ideal current source

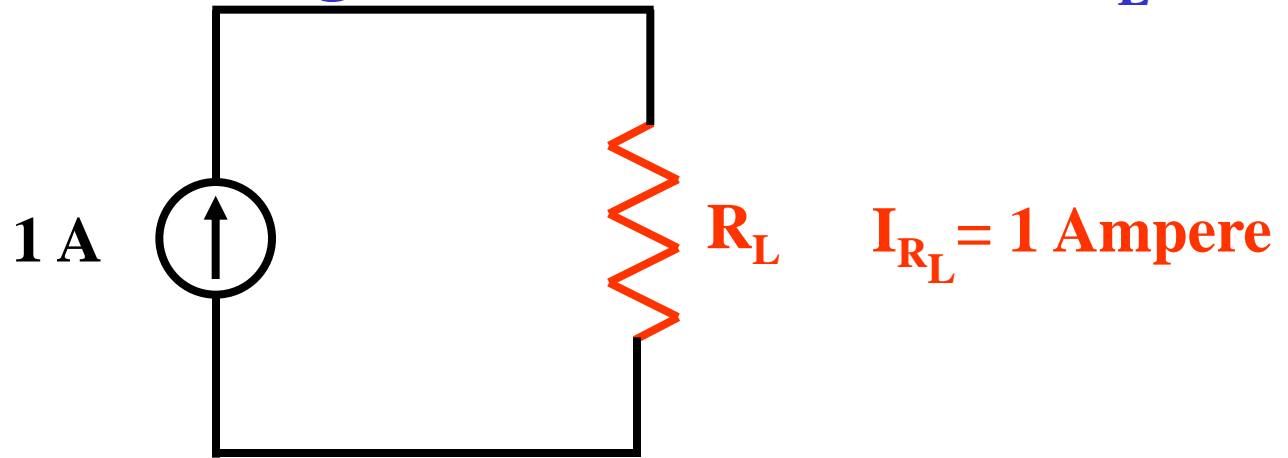
Maintains a constant output current, regardless of the value of R_L .



The ideal model can be called *the first approximation*.

Real current source

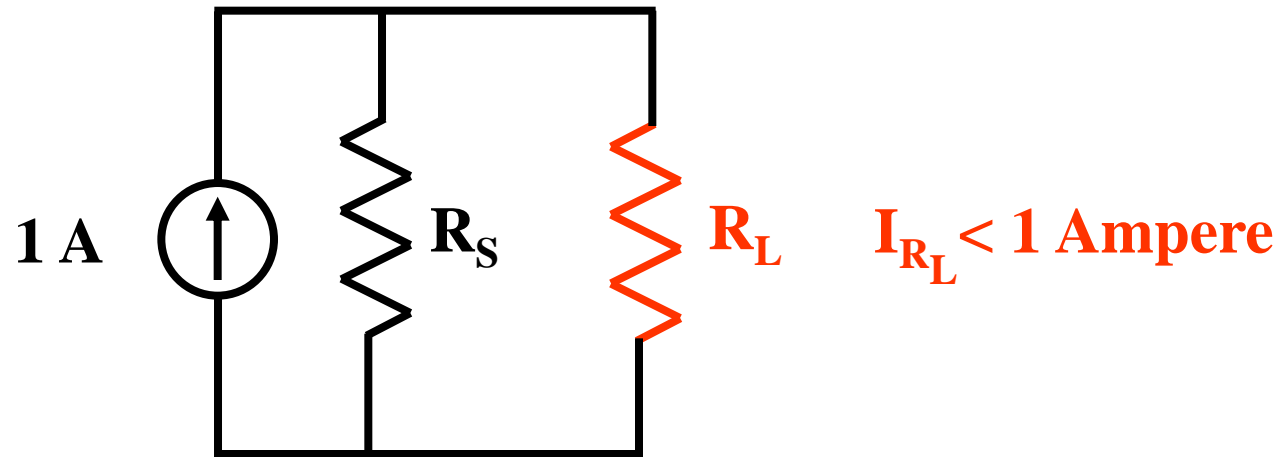Has a large internal resistance
in parallel with the source



This model is called the
the second approximation.


When R_S is equal to or greater than 100 times R_L , a real current source is *stiff* and the first approximation can be used.

Thevenin's Theorem


- Used to replace any linear circuit with an equivalent voltage source called V_{TH} and an equivalent resistance called R_{TH}

Thevenin Example

Original Circuit

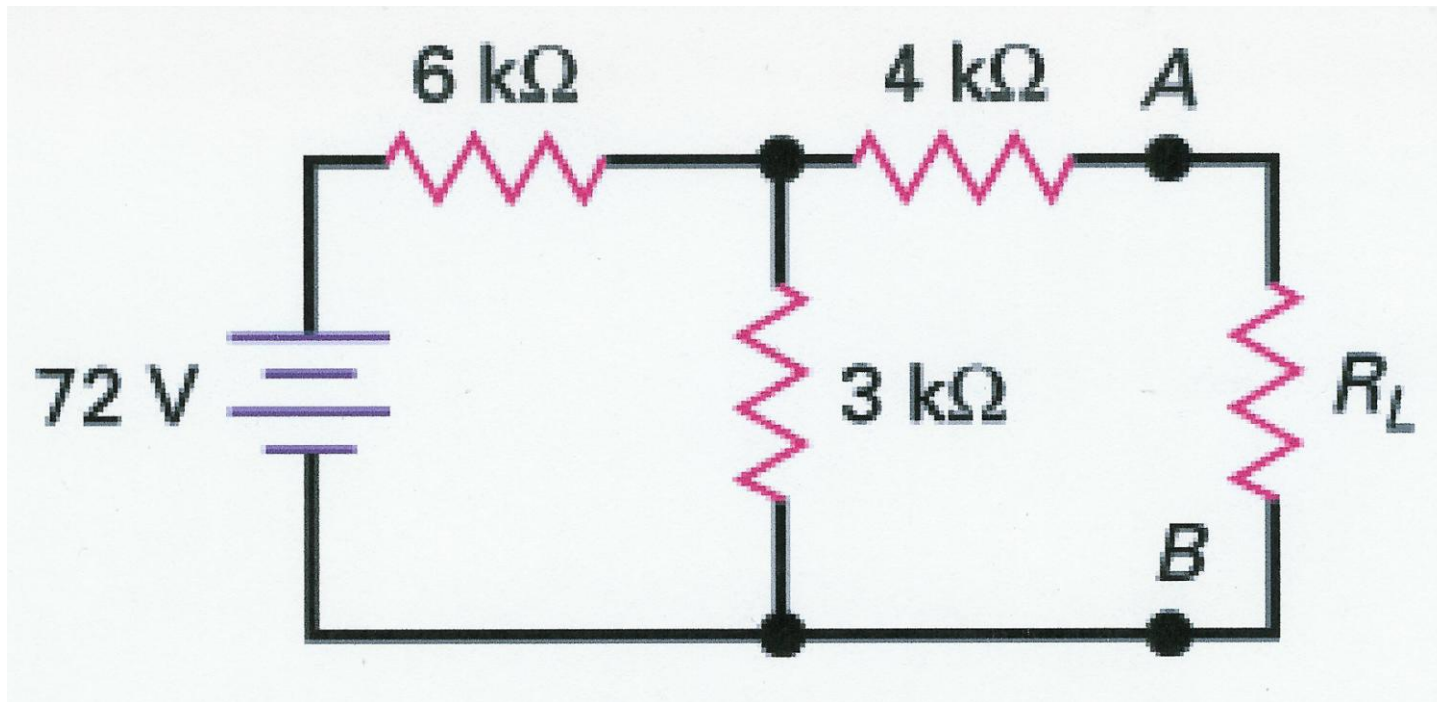


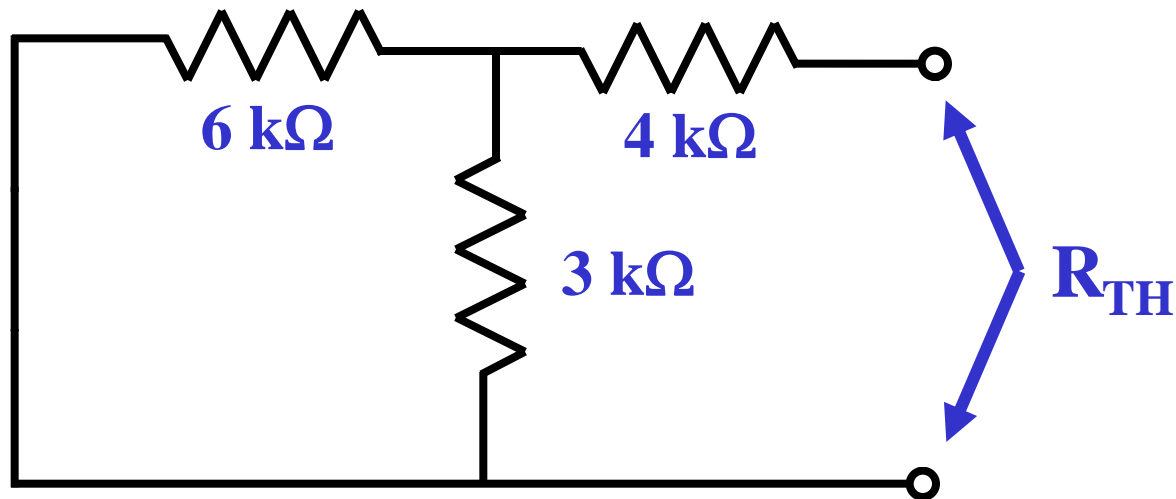Thevenin's theorem can be used to replace any linear circuit with an equivalent voltage source called V_{TH} and an equivalent resistance called R_{TH} .



Calculate or measure
Thevenin's resistance (R_{TH})

Thevenin's Voltage

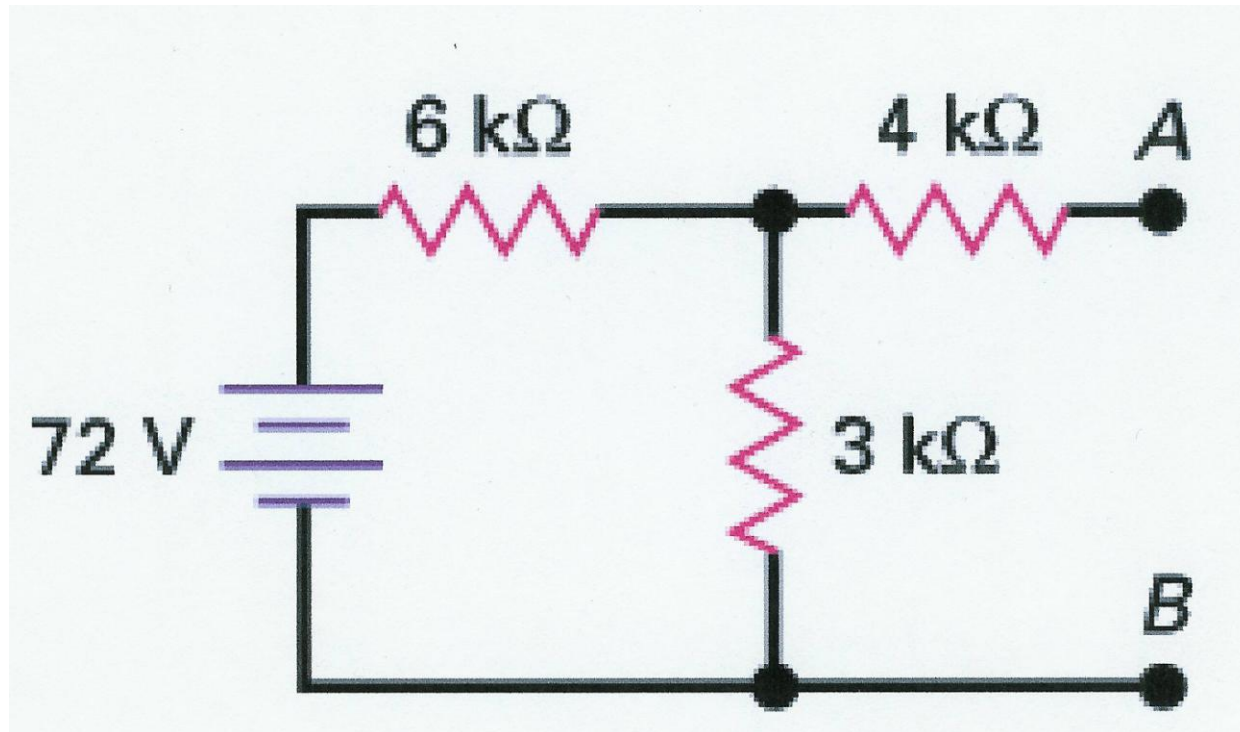

Voltmeter Tip


The input impedance of a voltmeter should be at least **100** times greater than the Thevenin resistance to avoid meter loading.

Meter loading errors cause inaccurate measurements.


DMMs are usually not a problem since they typically have an input impedance of **10 M Ω** .

Thevenin Equivalent Circuit

**Original
circuit**

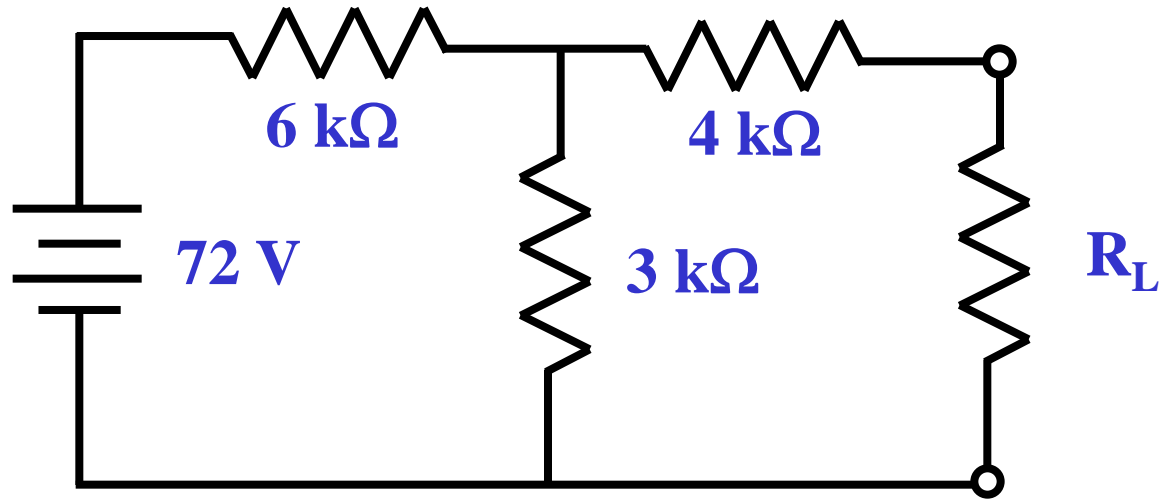


**Thevenin
equivalent circuit**

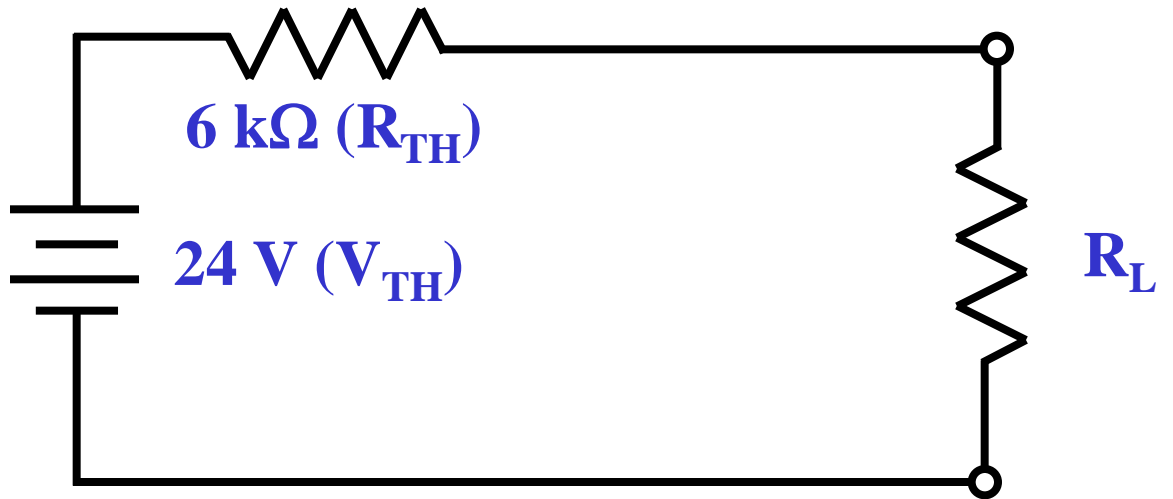

Norton's Theorem



Used to replace any linear circuit with an equivalent current source called I_N and an equivalent resistance called R_N

Norton's Resistance

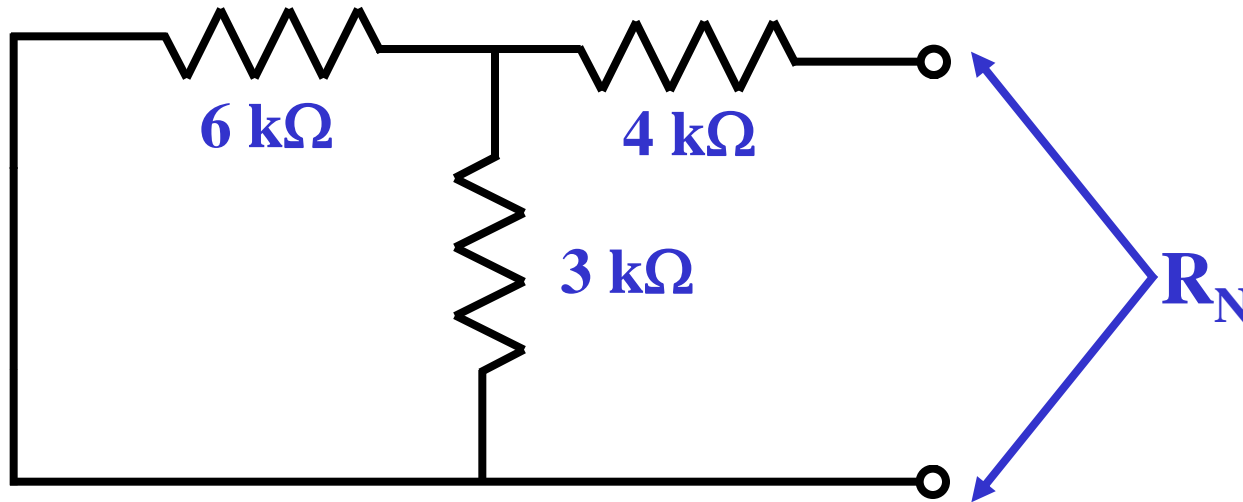

R_N is the same as R_{TH} .


Norton's Current

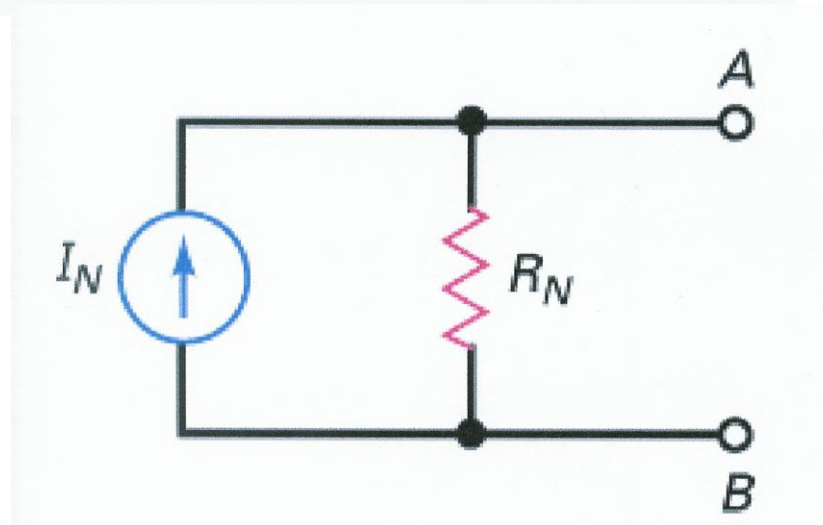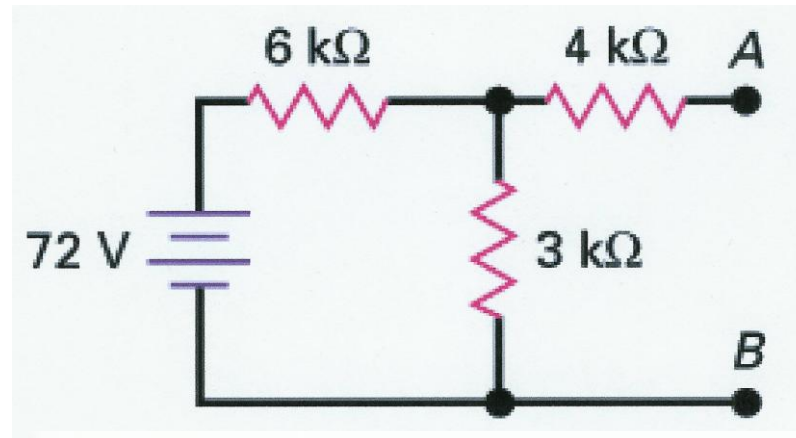


$$I_N = 4 \text{ mA}$$
$$R_N = 6 \text{ K}\Omega$$

Norton Equivalent Circuit


The original circuit

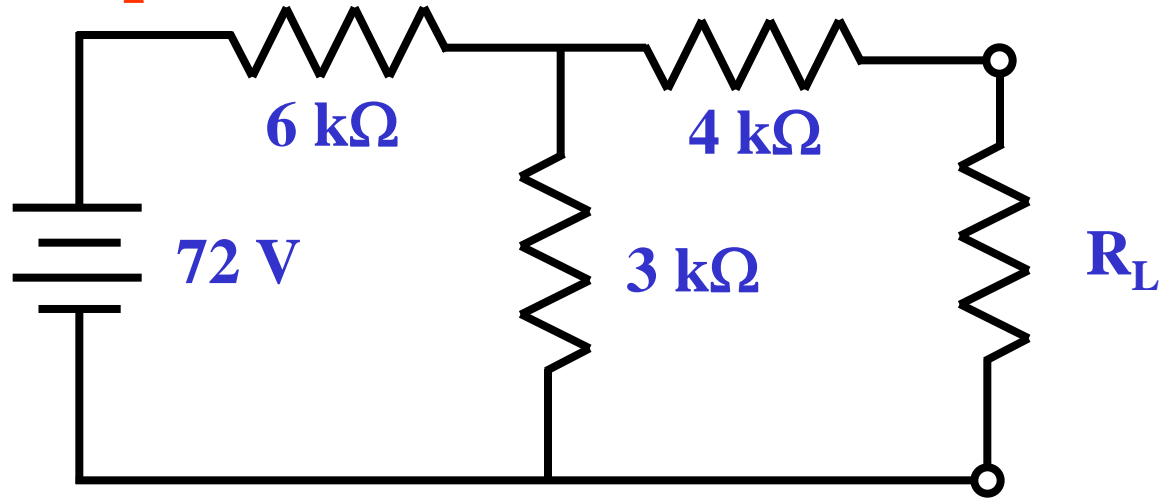

The Norton equivalent circuit

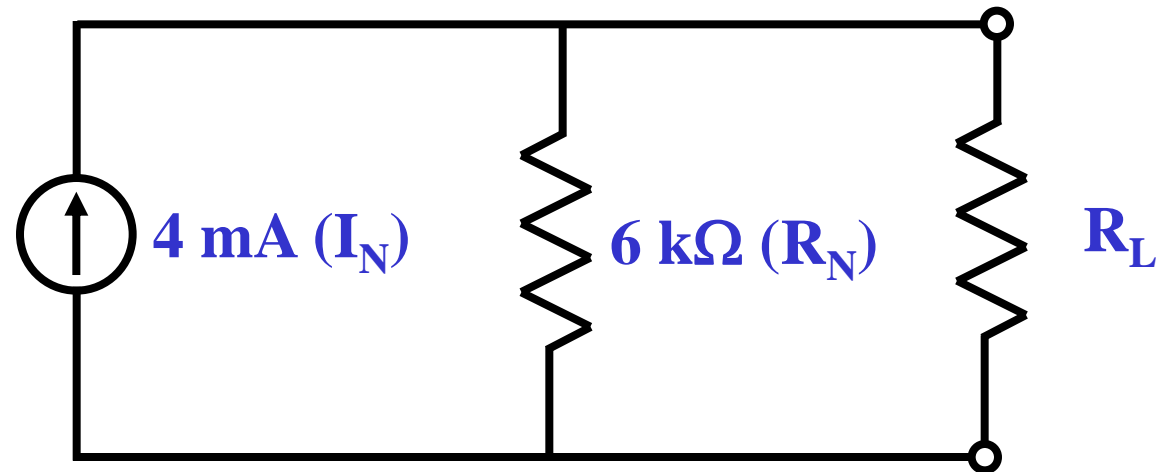

**A Thevenin
equivalent circuit**

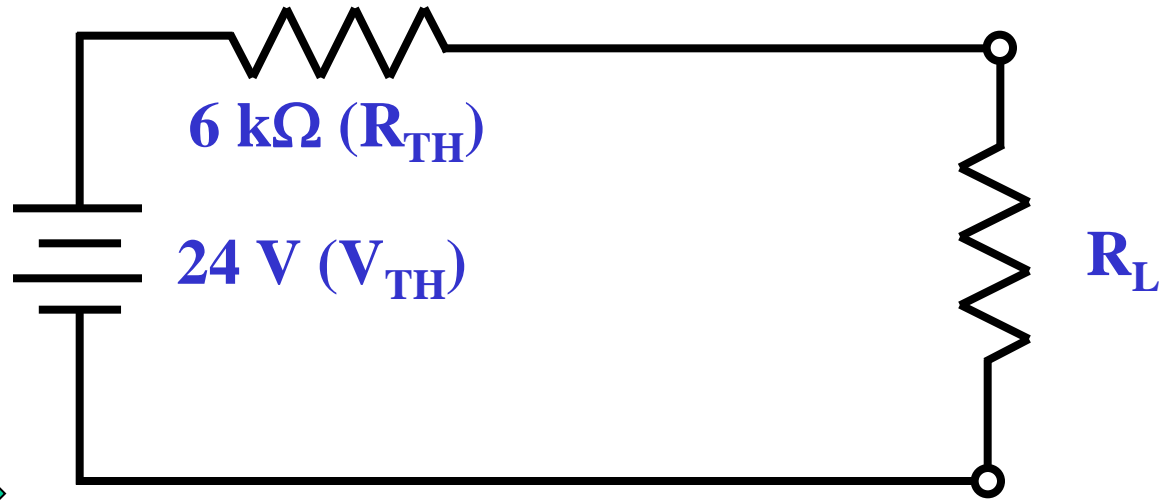


Circuit Conversion

$$R_N = R_{TH}$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$

**The Norton
dual**

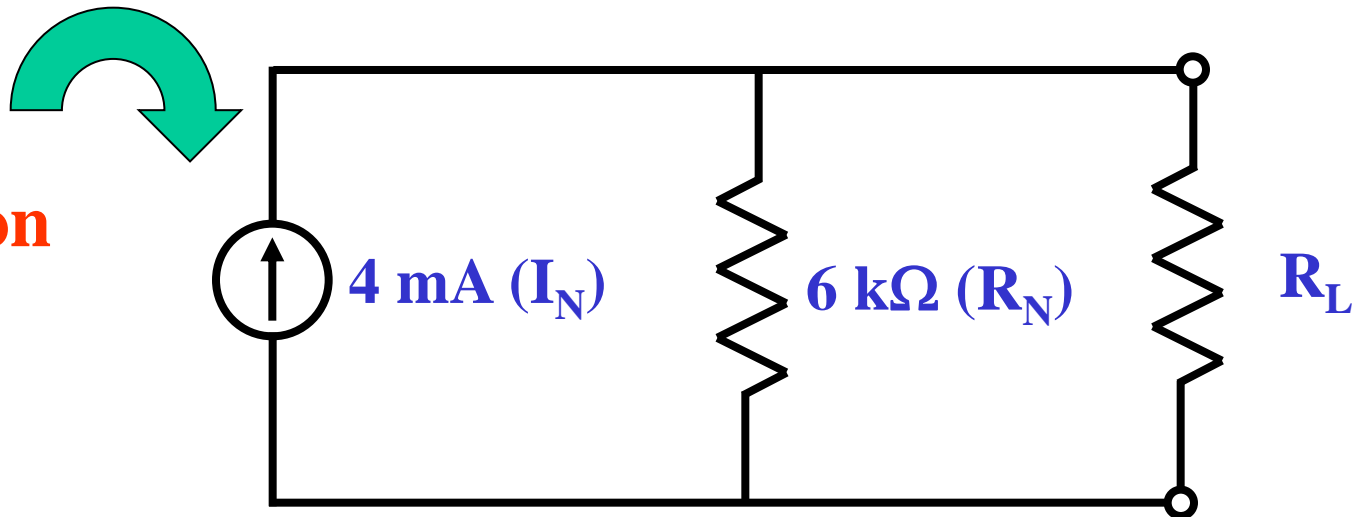

Solder and Connector Problems

- A **solder bridge** between two lines effectively shorts them together.
- A **cold solder joint** is effectively an open circuit.
- An **intermittent trouble** is one that appears and disappears (could be a cold solder joint or a loose connection).

Troubleshooting

- Finding out why a circuit is **not** doing what it is supposed to do
- Common problems are **opens** and **shorts**

An open device


- The current through it is zero.
- The voltage across it is unknown.
- $V = \text{zero} \times \text{infinity}$ {indeterminate}

A shorted device

- The voltage across it is zero.
- The current through it is unknown.
- $I = 0/\text{infinity}$ {indeterminate}

A troubleshooting example:

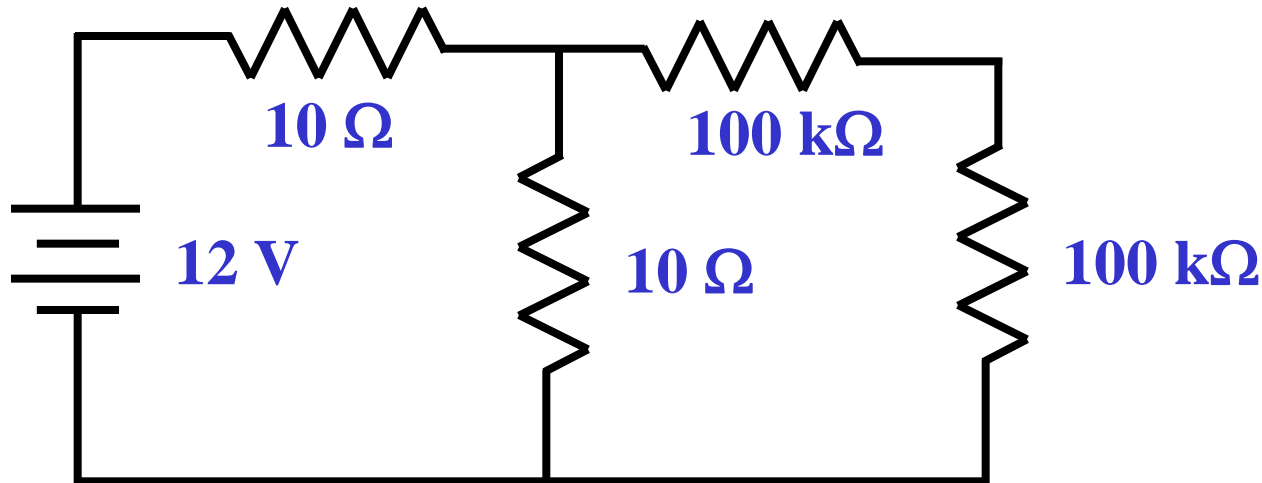
Do the two $10\ \Omega$ resistors form a *stiff* voltage divider?



Why?


A troubleshooting example:

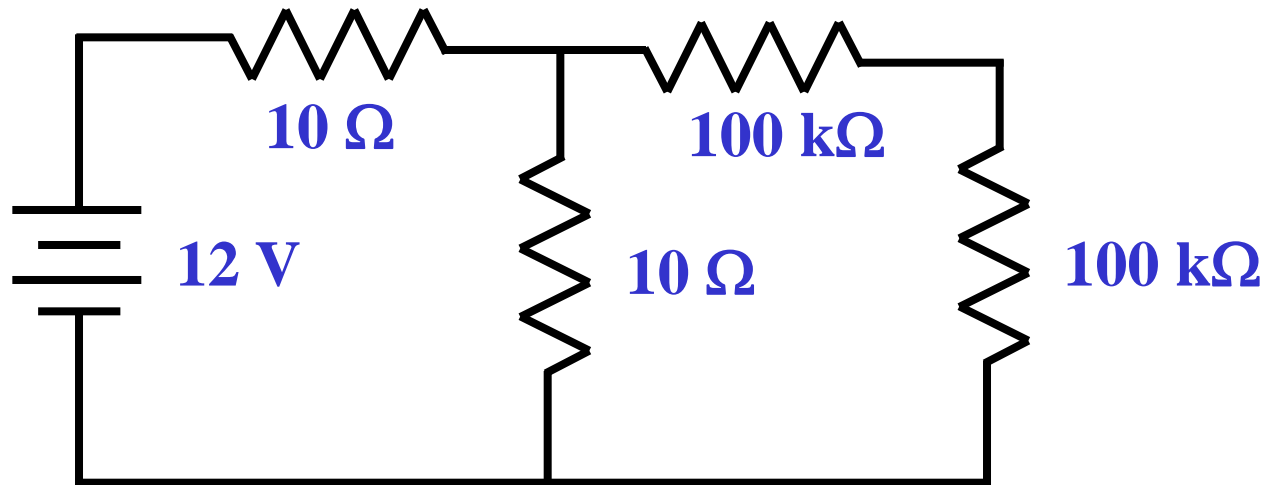What are the expected
voltages in this circuit?



A troubleshooting example:

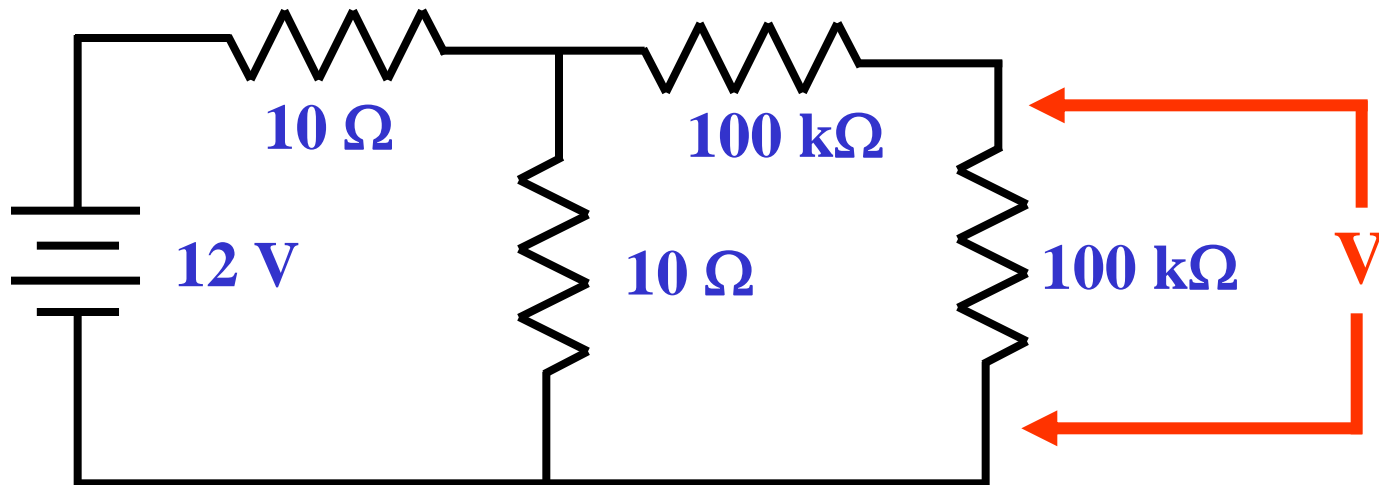What are some causes for
this voltage (V) being too high?



A troubleshooting example:

What are some causes for
this voltage (V) being too low?

