

**MALVINO & BATES**

**Electronic  
PRINCIPLES**

**SEVENTH EDITION**



# Diode Theory



# Topics Covered in Chapter 3

- **Basic ideas**
- **The ideal diode**
- **The second approximation**
- **The third approximation**
- **Troubleshooting**
- **Up-down circuit analysis**


# Topics Covered in Chapter 3 (Continued)

- **Reading a data sheet**
- **How to calculate bulk resistance**
- **DC Resistance of a diode**
- **Load lines**
- **Surface-mount diodes**

# Diode

- A **nonlinear** device
- The **graph** of current vs. voltage is not a straight line
- The diode voltage must exceed the **barrier** voltage to conduct

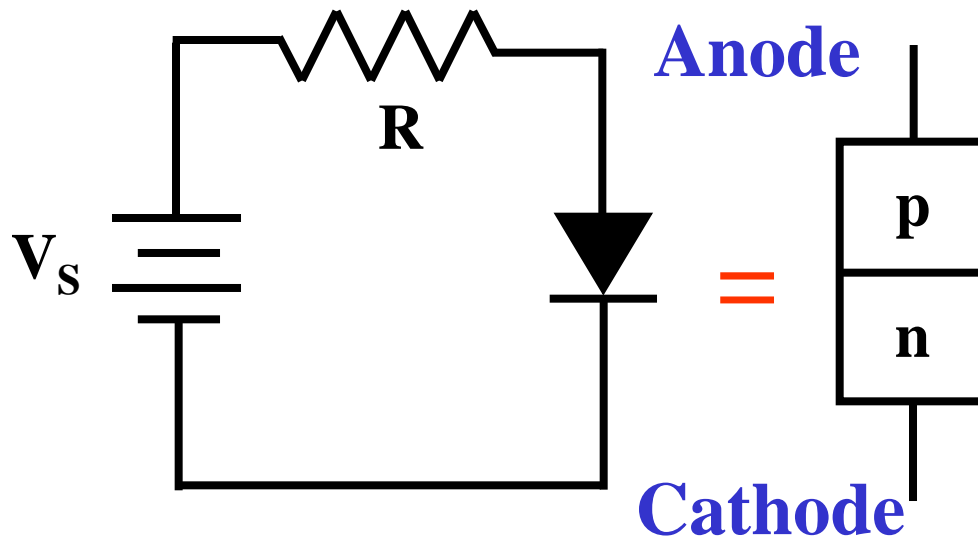
**The diode symbol looks like an arrow that points from the p side to the n side.**



**The arrow points in the direction of conventional current flow. This diode is forward biased by  $V_S$ .**
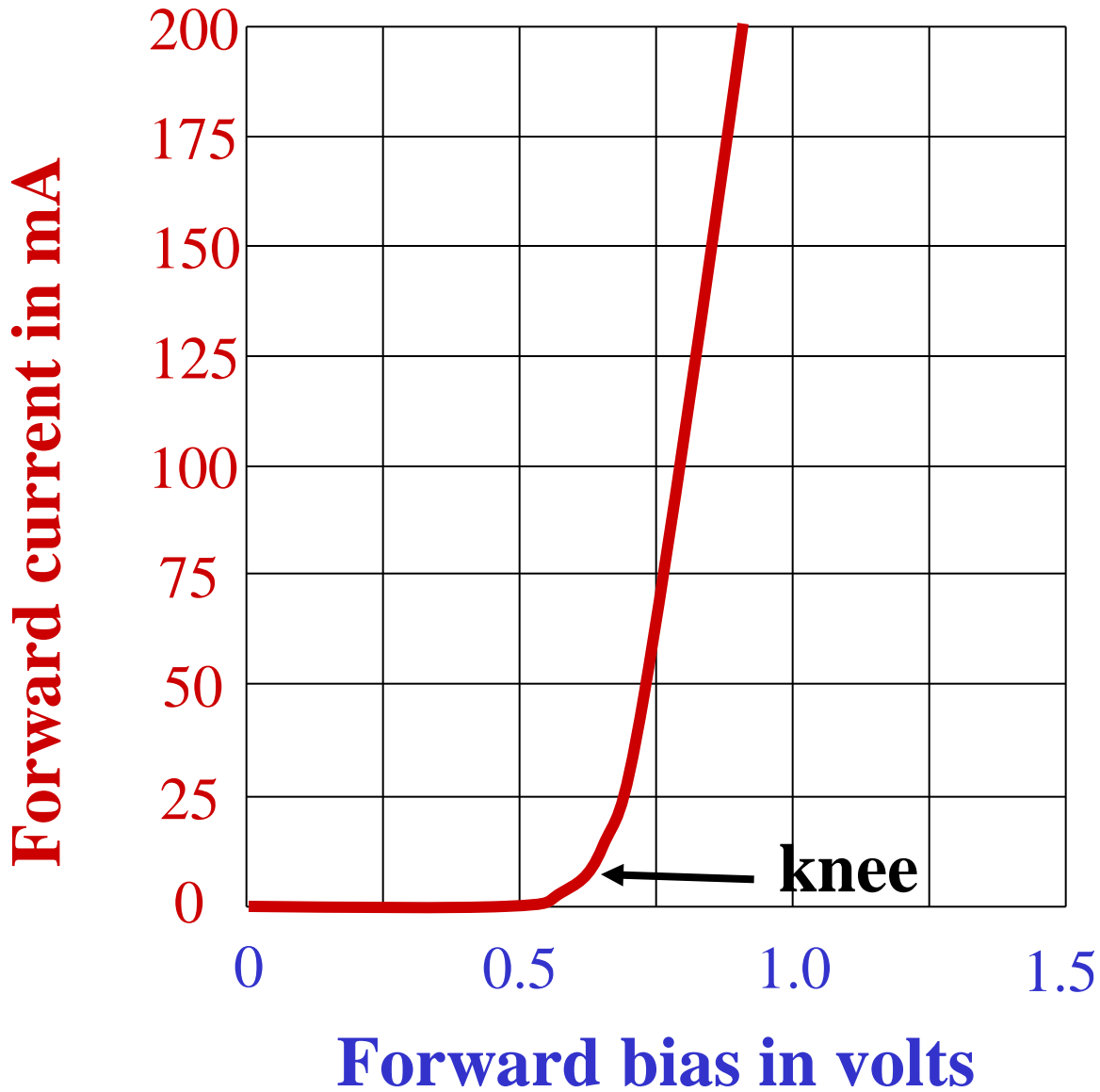
# Linearity

- The volt-ampere characteristic curve for a **resistor** is a straight line (linear).
- A **diode** has a non-linear characteristic curve.
- The barrier potential produces a knee in the diode curve.
- The **knee voltage** is about **0.7** volts for a silicon diode.




# Silicon diode volt-ampere characteristic curve



**breakdown**

Reverse bias in Volts

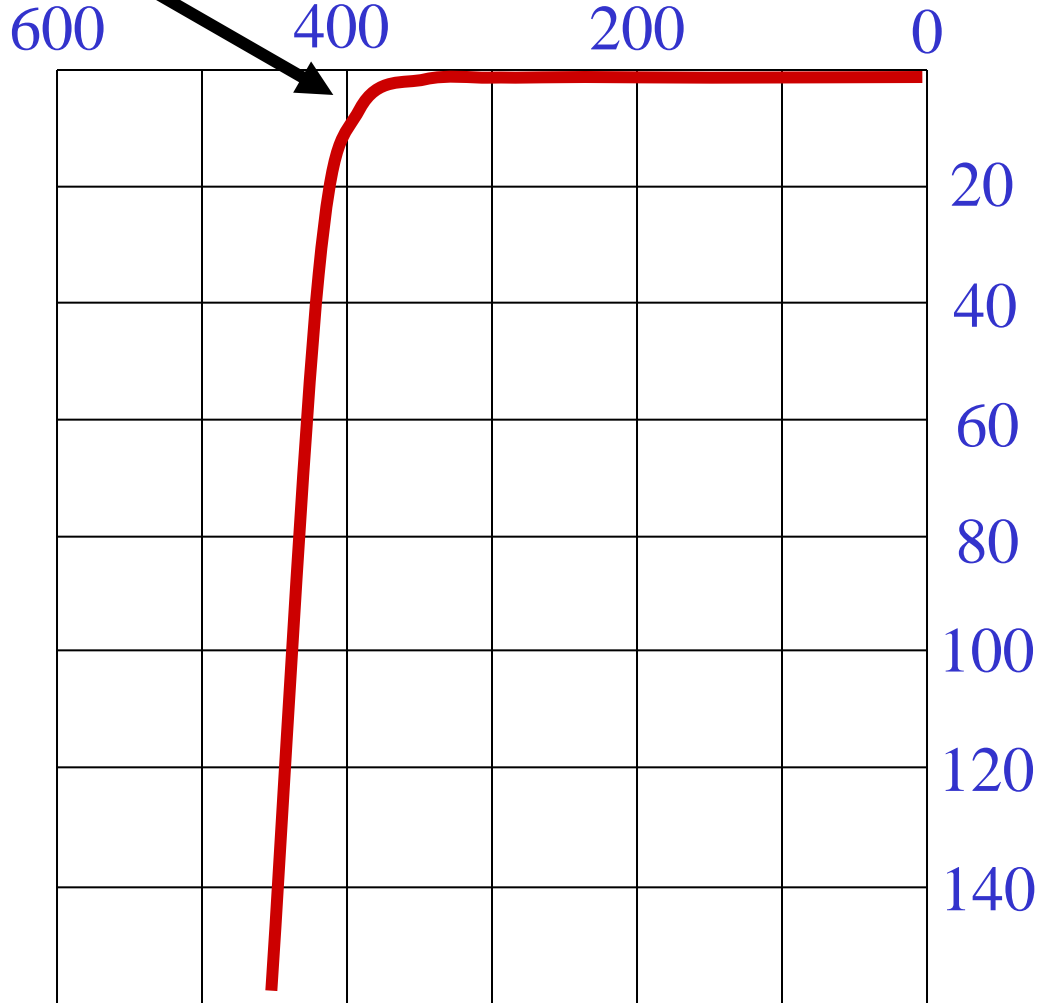

Reverse  
current  
in mA

## Silicon diode reverse bias characteristic curve

# Bulk resistance

- The ohmic resistance of the p and n material is called the **bulk** resistance.
- The bulk resistance is often less than **1  $\Omega$** .
- With forward bias, diode current increases rapidly beyond the knee voltage.
- **Small** increases in voltage cause **large** increases in current.


# Diode ratings

- Specified on manufacturers' **data** sheets
- The **maximum** reverse bias rating must not be exceeded.
- The **maximum** forward current rating must not be exceeded.
- The **power** rating of a diode is determined by its maximum current rating and the forward voltage drop at that current flow.

# Diode first approximation

- This represents the diode as being **ideal**.
- The first approximation ignores leakage current, barrier potential and bulk resistance.
- When an ideal diode is **forward** biased, the model is a closed switch.
- When an ideal diode is **reverse** biased, the model is an open switch.


# First (ideal) approximation

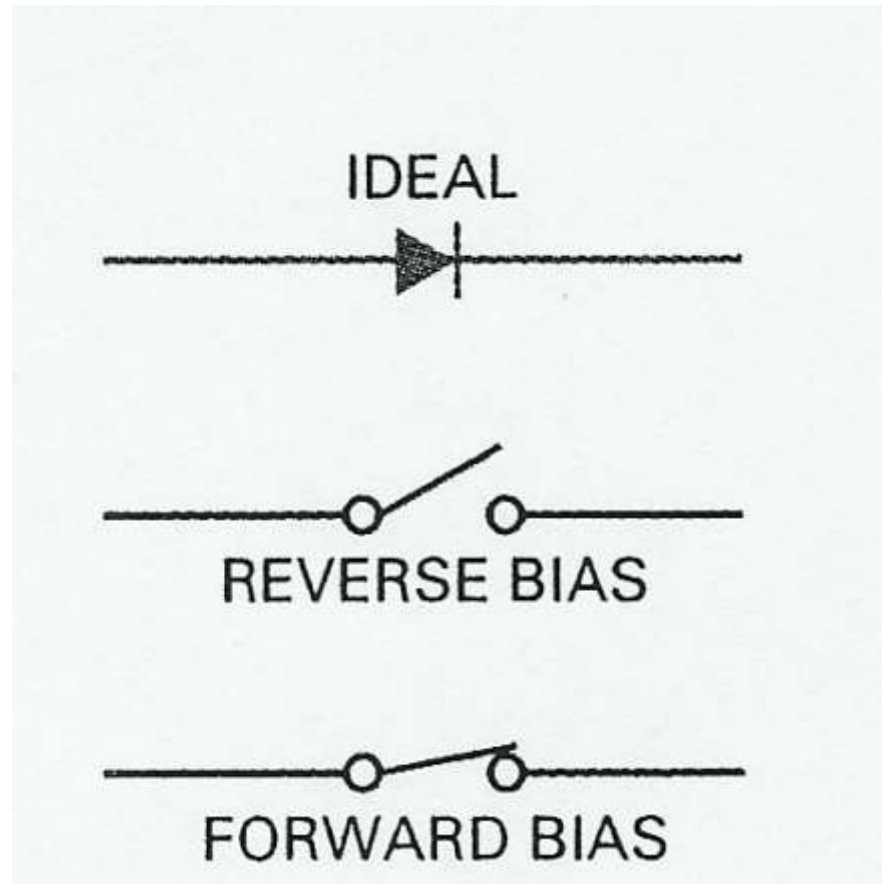

# Diode second approximation

- This model assumes that no diode current flows until the **forward** bias across the diode reaches **0.7** volts.
- This model ignores the exact shape of the knee.
- This model ignores the diode's bulk resistance.

# Second approximation

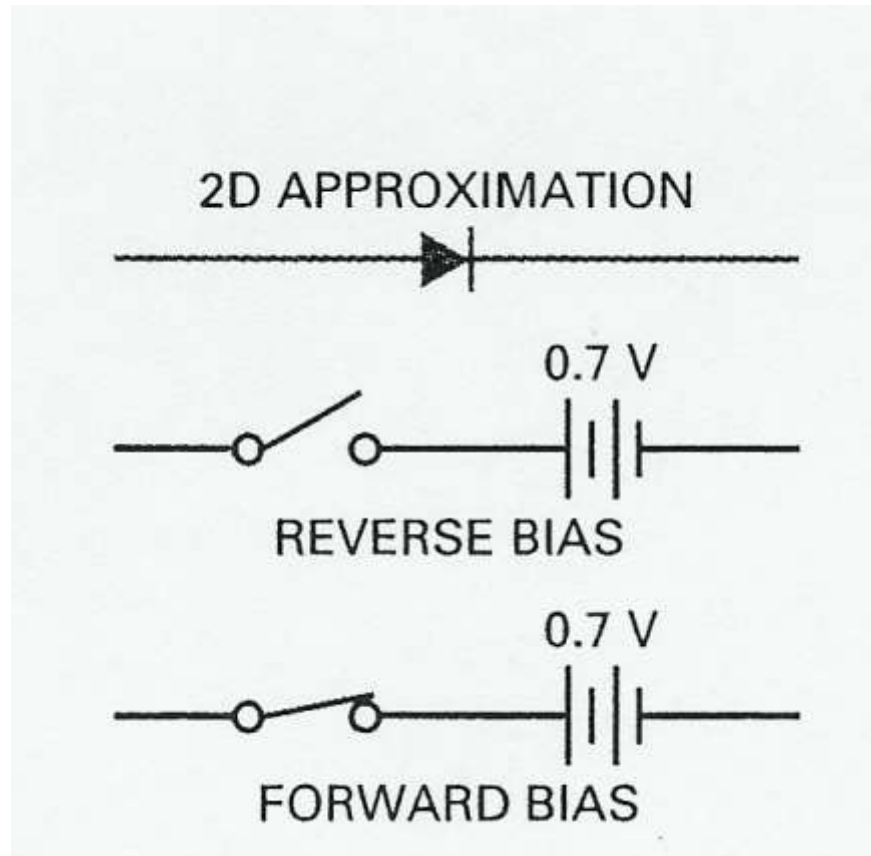



# Diode third approximation

- This model assumes that no diode current flows until the forward bias across the diode reaches **0.7** volts.
- This model ignores the exact shape of the knee.
- This model does account for the diode's **bulk** resistance.


However, bulk resistance that is less than  $1 \Omega$  can be ignored.



# Third approximation

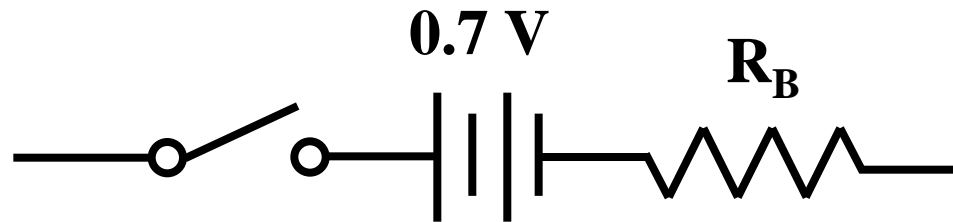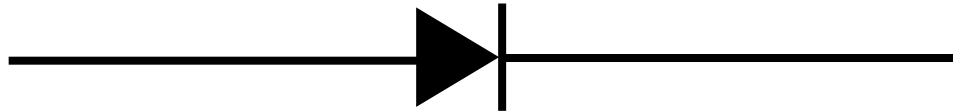

Reverse bias

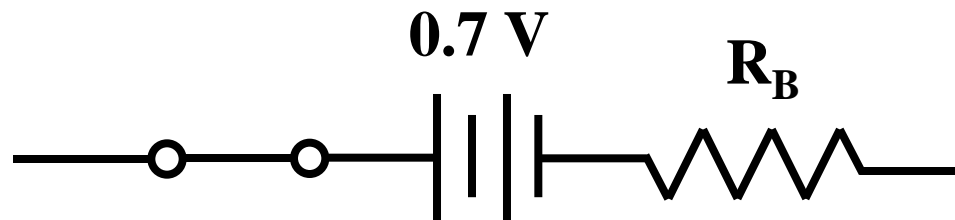

Forward bias

# Appropriate approximation

- The **first** approximation is adequate for most troubleshooting situations.
- The **second** approximation is often used if more accurate values for load current and voltage are required.
- The **third** approximation improves accuracy when the diode's bulk resistance is more than 1/100 of the Thevenin resistance facing the diode.

# Silicon diode testing using an ohmmeter

- **Low** resistance in both directions: the diode is shorted.
- **High** resistance in both directions: the diode is open.
- **Relatively low** resistance in the reverse direction: the diode is leaky.
- If the **ratio** of reverse to forward resistance is **> 1000**: the diode is good.

# Silicon diode testing using a DMM

- Set DMM to diode test function
- A connected **forward**-biased diode will display the pn-junction's forward voltage (~**0.5V** to **0.7V**)
- When the diode is **reversed**-biased by the test leads, meter displays over-range indication such as “**OL**” or “**1**”


# Silicon diode testing using a DMM (continued)

- A shorted diode displays a voltage less than **0.5V** in both directions
- An open diode would be indicated by an **over-range** display in both directions
- A leaky diode would display a voltage less than **2.0V** in both directions


# Data sheets

- Useful to circuit designers
- Useful to repair technicians
- Typical entries include:
  - ✓ Breakdown voltage
  - ✓ Maximum forward current
  - ✓ Forward voltage drop

# Bulk resistance calculation

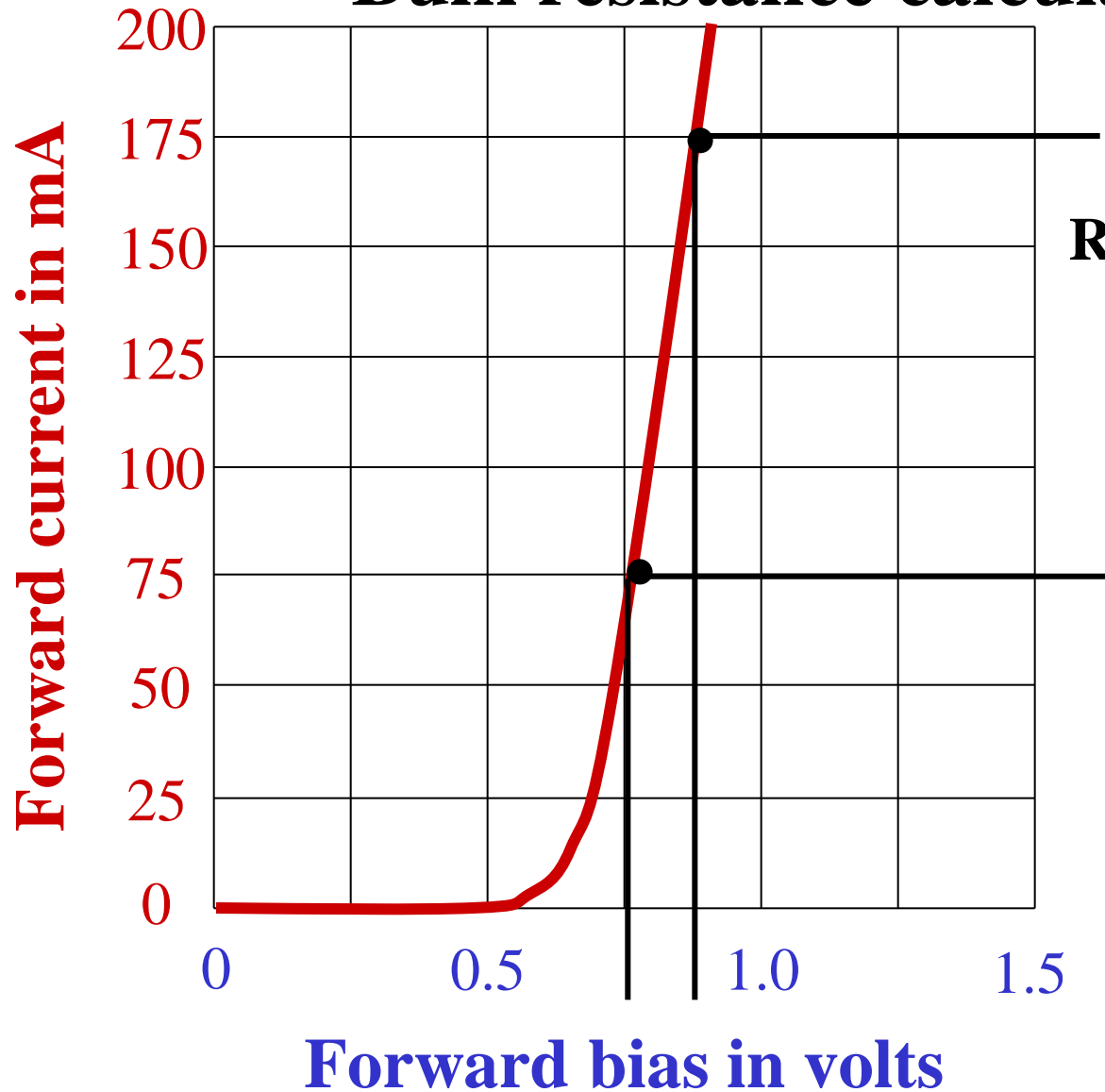
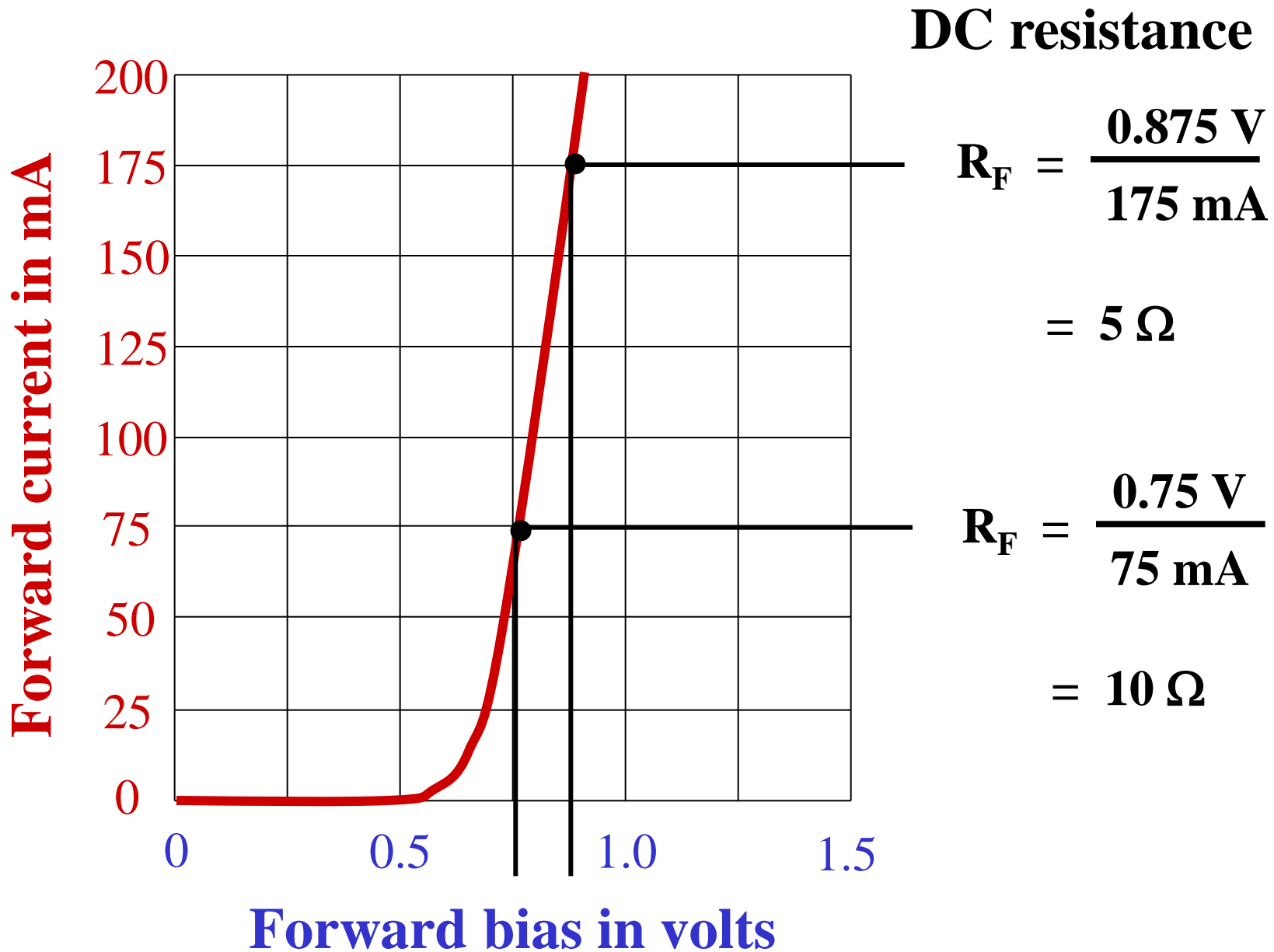
$$R_B = \frac{0.875 \text{ V} - 0.75 \text{ V}}{175 \text{ mA} - 75 \text{ mA}}$$
$$= 1.25 \Omega$$




**The forward resistance decreases as current increases.**



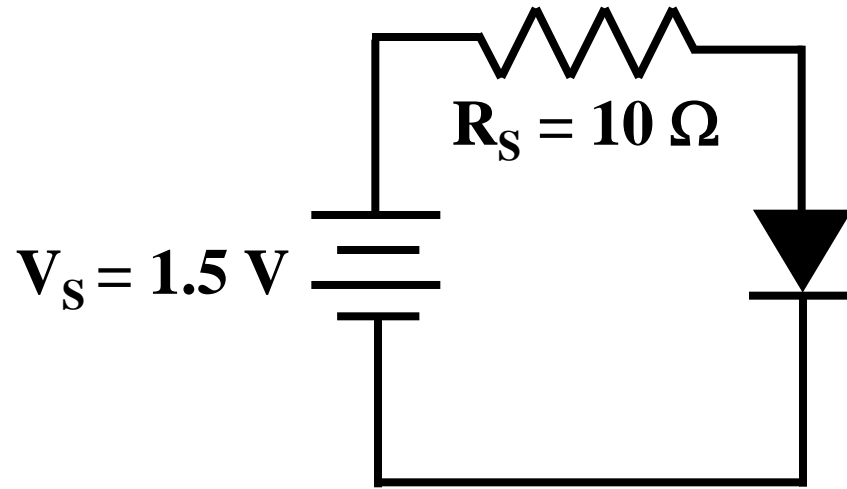
# Silicon diode resistance values

- The **reverse** resistance is very high: typically tens or hundreds of megohms.
- The **forward** resistance is not the same as the bulk resistance.
- The **forward** resistance is always greater than the bulk resistance.
- The **forward** resistance is equal to the bulk resistance plus the effect of the barrier potential.



**A circuit like this can be solved in several ways:**


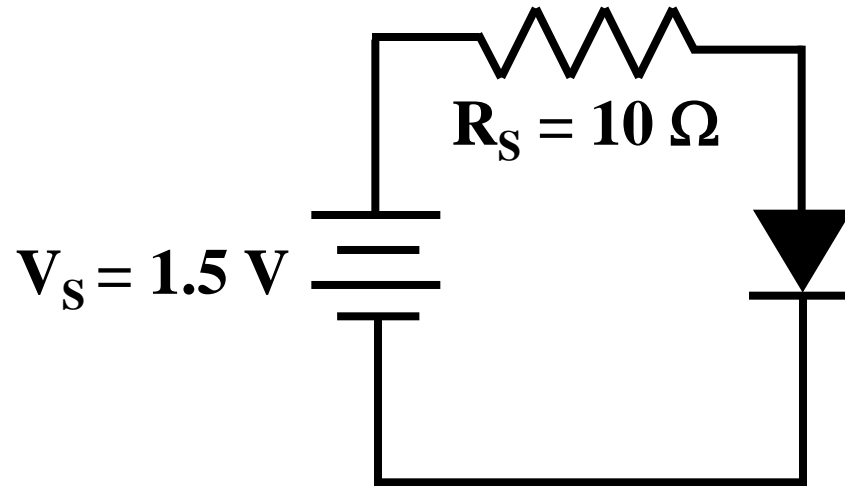
- 1. Use the first (ideal) approximation.**
- 2. Use the second approximation.**
- 3. Use the third approximation.**
- 4. Use a circuit simulator.**
- 5. Use the diode's characteristic curve.**



Using the characteristic curve is a graphical solution:

1. Find the **saturation** current using Ohm's law.
2. The **cutoff** voltage is equal to the supply voltage.
3. Locate these two points on the diode's curve.
4. Connect them with a load line.
5. The intersection is the graphical solution.

# Graphical Solution

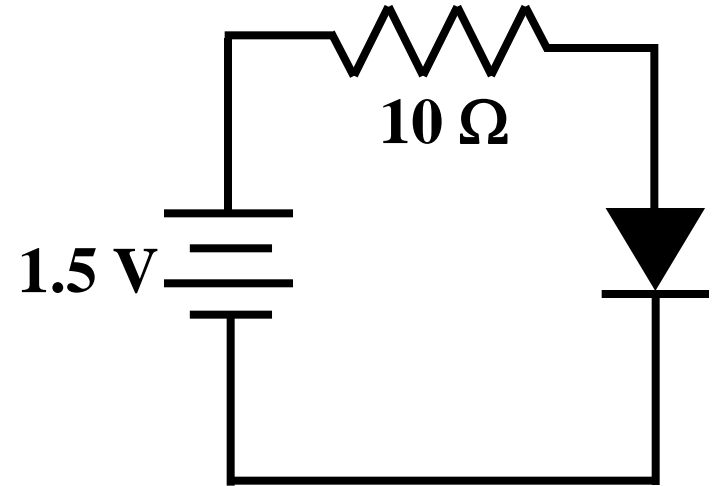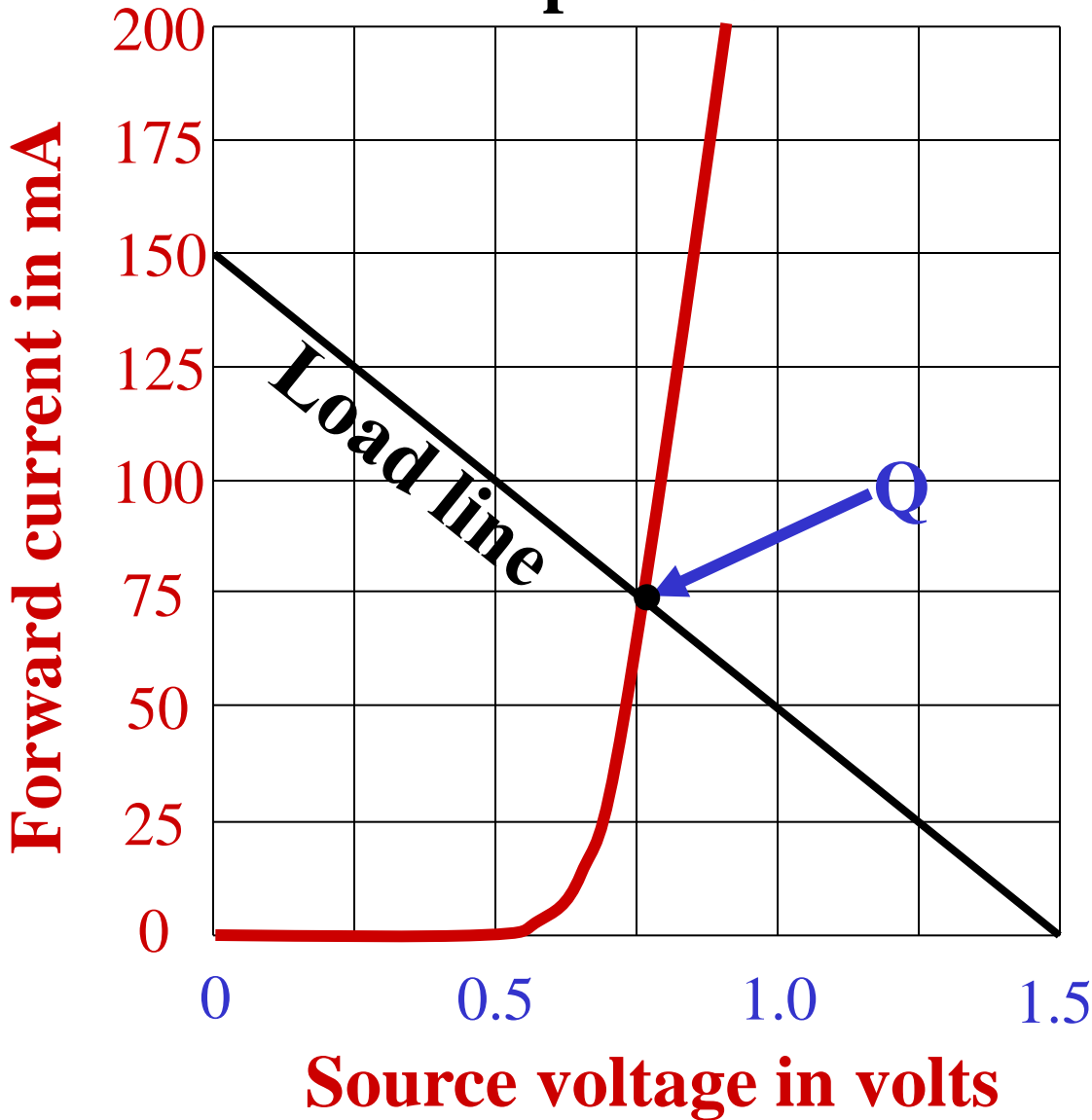

$$I_{\text{SAT}} = \frac{1.5 \text{ V}}{10 \Omega} = 150 \text{ mA}$$

$$V_{\text{CUTOFF}} = 1.5 \text{ V}$$

**Q is the operating point**