

MALVINO & BATES

**Electronic
PRINCIPLES**

SEVENTH EDITION



Diode Circuits



Topics Covered in Chapter 4

- **Half-wave rectifier**
- **Transformer**
- **Full-wave rectifier**
- **Bridge rectifier**
- **Choke-input filter**
- **Capacitor-input filter**



Topics Covered in Chapter 4 (Continued)

- **Peak inverse voltage and surge current**
- **Other power supply topics**
- **Troubleshooting**
- **Clippers and limiters**
- **Clampers**
- **Voltage multipliers**


Half-wave rectifier

- Has a diode in **series** with the load resistor
- Load voltage is a **half-wave** output

The half-wave rectifier

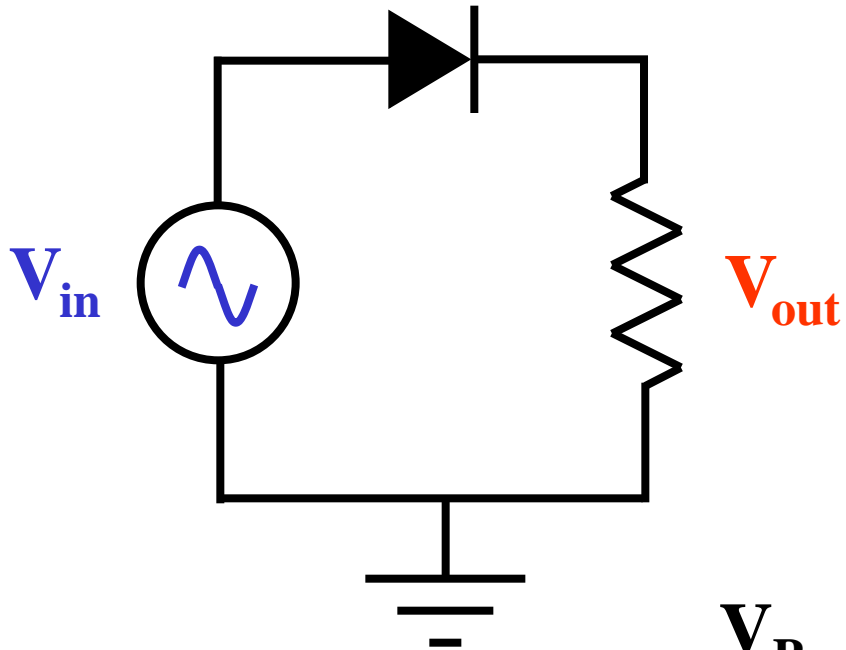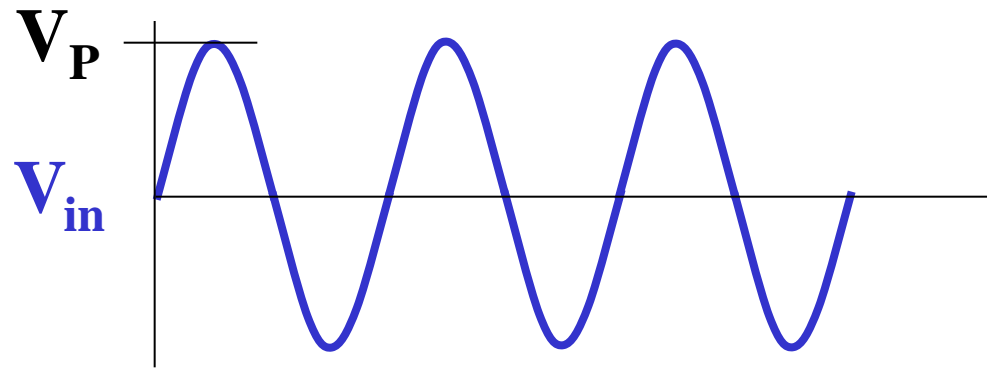

Ideal: $V_{P(in)} = V_{P(out)}$

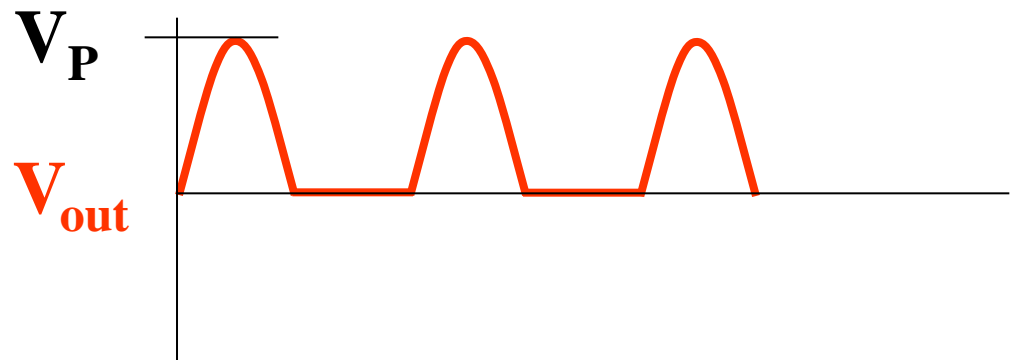

Half-wave rectifier signals

- The dc value of the output is the average value.
- $V_{dc} = V_P/\pi$
- $f_{out} = f_{in}$
- **Second approximation:**
$$V_{P(out)} = V_{P(in)} - 0.7 V$$

Input transformer

- **Step down**
- **Voltage steps down**
- **Current steps up**
- **Secondary voltage **equals** the primary voltage divided by the turns ratio**




Transformer review

- When the turns ratio (N_1/N_2) is greater than 1, the **primary** voltage is stepped down.
- When the turns ratio is less than 1, the **primary** voltage is stepped up.
- Dotted ends have the **same** instantaneous phase.
- **Full-wave** rectifiers require a winding with a center tap.

Full-wave rectifier

- Has a **center-tapped** transformer with two diodes and a load resistor
- Load voltage is a **full-wave** signal whose peak is half of the secondary voltage

The full-wave rectifier

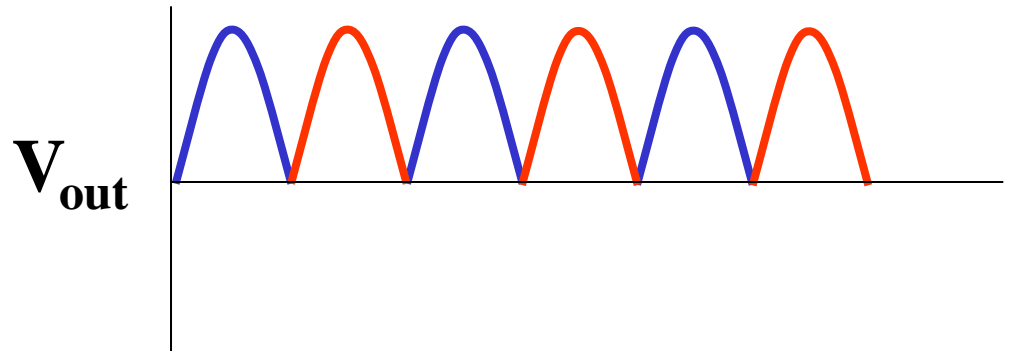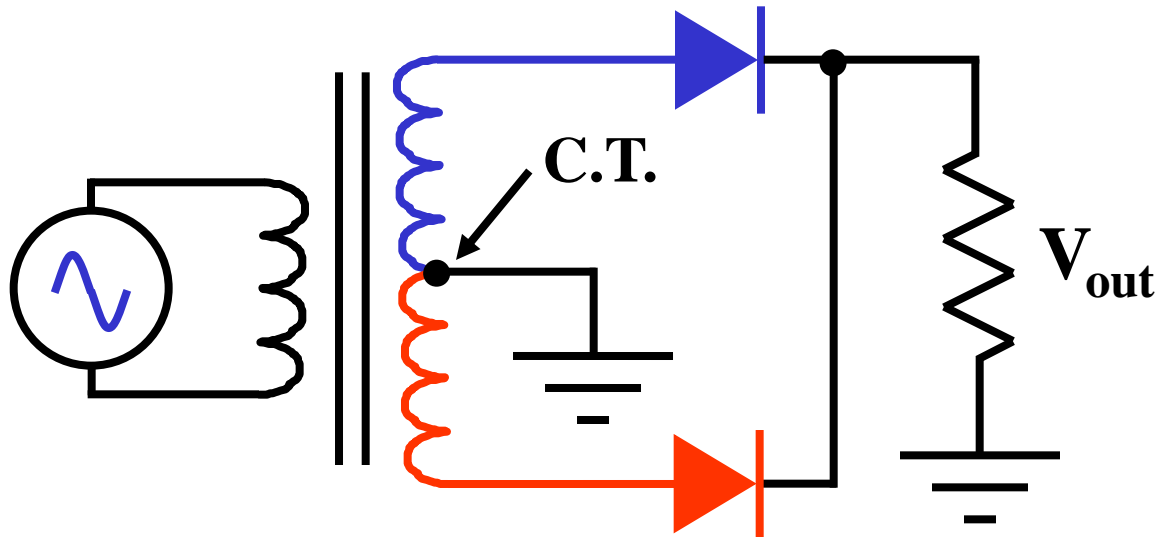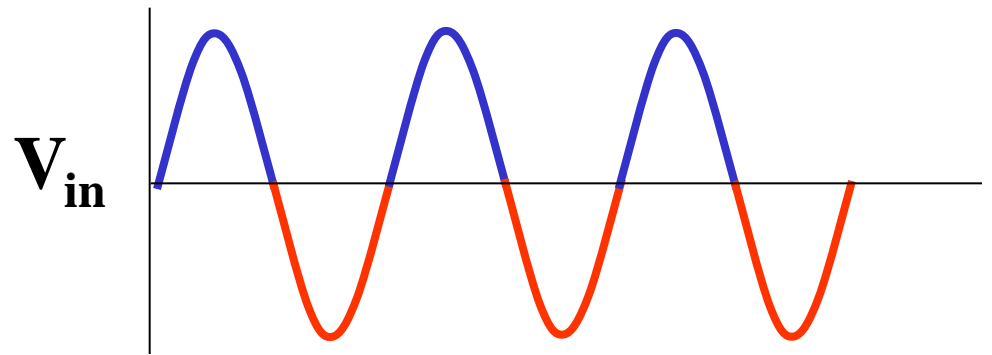

Full-wave rectifier signals




- The **dc** value of the output is the average value.
- $V_{dc} = 2V_P/\pi$
- $f_{out} = 2f_{in}$
- The **input** to each diode is half the secondary voltage.
- **Second approximation:**

$$V_{P(out)} = V_{P(in)} - 0.7 \text{ V}$$

Bridge rectifier

- Has four diodes
- **Load** voltage is a full-wave signal with peak value equal to the secondary voltage

The bridge rectifier

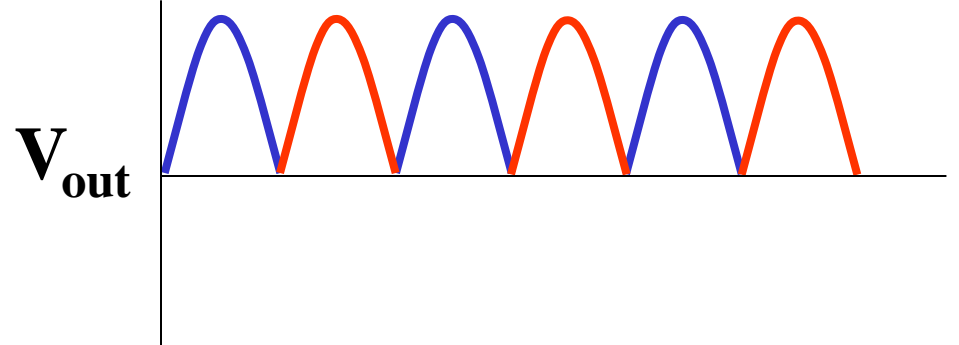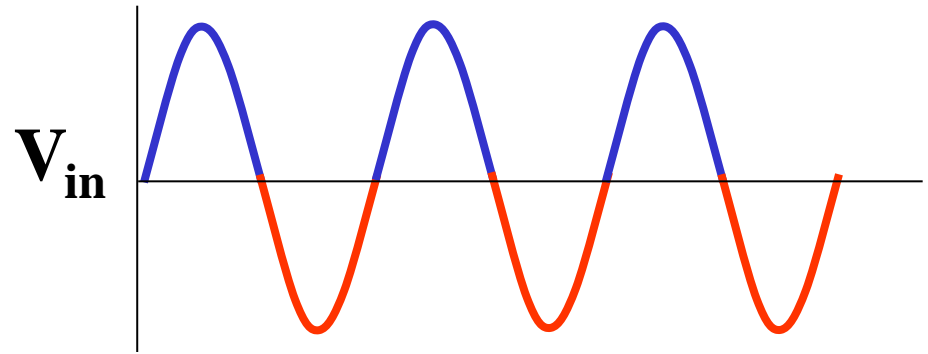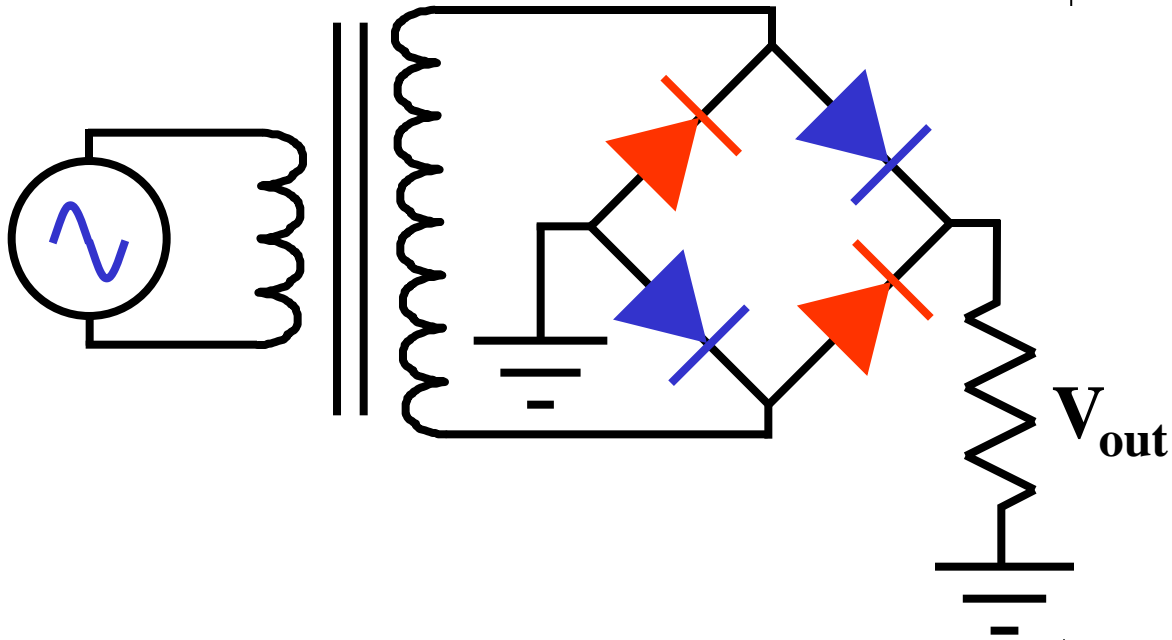

Bridge rectifier signals

- The **dc** value of the output is the **average value**.

- $V_{dc} = 2V_P/\pi$

- $f_{out} = 2f_{in}$


- **Second approximation:**

$$V_{P(out)} = V_{P(in)} - 1.4 \text{ V}$$

Choke-input filter

- LC voltage divider
- $X_L \gg X_C$
- The **average** value of a rectified signal passes to the load resistor

The choke-input filter

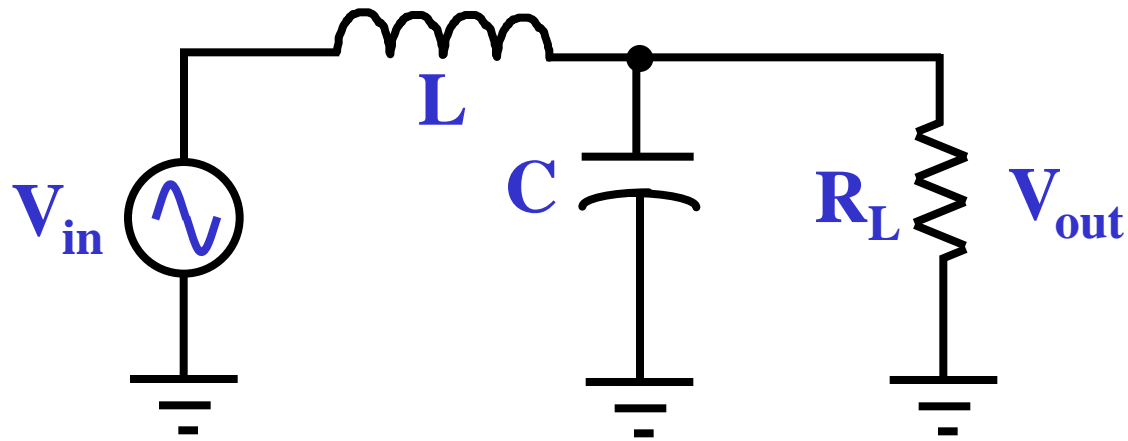



When $X_L \gg X_C$:

$$V_{out} \approx \frac{X_C}{X_L} V_{in}$$

Capacitor-input filter

- Most widely used
- The **peak** value of the rectified signal passes to the load resistor
- With a large capacitor, **ripple** is small

The capacitor-input filter

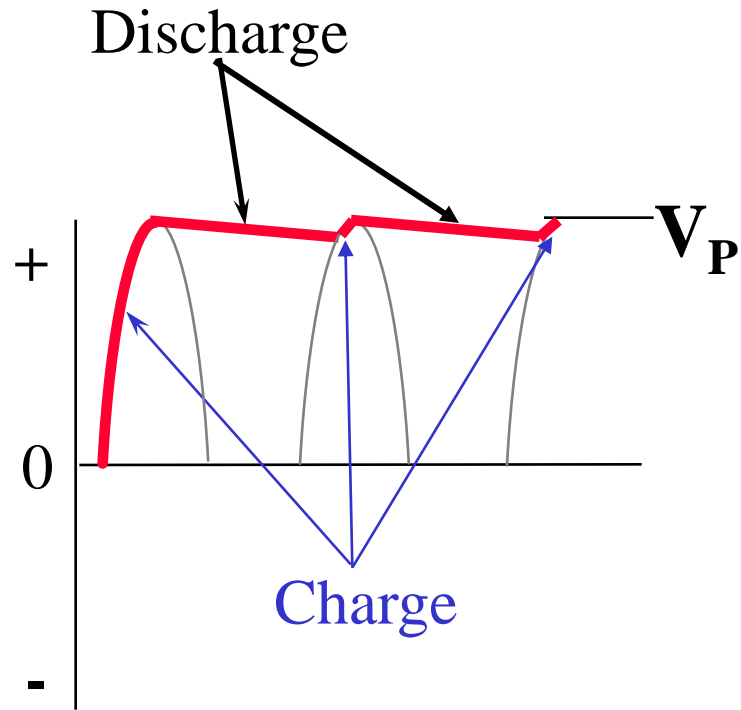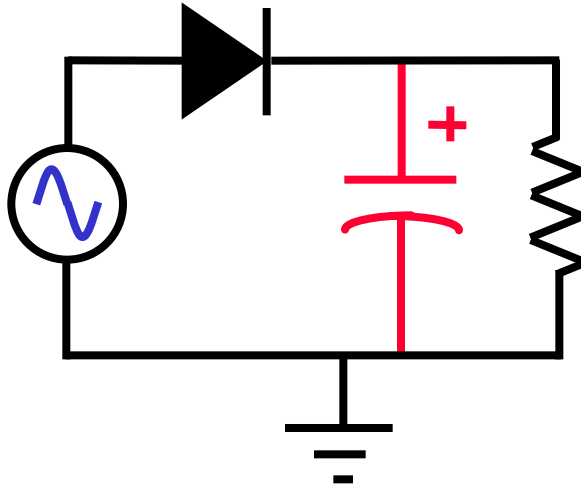

$$V_R = \frac{I}{fC}$$

Where V_R is the peak-to-peak ripple voltage


Effects on voltage and current

- **Ac line** regulation can have an effect
- **Bulk** resistance of rectifiers causes a voltage drop
- **Resistance** of transformer windings causes a voltage drop
- **Ac ripple** increases and **average dc** decreases when load current increases

Power supply block diagram

Summary Table 4-3

Power Supply Block Diagram

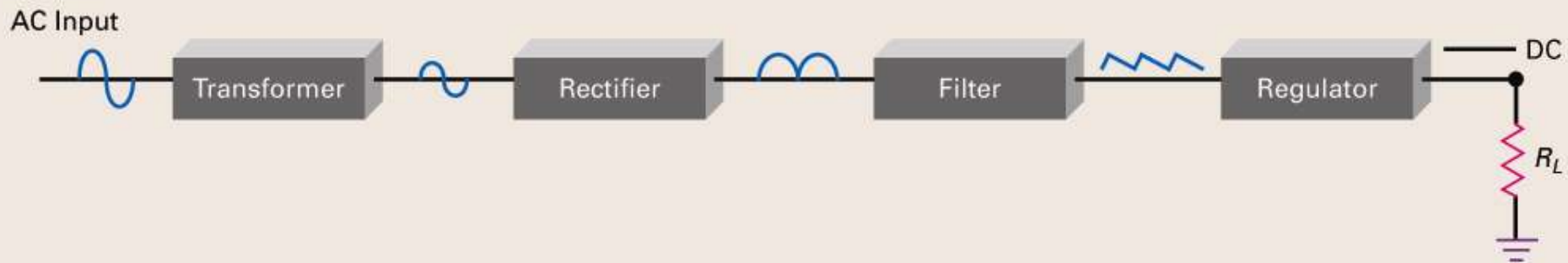

| | | | | |
|---------|--|--|------------------------------|---|
| Purpose | Provides proper secondary ac voltage and ac ground isolation | Changes ac input to pulsating dc | Smooths out dc pulses | Provides a constant output voltage under varying loads and ac input voltage |
| Types | Step-up, step-down, isolation (1:1) | Half-wave, full-wave, full-wave bridge | Choke-input, capacitor input | Discrete components, integrated circuit (IC) |

Peak inverse voltage

- **Maximum** voltage across the nonconducting diode of a rectifier circuit
- Voltage must be less than diode **breakdown** voltage

Diode ratings

- **Half-wave** rectifier with capacitor-input filter: $PIV = 2V_P$ $I_{diode} = I_{dc}$
- **Full-wave** rectifier with capacitor-input filter: $PIV = V_P$ $I_{diode} = 0.5I_{dc}$
- **Bridge** rectifier with capacitor-input filter: $PIV = V_P$ $I_{diode} = 0.5I_{dc}$


Typical bridge supply problems

- **No output** - - blown fuse, two or more diodes open, load shorted
- **Low output/extra ripple** - - bad filter, open diode, shorted winding, overload
- **Full-wave signal at output** - - open filter capacitor
- **Half-wave ripple frequency** - - open diode


Power supply topics

- **Real** transformers usually specify secondary voltage at a rated load current
- **Slow-blow** fuses are often used to protect against surge current
- **Average** diode current in a half-wave rectifier equals the dc load current
- In a **full-wave or bridge**, the average current in any diode is half the dc load current


Positive clipper

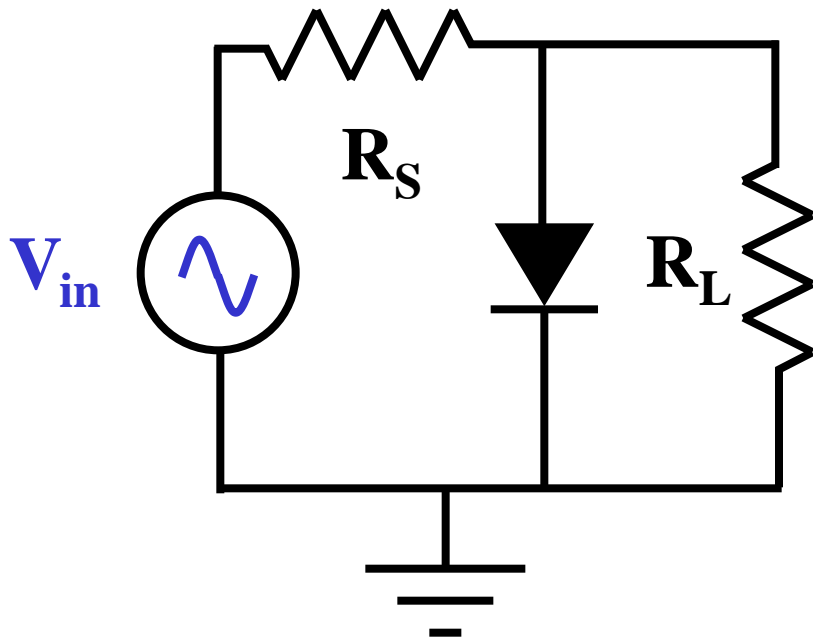


V_{out}

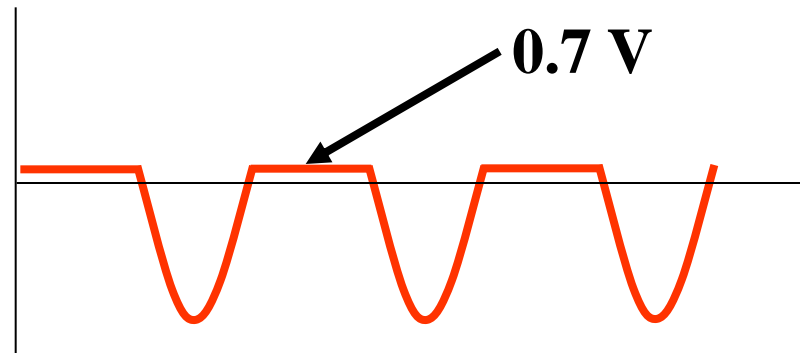

Negative clipper

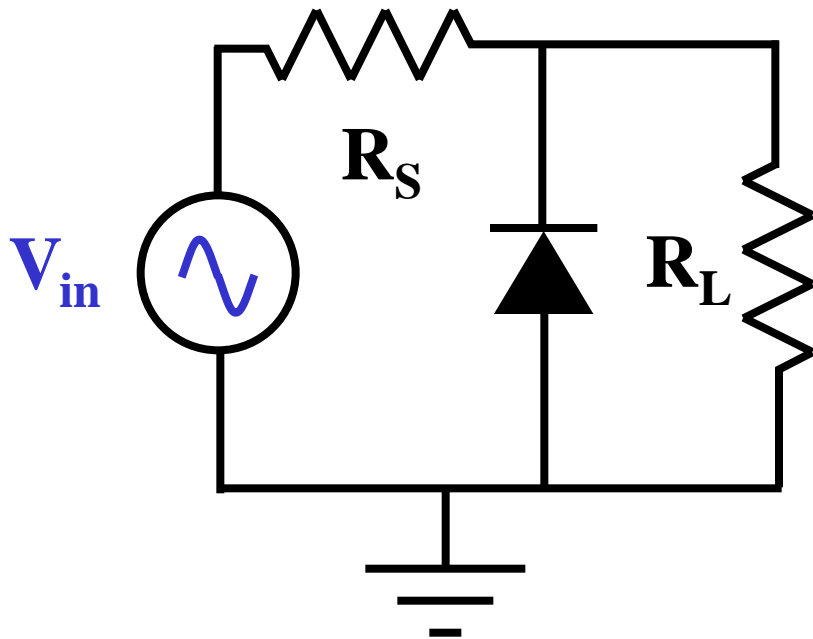

V_{out}

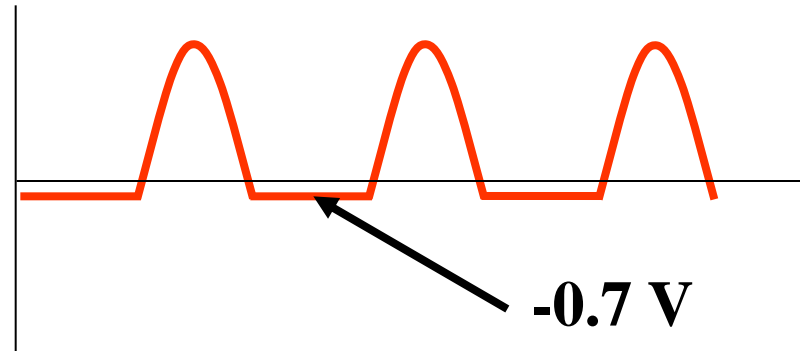



Clippers and limiters

- A **clipper** shapes the signal by clipping off positive or negative parts of the signal
- The **limiter** or **diode clamp** protects sensitive circuits from too much input

Clamper


- Shifts a signal positively or negatively by adding a **dc** voltage to the signal
- Peak-to-peak detector produces a load voltage equal to the peak-to-peak value

Positive clamper

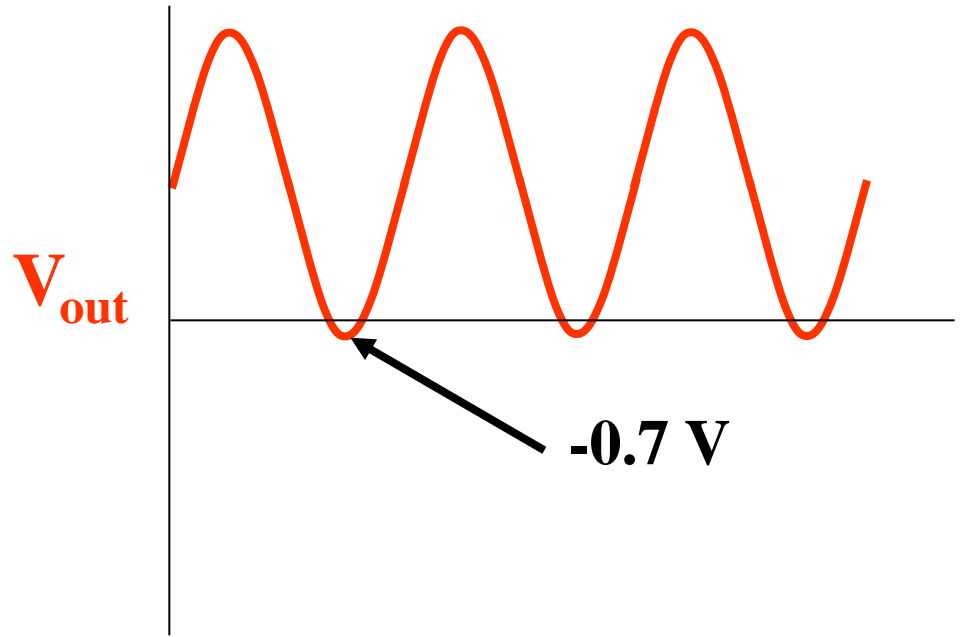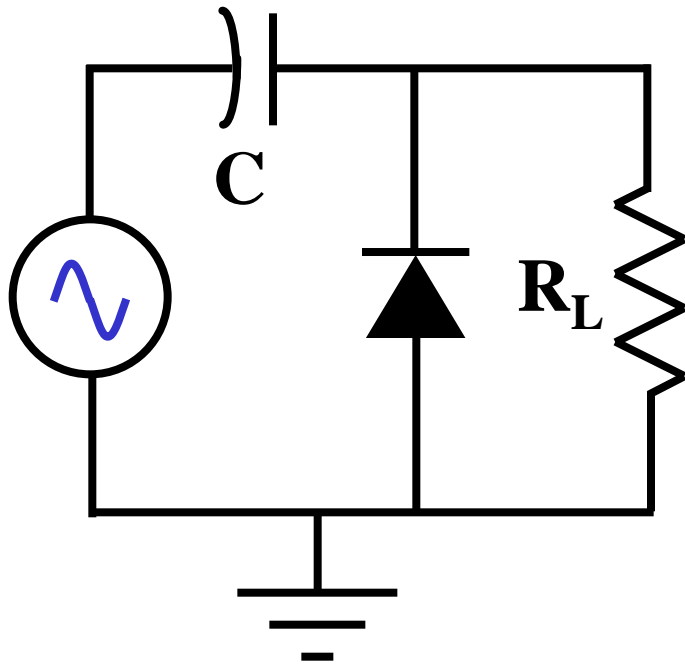


Stiff clamper: $R_L C > 100T$

Negative clamper

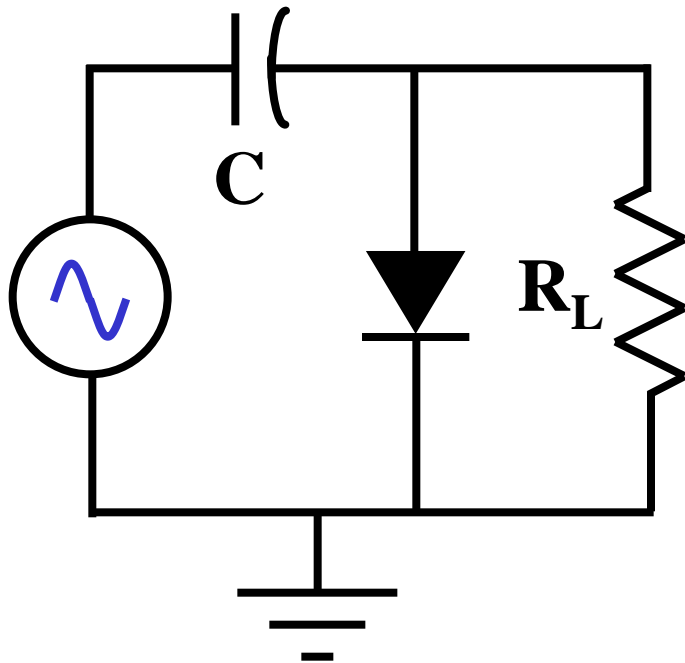

V_{out}

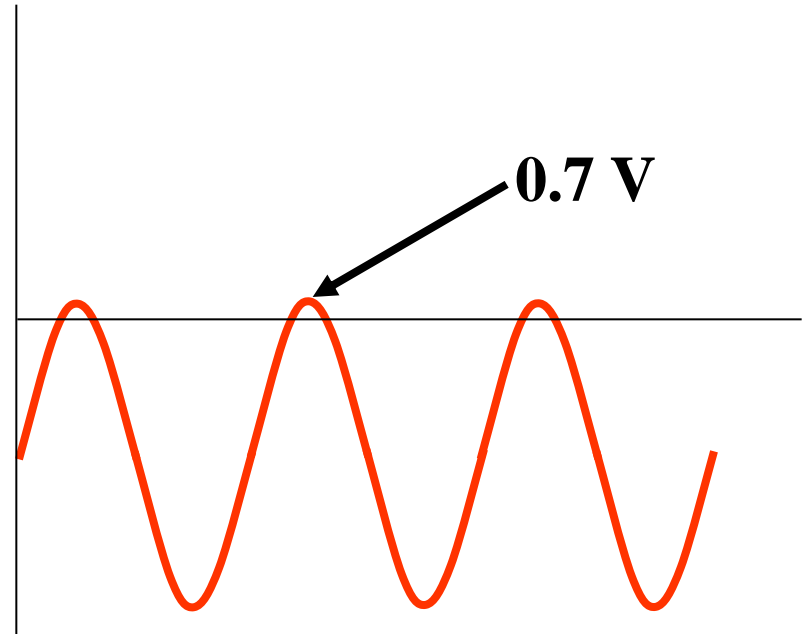


Stiff clamper: $R_L C > 100T$

Voltage multipliers

- A **voltage doubler** is similar to the peak-to-peak detector but uses rectifier diodes instead of small-signal diodes
- **Voltage triplers and quadruplers** multiply the input peak by factors of 3 and 4

Half-wave voltage doubler

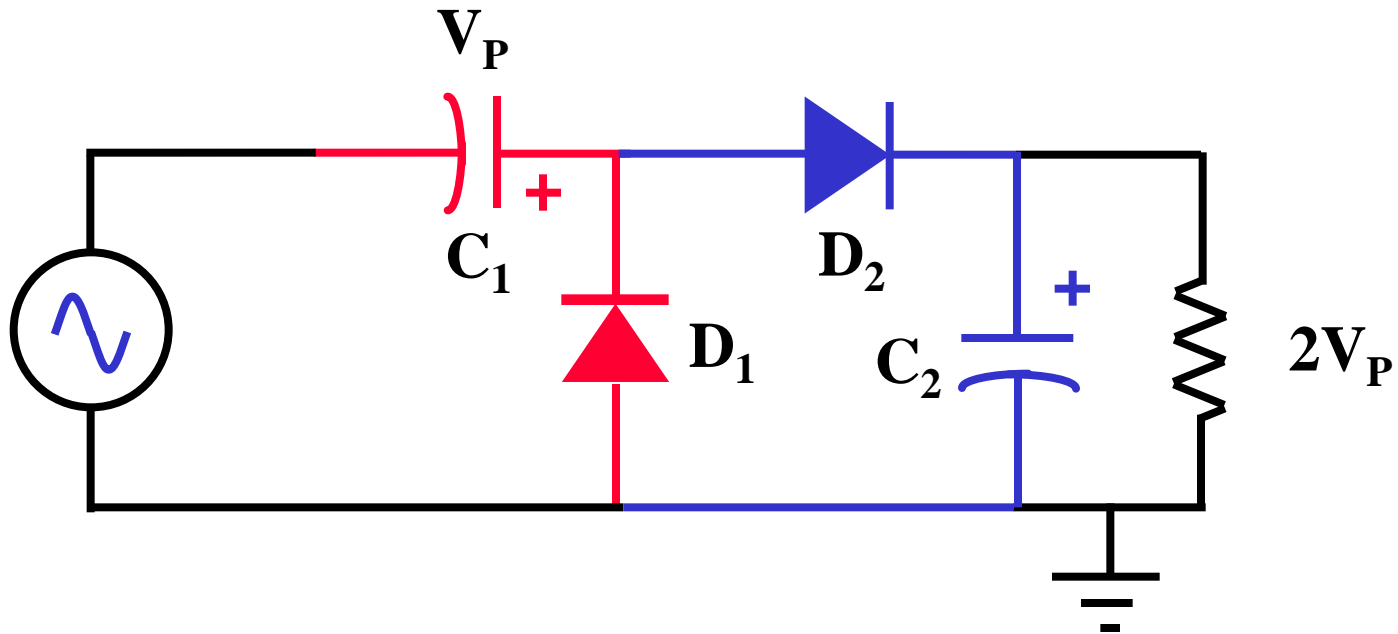

Full-wave voltage doubler

