

MALVINO & BATES

**Electronic
PRINCIPLES**

SEVENTH EDITION



Special-Purpose Diodes



Topics Covered in Chapter 5


- **Zener diode**
- **Loaded zener regulator**
- **Second approximation of a zener diode**
- **Zener drop-out point**
- **Reading a data sheet**
- **Troubleshooting**

Topics Covered in Chapter 5 (Continued)

- **Load lines**
- **Optoelectronic devices**
- **Schottky diode**
- **Varactor**
- **Other diodes**


Zener diode

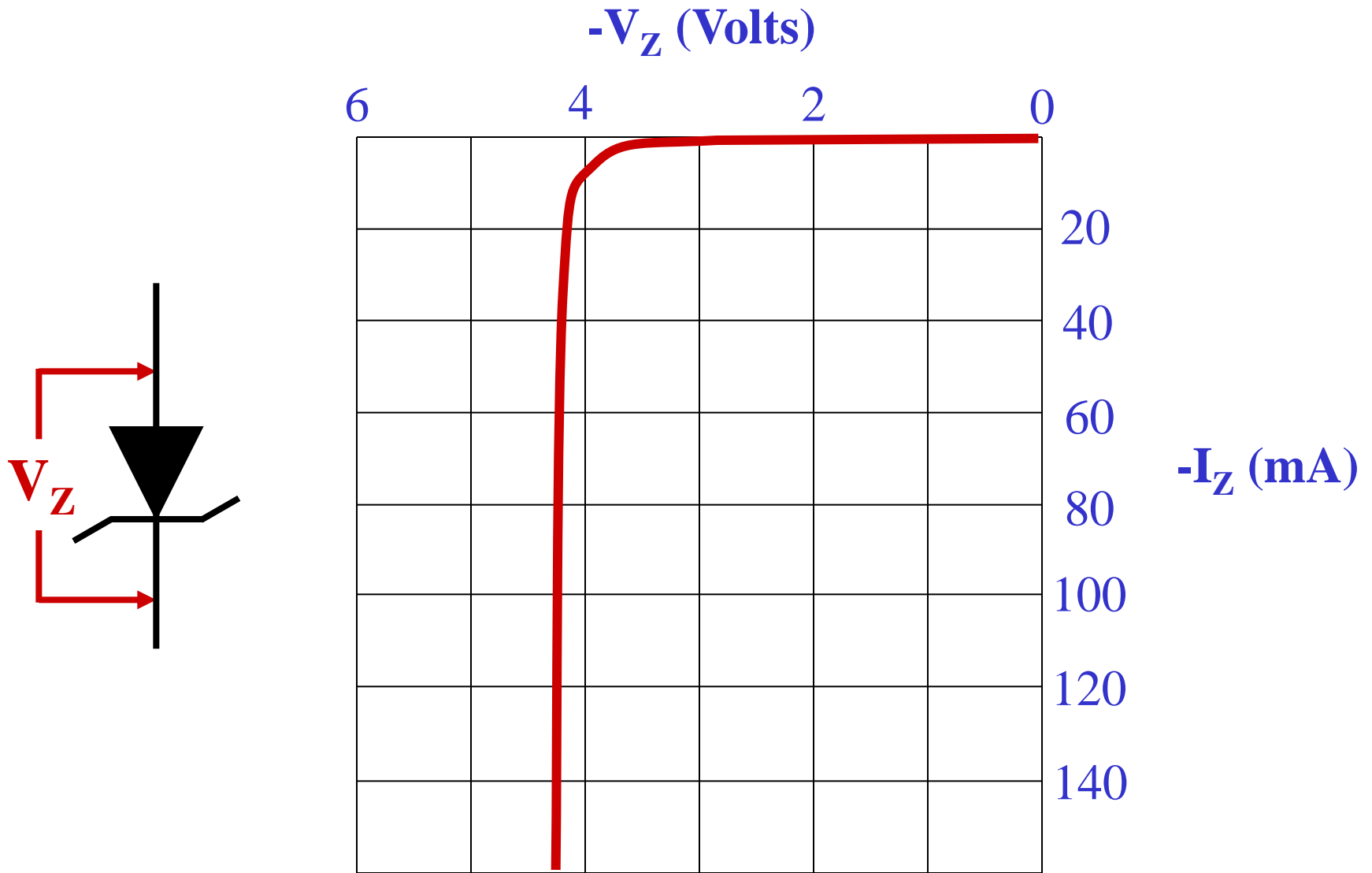- Optimized for operation in the **breakdown** region
- Main use: **voltage regulation**




Graph of zener current versus voltage

A zener diode voltage regulator

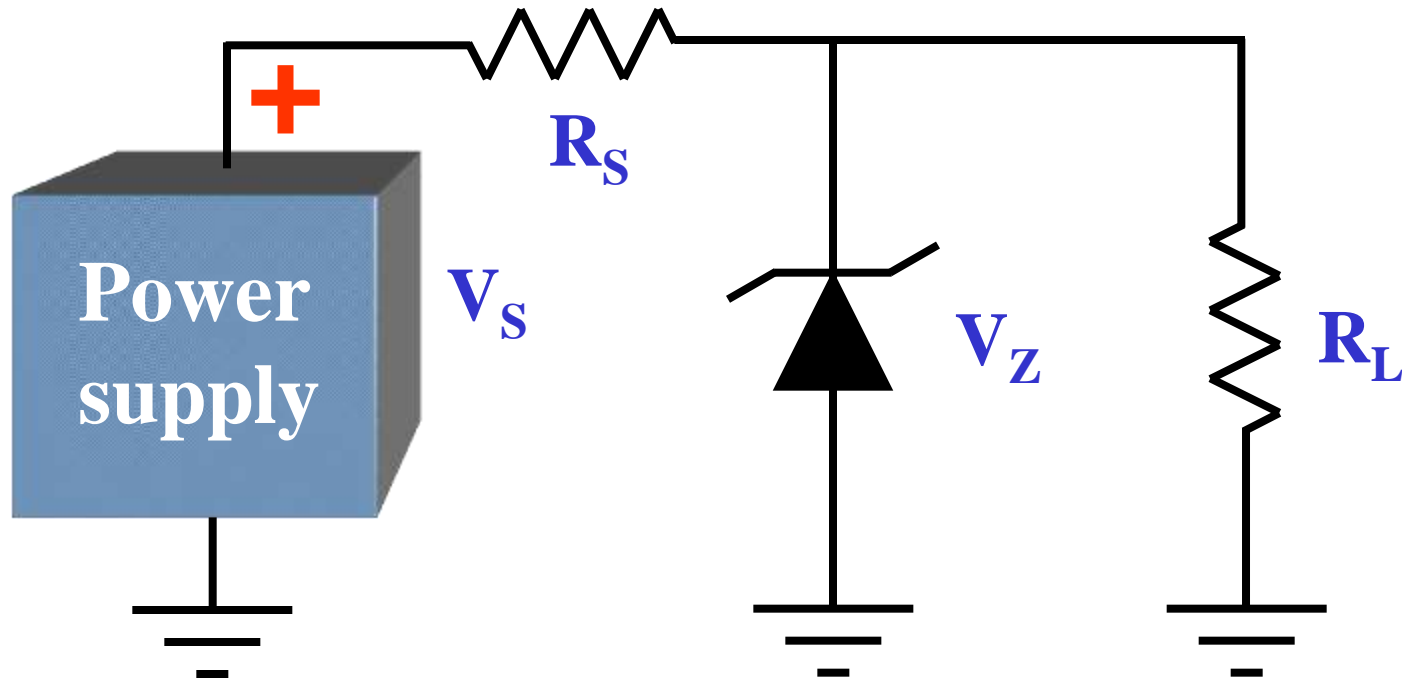

This circuit will **regulate** when the Thevenin voltage facing the zener diode is greater than the zener voltage.

$$V_{TH} = \frac{R_L}{R_S + R_L} V_S$$

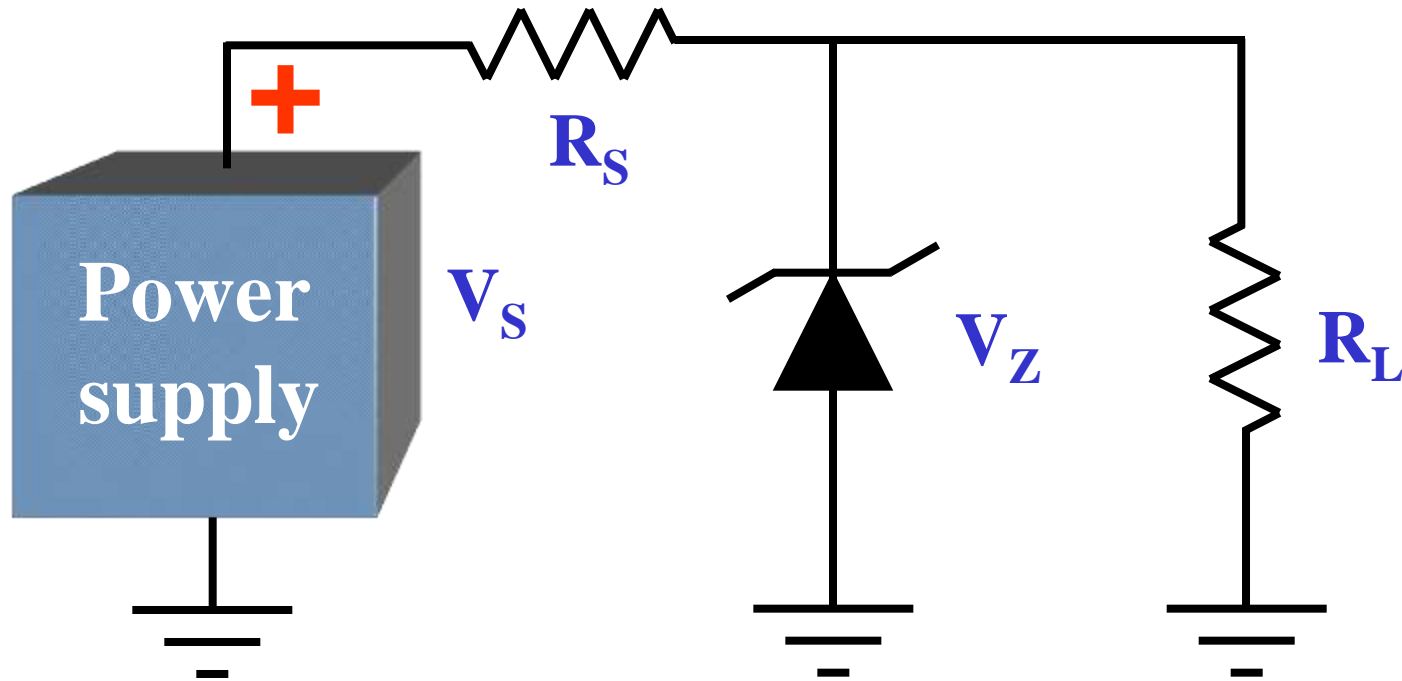

Assuming the zener is conducting:

$$I_S = \frac{V_S - V_Z}{R_S}$$



$$I_L = \frac{V_Z}{R_L}$$

$$I_Z = I_S - I_L$$


Zener waveshaping

- **Back-to-back zeners:**
 - ✓ **One zener conducts as one breaks down**
 - ✓ **Clipping results**


A zener waveshaping circuit

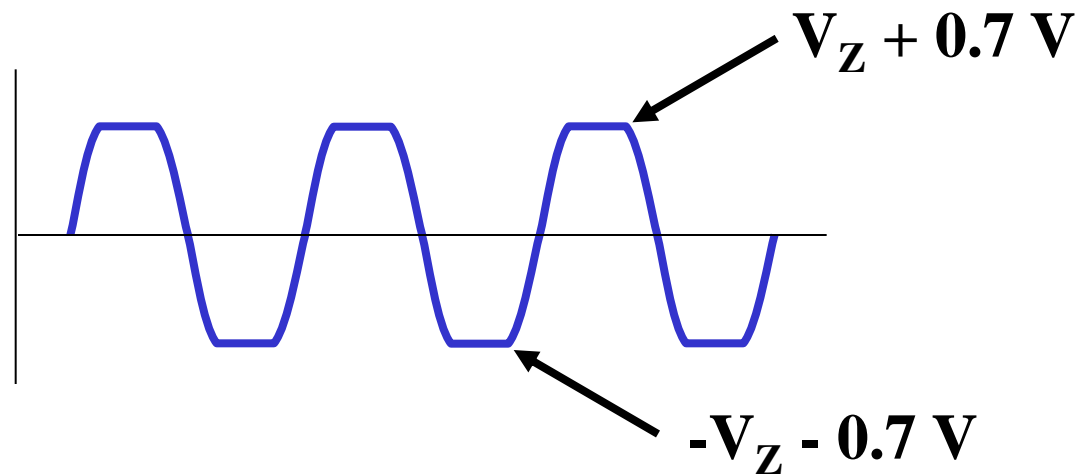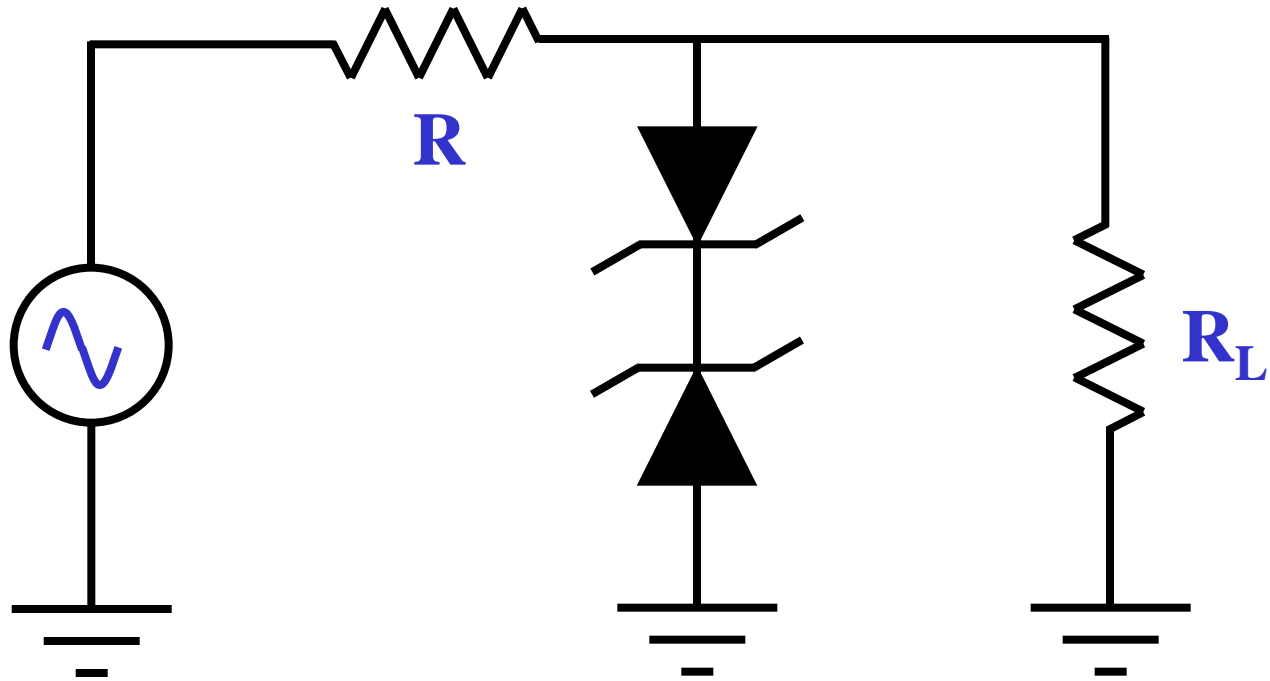

Zener diode
second approximation

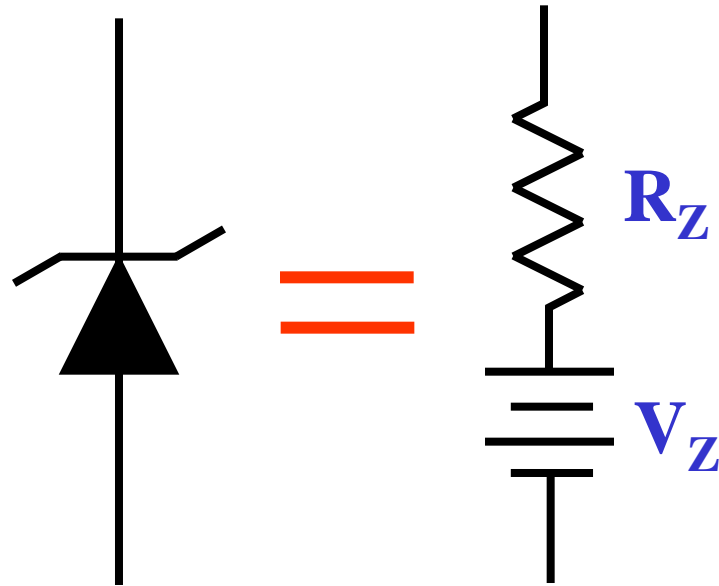


Applying the second approximation

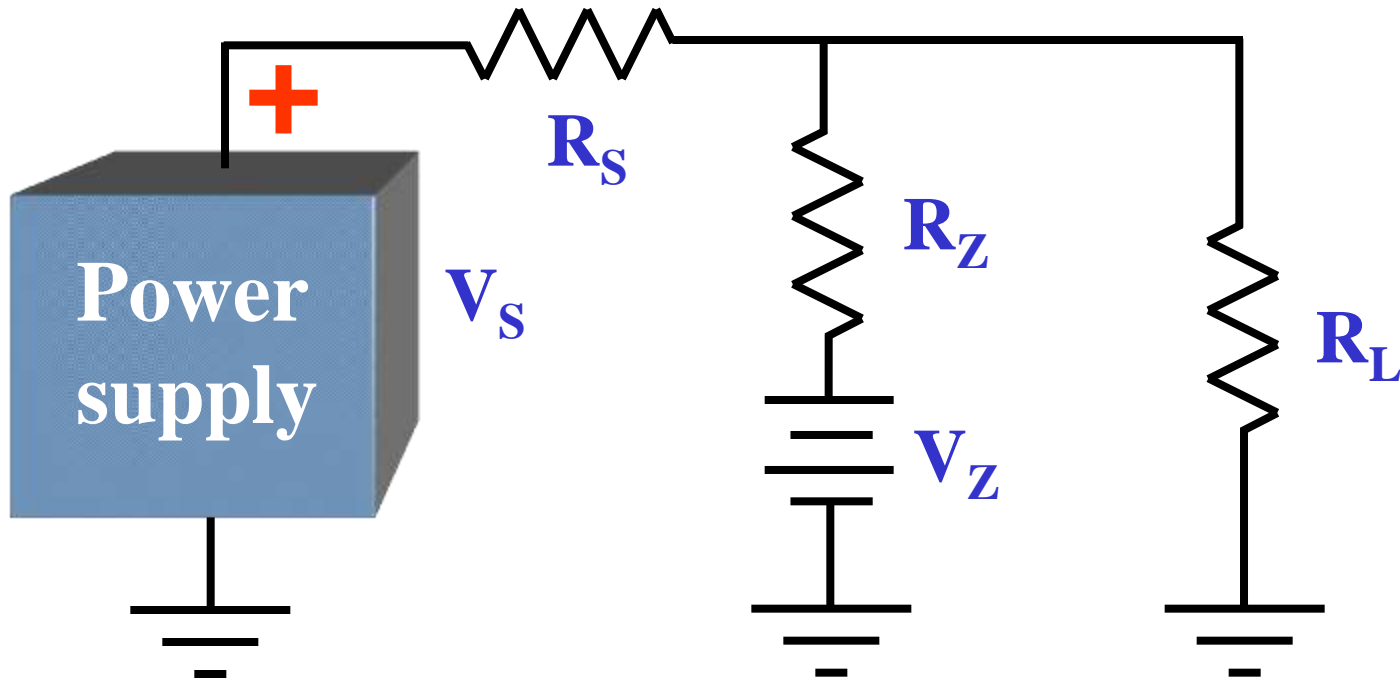

The deviation in load voltage from the ideal case:

$$\Delta V_L = I_Z R_Z$$

The zener regulator also reduces ripple

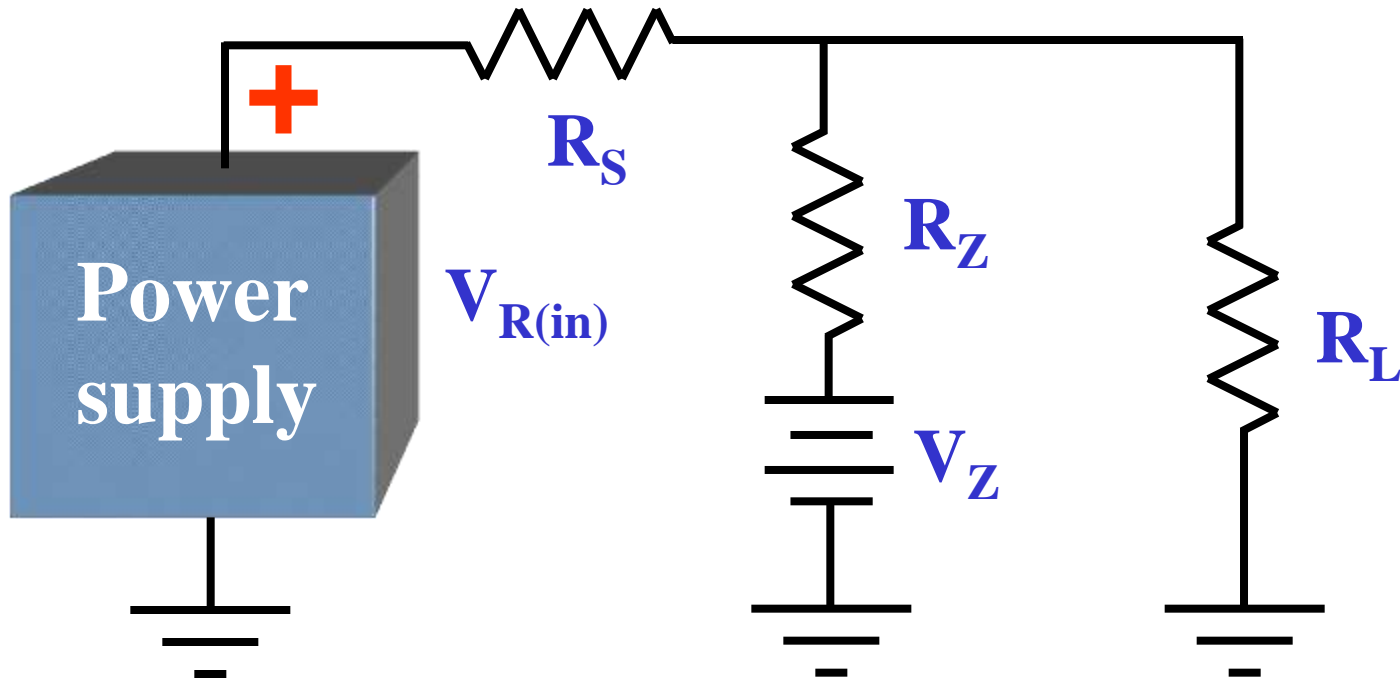

Assuming that both R_L and $R_S \gg R_Z$:

$$V_{R(out)} \cong \frac{R_Z}{R_S} V_{R(in)}$$

Zener diode ratings


- **Maximum power = $P_{Z(\max)} = V_Z I_{Z(\max)}$**
- **Available tolerances: 1, 2.5 and 20 percent**
- **Zener resistance, R_{ZT} , increases at the knee of the characteristic curve**
- **A derating factor such as 6.67 mW per degree for temperatures above 50 degrees Celsius is typical.**

Troubleshooting


- Usually begin by measuring voltages
- Analyze symptoms
- Ask “what if” on the way to a solution

Load lines

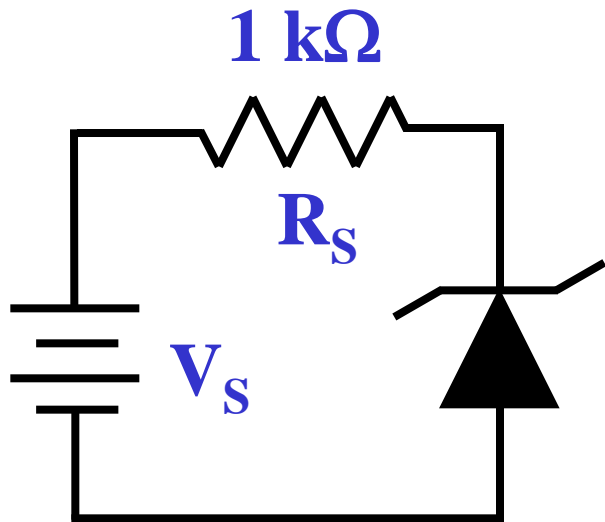- The intersection of the load line and the zener diode is the **Q (operating) point**
- When the source voltage changes, a different load line appears with a different Q point



$$V_S = 30\text{ V}$$

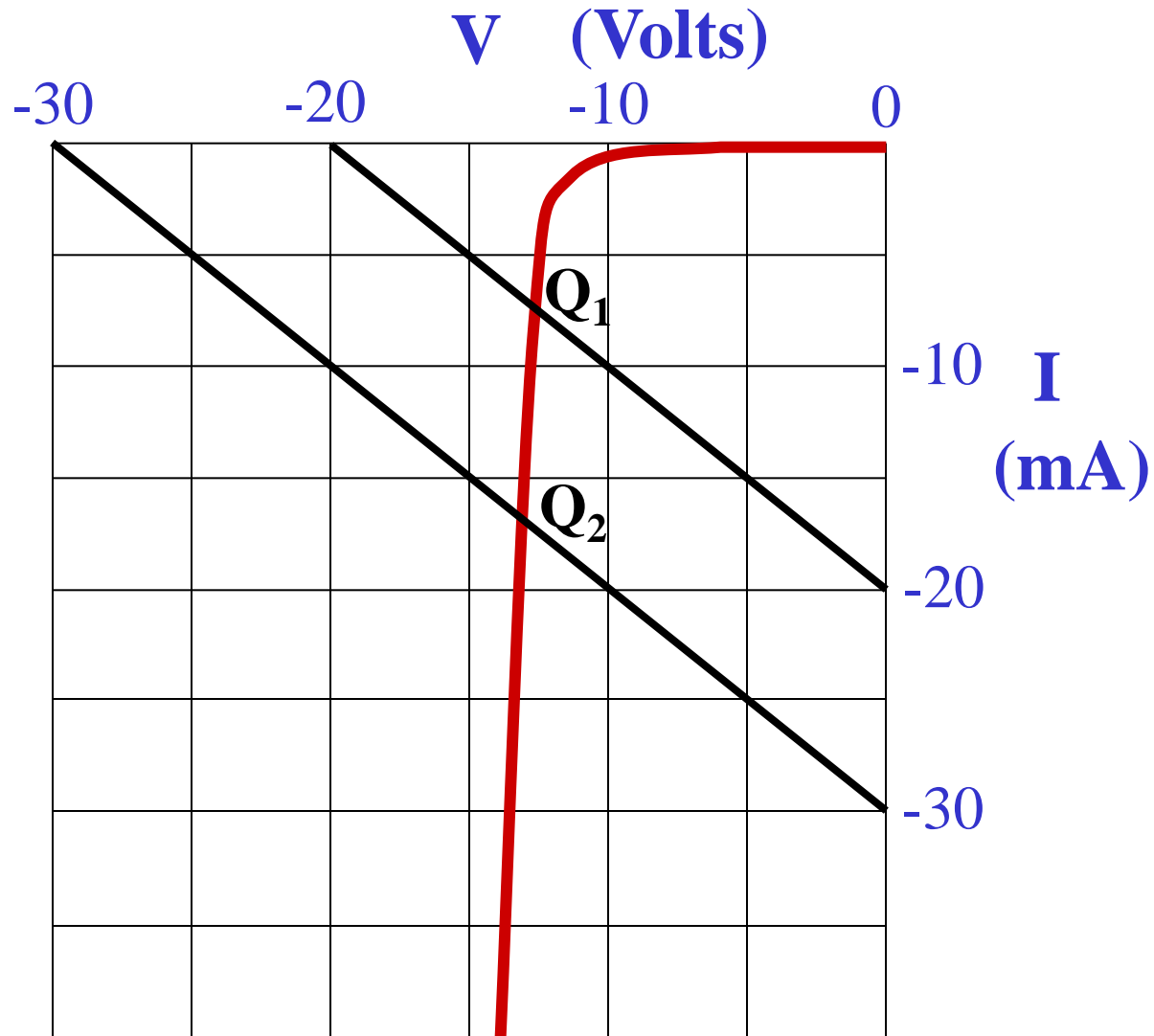


What happens to V_Z when V_S varies from 20 to 30 volts?


Load lines provide a graphical solution.

Optoelectronics

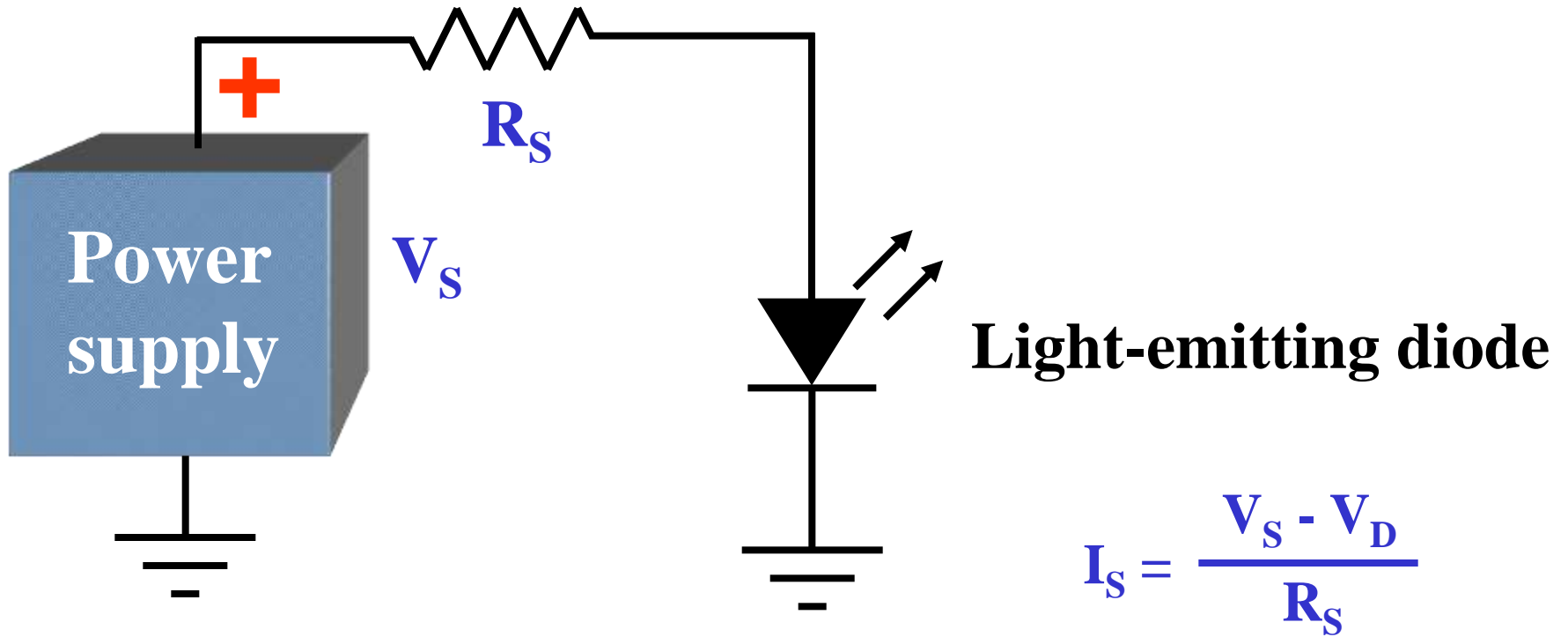
- **Technology of optics and electronics**
- **LEDs**
- **Photodiodes**
- **Optocouplers**
- **Laser diodes**



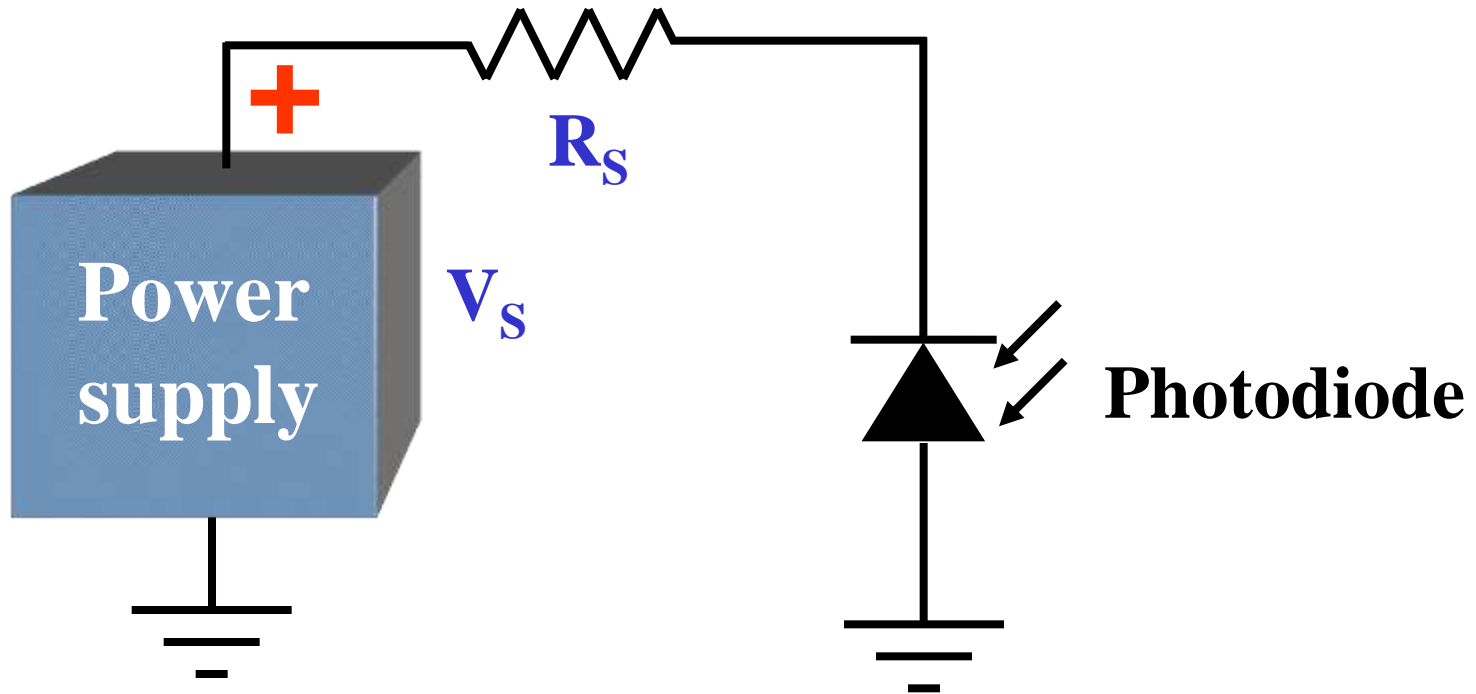The typical voltage drop for most LEDs is from 1.5 to 2.5 V.



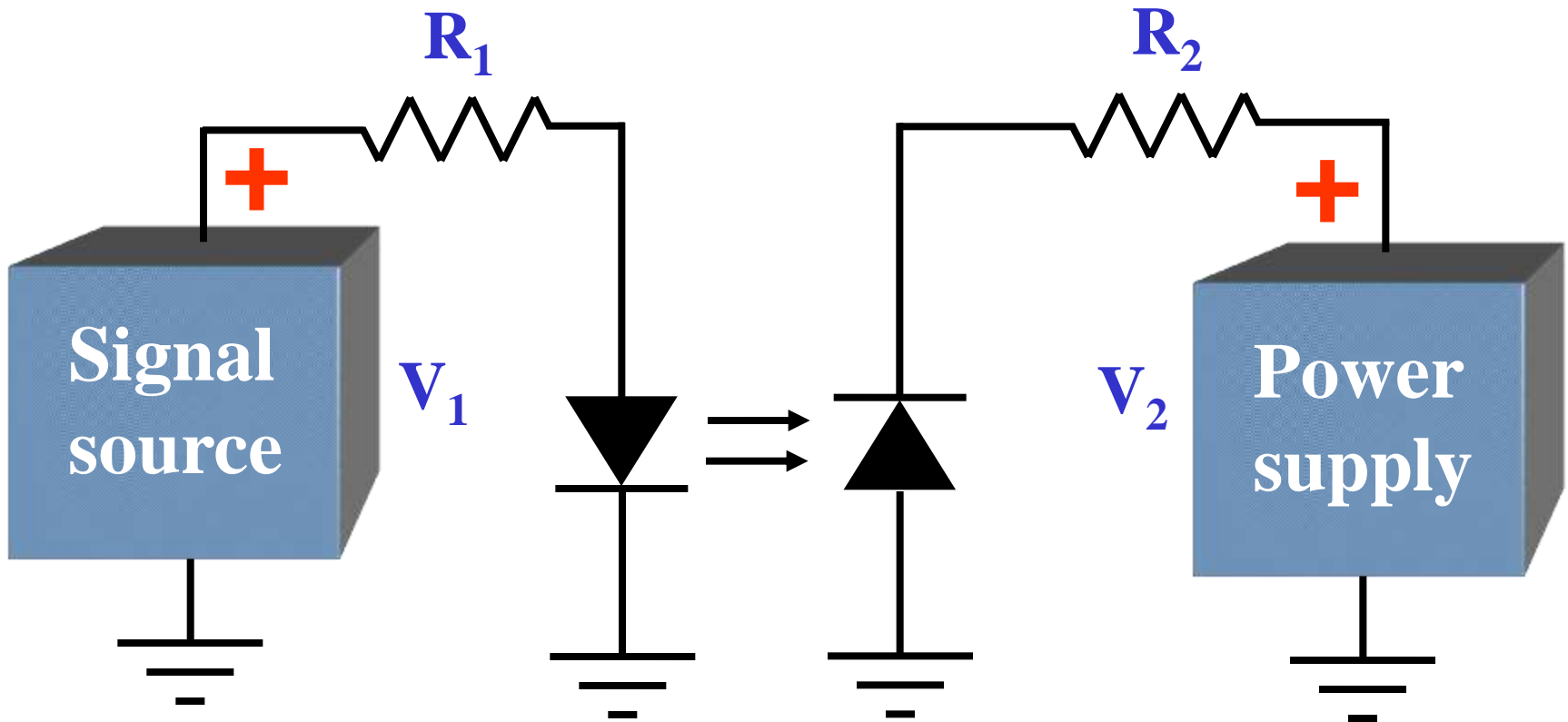Photodiodes are reverse biased and conduct when struck by light





Optocoupler combines an LED and a photodiode


Schottky diode

- A special diode with almost zero reverse recovery time
- Useful at high frequencies where short switching times are needed



High-frequency rectification

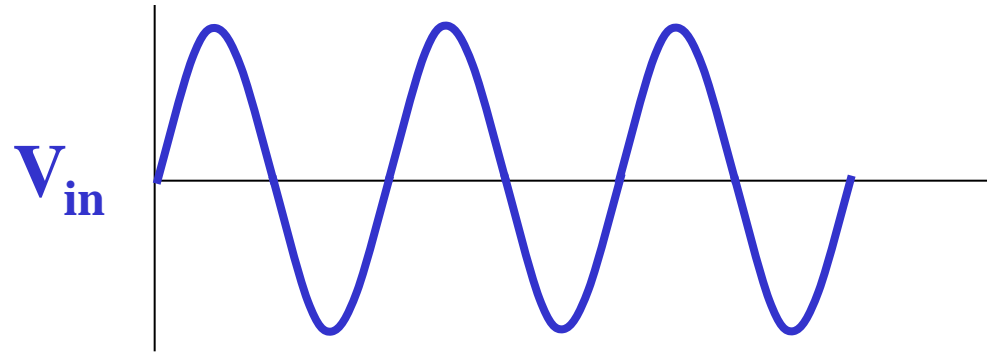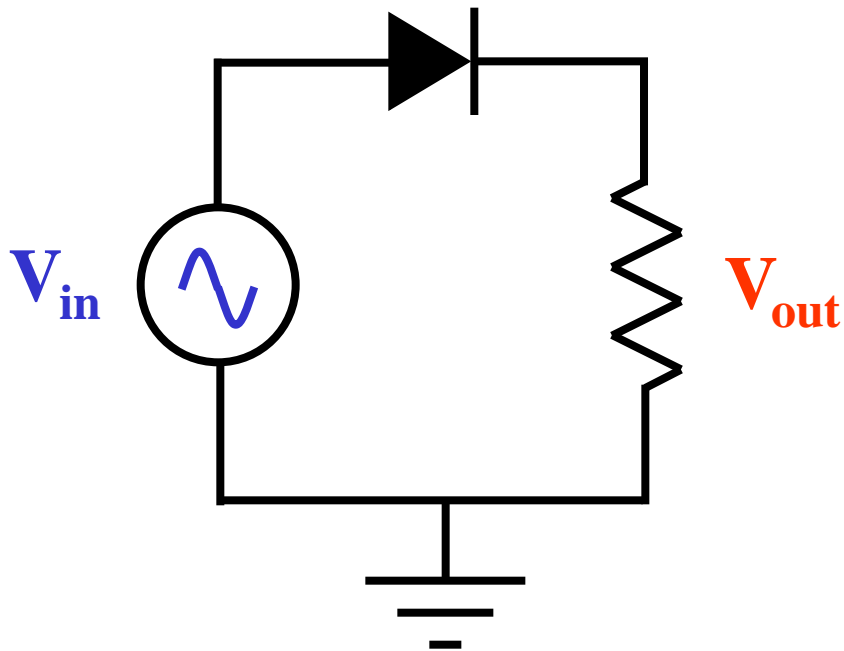

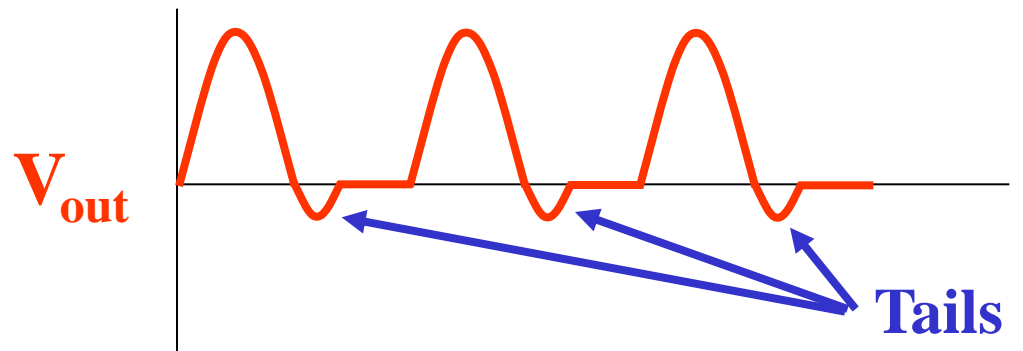
Charge storage can cause poor performance at high frequencies.



Hot-carrier rectifier

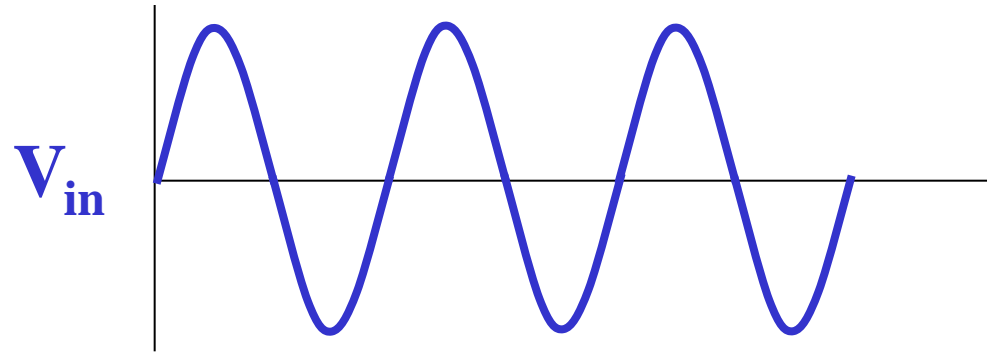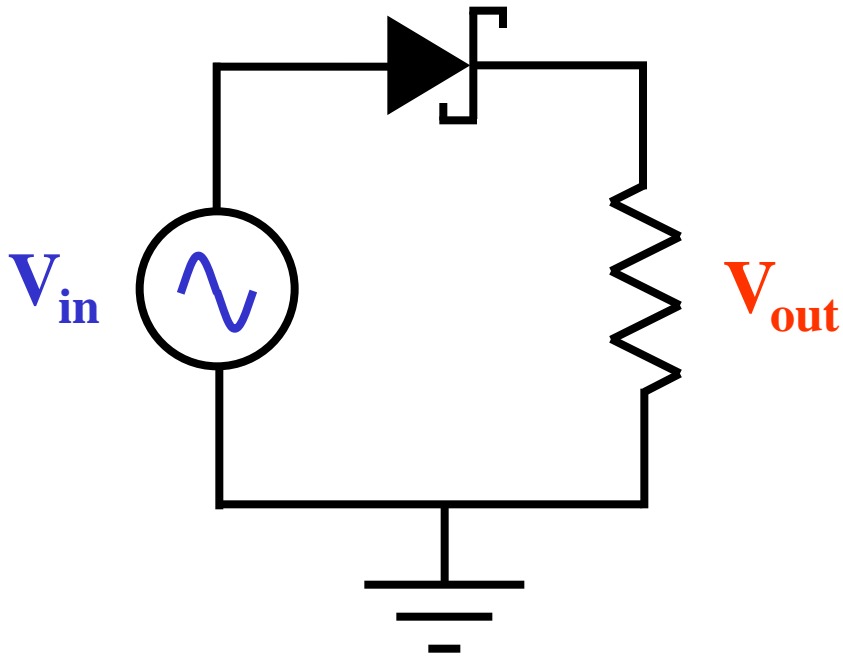


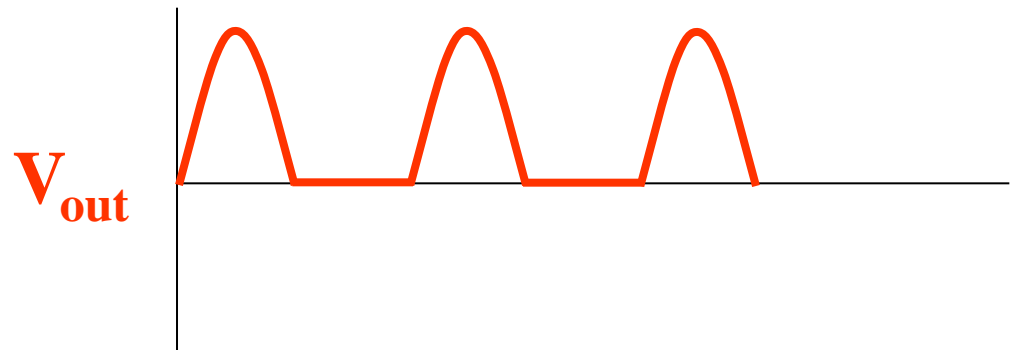Schottky diodes eliminate tails at high frequencies.




Varactor diode

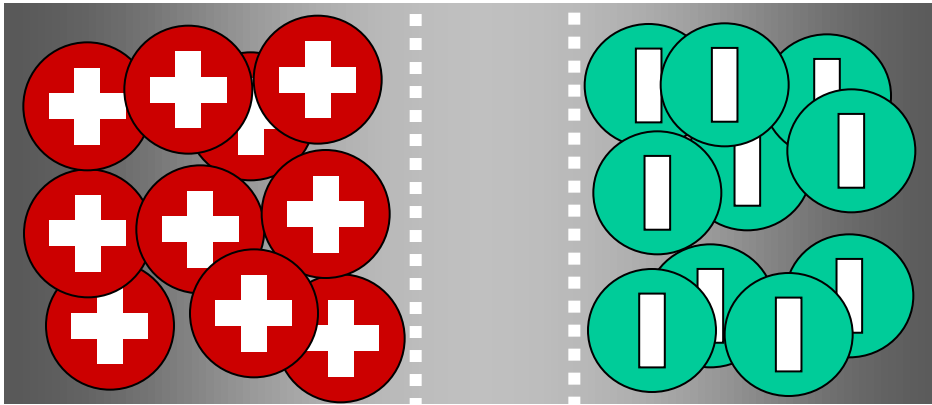
- Exhibits variable capacitance
- Can tune resonant circuits
- Applications include radio and television tuning



Less reverse bias
(**more** capacitance)

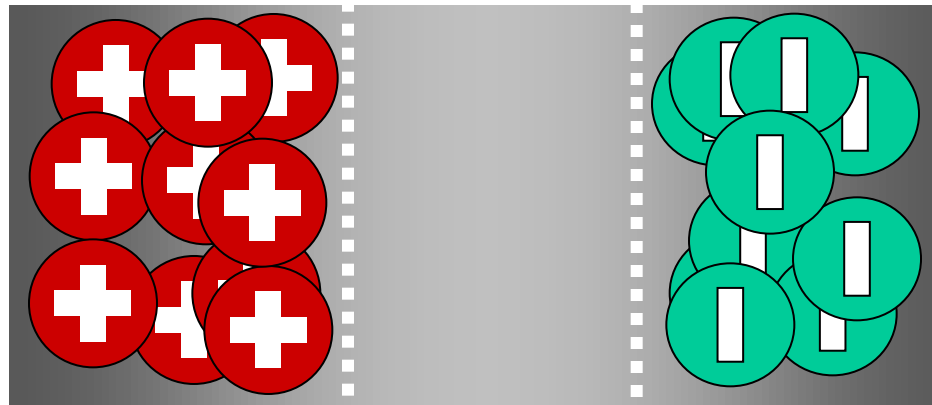


More reverse bias
(**less** capacitance)

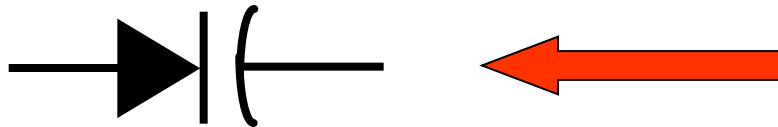


Varactor symbol

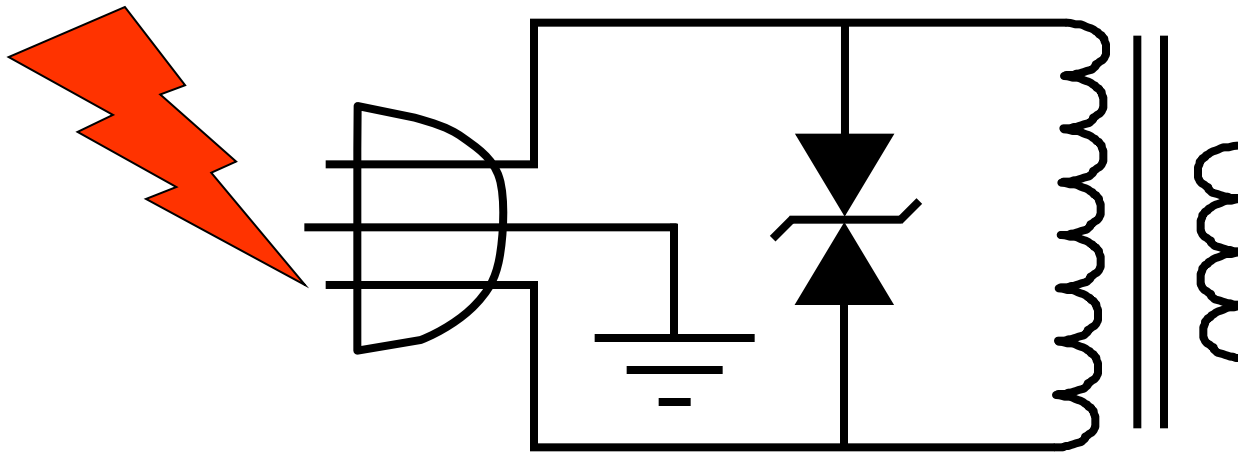A varistor diode can be used to protect line-operated equipment from voltage surges.



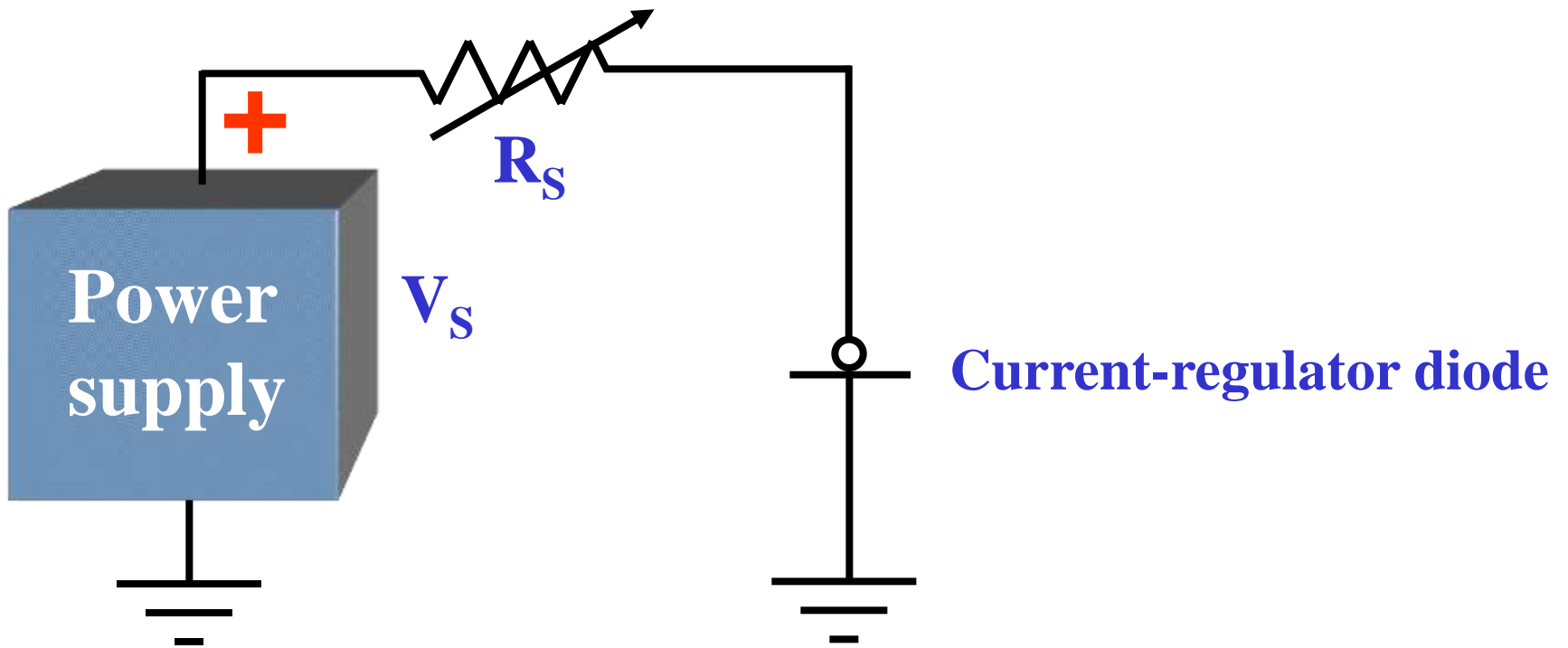A varistor diode is also called a **transient suppressor**



R_S can vary over a wide range and the current stays the same

Other diode types

- Laser: emits coherent light
- Step-recovery: snaps off when reverse biased
- Back: conducts better when reverse biased
- Tunnel: has a negative resistance region
- PIN: operates as a variable resistor at RF and microwave frequencies

Other diode applications

- **Laser: CD players, communications**
- **Step-recovery: Frequency multipliers**
- **Back: Small-signal rectifiers**
- **Tunnel: High-frequency oscillators**
- **PIN: RF and microwave modulator circuits**