

MALVINO & BATES

**Electronic
PRINCIPLES**

SEVENTH EDITION



Bipolar Junction Transistors



Topics Covered in Chapter 6

- **Unbiased transistor**
- **Biased transistor**
- **Transistor currents**
- **The CE connection**
- **The base curve**


Topics Covered in Chapter 6 (Continued)

- **Collector curves**
- **Transistor approximations**
- **Reading data sheets**
- **Surface mount transistors**
- **Troubleshooting**

Unbiased transistor

- Three doped regions: emitter, base, and collector
- Two pn junctions: emitter-base and base-collector
- NPN or PNP
- Silicon or germanium

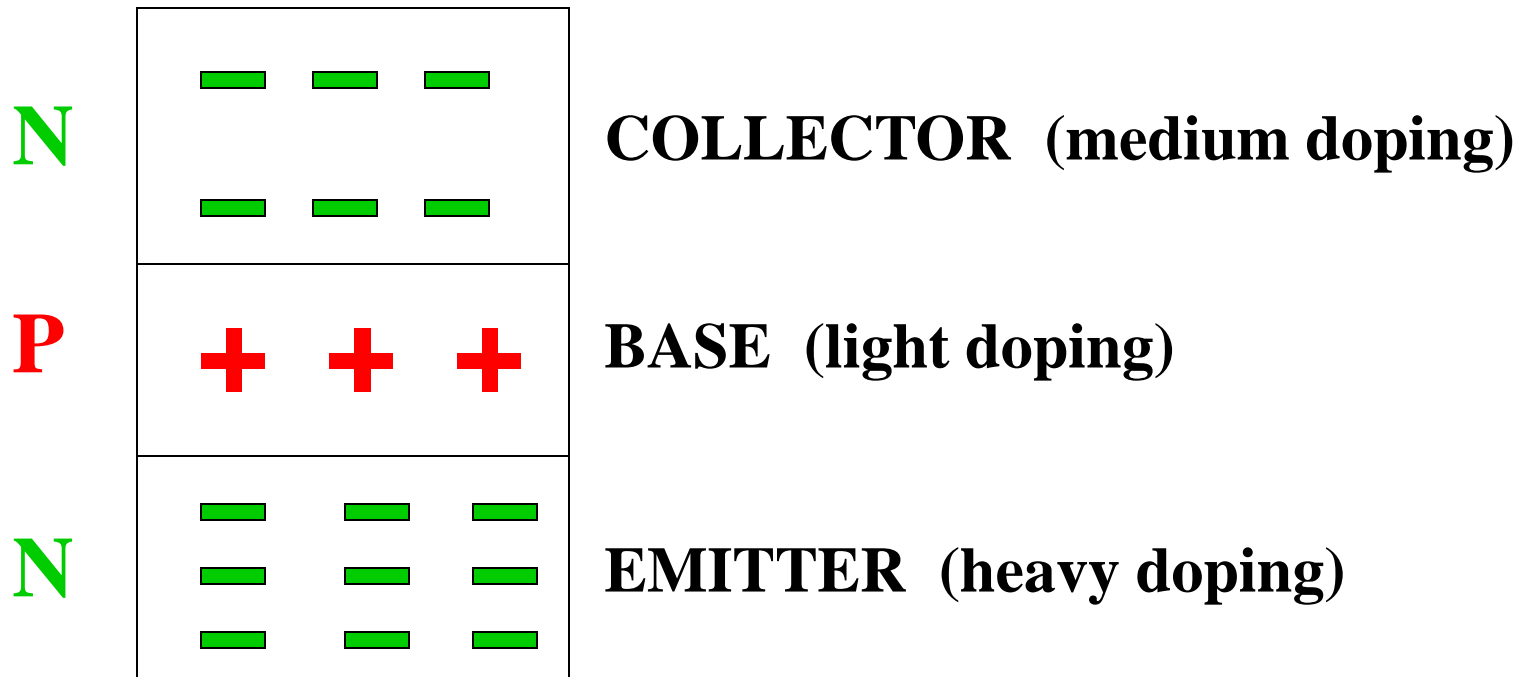
The bipolar junction transistor has 3 doped regions.



Biased transistor


- Forward bias the **emitter** diode
- Reverse bias the **collector** diode

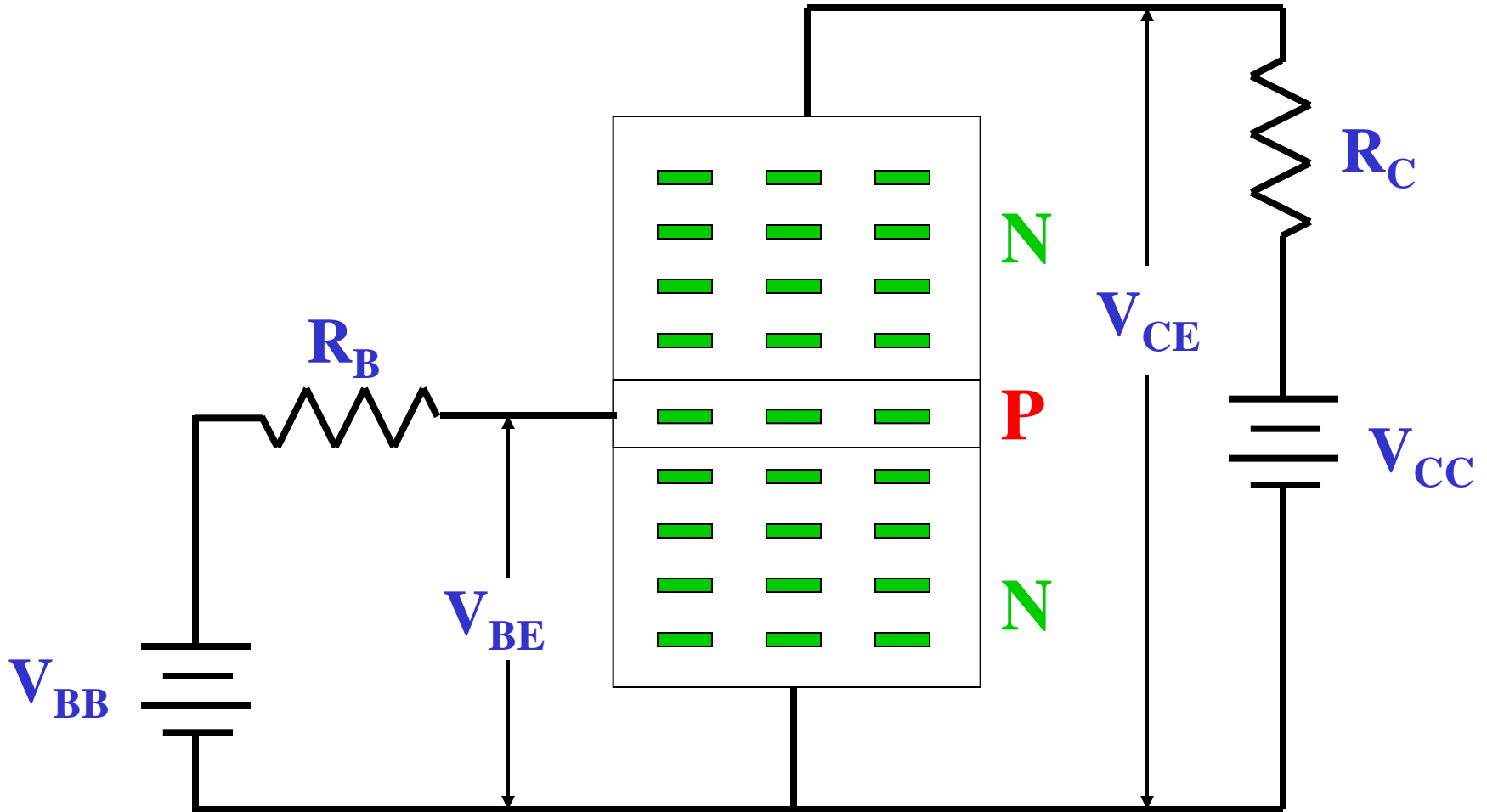In a properly biased NPN transistor, the emitter electrons diffuse into the base and then go on to the collector.



Transistor currents

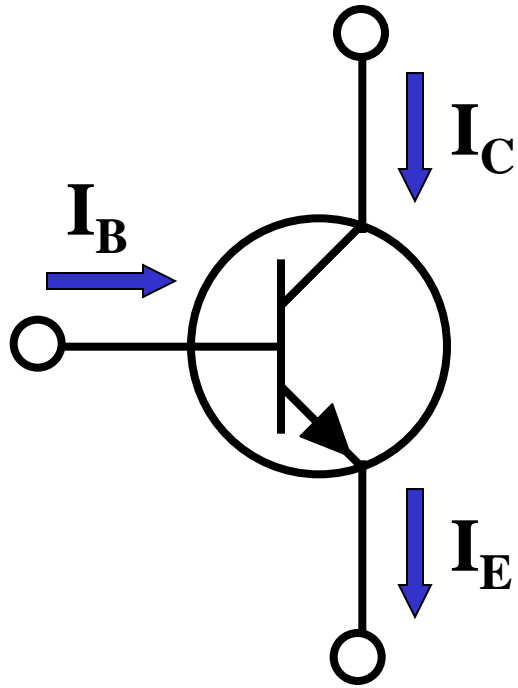
- The ratio of collector current to base current is **current gain** (β_{dc} or h_{FE})
- Current gain is typically **100 to 300**



Conventional flow

$$I_E = I_C + I_B$$

$$\alpha_{dc} = \frac{I_C}{I_E}$$

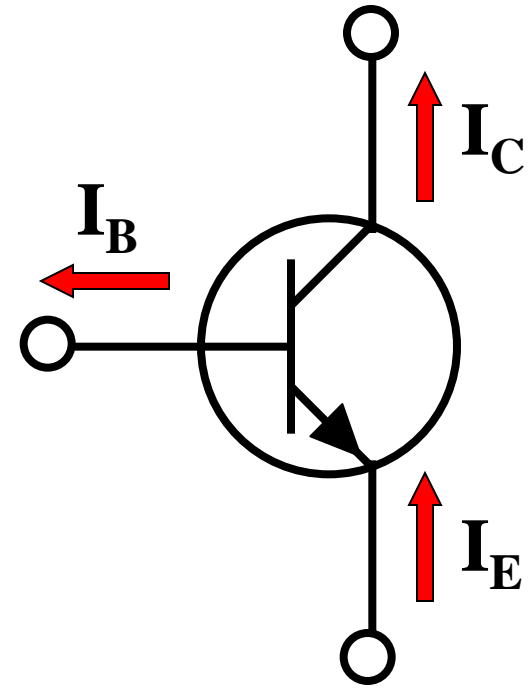

Electron flow

$$I_C \cong I_E$$


$$\beta_{dc} = \frac{I_C}{I_B}$$

$$I_B \ll I_C$$

The CE connection

- The emitter is grounded or common
- The base-emitter acts like a diode
- The base-collector acts like a current source that is equal to β_{dc} times the base current

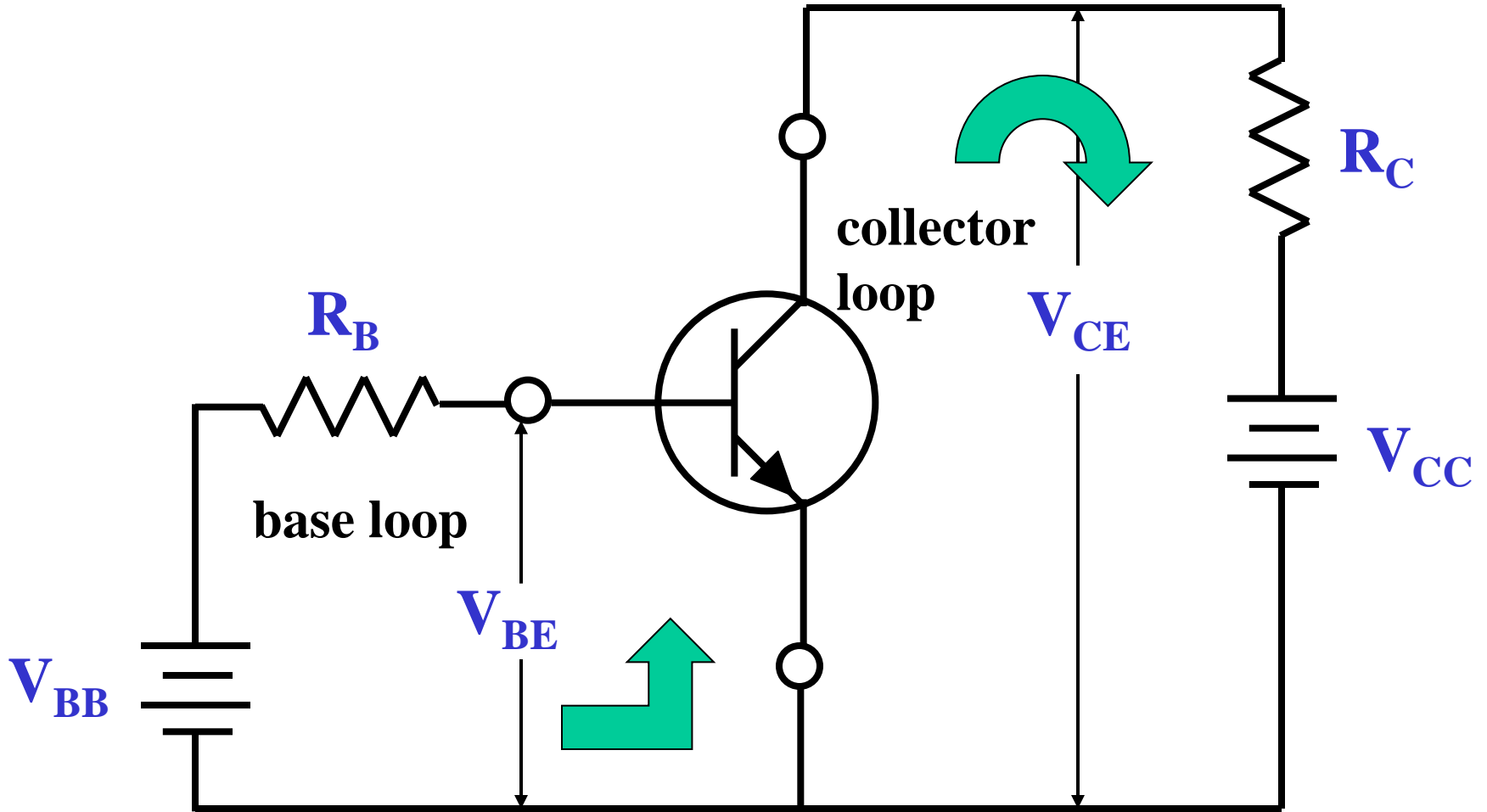The common emitter connection has two loops:
the **base** loop and the **collector** loop.




Subscript notation

- When the subscripts are the same, the voltage represents a source (V_{CC}).
- When the subscripts are different, the voltage is between two points (V_{CE}).
- Single subscripts are used for node voltages with ground serving as the reference (V_C).

Base curve


- **Graph similar to that of a diode**
- **Diode approximations are used for analysis (typically - ideal or second)**

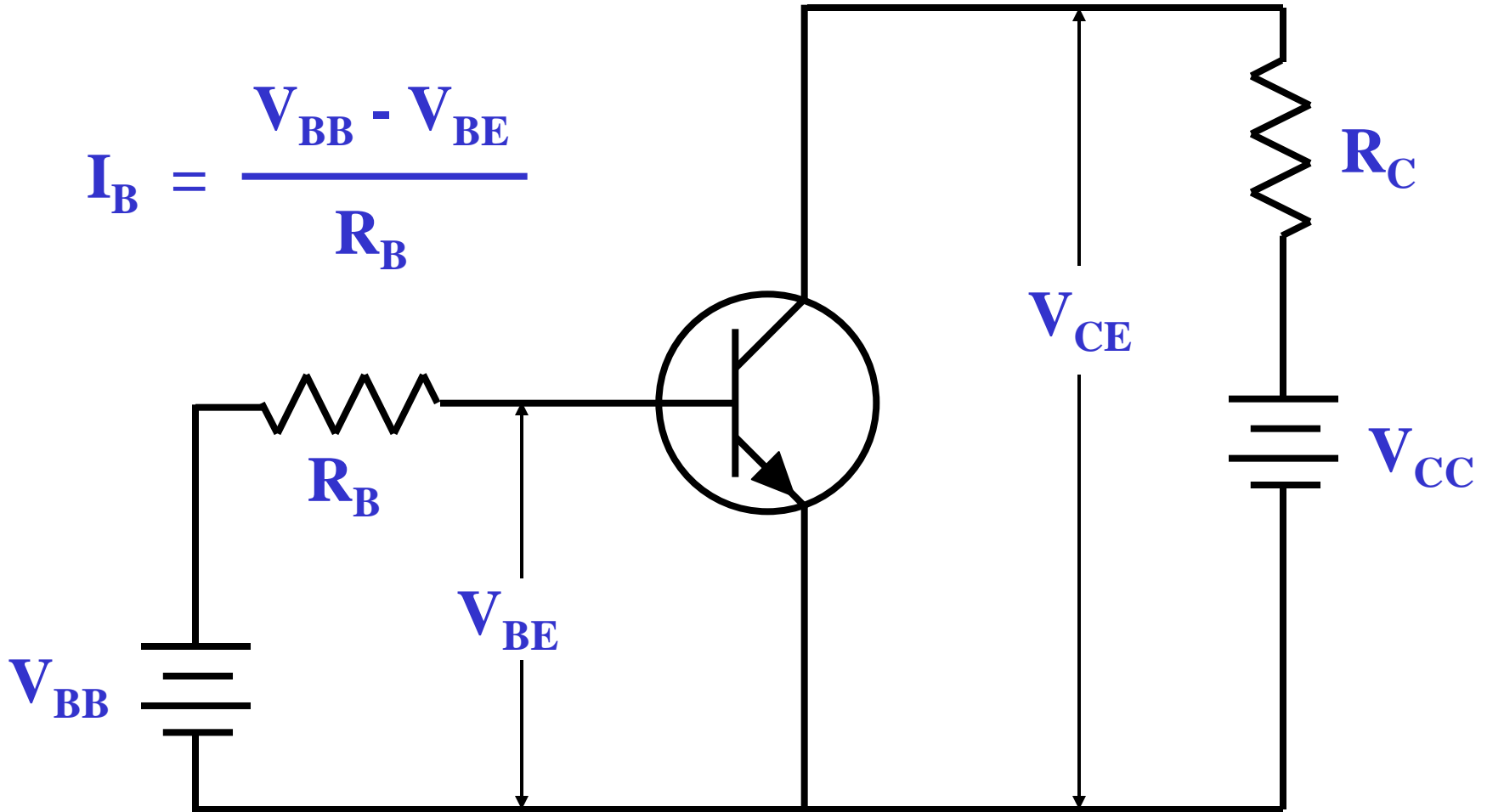The base circuit is usually analyzed with the same approximation used for diodes.



A graph of I_C versus V_{CE}

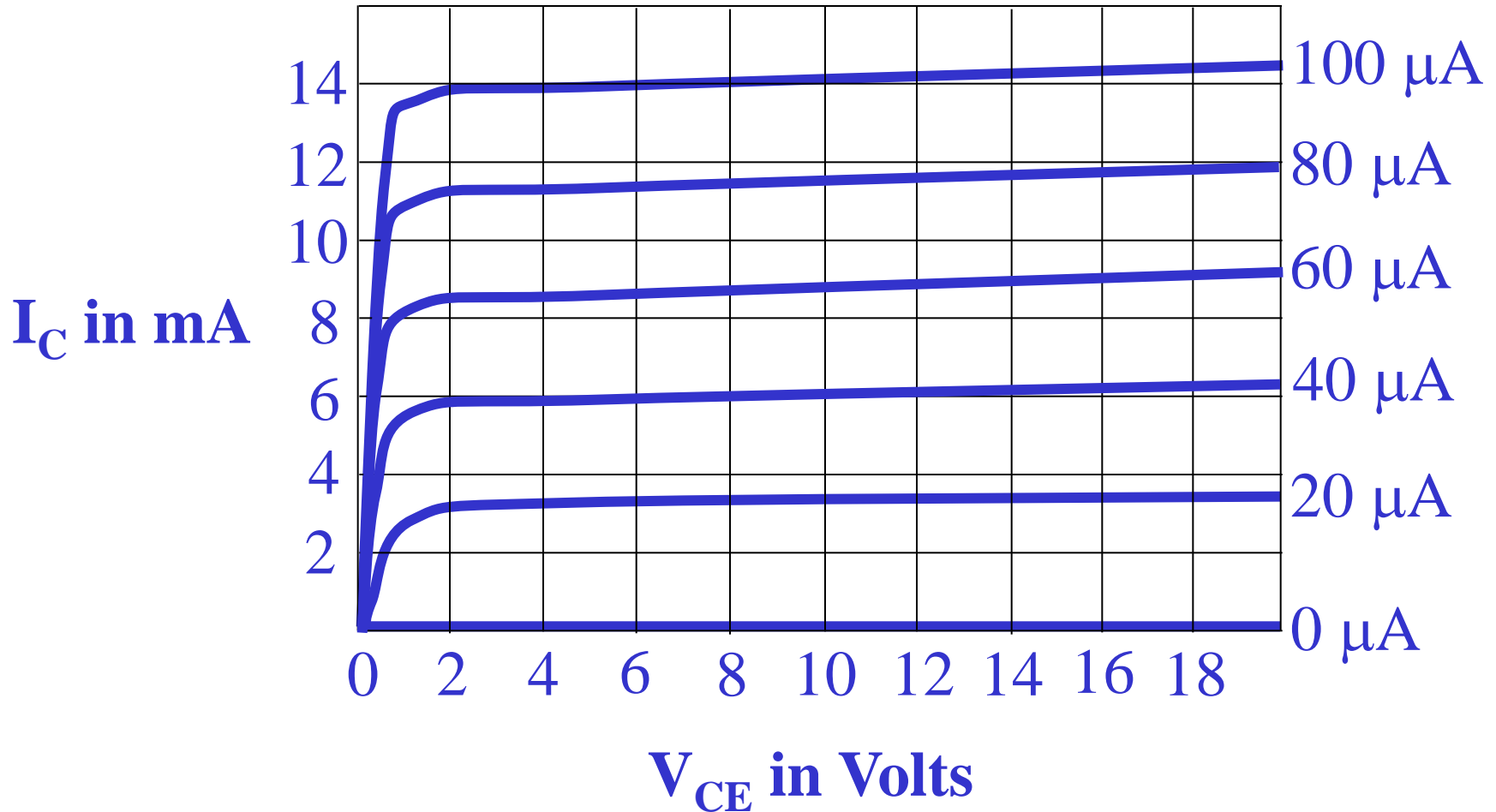(Note that each new value of I_B presents a new curve.)



This set of curves is also called a family of curves.


Regions of operation

- **Active** - - - used for linear amplification
- **Cutoff** - - - used in switching applications
- **Saturation** - - - used in switching applications
- **Breakdown** - - - can destroy the transistor and should be avoided

Transistor circuit approximations


- **First:** treat the base-emitter diode as ideal and use βI_B to determine I_C . Use for troubleshooting.
- **Second:** correct for V_{BE} and use βI_B to determine I_C .
- **Third (and higher):** correct for bulk resistance and other effects. Usually accomplished by computer simulation. Use for design work.

The second approximation:

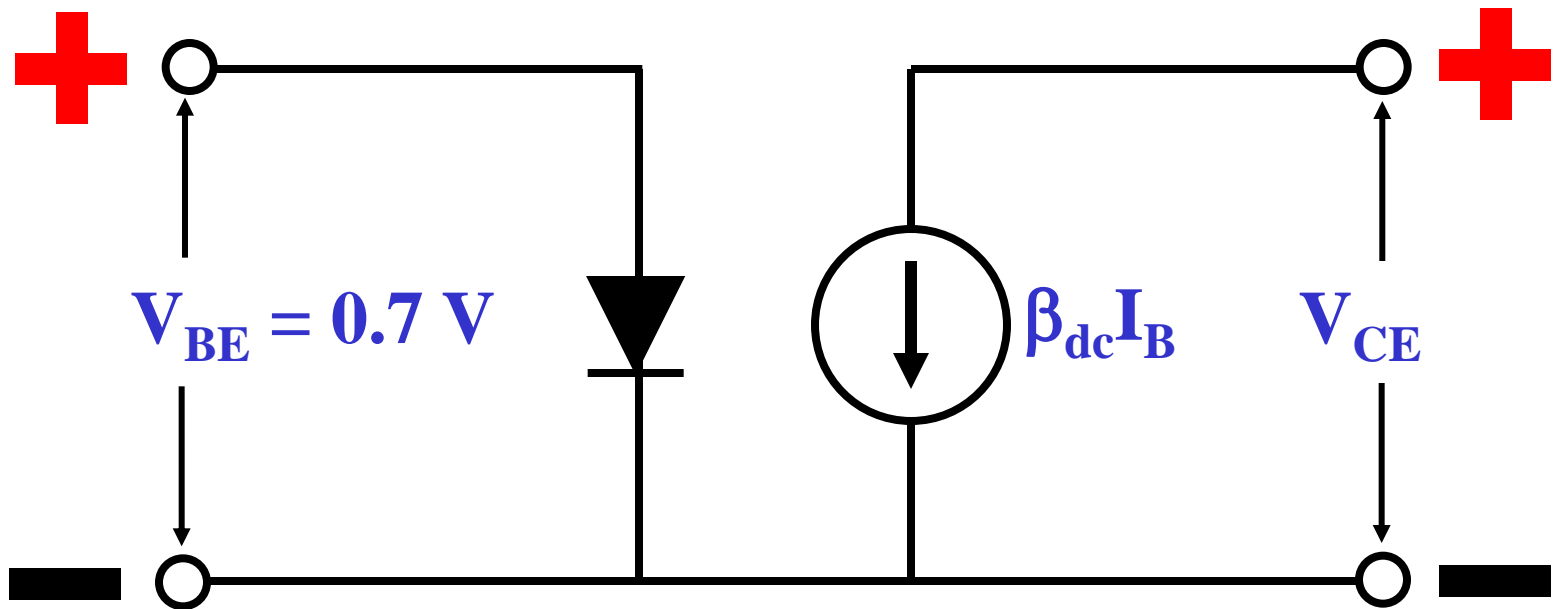


$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$
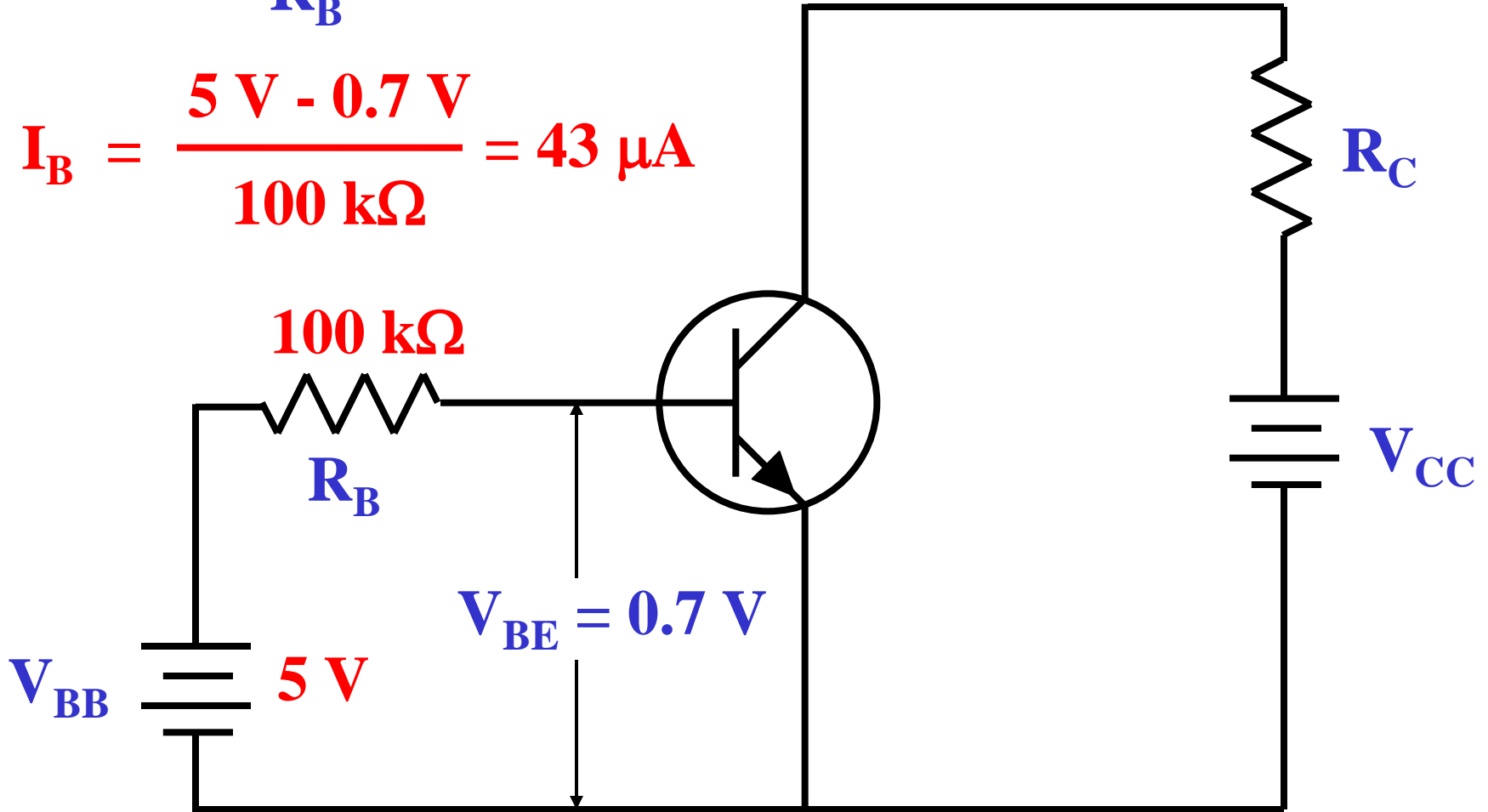
$$I_B = \frac{5\text{ V} - 0.7\text{ V}}{100\text{ k}\Omega} = 43\ \mu\text{A}$$




$$I_C = \beta_{dc} I_B$$
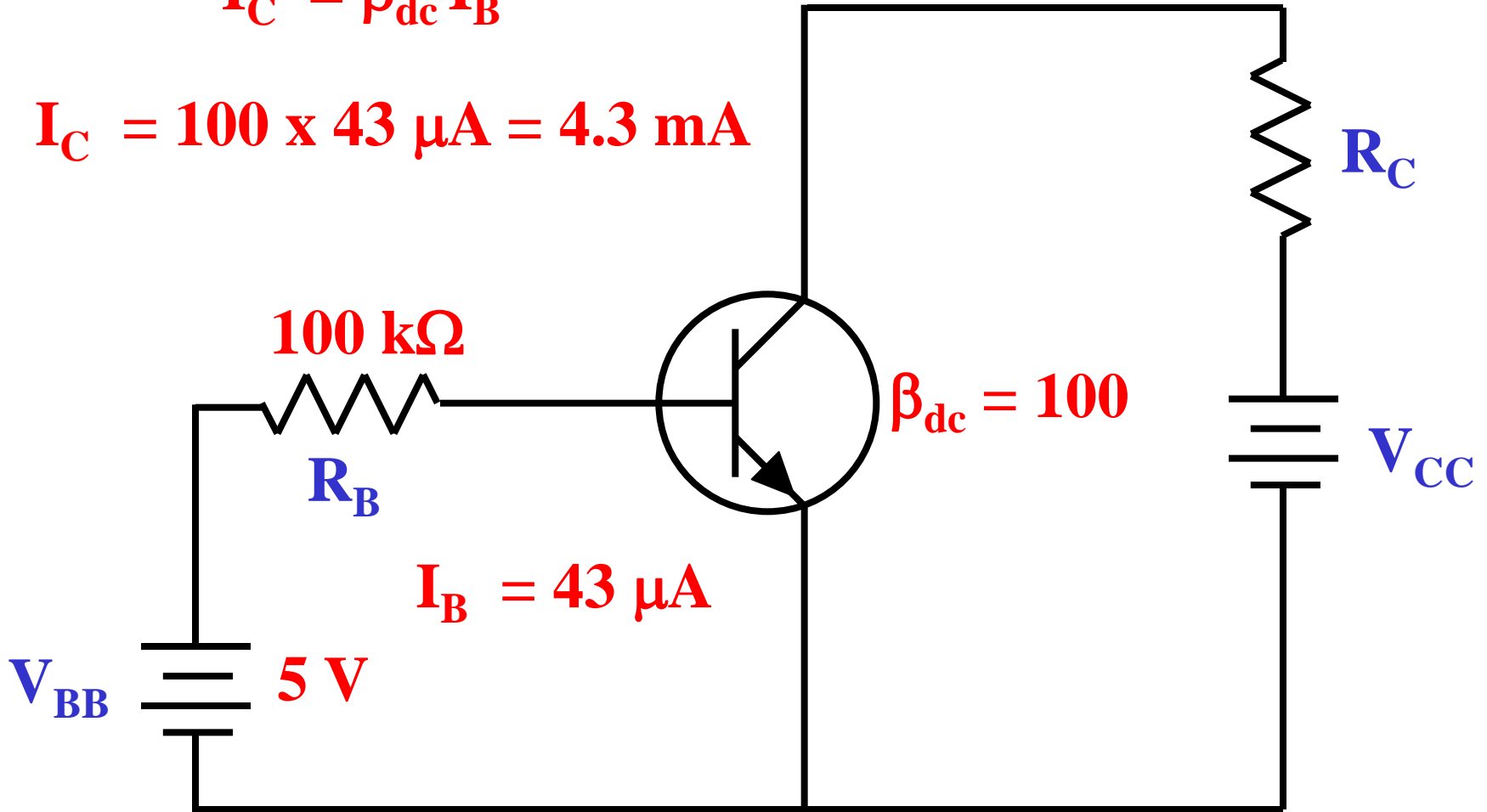
$$I_C = 100 \times 43 \mu\text{A} = 4.3 \text{ mA}$$



$$V_{R_C} = I_C \times R_C$$

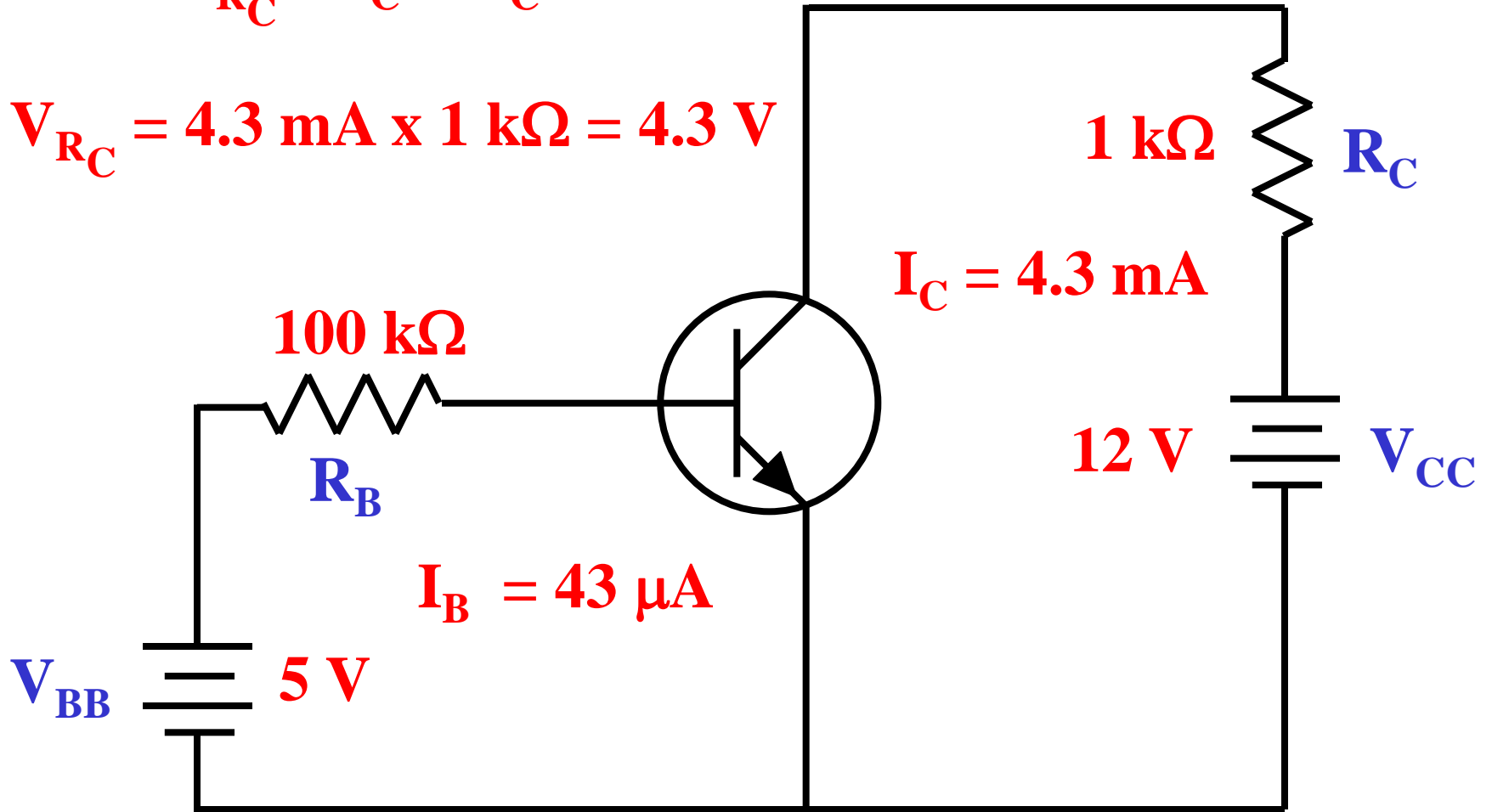
$$V_{R_C} = 4.3 \text{ mA} \times 1 \text{ k}\Omega = 4.3 \text{ V}$$



$$V_{CE} = V_{CC} - V_{R_C}$$

$$V_{CE} = 12\text{ V} - 4.3\text{ V} = 7.7\text{ V}$$

$$I_C = 4.3\text{ mA}$$

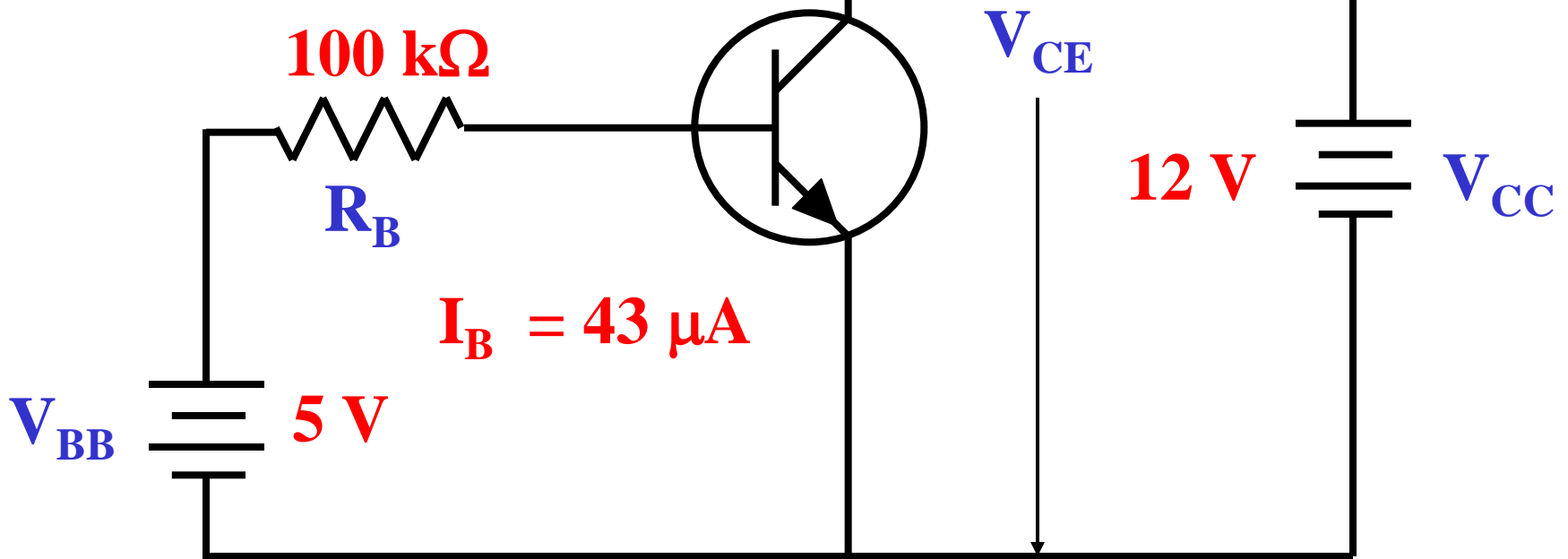

Reading transistor data sheets


- Maximum ratings on voltage, current, and power
- Power transistors dissipate more than **1 watt**
- Temperature can change the value of a transistor's characteristics

Typical Breakdown Ratings

- $V_{CBO} = 60 \text{ V}$
- $V_{CEO} = 40 \text{ V}$
- $V_{EBO} = 6 \text{ V}$

- **Note: these are reverse breakdown ratings with one transistor leg open (e.g. V_{CBO} is voltage collector to base with emitter open)**

A graphic view of collector breakdown

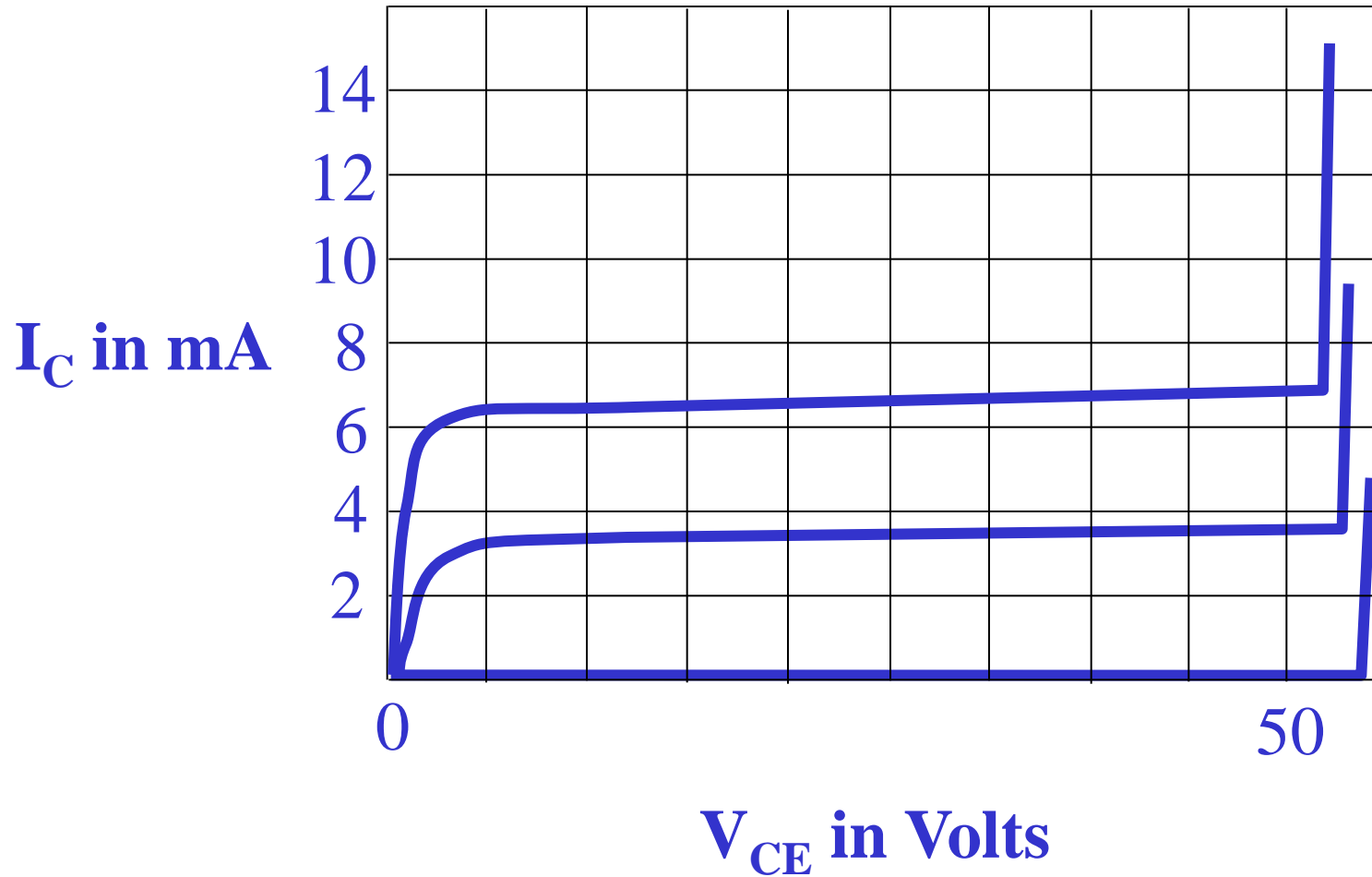

Typical Maximum Ratings

- $I_C = 200 \text{ mA dc}$
- $P_D = 250 \text{ mW}$ (for $T_A = 60 \text{ }^\circ\text{C}$)
- $P_D = 350 \text{ mW}$ (for $T_A = 25 \text{ }^\circ\text{C}$)
- $P_D = 1 \text{ W}$ (for $T_C = 60 \text{ }^\circ\text{C}$)

Data sheet h_{FE} “On Characteristics”

I_C in mA	$h_{FE(\min)}$	$h_{FE(\max)}$
0.1	40	_____
1	70	_____
10	100	300
50	60	_____
100	30	_____

Surface-mount transistors

- A variety of **package** styles (three-terminal gull-wing is typical)
- Some SMTs can dissipate **1 watt or more**
- Some SMTs house multiple transistors

Troubleshooting

- Look for **gross** voltage errors.
- First approximation and **mental estimates** will usually suffice.
- Resistors generally don't **short** but circuit boards can.
- Circuit boards can and do **open**.
- Junctions can and do **short**.
- Junctions can and do **open**.