

MALVINO & BATES

**Electronic
PRINCIPLES**

SEVENTH EDITION



Transistor Biasing



Topics Covered in Chapter 8


- **Voltage-divider bias**
- **Accurate VDB analysis**
- **VDB load line and Q point**
- **Two-supply emitter bias**
- **Other types of bias**
- **Troubleshooting**
- **PNP transistors**

Voltage divider bias

- Base circuit contains a **voltage divider**
- Most widely used
- Known as **VDB**

Voltage divider bias circuit


R_1 and R_2 form
a voltage divider

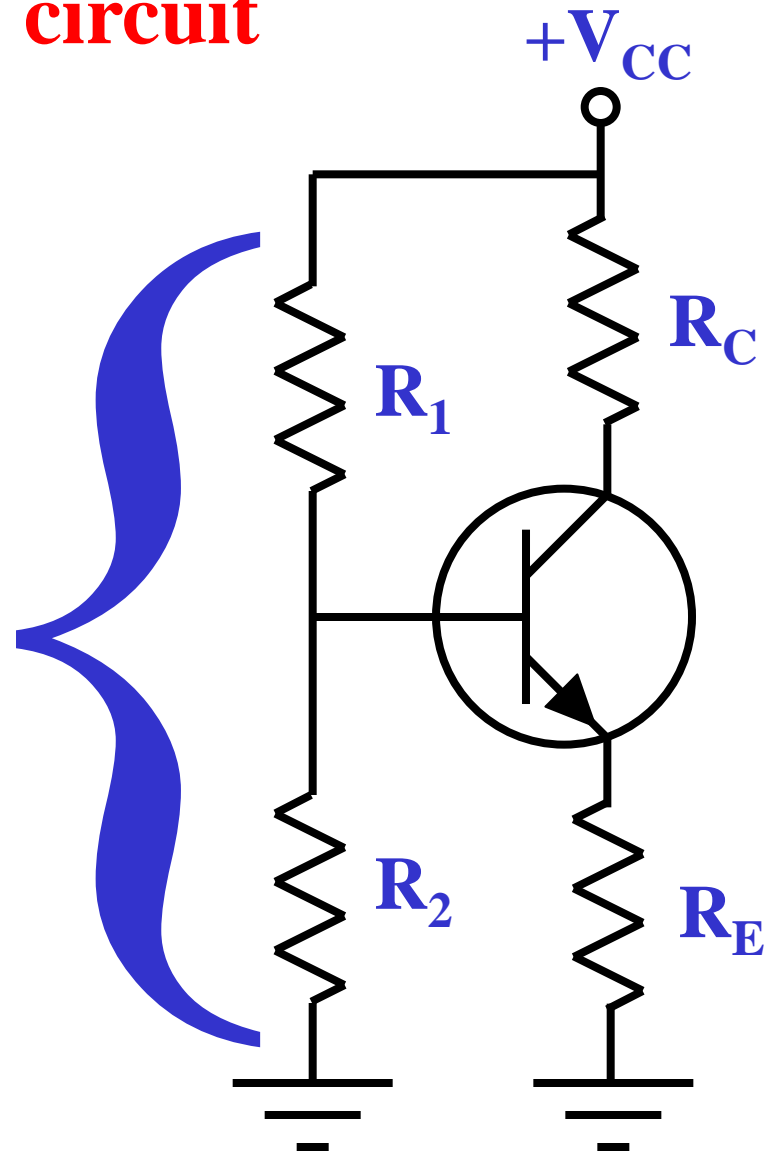

Divider analysis:

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC}$$

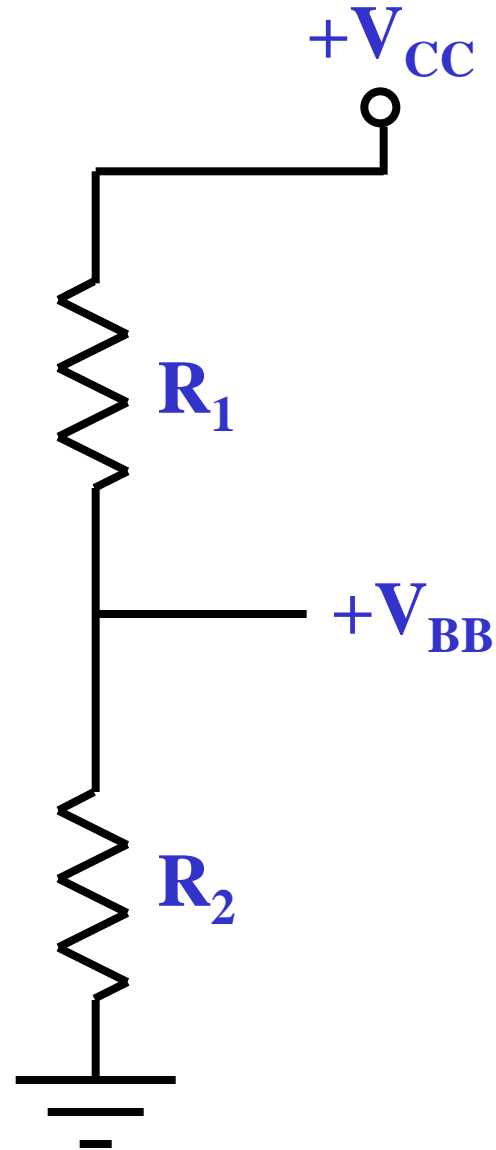ASSUMPTION: The base current is normally much smaller than the divider current.



Now the circuit can be viewed this way:


To complete the analysis:

$$I_E = \frac{V_{BB} - V_{BE}}{R_E}$$

$$I_C @ I_E$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

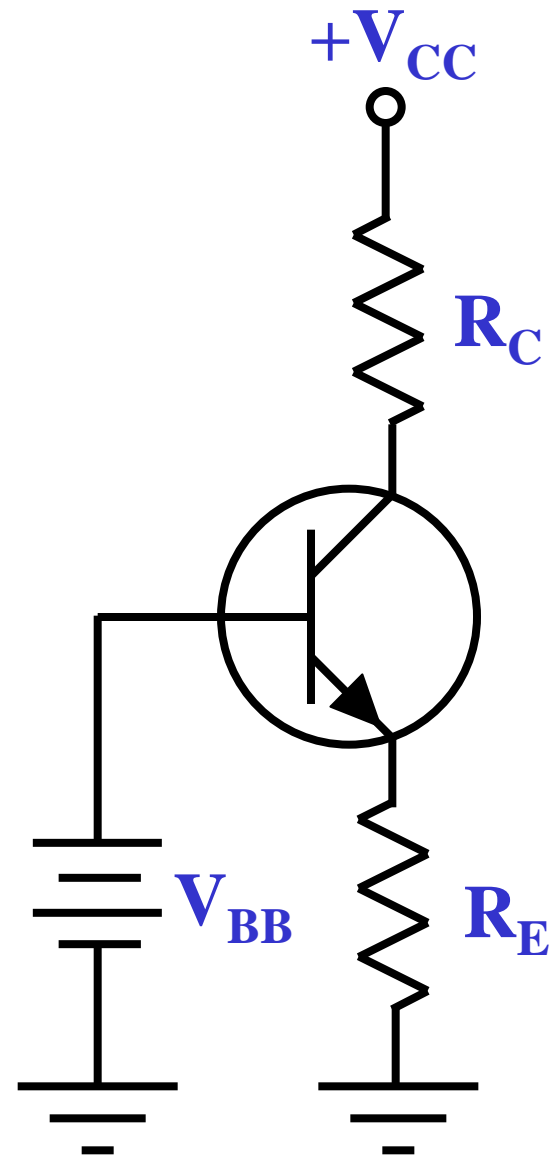

The six-step process

1. Calculate the base voltage using the voltage divider equation.
2. Subtract 0.7 V to get the emitter voltage.
3. Divide by emitter resistance to get the emitter current.
4. Determine the drop across the collector resistor.

The six-step process (Continued)

5. Calculate the collector voltage by subtracting the voltage across the collector resistor from V_{CC} .
6. Calculate the collector-emitter voltage by subtracting the emitter voltage from the collector voltage.


VDB analysis

- The **base** current must be much smaller than current through the divider
- With the base voltage constant, the circuit produces a **stable Q point** under varying operational conditions


Is the divider a stiff source?

Find the Thevenin
resistance.


$$R_{TH} = R_1 || R_2$$

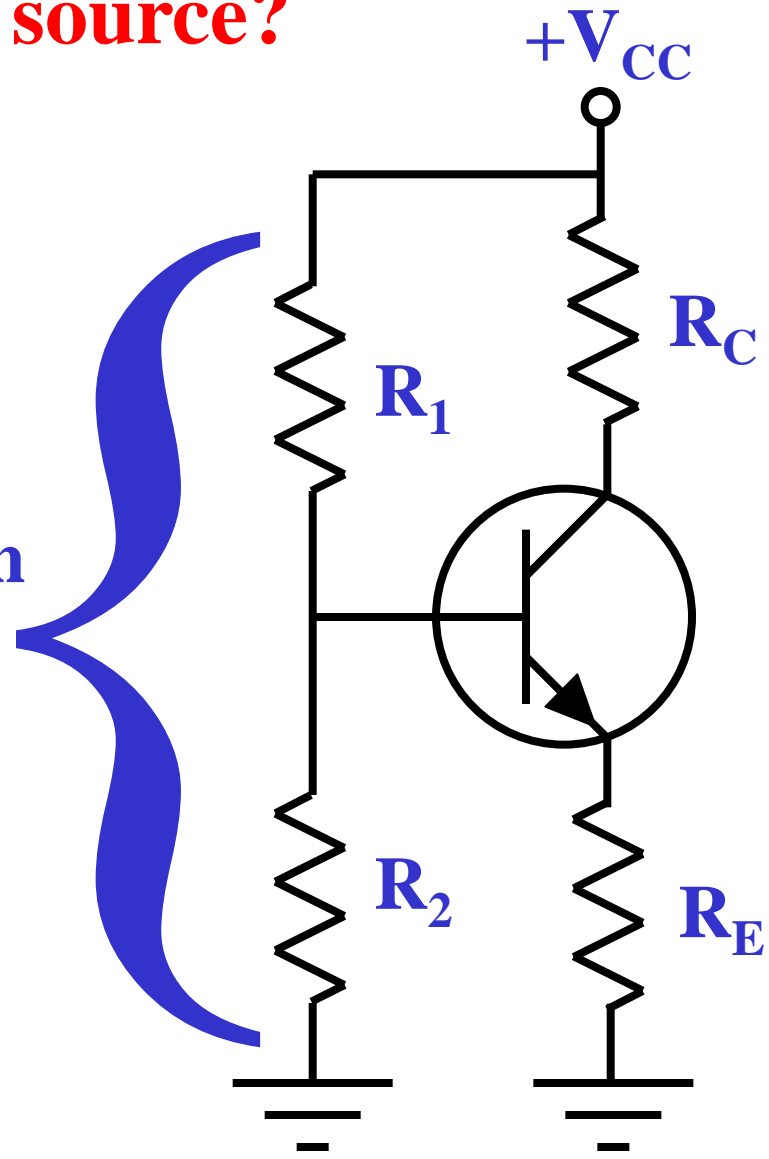

A Thevenin model of the bias circuit:

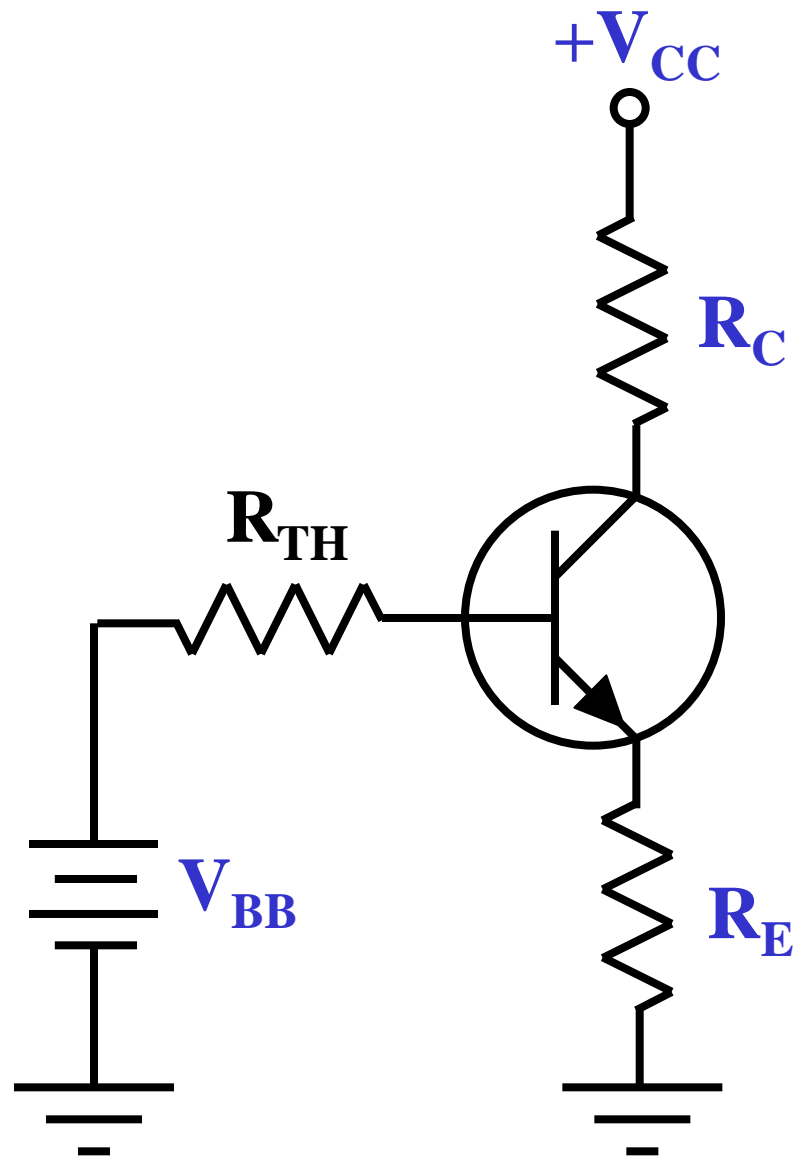

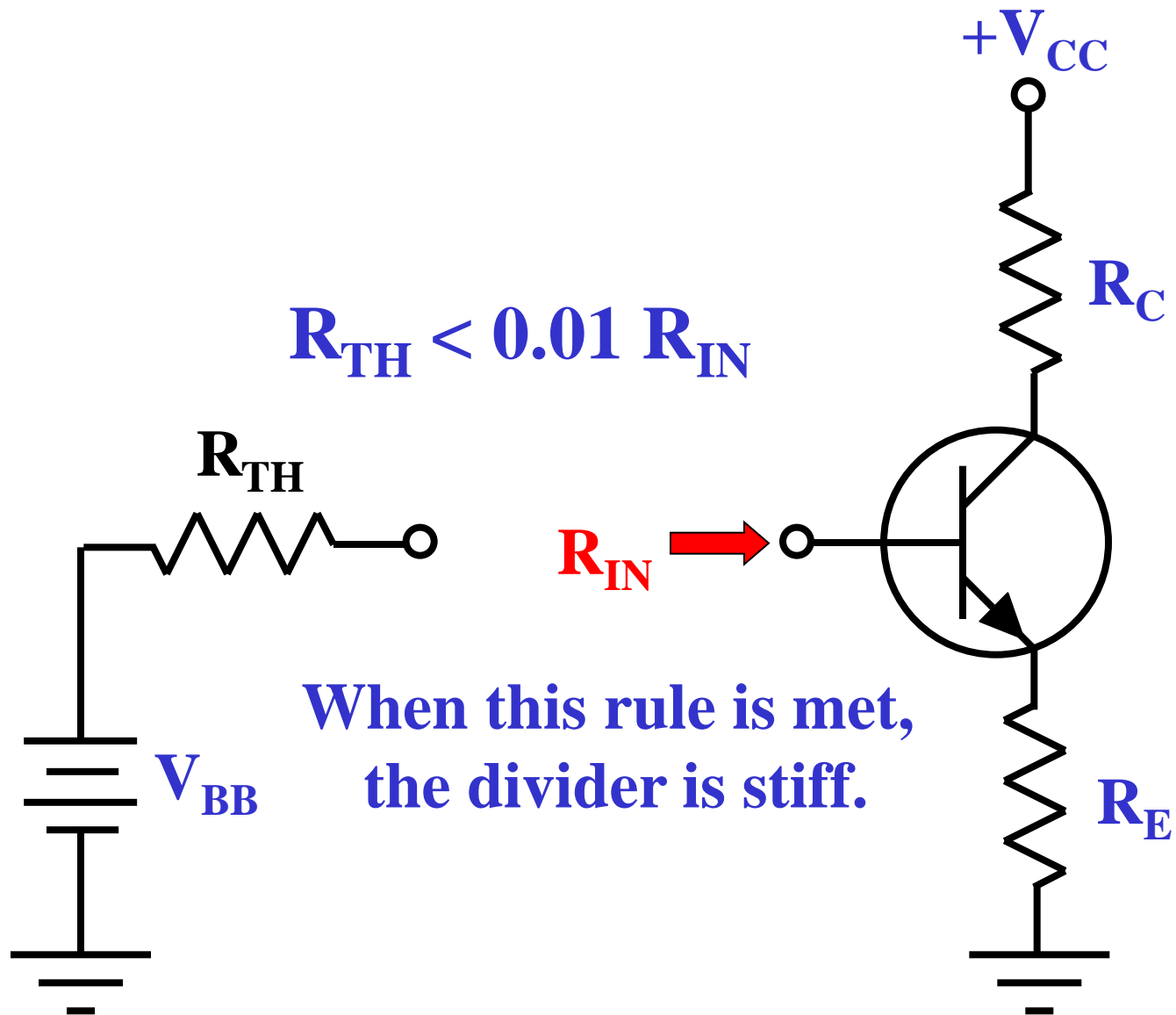The 100:1 rule applied to the bias circuit:



Firm voltage divider


- Used because divider resistors (e.g. R_1 and R_2) in a stiff design would be too small
- The collector current will be about **10%** lower than the stiff value

Sometimes a firm divider is chosen. $+V_{CC}$

$$R_1 \parallel R_2 < 0.1 b_{dc} R_E$$

A closer approximation:
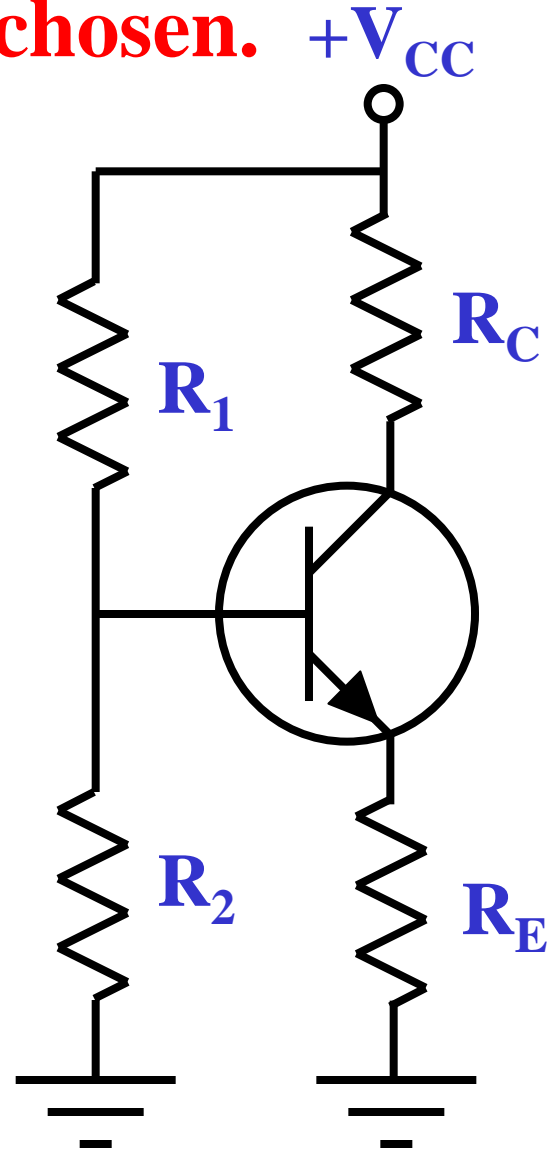
$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_1 \parallel R_2}{b_{dc}}}$$



VDB load line and Q point


- VDB is derived from **emitter bias**
- The Q point is immune to changes in current gain
- The Q point is moved by varying the emitter resistor

Two-supply stiff emitter bias:

$$I_E = \frac{V_{EE} - 0.7 \text{ V}}{R_E}$$

Assume 0 V →

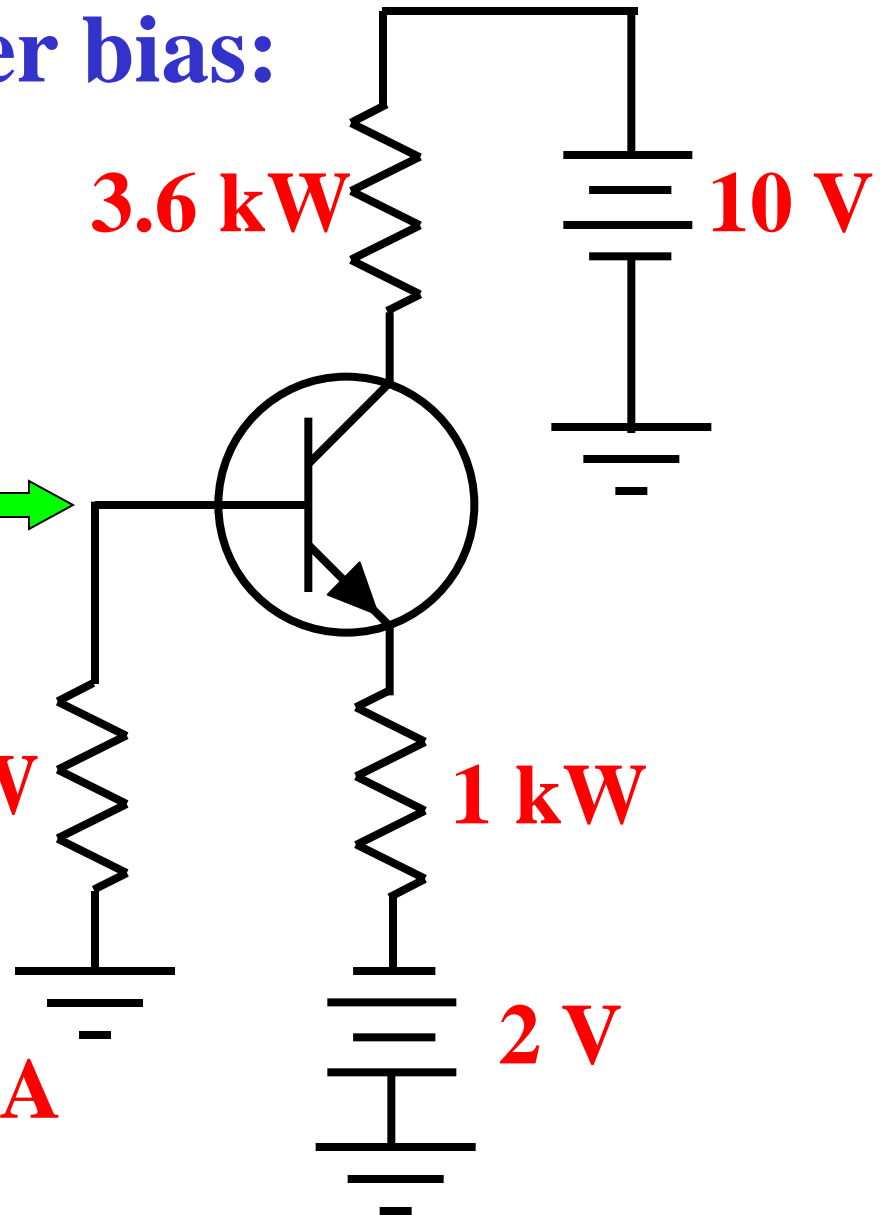
$$I_E = \frac{2 \text{ V} - 0.7 \text{ V}}{1 \text{ kW}} = 1.3 \text{ mA}$$



Find the voltages:


$$V_C = 10 \text{ V} - (1.3 \text{ mA})(3.6 \text{ kW}) = 5.32 \text{ V}$$
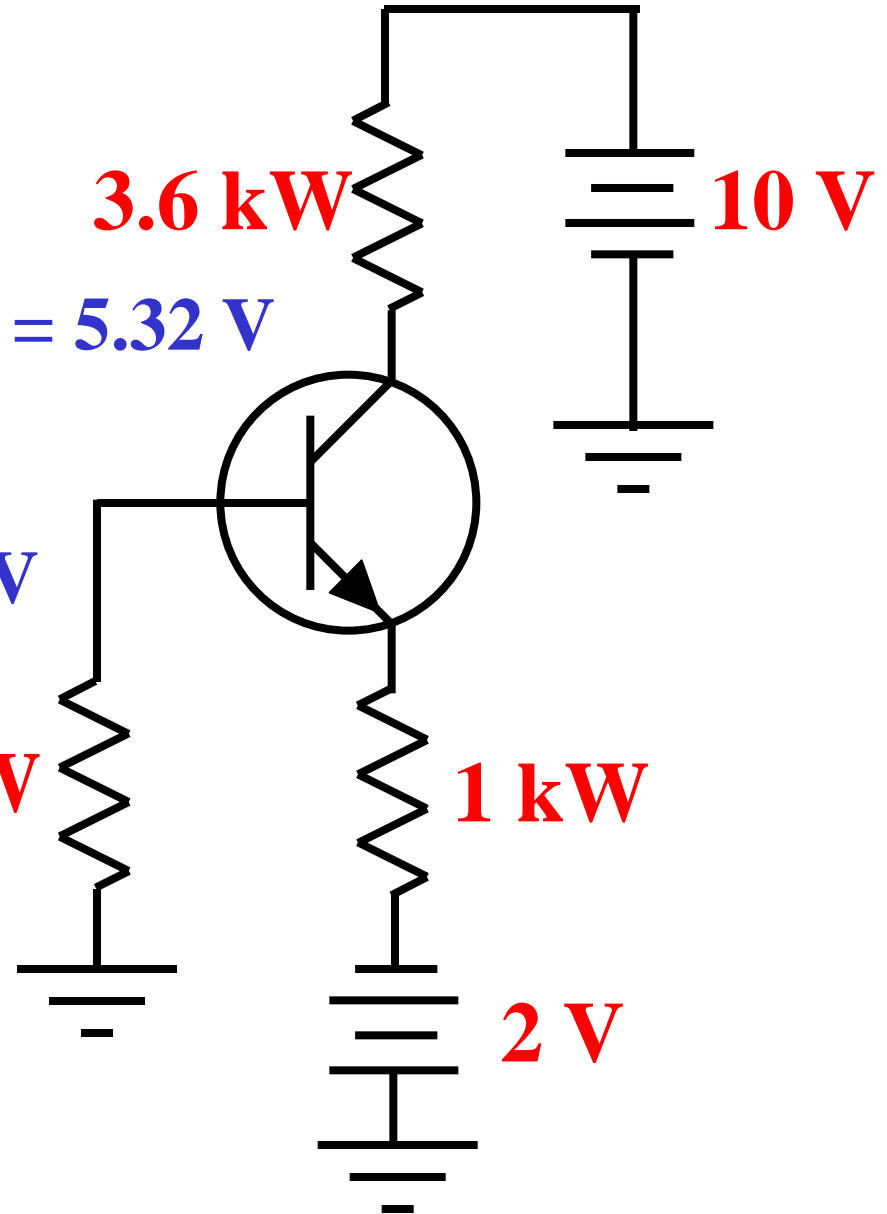
$$V_{CE} = 5.32 \text{ V} - (-0.7 \text{ V}) = 6.02 \text{ V}$$




Base bias:

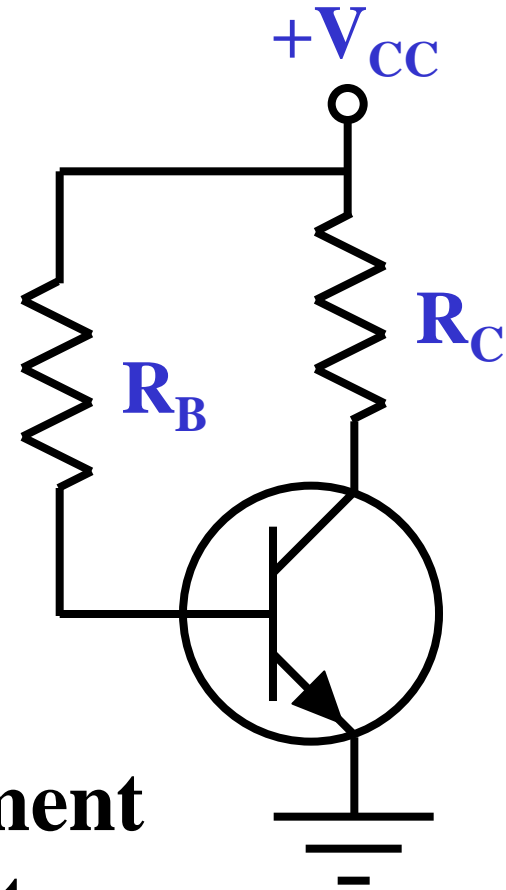- The least predictable
- Q point moves with replacement
- Q point moves with temperature
- Not practical




Emitter-feedback bias:

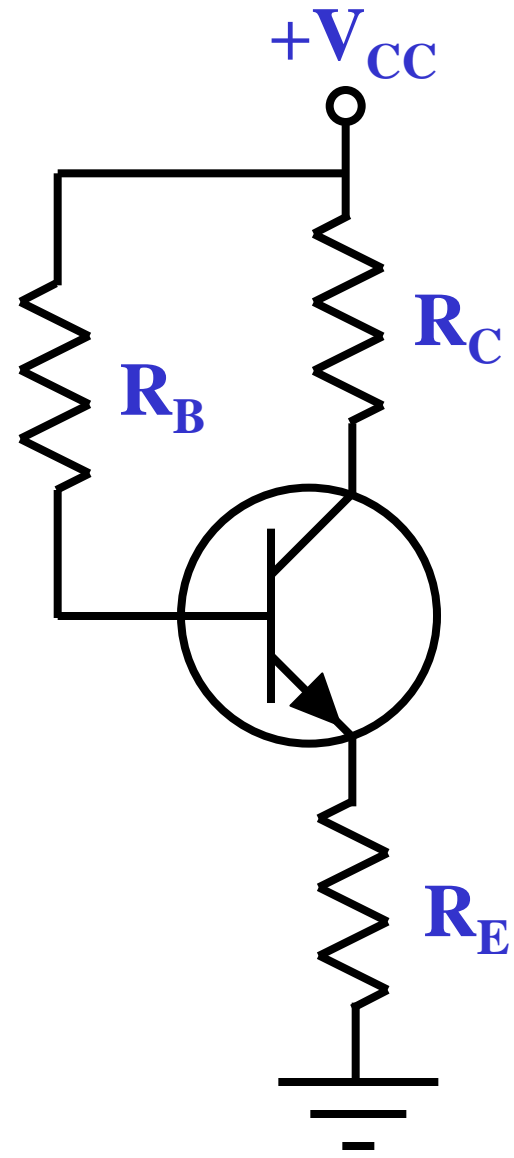- Better than base bias
- Q point still moves
- Not popular




Collector-feedback bias:

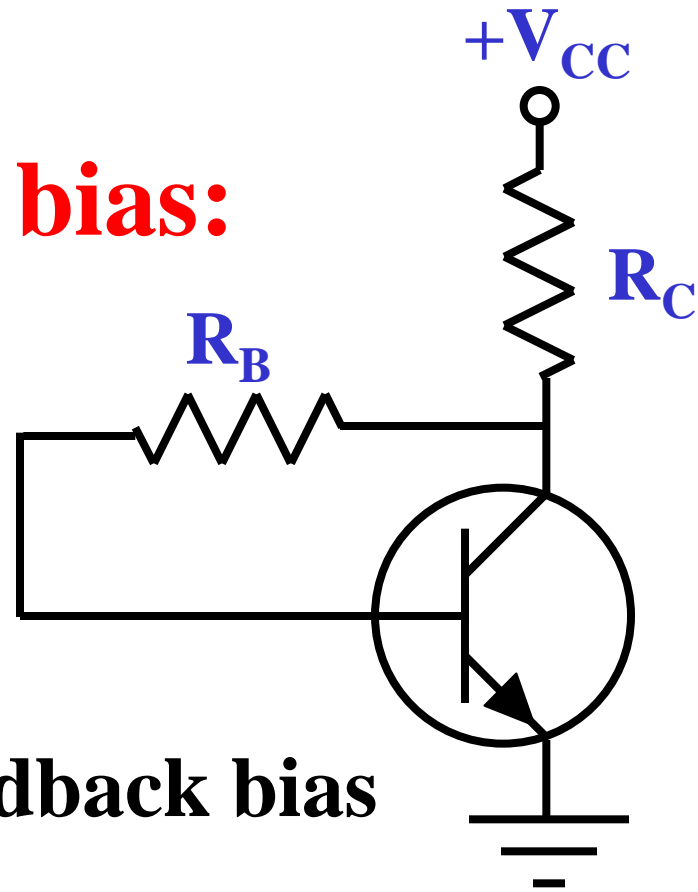

- Better than emitter-feedback bias
- Q point still moves
- Some applications because of circuit simplicity

Collector- and emitter -feedback bias:

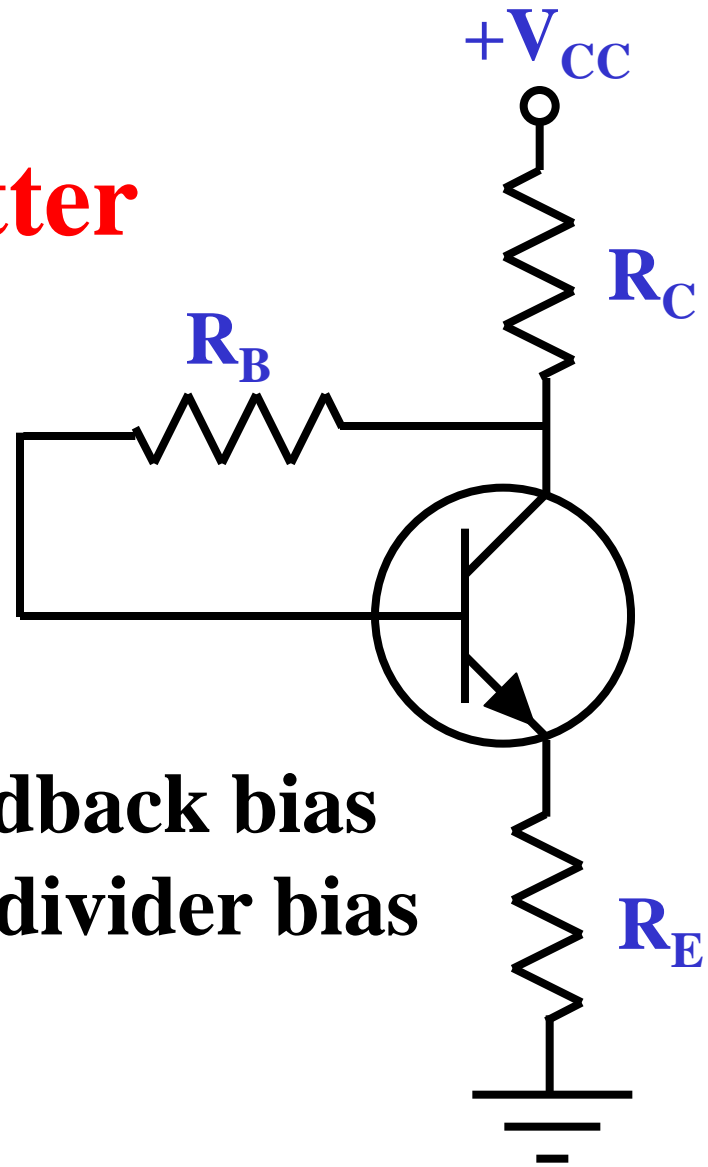


- Better than emitter-feedback bias
- Not as good as voltage-divider bias
- Limited application

Two-supply emitter bias:

- **Very stable**
- **Requires 2 supplies**


Note: Also called TSEB

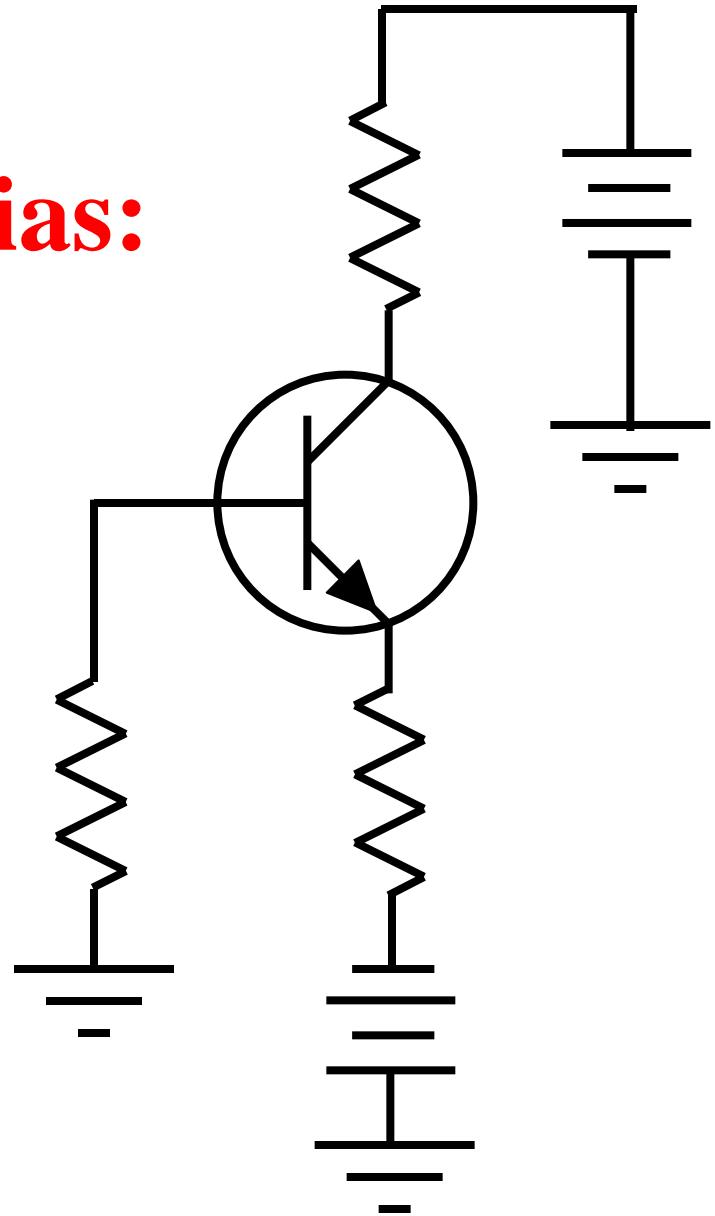

Voltage divider bias:

- **Very stable**
- **Requires 1 supply**
- **The most popular**

Note: Also called VDB

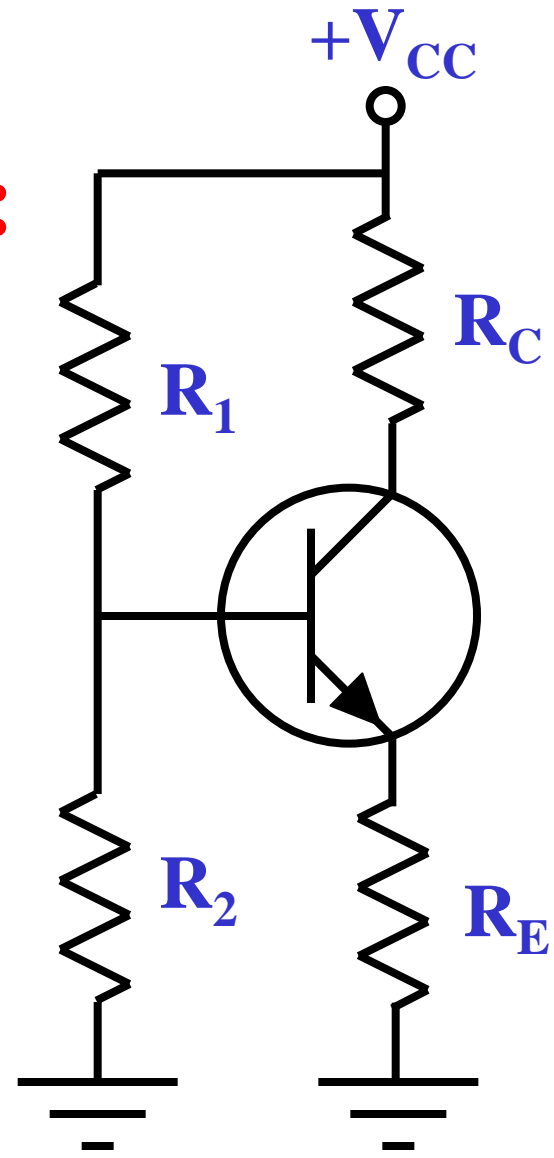


Troubleshooting

- **Voltage measurements**
- **Use 10 M Ω input voltmeter**
- **Troubles include:**
 - ü **Opens**
 - ü **Shorts**
 - ü **Faulty transistors**


PNP transistor

- The base is **n-type** material
- The collector and emitter are **p-type** material
- The emitter arrow points in
- Can be used with a negative power supply

PNP transistor symbol and current flow

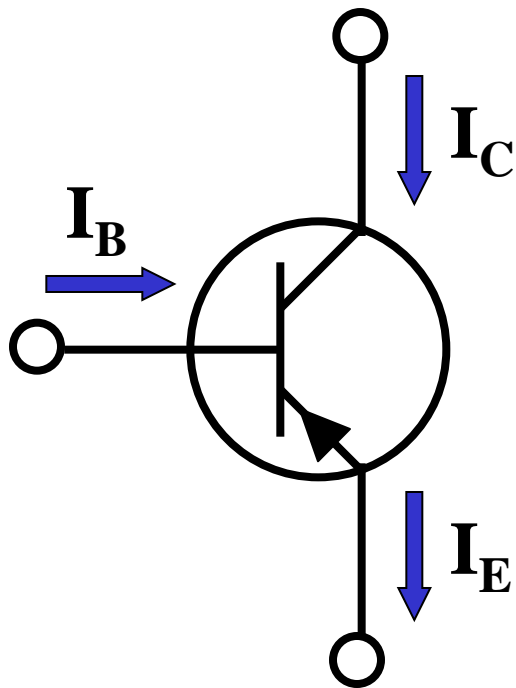


Electron flow

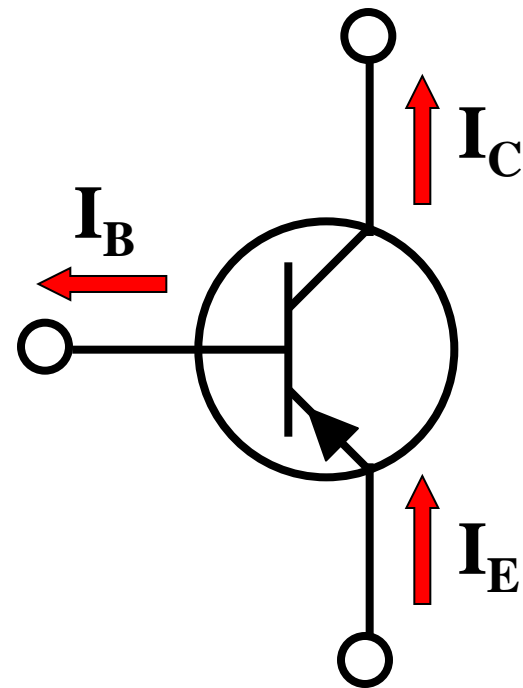

Conventional flow

PNP Biasing with a negative supply

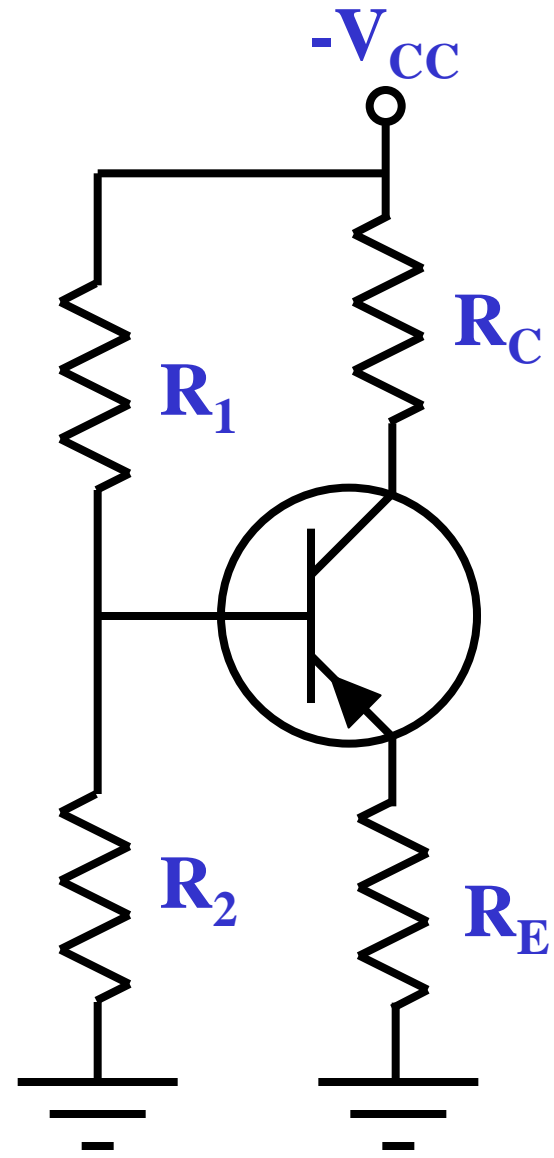

PNP Biasing with a positive supply

