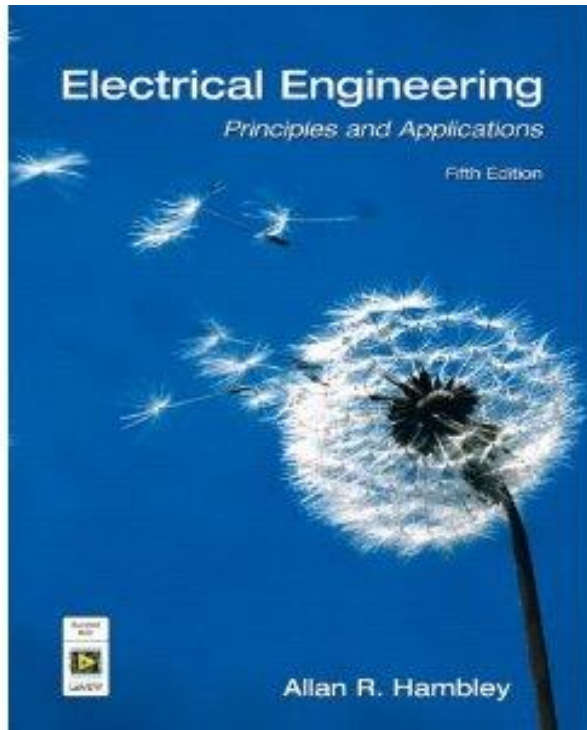


Operational Amplifiers



1. *Ideal op-amps*
2. *Negative feedback*
3. *Applications*
4. *Useful designs*
5. *Integrators, differentiators and filters*

Chapter 14: Operational Amplifiers

Introduction: Ideal Operational Amplifier

Operational amplifier (Op-amp) is made of many transistors, diodes, resistors and capacitors in integrated circuit technology.

Ideal op-amp is characterized by:

- Infinite input impedance
- Infinite gain for differential input
- Zero output impedance
- Infinite frequency bandwidth

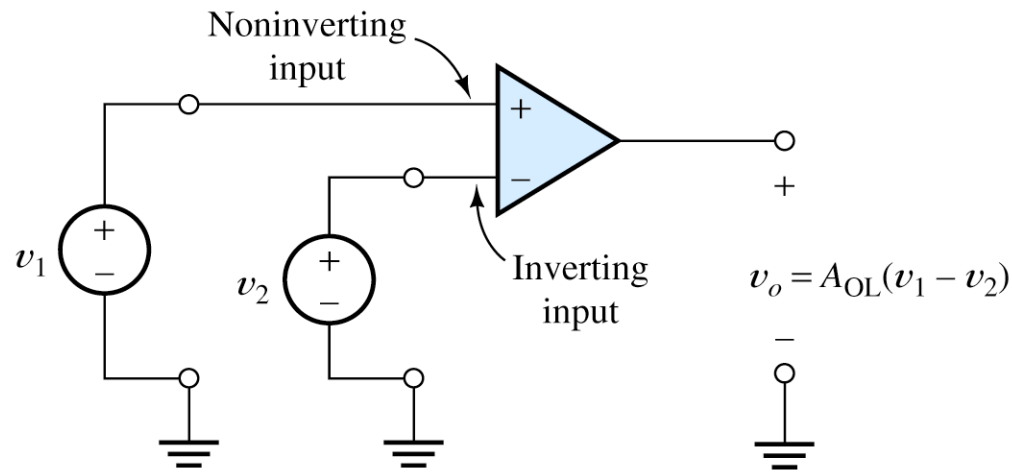


Figure 14.1 Circuit symbol for the op amp.

Ideal Operational Amplifier

Equivalent circuit of the ideal op-amp can be modeled by:

- Voltage controlled source with very large gain A_{OL} known as open loop gain
- Feedback reduces the gain of op-amp
- Ideal op-amp has no nonlinear distortions

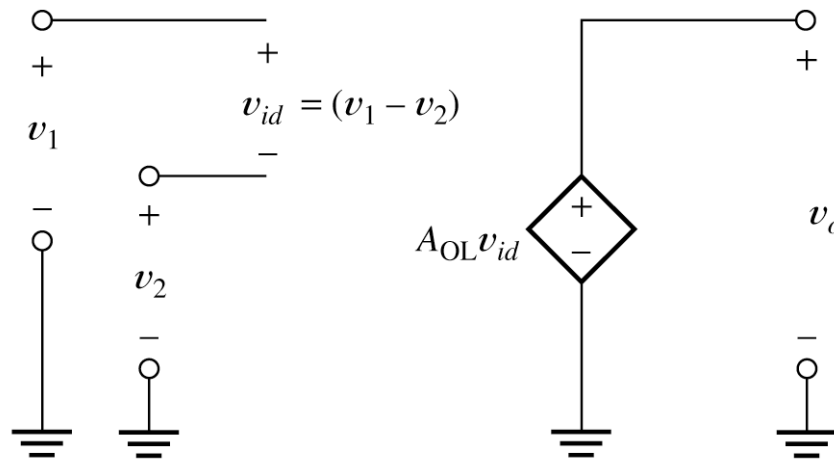


Figure 14.2 Equivalent circuit for the ideal op amp. The open-loop gain A_{OL} is very large (approaching infinity).

Ideal Operational Amplifier

A real op-amp must have a DC supply voltage which is often not shown on the schematics

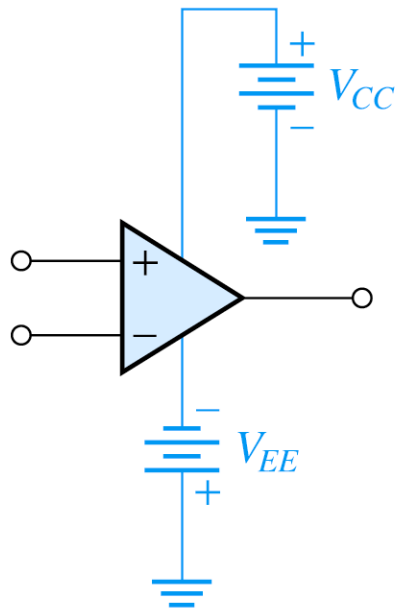


Figure 14.3 Op-amp symbol showing the dc power supplies, V_{CC} and V_{EE} .

Inverting Amplifier

Op-amp are almost always used with a negative feedback:

- Part of the output signal is returned to the input with negative sign
- Feedback reduces the gain of op-amp
- Since op-amp has large gain even small input produces large output, thus for the limited output voltage (lest than V_{CC}) the input voltage v_x must be very small.
- Practically we set v_x to zero when analyzing the op-amp circuits.

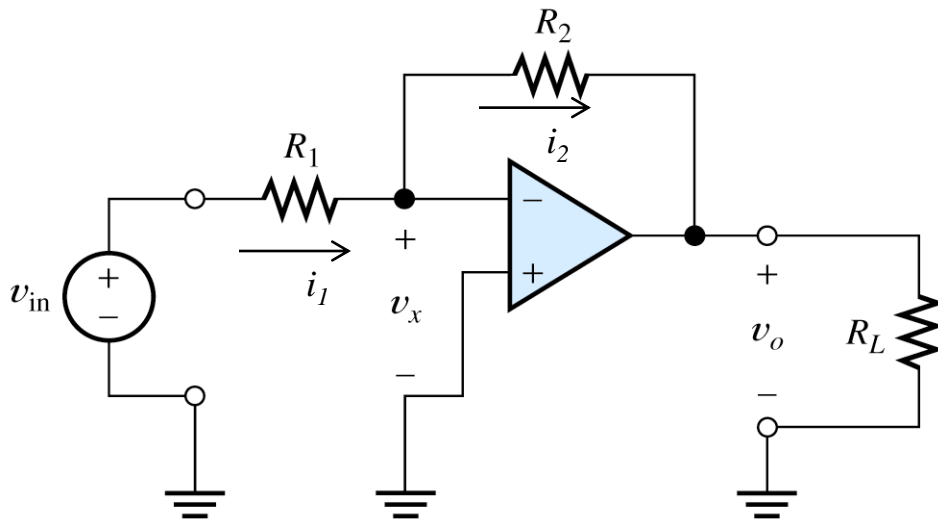


Figure 14.4 The inverting amplifier.

$$\text{with } v_x = 0 \quad i_1 = v_{in} / R_1$$

$$i_2 = i_1 \quad \text{and}$$

$$v_o = -i_2 R_2 = -v_{in} R_2 / R_1$$

SO

$$A_v = v_o / v_{in} = -R_2 / R_1$$

Inverting Amplifier

Since $v_o = -i_2 R_2 = -v_{in} R_2 / R_1$

Then we see that the output voltage does not depend on the load resistance and behaves as voltage source.

Thus the output impedance of the inverting amplifier is zero.

The input impedance is R_1 as $Z_{in} = v_{in} / i_1 = R_1$

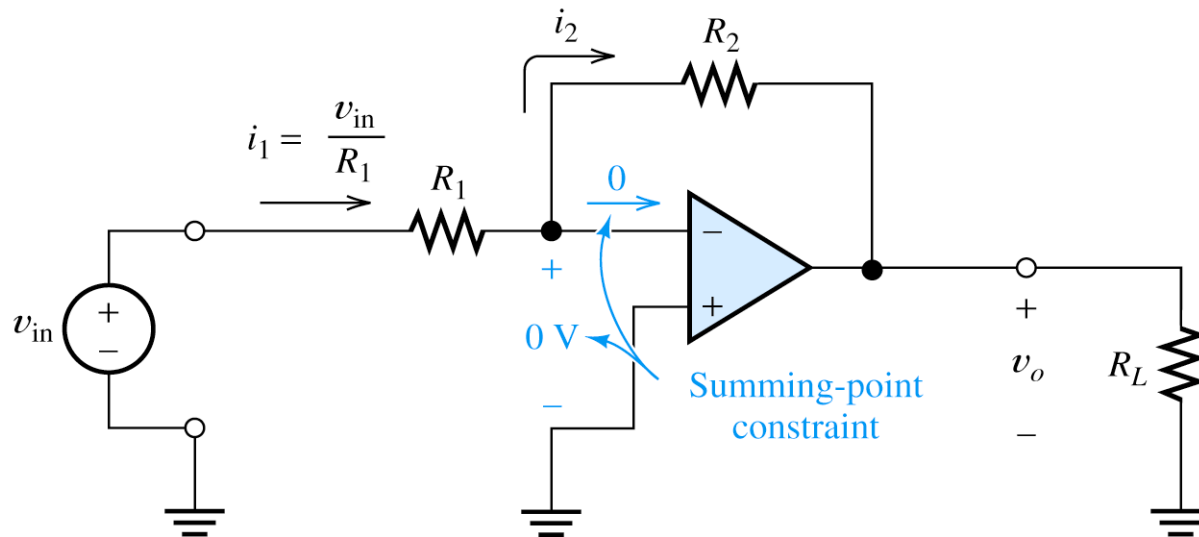


Figure 14.5 We make use of the summing-point constraint in the analysis of the inverting amplifier.

Inverting Amplifier with higher gain

Inverting amplifier gain $v_o = -i_2 R_2 = -v_{in} R_2 / R_1$

Is limited due to fact that it is hard to obtain large resistance ratio.

Higher gains can be obtained in the circuit below where we have:

$$i_1 = v_{in} / R_1 = i_2$$

from KCL at N_2 we have:

$$i_2 + i_3 = i_4$$

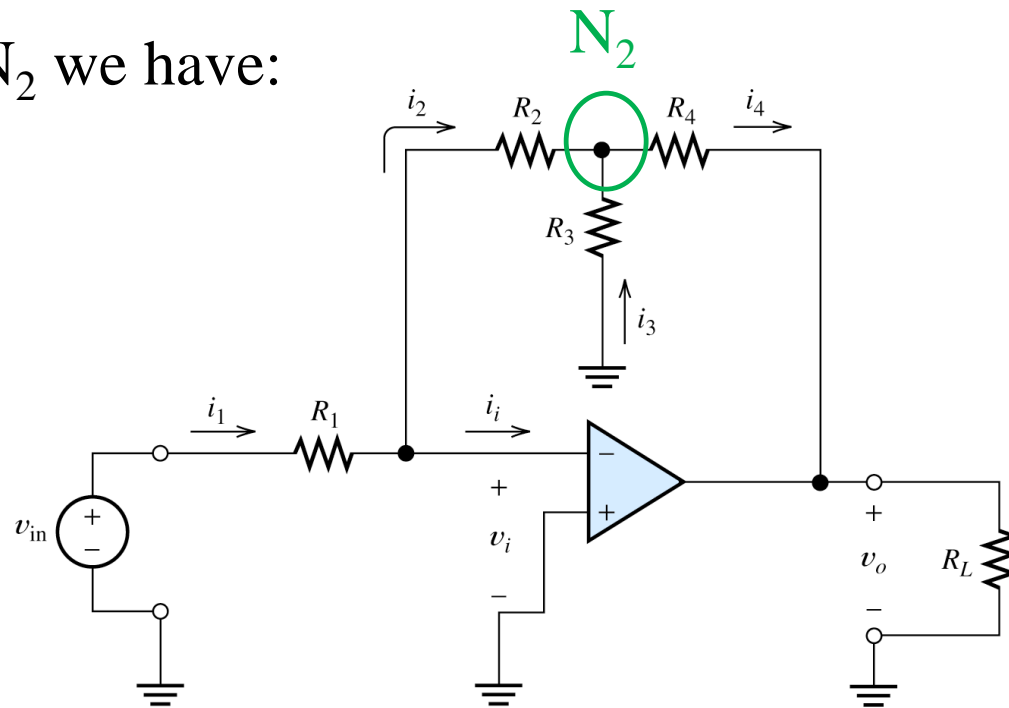


Figure 14.6 An inverting amplifier that achieves high gain magnitude with a smaller range of resistance values than required for the basic inverter. See Example 14.1.

Inverting Amplifier with higher gain

Higher gains can be obtained in the circuit below where we have:

$$i_1 = v_{in}/R_1 = i_2 \quad \text{from KCL at N2 we have: } i_2 + i_3 = i_4$$

$$\text{Also from KVL1: } -v_o = i_2 R_2 + i_4 R_4 \Rightarrow i_4 = (-v_o - i_2 R_2)/R_4$$

$$\text{and from KVL2: } i_2 R_2 = i_3 R_3 \Rightarrow i_3 = i_2 R_2 / R_3$$

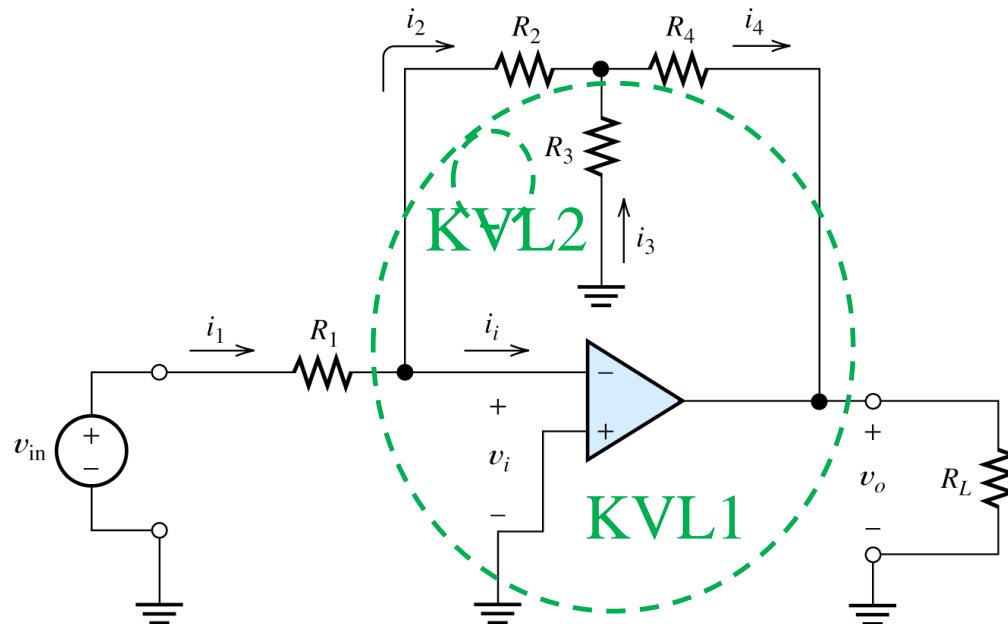


Figure 14.6 An inverting amplifier that achieves high gain magnitude with a smaller range of resistance values than required for the basic inverter.

See Example 14.1.

Inverting Amplifier with higher gain

Finally using: $i_2 + i_3 = i_4$ and

$$i_4 = (-v_o - i_2 R_2) / R_4$$

$$i_3 = i_2 R_2 / R_3$$

we have

$$i_2 + i_2 R_2 / R_3 = (-v_o - i_2 R_2) / R_4 \quad \Rightarrow \quad i_2 (1 + R_2 / R_3 + R_2 / R_4) = -v_o / R_4$$

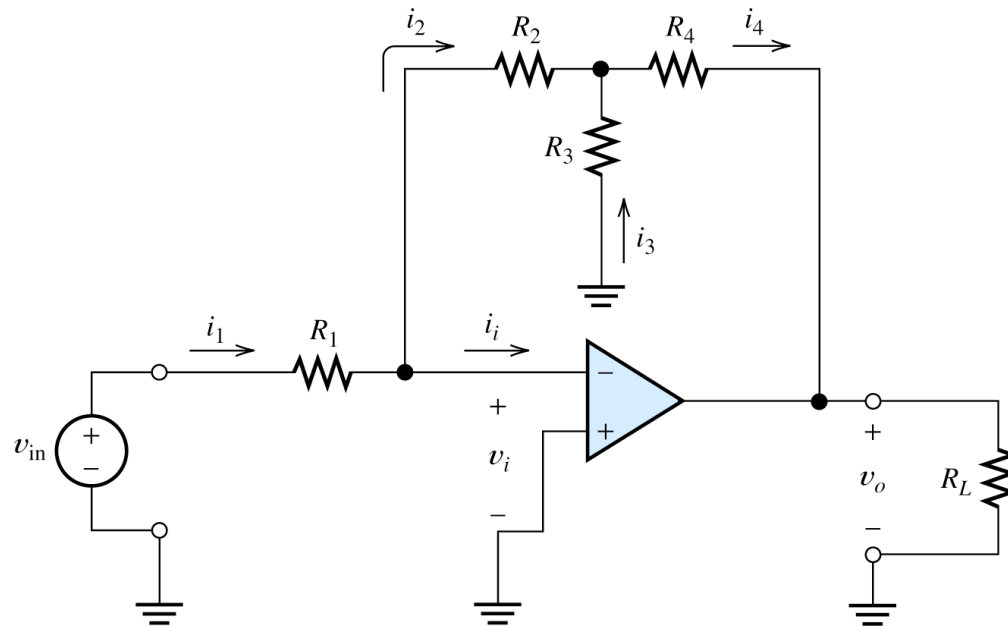


Figure 14.6 An inverting amplifier that achieves high gain magnitude with a smaller range of resistance values than required for the basic inverter.

See Example 14.1.

Inverting Amplifier with higher gain

$$i_2(1 + R_2/R_3 + R_2/R_4) = -v_o/R_4$$

Substitute

$$i_2 = v_{in}/R_1 \quad \Rightarrow \quad v_{in}/R_1 * (1 + R_2/R_3 + R_2/R_4) = -v_o/R_4$$

to get the voltage gain

$$v_o/v_{in} = -R_4/R_1 * (1 + R_2/R_3 + R_2/R_4)$$

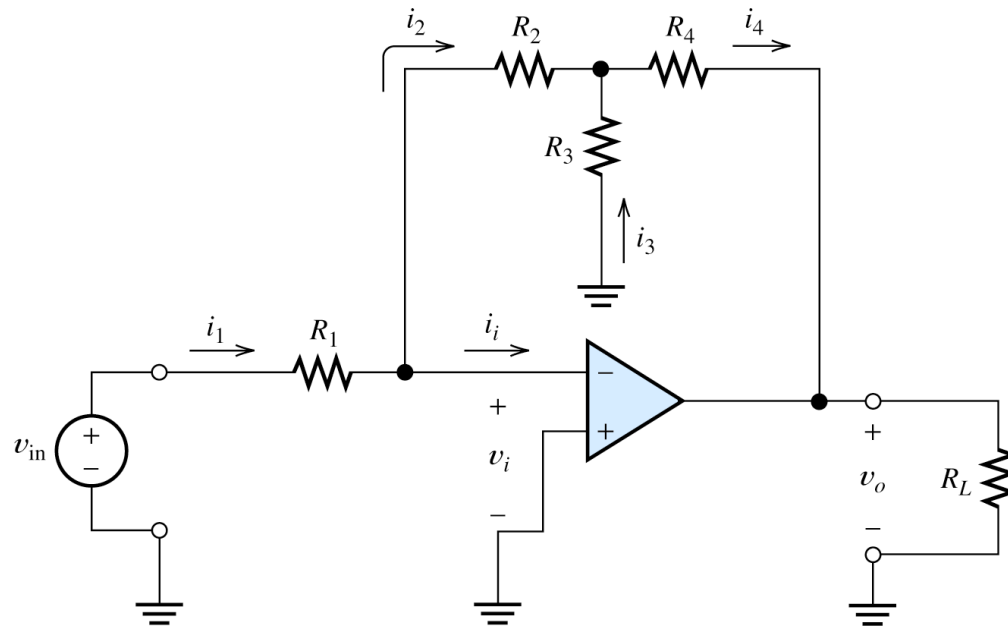


Figure 14.6 An inverting amplifier that achieves high gain magnitude with a smaller range of resistance values than required for the basic inverter.

See Example 14.1.

Inverting Amplifier with higher gain

So if we chose $R_1=R_3=1\text{k}\Omega$ and $R_2=R_4=10\text{ k}\Omega$ then the voltage gain is

$$\begin{aligned} A_v &= v_o/v_{in} = \\ &= -R_4/R_1 * (1 + R_2/R_3 + R_2/R_4) = \\ &= -10 * (1 + 10 + 1) = \\ &= -120 \end{aligned}$$

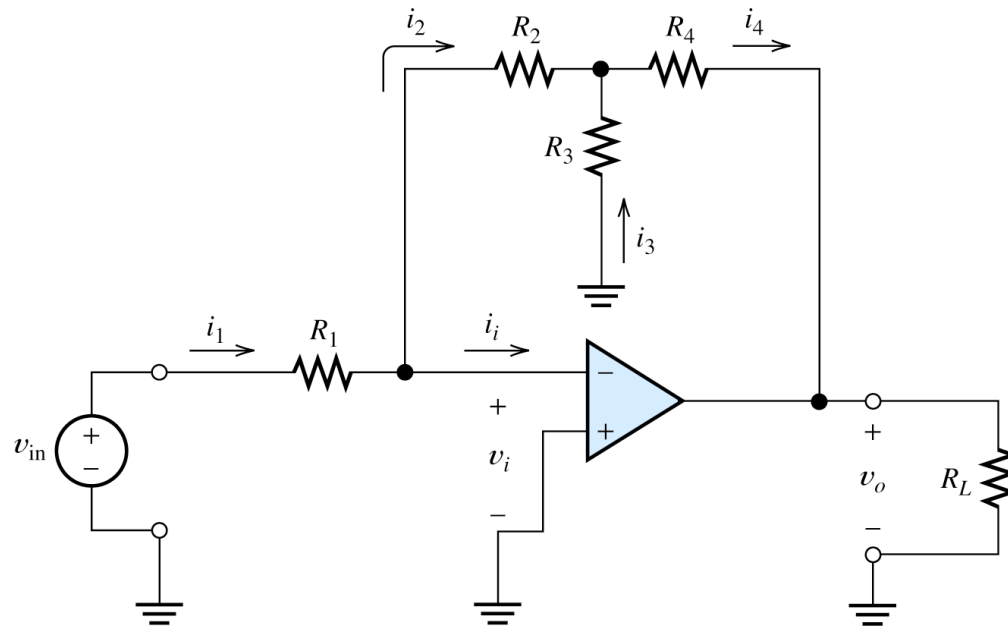


Figure 14.6 An inverting amplifier that achieves high gain magnitude with a smaller range of resistance values than required for the basic inverter.

See Example 14.1.

Summing Amplifier

The output voltage in summing amplifier is

$$v_o = -i_f * R_f \quad \text{since } v_i = 0$$

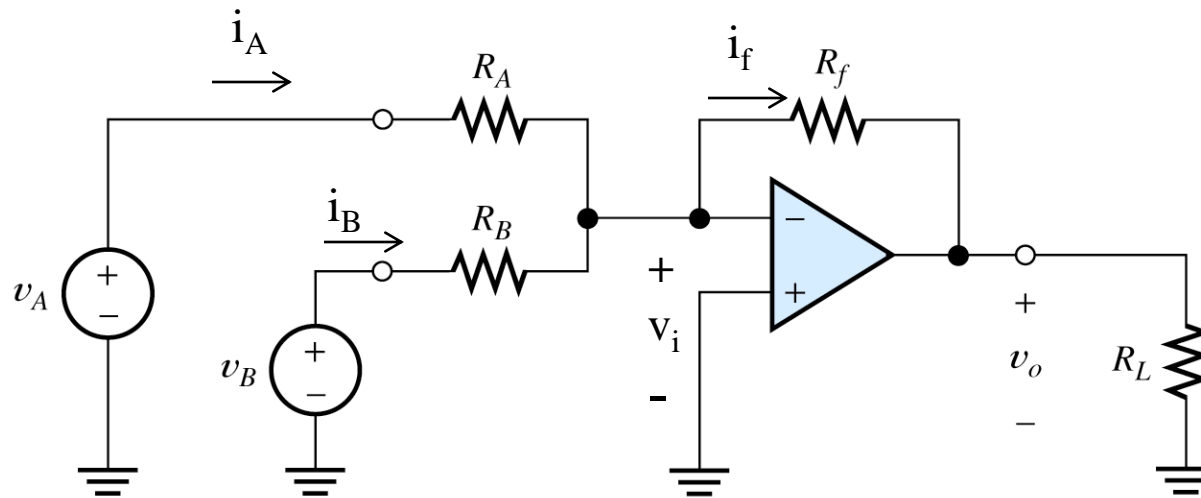


Figure 14.7 Summing amplifier. See Exercise 14.1.

Summing Amplifier

The output voltage in summing amplifier is

$$v_o = -i_f * R_f \quad \text{since } v_i = 0$$

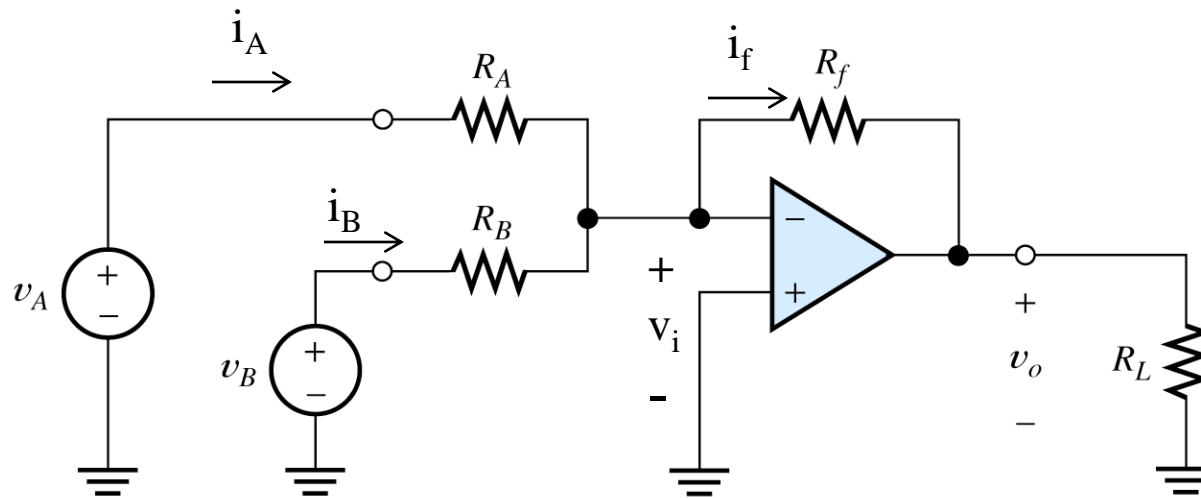


Figure 14.7 Summing amplifier. See Exercise 14.1.

Summing Amplifier

The output voltage in summing amplifier is

$$v_o = -i_f * R_f \quad \text{since } v_i = 0$$

$$i_f = i_A + i_B = v_A/R_A + v_B/R_B \quad \Rightarrow \quad v_o = -(v_A/R_A + v_B/R_B) * R_f$$

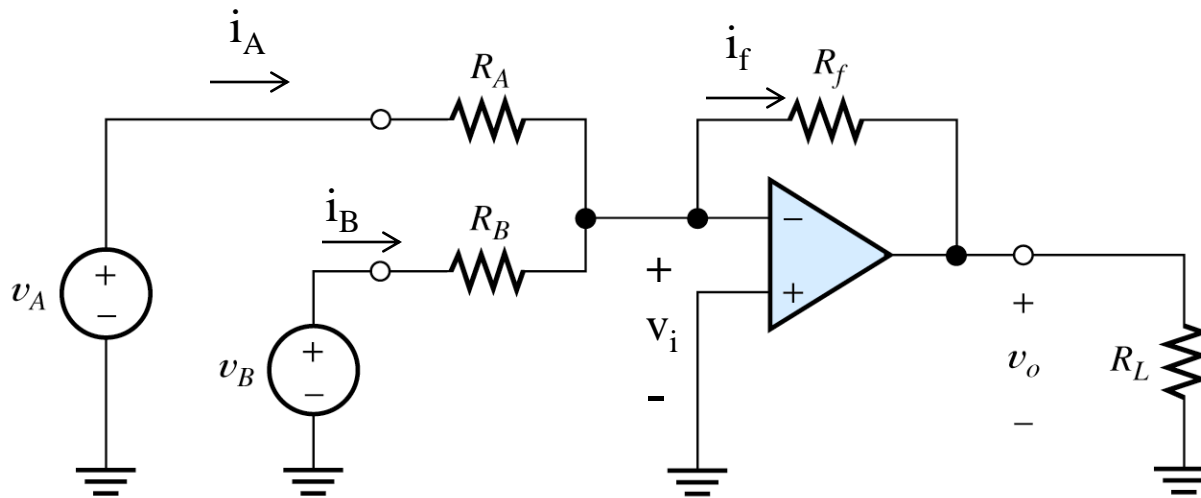


Figure 14.7 Summing amplifier. See Exercise 14.1.

Summing Amplifier

The output voltage in summing amplifier is

$$v_o = -i_f * R_f \quad \text{since } v_i = 0$$

$$i_f = i_A + i_B = v_A/R_A + v_B/R_B \quad \Rightarrow \quad v_o = -(v_A/R_A + v_B/R_B) * R_f$$

For n inputs we will have

$$v_o = - R_f * \sum_i (v_i/R_i)$$


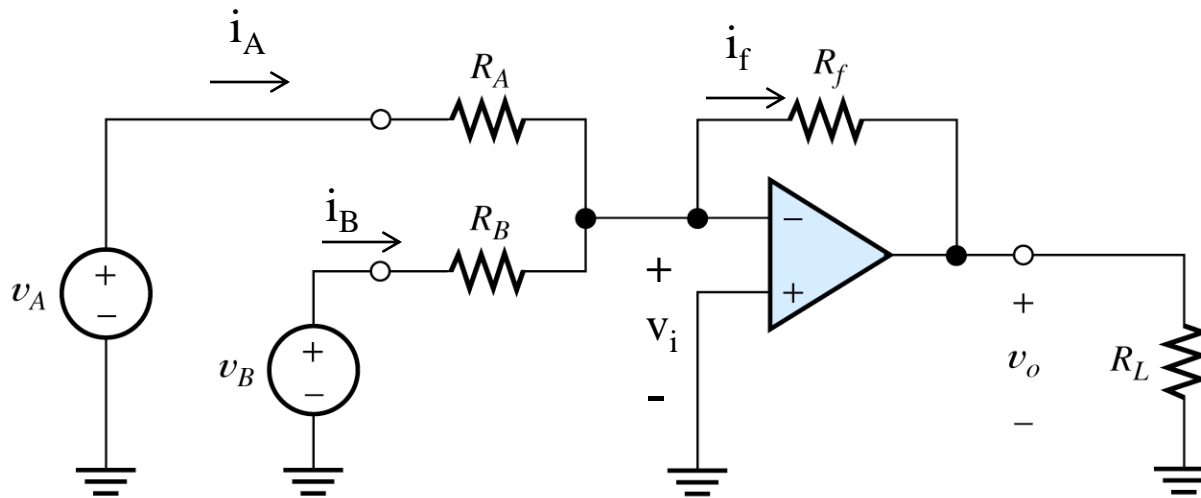


Figure 14.7 Summing amplifier. See Exercise 14.1.

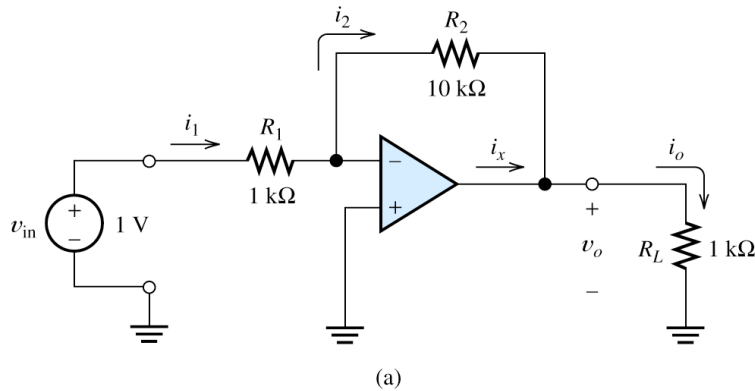Exercise 14.2

Find the currents and voltages in these two circuits:



$$a) \quad i_1 = v_{in} / R_1 = 1V / 1k\Omega = 1mA$$

$$i_2 = i_1 = 1mA$$


$$v_o = -i_2 * R_2 = -10V$$

$$i_o = v_o / R_L = -10mA$$

from KCL

from KVL

from Ohms law

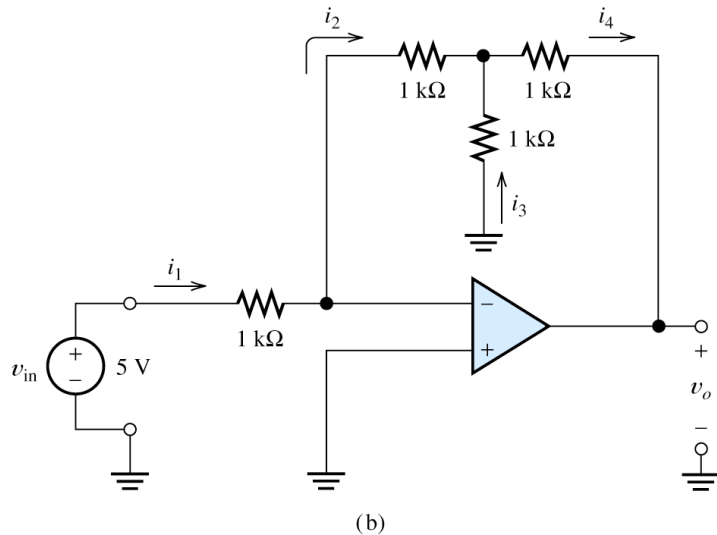


$$i_x = i_o - i_2 = -10mA - 1mA = -11mA$$

Figure 14.8 Circuits for Exercise 14.2.

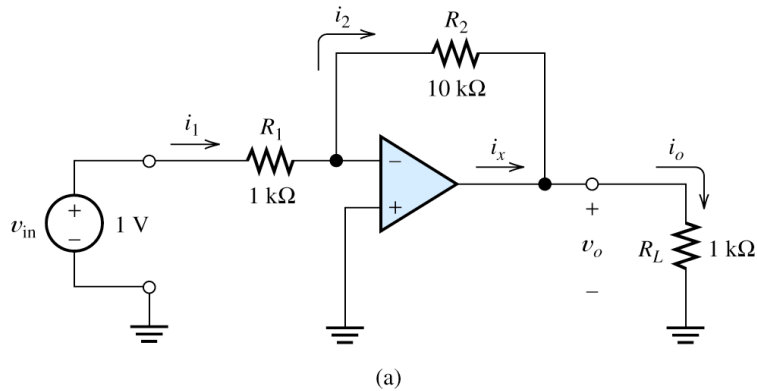Exercise 14.2

Find the currents and voltages in these two circuits:



$$b) \quad i_1 = v_{in} / R_1 = 5 \text{ mA}$$

$$i_2 = i_1 = 5 \text{ mA}$$

$$i_2 * 1 \text{ k}\Omega = i_3 * 1 \text{ k}\Omega \quad \Rightarrow \quad i_3 = 5 \text{ mA}$$

$$i_4 = i_2 + i_3 = 10 \text{ mA}$$

$$v_o = -i_2 * 1 \text{ k}\Omega - i_4 * 1 \text{ k}\Omega = -10 \text{ V}$$

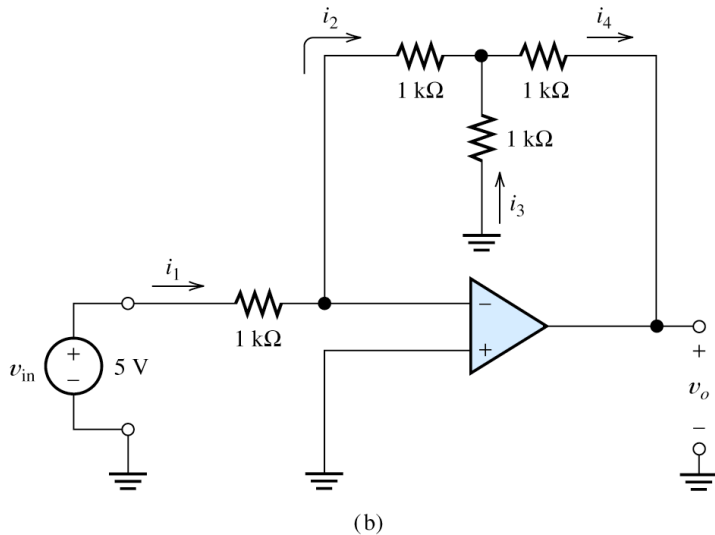


Figure 14.8 Circuits for Exercise 14.2.

Exercise 14.2

Find expression for the output voltage in the amplifier circuit:

$$i_1 = v_1 / R_1 = v_1 / 10 \text{ k}\Omega$$

$$i_2 = i_1 = v_1 / 10 \text{ mA}$$

$$v_3 = -i_2 * R_2 = -v_1 / 10 \text{ k}\Omega * 20 \text{ k}\Omega = -2v_1$$

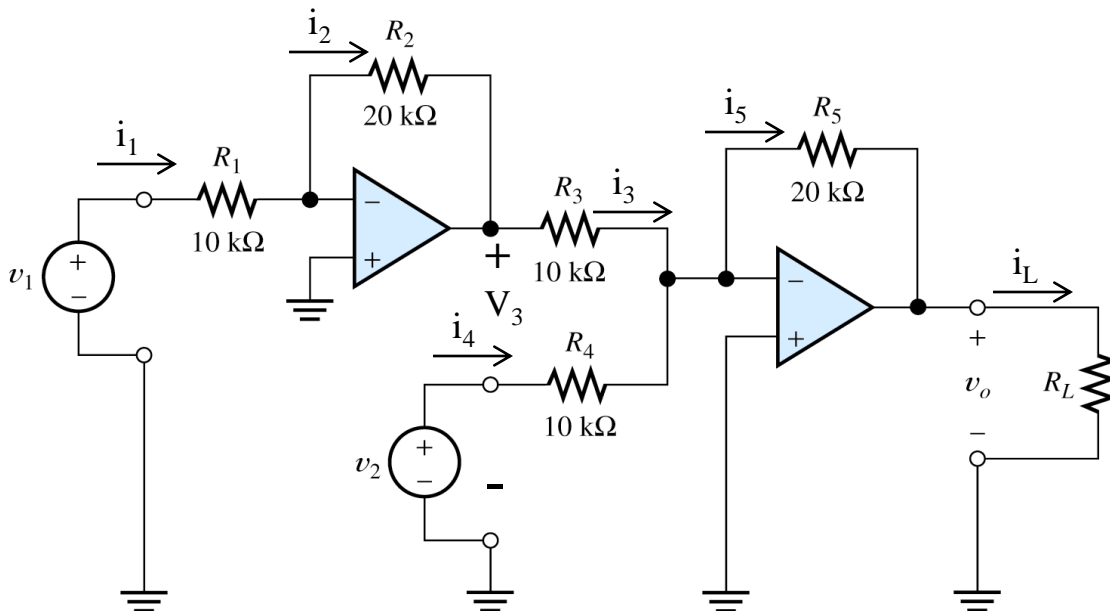


Figure 14.9 Circuit for Exercise 14.3.

Exercise 14.2

Find expression for the output voltage in the amplifier circuit:

$$v_3 = -i_2 * R_2 = -v_1 / 10k\Omega * 20k\Omega = -2v_1$$

$$i_5 = i_3 + i_4 = v_3 / 10k\Omega + v_2 / 10k\Omega$$

$$v_o = -i_5 * R_5 = -(v_3 / 10k\Omega + v_2 / 10k\Omega) * 20k\Omega = -2v_3 - 2v_2 = 4v_1 - 2v_2$$

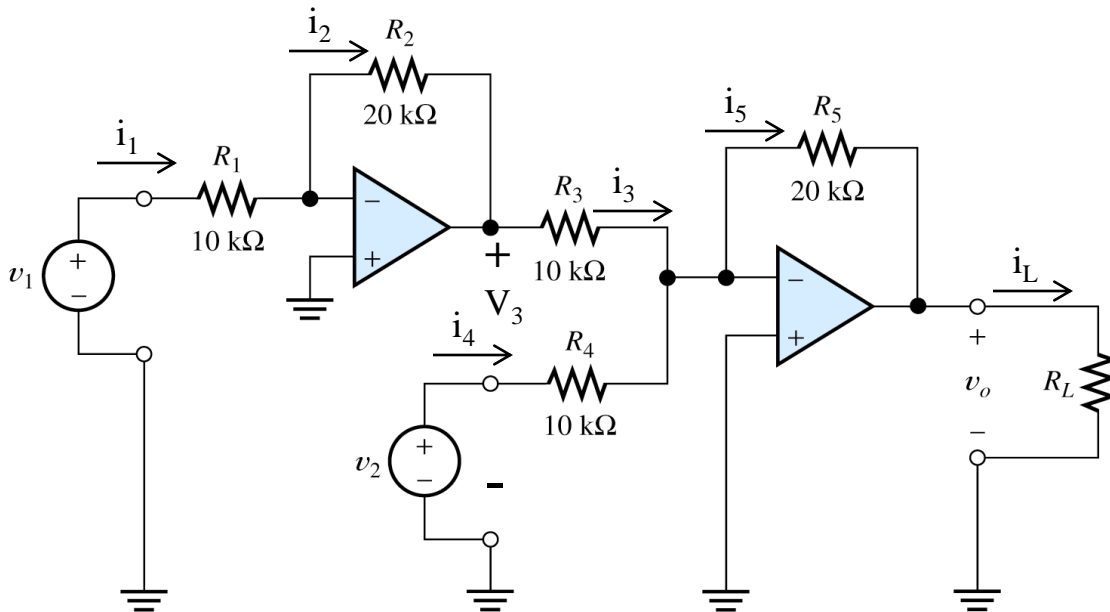


Figure 14.9 Circuit for Exercise 14.3.

Positive Feedback

When we flip the polarization of the op-amp as shown on the figure we will get a positive feedback that saturates the amplifier output.

This is not a good idea.

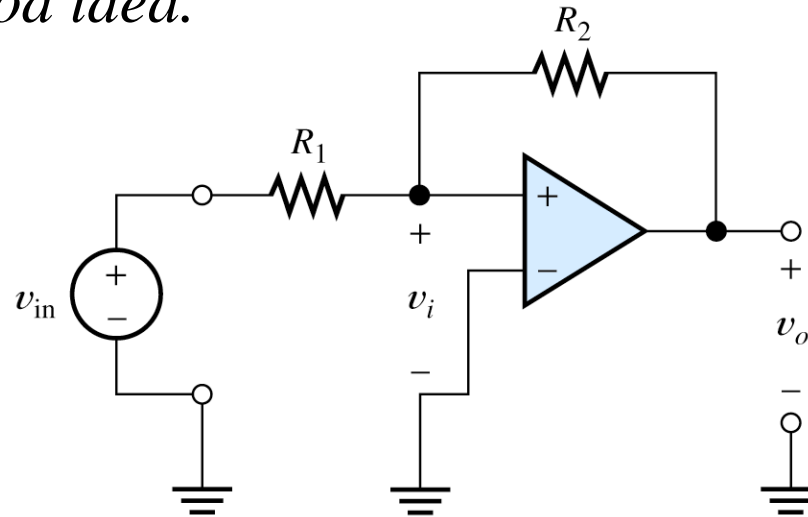


Figure 14.10 Circuit with positive feedback.

Noninverting amplifier

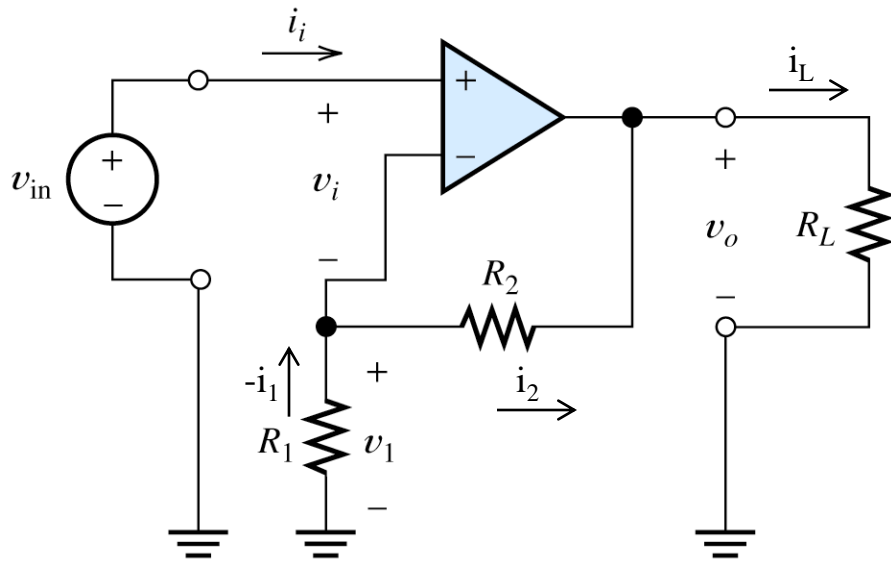


Figure 14.11 Noninverting amplifier.

$$v_1 = v_{in}$$

$$i_1 = v_1 / R_1$$

$$i_2 = -i_1$$

$$v_o = v_1 - i_2 * R_2 = v_1 + i_1 * R_2 =$$

$$= v_1 + R_2 * v_1 / R_1 = v_1 (1 + R_2 / R_1)$$

Thus the voltage gain of noninverting amplifier is:

$$A_v = v_o / v_{in} = 1 + R_2 / R_1$$

Voltage Follower

Special case of noninverting amplifier is a voltage follower

Since in the noninverting amplifier

$$v_o = v_i(1 + R_2/R_1) \quad \text{so when } R_2=0$$

$$v_o = v_i$$

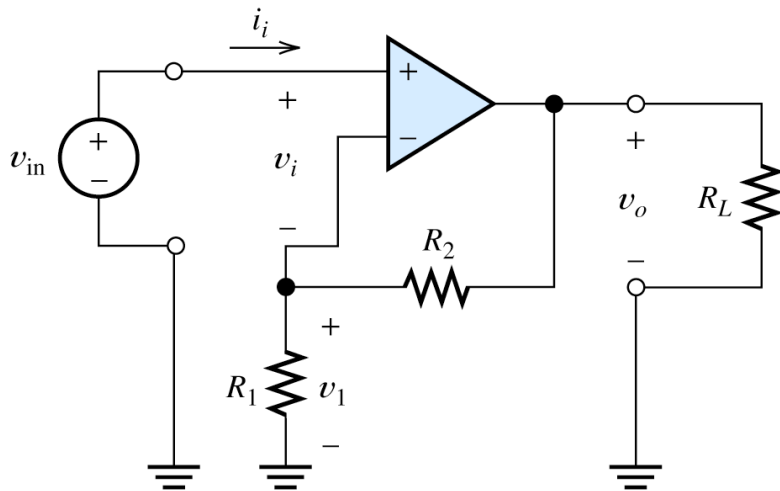


Figure 14.11 Noninverting amplifier.

=>

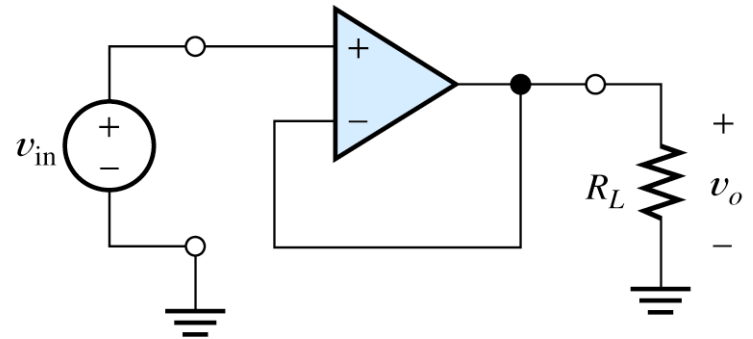


Figure 14.12 The voltage follower which has $A_v = 1$.

Exercise 14.4

Find voltage gain $A_v = v_o / v_{in}$ and input impedance

- With the switch open
- With the switch closed

a.

From KVL: $v_{in} = i_1 * R + i_1 * R + v_o$

$$i_2 = 0 \text{ and } i_1 * R = i_2 * R \quad \Rightarrow \quad i_1 = 0$$

so $v_{in} = v_o$ and $A_v = v_o / v_{in} = 1$

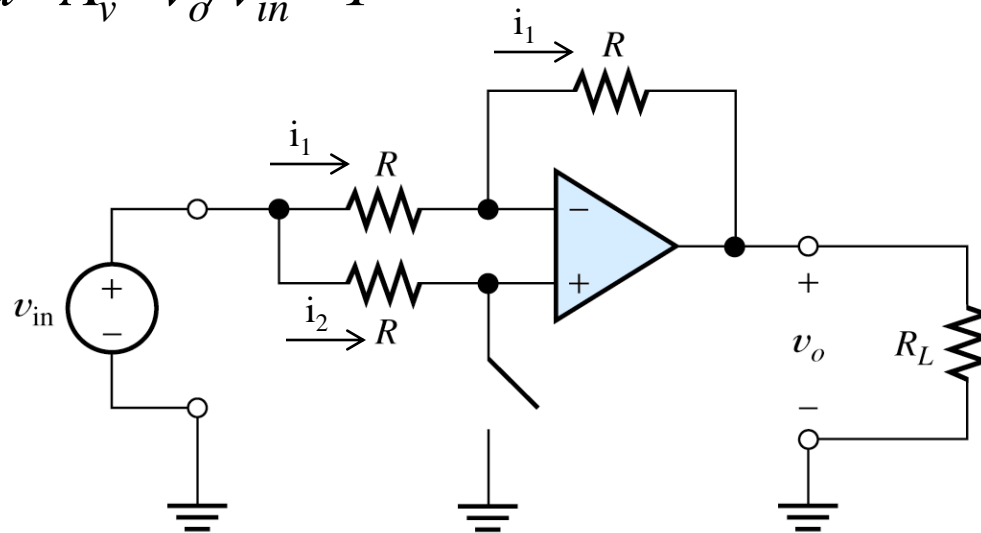


Figure 14.13 Inverting or noninverting amplifier. See Exercise 14.4.

Exercise 14.4

Find voltage gain $A_v = v_o / v_{in}$ and input impedance

- With the switch open
- With the switch closed

a.

Input impedance: $Z_{in} = v_{in} / i_{in} = v_{in} / 0 = \text{inf}$

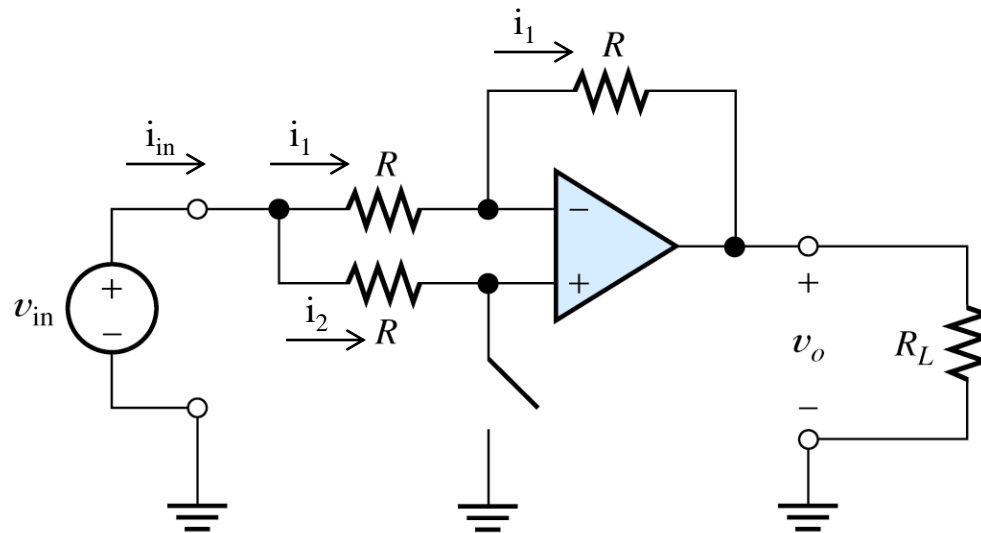


Figure 14.13 Inverting or noninverting amplifier. See Exercise 14.4.

Exercise 14.4

Find voltage gain $A_v = v_o / v_{in}$ and input impedance

- With the switch open
- With the switch closed

b. for closed switch: $i_2 = v_{in} / R$

and $i_1 * R = i_2 * R \Rightarrow i_1 = i_2 \Rightarrow v_{in} = i_1 * R + i_1 * R + v_o$

so $v_{in} = v_{in} / R * R + v_{in} / R * R + v_o \Rightarrow -v_{in} = v_o$

and $A_v = v_o / v_{in} = -1$

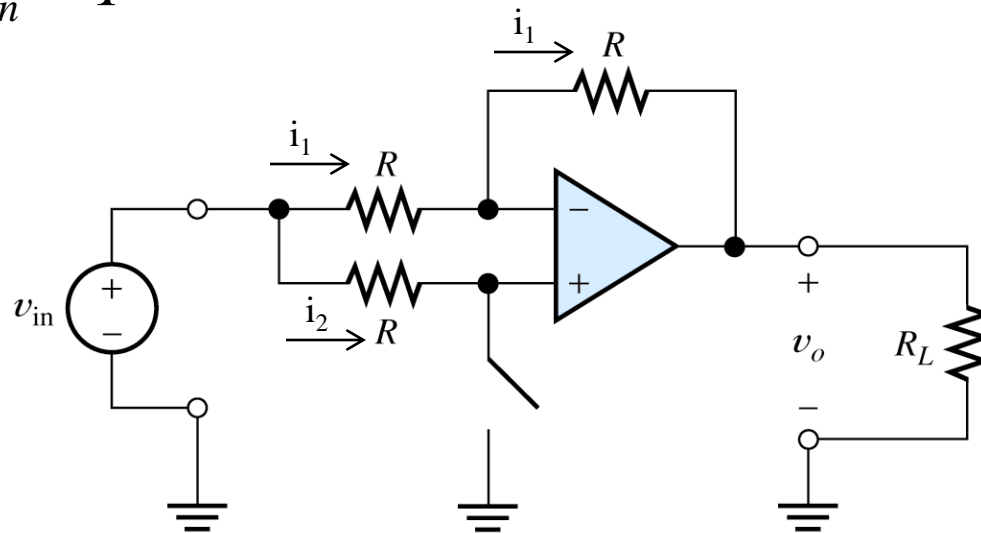


Figure 14.13 Inverting or noninverting amplifier. See Exercise 14.4.

Exercise 14.4

Find voltage gain $A_v = v_o/v_{in}$ and input impedance

- With the switch open
- With the switch closed

b. $i_2 = v_{in}/R$

Input impedance: $Z_{in} = v_{in}/i_{in} = v_{in}/(i_1 + i_2)$

and $i_1 = i_2 \Rightarrow$

$Z_{in} = v_{in}/i_{in} = v_{in}/(2 * v_{in}/R) = R/2$

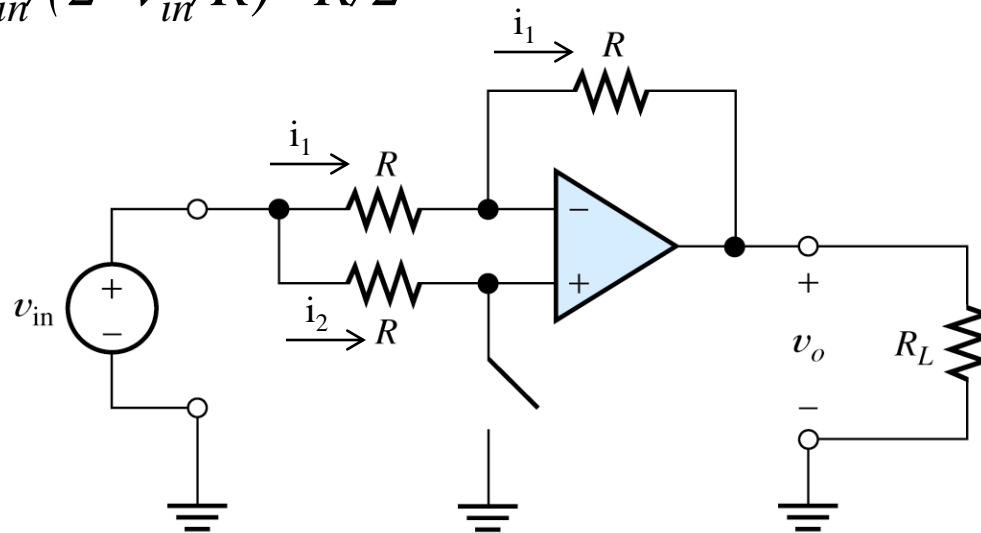


Figure 14.13 Inverting or noninverting amplifier. See Exercise 14.4.

Voltage to Current Converter

Find the output current i_o as a function of v_{in}

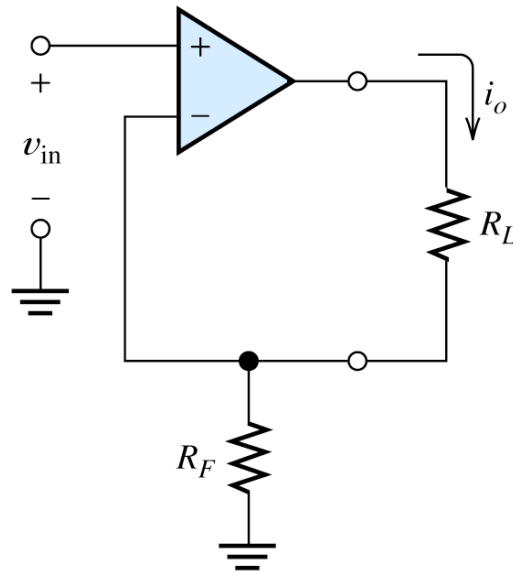


Figure 14.14 Voltage-to-current converter (also known as a transconductance amplifier). See Exercise 14.5.

Voltage to Current Converter

Find the output current i_o as a function of v_{in}

$$v_{in} = i_o * R_f$$

SO

$$i_o = v_{in} / R_f$$

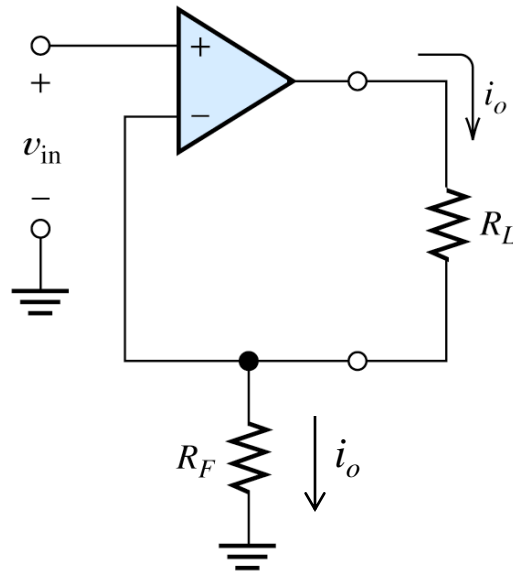


Figure 14.14 Voltage-to-current converter (also known as a transconductance amplifier). See Exercise 14.5.

Exercise 14.6

- Find the voltage gain v_o/v_{in}
- Calculate the voltage gain v_o/v_{in} for $R_1=10\text{ k}\Omega$, $R_2=100\text{ k}\Omega$
- Find the input resistance

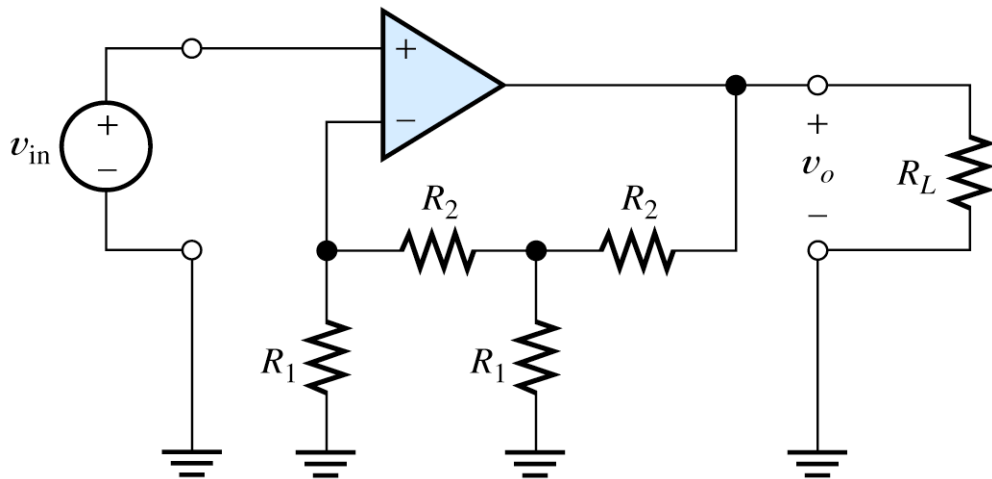


Figure 14.15 Circuit for Exercise 14.6.

Exercise 14.6

- Find the voltage gain v_o/v_{in}
- Calculate the voltage gain v_o/v_{in} for $R_1=10\text{ k}\Omega$, $R_2=100\text{ k}\Omega$
- Find the input resistance

From KCL1: $v_{in}/R_1 = (v_2 - v_{in})/R_2 \Rightarrow v_2/R_2 = v_{in}(1/R_2 + 1/R_1)$

From KCL2: $(v_2 - v_{in})/R_2 + v_2/R_1 + (v_2 - v_o)/R_2 = 0 \Rightarrow$

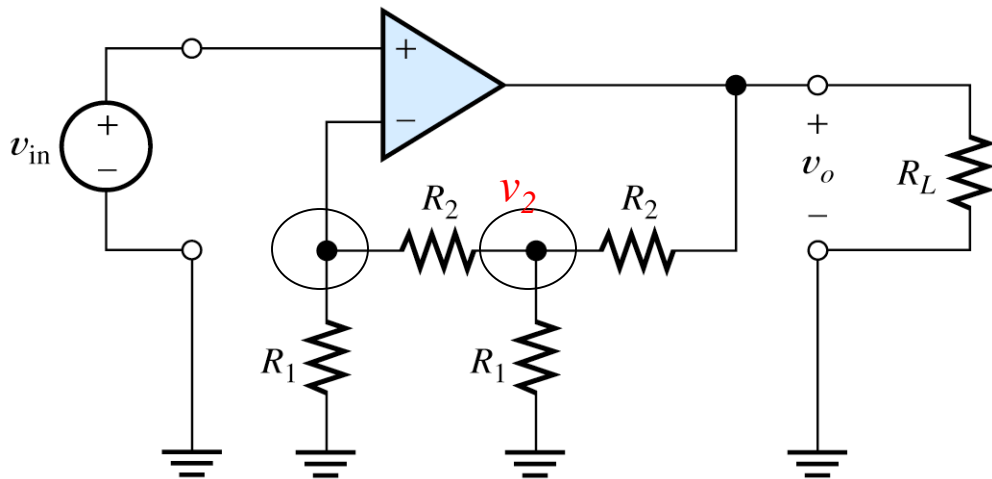


Figure 14.15 Circuit for Exercise 14.6.

Exercise 14.6

- a) Find the voltage gain v_o/v_{in}
- b) Calculate the voltage gain v_o/v_{in} for $R_1=10\text{ k}\Omega$, $R_2=100\text{ k}\Omega$
- c) Find the input resistance


From KCL1: $v_{in}/R_1=(v_2-v_{in})/R_2 \Rightarrow v_2/R_2=v_{in}(1/R_2+1/R_1)$ (*)

From KCL2: $(v_2-v_{in})/R_2+v_2/R_1+(v_2-v_o)/R_2=0 \Rightarrow$

$$v_2(2/R_2+1/R_1)=(v_{in}+v_o)/R_2$$

(*) $v_2=v_{in}(1+R_2/R_1) \Rightarrow v_{in}(1+R_2/R_1)(2/R_2+1/R_1)=(v_{in}+v_o)/R_2$
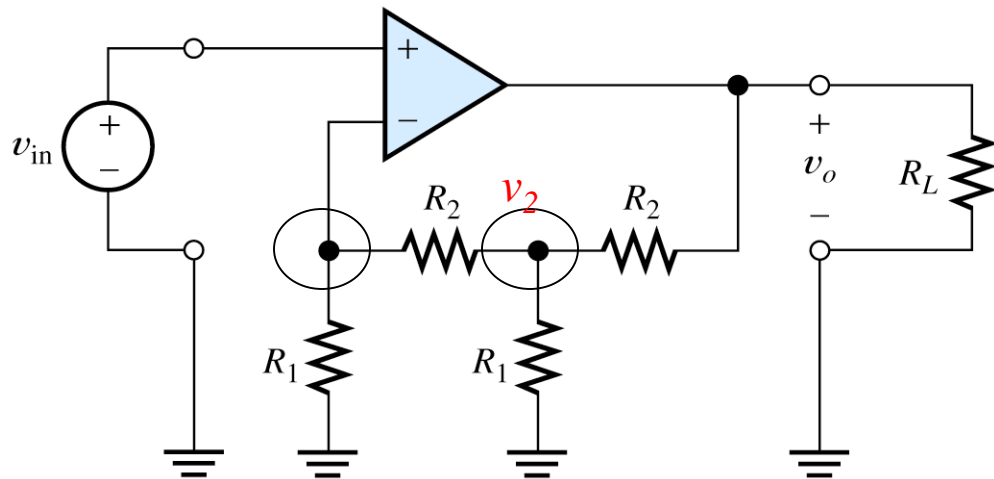
$$v_{in}(R_2(1+R_2/R_1)(2/R_2+1/R_1)-1)=v_o$$



$$v_o/v_{in} = 131$$

Figure 14.15 Circuit for Exercise 14.6.

Exercise 14.6

- a) Find the voltage gain v_o/v_{in}
- b) Calculate the voltage gain v_o/v_{in} for $R_1=10\text{ k}\Omega$, $R_2=100\text{ k}\Omega$
- c) Find the input resistance


From KCL1: $v_{in}/R_1=(v_2-v_{in})/R_2 \Rightarrow v_2/R_2=v_{in}(1/R_2+1/R_1)$ (*)

From KCL2: $(v_2-v_{in})/R_2+v_2/R_1+(v_2-v_o)/R_2=0 \Rightarrow$

$$v_2(2/R_2+1/R_1)=(v_{in}+v_o)/R_2$$

(*) $v_2=v_{in}(1+R_2/R_1) \Rightarrow v_{in}(1+R_2/R_1)(2/R_2+1/R_1)=(v_{in}+v_o)/R_2$
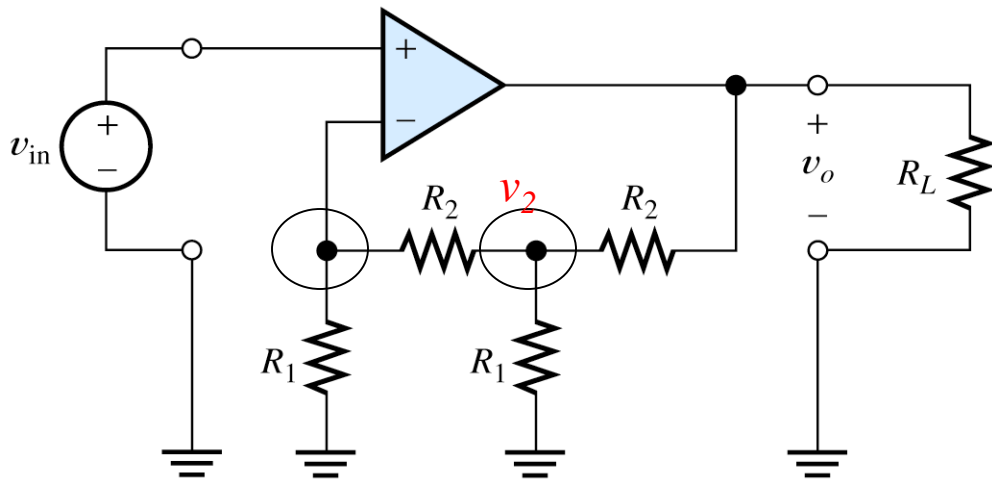
$$v_{in}(R_2(1+R_2/R_1)(2/R_2+1/R_1)-1)=v_o \Rightarrow v_o/v_{in}=100(1+10)0.12-1$$




$$v_o/v_{in}=131$$

Figure 14.15 Circuit for Exercise 14.6.


Matrix equations for op-amp circuits

For Op Amps: write **equal voltages** at the **input** terminals (if one is grounded both are equal zero). Do not write KCL equations **at the output** node of Op Amps.

Example

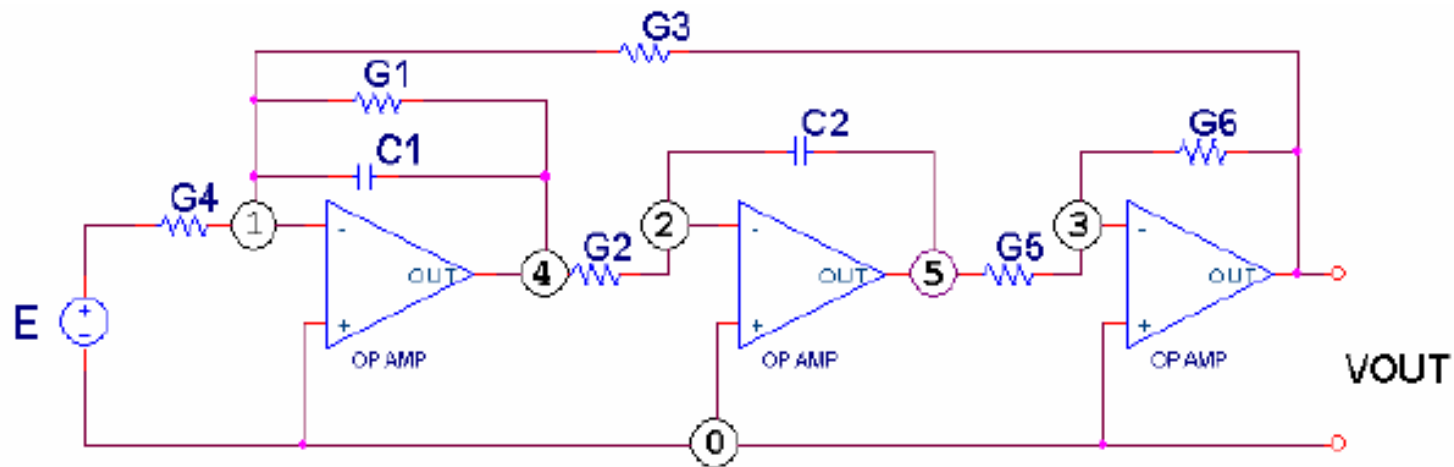

Example

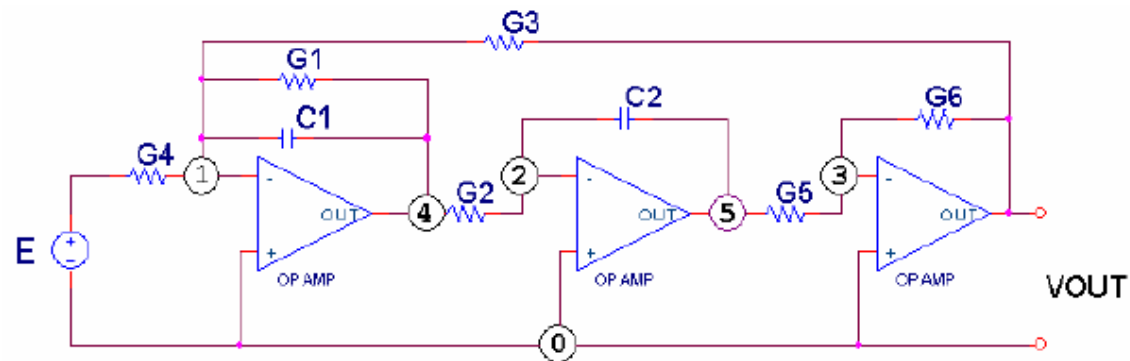

Nonzero voltages are V_4 , V_5 , V_{out} & E

Since we do not write KCL equations at the output nodes of Op Amps, we have for nodes 1, 2 & 3

$$\text{Node (1)} \quad -(G_1 + sC_1)V_4 - G_3V_{out} = EG_4$$

$$\text{Node (2)} \quad -G_2V_4 - sC_2V_5 = 0$$

$$\text{Node (3)} \quad -G_5V_5 - G_6V_{out} = 0$$

Or in the matrix form

$$\begin{bmatrix} -(G_1 + sC_1) & 0 & -G_3 \\ -G_2 & -sC_2 & 0 \\ 0 & -G_5 & -G_6 \end{bmatrix} \begin{bmatrix} V_4 \\ V_5 \\ V_{out} \end{bmatrix} = \begin{bmatrix} EG_4 \\ 0 \\ 0 \end{bmatrix}$$

Design of Simple Amplifiers

Practical amplifiers can be designed using op-amp with feedback.

We know that for noninverting amplifier

$$A_v = v_o / v_{in} = 1 + R_2 / R_1$$

so to obtain $A_v = 10$ we could use $R_1 = 1 \Omega$ and $R_2 = 9 \Omega$

But such low output resistance will draw too much current from the power supply

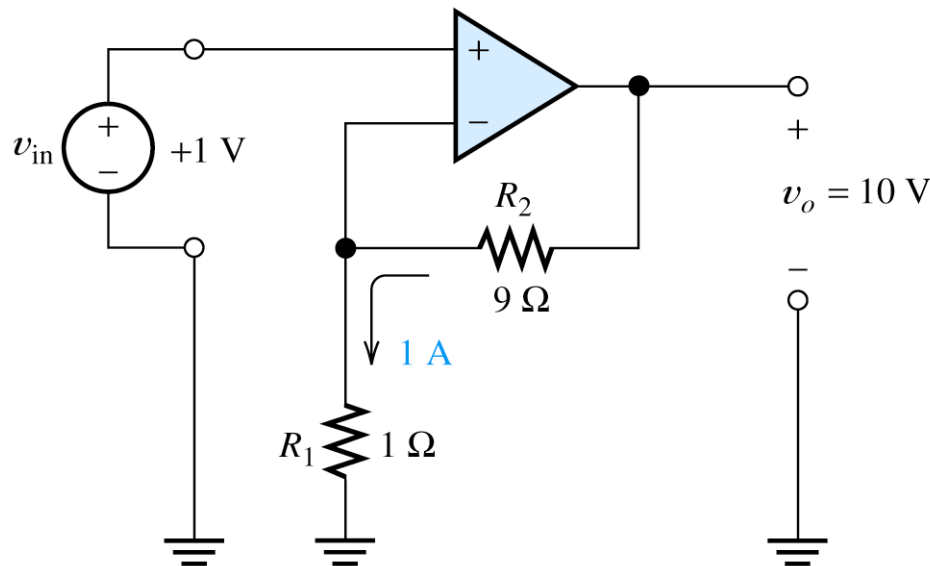


Figure 14.16 If low resistances are used, an excessively large current is required.

Design of Simple Amplifiers

The same gain can be obtained with large resistance values.

$$A_v = v_o / v_{in} = 1 + R_2 / R_1$$

But for high output resistance are sensitive to bias current and we must use a filtering output capacitor to remove the noise.

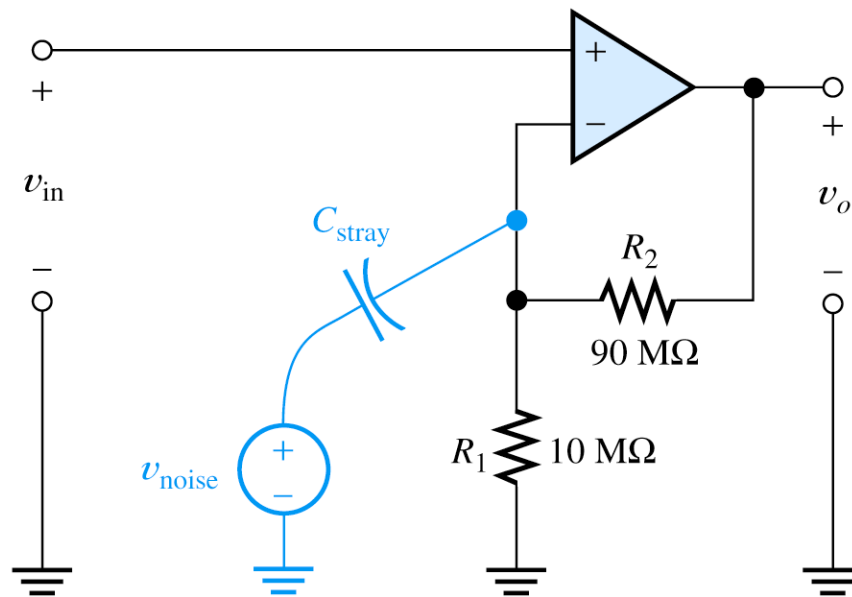


Figure 14.17 If very high resistances are used, stray capacitance can couple unwanted signals into the circuit.

Op-Amp Imperfections in a Linear Mode

We consider the following op-amp imperfections:

- 1) *Nonideal linear operation,*
- 2) *Nonlinear characteristics*
- 3) *Dc offset values.*

Input and output impedances:

- 1) *Ideal opamp have $R_{in}=0$,*

$$R_{in} = \infty; \quad R_{out} = 0\Omega$$

- 2) *Real op-amp has*

$$R_{in} = 1M\Omega - 10^{12}\Omega;$$

$$R_{out} = 1\Omega - 100\Omega$$

Op-Amp Imperfections in a Linear Mode


We consider the following op-amp imperfections:

- 1) *Nonideal linear operation,*
- 2) *Nonlinear characteristics*
- 3) *Dc offset values.*

Voltage gain:

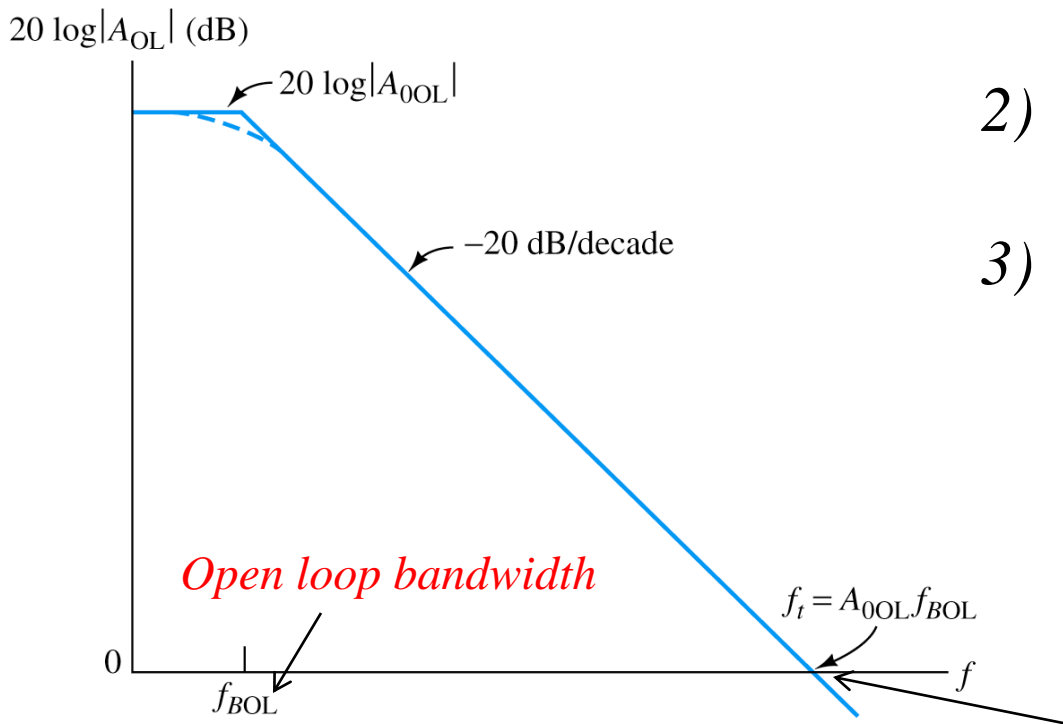- 1) *Ideal op-amp has infinite gain and bandwidth,*
- 2) *Real op-amp has the gain that changes with frequency.*
- 3) *Open loop gain:*

$$A_{OL}(f) = \frac{A_{0OL}}{1 + j \frac{f}{f_{BOL}}}$$



Terminal frequency f_t – gain drops to 1

Figure 14.20 Bode plot of open-loop gain for a typical op amp.

Op-Amp Imperfections in a Linear Mode

Negative feedback is used to lower the gain and extend the bandwidth.

Open loop gain $A_{OL}(f) = \frac{V_o}{V_{id}}$

From KVL $V_{in} = V_{id} + \beta V_o \quad \longrightarrow \quad V_{in} = \frac{V_o}{A_{OL}} + \beta V_o$

So the closed loop gain

$$A_{CL} = \frac{V_o}{V_{in}} = \frac{1}{\frac{1}{A_{OL}} + \beta} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

where $\beta = \frac{R_1}{R_1 + R_2}$

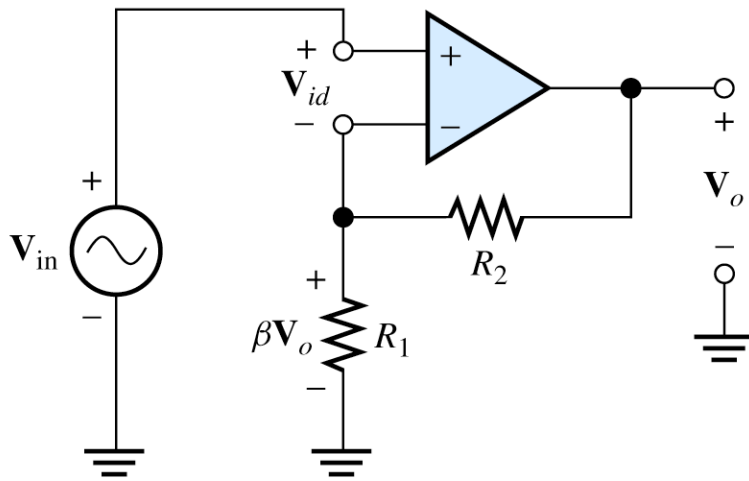


Figure 14.21 Noninverting amplifier circuit used for analysis of closed-loop bandwidth.

Op-Amp Imperfections in a Linear Mode

Using open loop gain

$$A_{CL}(f) = \frac{V_o}{V_{id}} = \frac{A_{0OL}}{1 + j \frac{f}{f_{BOL}}}$$

We get

$$A_{CL} = \frac{V_o}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}} = \frac{A_{0OL}}{1 + j \frac{f}{f_{BOL}} + \beta A_{0OL}} = \frac{\frac{A_{0OL}}{1 + \beta A_{0OL}}}{1 + j \frac{f}{f_{BOL}(1 + \beta A_{0OL})}}$$

So we will get closed loop dc gain

$$A_{0CL} = \frac{V_o}{V_{in}} = \frac{A_{0OL}}{1 + \beta A_{0OL}}$$

closed loop voltage gain

closed loop bandwidth


$$f_{BCL} = f_{BOL}(1 + \beta A_{0OL})$$

$$A_{CL}(f) = \frac{A_{0CL}}{1 + j \frac{f}{f_{BCL}}}$$

Op-Amp Imperfections in a Linear Mode

Comparing to open loop, the closed loop gain is reduced
And closed loop bandwidth is larger

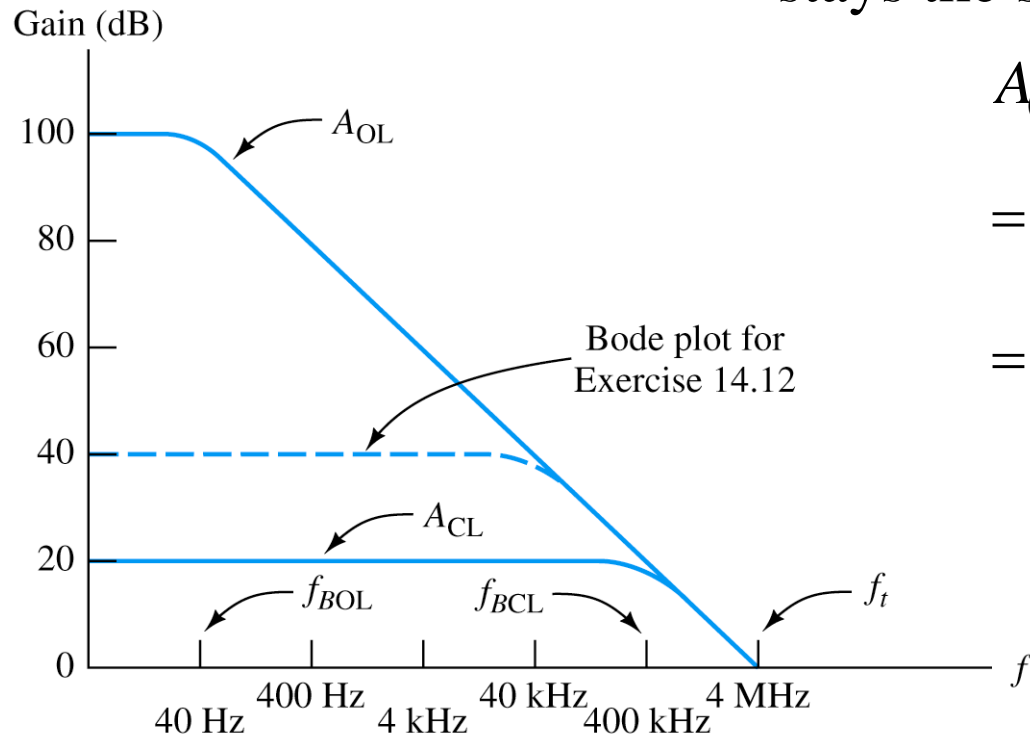The gain*bandwidth product stays the same



$$\begin{aligned}
 A_{0CL} f_{BCL} &= \\
 &= \frac{A_{0OL}}{1 + \beta A_{0OL}} \times f_{BOL} (1 + \beta A_{0OL}) \\
 &= A_{0OL} \times f_{BOL}
 \end{aligned}$$

Figure 14.22 Bode plots for Example 14.5 and Exercise 14.12.

Nonlinear Limitations

Nonlinear limitations:

1) Output voltage swing is limited and depend on power supply voltage

for $V_{DD} \in (-15V, +15V), \quad v_o(t) \in (-12V, +12V)$

2) Maximum output current is limited

for $\mu A741$ amplifier $i_o(t) \in (-40mA, +40mA)$

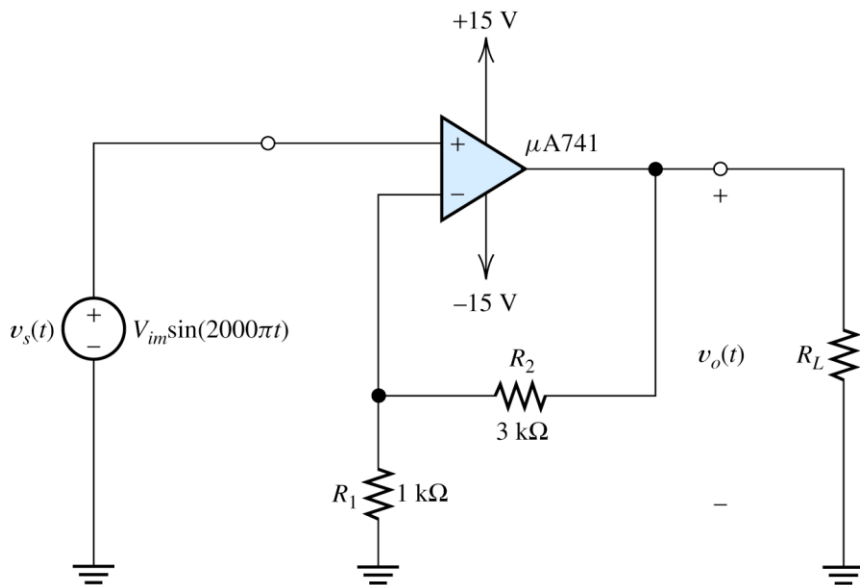


Figure 14.23 Noninverting amplifier used to demonstrate various nonlinear limitations of op amps.

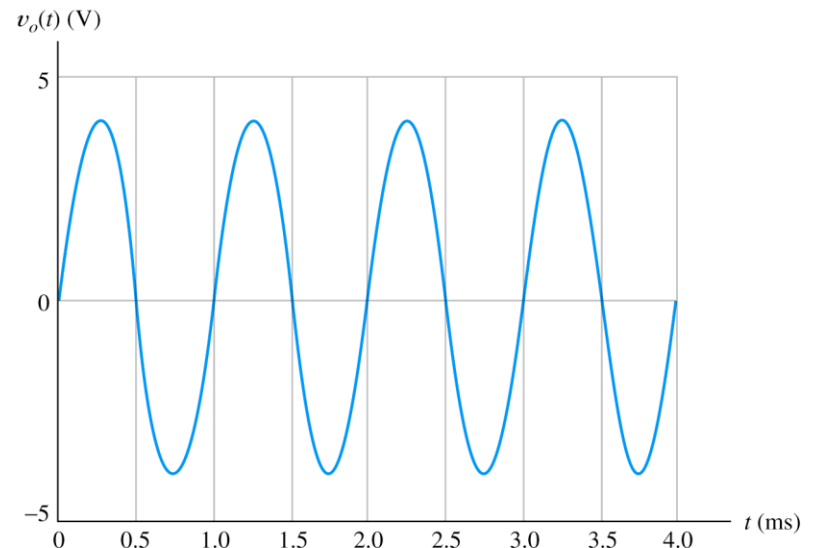


Figure 14.24 Output of the circuit of Figure 14.23 for $R_L = 10 \text{ k}\Omega$ and $V_{im} = 1 \text{ V}$. None of the limitations are exceeded, and $v_o(t) = 4v_s(t)$.

Nonlinear Limitations

When voltage or current limits are exceeded, clipping of the output signal occurs causing large nonlinear distortions

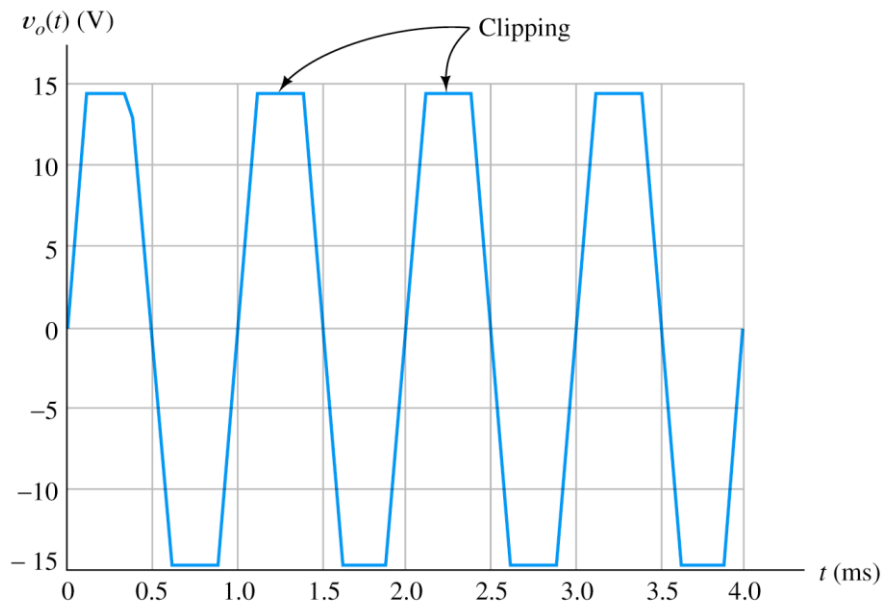


Figure 14.25 Output of the circuit of Figure 14.23 for $R_L = 10 \text{ k}\Omega$ and $V_{im} = 5 \text{ V}$. Clipping occurs because the maximum possible output voltage magnitude is reached.

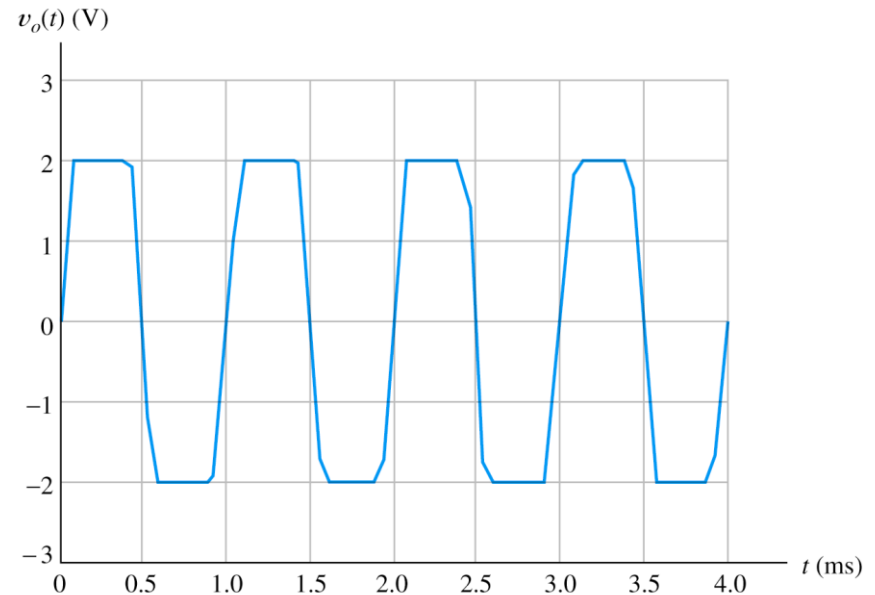


Figure 14.26 Output of the circuit of Figure 14.23 for $R_L = 50 \Omega$ and $V_{im} = 1 \text{ V}$. Clipping occurs because the maximum output current limit is reached.

Nonlinear Limitations

Another nonlinear limitation is limited rate of change of the output signal known as the **slew-rate limit SR**

$$\left| \frac{dv_o}{dt} \right| \leq SR$$

Using slew rate we can find maximum frequency known as full-power bandwidth.

Assuming

$$v_o(t) = V_{om} \sin(\omega t)$$

$$\frac{dv_o}{dt} = \omega V_{om} \cos(\omega t) \leq$$

$$\leq 2\pi f V_{om} \leq SR$$

So the **full-power bandwidth**

$$f_{FP} \leq \frac{SR}{2\pi V_{om}}$$

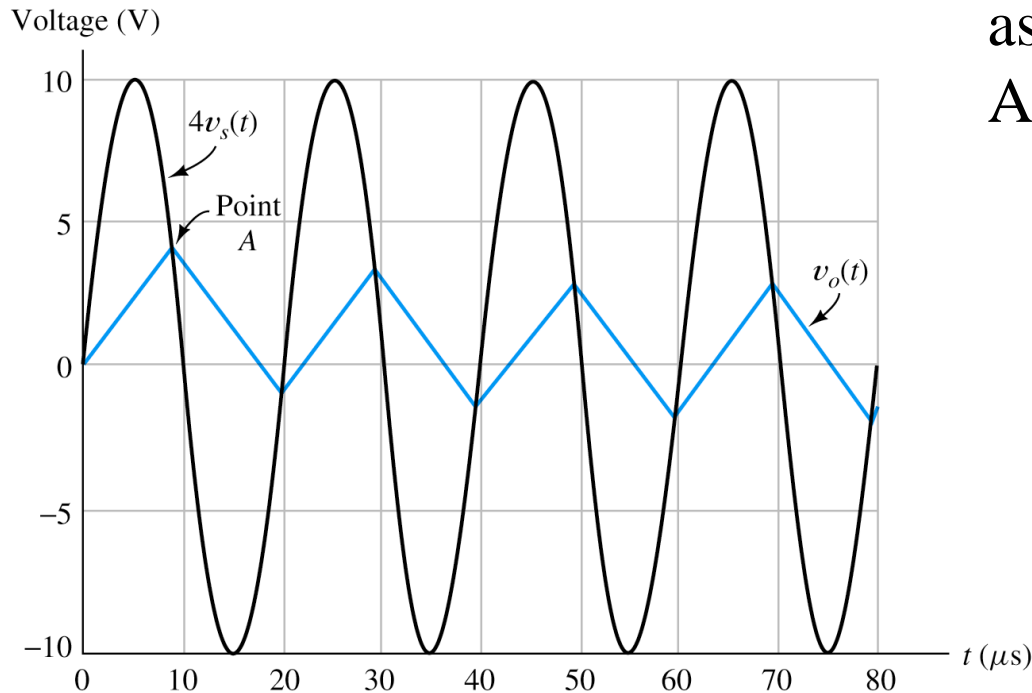



Figure 14.27 Output of the circuit of Figure 14.23 for $R_L = 10 \text{ k}\Omega$ and $v_s(t) = 2.5 \sin(10^5 \pi t)$. The output waveform is a triangular waveform because the slew-rate limit is exceeded. The output for an ideal op amp, which is equal to $4v_s(t)$, is shown for comparison.

Dc offset values

There are three dc offset values related to op-amp design:

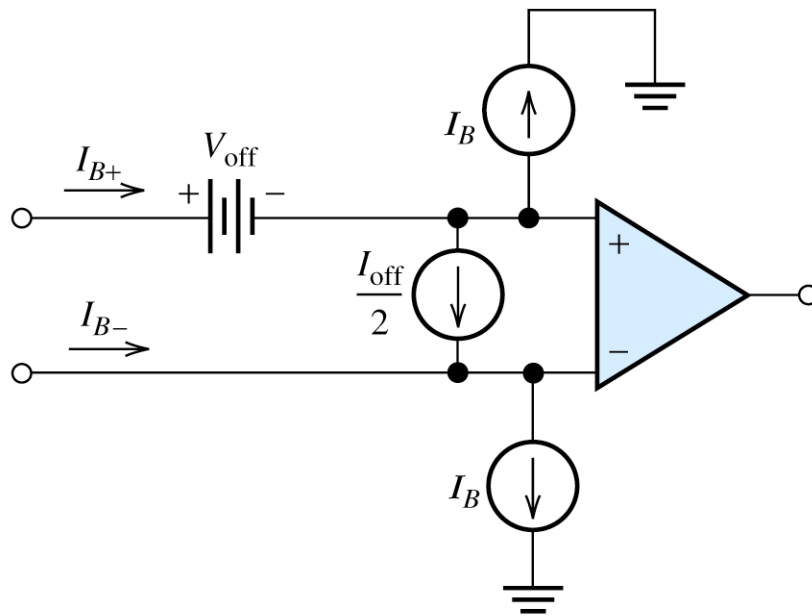- 1) *Bias currents* I_{B+} , I_{B-} – related to differential inputs
- 2) *Offset current* – ideally zero value
- 3) *Offset voltage* – results in nonzero output for zero input

They can be represented as additional dc sources in the op-amp model





$$I_B = \frac{I_{B+} + I_{B-}}{2}$$

$$I_{\text{off}} = I_{B+} - I_{B-}$$

Figure 14.29 Three current sources and a voltage source model the dc imperfections of an op amp.


Industrial op-amp

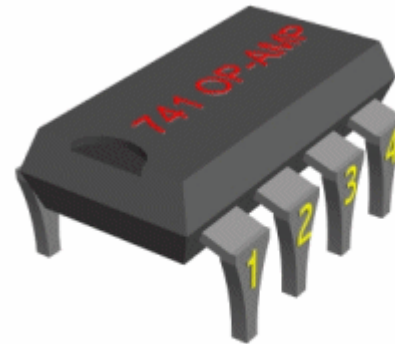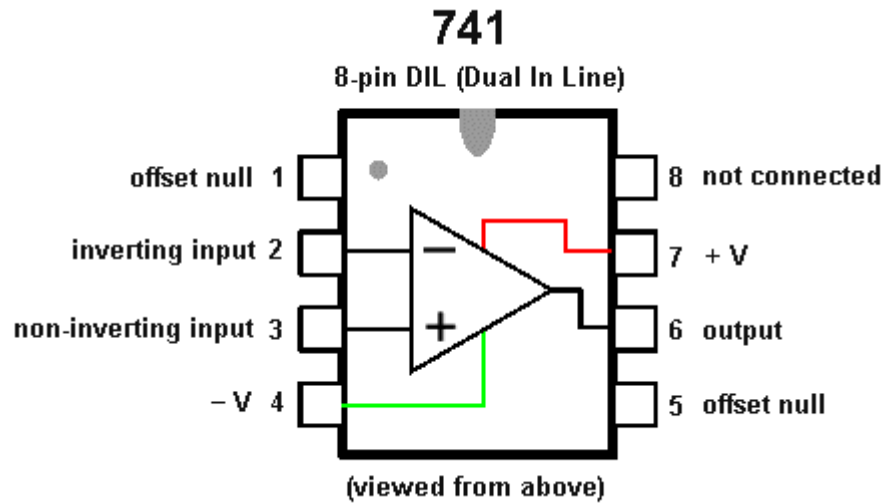741 Amplifier is the most popular amplifier it has
 $A_{OL}=100000$



Industrial op-amp

741 Amplifier BJT transistor level schematic

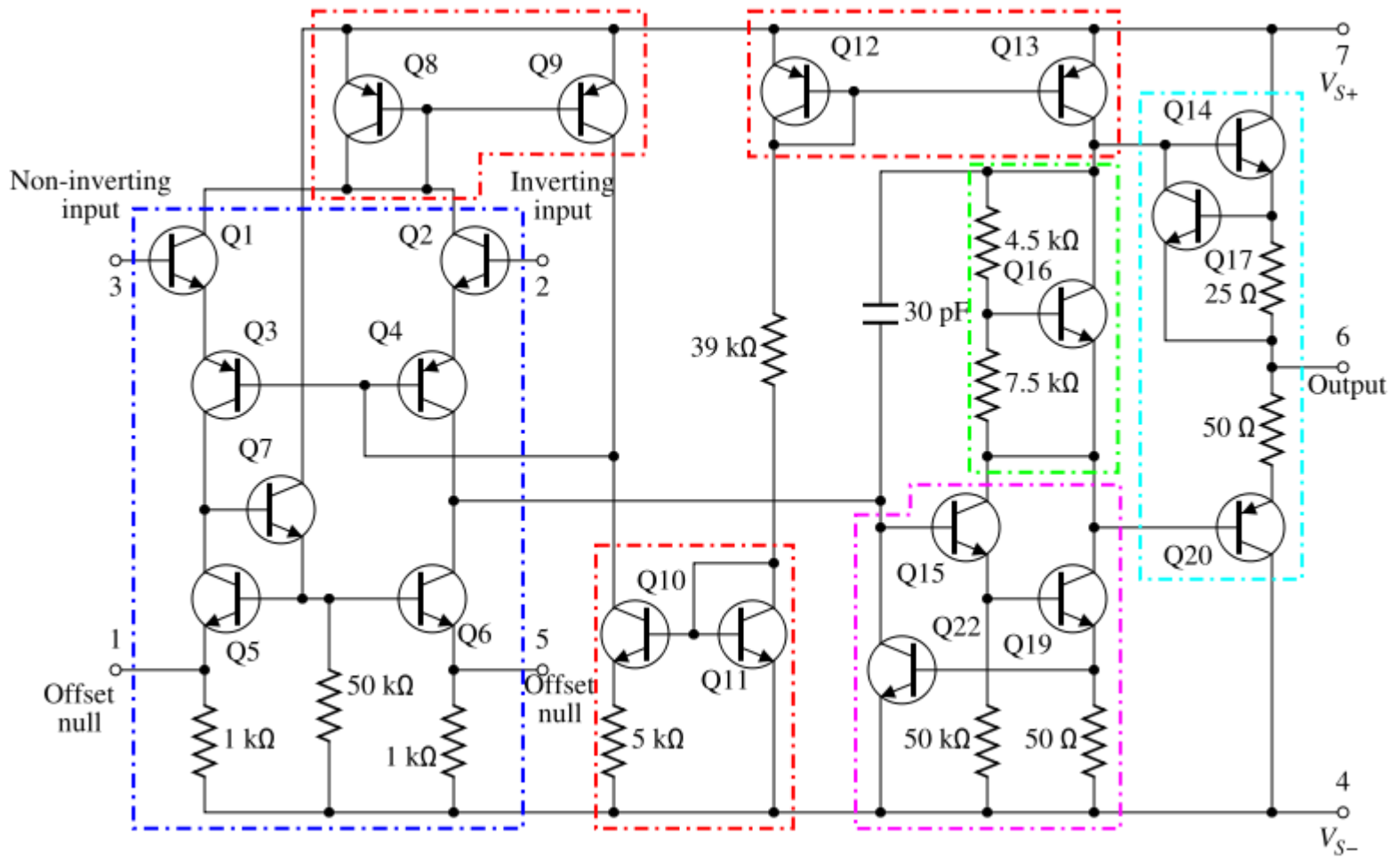



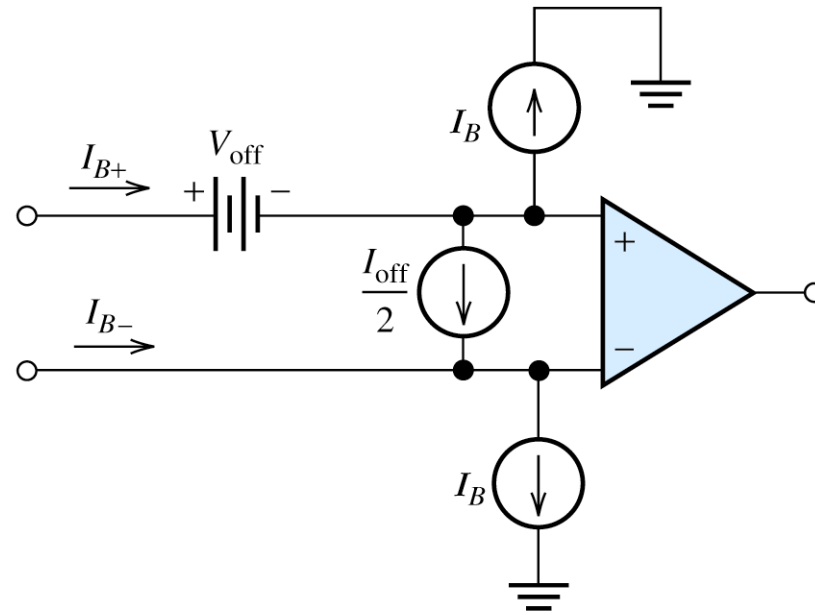



Figure 14.29 Three current sources and a voltage source model the dc imperfections of an op amp.

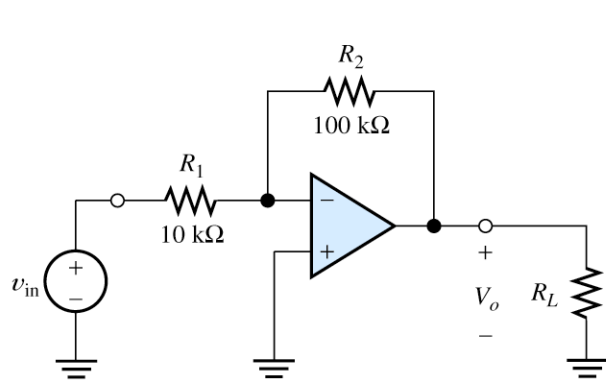


(a) Original circuit

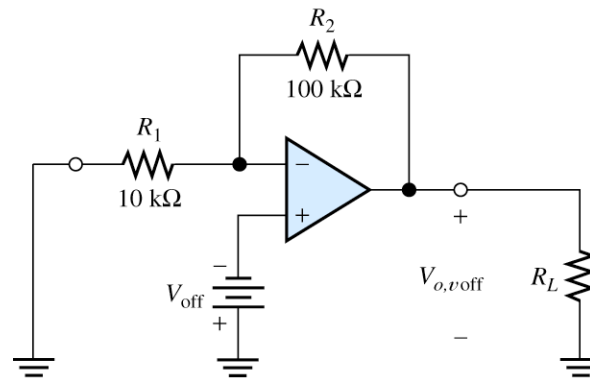

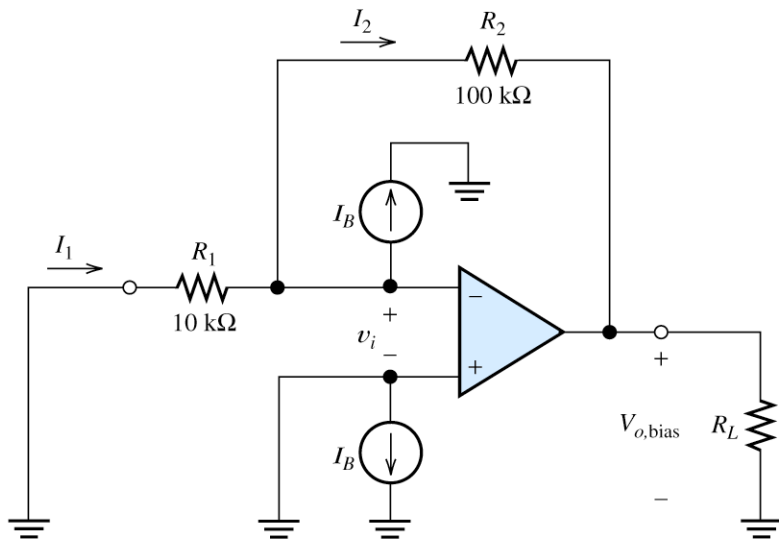(b) Circuit with $v_{in} = 0$ showing the input offset voltage source



(c) Circuit with bias current sources

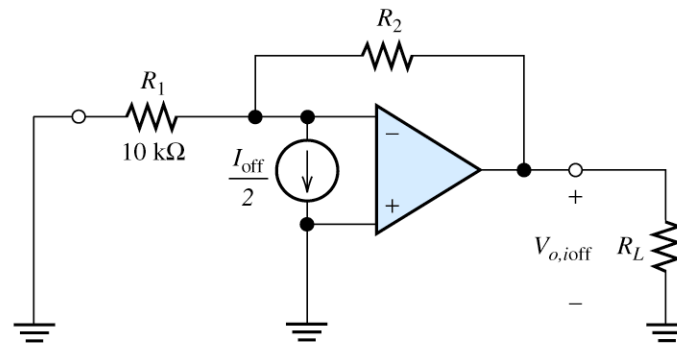

(d) Circuit with offset current source

Figure 14.30 Circuits of Example 14.7.

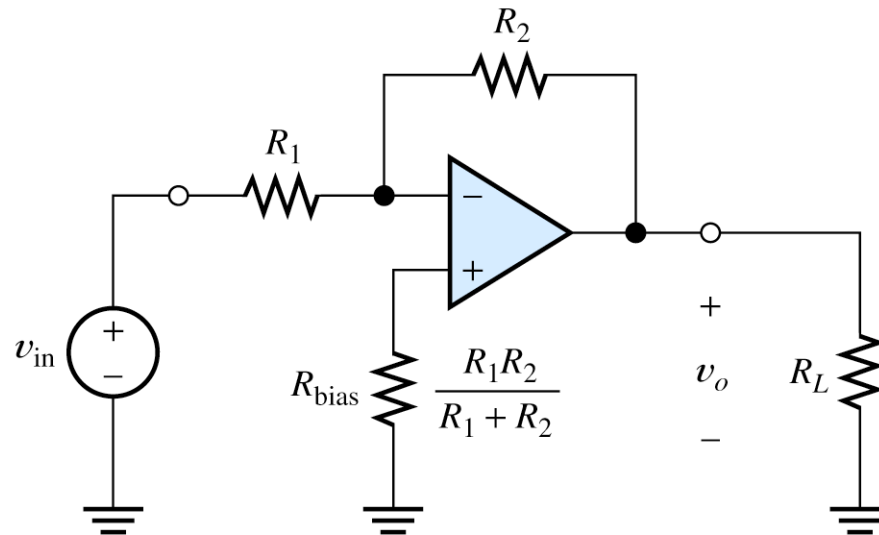


Figure 14.31 Adding the resistor R_{bias} to the inverting amplifier circuit causes the effects of bias currents to cancel.

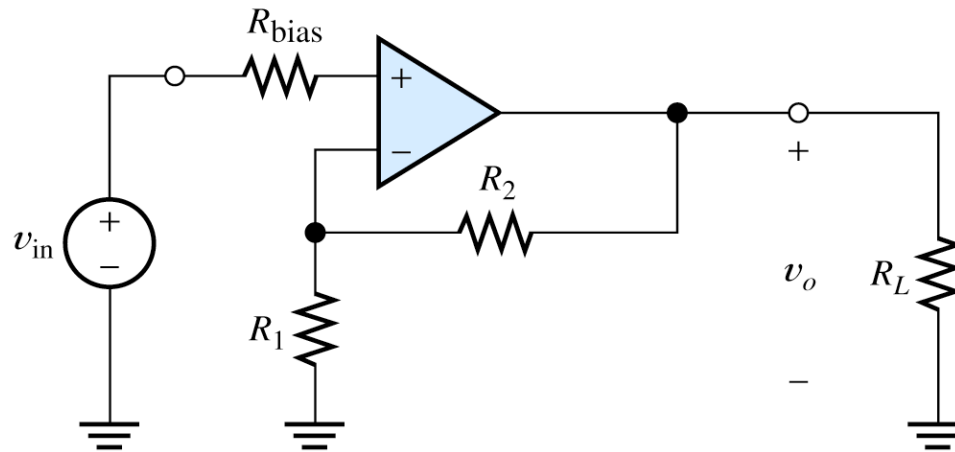


Figure 14.32 Noninverting amplifier, including resistor R_{bias} to balance the effects of the bias currents. See Exercise 14.15.

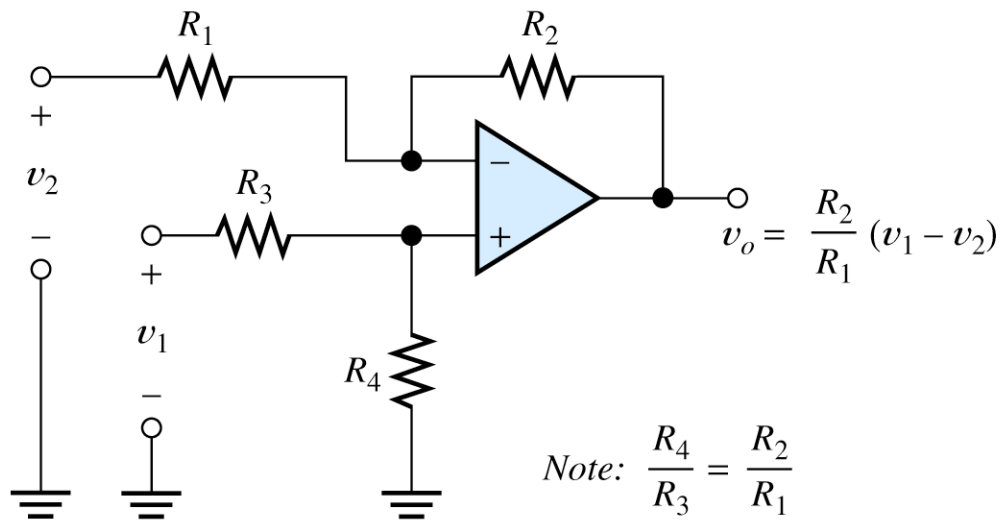


Figure 14.33 Differential amplifier.

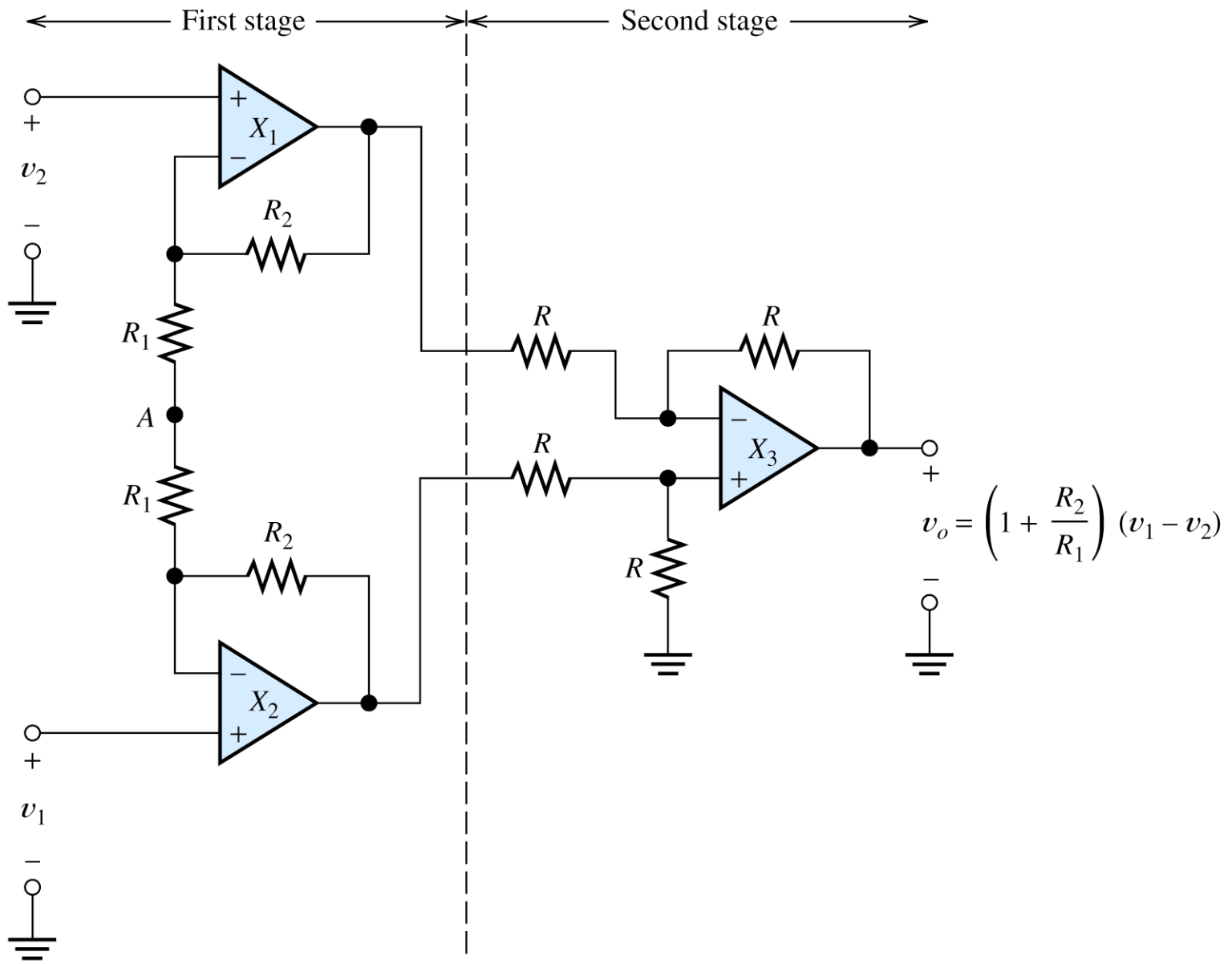


Figure 14.34 Instrumentation-quality differential amplifier.

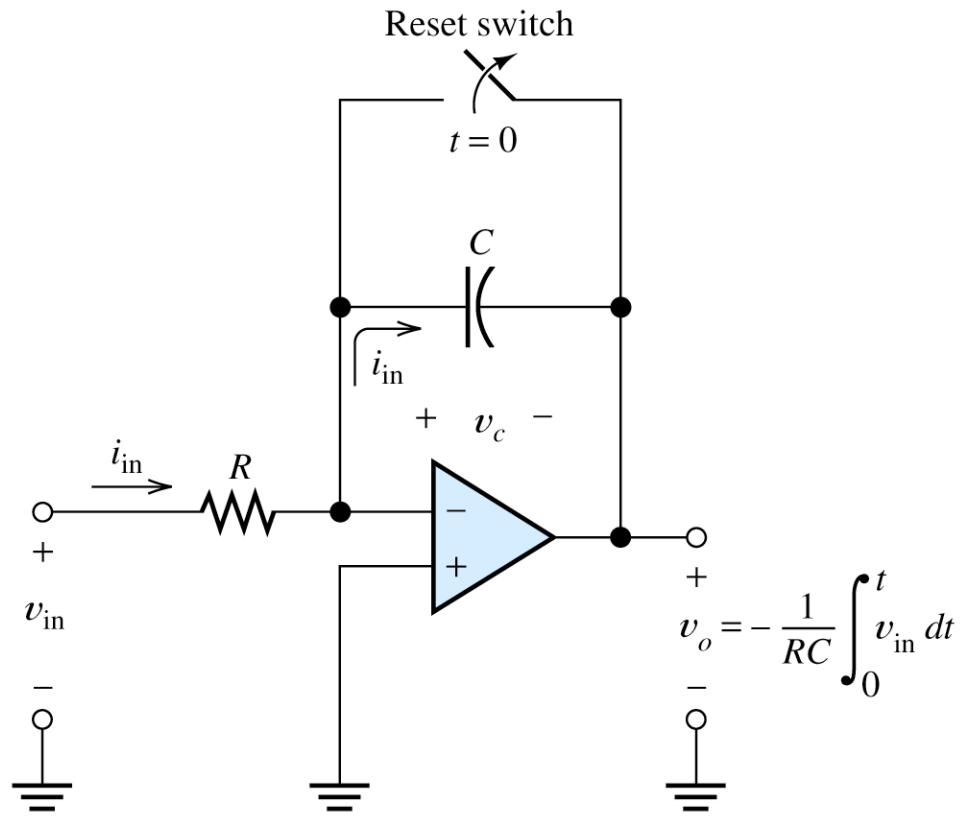


Figure 14.35 Integrator.

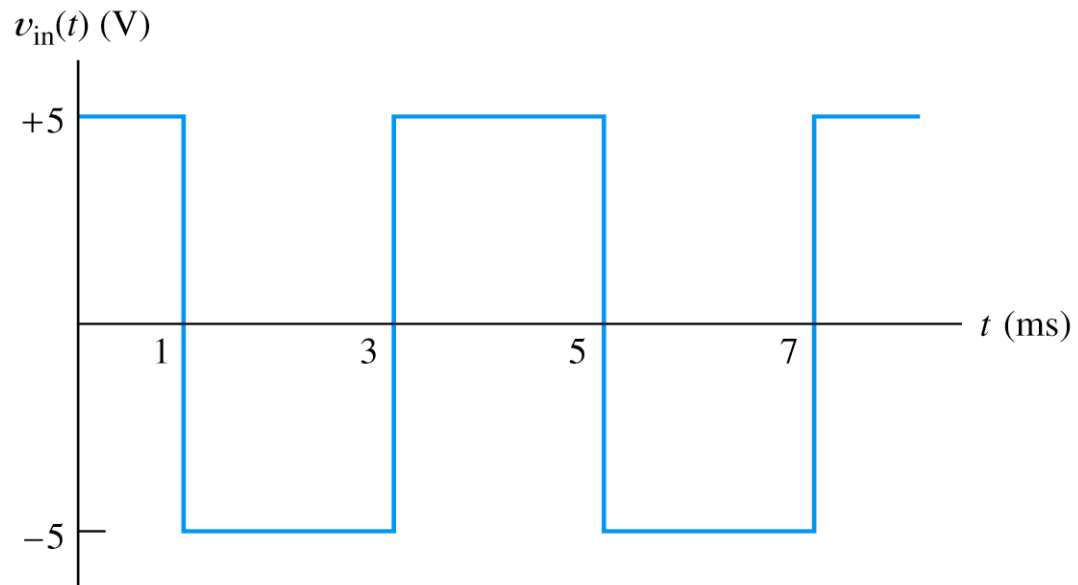


Figure 14.36 Square-wave input signal for Exercise 14.17.

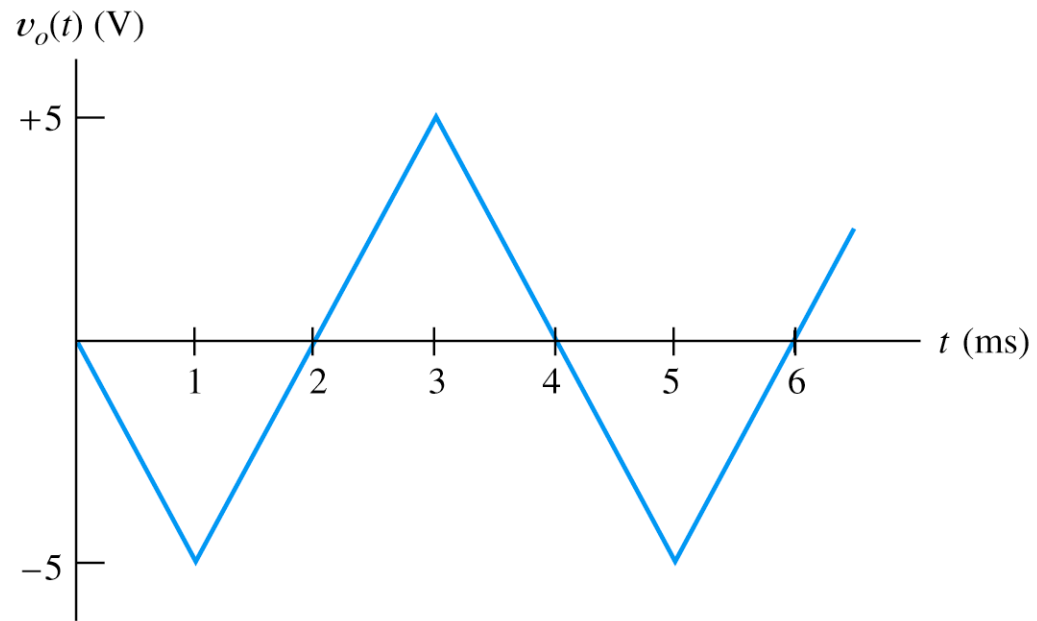


Figure 14.37 Answer for Exercise 14.17.

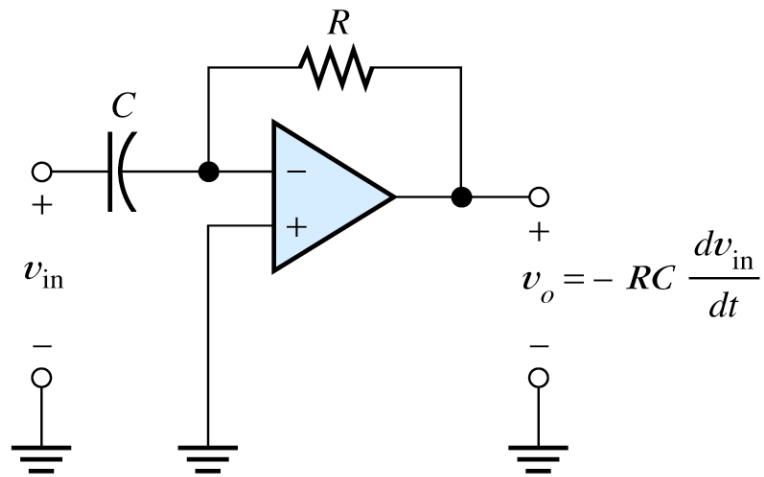


Figure 14.38 Differentiator.

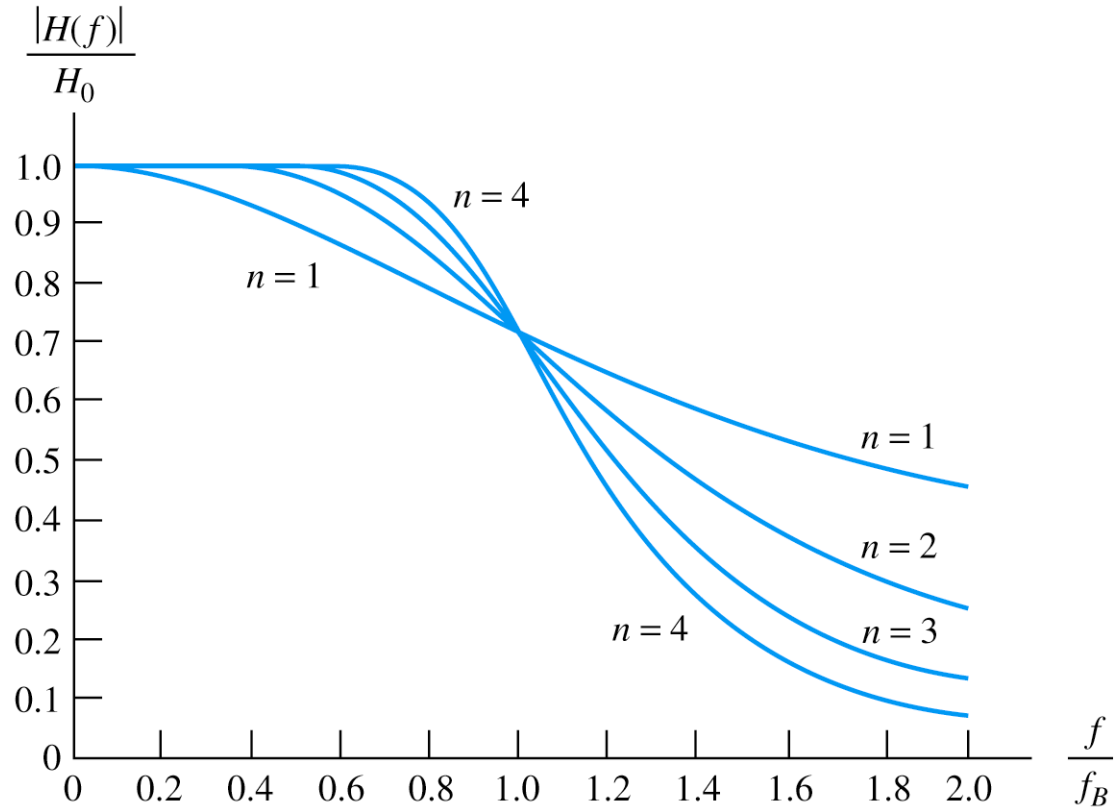


Figure 14.39 Transfer-function magnitude versus frequency for lowpass Butterworth filters.

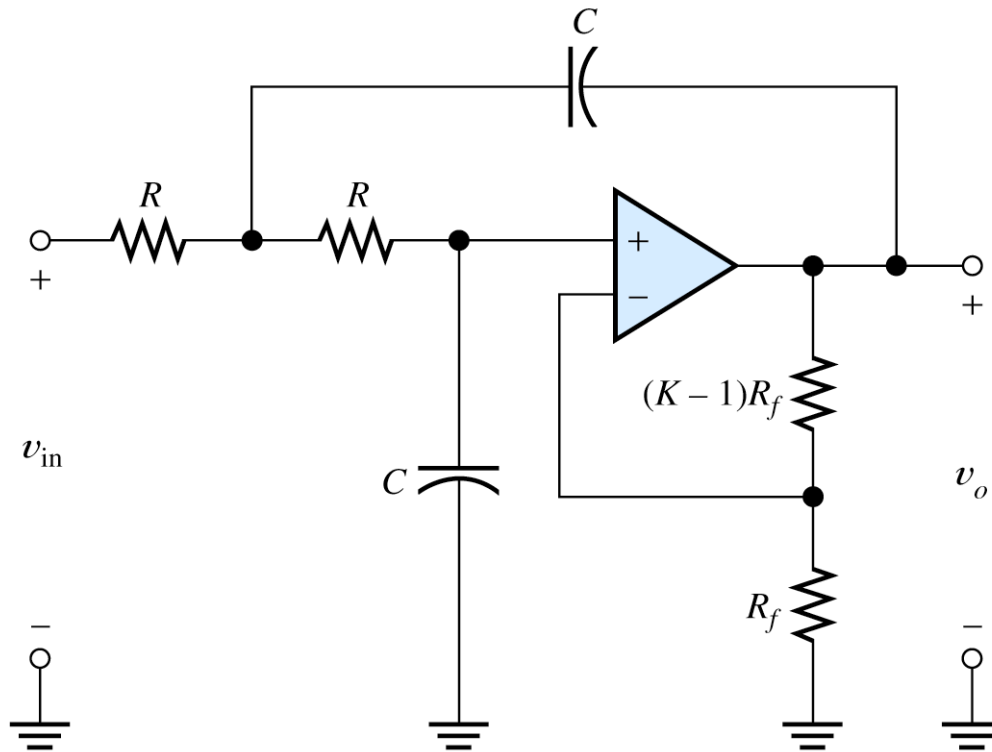


Figure 14.40 Equal-component Sallen–Key lowpass active-filter section.

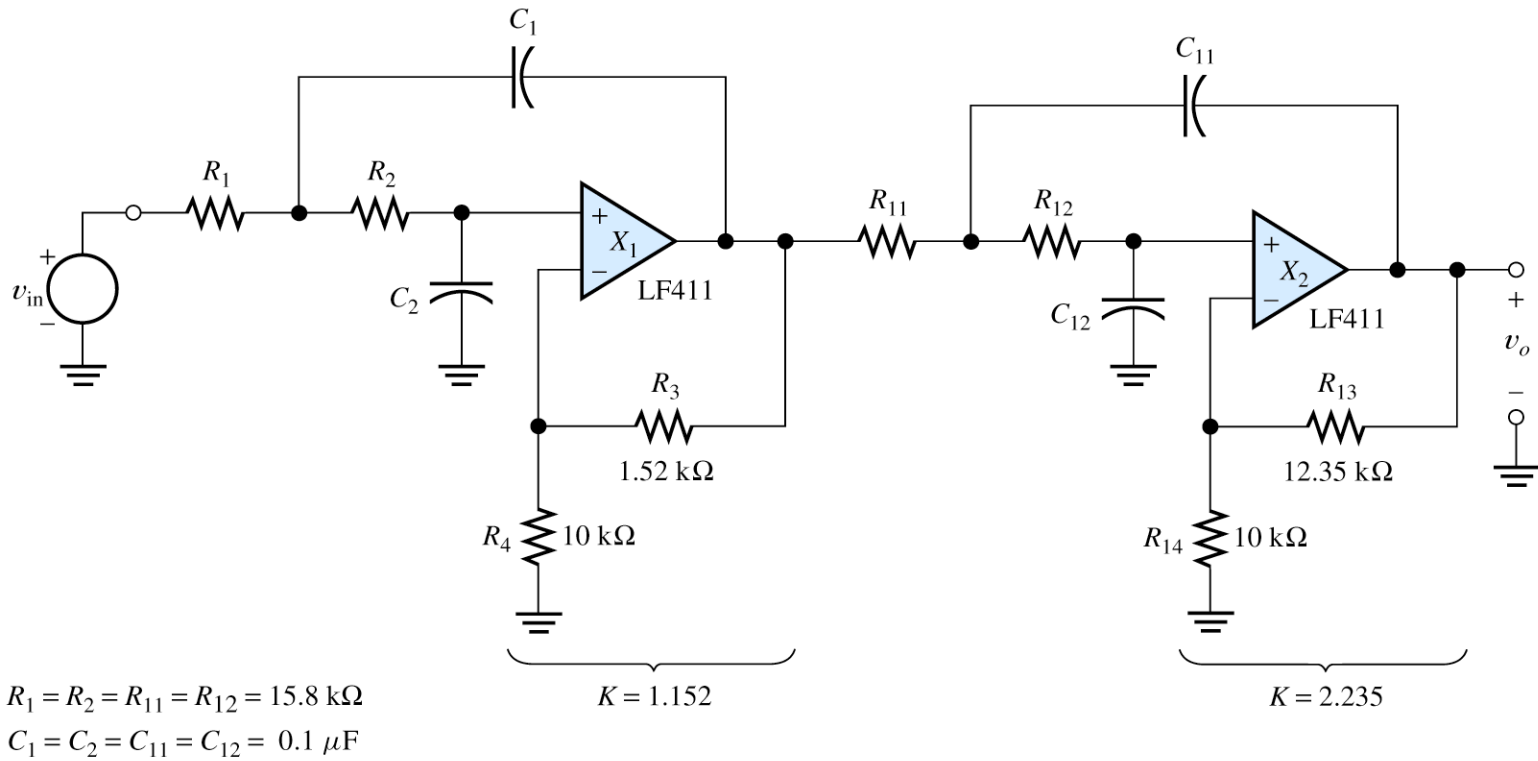


Figure 14.41 Fourth-order Butterworth lowpass filter designed in Example 14.8.

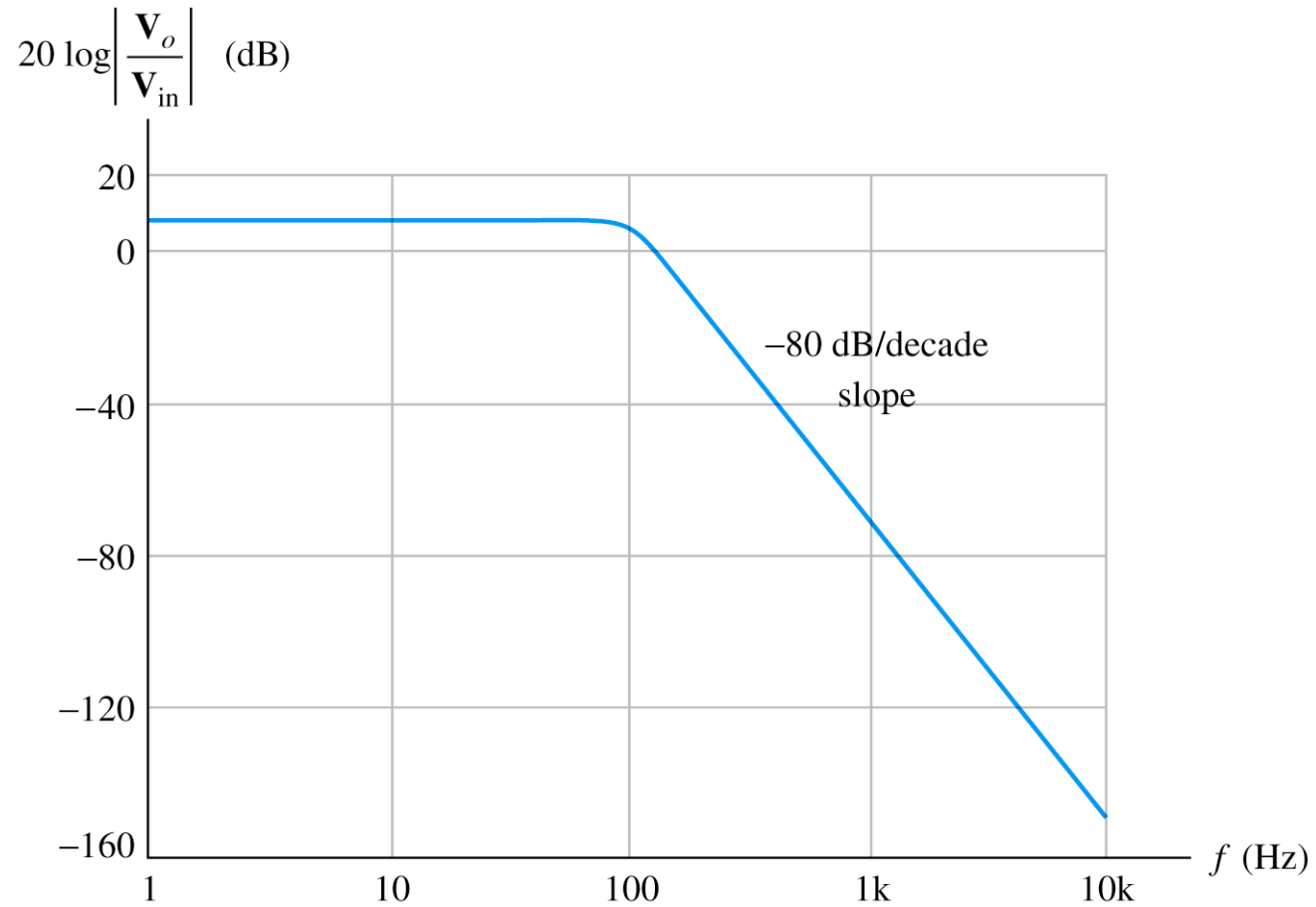


Figure 14.42 Bode magnitude plot of the gain for the fourth-order lowpass filter of Example 14.8.