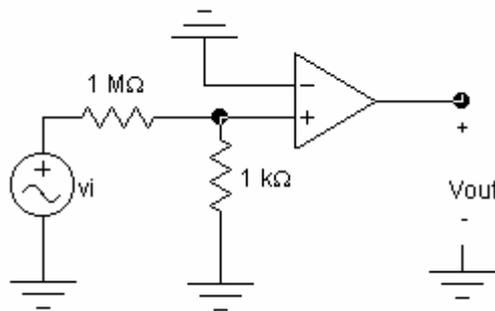




1. What is the minimum number of terminals required by a single op amp? What is the minimum number of terminals required on an IC package containing four op amps (called a quad op amp)?
2. The circuit shown below uses op amp that is ideal except for having a finite gain  $A$ . Measurements indicate that  $v_o=3.5V$  when  $v_i=3.5V$ . What is the op amp gain?



3. An inverting amplifier uses an ideal op amp with  $R_1=33k\Omega$  and  $R_2=330k\Omega$ . What is the closed-loop gain you would expect? A second resistor is connected at the input:
  - a- in series with the existing  $33k\Omega$ .
  - b- in parallel with the existing  $33k\Omega$
  - c- What values of gain result?
4. Assuming ideal op amps, find the voltage gain  $v_o/v_i$  and input  $R_{in}$  in each of the circuit below:

