



1. A particular op amp using $\pm 15\text{V}$ supplies operates linearly for outputs in the range -13V to $+13\text{V}$. If used in an inverting amplifier configuration of gain -100 , what is the rms value of the largest possible sinewave that can be supplied at the input without output clipping?
2. For an op amp differentiator circuit having a time constant of 1 ms , using an op amp whose linear output range is $\pm 11\text{V}$, what is the maximum rate of rise of acceptable input signals?
3. An op amp having a slew rate of $10\text{V}/\mu\text{s}$ is to be used in the unity gain follower configuration, with input pulses that rise from 0 to 5V . What is the shortest pulse that can be used while ensuring full-amplitude output? For such a pulse, describe the output resulting.
4. Show that for an op amp having the internal structure discussed in the lecture, the relationship between the slew rate and the unity-gain frequency is given by:

$$SR = \left[\frac{I_{\max}}{G_m} \right] \omega_t$$

where I_{\max} is the maximum current available from the input stage and G_m is the transconductance of the input stage.

