



- 1- For the circuit shown in figure (1) find $L(s)$, $L(j\omega)$, the frequency for zero loop phase, and R_2/R_1 for oscillation.
- 2- Consider the bistable circuit shown in Fig. (2):
 - a) Derive an expressions for the threshold voltages V_{TL} and V_{TH} in terms of op-amp saturation levels L_+ and L_- , R_1 , R_2 and V_R .
 - b) If $L_+ = -L_- = V$ and $R_1 = 10\text{ k}\Omega$, find R_2 and V that results in the threshold voltages of 0 and $V/10$.
- 3- Figure (3) shows a monostable MV circuit. In the stable state, $v_O = L_+$, $V_A = 0$, and $V_B = -V_{ref}$. The circuit can be triggered by applying a positive input pulse of height greater than V_{ref} . For normal operation, $C_1 R_1 \ll CR$. Show the resulting waveform of v_O and V_a . Also show that the pulse generated at the output will have a width T given by:

$$T = CR \ln \left(\frac{L_+ - L_-}{V_{ref}} \right)$$

Note that this circuit has the interesting property that the pulse width can be controlled by changing V_{ref} .

- 4- Consider the 555 timer when the Threshold and the Trigger input terminals are joined together and connected to an input voltage v_I . Verify that the transfer characteristics $v_O - v_I$ is that of an inverting bistable MV circuit with thresholds $V_{TL} = \frac{1}{3} V_{CC}$ and $V_{TH} = \frac{2}{3} V_{CC}$ and output levels of 0 and V_{CC} .



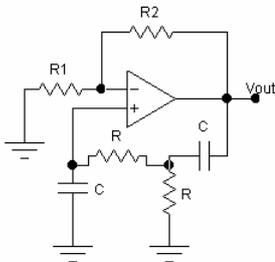


Figure (1)

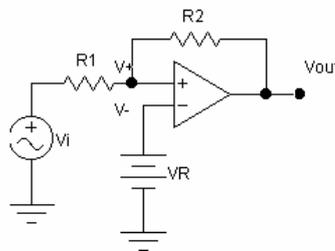

Figure(2)

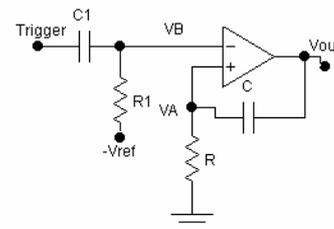

Figure(3)