


# Some Simple Examples

---

1. We already did the counter. It's a FSM whose outputs and state bits are one and the same!

 2. The Edge Finder:

We'd like to build a circuit that outputs a "1" each time it sees a 0-to-1 transition on its input



Interpretation of the clock input "Clk":



On each 'active' (falling) edge, the circuit examines "input" and figures out what to put on "output".

# State Transition Graph

English description of operation:

- If input = 0 on previous cycle, and it's still 0, output=0.
- If input = 0 on previous cycle and now it's a 1, output=1.
- If previous input = 1 and it's still = 1, output = 0.
- If previous input = 1 and now it's = 0, output = 0.

  Can be economically captured in graphical form:




# Assignment of State Bits

---


Only 2 state, so only 1 state bit is needed. State assignment is trivial:

State:	State bit S:
Wait_for_1	0
Wait_for_0	1

 

If there are more than 2 states, things get a bit more interesting; the encoding of the state can have a large effect on the amount of logic circuitry needed to implement the FSM!

# Logic Design

 

From the transition graph, we can write logic equations for the "1s" for S and Output:

$$\text{Next\_S} = \text{!S} \cdot \text{Input} + \text{S} \cdot \text{Input}$$

$$+$$

$$\text{S} \cdot \text{Input}$$

For each arrow leading to the state where S=1, find the previous state and input that got us there!

$$\text{Output} = \text{!S} \cdot \text{Input}$$


For each arrow in which Output = 1, find the previous state and input that produced that arrow (transition)

Next, perform logic simplification (by inspection, Karnaugh maps, or other techniques):


$$\text{Next\_S} = \text{!S} \cdot \text{Input} + \text{S} \cdot \text{Input} = \text{Input}$$

$$\text{Output} = \text{!S} \cdot \text{Input}$$

# Logic Equations to Gates

 

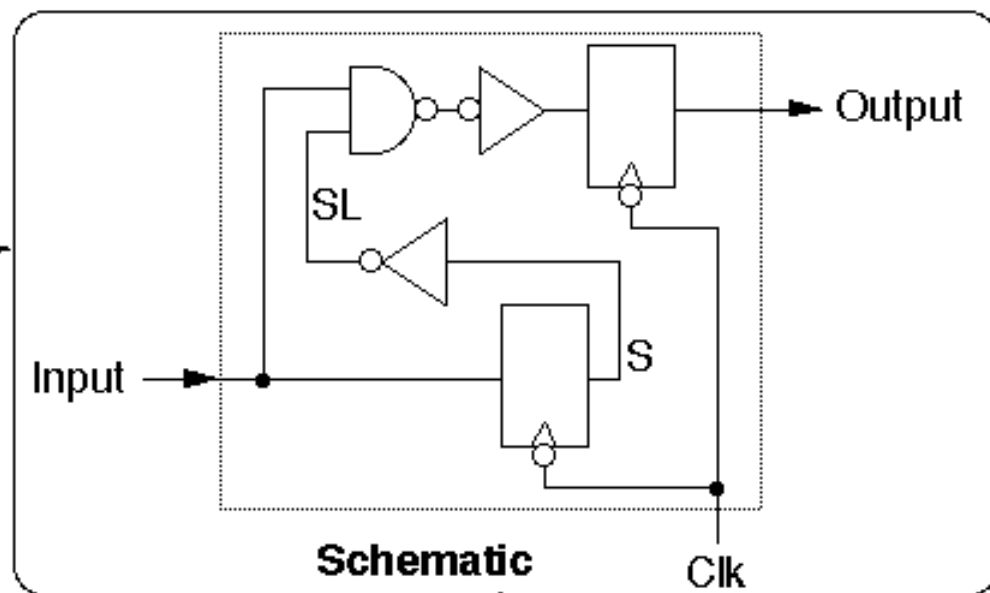Next\_S = Input  
Output = !S•Input  
**Logic Equations**  
(e.g., reduced SOP form)



Notation for Logical Inverse:  
 $!S = \bar{S} = SL$

Layout